

Total 10 modules.

- ① Basics.
- ② Mesh & Node Analysis.
- ③ Linearity, Superposition
→ Source transformation.
- ④ Network Th.

- ⑤ Circuit Analysis. ✓
- ⑥ Time & frequency response.
- ⑦ Two port No.
- ⑧ Fourier Series.
- ⑨ Fourier Transform

Books :-

A Sudhakar & S P

Shyam Mohan

(Circuit & Networks)


Network Analysis - Von
Valkenburg

3) Engg ckt Analysis.

William H Hayt.
Jack E Kemmerly.

Mechanism of Electrical Energy flow through the conductor


the Ohm's Law

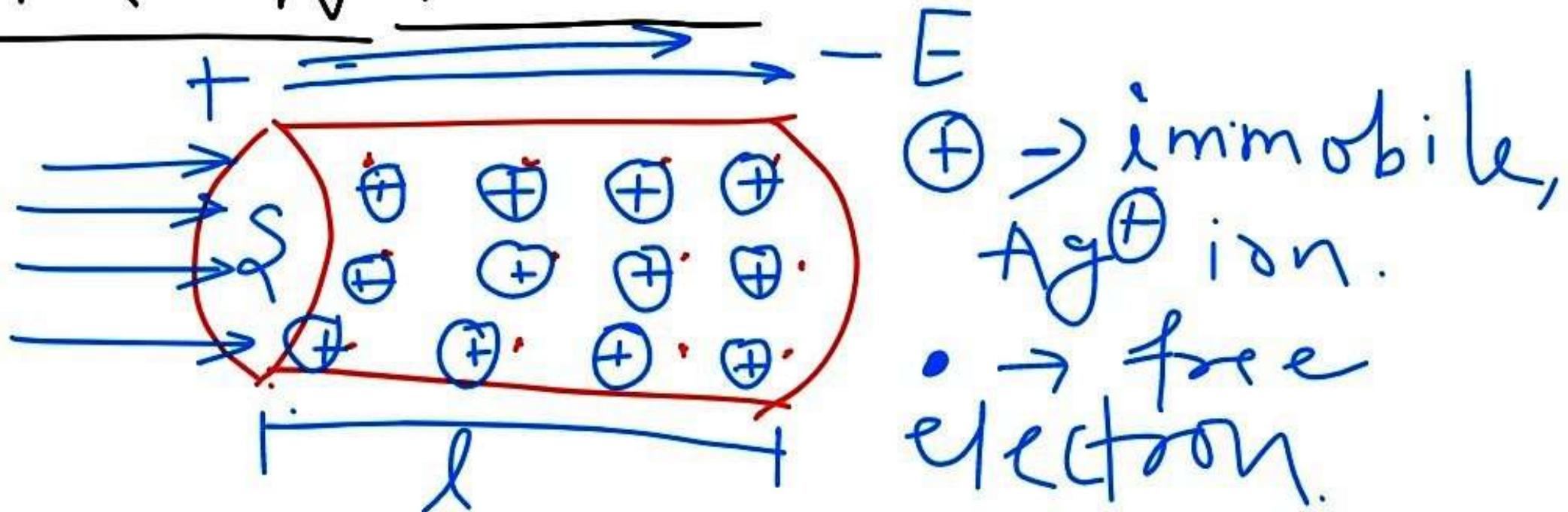

The four best conductors.

Ag^{+1} ← Silver ✓
 Cu^{+2} ← copper.
 Au^{+2} ← Gold.
 ~~Al^{+3}~~ ← Aluminum.

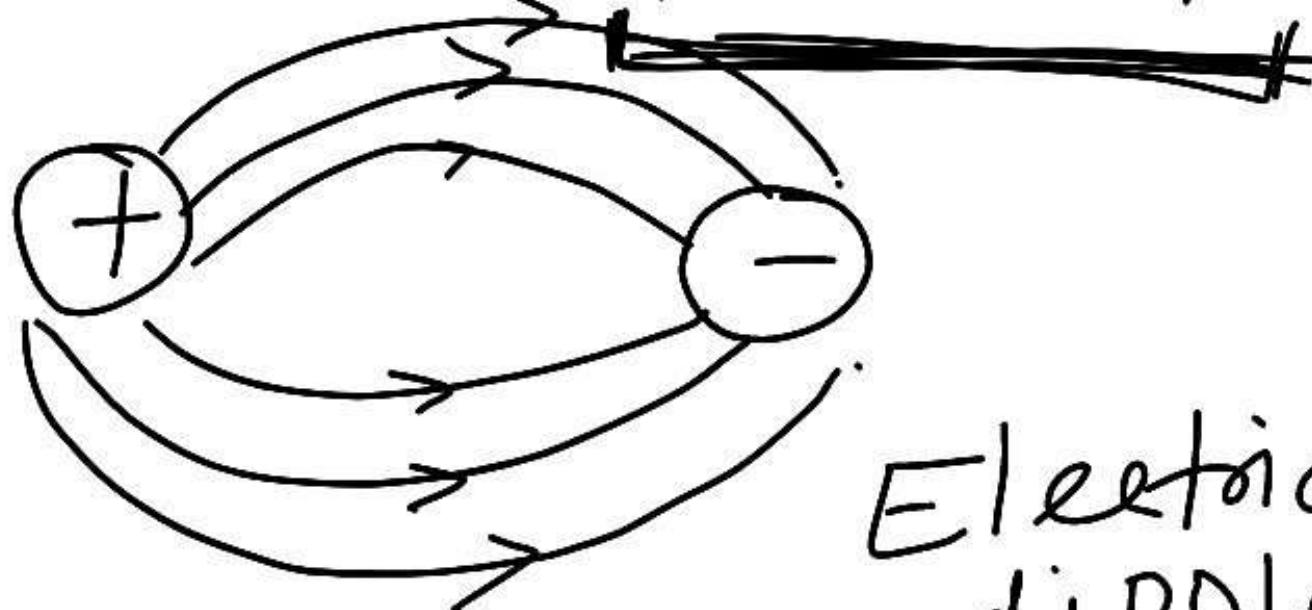Generally in any conductor.
there are 10^{18} to 10^{23} Atoms



Electrical
dipole.

unit
 Vs/m^2

When your conductor is subjected to an axial electric field, the force exerted by the field on each free electron $\Rightarrow F = \vec{E}e\vec{v}$

$$e = -1.6 \times 10^{-19} \text{ coulomb}$$

Due to the opposite direction
of F & E there exists a
net electron motion. (charge
motion)

The amount of charge flowing
is given by $q = ne$ Coulomb

i.e $q(t) = n(t) \cdot e$ Coulomb.

$n \Rightarrow$ No. of free electrons
(crossing cross sectional area)

Current :-

$$i = \frac{dq}{dt}$$
 Amperes.

The time rate of flow of
these electric charges.

Since q is -ve.

The current direction is
opposite to that of charge
motion. (i.e. free electron
motion)

Current density (J)

The current per unit cross section area.

$$J = \frac{I}{S} \text{ Amp/m}^2$$

Note:- \Rightarrow Scalar quantity
The direction of ' J ' is in
direction of ' i ', i.e. in the
direction of ' E '

$$F = \vec{E} \cdot e N.$$

$$q = n \cdot e \text{ Coulomb.}$$

$$i = \frac{dq}{dt} \text{ Amp.}$$

$$J = \frac{i}{s} \text{ Amp/m}^2$$

Observation

① As $E \uparrow \Rightarrow E \uparrow \Rightarrow n \uparrow \Rightarrow q \uparrow \Rightarrow i \uparrow \Rightarrow j \uparrow$
linearly.

② As $E = 0 \Rightarrow f = 0 \Rightarrow n = 0 \Rightarrow q = 0$
 $\Rightarrow i = 0 \Rightarrow j = 0$
(All core electrons are at rest)

Ohms law :-

$$\frac{I \propto E}{}$$

According to Ohm's law.
there exist a relation b/w
E & I

$J = \sigma E$ \rightarrow Basic Ohm's law
in field theory

σ \Rightarrow Conductivity of the
material

$$J = \delta E$$

$$\delta = \frac{J}{E} \sqrt{m}$$

$$-E$$

$$\delta$$

$$J$$

$$-J$$

$$E$$


$$\delta$$



Limitation of Ohm's Law :-

ohm's Law, i.e. linear J-E relation is valid only when the proportionality constant σ is kept constant i.e. (Temp. is kept constant)

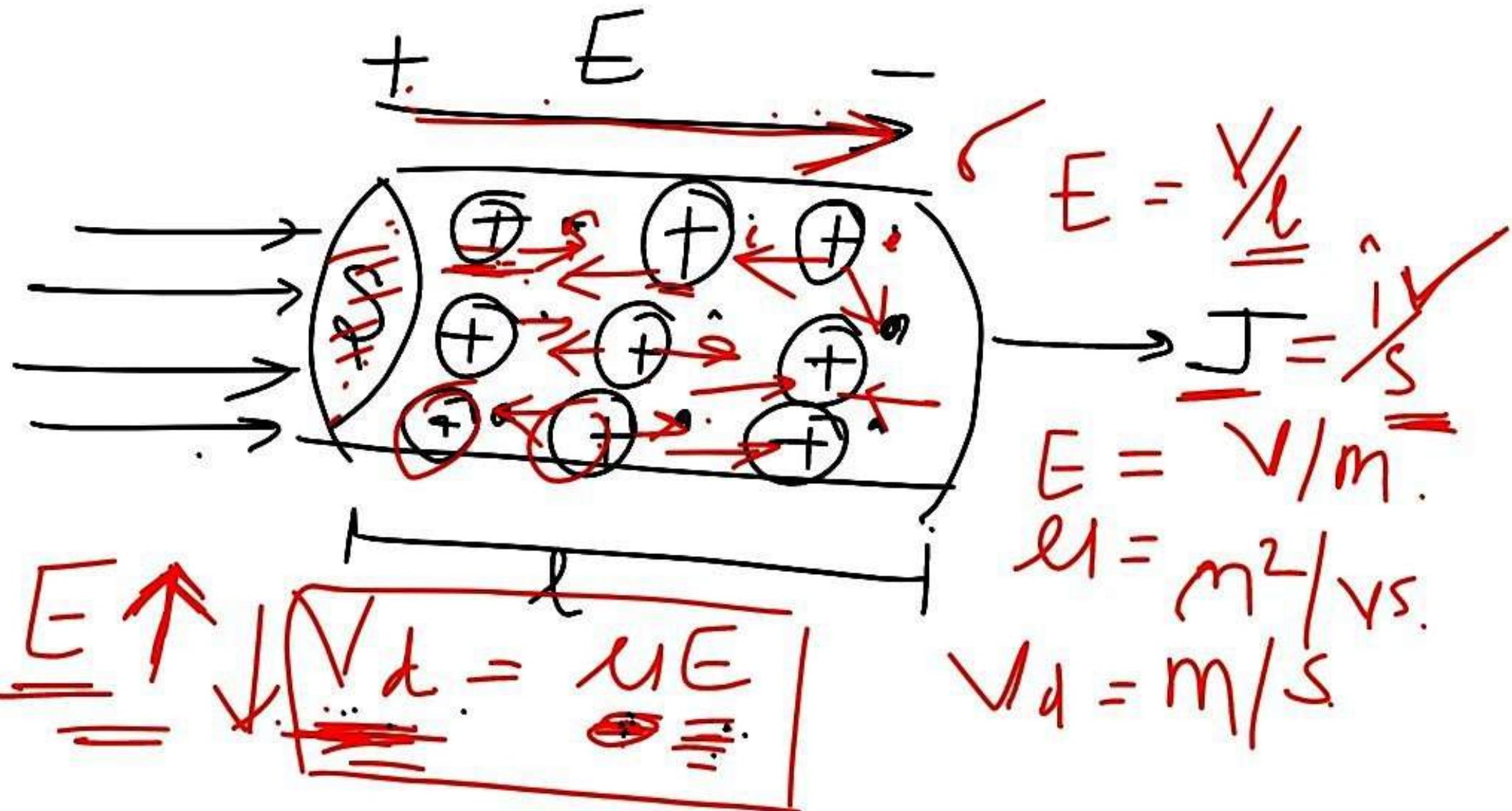Why voltage drop occurs in any
Practical conductor
whenever it carries
electrical energy?



$$K.E = \frac{1}{2} m v^2$$

$$m = 9.1 \times 10^{-31} \text{ kg}$$

Here the loss is in the form
heat.

$P \Rightarrow \underline{\text{Power density}}$:-

It is power dissipation per unit volume (unit cube) within the conductor due to the resistance effect of the conductor.

$$P = JE \quad J = \frac{\delta E}{\epsilon} = \cancel{\frac{\epsilon}{J}}$$

~~J~~


$\overline{Amp/m^2} \cdot \overline{volt/meter}$.

$$= \epsilon E \cdot E \frac{Amp \cdot volt}{m^3}$$


$$\boxed{P = \epsilon E^2} \frac{Watt}{m^3}$$

Observation

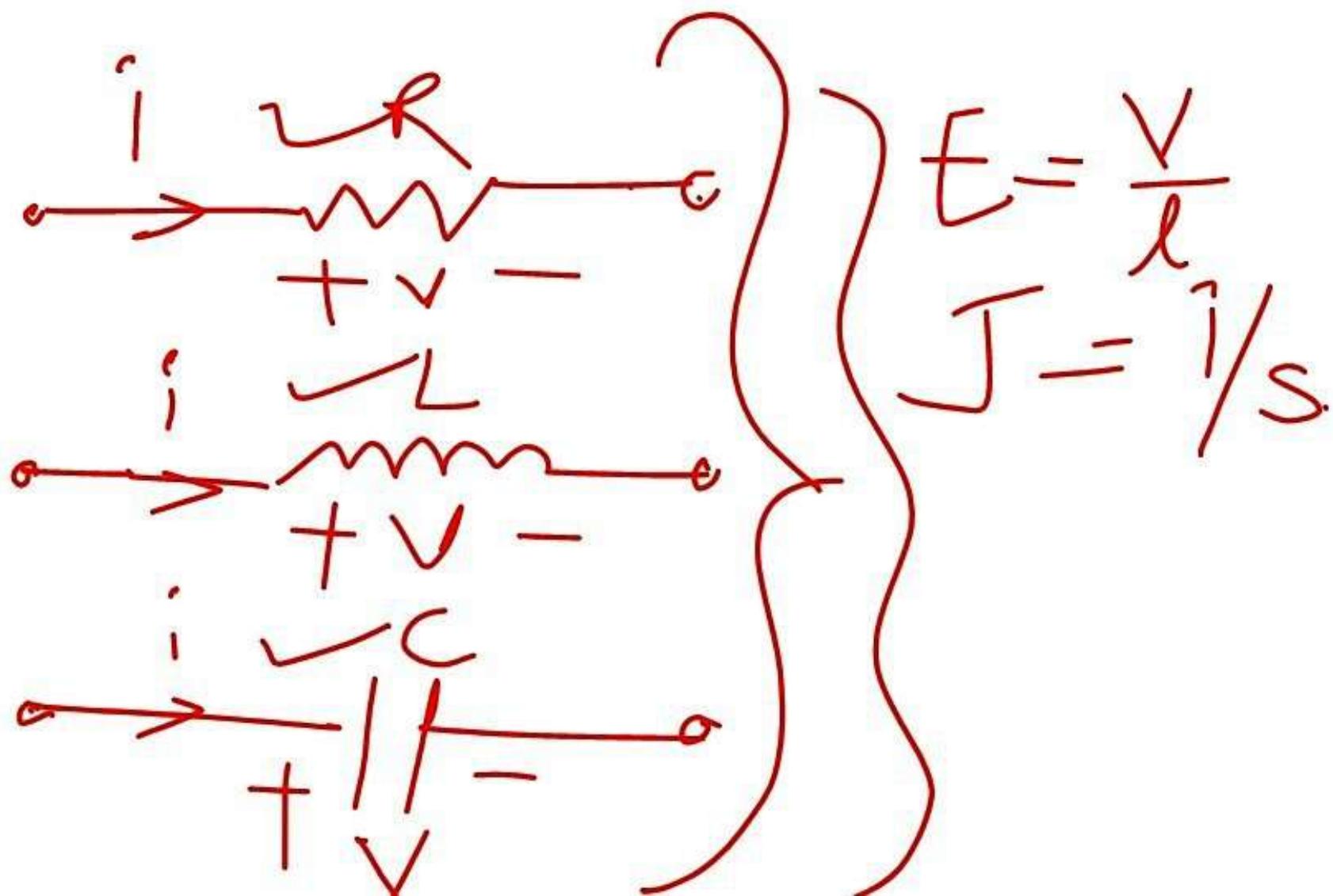As $E = 0 \Rightarrow u = 0$ (\because All the electrons are at rest)
 $\Rightarrow Vd = 0 \Rightarrow KE = 0 \Rightarrow P = 0$
OR. $P = JE$
 $E = 0 \Rightarrow J = 0 \Rightarrow \underline{P = 0}$




Conclusion :-

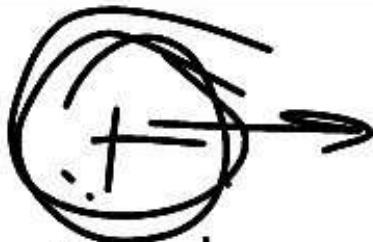

When a conductor is carrying electrical energy, the current through all lumped (R, L, C) will always flow from +ve to -ve terminal.

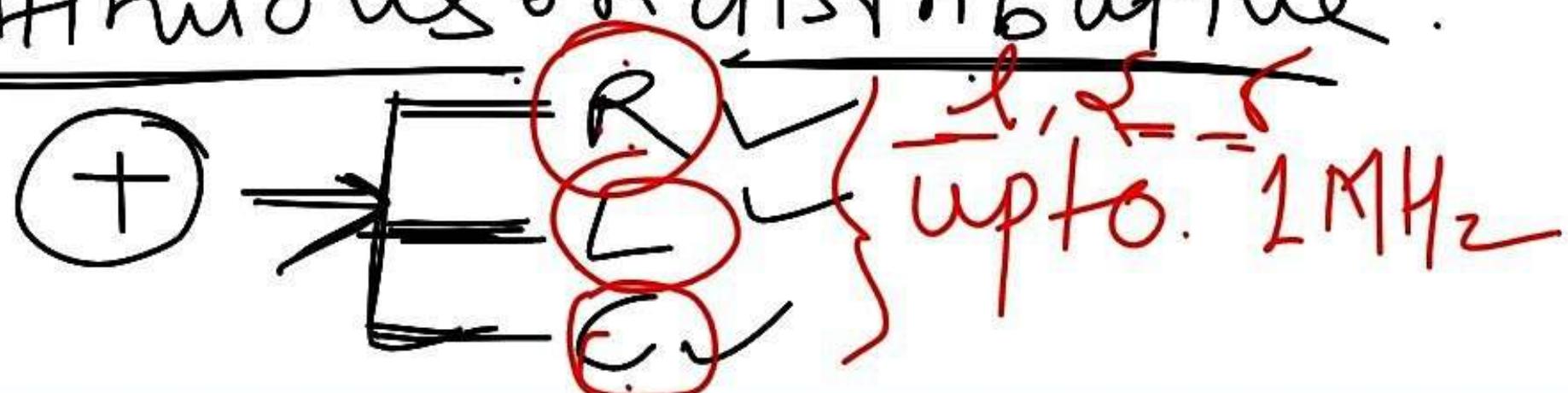The opposition by  for the flow of Electrical energy through the conductor is continuous and distributive.




Electrical circuit \rightarrow Interconnection
of R L C.

1 kHz.
 $> 1 \text{ MHz}$

There are two scenarios we will encounter in Network Theory. & LC

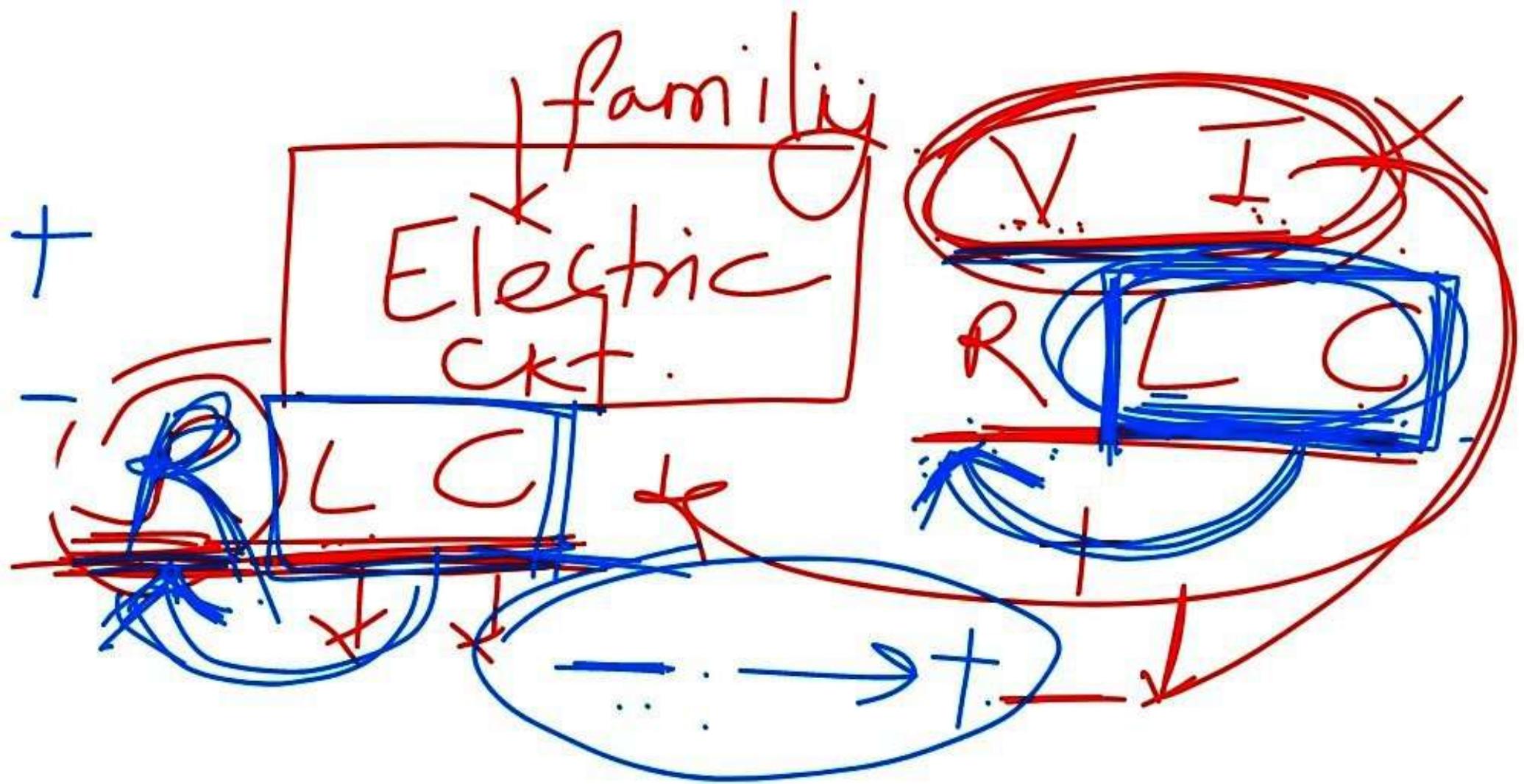- ① In presence of your Active sources.
- ② In absence of Active sources.




Basic Diff' b/w Network
circuit :-

Circuit :- Loop or Mesh. or N/a.

loop \rightarrow closed path.

mesh \rightarrow Inter connection of ckt

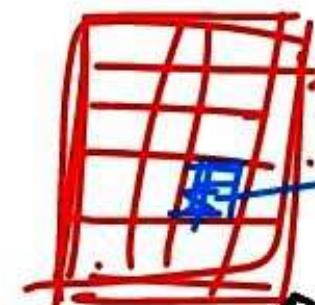

Network


ckt.

N/a.

Resistance:

$$J = \sigma E$$

↑
1st form
of Ohm's law.

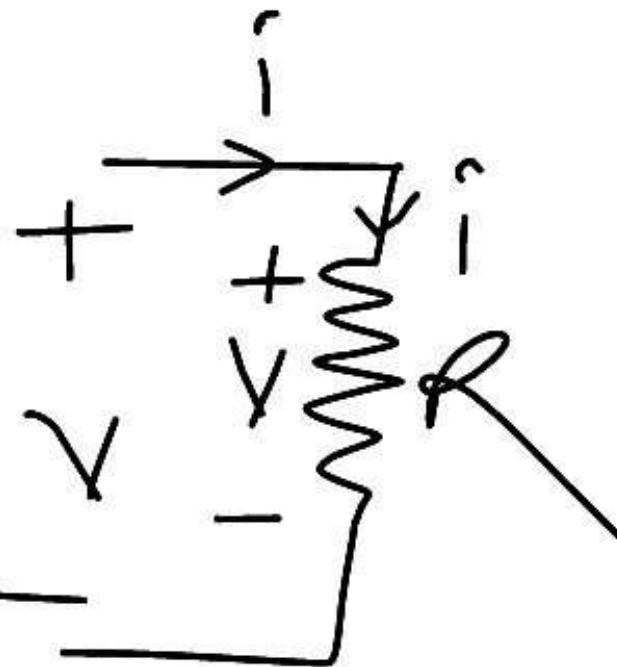

$$J = \sigma E \leftarrow \text{Electrical field theory form}$$
$$\frac{i}{\sigma} = \sigma \frac{V}{l} \Rightarrow V = \frac{\sigma i}{\sigma l}$$

$$V = R i$$

→ 2nd form
of Ohm's law.
Circuit theory form.

$$R = \frac{l}{\sigma A} = \text{Ohm} \Rightarrow \Omega$$

~~$R = \frac{l}{\sigma A}$~~

$\sim = R$

As temp \uparrow
 $l \uparrow \quad \sigma \downarrow$

$\frac{l}{\sigma A} = \text{almost constant}$

$\sigma \downarrow \quad R \uparrow$

$$\underline{\underline{R}}_t = R_0(1 + \underline{\underline{\alpha}}t)$$

$\underline{\underline{\alpha}}$ → Temp coefficient ν

t → temp in $^{\circ}\text{C}$ i

$t \uparrow \underline{\underline{R}}_t \uparrow \underline{\underline{R}}$

$$R = \frac{l}{\sigma S}$$

$$\sigma = \frac{l}{RS} = \frac{\text{meter}}{\text{ohm} * \text{m}^2}$$

$$\delta = -\omega / m.$$

$$V = RI$$

$$i = \frac{V}{R}$$

$$\boxed{i = GV} \rightarrow \text{3rd form of Ohm's law.}$$

$G \rightarrow \sigma \rightarrow \text{mho.}$


$$\overset{\circ}{i} = \frac{dq}{dt}$$

$$V = R \frac{dq}{dt}$$

4th form
of Ohm's
law.

Basic Concepts:-

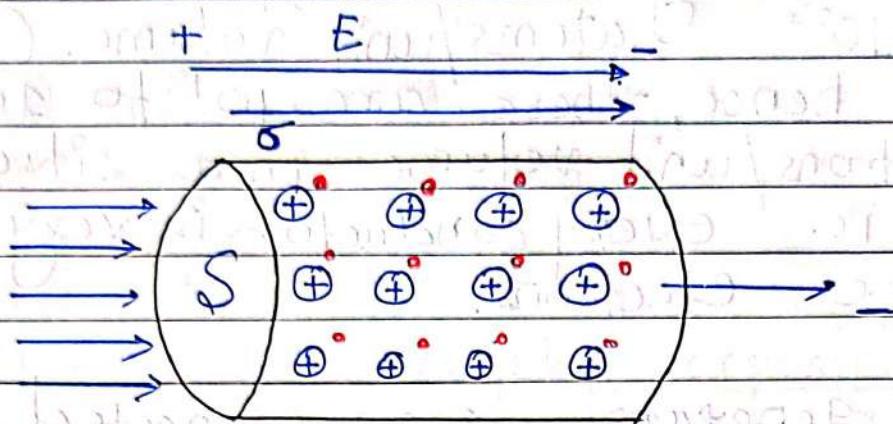Mechanism of Electrical Energy flow through the conductor and the Ohm's Law:-



$\oplus \Rightarrow \text{Ag}^+$ ion, immobile, larger in size

$\ominus \Rightarrow \text{free electron}$.

The four best conductors are:


Ag^{+1}	Cu^{+2}	Au^{+2}	Al^{+3}
$1e^-$	$2e^-$	$2e^-$	$3e^-$

\rightarrow silver is the best conductor because mobility of free electron in silver conductor is several times to that of other conductors.

So, its conductivity is very high. i.e. the conductivity of any material is mainly a function of free electrons mobility within the material.

→ Generally in any conductor, there are 10^{18} to 10^{23} atoms/unit volume. (i.e. unit cell) and hence, there are 10^{18} to 10^{23} free electrons/unit volume in a silver conductor. i.e. every conductor is very rich in free electrons.

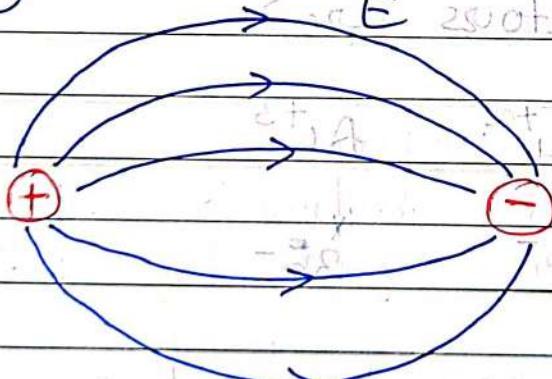→ Whenever generators are connected to the transmission lines (basically conductors), electrical energy will be launched axially, which results in axial electric field (a perpendicular magnetic field) and hence, axial current density along the length of the conductor.



An electric dipole consists of two opposite charges. An electric dipole has a net dipole moment equal to the product of charge and distance between them.

→ When a conductor is subjected to an axial electric field, the force exerted by the field on each free electron is given by

$$\rightarrow F = \vec{E} \cdot e \quad \text{Newton.}$$

$$\text{value } e = -1.6 \times 10^{-19} \text{ coulomb}$$

→ Since 'e' is negative, the direction of force is in the direction opposite to that of 'E' and hence, there exists a net electron motion (ie charge motion) in the direction opposite to that of 'E'.

→ The amount of charge flowing is given by

$$q = ne \quad \text{coulomb.}$$

$$\text{i.e. } q(t) = n(t) \cdot e \text{ coulomb.}$$

$n =$ The number of free electrons crossing a reference cross-section area 's', a variable quantity due to large number of free electrons within the conductor (so called random variable)

→ The time rate of flow of these electric charges (i.e. free electrons) is nothing but the electric current.

$$i = \frac{dq}{dt} \text{ Ampere}$$

→ since 'q' is negative, the current direction is opposite to that of charge motion (i.e. free electrons motion) i.e. in the direction of 'E'.

→ The current per unit cross section area is nothing but the current density resulted within the conductor. i.e.

$$J = \frac{i}{s} \text{ Ampere/meter}^2$$

→ Since 's' is scalar, the direction of 'J' is in the direction of 'i' i.e. in the direction of 'E'.

$\rightarrow F = E \cdot q$

* $F = E \cdot q$ Newton.

* $q = n e$ coulomb.

$$* i = dq/dt \text{ Ampere}$$

$$* J = i/s \text{ Ampere/meter}^2$$

Observation :-

→ As $E \uparrow \Rightarrow F \uparrow \Rightarrow n \uparrow \Rightarrow q \uparrow \Rightarrow i \uparrow \Rightarrow J \uparrow$
linearly.

→ As $E = 0 \Rightarrow F = 0 \Rightarrow n = 0 \Rightarrow q = 0 \Rightarrow i = 0 \Rightarrow J = 0$

i.e. All the free electrons are at rest.

Definition of Ohm's Law :-

According to Ohm, there exists a linear relation between the applied electric field (E) and the resulted current density (J)

by ~~in more than one case~~ ~~in more than one case~~

$J \propto E$

$$\boxed{\vec{J} = \sigma \vec{E}} \quad \leftarrow \text{Basic Ohm's law in field theory form.}$$

σ = Conductivity of the material i.e conductor.

J-E Characteristics :-

$$J = \sigma E$$

$$\sigma = \frac{J}{E} \text{ in } \Omega^{-1} \text{ m}^{-1}$$

-E

-E

-J

Limitations :-

Ohm's law i.e. a linear J-E relation is valid only when the proportionality constant σ is kept constant. i.e. temperature is kept constant.

* What happens to the conductivity of all the conductors, if the temperature increases beyond room temperature?

→ When the temperature increases from room temperature (i.e. 27°C or 300 K), free electrons will acquire extra thermal energy at higher temperatures, which results in increase in collisions among the free electrons and hence, net free electron mobility (i.e. carrier mobility) falls, so conductivity decreases.

* Why voltage drop occurs in any practical conductor whenever it carries electrical energy? (with explanation)

→ Voltage Drop :- Decrease in electrical potential along the path of current flowing.

As 'E' increases, there exists an increase in collisions between the free electrons and immobile positive ions (large in size), which results in fall in drift velocity ($v_d = eE$) m/s.

\Rightarrow Average mobility of free electrons in $\text{m}^2/\text{Vs.}$ (meter²/volt second)

$E \Rightarrow$ External electric field in volt/meter.

Loss in kinetic energy

$$KE = \frac{1}{2}mv_0^2 \text{ Joule}$$

$$(m = 9.11 \times 10^{-31} \text{ kg}),$$

This loss in energy will be dissipated in the form of heat energy, which results in voltage drop across the conductor.

Power density (P)

Amount of power dissipated within the conductor per unit volume (unit cube) within the conductor due to the effect of the conductor.

Due to this effect, the conductor gets heated up.

$$P = J \cdot E \text{ Ampere/meter}^2 \cdot \text{volt/meter}$$


$$P = \sigma E \cdot E \frac{\text{Amper} \cdot \text{volt}}{\text{meter}^2}$$

$$P = \sigma E^2 \text{ watt/meter}^3$$

Observation :-


- As $E=0 \Rightarrow V=0$ C (since all the electrons are at rest)
- ⇒ $V_d=0 \Rightarrow KE=0 \Rightarrow P=0$ Watt/m³.
- As $E=0 \Rightarrow J=0 \Rightarrow P=JE = 0$ Watt/m³.

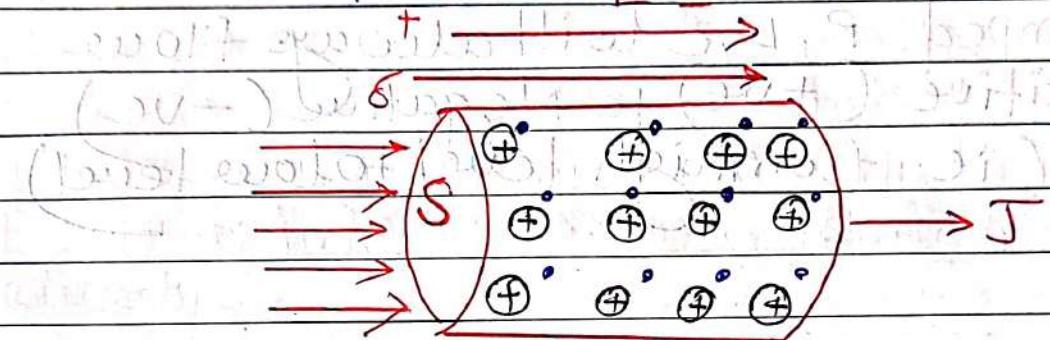So when no energy flow through the conduction → no voltage drop across the conductor.



(Electron flow is from left to right)

~~Electron flow is from left to right~~

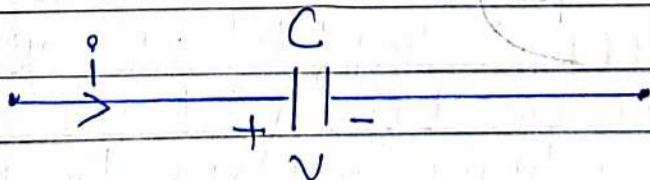

Date _____
Page _____

→ Since $E = \frac{V}{l}$ & $J = \frac{i}{s}$ as 'l' & 's' are

scalars, the drop polarities are same as electric field 'E' polarities and the current direction is same as current density 'J' direction.

Conclusion :-

Whenever a conductor is carrying electrical energy, currents through all the three passive lumped R, L, C will always flow from positive (+ve) to Negative (-ve) terminals (ie. from high level to low level)

See

The opposition (by immobile positive ions) for electrical energy flow (ie free electron motion) through the conductor is continuous or distributive in nature, but practically, we can approximate this single distributive opposition into three lumped oppositions called resistance (R), inductance (L) & capacitance (C) for lower frequencies (ie upto 1 MHz)

Date _____
Page _____

magnitude of these lumped R , L , C are function of length (l), cross section area (s) & conductivity (σ) of the conductor.

→ Interconnection of these lumped (R , L , C) elements is nothing but a lumped electric circuit. Network theory is used to analyse only these lumped electric circuits at lower frequencies (ie. upto 1 MHz).

→ At higher frequencies (ie above 1 MHz) we cannot approximate distributive elements into lumped elements & hence, no lumped electric circuit, so no Network theory. Here Field theory approach is used directly on distributive conductors.

→ field theory approach of solving distributive electric networks is valid for all the frequencies starting from zero (ie. 0 Hz \Rightarrow D.C.)

(\rightarrow High and low frequency regions
 \rightarrow best and most useful region
 \rightarrow \approx 1000 Hz to 100 MHz)

There are two scenarios we will encounter in Network theory.


Scenario 1 :- In the presence of Active Sources :-

In the presence of sources, all the three passive lumped R, L, C will always absorb energy. Whenever they are absorbing energy, current through them will always flow from positive (+ve) to Negative (-ve) terminals (i.e. from high level to low level).

Scenario 2 :- In the absence of Active Sources

In the absence of sources, stored energy in the memory elements (L & C) will be delivered (on a memoryless ~~test~~ resistance) whenever L & C elements are delivering energy, currents through them will always flow from low level (-ve) to high level (+ve) terminals.

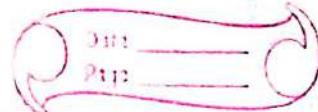As the resistor always absorbs energy, current through it will always flow from positive (+ve) to negative (-ve) terminals.



* What is the difference between Network & Circuit?

→ Circuit \Rightarrow Loop or mesh
i.e. A closed path.

Network \Rightarrow Interconnection of circuits.

Eg. Network is like a building, whereas the circuits are like rooms in a building.


Passive Lumped RLC Elements

Ohm's Law :-

(1) Resistance (R)

$$\text{Since } J = \sigma E$$

$$\frac{J}{S} = \frac{\sigma E}{L}$$

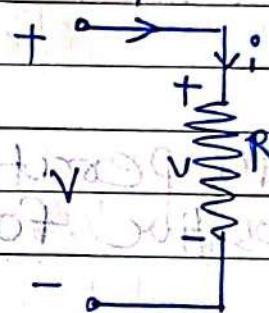

$$V = \frac{l}{S} i$$

(2nd form of Ohm's Law)

$$V = R i$$

← Ohm's law in circuit theory form.

$$\text{Where } R = \frac{l}{S}, \text{ Ohm} (\Omega)$$

R \rightarrow Resistance parameter of the conductor.

Limitations:

→ Ohm's law i.e. a linear voltage and current relation is valid only when the proportionality constant 'R' is kept constant. i.e. the temperature is kept constant.

→ As temperature increases $\rightarrow \frac{l}{s} \uparrow$, $\sigma \downarrow$

$$\frac{l}{s} = \text{Almost constant}, \sigma \downarrow \text{so } R \uparrow.$$

$$\rightarrow R_t = R_0 (1 + \alpha t) \quad (\text{R}) \text{ resistance}$$

where

α = temperature coefficient in $^{\circ}\text{C}$, positive for all the conductors

t = temperature in $^{\circ}\text{C}$.

So $t \uparrow \Rightarrow R_t \uparrow$ for all the conductors

$$\rightarrow R_t = \frac{l}{s} \Rightarrow \sigma = \frac{l}{R_s} \text{ ohm}^{-1} \text{ meter}^{-2}$$

$$= (-2 \text{ m})^{-1} = -2 \text{ m}^{-1} = -0.5 \text{ m} \text{ ohm}^{-1} \text{ meter}^{-2}$$

→ Resistivity or specific resistance = ρ

$$= \frac{1}{\sigma} = \frac{R_S l}{A} = \frac{\Omega m^2}{m} = (\Omega \text{meter})$$

since $V = RI$

$$i = \frac{V}{R}$$

$$\boxed{i = GV} \leftarrow 3^{\text{rd}} \text{ form of Ohm's law.}$$

$$\text{where } G = \frac{1}{R} - \text{mho} (\text{---})$$

$G \Rightarrow$ conductance parameter of the conductor

Since $i = \frac{dq}{dt}$

$$\boxed{V = R \frac{dq}{dt}} \leftarrow 4^{\text{th}} \text{ form of Ohm's Law.}$$

Electric Power (P)

$$P = \frac{dwe}{dt} = \frac{dwe}{dq} \cdot \frac{dq}{dt}$$

$$\boxed{P = VI \text{ watt}} \leftarrow \text{Instantaneous power.}$$

i.e. $P(t) = V(t) \cdot I(t) \text{ watt.}$

Electrical Energy (Watt)

Since $\frac{dW}{dt} = P \Rightarrow dW = Pdt$

$$\boxed{W = \int P dt}$$

Joule

For R :-

$$P = V \cdot i = R \cdot i \cdot i$$

$$\boxed{P = i^2 R} \text{ Watt}$$

$$\text{i.e. } P(t) = i^2(t) \cdot R \text{ Watt}$$

$$P = V I = V \frac{V}{R}$$

$$\boxed{P = \frac{V^2}{R}}$$

$$\text{i.e. } P(t) = \frac{V^2(t)}{R} \text{ Watt}$$

$$W = \int P dt \text{ Joule}$$





$$W = \int i^2 R dt \text{ Joule}$$

$$\boxed{W = \int \frac{V^2}{R} dt \text{ Joule}}$$



N- i Characteristics :-

$$V = R^i$$

$$R = \frac{V}{I} \Omega$$

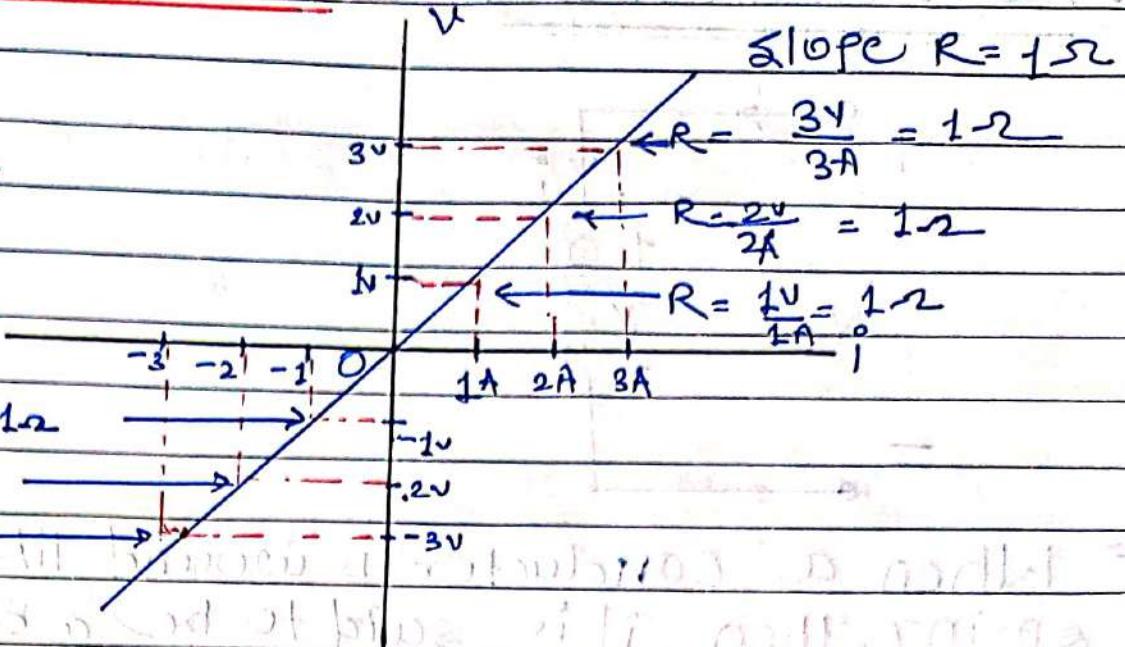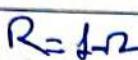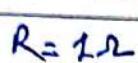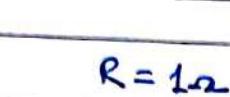


1st quadrant 3rd quadrant

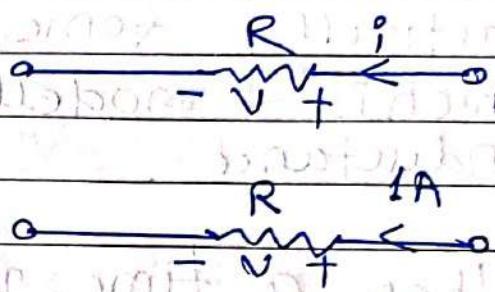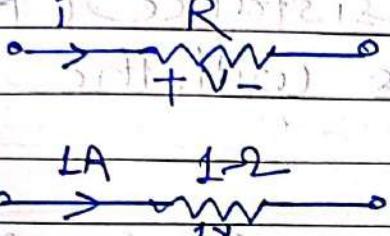

Observation :-

So, from the characteristics, resistor is a linear, passive, bilateral and time invariant in V-i plane (these are possible only at a constant temperature, where length (l), cross section area (s) and conductivity (σ) are kept constant. i.e. $R = \rho \frac{l}{s}$ is kept constant.

② Inductance (L)

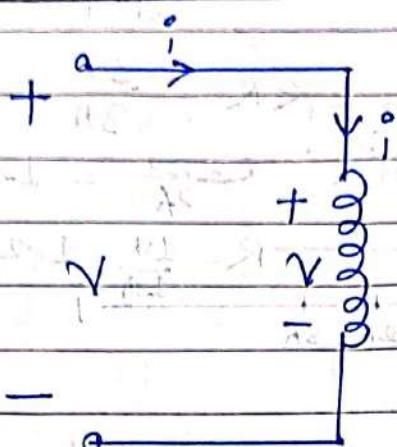

→ When a conductor is wound like a spring, then it is said to be a coil. The coil will exhibit ideally inductance (L) & practically some leakage resistance (R) which is modelled in series with the inductance.

→ When a time varying current is flowing through the coil, a time varying magnetic flux will be produced (by Faraday's law). The total flux produced is

where $N =$ The number of turns

$\Phi =$ flux per turn

$$\text{i.e. } \psi(t) = N \phi(t) \text{ Weber.}$$

→ This total flux produced is proportional to the current flowing through the coil

i.e. $\psi \propto i \Rightarrow \psi = Li$

where L = inductance parameter of the coil.

→ The voltage drop across the coil is

$$V = \frac{d\psi}{dt} \quad (\text{By Faraday's law})$$

$$V = \frac{d}{dt} (Li)$$

$$V = L \frac{di}{dt} \quad \text{Volt. representing Lohnt}$$

representing the inductance of the coil.

$di = I dt$ represents the change in current with time.

$$H \cdot i = L \int_{-\infty}^t Amperes$$

$$H = \frac{N}{L} \cdot i = \frac{N}{L} \cdot \frac{di}{dt} \cdot t$$

$$P = Lim \frac{di}{dt} \cdot i \cdot L \quad \text{Watt (Instantaneous power)}$$

$$W = \int P dt \text{ Joule}$$

$$W = L_i \left(\frac{di}{dt} \right) \cdot dt \text{ Joule}$$

$$P = L_i \frac{di}{dt} = \frac{d}{dt} \left(\frac{1}{2} L_i i^2 \right)$$

Since $W = \int P dt \text{ Joule}$

$$W = \int dt \left(\frac{1}{2} L_i i^2 \right)$$

$$W = \frac{1}{2} L_i i^2 \text{ Joule} \quad (i) \quad b = V$$

= Instantaneous energy

= Total energy

i.e. the energy stored in an inductor at any instant will depend on the current flowing through the inductor at that instant.

Since $W = \int P dt \text{ Joule}$) This is the

$$W = \int dt \left(\frac{1}{2} L_i i^2 \right)$$


$$W = \frac{1}{2} L_i i^2 \text{ Joule}$$

This is the total energy stored by the inductor from past ($-\infty$) to the present time $t=1$

ψ - i Characteristics

$$\psi = L i$$

$$L = \frac{\psi}{i} H$$

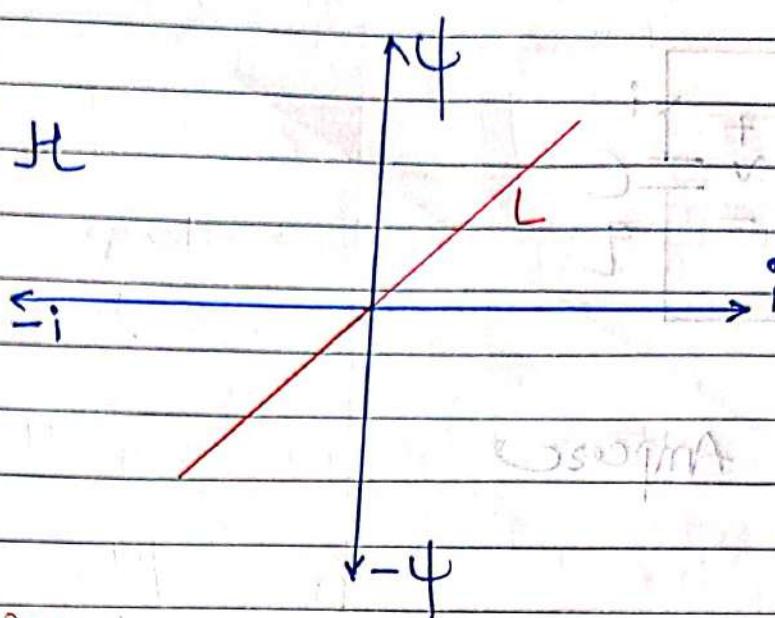


Observation :-

So from the characteristics, inductor is a linear, passive, bilateral and time-invariant in ψ - i plane (these are possible only at a constant temperature), where length (L), cross section area (A) and conductivity (σ) are kept constant. i.e. ' L ' is kept constant.

How	ψ	i	$= V$	\in	H	i	$= v$
-----	--------	-----	-------	-------	-----	-----	-------

③ Capacitance (C)

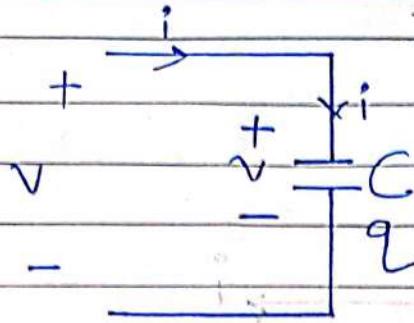

$$i = \frac{dq}{dt} \text{ Amperes}$$

$$q \propto V$$

$C = \text{Capacitance}$ parameter of the conductor.

$$i = \frac{d}{dt}(CV)$$

$$i = C \frac{dv}{dt} \text{ Amperes}$$

$$dv = \frac{1}{C} idt \Rightarrow v = \frac{1}{C} \int_{-\infty}^t idt \text{ volt}$$

$$P = v \cdot i$$

$$= v \cdot C \frac{dv}{dt}$$

$P = Cv \frac{dv}{dt}$ Watt. = Instantaneous power.

$$W = \int P dt \text{ Joule}$$

$$W = \int Cv \left(\frac{dv}{dt} \right) dt \text{ Joule}$$

$$W = \int Cv \left(\frac{dv}{dt} \right) dt \text{ Joule}$$

$$(2) P = Cv \cdot \frac{dv}{dt} = \frac{d}{dt} \left(\frac{1}{2} Cv^2 \right)$$

Since $W = \int p \cdot dt \text{ Joule}$

$$W = \frac{1}{2} Cv^2 \text{ Joule}$$


$W \Rightarrow$ Instantaneous energy = Total energy

q - v Characteristic

$$i \cdot v = q$$

$$q = cv$$

$$c = q/v \propto f$$

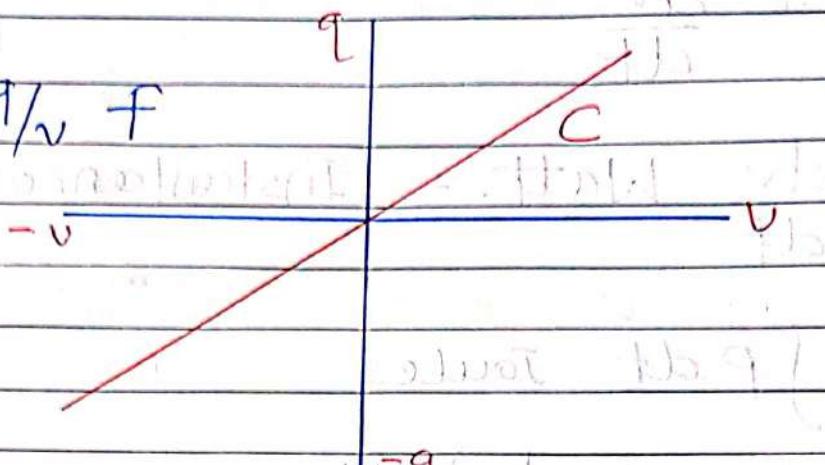

Observation :-

So from the characteristics, capacitor is a linear, passive, bilateral and time invariant in $q-v$ plane (these are possible only at constant temperature, where length (l), cross section area (s), and conductivity (σ) are kept constant. i.e. 'C' is kept constant.

Relation between voltage & current in L & C elements :-

① L :-

$$V = L \frac{di}{dt}$$

$$V_1 = L \frac{di_1}{dt} \quad \textcircled{1} \quad V_1 \leftarrow i_1$$

$$V_2 = L \frac{di_2}{dt} \quad \textcircled{2} \quad V_2 \leftarrow i_2$$

$$V = L \frac{di_1}{dt} + L \frac{di_2}{dt}$$

$$V = L \frac{d}{dt} (i_1 + i_2)$$

$$V_1 + V_2 \leftarrow i_1 + i_2$$

$$V = V_1 + V_2$$

relation between voltage and current in an inductor is linear & hence

$$V = L \frac{di}{dt}$$

→ 5th form of
Ohm's law.

② C : \rightarrow

$$i = C \frac{dv}{dt}$$

$$i_1 = C \frac{dv_1}{dt}$$

$$\leftarrow i_1 \leftarrow v_1$$

$$i_2 = C \frac{dv_2}{dt}$$

$$i_2 \leftarrow v_2$$

$$i = C \frac{d}{dt} (v_1 + v_2)$$

$$i_1 + i_2 \leftarrow v_1 + v_2$$

The relation between voltage & current in a capacitor is linear & hence

$$i = C \frac{dv}{dt}$$


\leftarrow 7th form of
Ohm's law

as in forward bias operation needed positive
Similarly & D'arsonval ammeter


$$v = \frac{1}{C} \int_{-\infty}^t i dt$$

\leftarrow 8th form of
Ohm's law.

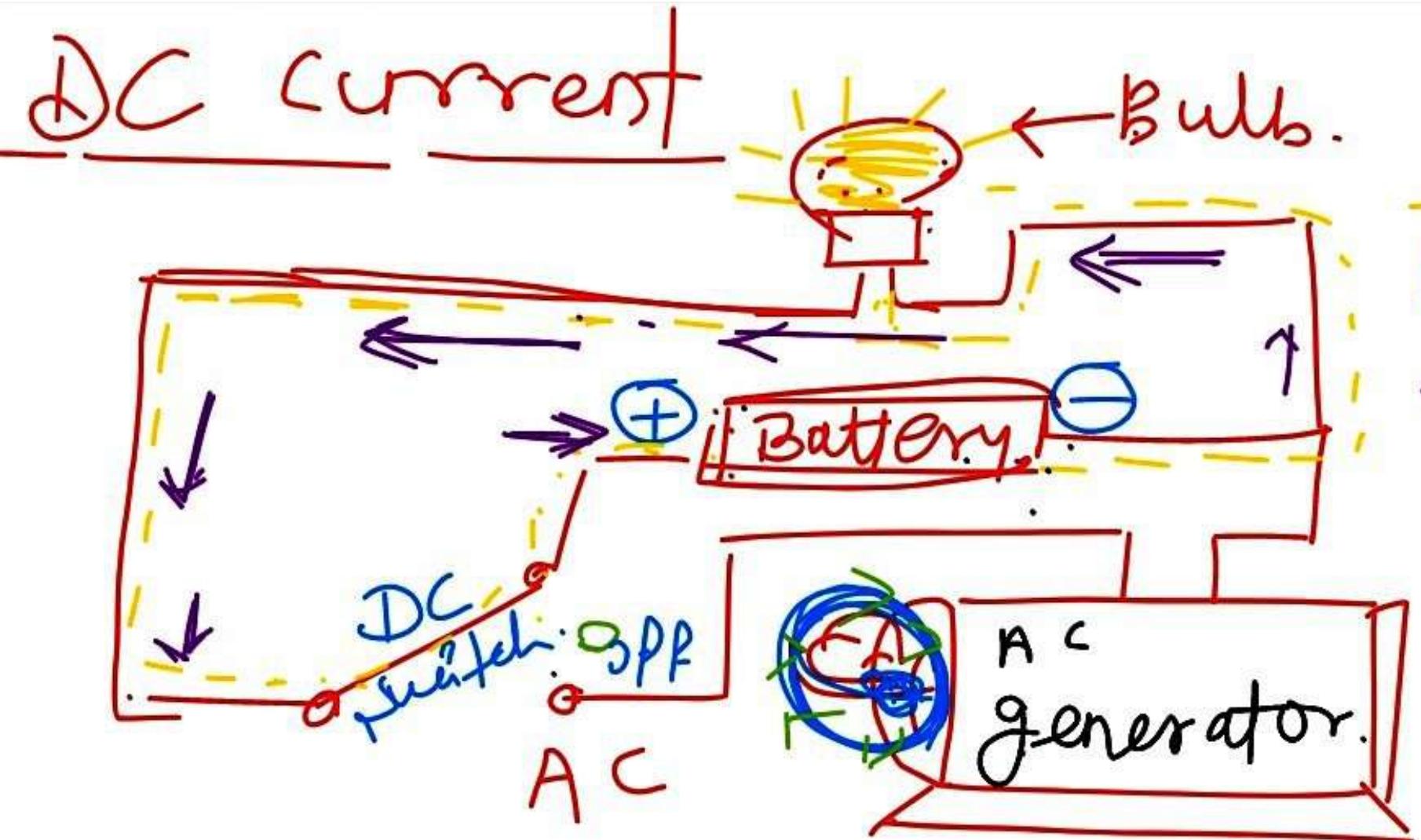Due to resistance, inductance & capacitance effects of the conductor, energy loss will occur in the conductor.



AC Current :-

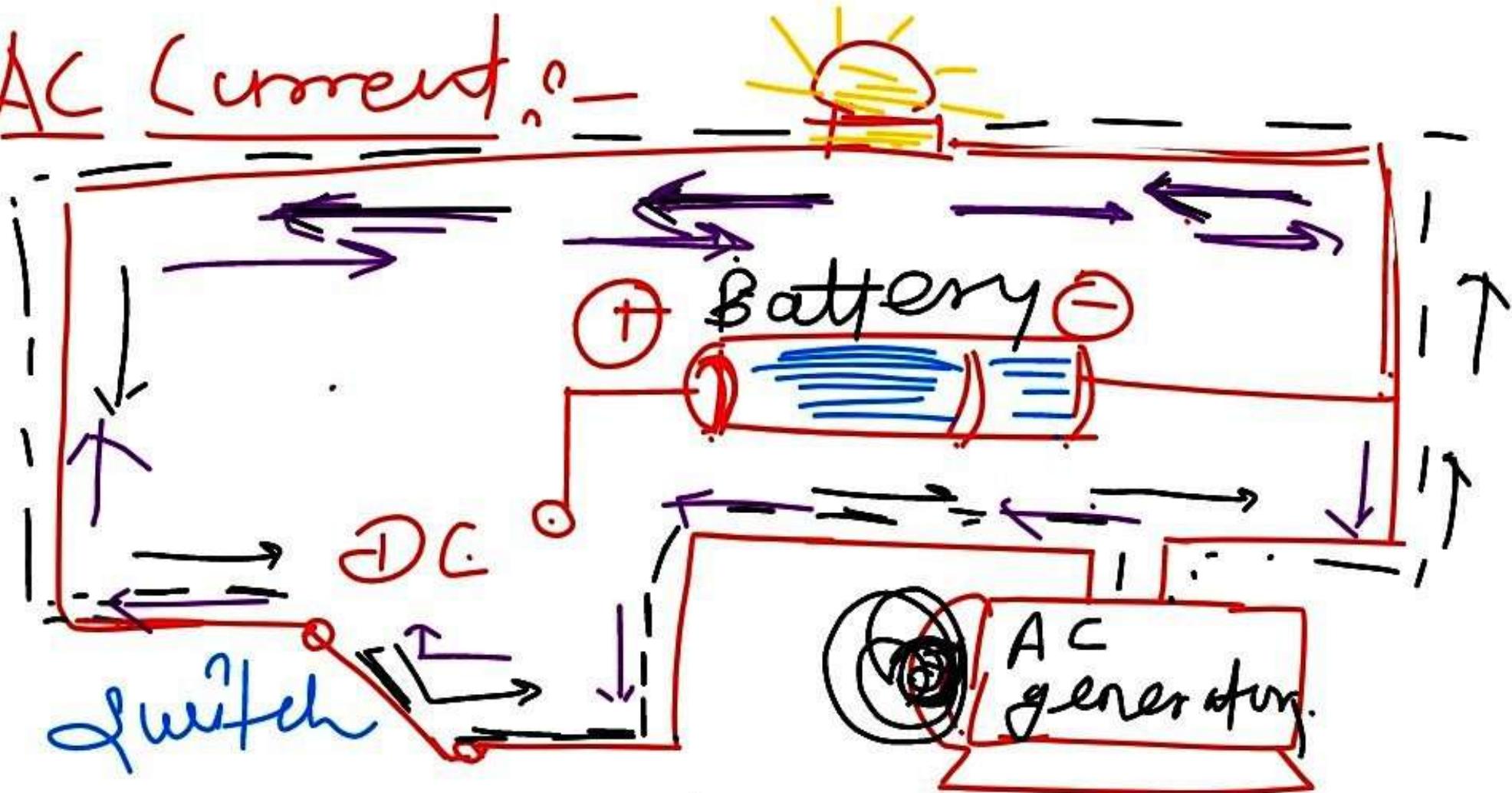

DC → use for shorter distance

AC → Is safe for longer
distance without
any power loss.

(Less power loss)

Houses, offices, buildings
use the AC supply.
→ freq. of AC supply is 50Hz.
or 60Hz.
(Depending upon country)

freq of DC is zero.

→ Power factor.

For AC → 0 to 1

for DC → Always 1

Types of AC signal.

Sinusoidal, Trapezoidal,
Triangular, Square.

Types of DC :-

Pure & pulsating.

Passive Parameters

AC → Impedance → (Generators)
DC → Resistance only →
((cell or
battery))

Frequency of AC in India

is 50Hz.

AC supply 50Hz / 220volt.


In USA

60Hz / 110volt.

Types of Element :-

(5 pairs. Total elements 10)

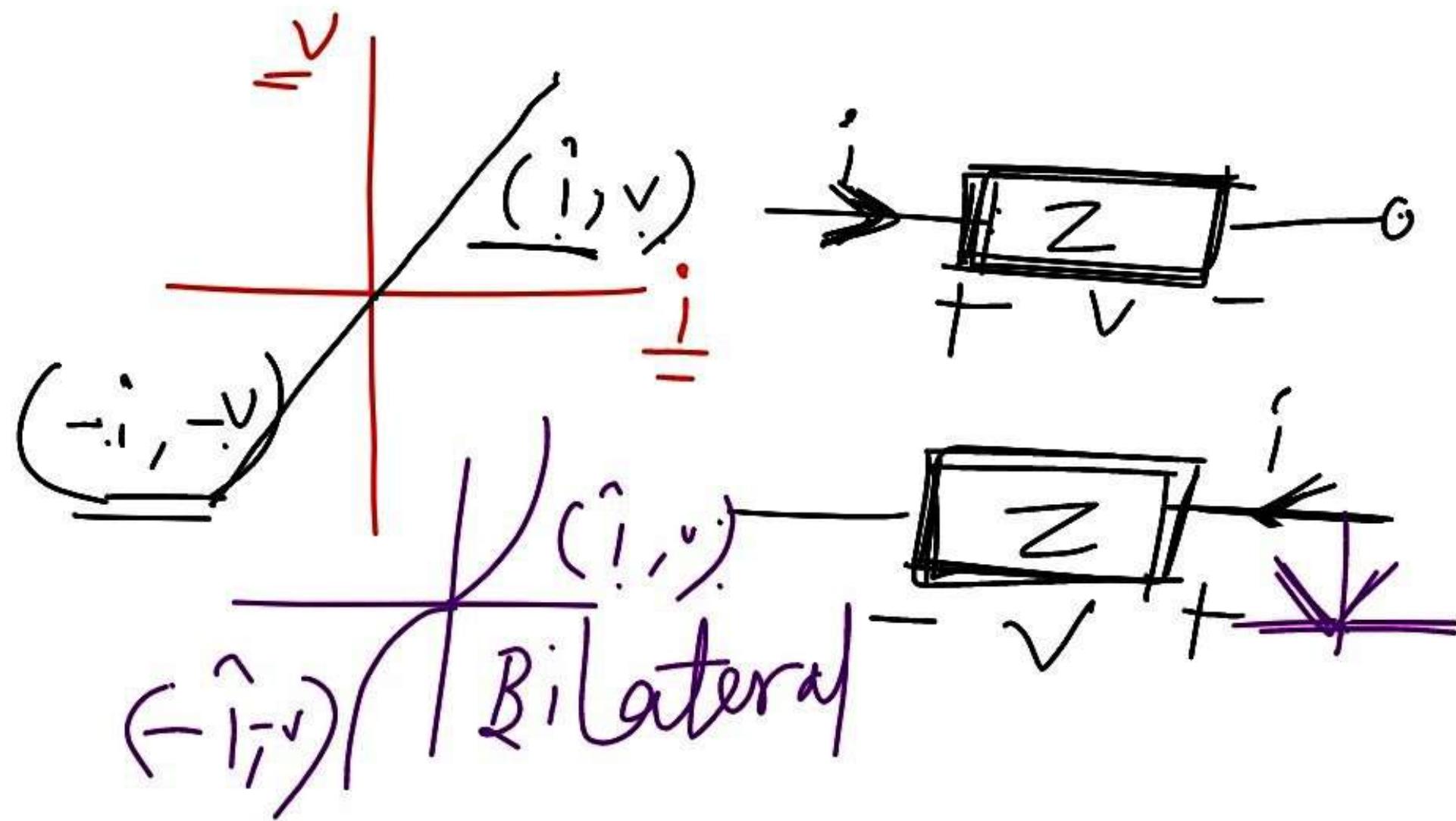- ① Linear & Non linear.
- ② Passive & Active.
- ③ Bilateral & Unilateral
- ④ Distributed & lumped.
- ⑤ Time invariant & Time varying.



Z \rightarrow Leakage Resistance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

↓ Impedance
↓ Resistor. Inductive Reactance
↓ Capacitive Reactance

① Distributed \Rightarrow Lumped

(R, L, C) \leftarrow Lumped


1 MHz

R LC \rightarrow Distributed across
entire ckt. $> 1 \text{ MHz}$

They are related to size
of the system.


⑤ Time invariant & Time varying

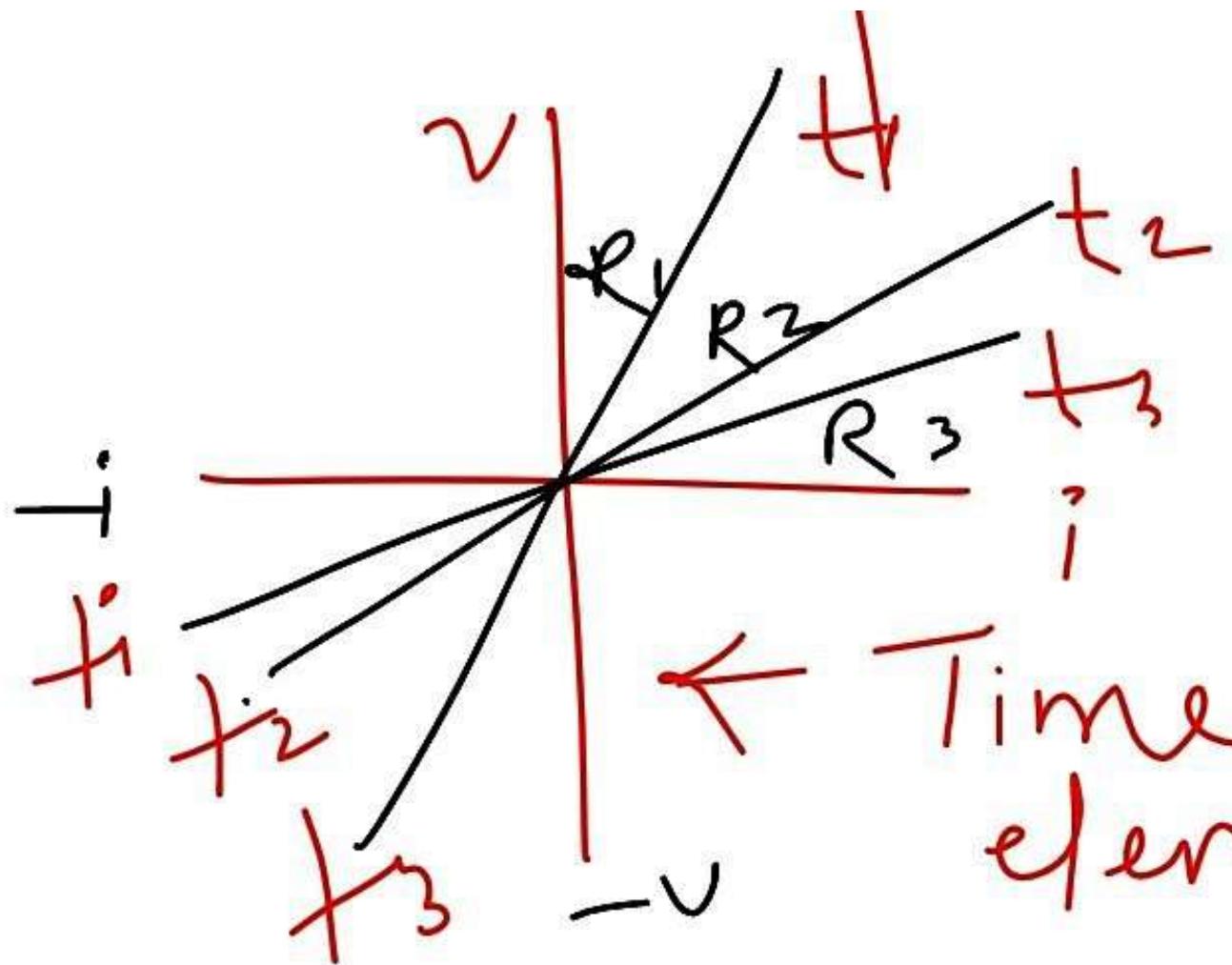An element is said to be time invariant if, for all time t , its characteristics do not change with time.




Time varying
element!

Kirchhoff's Law

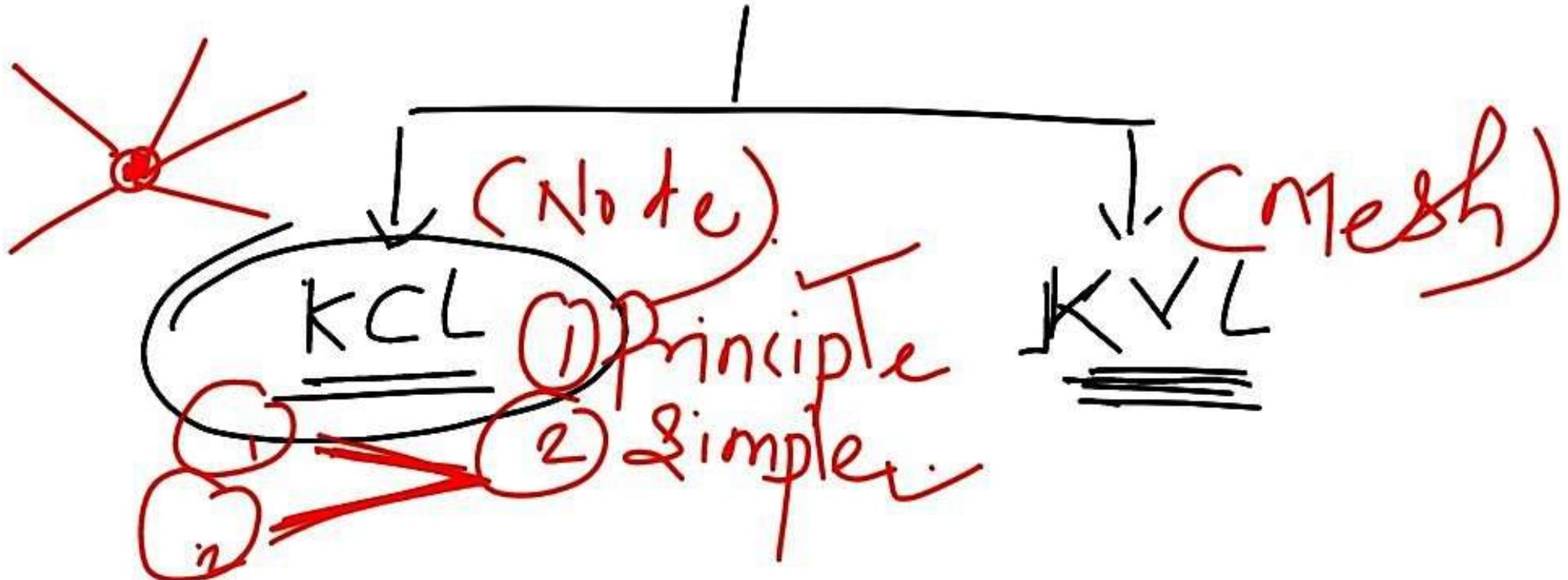

KCL (It is defined at node)

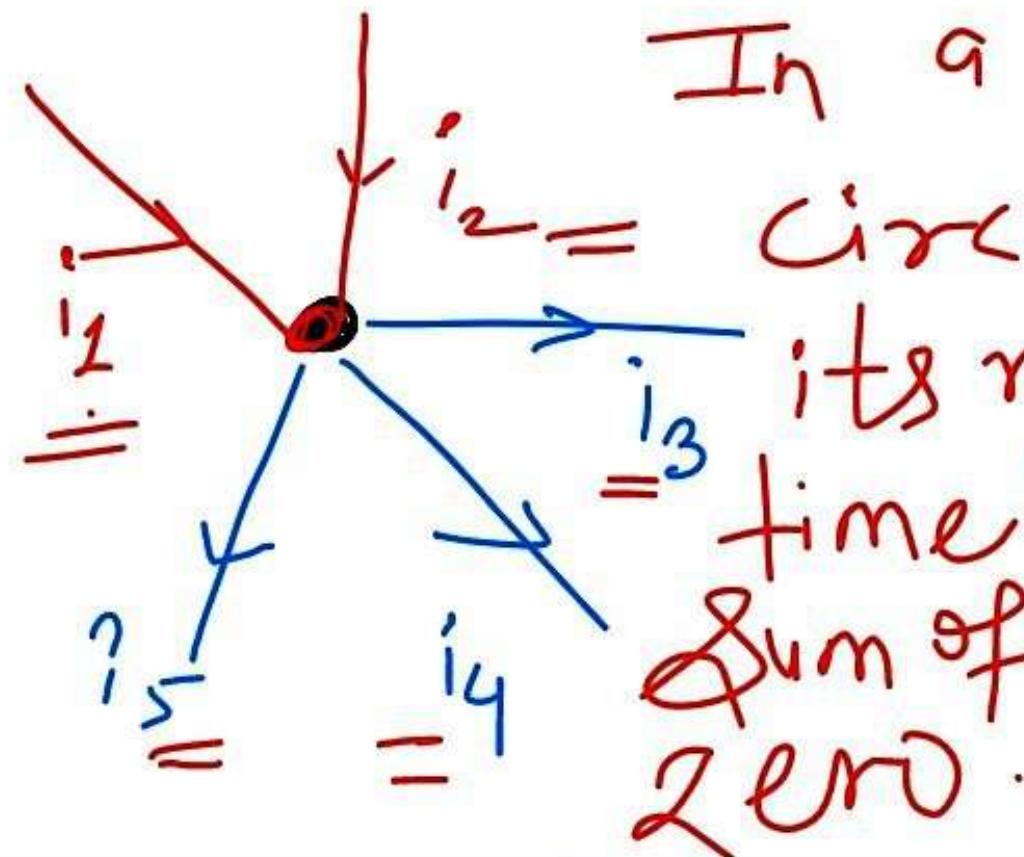

In a lumped electric circuit for any of its nodes and at any time 't' the algebraic sum of branch currents is zero.

By KCL


$$i_1 + i_2 = i_3 + \underline{i_4 + i_5} \quad | \checkmark$$

$$-i_1 - i_2 + i_3 + i_4 + i_5 = 0$$

$$i = \frac{dq}{dt} \Rightarrow \cancel{\frac{dq_1}{dt}} + \frac{dq_2}{dt} = \frac{dq_3}{dt} + \frac{dq_4}{dt} + \frac{dq_5}{dt}$$

$$\Rightarrow q_1 + q_2 = q_3 + q_4 + q_5$$

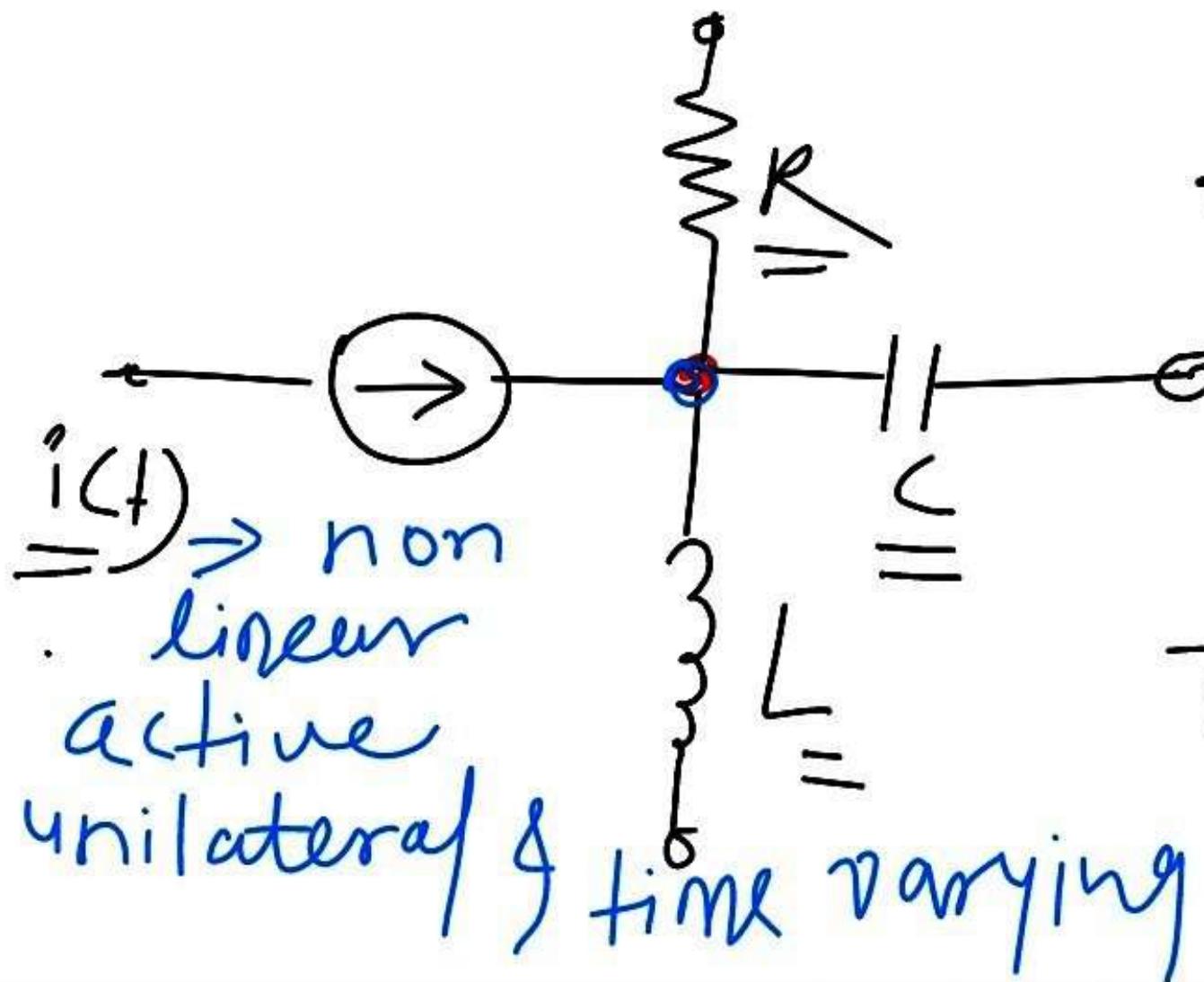i.e. Sum of entering charges
is equal to sum of leaving
charges.




$RLC \rightarrow$ linear
 \rightarrow passive
 bilateral
 time-invariant

- ⇒ KCL is independent of the nature of the element
- ⇒ It expresses conservation of charge at each & every node in lumped Electric ckt.

KVL \Rightarrow $\mathcal{I}F$ is defined in a
loop or mesh.
(i.e. closed path)

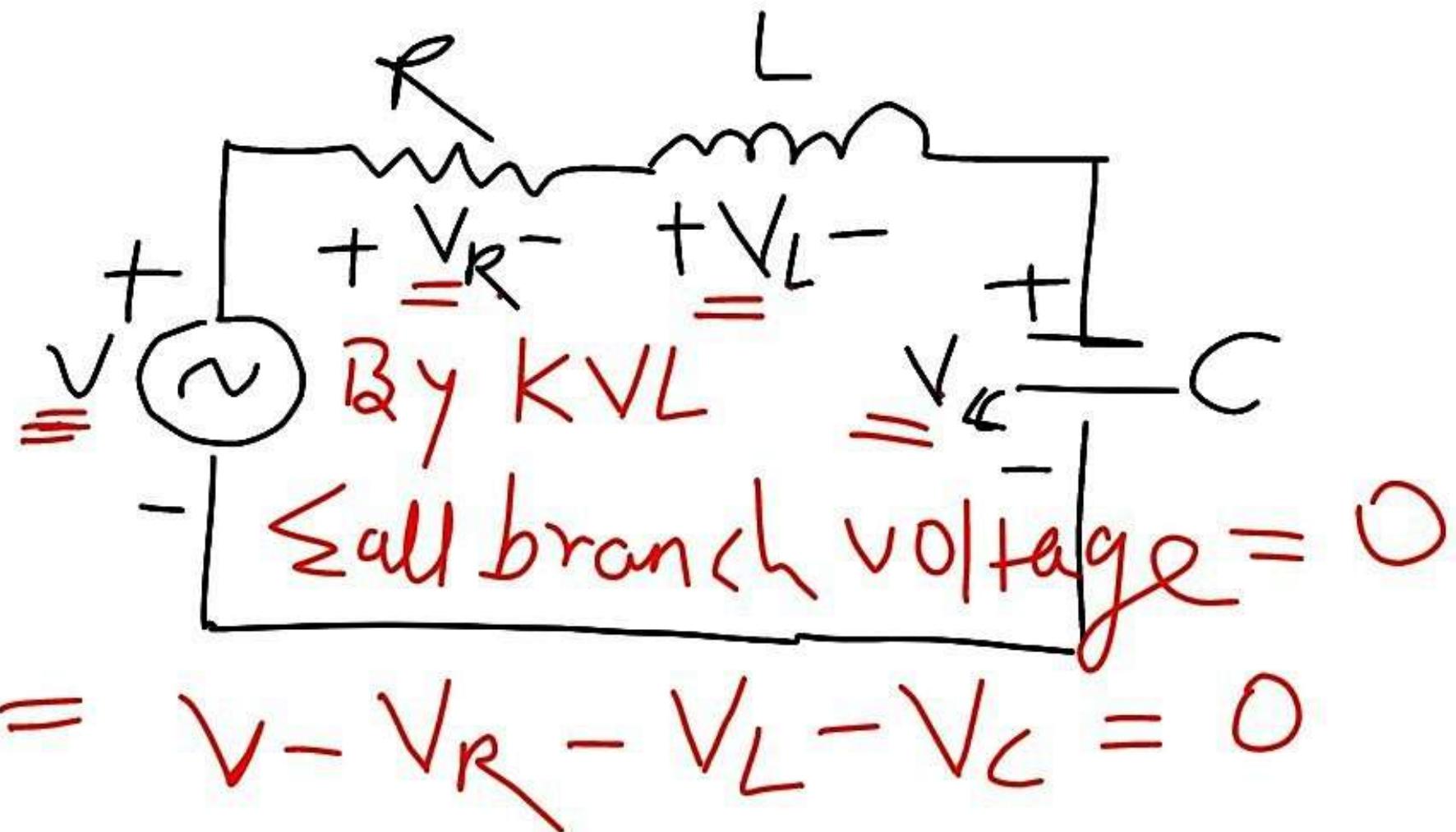KVL :- In a lumped electric circuit for any of its loops and at any time 't' the algebraic sum of branch voltages around the loop is zero.



Total voltage

$$\underline{V} = \underline{V_R} + \underline{V_L} + \underline{V_C}$$

Algebraic sum = 0

$$\underline{V} = \frac{\underline{W}}{q} = \frac{\underline{W_R}}{q} + \frac{\underline{W_L}}{q} + \frac{\underline{W_C}}{q}$$

$$W = W_R + W_L + W_C$$

- ① KVL is independent of nature of the element
- ② KVL expresses conservation of energy in every loop of lumped electric Ckt.

Nodal & Mesh Analysis Technique.


Nodal Analysis \Rightarrow KCL + Ohm's law.

Mesh Analysis \Rightarrow KVL + Ohm's law.

Ohm's law \rightarrow function of nature
of element (8 diff forms
of Ohm's law)


(R, L, C) ~~✓~~ Not Applicable
 $J = \sigma E$ for active elements,
Ex. source (Generators)

① Nodal Analysis

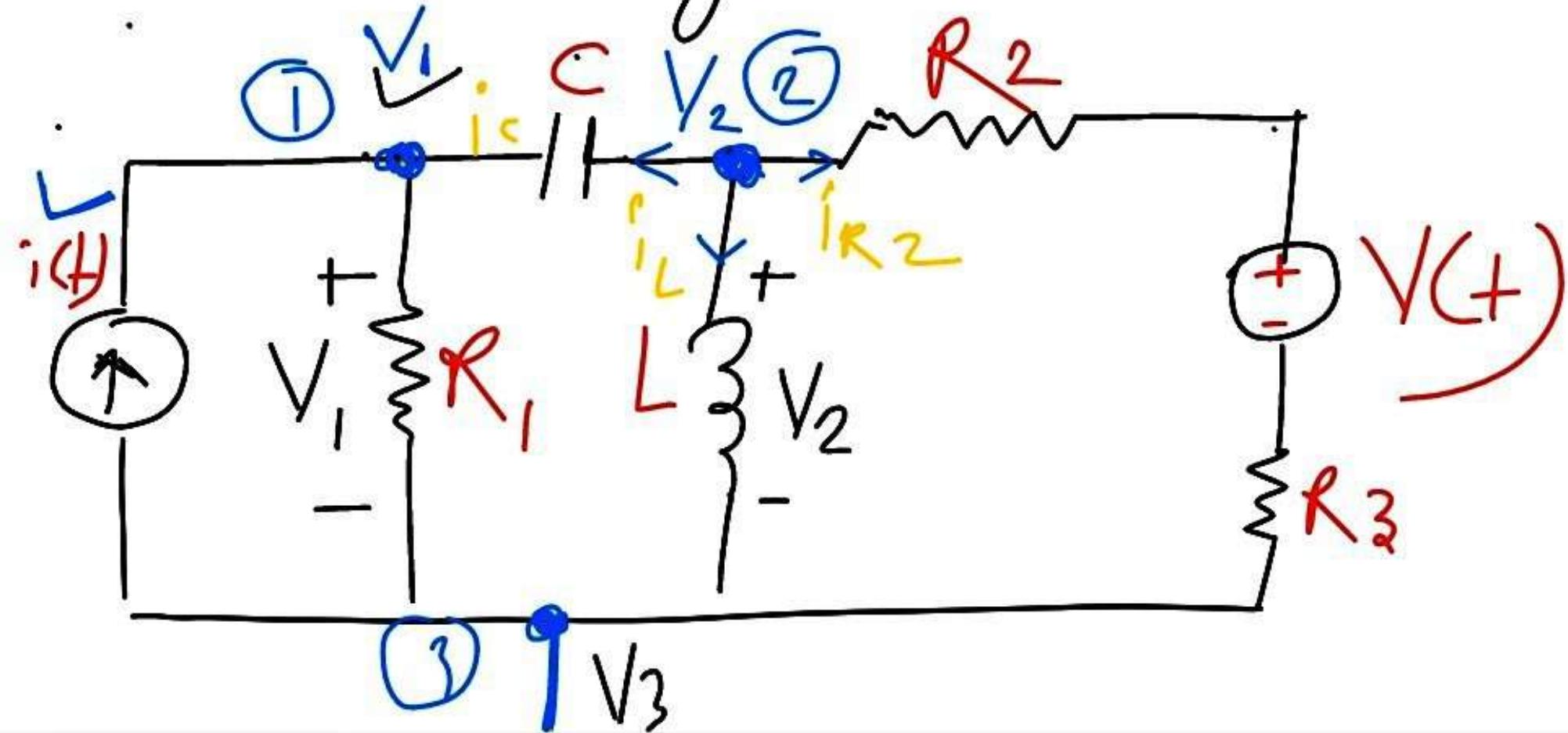

- ① Identify the nodes
- ② Assign node voltages w.r.t. ground node (whose voltage is always zero)
- ③ KCL first \leftarrow 1st
 Ohms law \leftarrow 2nd

① Nodal Analysis

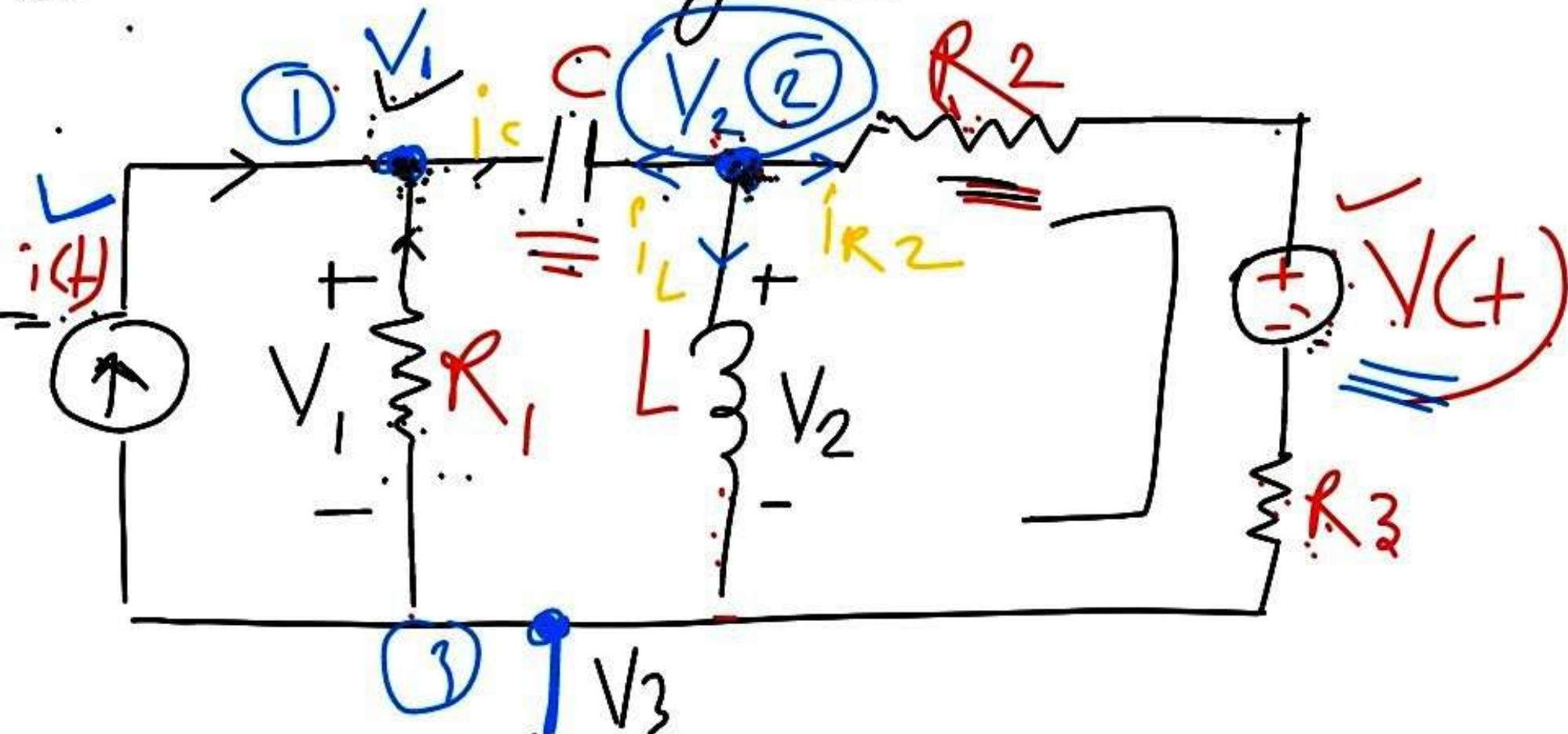


- ① Identify the nodes
- ② Assign node voltages w.r.t
ground node (whose voltage
is always zero)
- ③ KCL first \leftarrow 1st ✓
Ohms law \leftarrow 2nd ✓

Node ② ($V_2 > V_1$)
 $V_2 > 0$
 $V_2 > v(t)$)

By KCL $\Rightarrow \underline{I_C} + \underline{I_L} + \underline{I_R} = 0$


$C \frac{d(V_2 - V_1)}{dt} + \frac{1}{L} \left(\underline{\int_{-\infty}^t V_2 dt} + \frac{V_2 - v(t)}{R_L + R_3} \right) = 0$ ————— ①

(by Ohm's Law)

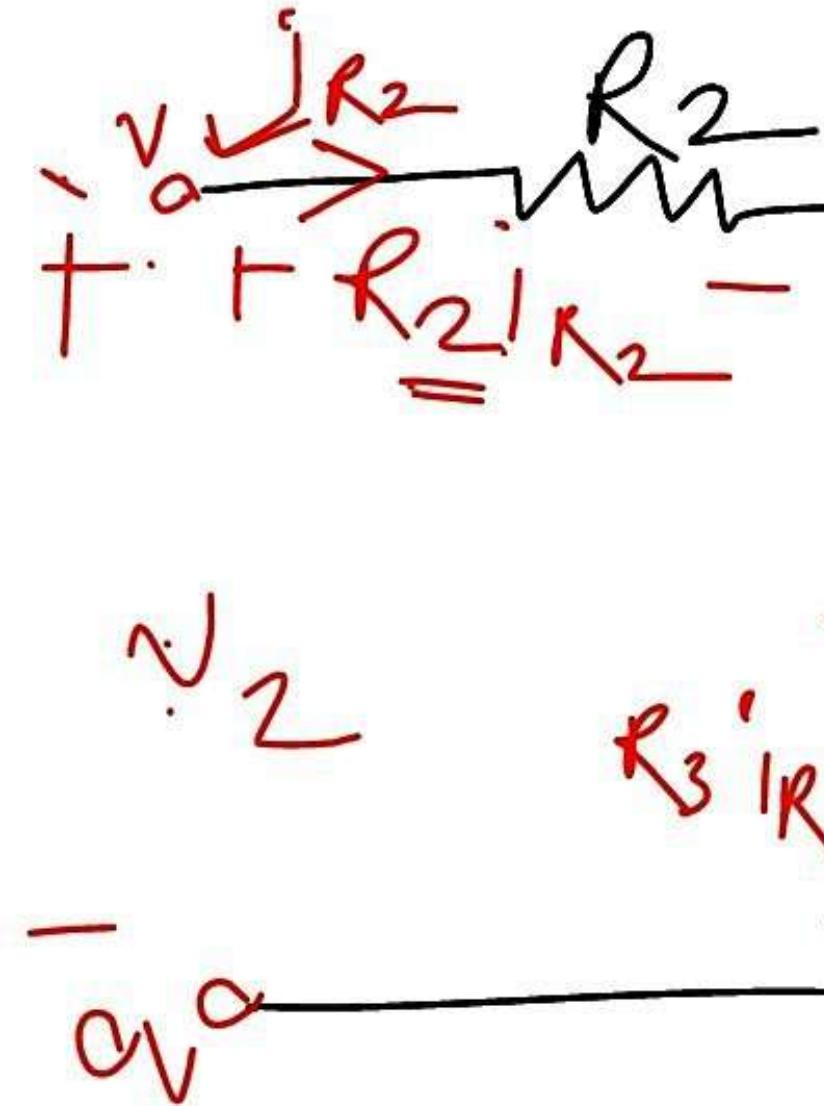


By KVL

$$V_2 - R_2 i_{R_2} - v(+)$$

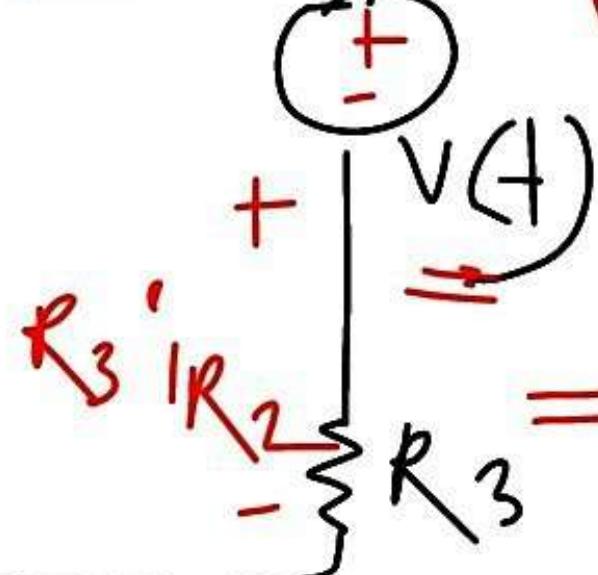

$$R_3 i_{R_2} = 0$$
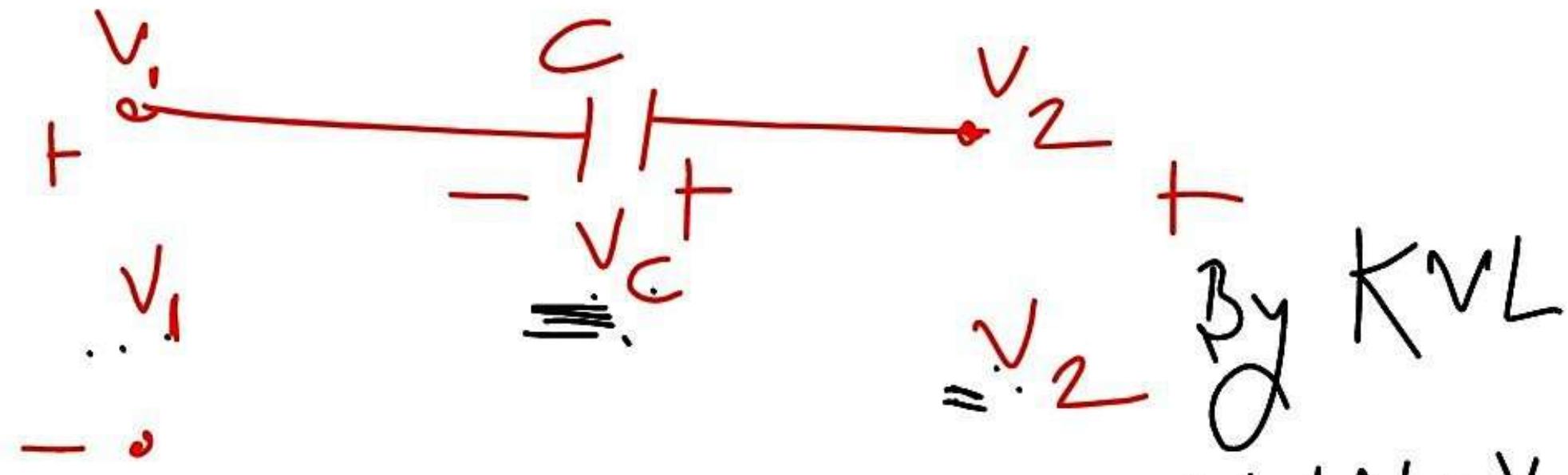
$$i_{R_2} = \frac{V_2 - v(+)}{R_2 + R_3} \text{ A.}$$



$$V_2 = V_1 + V_C \quad \text{By KVL}$$

$$V_C = V_2 - V_1$$

By Ohm's law $\frac{V_C}{R} = i_C$

$$i_C = C \frac{dV_C}{dt}$$

Current through C.

$$\Rightarrow \dot{C} = C \frac{d}{dt} (V_2 - V_1)$$

Node ①. ($v_1 > 0$, $v_1 > v_2$)

$$-i(+)+\frac{v_1}{R_1}+\left(\frac{d}{dt}(v_1-v_2)\right)=0$$


— ②

(By Nodal Analysis)

$$+V_1 \xrightarrow{+} \text{---} \xleftarrow{V_C} \text{---} +V_2$$
 By KVL
 $V_C = V_1 - V_2$


Ohm's Law : $-V_2$
 $\bar{I}_c = C \frac{dV_C}{dt}$ $\bar{I}_c = C \frac{d}{dt} (V_1 - V_2)$

Mesh Analysis :-

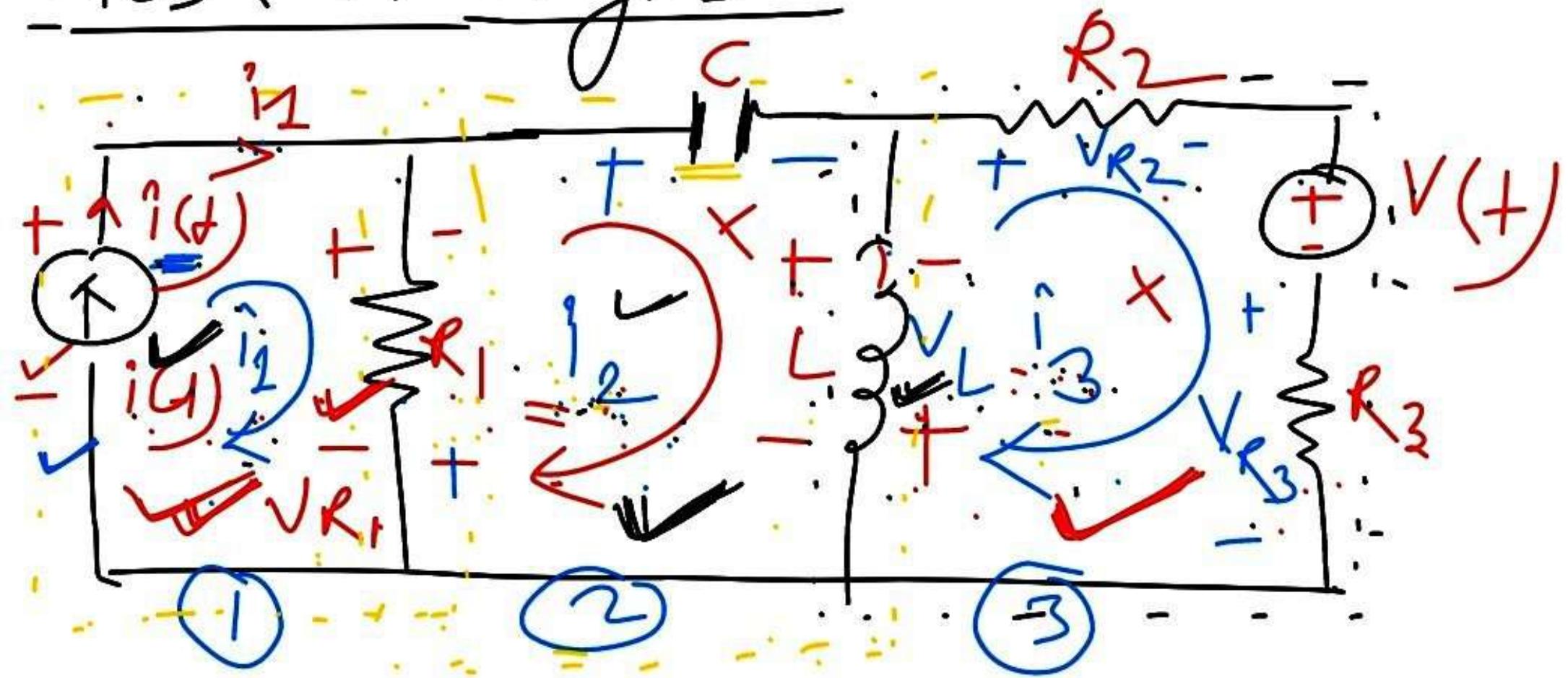


- ① Identify the mesh.
- ② Assign mesh current
(clockwise direction)
- ③ By using KVL & Ohm's Law
next. write the mesh eqn.

Mesh ① ($i_1 > i_2 \& i_1 > i_3$)

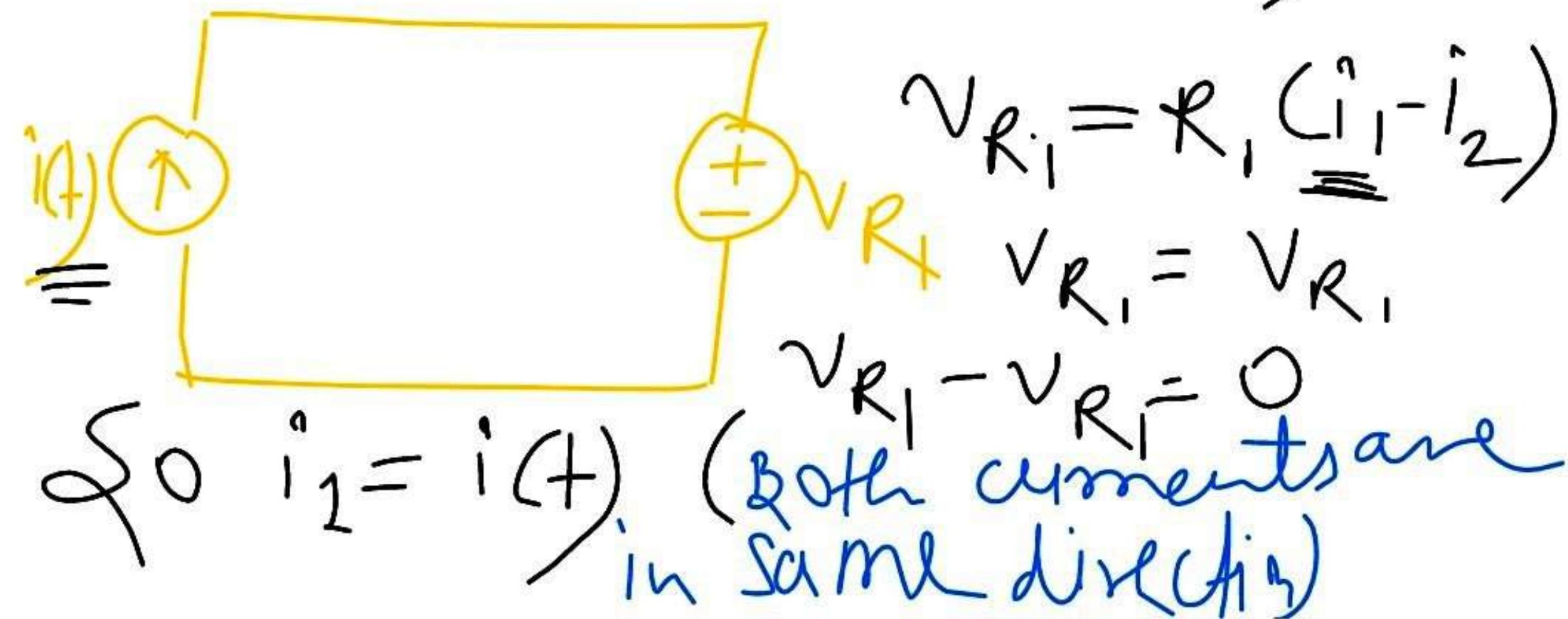

Mesh ②

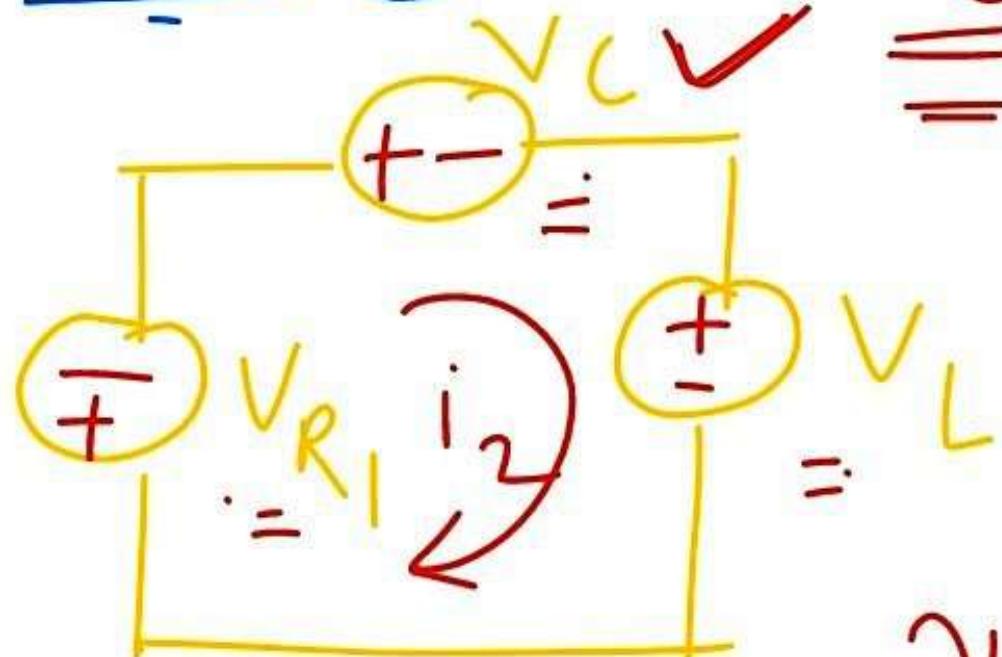

$$V_C = \frac{1}{C} \int_{-\infty}^t i_2 dt$$


$$V_L = L \frac{di}{dt} (i_2 - i_3)$$
$$\equiv V_{R1} = R_1 (i_2 - i_1)$$

By KVL $V_{R_1} + V_C + V_L = 0$

⇒ By Ohm's Law.

$$-R_1(i_2 - i_1) - \frac{1}{C} \int_{-\infty}^t i_2 dt - L \frac{d}{dt}(i_2 - i_3) = 0$$

— (2)

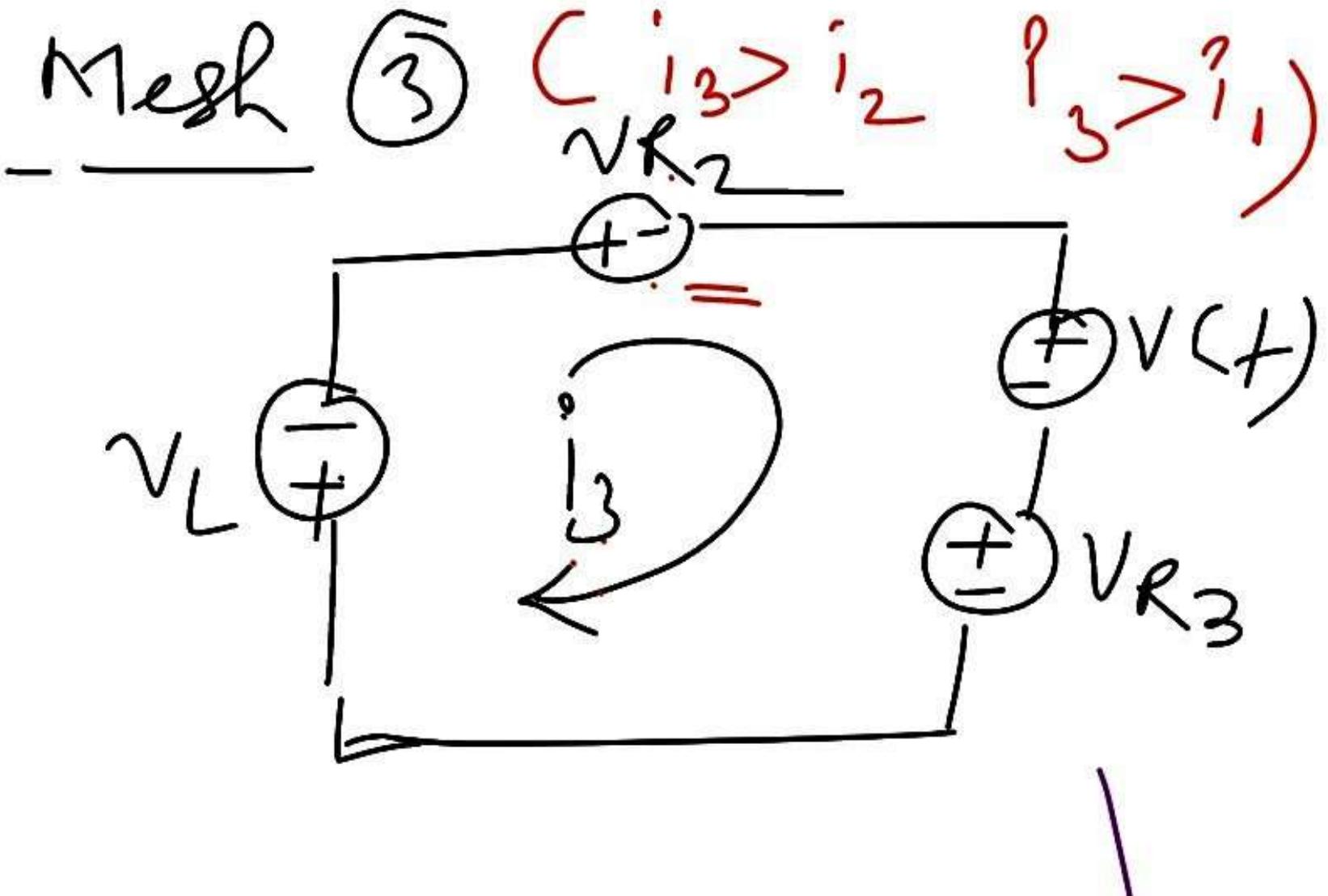

$$\checkmark v_{R_2} = R_2 \dot{i}_3 \quad \checkmark$$

$$\checkmark v_{R_3} = R_3 \dot{i}_3 \quad \checkmark$$

$$\checkmark v_L = L \frac{d}{dt} (\dot{i}_3 - \dot{i}_2) \quad \checkmark$$

$$v(+) =$$


$$-V_L - V_{R_2} - V_{R_3} - \underline{v(t)} = 0$$

(KVL)


$$= -L \frac{d}{dt}(i_2 - i_3) - R_2 i_3 - R_3 i_3 - \underline{v(t)} = 0$$

(Ohm's law)

find current in 3Ω

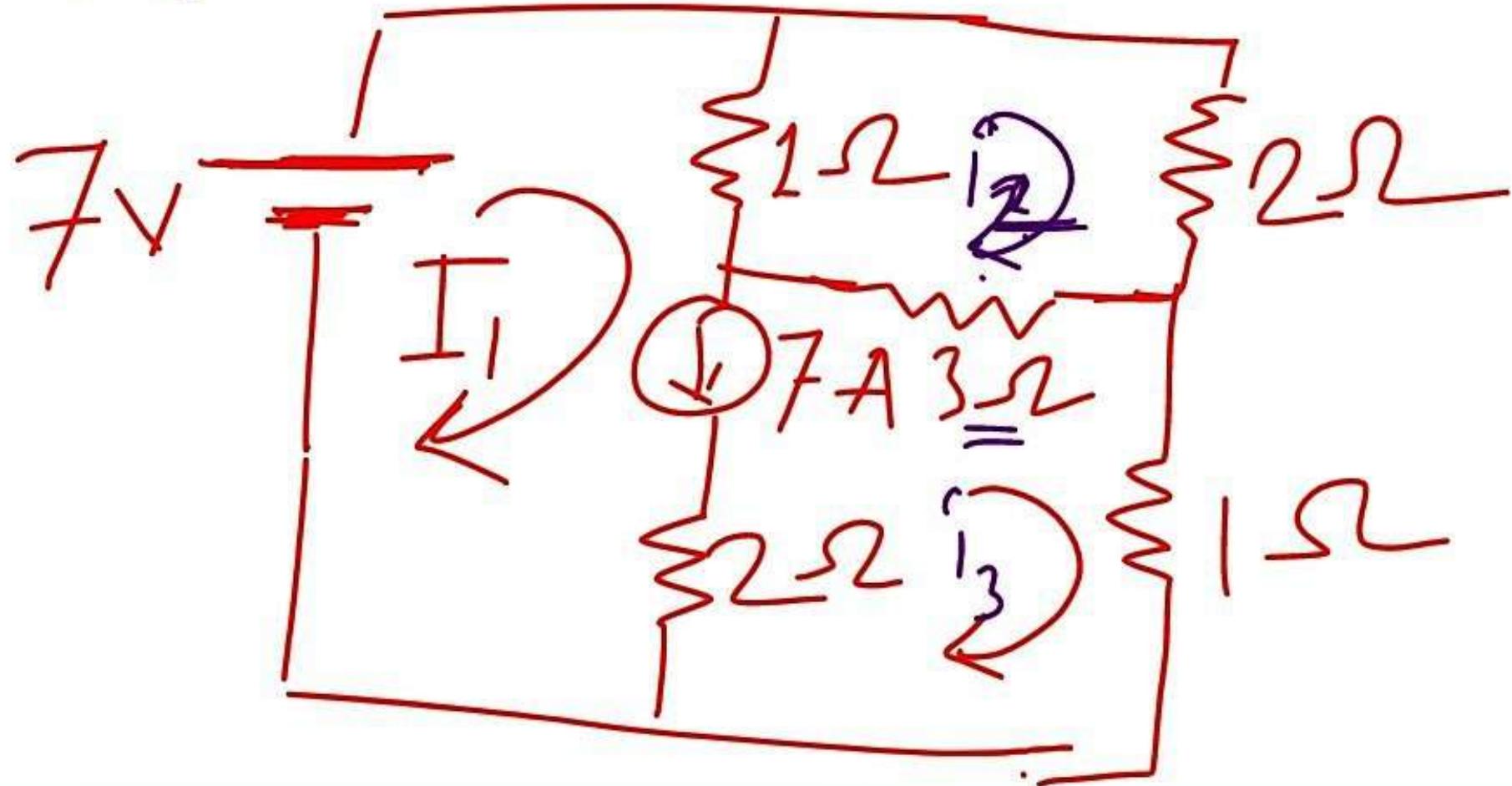

find the current in ω_3 -resistor

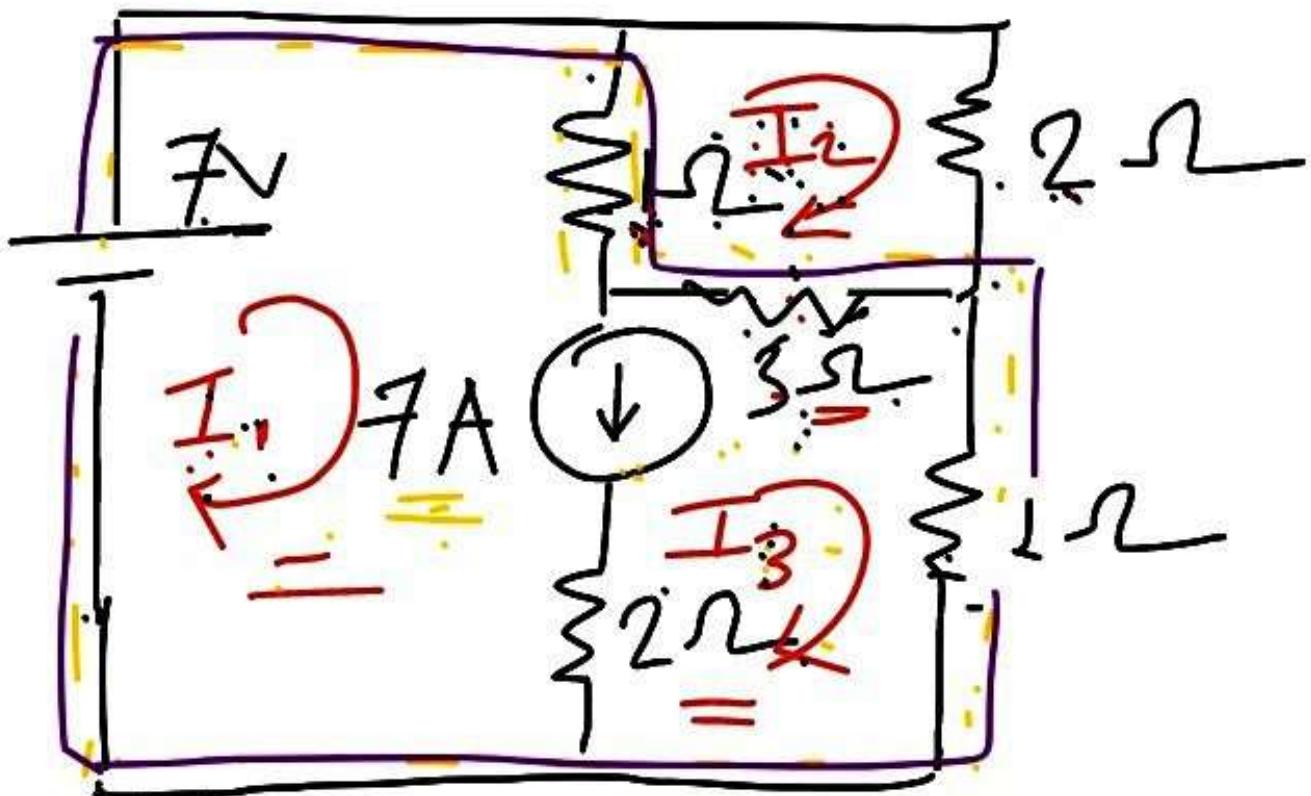

$$\underline{I_2 - I_3}$$

$$I_1 - I_3 = 7 \quad \text{--- } ①$$

By Applying KVL to Supermesh.

$$7 - 1(I_1 - I_2) - 3(I_3 - I_2) - I_3 = 0$$

$$\begin{aligned} 7 - I_1 + 4I_2 - 4I_3 &= 0 \\ -I_1 + 4I_2 - 4I_3 &= -7 \quad \text{--- } ② \end{aligned}$$

Applying KVL to mesh ②

$$\Rightarrow -1(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) = 0$$
$$= \underline{I_1} - 6I_2 + 3I_3 = 0$$

— ③

$$I_1 = 9 \text{ Amp.}$$

$$I_2 = 2.5 \text{ Amp.}$$

$$I_3 = 2 \text{ Amp.}$$

Current through $3\Omega = I_2 - I_3$

$$= 2.5 - 2 = 0.5 \text{ Amp.}$$


Equivalent ckt w.r.t passive
RLC

Two elements are in series

→ Some current through the element

→ Two elements are in ||el.

→ Same voltage across the eleme

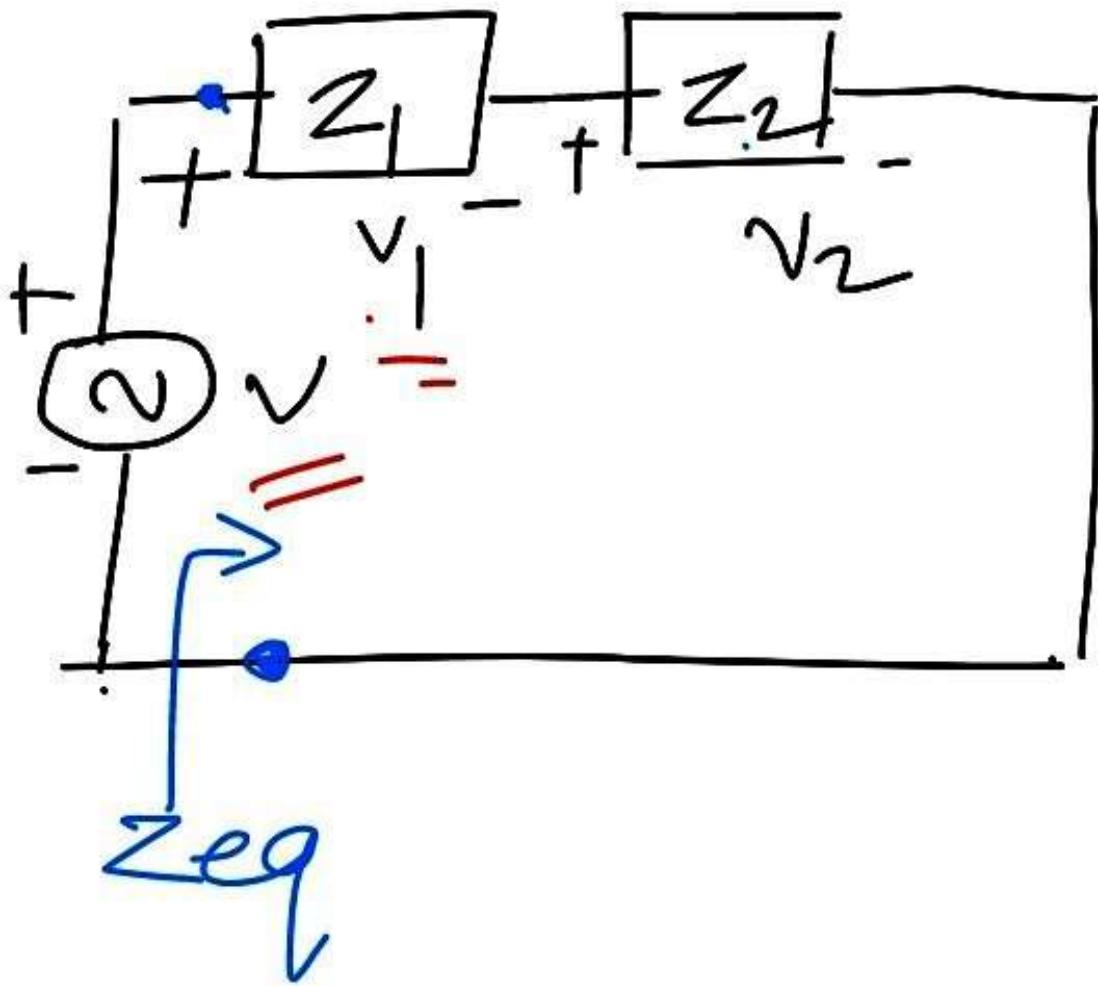

$$\begin{aligned}
 Z &= Z_R = R \\
 Z_L &= j\omega L \\
 Z_C &= \frac{1}{j\omega C}
 \end{aligned}$$

$$Z_{eq} = Z_1 + Z_2$$

$$R_{eq} = R_1 + R_2$$

$$L_{eq} = L_1 + L_2$$

$$C = \frac{1}{C_{eq.}} = \frac{1}{C_1} + \frac{1}{C_2}$$

If $C_1 \neq C_2 = C$

$$C_{eq} = \frac{C}{2}$$

Voltage division principle.

$$V = Z_{eq} I \quad (\text{By Ohm's law})$$

$$I = \frac{V}{Z_{eq}} = \frac{V}{Z_1 + Z_2}$$

$$V_1 = Z_1 I \quad (\text{Ohm's law})$$

$$V_1 = \frac{Vz_1}{z_1 + z_2}$$

$$V_2 = z_2 I \text{ (Ohm's law)}$$

$$V_2 = \frac{z_2 V}{z_1 + z_2}$$


By KVL $V - V_1 - V_2 = 0$

$$\boxed{V_1 + V_2 = V}$$

R: $V_1 = \frac{VR_1}{R_1 + R_2} \quad V_2 = \frac{VR_2}{R_1 + R_2}$

L: $V_1 = \frac{VL_1}{L_1 + L_2} \quad V_2 = \frac{VL_2}{L_1 + L_2}$
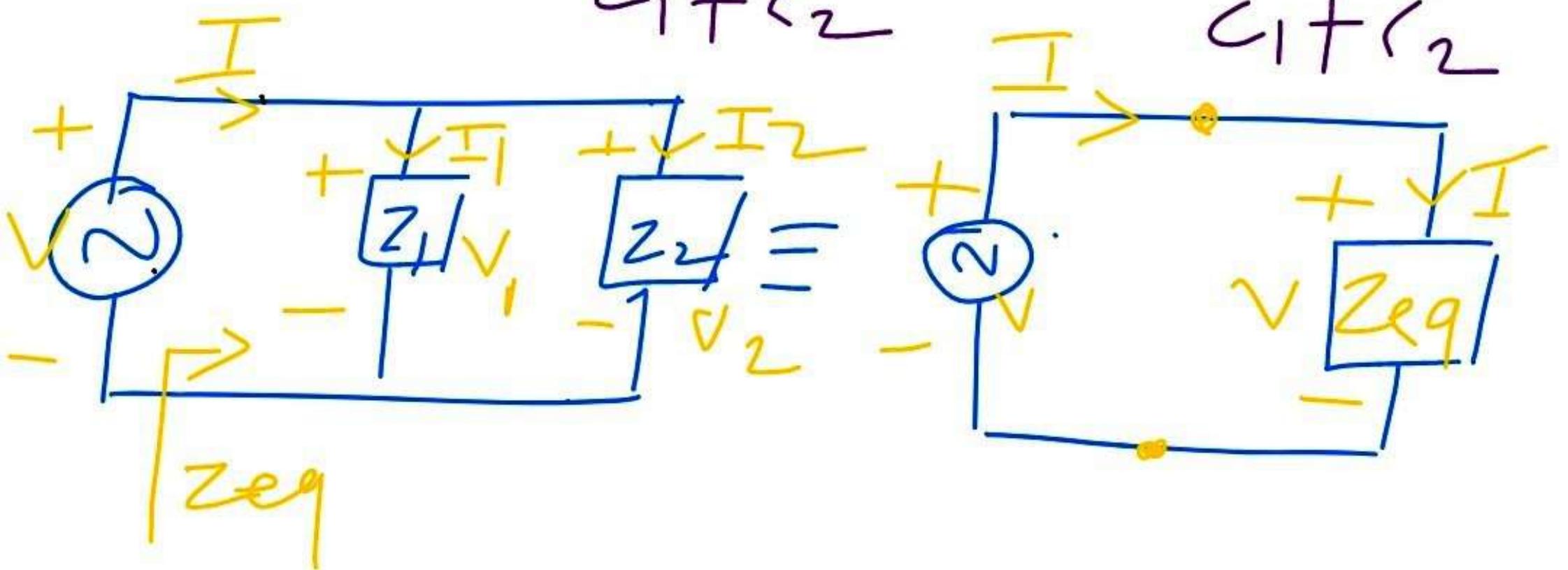
$$= C : \quad v_1 = \frac{vG}{C_1 + C_2} \quad v_2 = \frac{vC_2}{C_1 + C_2}$$



$$Y_{eq} = Y_1 + Y_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} \Rightarrow Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$R_{eq} = \frac{1}{R_{eq}} = \frac{1}{R_1 + R_2} \text{ if } R_1 = R_2 = R$$

$R_{eq} = R/2$

$$L = \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$C = C_{eq} = C_1 + C_2$$

Current division Principle

$$V = Z_{eq} \cdot I \quad (\text{By ohm's law})$$

$$\underline{V} = \frac{Z_1 Z_2}{Z_1 + Z_2} \cdot I$$

$$I_1 = \frac{V}{z_1}$$

$$I_1 = \frac{I \cdot z_2}{z_1 + z_2}$$

$$I_2 = \frac{V}{z_2} \Rightarrow \frac{I z_1}{z_1 + z_2}$$

By KCL


$$I = I_1 + I_2$$

$\Rightarrow I_1 = \frac{IR_2}{R_1 + R_2} \quad I_2 = \frac{IR_1}{R_1 + R_2}$

$\Rightarrow I_1 = \frac{IL_2}{L_1 + L_2} \quad I_2 = \frac{IL_1}{L_1 + L_2}$

$$C \Rightarrow I = \frac{Ic_1}{C_1 + C_2} \quad I_2 = \frac{Ic_2}{C_1 + C_2}$$

Star(Y) - Delta(Δ) Transformation

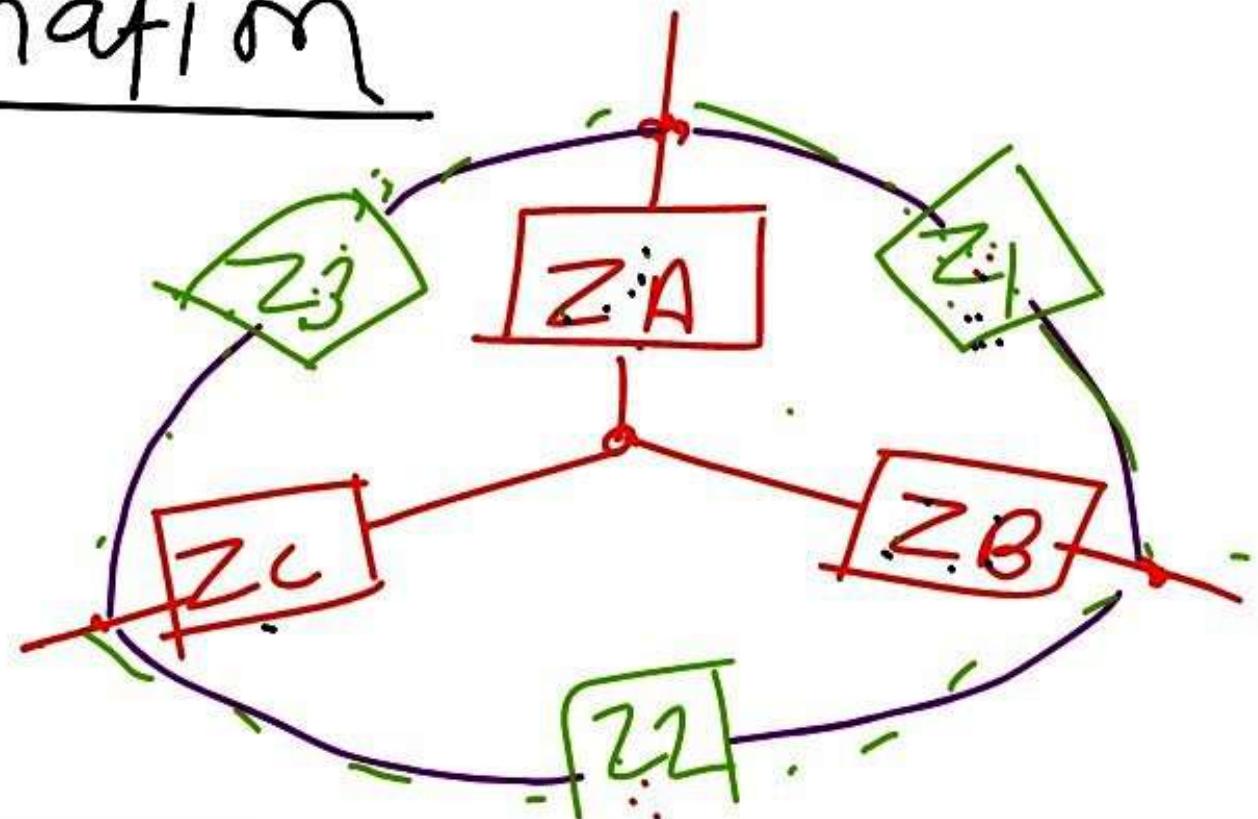

Case 1 $\Delta \rightarrow Y$.

Δ is given (z_1, z_2, z_3)

$$\textcircled{1} \quad z_A = \frac{z_1 \cdot z_3}{z_1 + z_2 + z_3} \Rightarrow \left(\begin{array}{l} \text{Product} \\ \text{Total} \end{array} \right)$$

$$\textcircled{2} \quad z_B \Rightarrow \frac{z_1 \cdot z_2}{z_1 + z_2 + z_3}$$

$$\textcircled{3} \quad z_C \Rightarrow \frac{z_2 \cdot z_3}{z_1 + z_2 + z_3}$$

If
 $z_1 = z_2 = z_3$
then
 $z_A = z_B = z_C$
 $\Rightarrow z_1/z_3 \checkmark$

Note :- Δ to Y Transformation

Impedance reduces by
3 times.

$$\underline{\underline{Y - \Delta}} \quad (z_A, z_B, z_C)$$
$$z_I = z_A + z_B + \left(\frac{z_A \cdot z_B}{z_C} \right)$$
$$= \cancel{\text{Sum}} \left(\frac{\text{Their product}}{\text{Remaining}} \right)$$

$$Z_2 = Z_B + Z_C + \left(\frac{Z_B \cdot Z_C}{Z_A} \right)$$

$$Z_3 = Z_C + Z_A + \left(\frac{Z_C \cdot Z_A}{Z_B} \right)$$


If $Z_A = Z_B = Z_C = Z$

$$Z_1 = Z_2 = Z_3 = 3Z \checkmark$$


If $Z_A = Z_B = Z_C = Z$


then $Z_1 = Z_2 = Z_3 = 3Z$

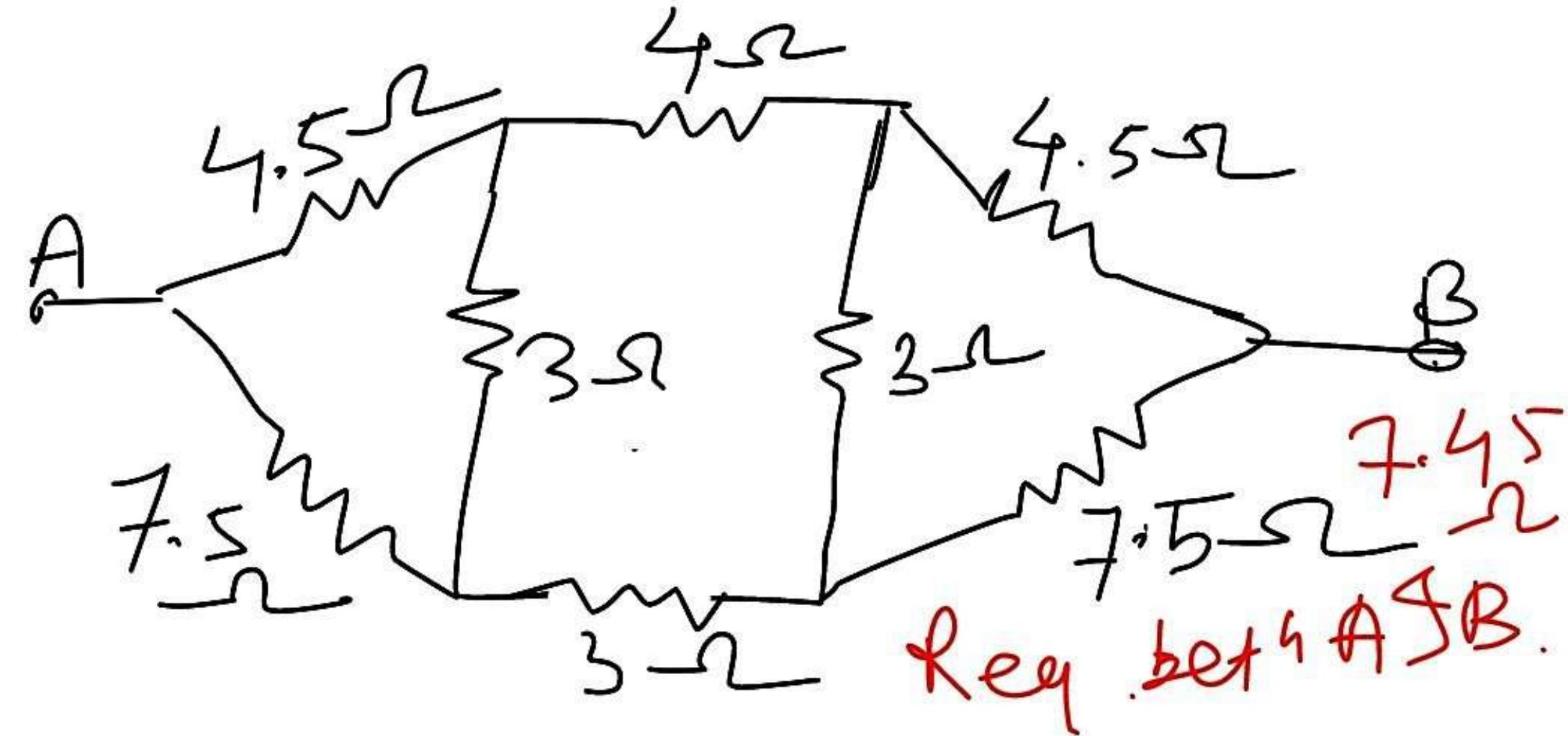
($\gamma + j\Delta \Rightarrow$ Impedance increase by 3 times.)



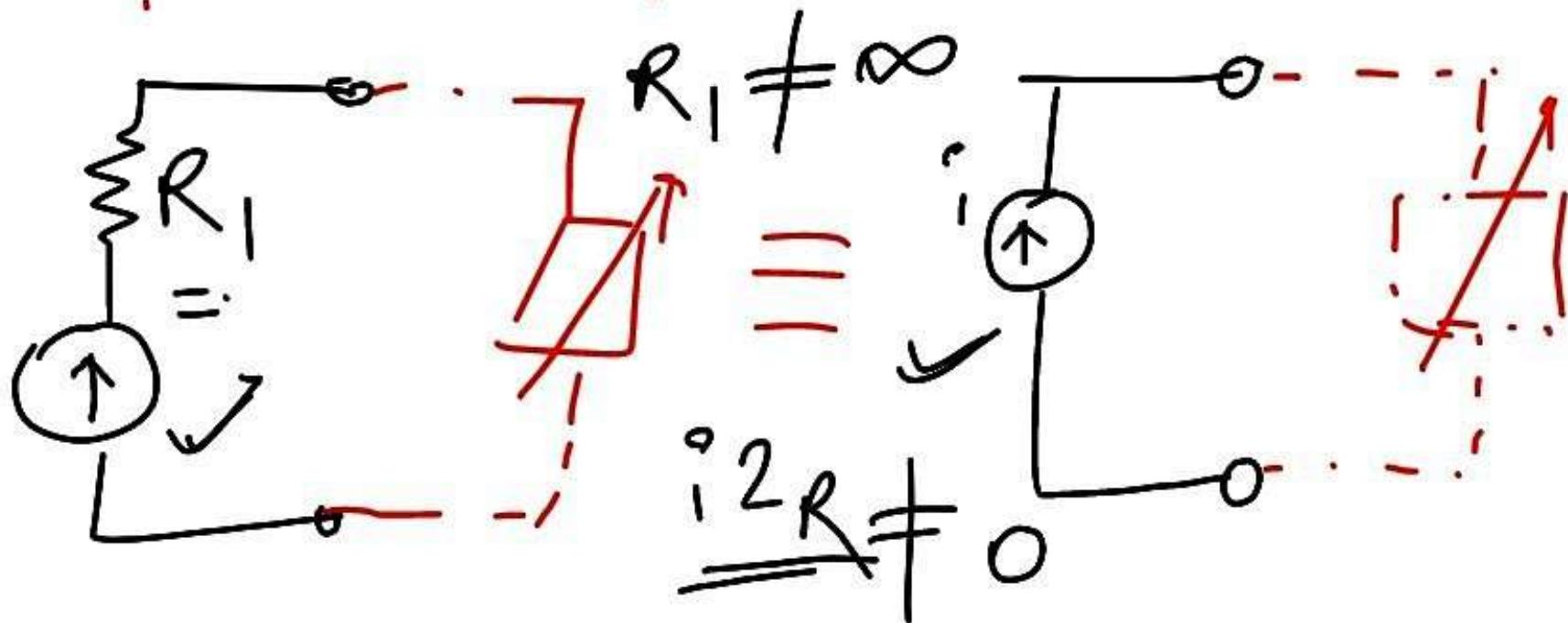
Equivalent Circuits w. σ to Active Sources



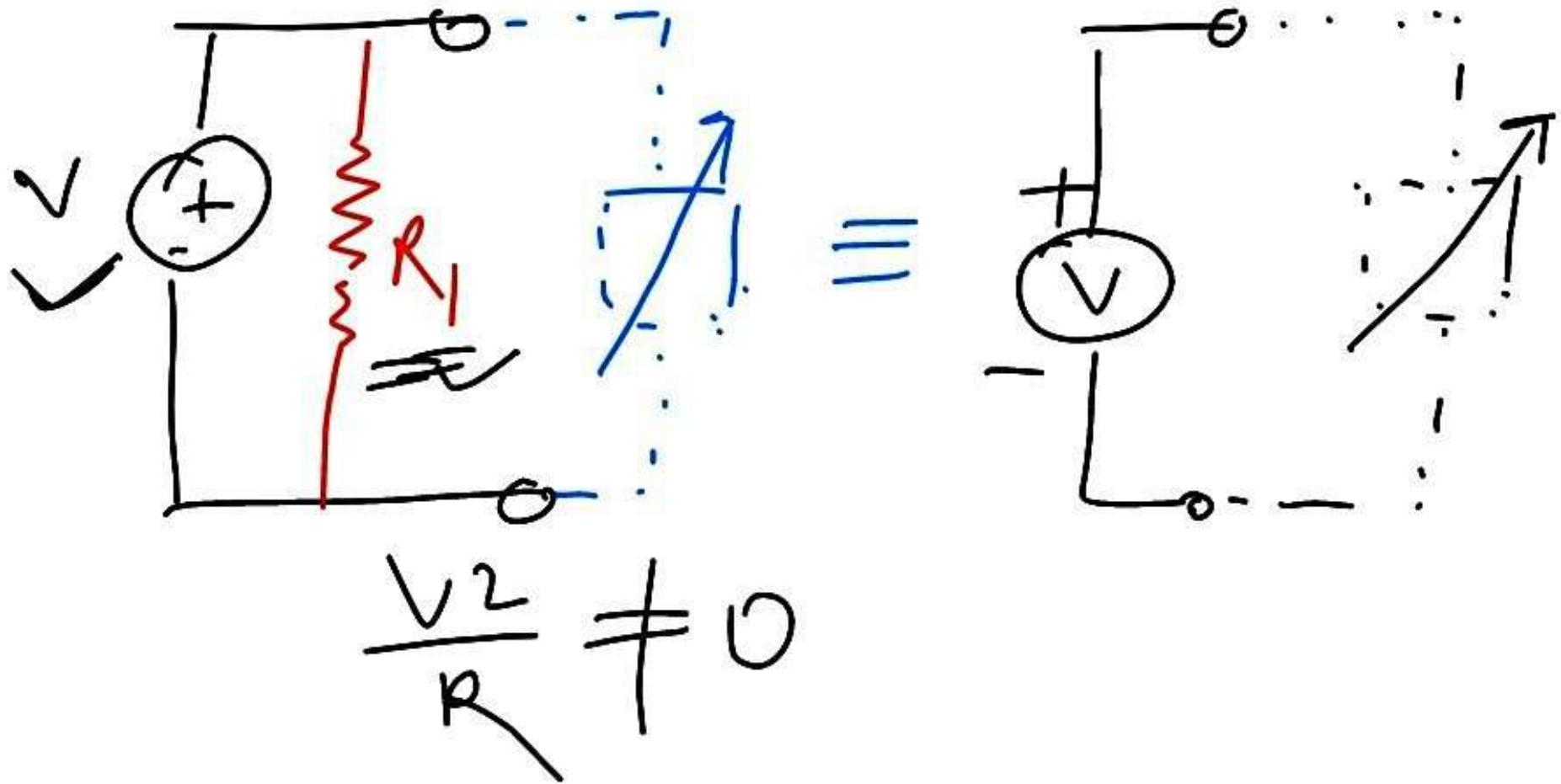


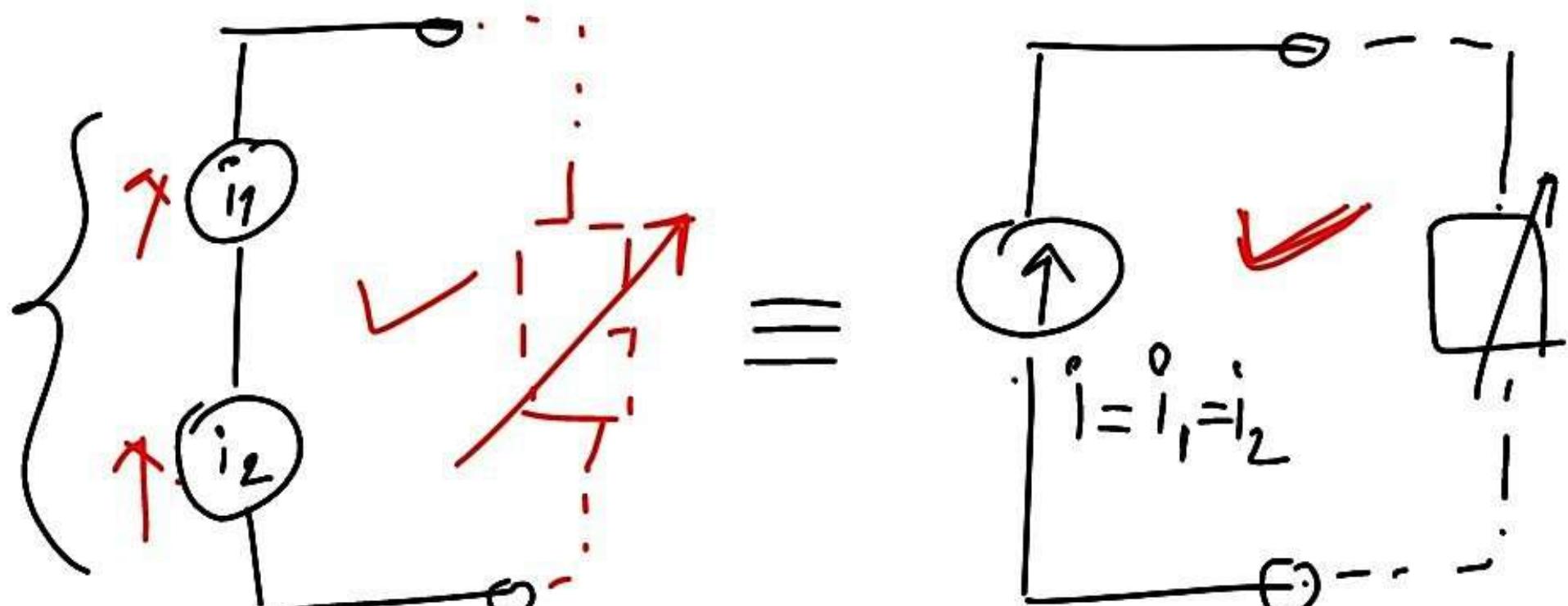


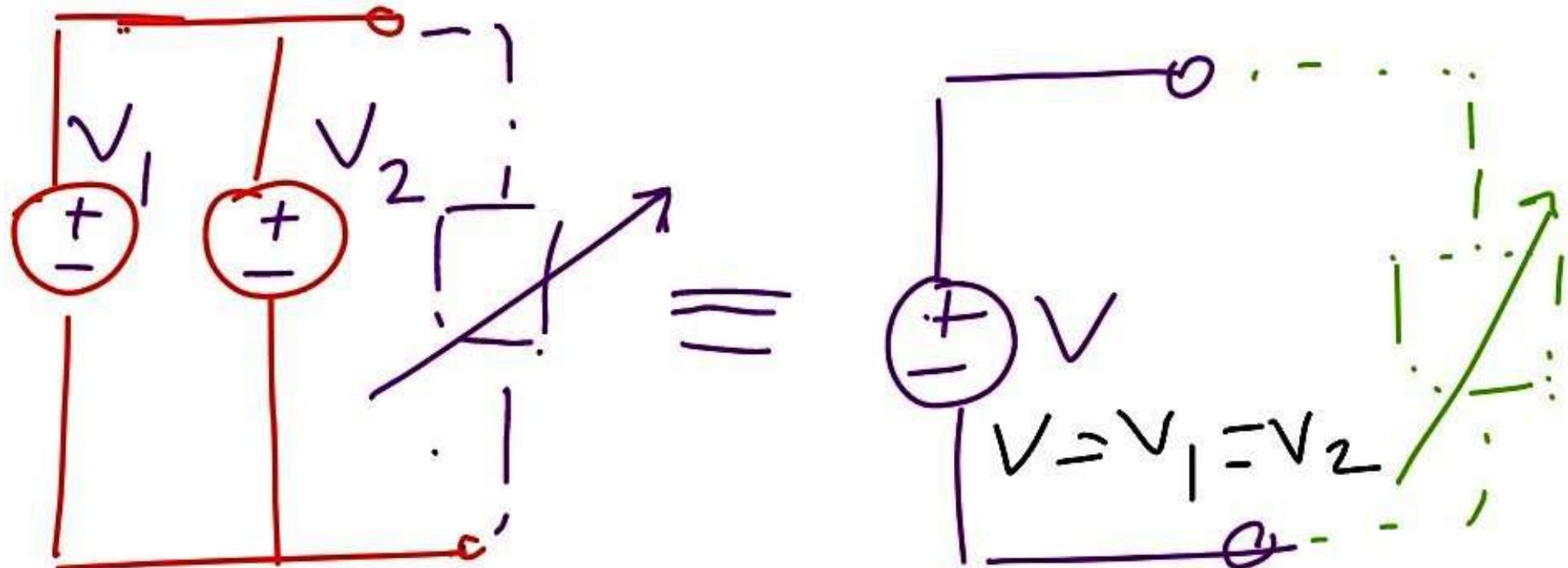
$$\text{By KCL} \Rightarrow i_2 + i_1 = 0 \quad i_1 = i_2$$



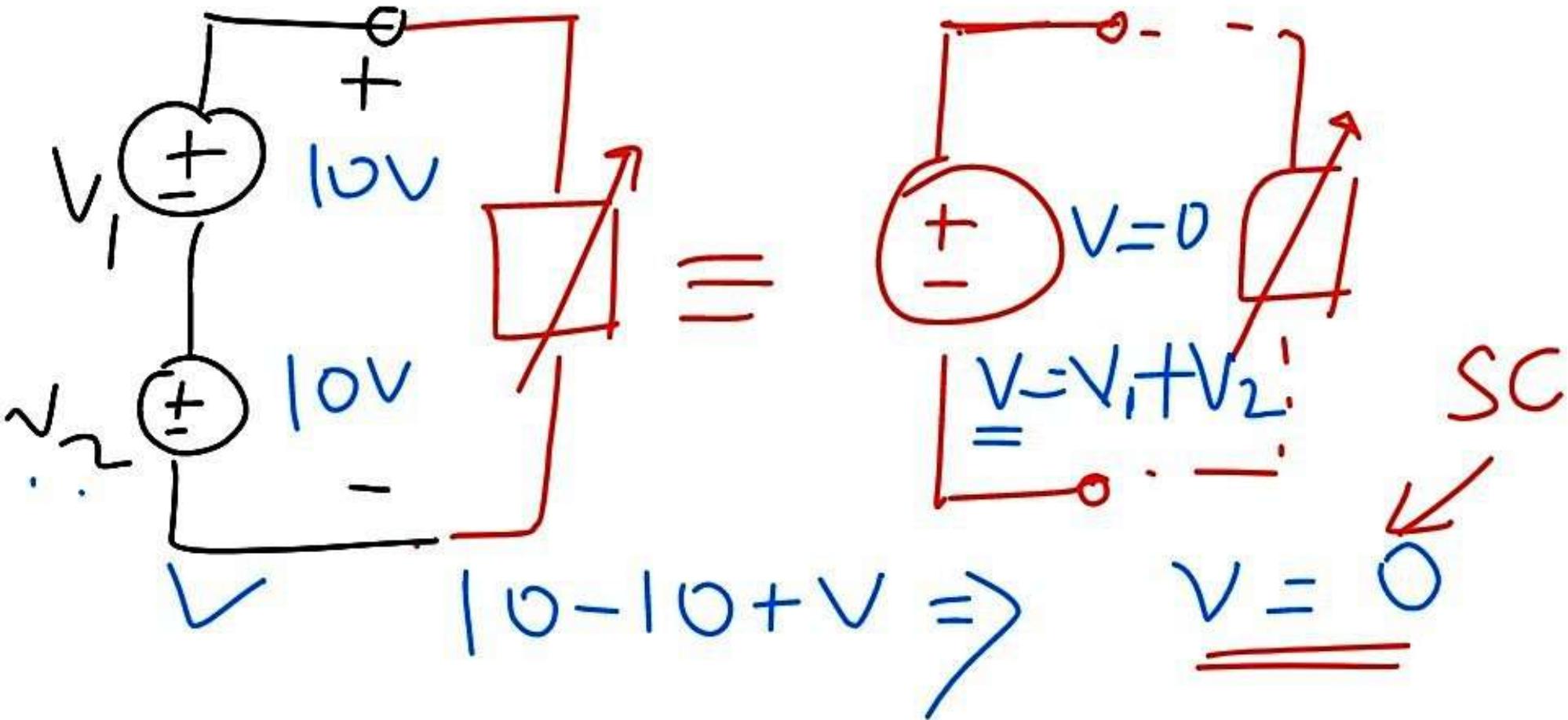
$$\text{By KVL } V_1 - V_2 = 0 \therefore \underline{\underline{V_1 = V_2}}$$



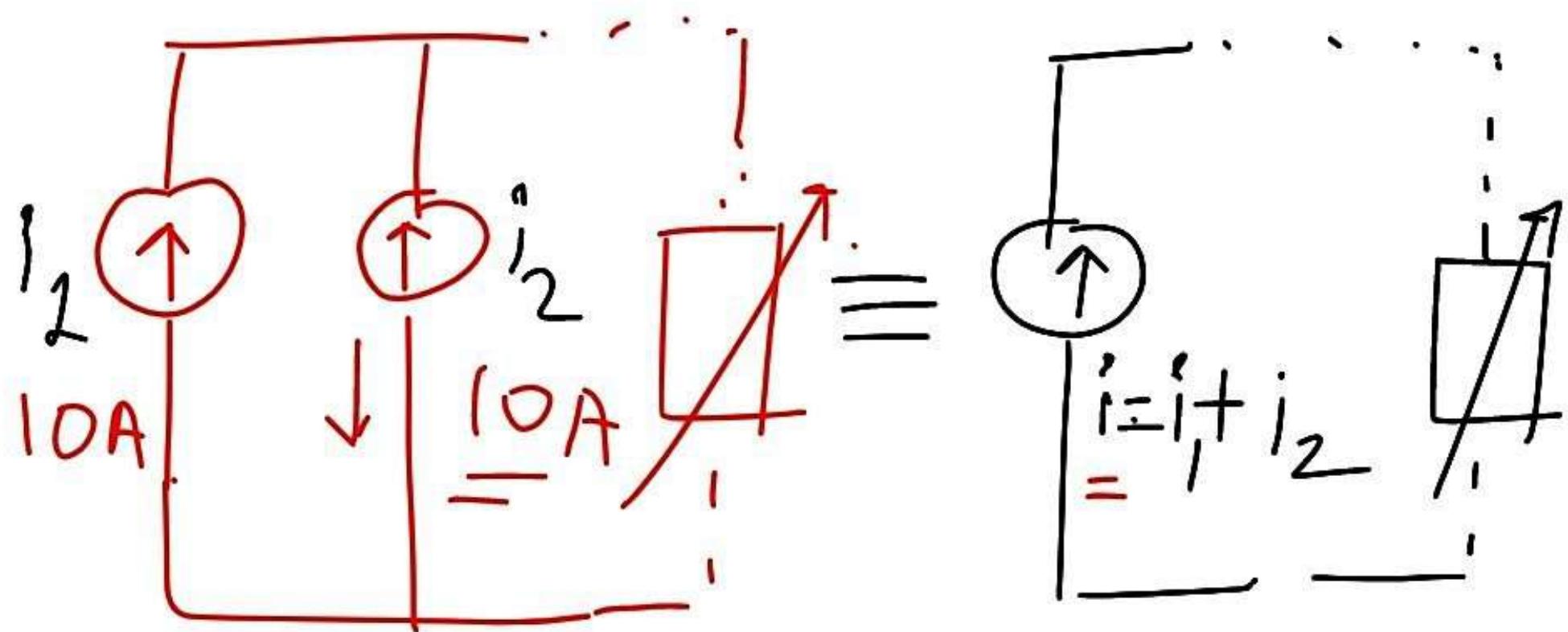

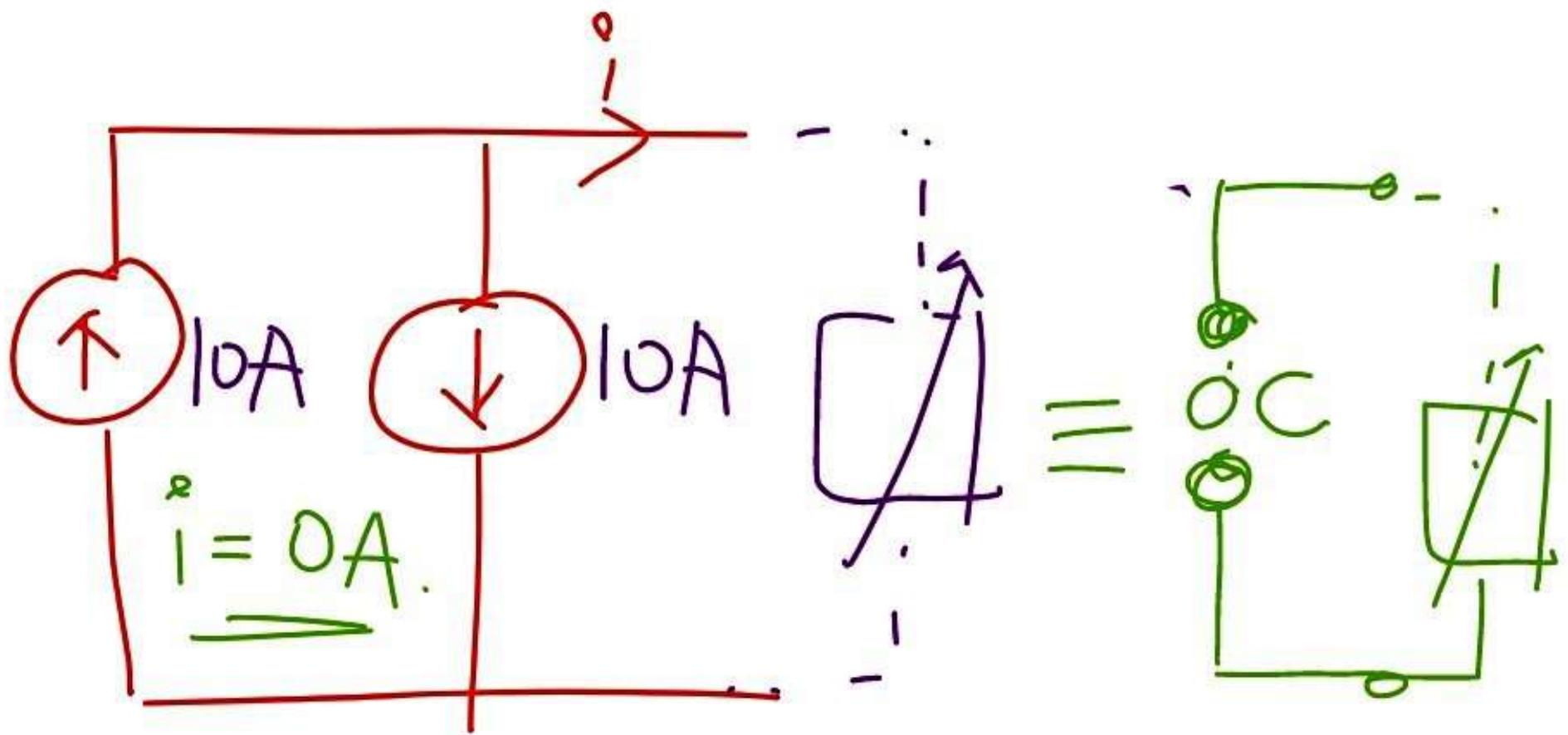

Source Transformation

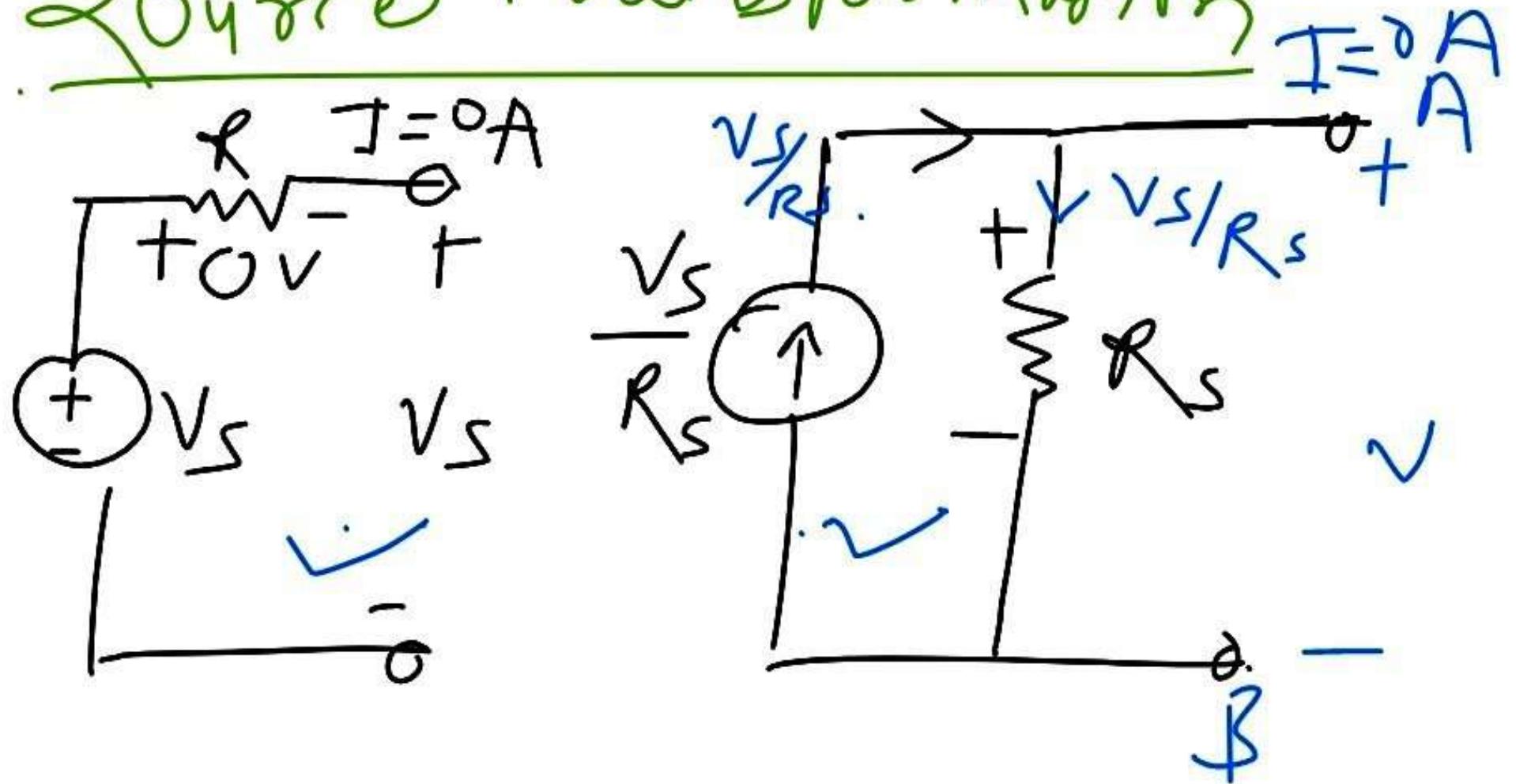

Power calculations by Tellegen's thm.

Defn → In an arbitrary n/w.
the algebraic sum of powers
at any given instant is zero

i.e. power delivered by
some element is equal to
power absorbed by remaining
element present in n/w.

$$\sum_{k=1}^b v_k i_k = 0$$

b = Total No. of branches.

→ When current enters at
-Ve terminal of an element
Then that element will
deliver power, otherwise
it will absorb the power.

Superposition Thm, - (Module 3)


(SPT)

Defn:- In a linear network with several independant sources, the response in particular branch when all the sources are acting simultaneously

is equal to linear sum of
individual responses calculated
by taking one independent
source at a time.




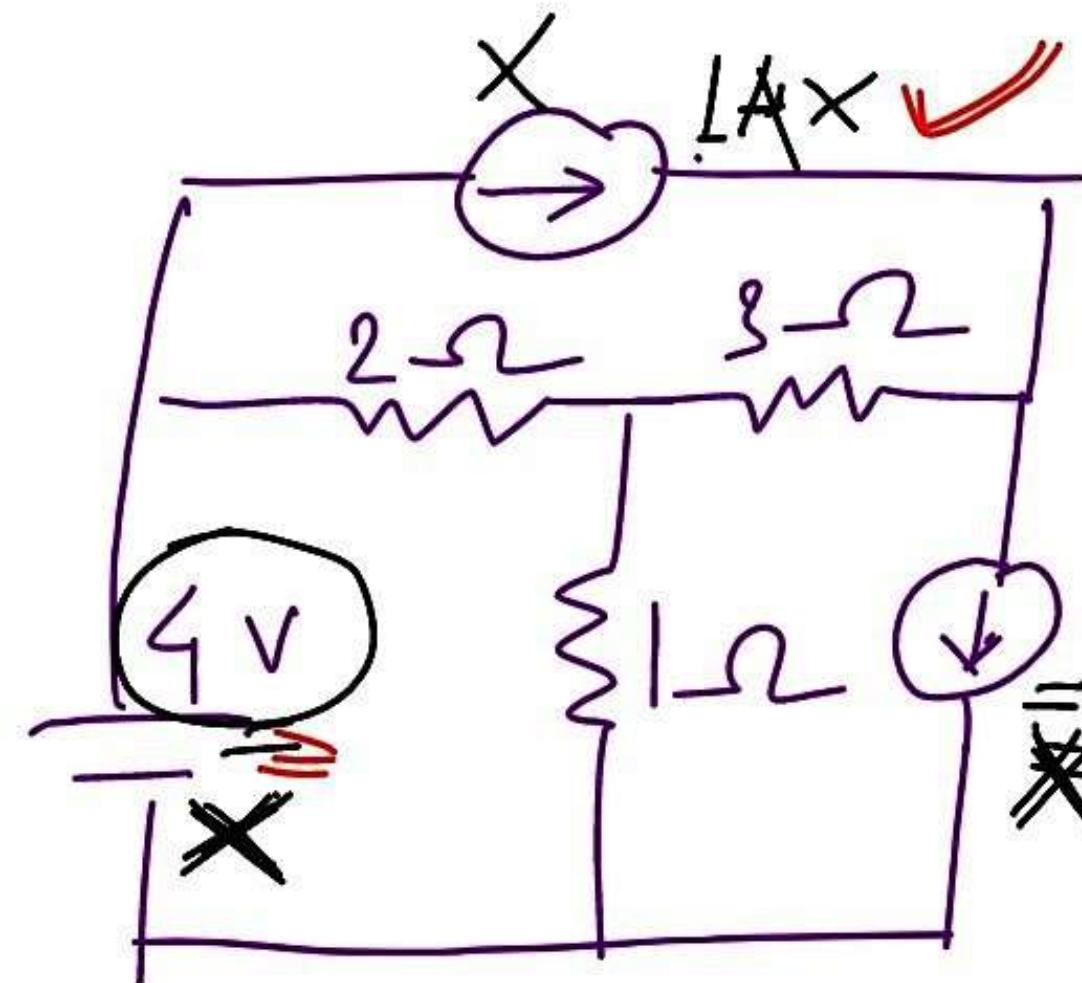is equal to linear sum of individual responses calculated by taking one independent source at a time.




find current
in 2Ω
~~3V~~ resistor
using SPT



Step 1 When 4V source is acting.

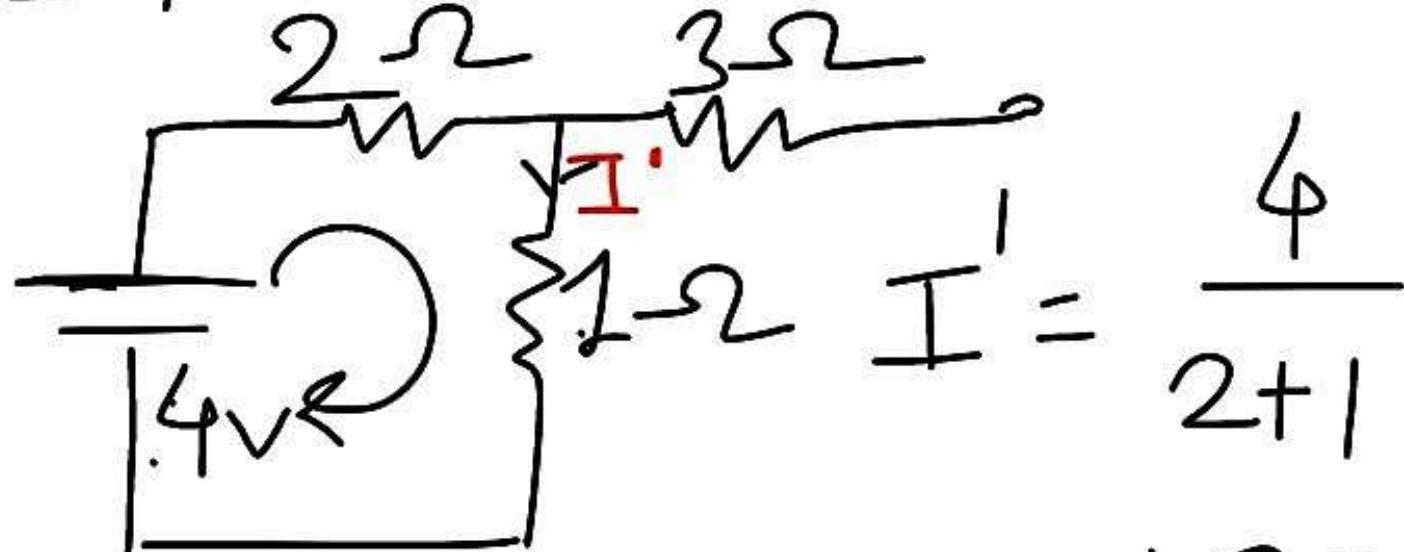
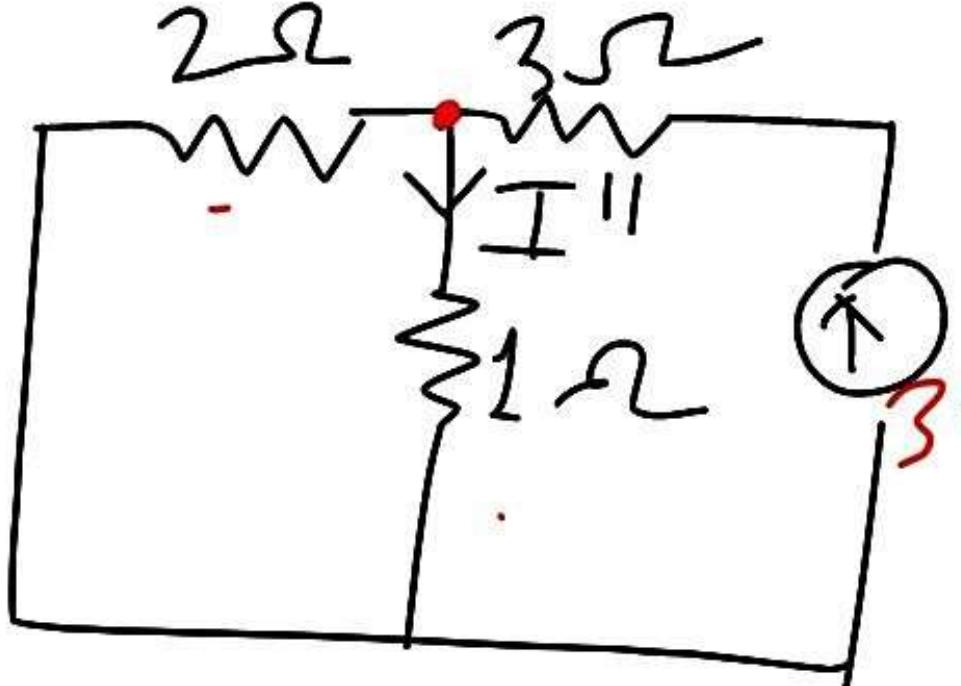
$$I = \frac{4}{2+1} = 1.33 \text{ Amp.}$$


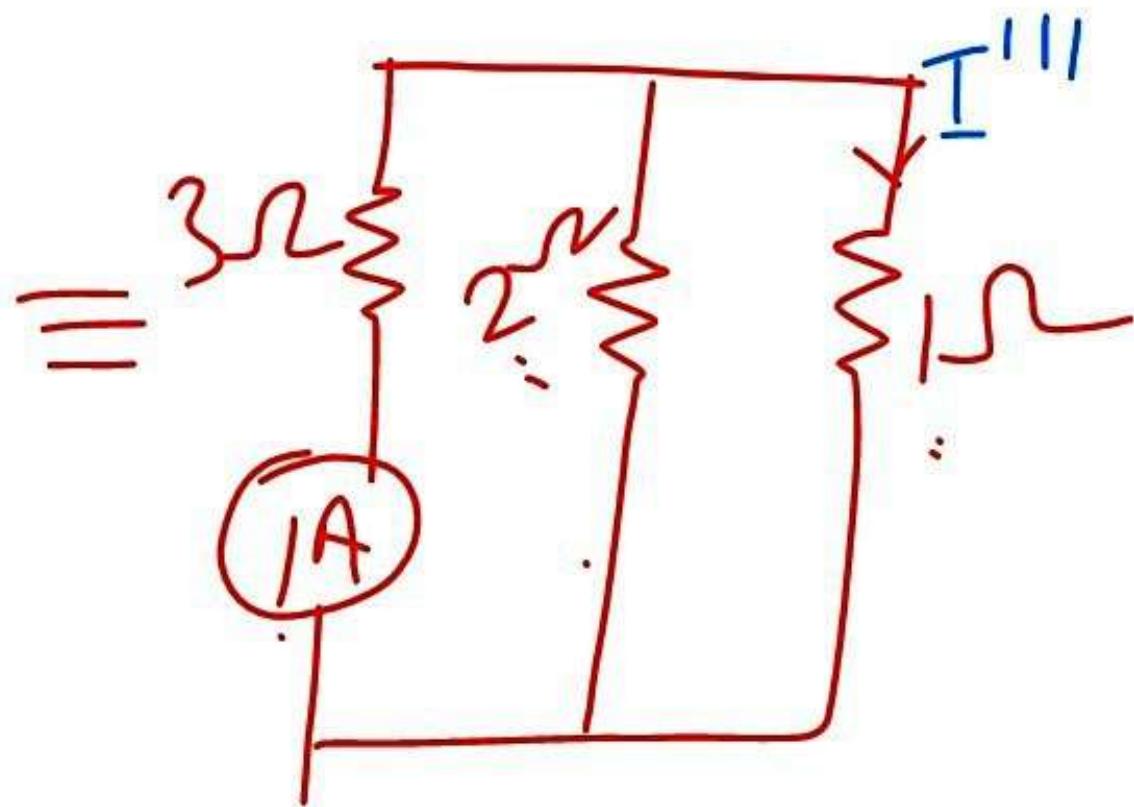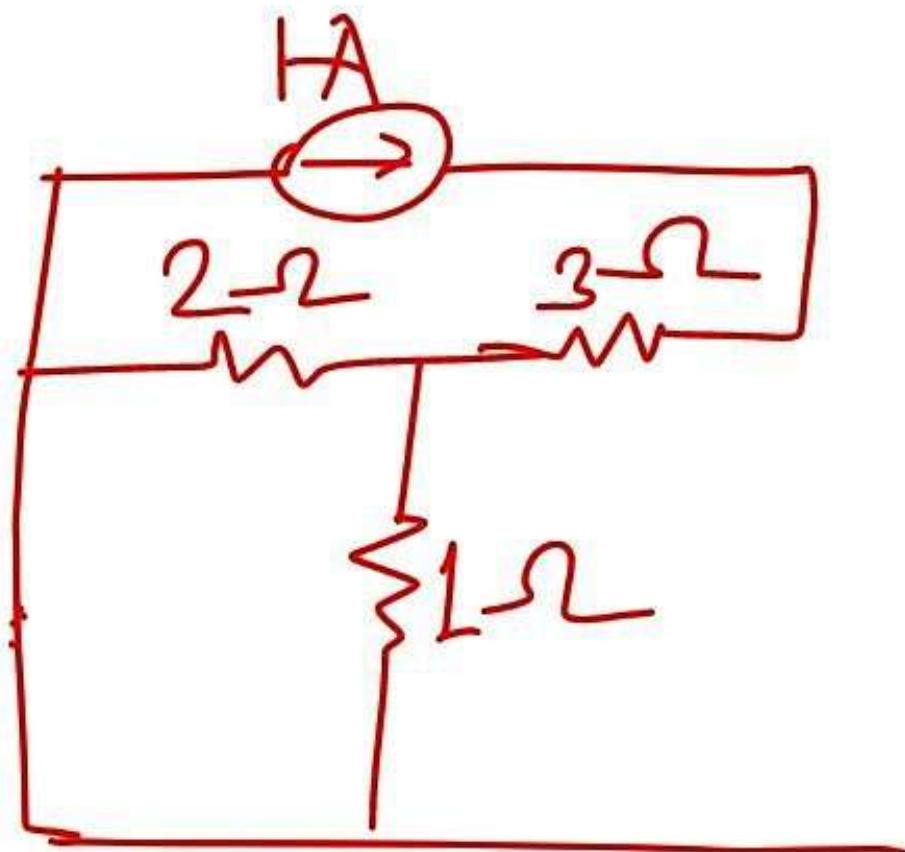
$$\begin{aligned}
 I''' &= \\
 &3 \times \frac{2}{1+2} \\
 &= 2 \text{ Amp.}
 \end{aligned}$$




By current division formula.

$$I''' = 1 \times \frac{2}{2+1} = 1 \times \frac{2}{3} = 0.66 \text{ Amp}$$


By superposition Thm.
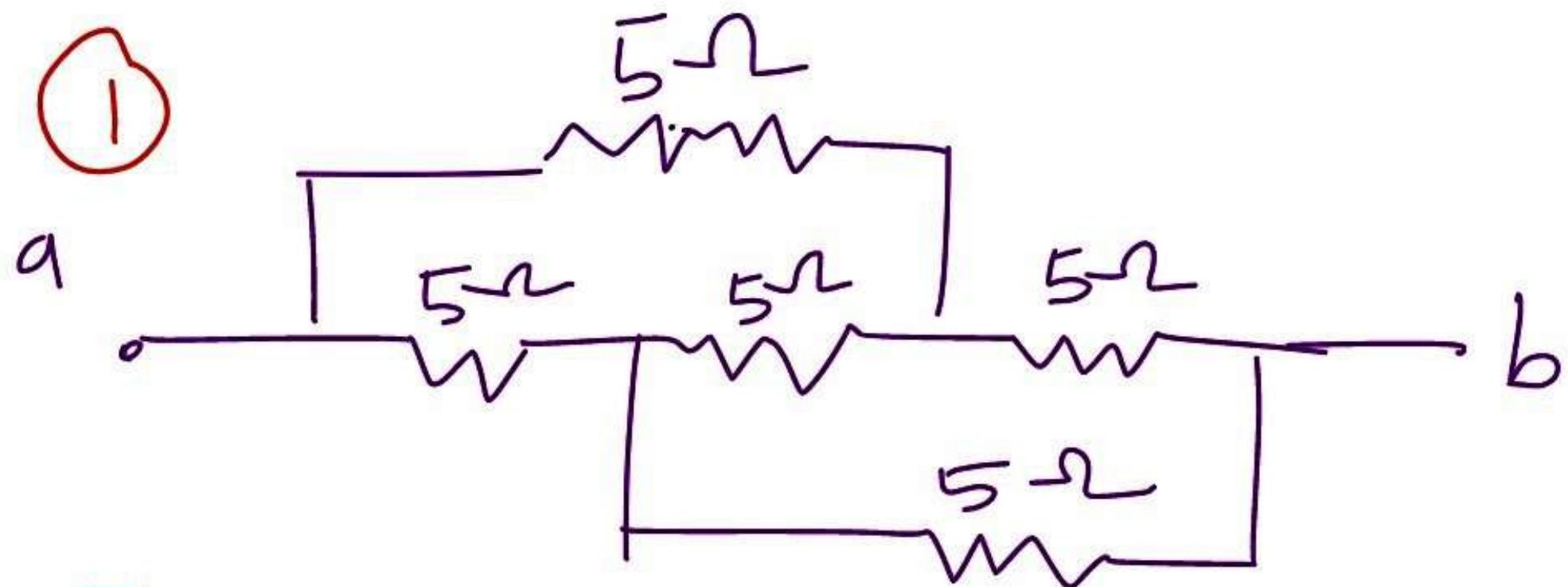
$$I = \underline{\underline{I' + I'' + I'''}} = 1.33 + 2 + 0.66 = 4 \text{ Amp. } \checkmark$$



Equivalent Resistance across
a & b.

② Determine C_1 , C_2 C_3

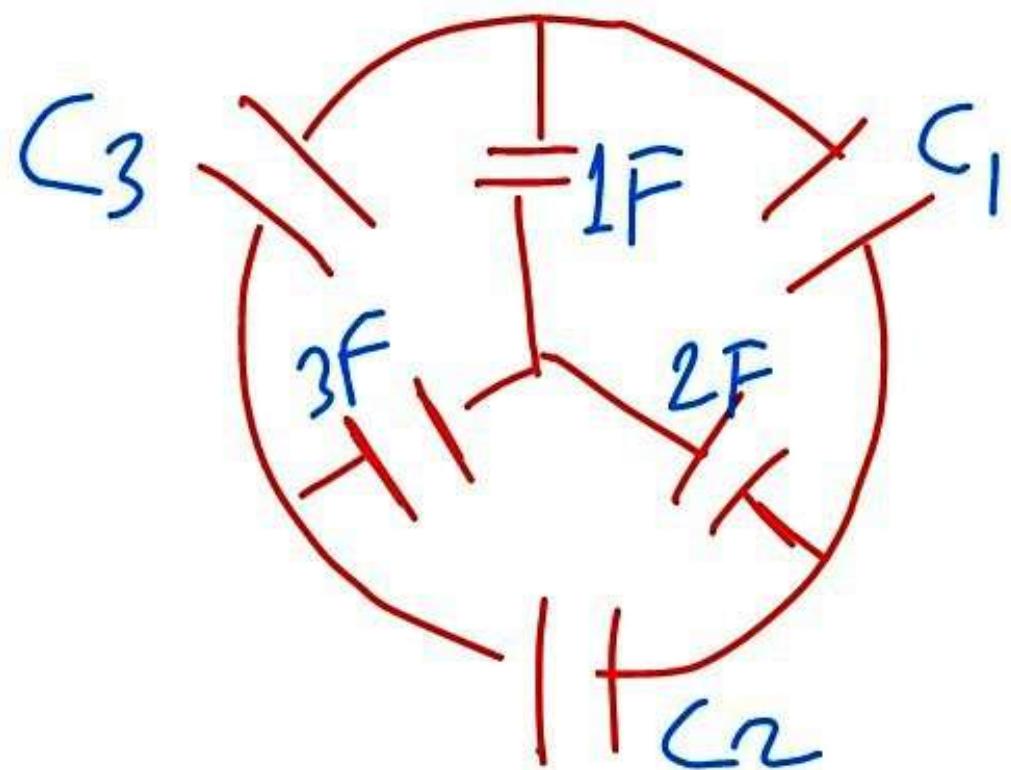

Types OF Elements :-

There are ten types of elements (ie. five pairs) as follows.

- 1) Linear & Non linear
- 2) Active and passive
- 3) Bilateral and unilateral
- 4) Distributed and lumped
- 5) Time invariant and Time varying.


Definitions :-

→ A two terminal element is said to be linear if for all time 't', its characteristics is a straight line through the origin, otherwise it is said to be nonlinear.

→ An element is said to be active if it delivers a net amount of energy to the outside world, otherwise it is said to be passive.

Active elements have the ability to supply energy while passive elements only receive the energy.

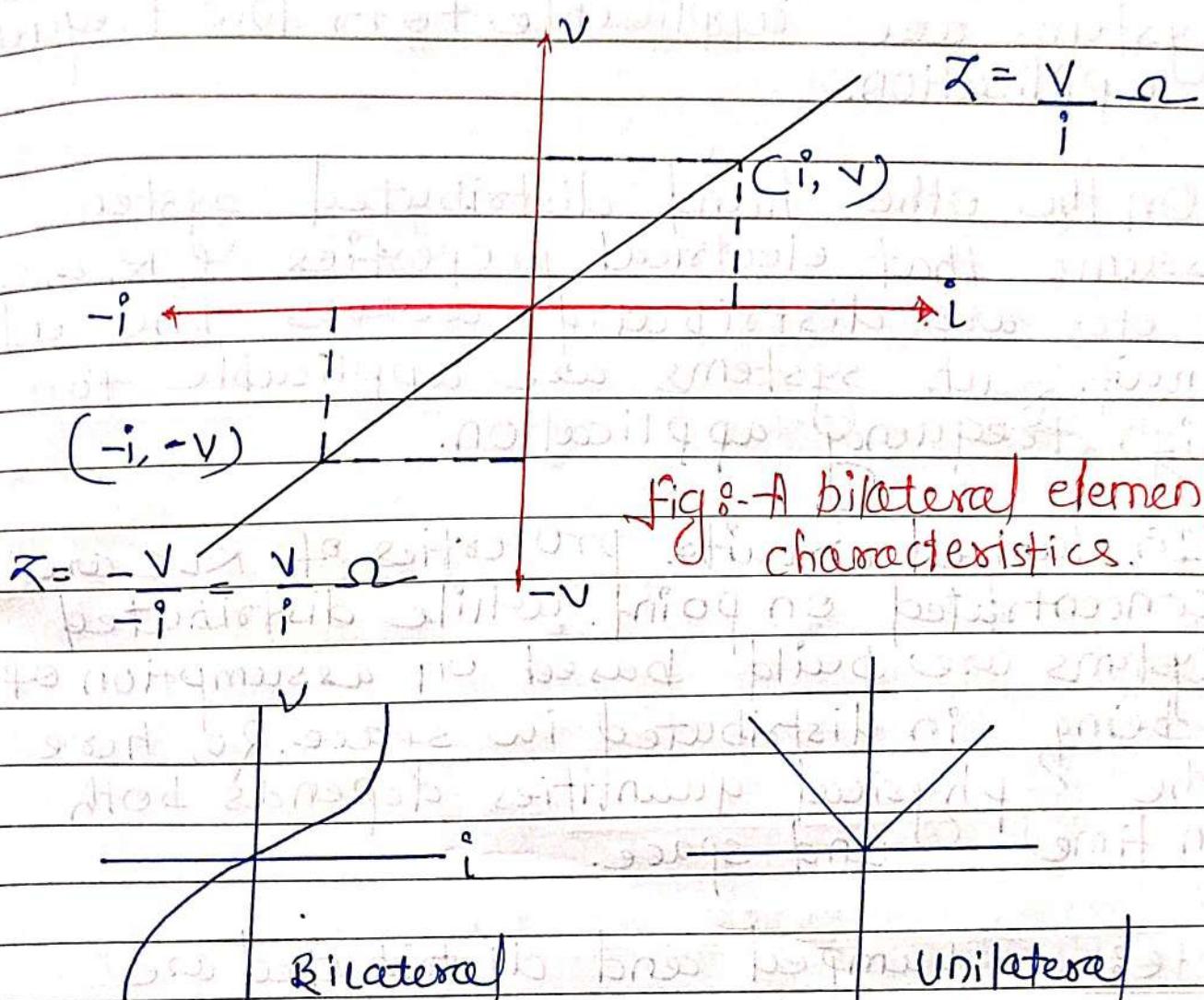→ An element is said to be bilateral if it offers same impedance for the different directions of same current flow. Otherwise it is said to be unilateral.



In other words, for a bilateral elements, if (i, v) is on the characteristic then $(-i, -v)$ must also be on the characteristic, then only same voltage for the different directions of same current flow and hence same impedance i.e. for a bilateral element, symmetry w.r.t. to origin exists.


→ Lumped systems are those systems in which electrical properties like R , L , C etc are assumed to be located on a small space of the circuit. These systems are applicable for low frequency application.

→ On the other hand distributed systems assume that electrical properties (R , L , C) etc. are distributed across the entire circuit. such systems are applicable for high frequency application.

→ In lumped circuits, properties of RLC are concentrated on point. while distributed systems are build based on assumption of being in distributed in space. So, here the physical quantities depends both on time and space.

Note:- Lumped and distributed are not properties of system itself. These are related to the size of the system compared to the wavelength of applied voltage & current.

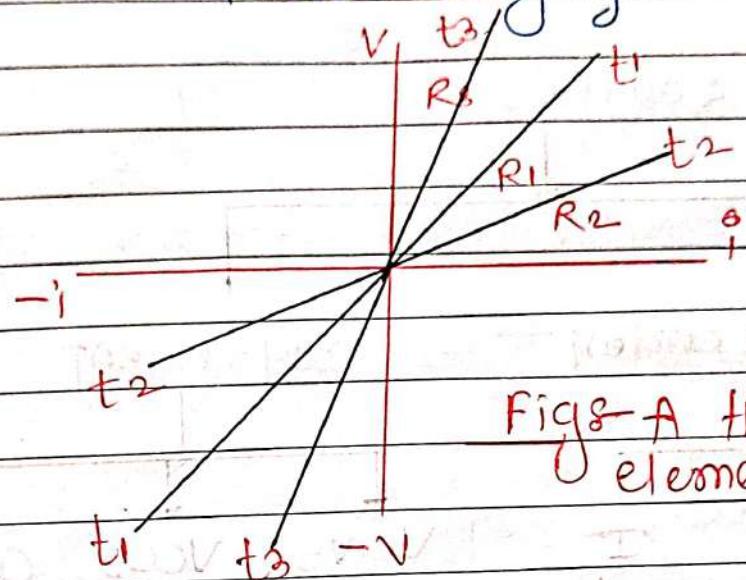→ An element is said to be time invariant if for all time 't', its characteristics do not change with time, otherwise it is said to be time varying.



Figs A time varying
element characteristics.



Observation :-

The above characteristics also present a linear, passive and bilateral element.

Note 8- The resistors, inductors and capacitors are said to be passive if and only if $R \geq 0$, $L \geq 0$ and $C \geq 0$ (i.e. Nonnegative slope of the V - i characteristics), otherwise they are said to be active i.e. $R < 0$, $L < 0$ & $C < 0$ (i.e. Negative slope of the V - i characteristic).

Sources

Sources are classified as shown below.

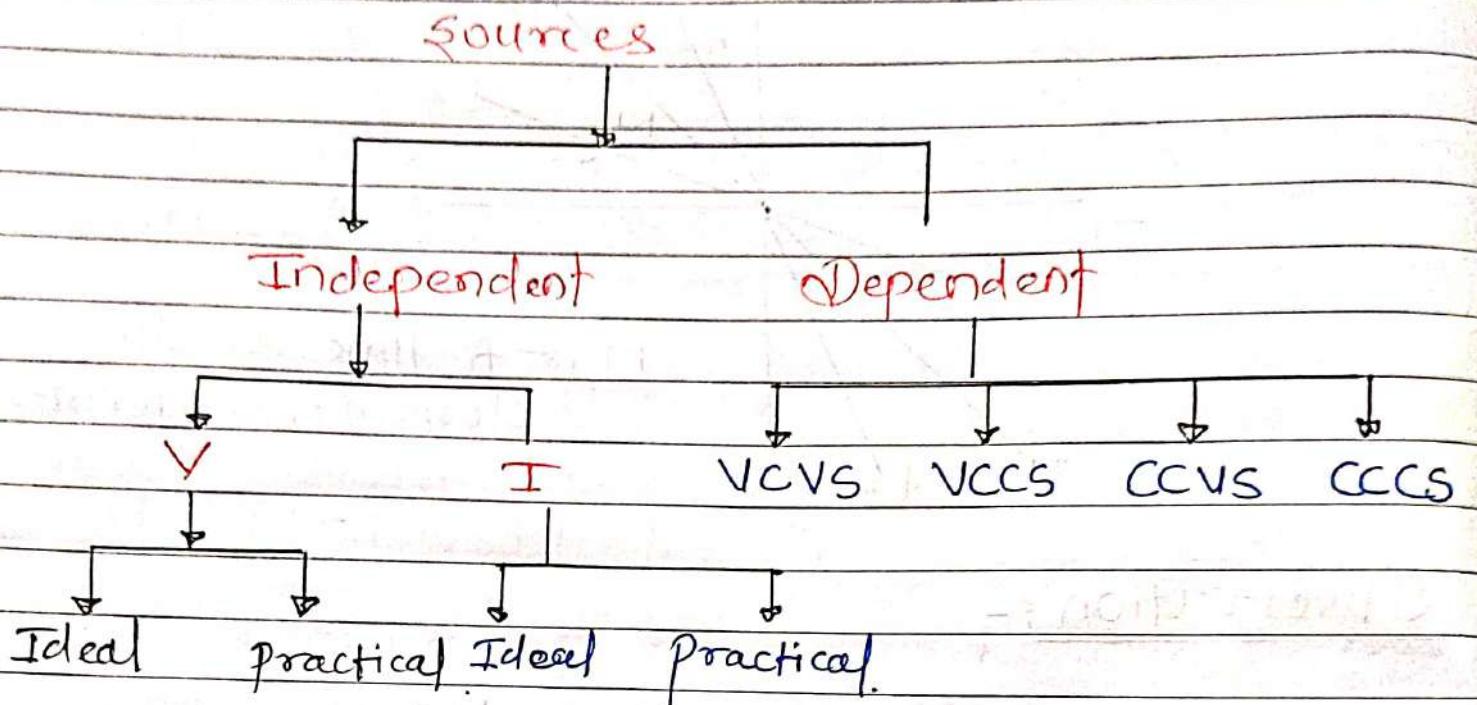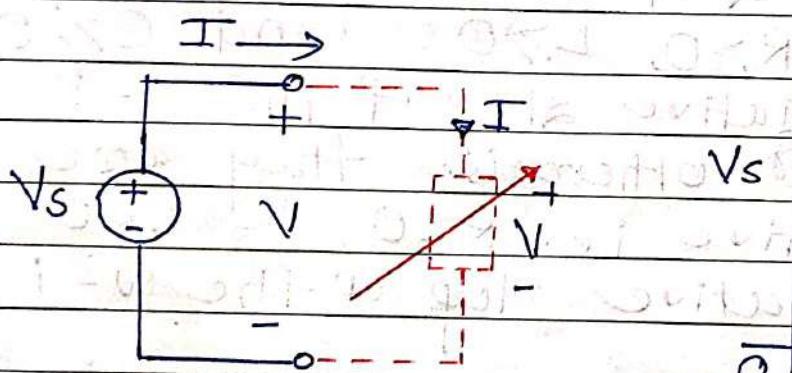① Independent Sources① Ideal Voltage Source

Notes:-


- Energy delivery i.e. current delivery in any source is always from the positive terminal i.e. current flows from negative to positive terminals.
- for the flow of current (i.e. free electron motion) always closed path is necessary i.e. $V = V_s$ for all I .

Property :-

- In an ideal voltage source, load voltage is independent of the load current drawn.

Note :- Inherently all the sources are nonlinear in nature, since their voltage and current relation is non-linear. They are basically active and unilateral elements. DC means Time invariant and AC means time varying elements.

② Practical Voltage Source

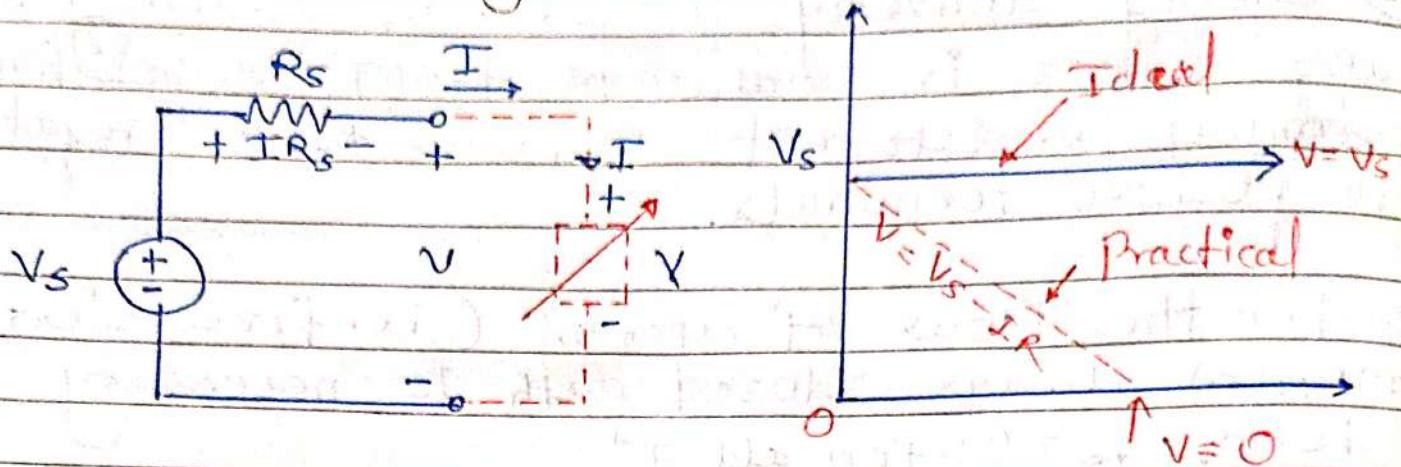

$$\text{By KVL} \Rightarrow V_s - I R_s - V = 0$$


$$\Rightarrow V = V_s - I R_s.$$

Properties :- No law of physics holds good.

In a practical voltage source, load voltage is a function of load current drawn.


Observations :-

When $I = 0$ Ampere, then $V = V_s$.

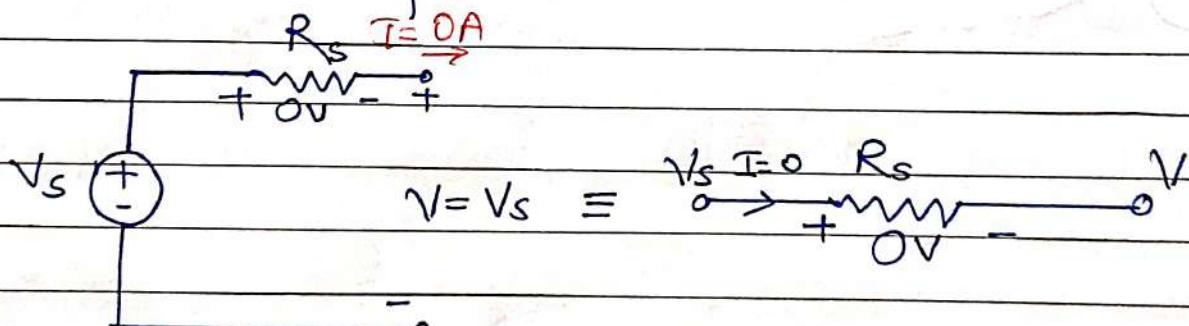

Conclusion :- When current through any passive element is zero, then the two end voltages are equal and vice versa.


Ideal Current Source :-

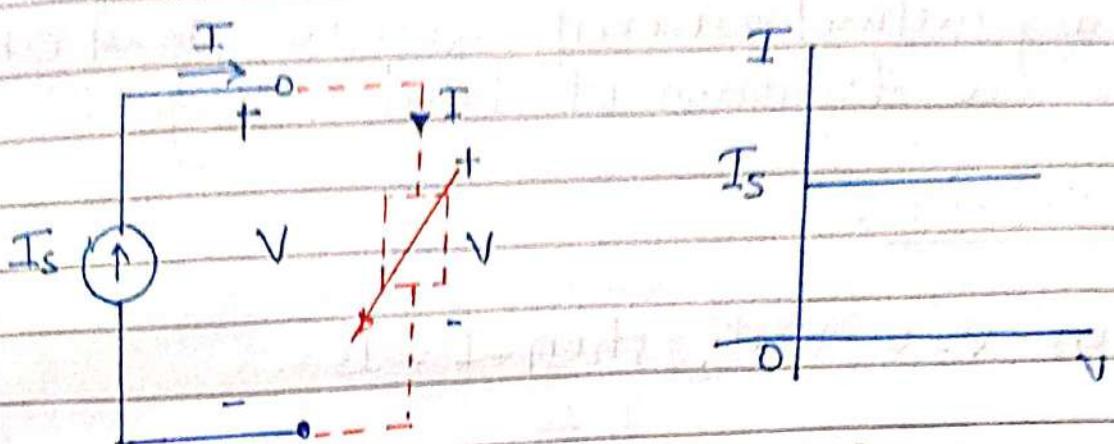

i.e. $I = I_s$ for all V .

Property :- In an ideal current source, load current is independent of load voltage.

Practical Current Sources :-

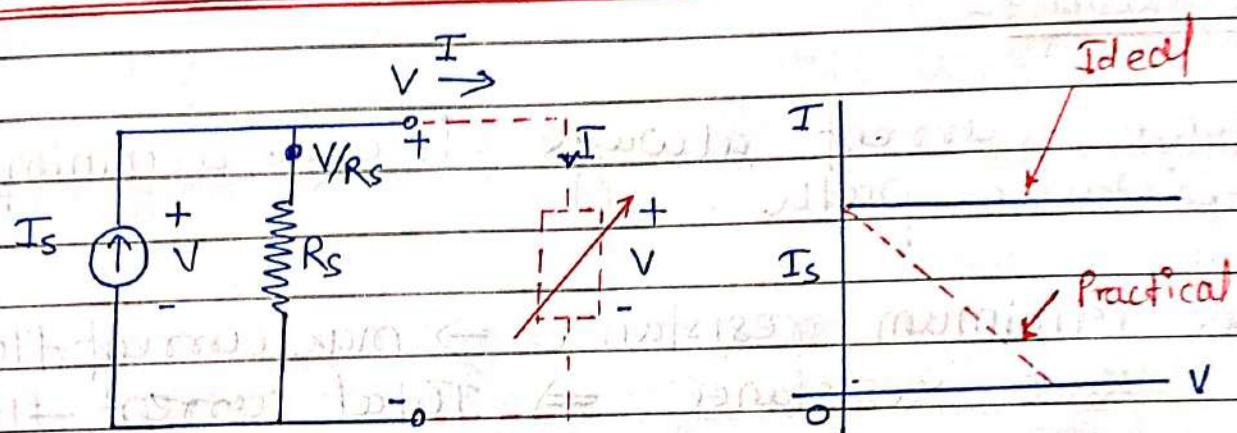

$$\text{By KCL} \Rightarrow -I_s + \frac{V}{R_s} + I = 0$$

$$\Rightarrow I = I_s - \frac{V}{R_s}$$


Property :-

In a practical current source, load current is a function of load voltage.

Observation :-

When $V=0$ volt, then $I=I_s$

$$I=I_s$$

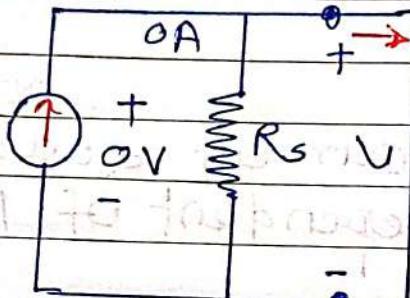

$$\Rightarrow V=0 \text{ volt.}$$

Conclusion :-


Hence, current always chooses a minimum resistance path.

i.e. Minimum resistance \Rightarrow max current flows
Zero Resistance \Rightarrow Total current flows.

$$V = I_s R_s + I_s r_s + I_s r_o$$

$$V = I_s R_s + E_o$$

Dependent OR controlled Sources :

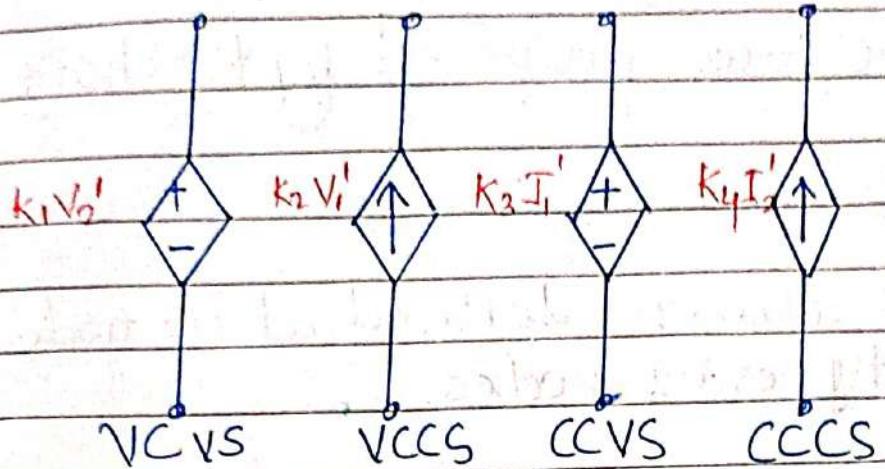

Linear controlled sources (with respect to the controlled variable, not w.r.t. to the voltage & current relation).

→ With respect to controlled variable only, the dependent source are said to be linear, active & bilateral. The presence of these elements makes the network a linear, an active and a bilateral.

→ Controlled sources are said to be sources i.e. active elements in the presence of least one independent source, then only controlled variables are non zero and hence their magnitudes are non zero.

Kirchoff's Laws :-

There are two laws proposed by Kirchoff's

KCL and KVL.

① KCL :- It is always defined at a node.

There are two types of nodes.

② Simple Node :-


It is an interconnection of only two branches.

③ Principle Node :-

It is an interconnection of at least three branches.

Definition :-

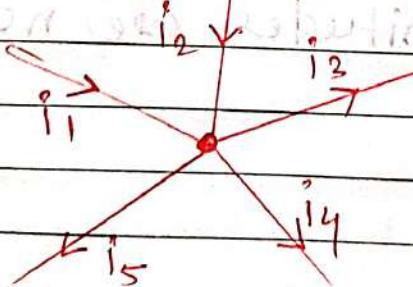"In a lumped electric circuit for any of its nodes and at any time 't', the algebraic sum of branch currents leaving the node is zero!"



By KCL $\rightarrow \sum$ currents = 0

$$\Rightarrow -i_1 - i_2 + i_3 + i_4 + i_5 = 0$$

$$i_L + i_2 = i_3 + i_4 + i_5$$

i.e. Sum of entering currents is equal to sum of leaving currents.

Since

$$i = \frac{dq}{dt} = \frac{dq_1}{dt} + \frac{dq_2}{dt} = \frac{dq_3}{dt} + \frac{dq_4}{dt} + \frac{dq_5}{dt}$$

At a given time t° , $\frac{d}{dt}$ is same for all branches.

$$\Rightarrow q_1 + q_2 = q_3 + q_4 + q_5$$


i.e. sum of entering charges is equal to sum of leaving charges.

Properties :-

→ KCL applies to any lumped electric circuit, it does not matter whether the elements are linear, non-linear,

active, passive, time varying, time invariant etc. i.e. KCL is independent of the nature of the elements connected to the node.

Ex.

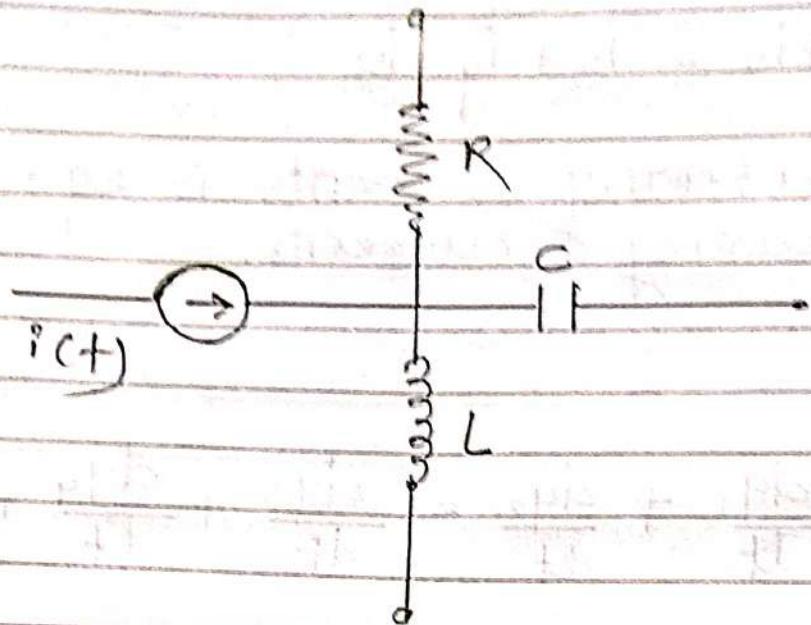


→ Here R , L , C are linear, passive, bilateral time invariant elements and $i(t)$ is a non linear, active, unilateral, time varying element.

→ Since there is no accumulation of charge at any node, KCL expresses conservation of charge at each and every node in a lumped electric circuit.

KVL :-

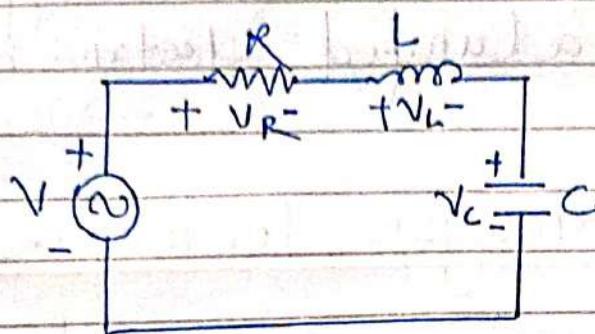"In a lumped electric circuit, for any of its loops and at any time t the algebraic sum of branch voltages around the loop is zero."



$$Z_R = R \Omega$$

$$Z_L = j\omega L \Omega$$

$$Z_C = \frac{1}{j\omega C} \Omega$$

By KVL $\Rightarrow \sum \text{Branch voltages} = 0$

$$V - V_R - V_L - V_C = 0$$

$$V = V_R + V_L + V_C$$

Since $V = \frac{W}{q}$ and $i = dq/dt$ in series current is same and hence charge flow is same through all the elements.

$$\frac{W}{q} = \frac{WR}{q} + \frac{WL}{q} + \frac{WC}{q}$$

$$W = WR + WL + WC$$

Properties :-

- KVL is independent of nature of the elements (linear, non-linear, active, passive etc.) present in a loop.
- KVL expresses conservation of energy in every loop of a lumped electric circuit.

Nodal and Mesh Analysis Techniques -


- KCL + Ohm's law = Nodal Analysis
- KVL + Ohm's law = Mesh Analysis.
- The above techniques are network solving procedures, valid only for lumped electric circuits (where KCL & KVL are valid) and that too at a constant temperatures (where Ohm's law is valid).
- Nodal & Mesh procedures are independent of each other, since KCL & KVL are independent of each other.

→ Ohm's law is a function of nature of the elements (eight different forms of Ohm's law), whereas Kirchoff's laws are independent of nature of the elements.

→ Ohm's law is defined across an element, that element can be lumped (R, L, C) or distributed ($J = \sigma E$), whereas Kirchoff's laws are defined to only for lumped electric circuits (one is at a node and another is in a loop or mesh).

→ Ohm's law is not applicable for active elements like sources (Generators), since the voltage & current relation is non linear. It is applicable only for linear passive elements like R, L, C where the voltage and current relation is linear.

Nodal Analysis :-

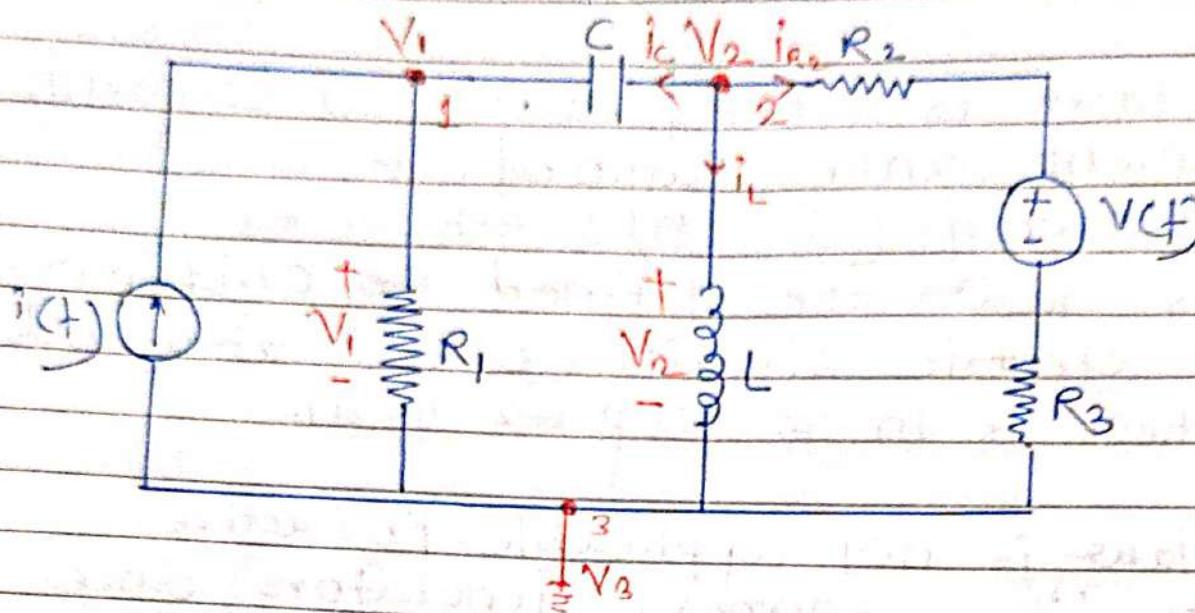

Steps :-


- ① Identify number of nodes.
- ② Assign node voltages with respect to the ground node, whose voltage is always equal to zero.
- ③ By using KCL first and Ohm's law next write the nodal equations.

Node 2 : $\begin{bmatrix} V_2 > V_1 \\ V_2 > 0 \\ V_2 > V(t) \end{bmatrix}$

$$i_c + i_L + i_R = 0 \quad (\text{By KCL})$$

$$C \frac{d}{dt}(V_2 - V_1) + \frac{1}{L} \int_{-\infty}^t V_2 dt + \frac{V_2 - V(t)}{R_2 + R_3} = 0$$

(By Ohm's law)

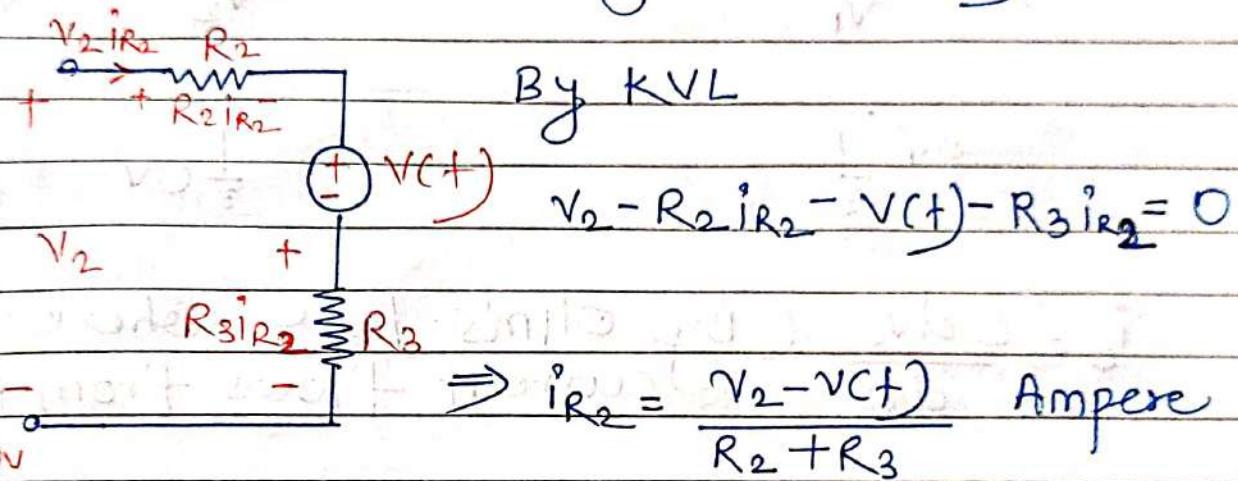

$$i_C = C \frac{dV_C}{dt} \quad (\text{By Ohm's law, where current flows from } + \text{ to } -)$$


$$V_1 + V_C - V_2 = 0$$

$$V_C = V_2 - V_1 \Rightarrow i_C = C \frac{d}{dt}(V_2 - V_1)$$

Node 1: $V_1 > 0$
 $V_1 > V_2$

$$\text{Nodal} \Rightarrow -i(t) + \frac{V_1}{R_1} + C \frac{d}{dt}(V_1 - V_2) = 0$$

(By KCL and Ohm's law simultaneously)

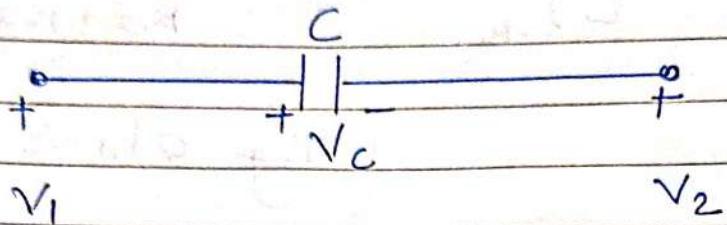

$$i_c = C \frac{dV_c}{dt}$$

(By Ohm's law, where current flows from + to -)

$$\text{By KVL} \Rightarrow V_1 - V_c - V_2 = 0$$


$$V_c = V_1 - V_2$$

$$\text{So } i_c = C \frac{d}{dt}(V_1 - V_2)$$

(most useful form)

$$(V_1 - V_2) = i_c \cdot C \cdot dt \Rightarrow V_1 - V_2 = i_c \cdot C \cdot t + \text{const}$$


Mesh Analysis

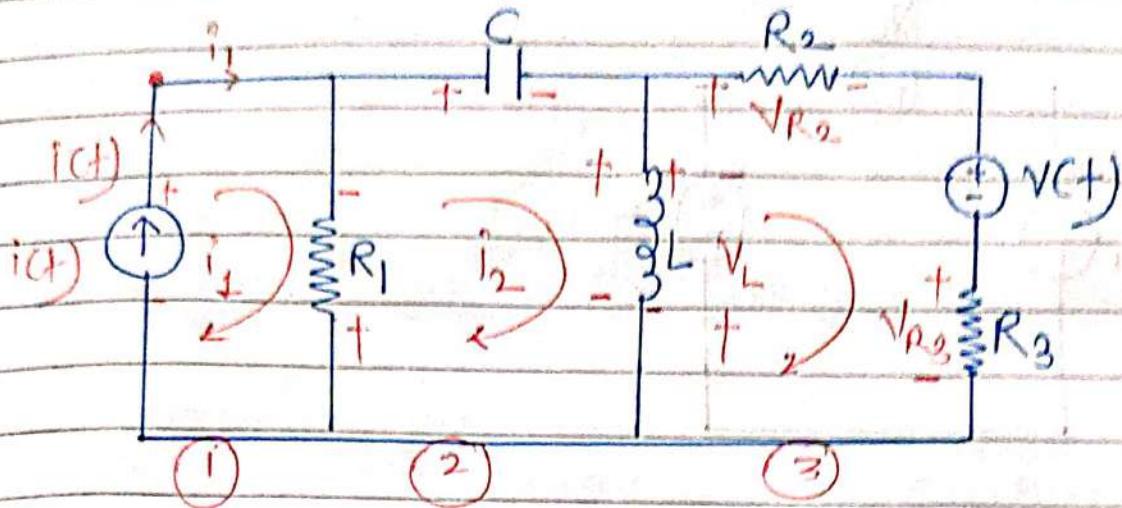

Steps :-

- ① Identify number of Meshes.
- ② Assign mesh currents in the clockwise direction.
- ③ By using KVL first and Ohm's Law next write the mesh equations.

Mesh ① :- $i_1 > i_2$
 $i_1 > i_3$

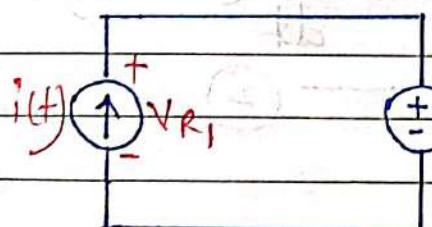

$$VR_1 = R_1(i_1 - i_2)$$

$$\text{By KVL} \Rightarrow VR_1 - VR_1 = 0$$


$$0 = 0$$

So, $i_1 = i(t) \rightarrow (1)$ (As both currents are in the same direction)

$$\text{By KCL} \Rightarrow -i(t) + i_1 = 0 \Rightarrow i_1 = i(t) - 1$$

Mesh (2) :- $i_2 > i_3$

$$i_2 > i_1$$

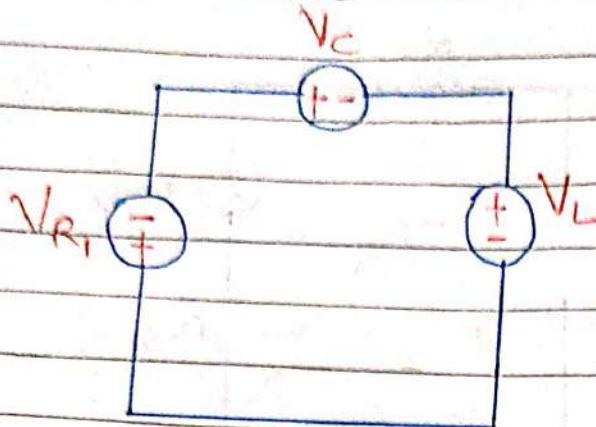

$$V_c = \frac{1}{C} \int_{-\infty}^t i_2 dt$$

$$V_L = L \frac{d}{dt} (i_2 - i_3)$$

$$V_{R1} = R_1 (i_2 - i_1)$$

$$-V_{R1} - V_c - V_L = 0$$

(By KVL)


$$-R_1 (i_2 - i_1) - \frac{1}{C} \int_{-\infty}^t i_2 dt - L \frac{d}{dt} (i_2 - i_3) = 0$$

(By Ohm's law)

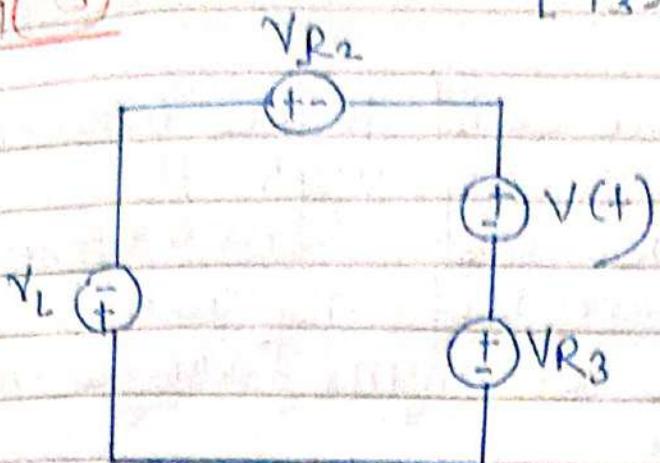--- (2)

Mesh 3

$$[i_3 > i_2 \text{ } \& \text{ } i_2 > i_1]$$



Note :- In a single branch, the branch current is equal to mesh current and in a common branch, the branch current is equal to the difference of mesh currents.

$$V_{R_2} = R_2 i_3$$

$$V_{R_3} = R_3 i_3$$

$$V_L = L \frac{d}{dt} (i_3 - i_2)$$


$$-V_L - V_{R_2} - V(t) - V_{R_3} = 0 \quad (\text{By KVL})$$

$$-L \frac{d}{dt} (i_3 - i_2) - R_2 i_3 - V(t) - R_3 i_3 = 0$$

(By Ohm's law) — ③

Equivalent Circuits w.r.t. to Passive R, L, C

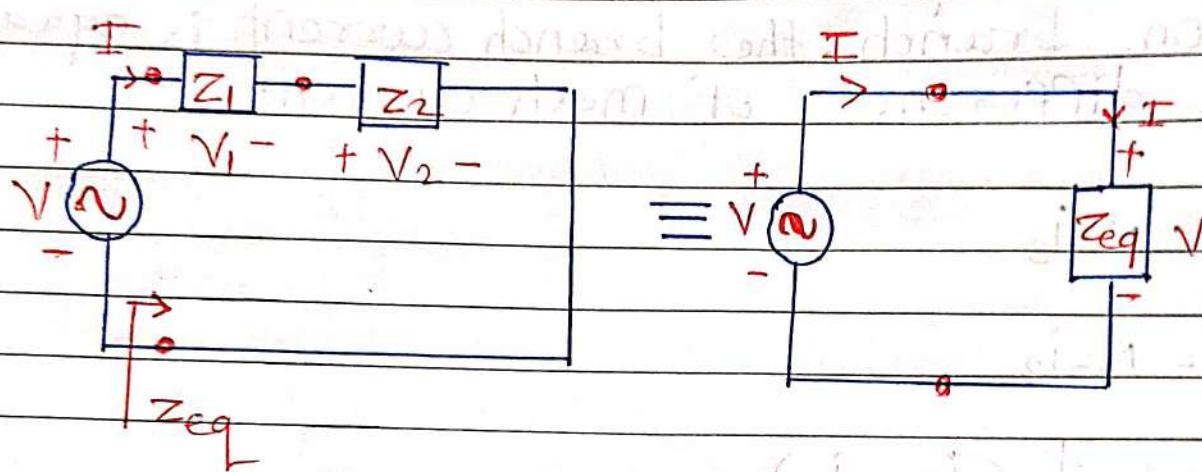- Two elements are said to be in series only when currents through the elements are same and two elements are said to be in parallel only when voltages across the elements are same.
- Impedances in series and admittances in parallel we can add.



$$Z = Z_R = R \Omega$$

$$Z_L = j\omega L \Omega$$

$$Z_C = \frac{1}{j\omega C} \Omega$$

$$Z_{eq} = Z_1 + Z_2$$

$$R : R_{eq} = R_1 + R_2$$

$$L : L_{eq} = L_1 + L_2$$

$$C : \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\text{If } C_1 = C_2 = C$$

$$C_{eq} = \frac{C}{2}$$

Voltage Division Principle :-

$$V = Z_{eq} \cdot I \quad (\text{By Ohm's law})$$

$$I = \frac{V}{Z_{eq}} = \frac{V}{Z_1 + Z_2}$$

$$V_1 = Z_1 I \quad (\text{By Ohm's law})$$

$$V_1 = \frac{V \cdot Z_1}{Z_1 + Z_2}$$

$$V_2 = Z_2 \cdot I \quad (\text{By Ohm's law})$$

$$V_2 = \frac{V \cdot Z_2}{Z_1 + Z_2}$$


Check :-

$$\text{By KVL} \Rightarrow V - V_1 - V_2 = 0$$
$$V = V_1 + V_2$$

$$R : \quad V_1 = \frac{V \cdot R_1}{R_1 + R_2}; \quad V_2 = \frac{V \cdot R_2}{R_1 + R_2}$$

$$L : \quad V_1 = \frac{V L_1}{L_1 + L_2}; \quad V_2 = \frac{V L_2}{L_1 + L_2}$$
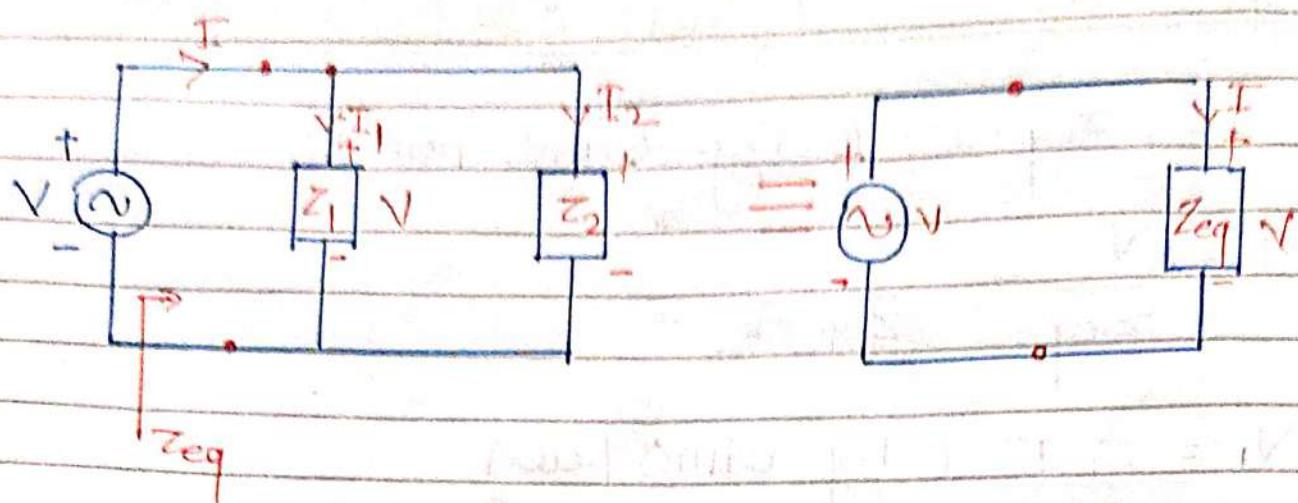
$$C : \quad V_1 = \frac{V C_1}{C_1 + C_2}; \quad V_2 = \frac{V C_2}{C_1 + C_2}$$



$$Y_{eq} = Y_1 + Y_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} \Rightarrow Z_{eq} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$

$$R : \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} ; R_1 = R_2 = R$$

$$R_{eq} = \frac{R}{2}$$

$$L : \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$C : C_{eq} = C_1 + C_2$$

Current Division Principle

$$V = Z_{eq} \cdot I \quad (\text{By Ohm's law})$$

$$\Rightarrow V = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} \cdot I$$

$$I_1 = \frac{V}{Z_1} \quad (\text{By Ohm's law})$$

$$I_1 = \frac{I \cdot Z_2}{Z_1 + Z_2}$$

$$I_2 = \frac{V}{Z_2} \quad (\text{By Ohm's law})$$

$$I_2 = \frac{I \cdot Z_1}{Z_1 + Z_2}$$

Check :- By KCL $\Rightarrow -I + I_1 + I_2 = 0$


$$\Rightarrow I_1 + I_2 = I$$

$$R: I_1 = \frac{IR_2}{R_1 + R_2} ; I_2 = \frac{IR_1}{R_1 + R_2}$$

$$L: I_1 = \frac{F \cdot L_2}{L_1 + L_2} ; I_2 = \frac{FL_1}{L_1 + L_2}$$

$$C: I_1 = \frac{F \cdot C_1}{C_1 + C_2} ; I_2 = \frac{F \cdot C_2}{C_1 + C_2}$$

Star (Y) - Delta (Δ) Transformation

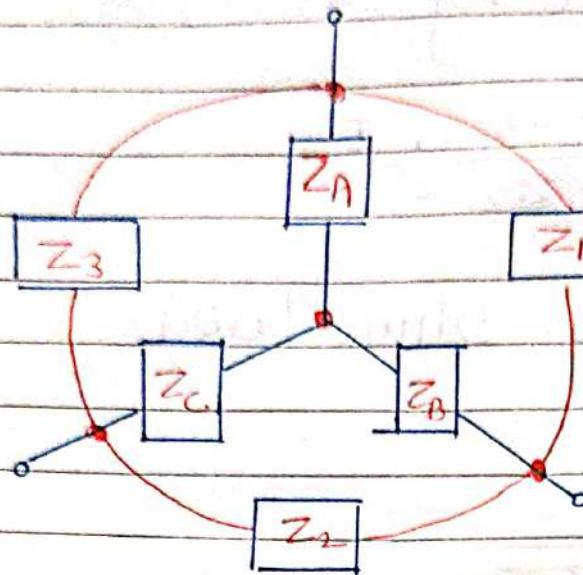

Let Δ -Network be given i.e. $Z_1, Z_2 \text{ & } Z_3$ are known,

$$Z_A = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3} = \left(\frac{\text{Product}}{\text{Total}} \right)$$

$$Z_B = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_C = \frac{Z_2 \cdot Z_3}{Z_1 + Z_2 + Z_3}$$

Observation

IP $Z_1 = Z_2 = Z_3 = Z$, then $Z_A = Z_B = Z_C = Z/3$

So, for the balanced case, Δ to Y transformation will reduce the impedance by 3 times.

Let Y-Network be given i.e. z_A , z_B and z_C
are known

$$z_1 = z_A + z_B + \left(\frac{z_A \cdot z_B}{z_C} \right)$$

= sum $\left(\frac{\text{Their Product}}{\text{Remaining}} \right)$

$$z_2 = z_B + z_C + \left(\frac{z_B \cdot z_C}{z_A} \right)$$


$$z_3 = z_C + z_A + \left(\frac{z_C \cdot z_A}{z_B} \right)$$

Observation:

If $z_A = z_B = z_C = z$ then $z_1 = z_2 = z_3 = 3z$


So for the balanced case, Y to Δ transformation will increase the impedance by 3 times.

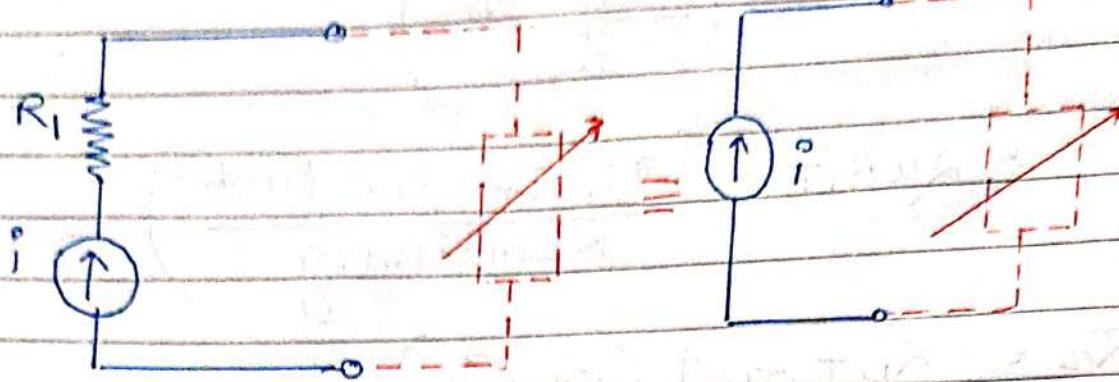Equivalent Circuits with respect to Active Sources :-



Here $R_1 \neq \infty$
since violation of KCL

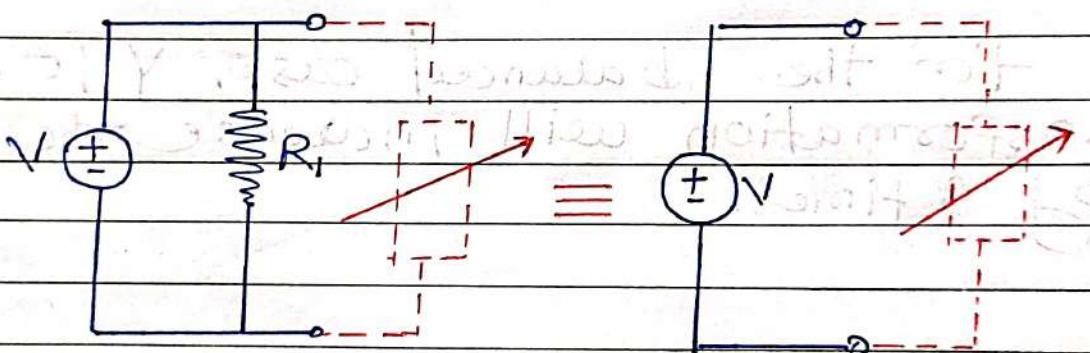
So, a resistor in series with an ideal current source can be neglected in the analysis i.e. the load current is independent of R_1 value. We cannot omit this resistor in power calculations since $i^2 R_1 \neq 0$




Here $R_1 \neq 0$, since
violation of KVL

so, a resistor in parallel with an ideal voltage source can be neglected in the analysis i.e. the load voltage is independent of R_L value. We cannot omit this resistor in power calculations

$$\text{since } \frac{V^2}{R_L} \neq 0$$

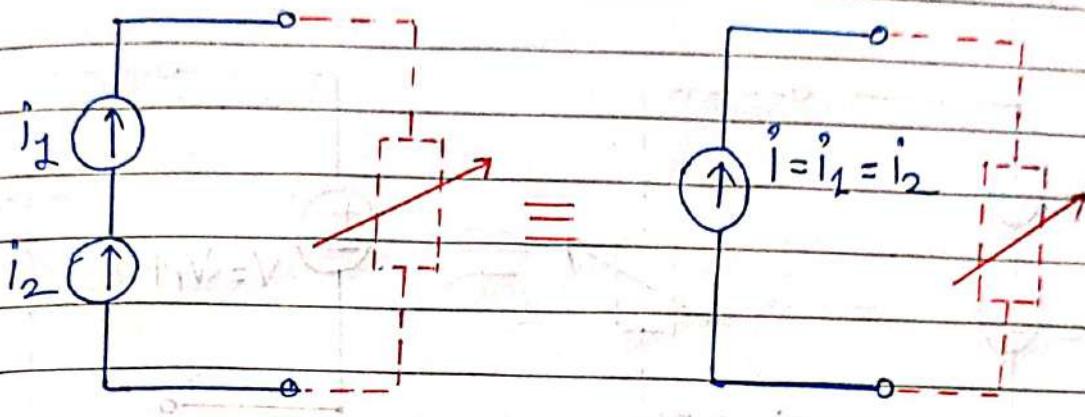

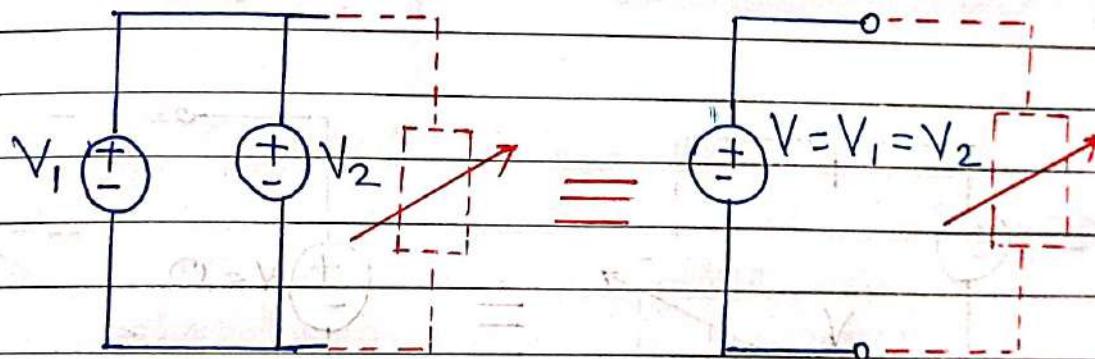
$$\text{By KCL} \Rightarrow -i_2 + i_1 = 0 \Rightarrow i_1 = i_2$$





$$\text{By KVL} \Rightarrow V_1 - V_2 = 0$$

$$V_1 = V_2$$

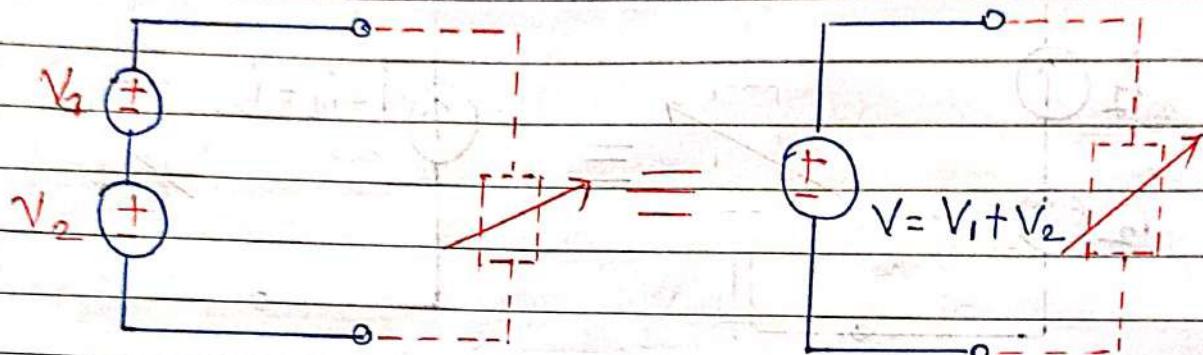So, two ideal current sources are connected in series only when their magnitudes are equal, otherwise violation of KCL, which results in the instability of the system and hence, physical connection is not possible i.e. the circuit does not exist. Similarly, for parallel connection of two ideal voltage sources, violation of KVL.



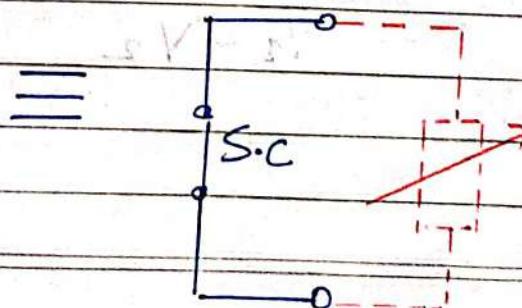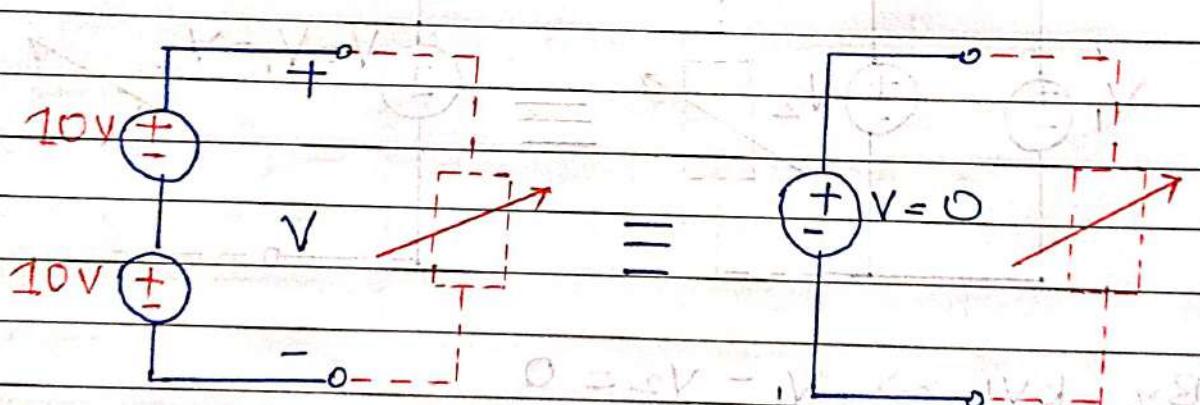
$$\text{By KVL} \Rightarrow V_2 + V_1 - V = 0 \Rightarrow V = V_1 + V_2$$




By KVL $\Rightarrow 10 - 10 - v = 0$
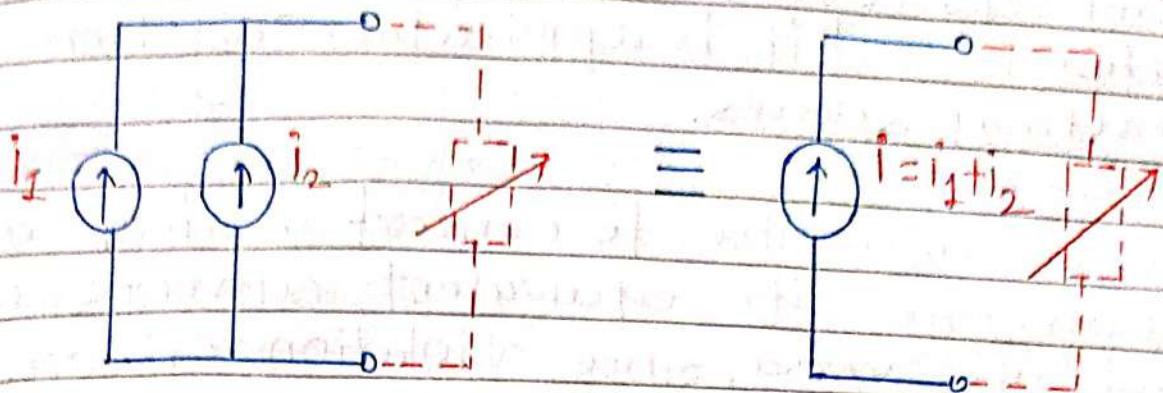
$$\Rightarrow v = 0 \Rightarrow \text{s.c.}$$



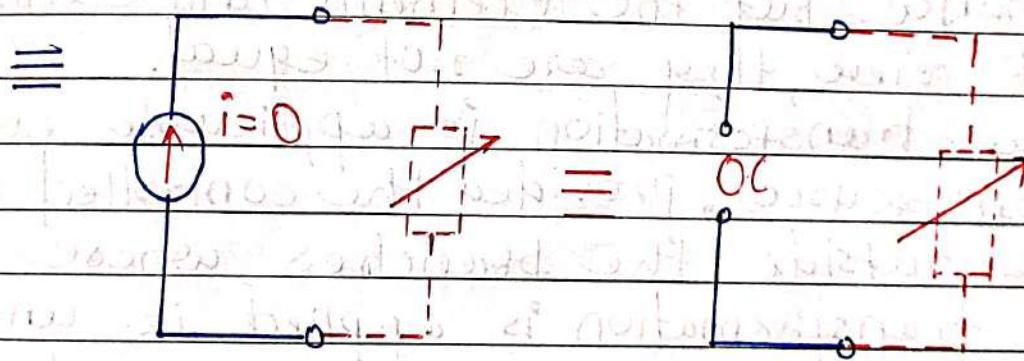By KCL $\Rightarrow -i_1 - i_2 + i = 0 \Rightarrow i = i_1 + i_2$




By KCL $\Rightarrow -10 + 10 + i = 0 \Rightarrow i = 0 \Rightarrow \text{o.c.}$

Source Transformation Techniques

→ It is a simplification technique, which eliminates extra nodes present in the network and it is applicable only for practical sources.

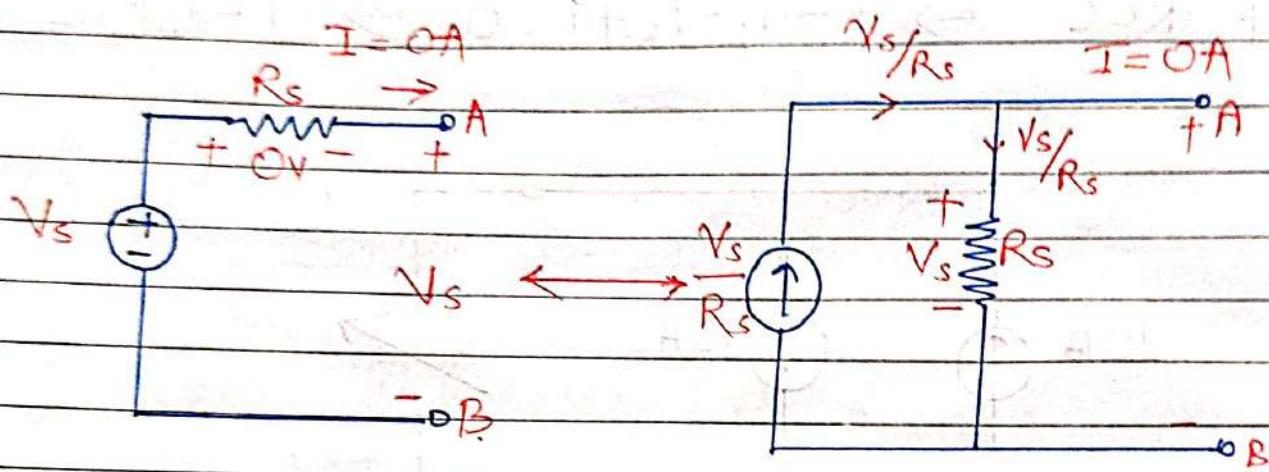→ It is impossible to convert an ideal voltage source into its equivalent current source and vice versa, since violation of KVL and KCL (as there is no resistance in the circuit).



→ The above circuits are equal only w.r.t. performance, but the elements and connections point of view, they are not equal.

→ Source transformation is applicable even for dependent sources, provided the controlled variable must be outside the branches where the source transformation is applied i.e. under any circumstances, controlled variable branch should not be disturbed, otherwise the controlled source magnitude will effect.

Power Calculations By Tellegen's Theorem

Definition:

→ In an arbitrary network, algebraic sum of powers at any given instant is zero. i.e. the power delivered by some elements is equal to the power absorbed by remaining elements present in the network.

$$\text{Mathematically } \sum_{k=1}^b v_k i_k = 0$$

Where b = total number of branches.

→ When current enters at the -ve terminal of an element, then that element will deliver the power, otherwise it will absorb the power.

→ Sources can deliver power or they can absorb power. (In order to protect KCL & KVL in the network ie. to ensure the stability of the network), whereas the passive elements will always absorb power, since current will enter at the positive terminal in the respective R, L, C (as the sources are present there.)


Properties:

- This theorem depends on the voltage & current product in an element, but not on the type of element (Linear, non linear, active, passive etc) i.e. Independent of the nature of the element (Like KCL & KVL)
- Tellegen's theorem expresses conservation of power (energy) in every lumped electric circuit.

Note:-

While verifying Tellegen's theorem do not disturb the original network given for evaluating voltages and currents in each and every elements of the network.
(i.e. Source transformation technique is not applied on the network)

Ques ① Find the current in 3Ω Resistor.

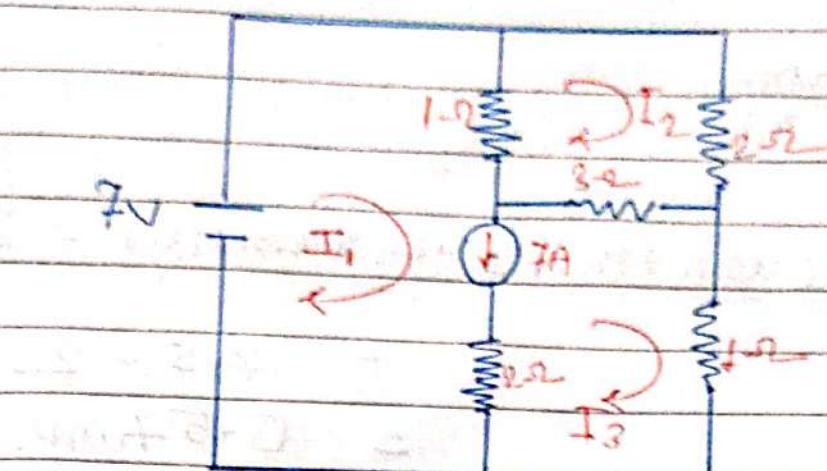

→ Mesh ① & ③ will form a supermesh
writing current equation for supermesh

$$I_1 - I_3 = 7 \quad \text{--- } ①$$

Applying KVL to the Other path of the supermesh

$$7 - 1(I_1 - I_2) - 3(I_3 - I_2) - I_3 = 0$$

$$-I_1 + 4I_2 - 4I_3 = 7 \quad \text{--- } ②$$

Applying KVL to mesh ②

$$-1(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) = 0$$

$$I_1 - 6I_2 - 3I_3 = 0 \quad \text{--- } ③$$

Solving eqn ①, ② & ③

$$I_1 = 9 \text{ Amp}$$

$$I_2 = 2.5 \text{ Amp}$$


$$I_3 = 2 \text{ Amp.}$$

Current through the 3-Ω resistor = $I_2 - I_3$


$$= 2.5 - 2$$

$$= 0.5 \text{ Amp.}$$

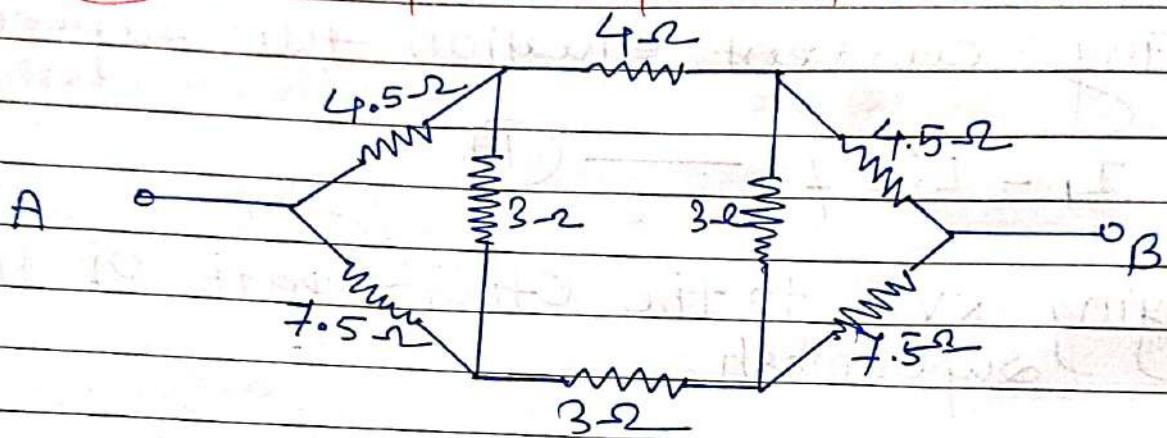Ques ② Find equivalent resistance betw A & B.



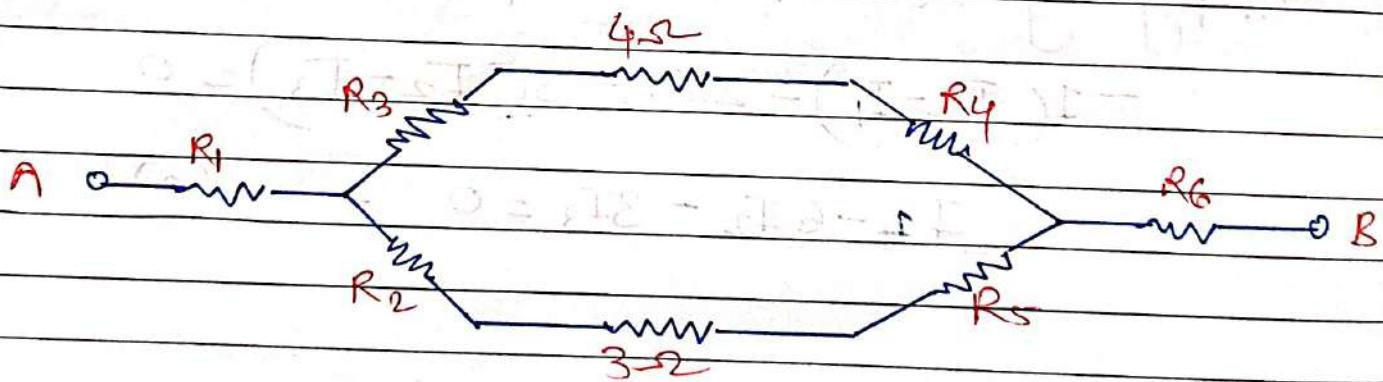→ Converting the two delta networks formed by resistors 4.5Ω , 3Ω & 7.5Ω into equivalent star networks, we have




$$R_1 = R_6 = \frac{4.5 \times 7.5}{4.5 + 7.5 + 3} = 2.25 \Omega$$



$$R_2 = R_5 = \frac{7.5 \times 3}{4.5 + 7.5 + 3} = 1.5 \Omega$$

$$R_3 = R_4 = \frac{4.5 \times 3}{4.5 + 7.5 + 3} = 0.9 \Omega$$

The simplified network is shown in fig.

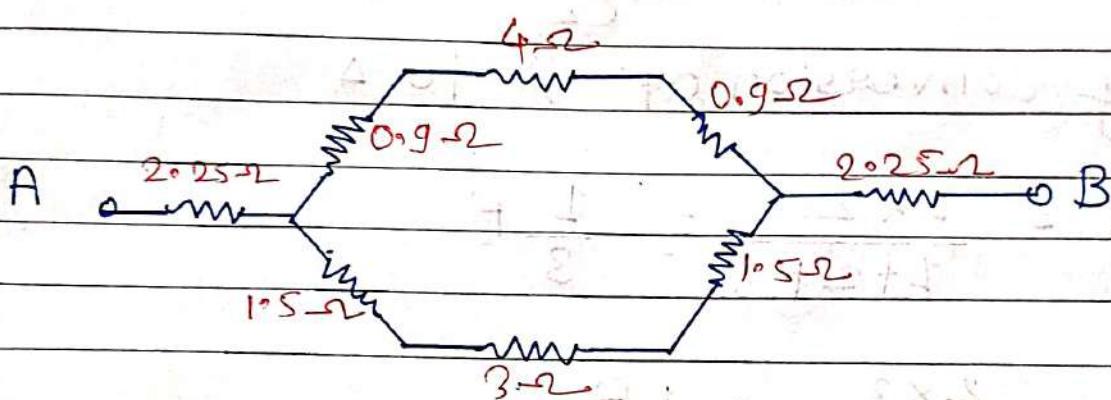

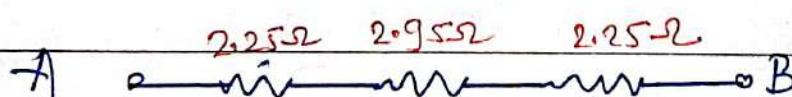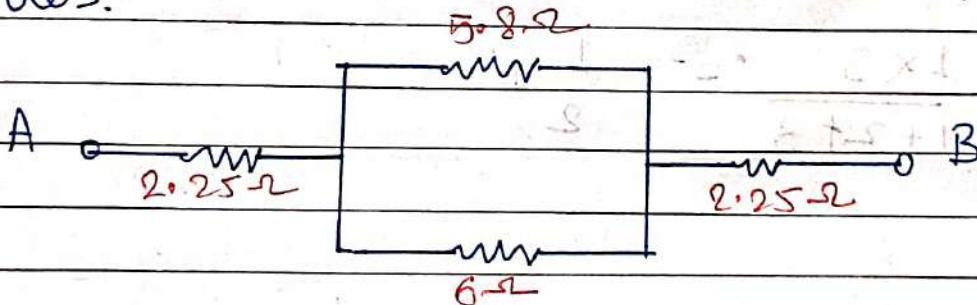
The network can be further simplified as follows.



$$7.45 \Omega$$

$$R_{AB} = 7.45 \Omega$$

Que. ③ Determine C_1 , C_2 , C_3 ?

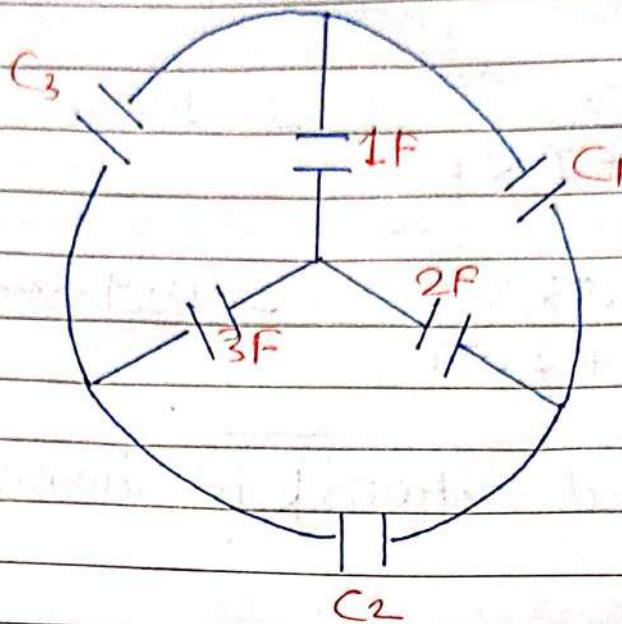


⇒ By conversion of λ to Δ

$$C_1 = \frac{1 \times 2}{1+2+3} = \frac{1}{3} F$$


$$C_2 = \frac{2 \times 3}{1+2+3} = 1 F$$

$$C_3 = \frac{1 \times 3}{1+2+3} = \frac{1}{2} F$$

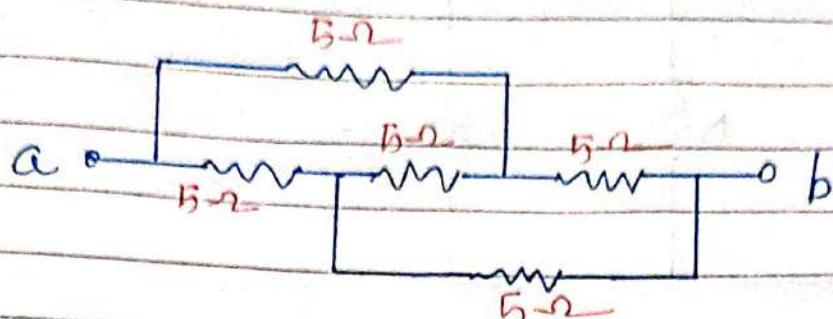Que 4) Find the equivalent resistance across $a \rightarrow b$.




→ By redrawing

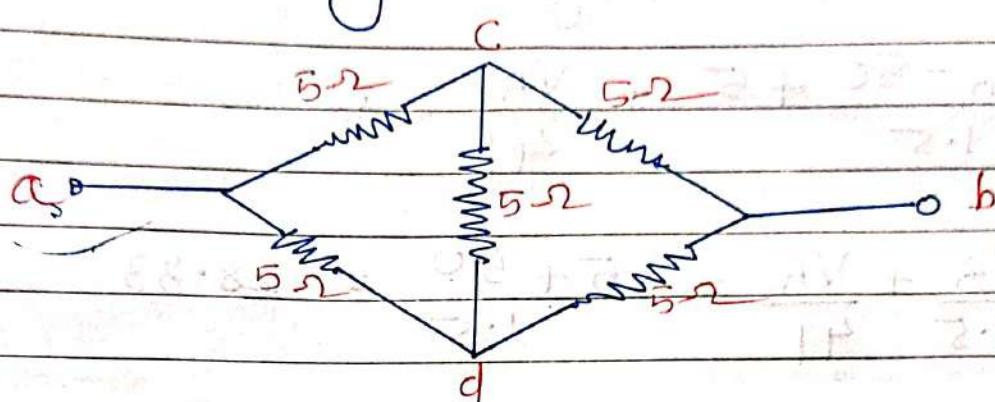

Here bridge is balanced, so no current will flow in branch cd .

$$R_{ab} = 10 // 10 = \frac{10 \times 10}{10 + 10} = 5 \Omega$$

Ques 5 Find the value of R

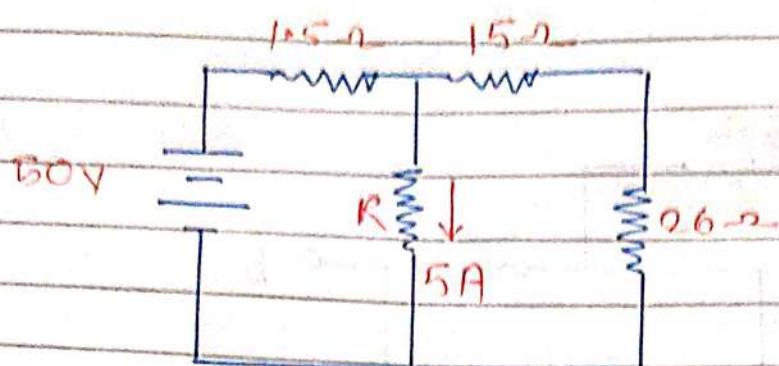

→ By nodal analysis

$$\frac{V_A - 50}{1.5} + 5 + \frac{V_A}{41} = 0$$

$$\frac{V_A}{1.5} + \frac{V_A}{41} - \frac{-5 + 50}{1.5} = 28.33$$

By solving

$$V_A = 40.99 \approx 41$$

$$so R = \frac{41}{5} = 8.2\Omega$$


$$\underline{R = 8.2\Omega}$$

Practice questions:


- ① What value of R ensures that the current through the $60\text{-}\Omega$ resistor of this circuit is 1A ?



- ② Find R_{ab} ?

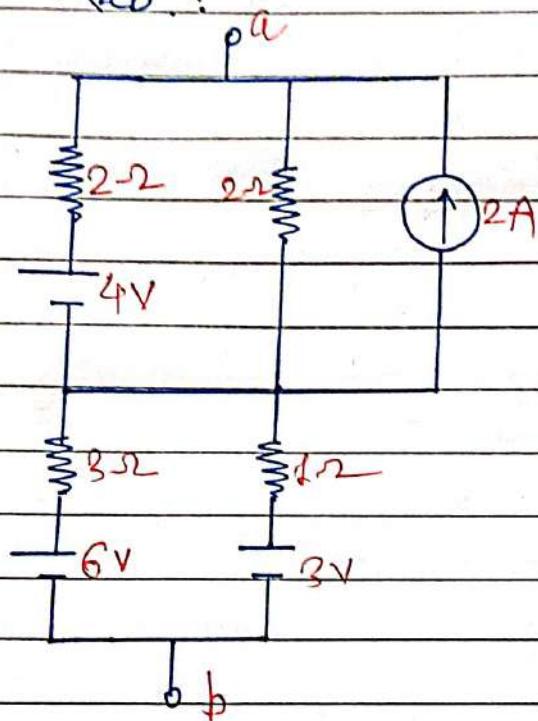

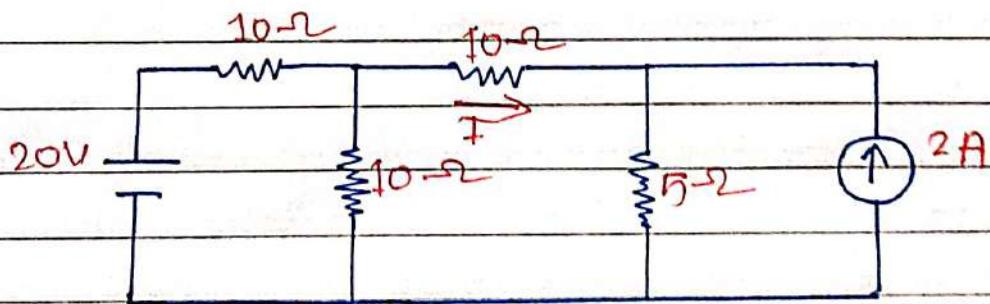
- ③ find current indicated in below figure



Thevenin's Theorem

linear
two
terminal
ckt

$$R_L \equiv \frac{V}{I} = R_L$$

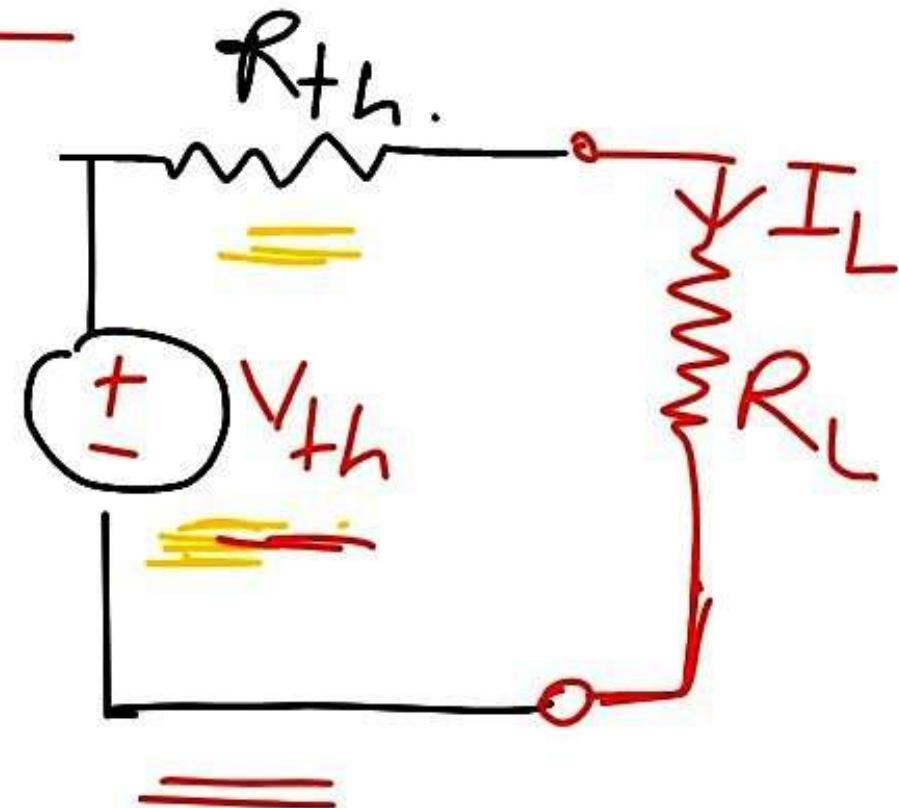


Thevenin's thⁿ States that a linear two terminal ckt can be replaced by equivalent ckt consisting of a Voltage source $\underline{V_{th}}$ in series with a resistor $\underline{R_{th}}$ where

$V_{th} \Rightarrow$ open ckt voltage at load terminal

$R_{th} \Rightarrow I/p$ or equivalent
resistance at load terminals
when the independent sources
are turned off & killed.

Norton's Theorem :-

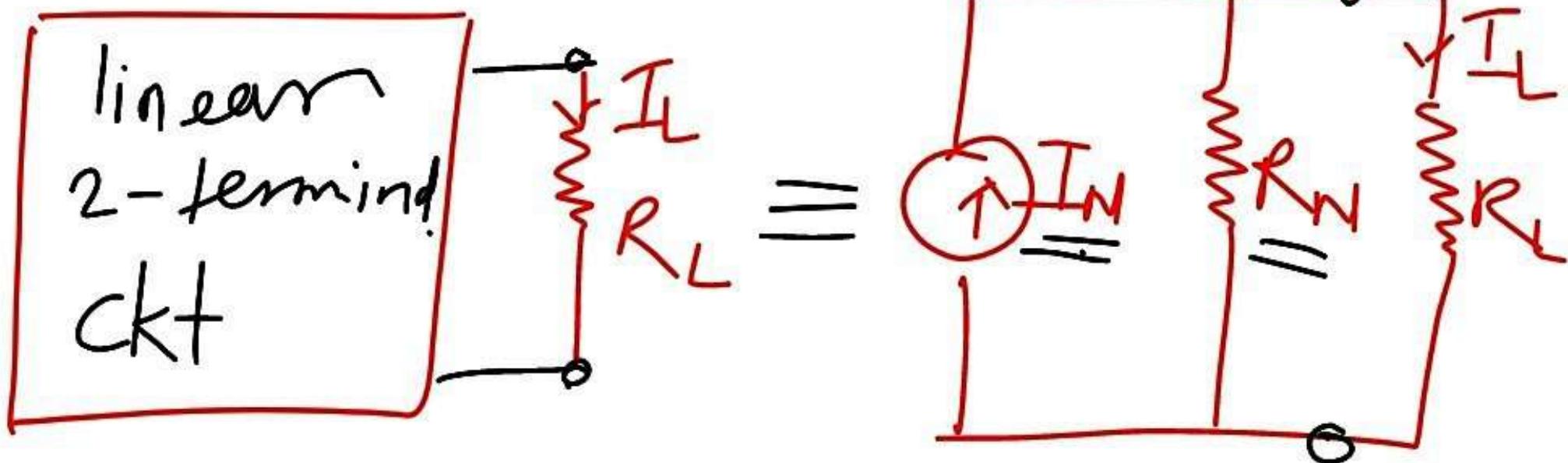


Statement



Norton's Th^m States that a linear two terminal circuit can be replaced by an equivalent ckt consisting of current source I_N in ||| with resistor $\underline{\underline{R_N}}$

$I_N \Rightarrow$ Short circuited current
through the load terminal



$R_N \Rightarrow$ i/p on equivalent resistance
at load terminal when
the independent sources are
turned off ie killed. $R_N = R_{th}$.


Procedure

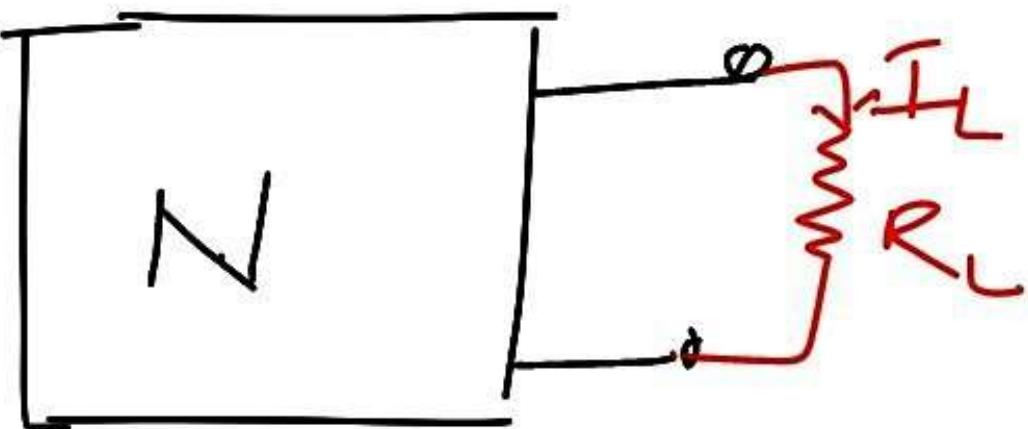

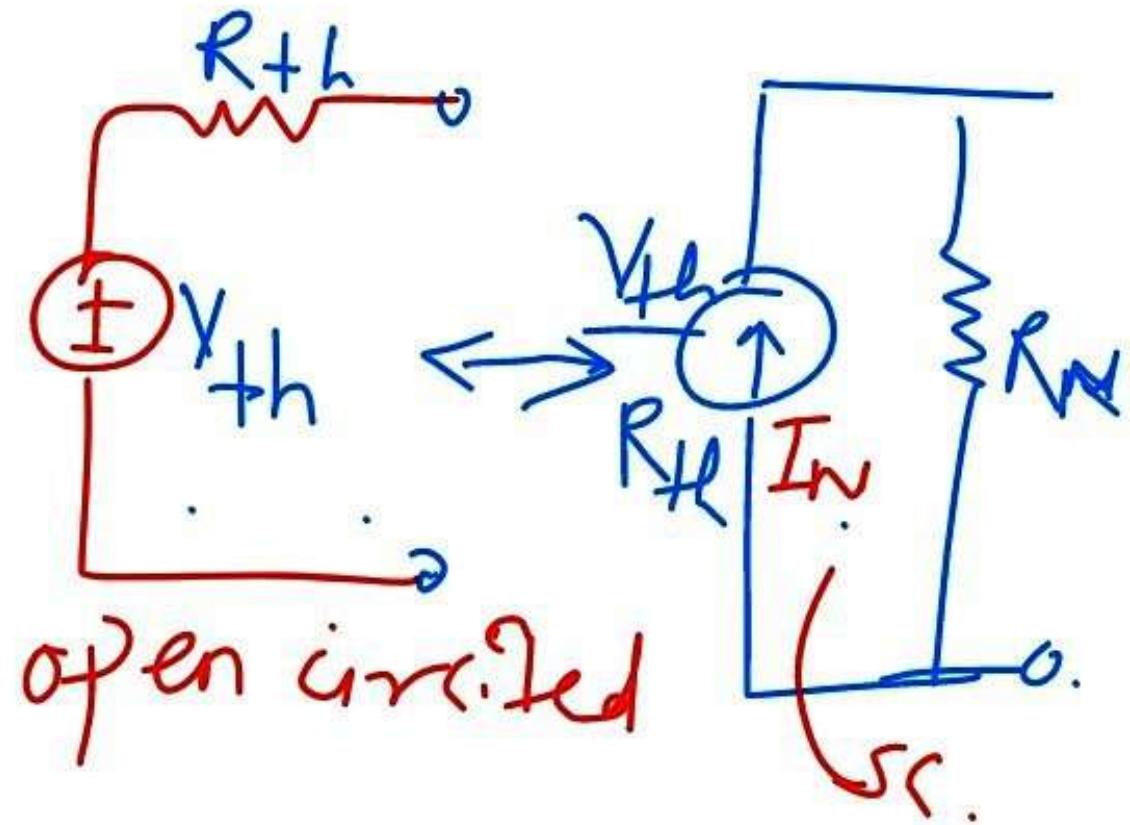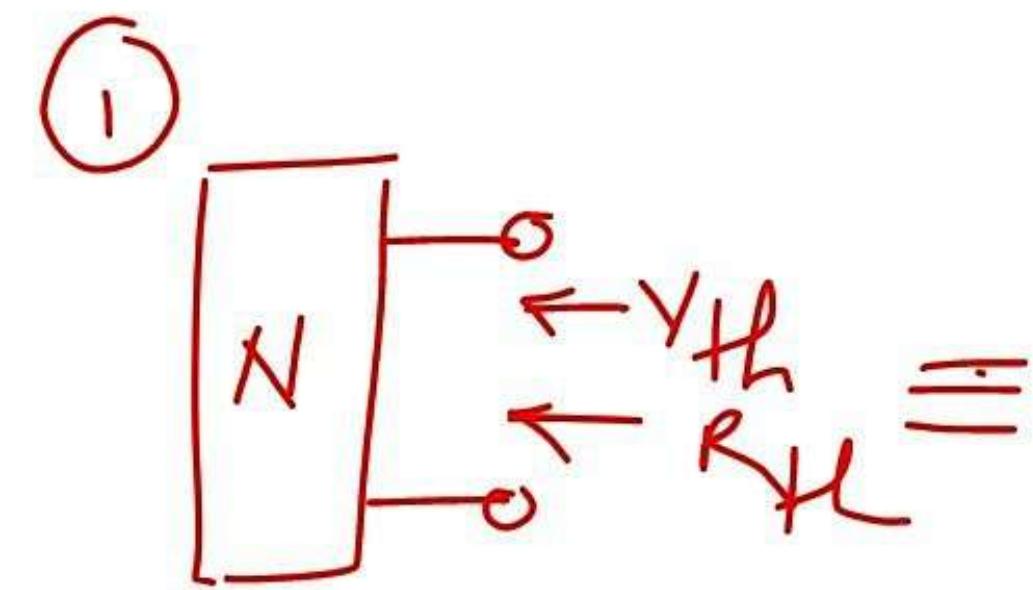

②

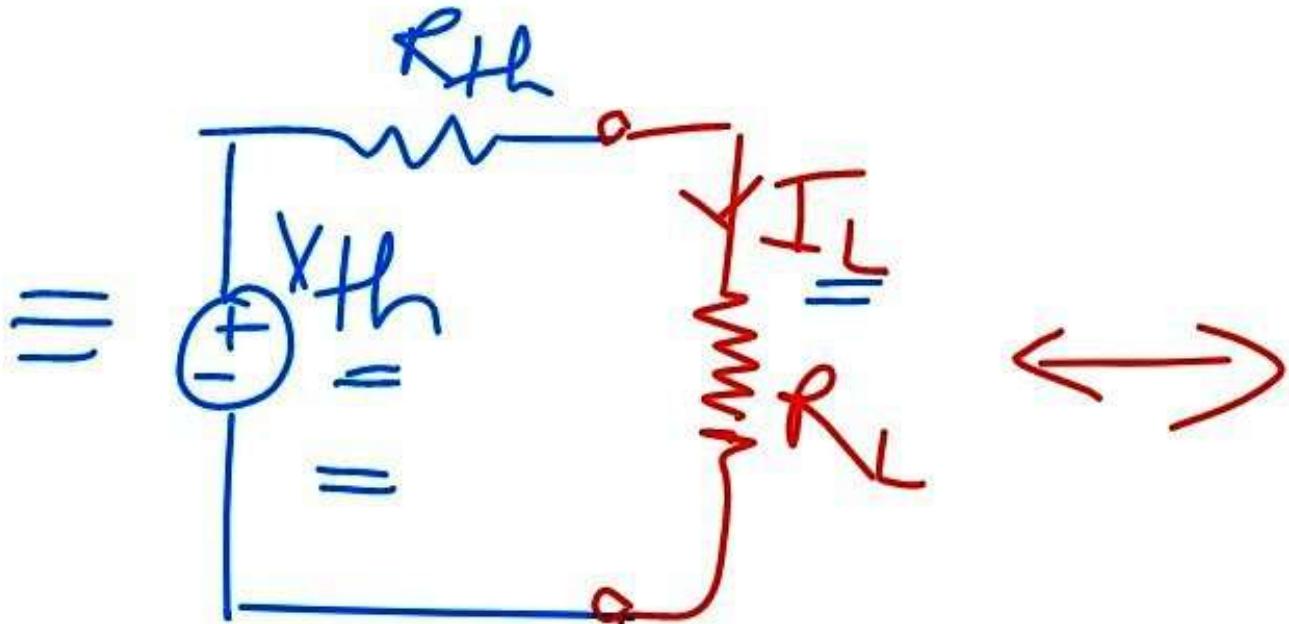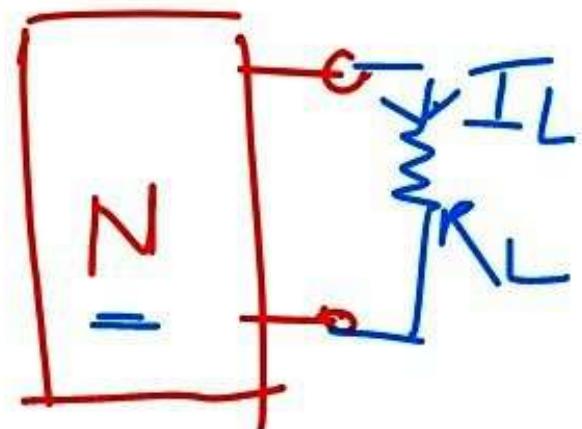

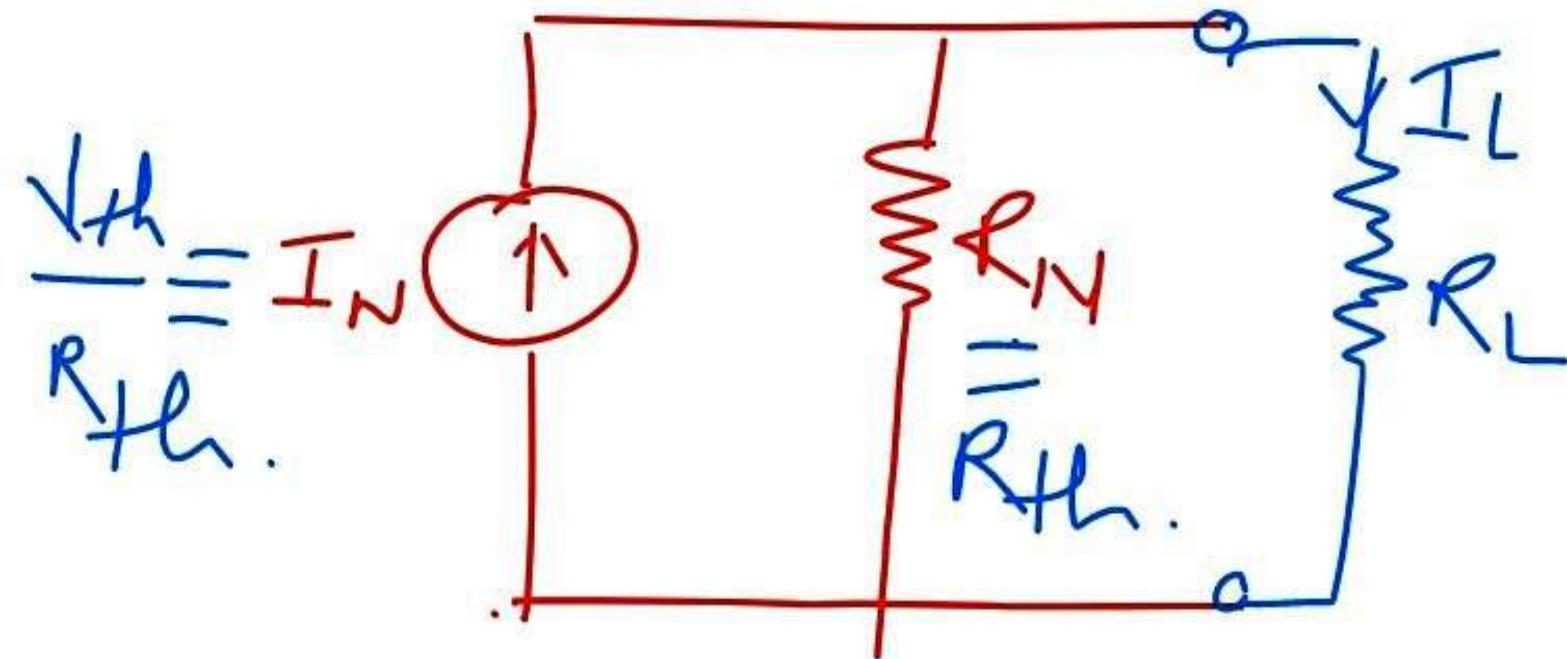

$$\frac{V_{th}}{R_{th.}} = I_N$$

By ohm's Law.


$$I_L = \frac{V_{th}}{R_{th} + R_L} \quad \text{Amp.}$$

$$I_L = \frac{\frac{V_{th}}{R_{th}} \times R_{th}}{R_{th} + R_L} =$$

3 cases in Thevenin's Thm
& Nortons. Thm based on
sources.

- ① All are Independent source. : $\underline{V_{TH}} = \underline{R_{TH}}$

Q

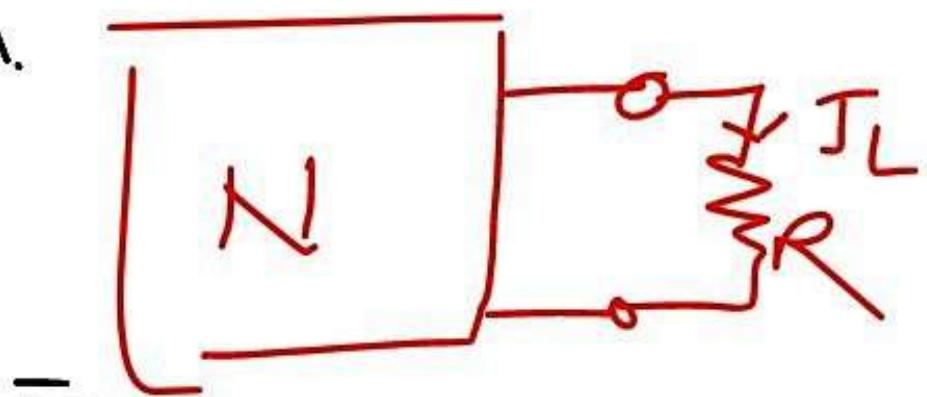

Several resistors


& DC sources

= The current $I = \underline{3 \text{ Amp}}$

$\frac{1.5 \text{ Amp}}{\text{resp.}}$ when $R = \underline{0\Omega \text{ & } 2\Omega}$
Determine I when $R = 1\Omega$

Method ① by Thevenin's

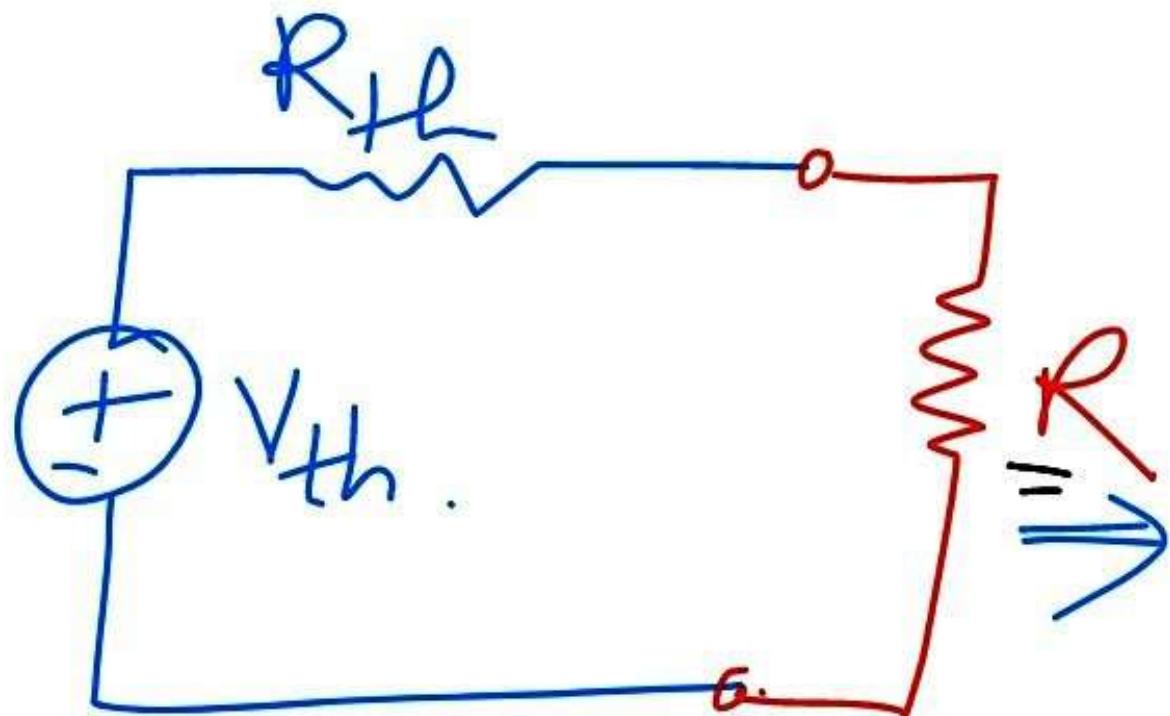Note :- Any n/w. with any no. of elements w.r.t load element can be written as a 3 element n/w.



$$I = \frac{V_{th}}{R_{th} + R}$$

$$V = \frac{V_{th}}{R_{th}} \times R$$

$$1 \cdot n = \frac{R_{th}}{R_{th} + 2} - \textcircled{2}$$

$$\frac{1}{n} = \frac{R_{th} + 2}{R_{th}}$$

$$R_{th} = 2n$$

$$2 = 1 + \frac{2}{R_{th}}$$


$$\beta = \frac{V_{th}}{2}$$

$$\boxed{V_{th} = 6V}$$

$$I = \frac{6}{2+1} = 2 \text{Amp.}$$

V_{th} , R_{th} are
independent of
load value

Nortons Thm

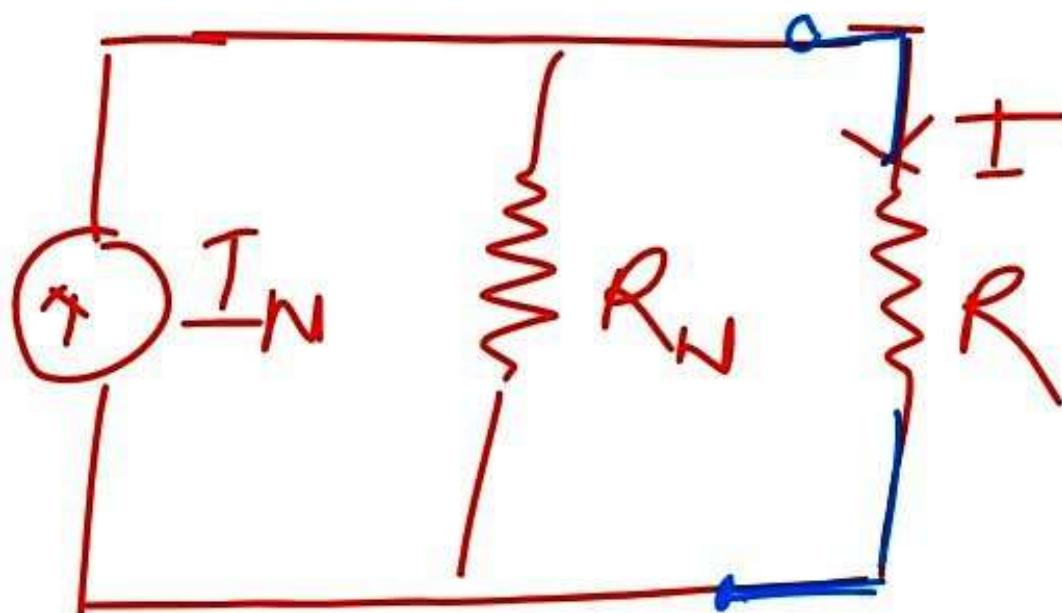

$$I = \frac{I_N R_L}{R + R_L}$$

$$V = \frac{I_N R_L}{R + R_L} R$$

$$= \frac{I_N R_L}{R + R_L} - \textcircled{1}$$

$$I \cdot \zeta = \frac{I_N R_N}{2 + R_N} \rightarrow ②$$

$$\frac{3}{I \cdot \zeta} = \frac{2 + R_N}{R_N}$$


$$2 = 3/R_N + 1 \Rightarrow$$

$$R_N = 2 \Omega$$



$$3 = \frac{I_N R_{\text{in}}}{R_{\text{in}}}$$

$$I_N = 3 \text{ Amp.}$$

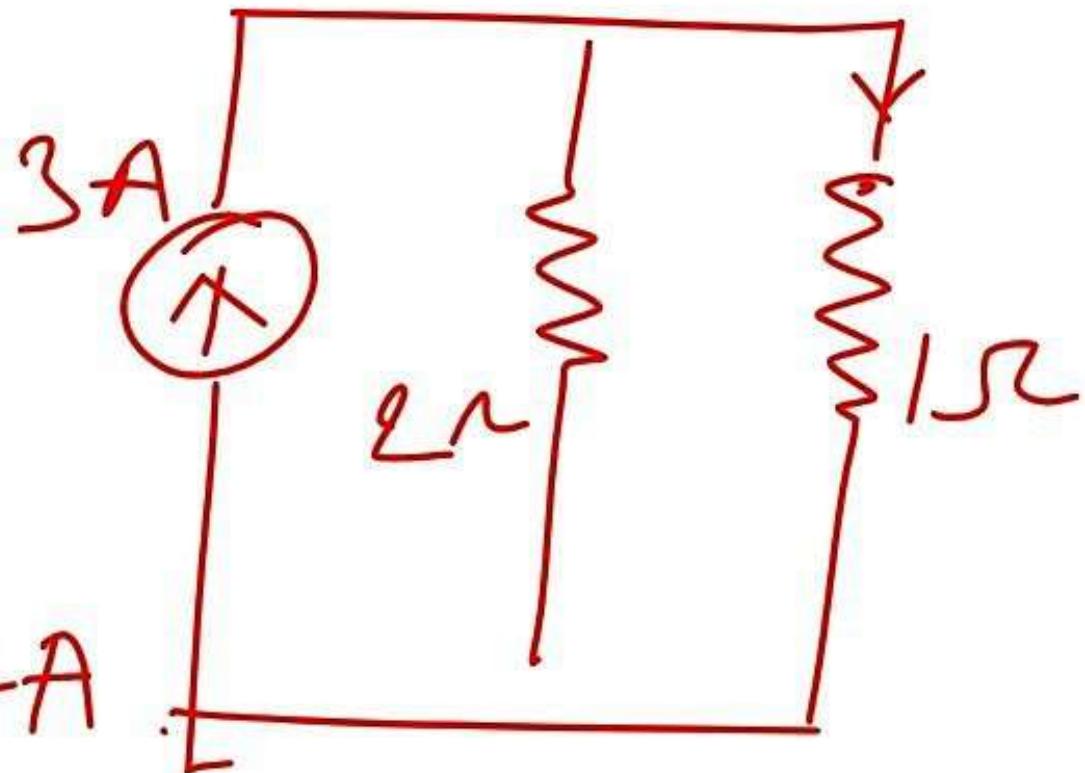
$$I = \frac{3 \times 2}{4 + 2} = 2 \text{ A}$$



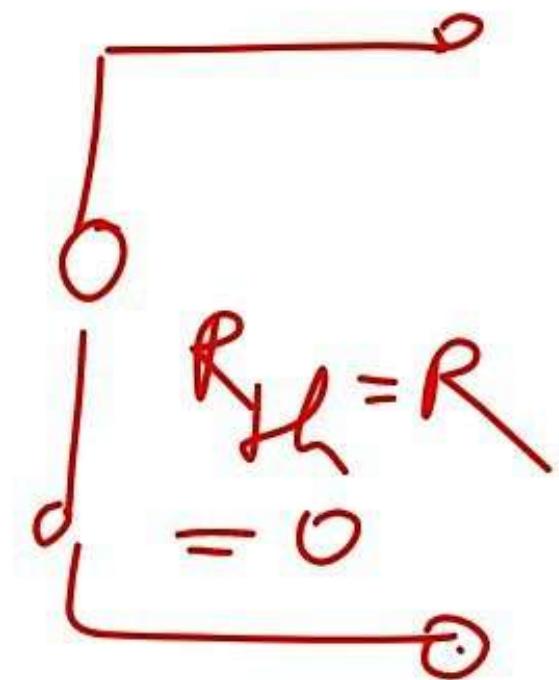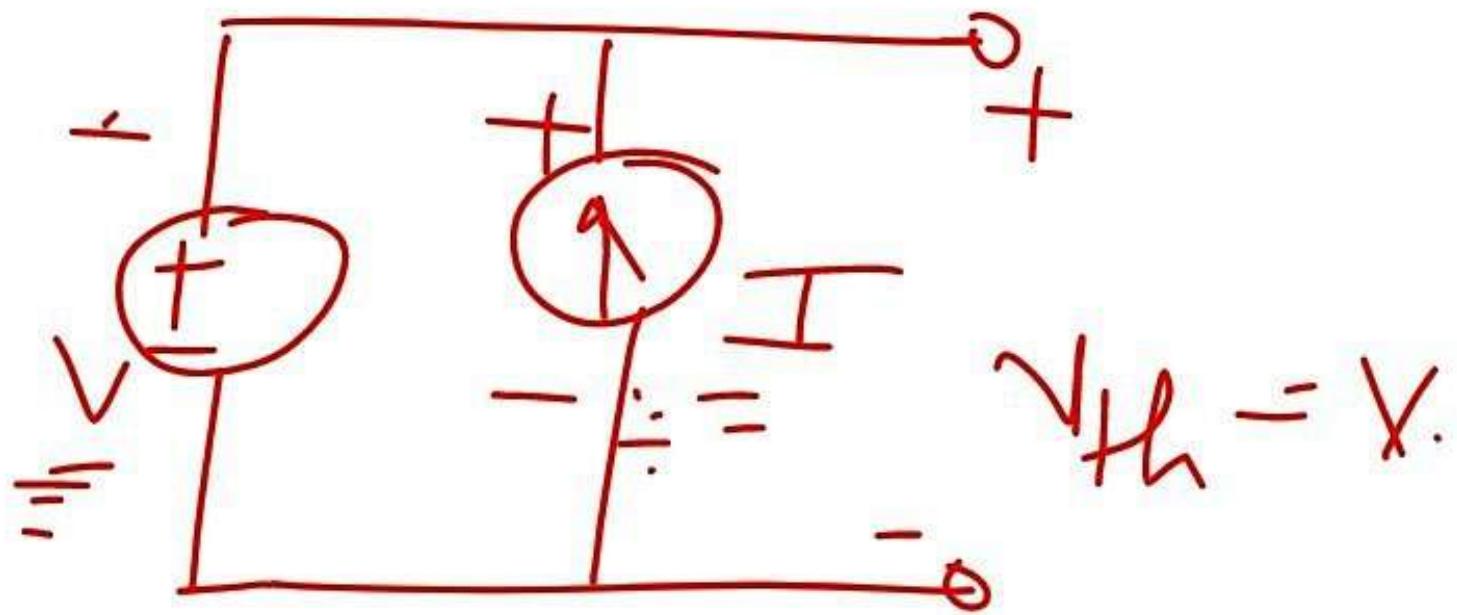- ② An ideal voltage & current sources are connected in parallel.
- Then combination will have
- ① Thvenins & Norton.
- ② Thvenin. \cancel{X}
- ③ Norton \cancel{X}
- ④ Neither Thvenin nor Norton.



Reason

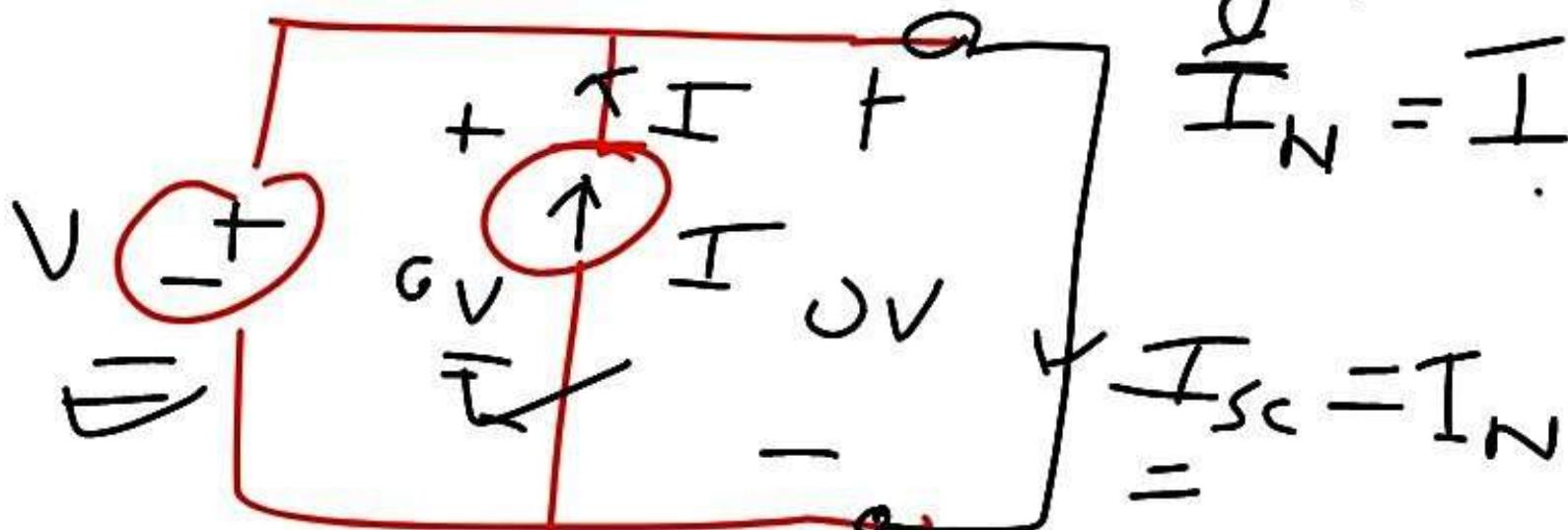


By KCL

$$I_N = I + \cancel{\text{any value}}$$

$$I_{sc} = I_N$$

$$V - 0 = 0$$

$$V = 0 \times$$

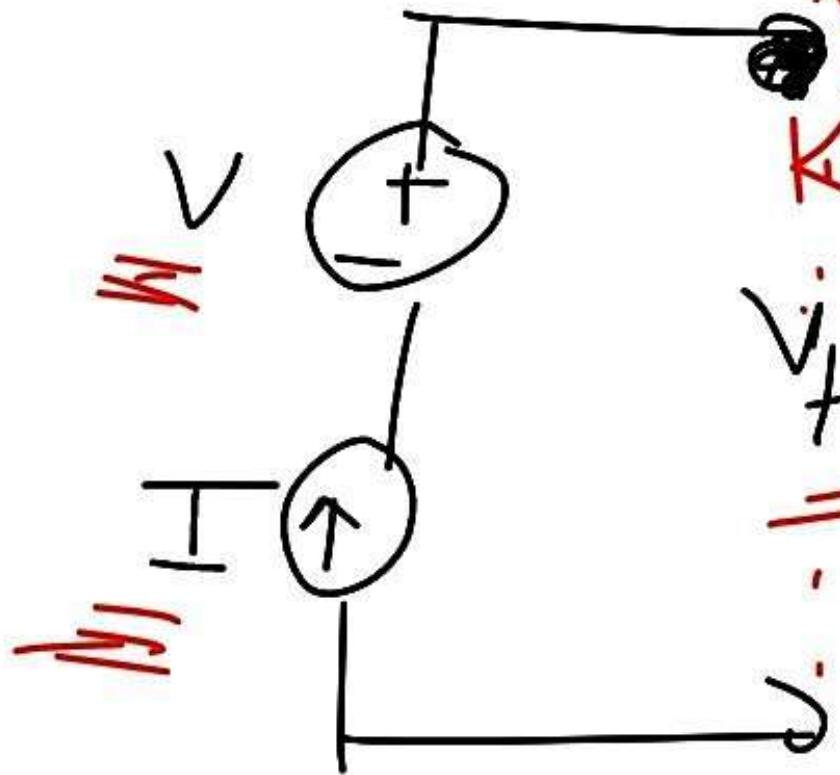

Violation of
KCL at this Node.

With KVL

$$V_{th} = V + \text{any value}$$

② At least one Independent and one dependent source.

$$V_{th}, I_{sc}$$

$$R_{th} = \frac{V_{th}}{\underline{I}_{sc}} \Omega$$


$$\underline{I}_{sc} = \frac{V_{th}}{R_{th}} = I_N =$$

Case 2 :- At least one independent
and one dependent source

$$\Rightarrow R_{th} = \frac{V_{th} \text{ (Inside)}}{I_{SL}}$$

$$I_{SL} = I_N$$

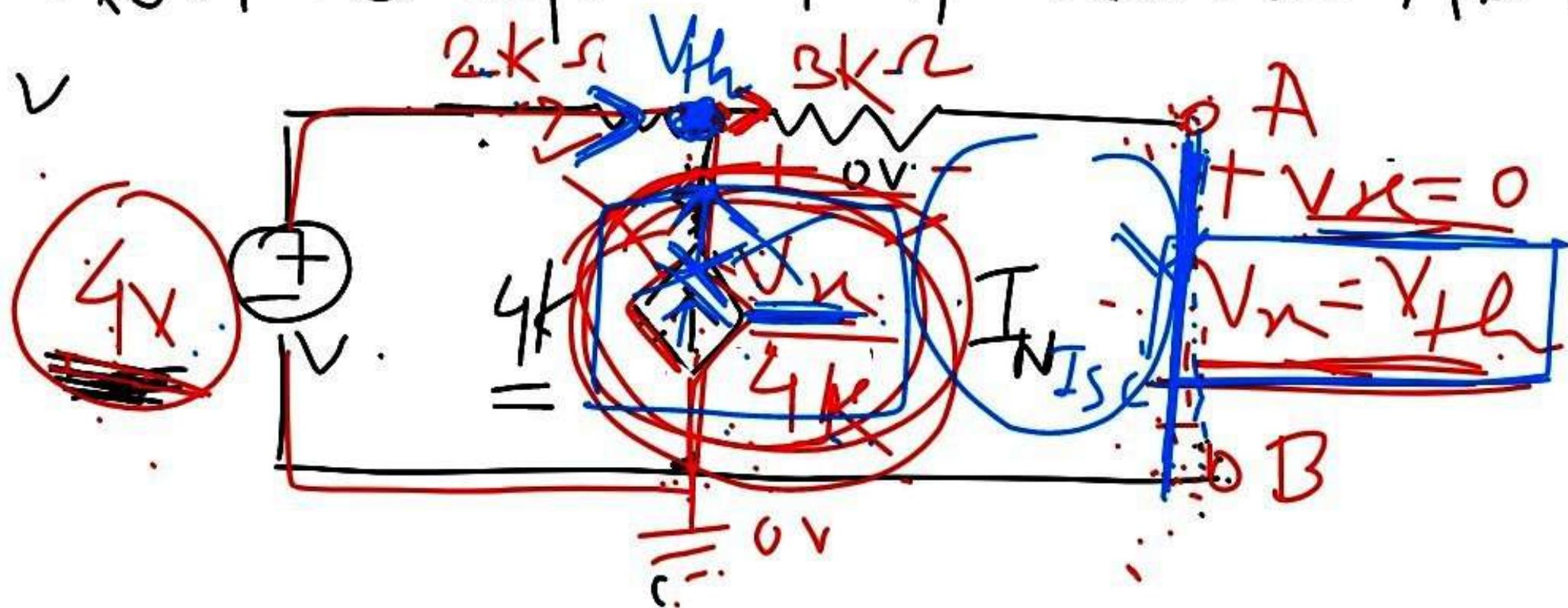Q. Determine the Thvenin's & Norton's equivalent across AB.




$$\rightarrow V_x = V_{th}$$

Today $\Rightarrow \frac{V_{th} - 4v}{2k} - \frac{V_x}{4k} + 0 = 0$

$$\Rightarrow \frac{V_{th} - 4}{2k} - \frac{V_{th}}{4k} = 0$$

$$\Rightarrow 2V_{th} - 8 - V_{th} = 0$$
$$V_{th} - 8 = 0$$


$V_{th} = 8v$

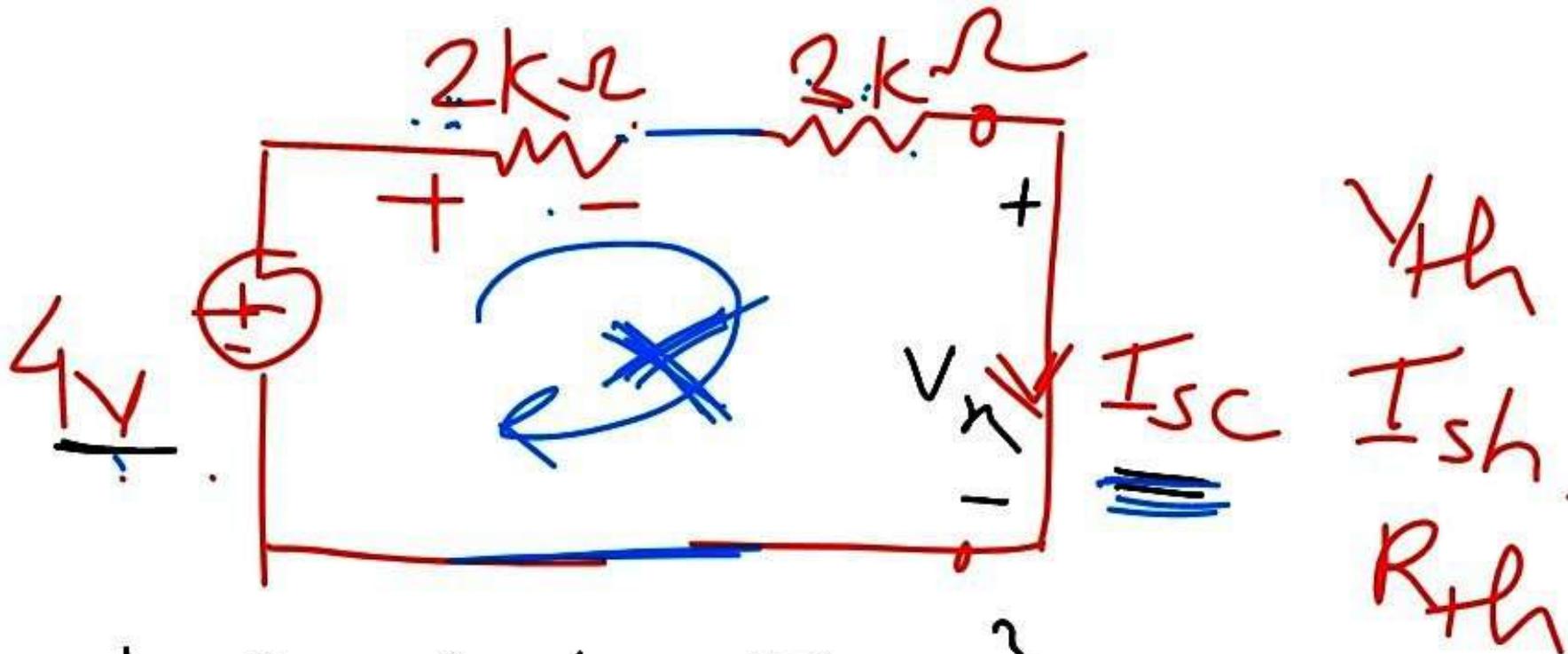


By KVL $\Rightarrow 4 - 5 \times 10^3 I_{SC}$

$$I_{SC} = 4/5 \text{ mA} - I_m$$
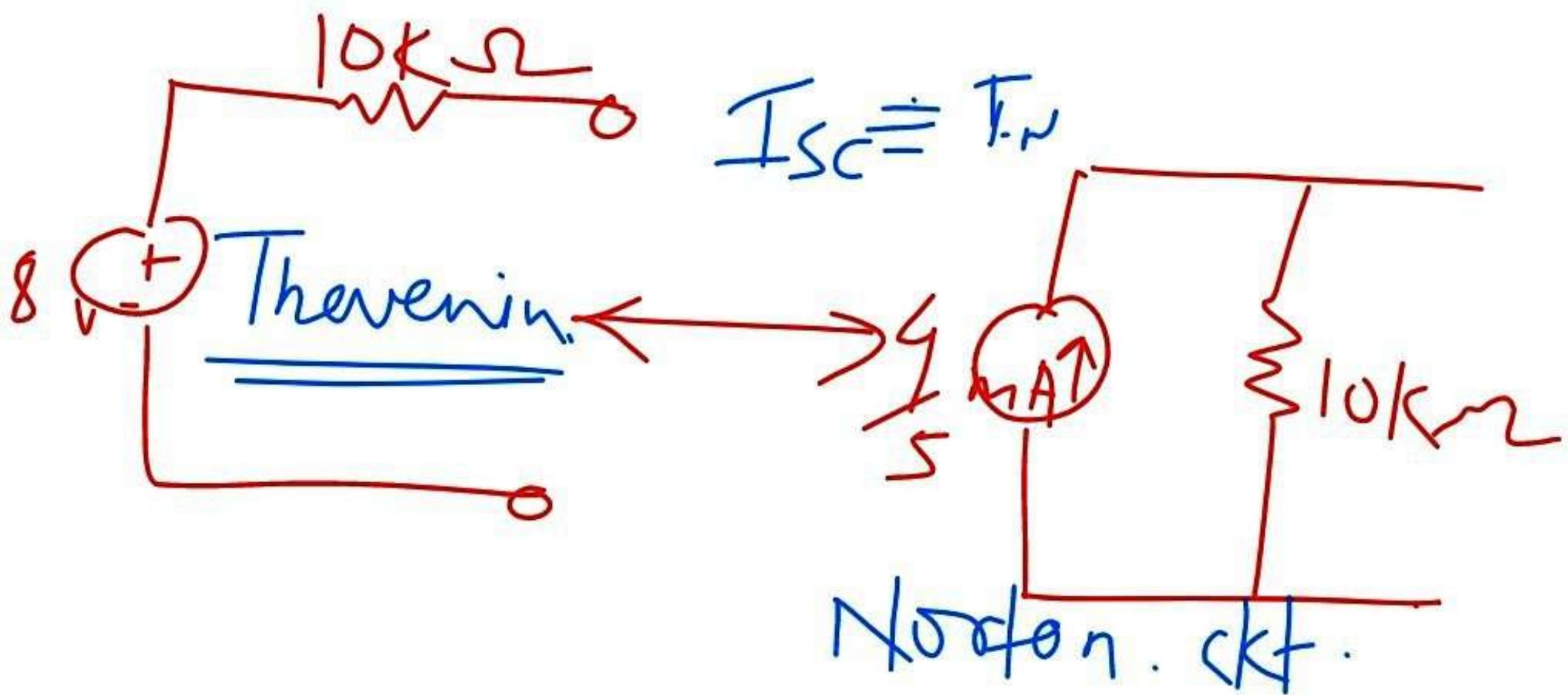
$$\begin{aligned}
 R_{Th} &= \frac{V_{Th}}{I_{SC}} \\
 &= \frac{8V}{4.5 \times 10^3} \quad R_{Th} = \frac{V_{Th}}{I_{SC}} \\
 R_{Th} &= 10K\Omega \quad I_{SC} = \frac{V_{Th}}{R_{Th}} = I_N
 \end{aligned}$$



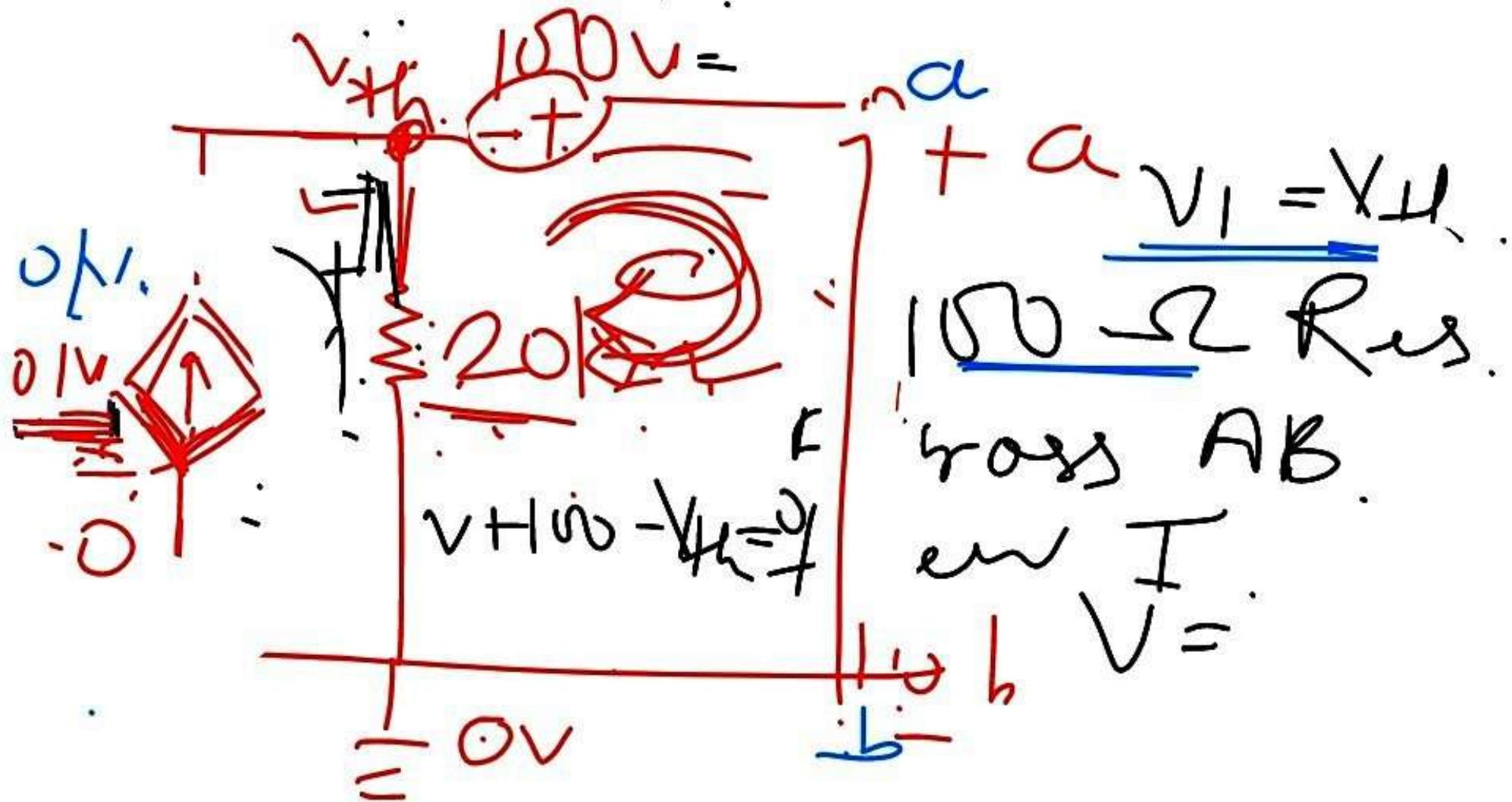


$$\begin{aligned}
 \textcircled{1} \quad & \underline{V_{th}} \Rightarrow \underline{V_{th} - 100} \\
 \text{Nodal} \Rightarrow & -0.01 V_1 + \frac{V}{20k} + 0 = 0 \\
 & -200 V_1 + V = 0 \\
 & -200 V_1 + V_{th} - 100 = 0 \\
 & -200 V_1 + V_1 - 100 = 0
 \end{aligned}$$

$$-199v_1 = 100$$

$$\underline{v_1} = \frac{100}{-199}$$
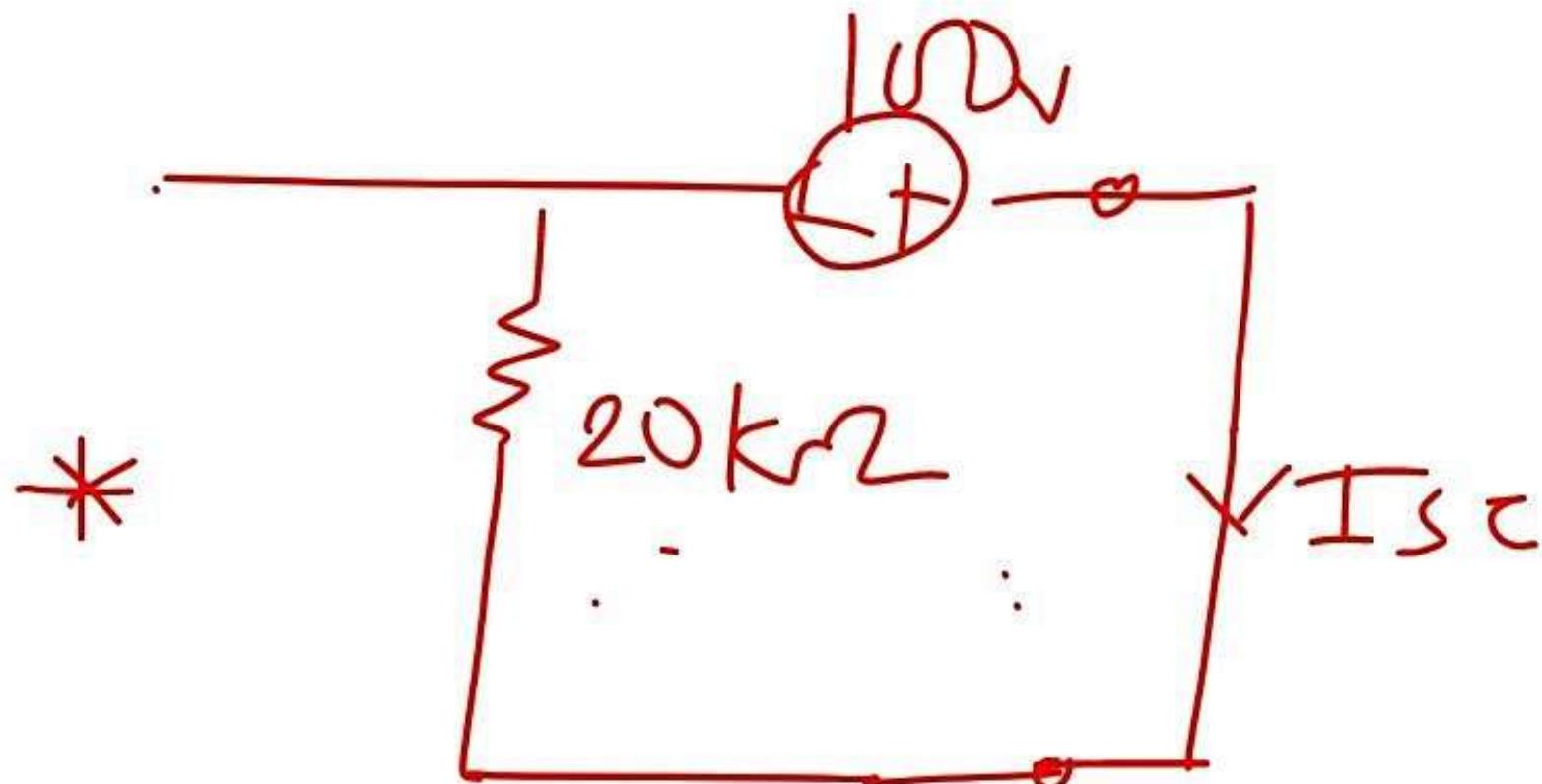
$$\underline{v_1} = \underline{v_{th}} = -502 \cdot \underline{\Sigma m v}$$




$$10V - 20kI_{sc} = 0$$


$$100 - 20 \times 10^3 I_{SC} = 0 \text{ kV}_L$$


$$I_{SC} = 5 \text{ mA}$$


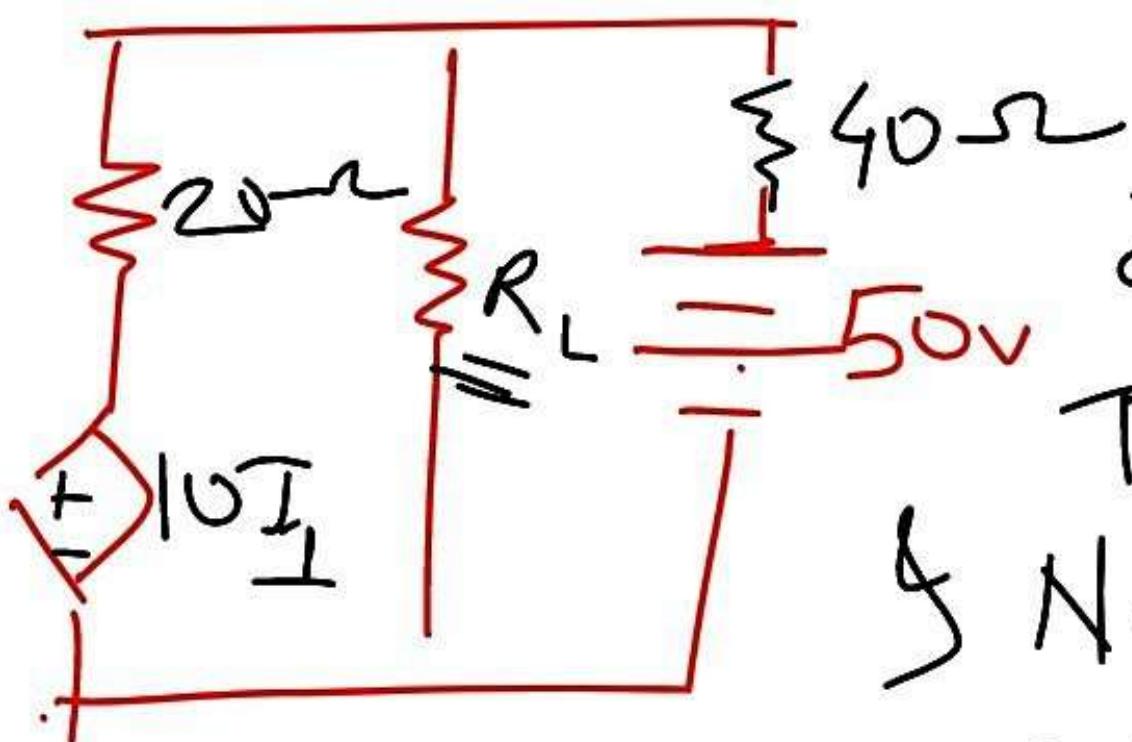
$$R_{Th} = \frac{V_{Th}}{I_{SC}} = \frac{V_{Th}}{5 \times 10^3} = R_{Th}.$$
$$= -100.5 \Omega$$



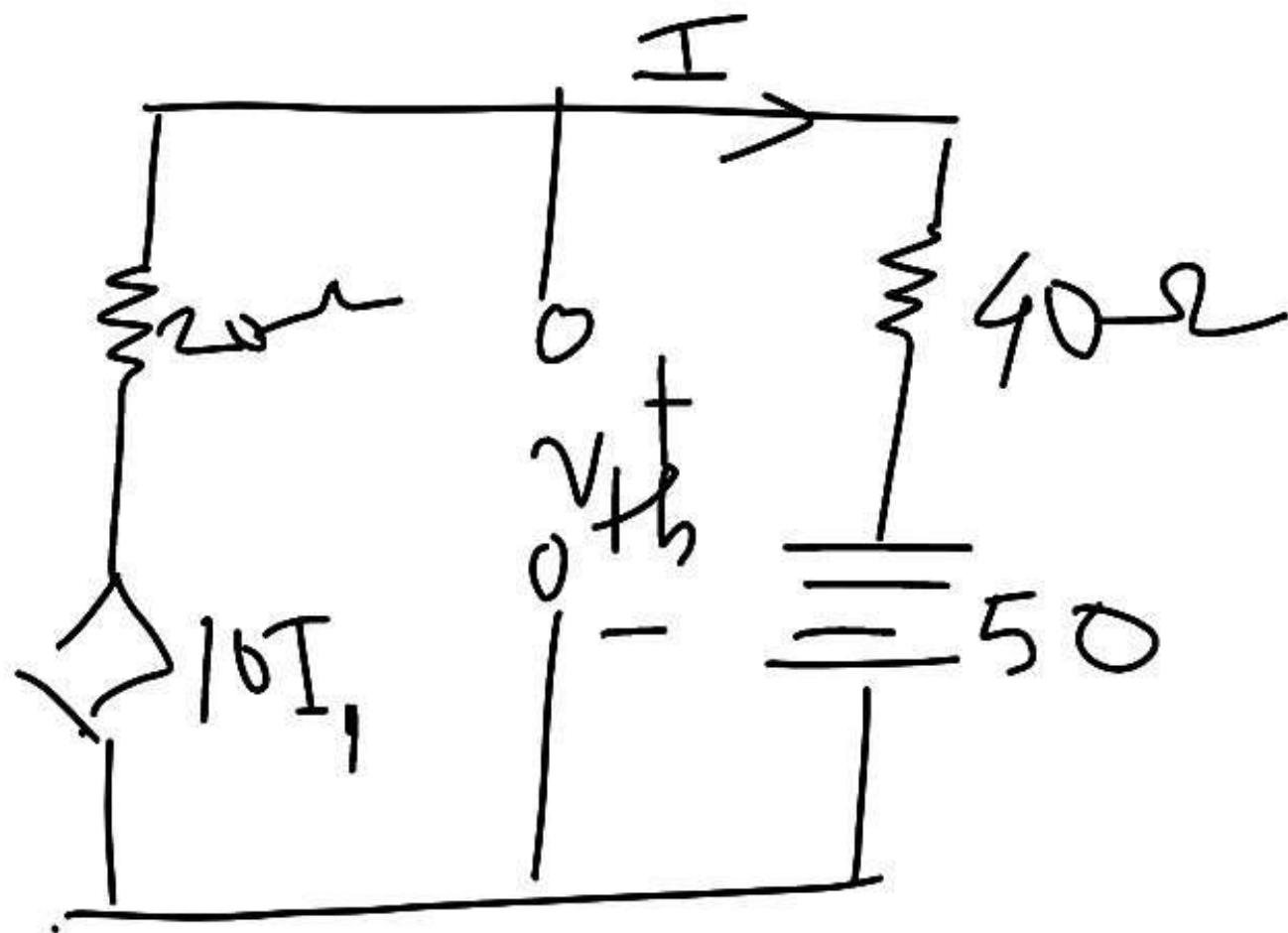
Determine
Thevening
& Norton's equivalent
across R_L



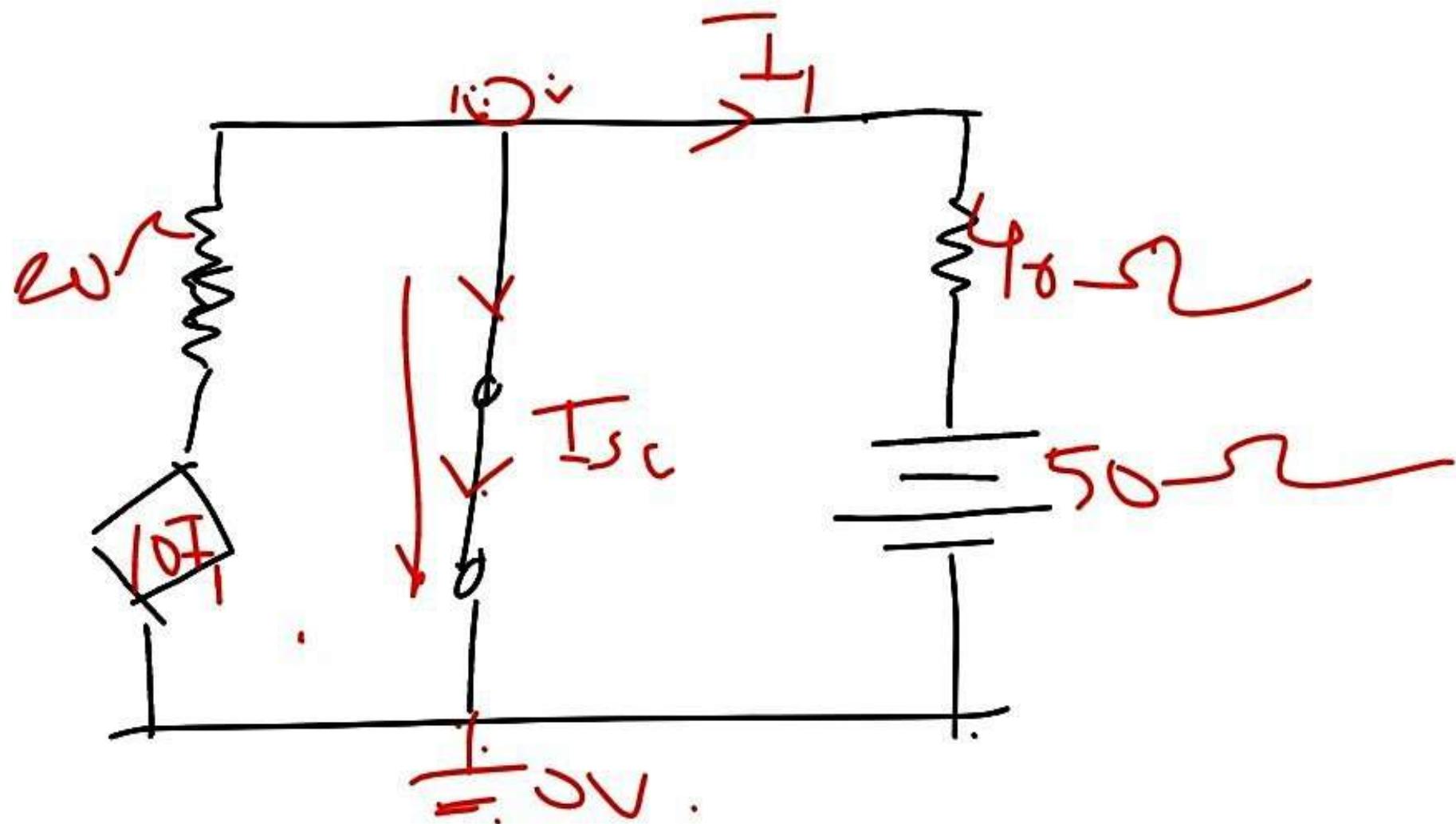

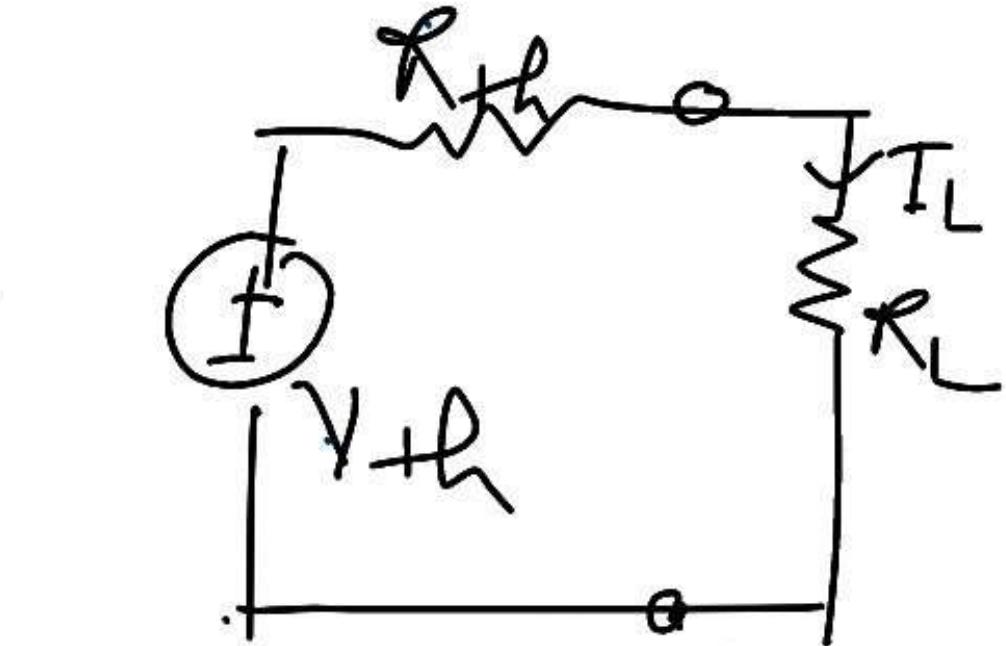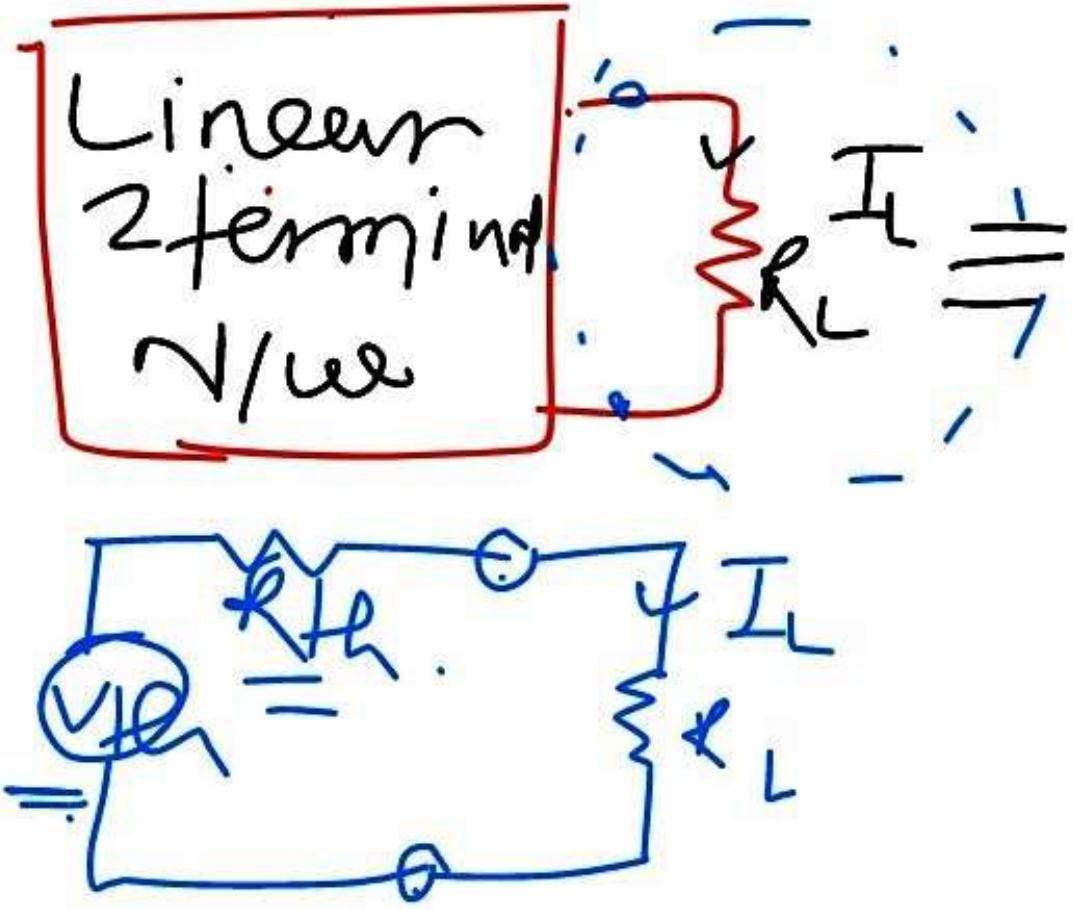


Thevenin's Thm.

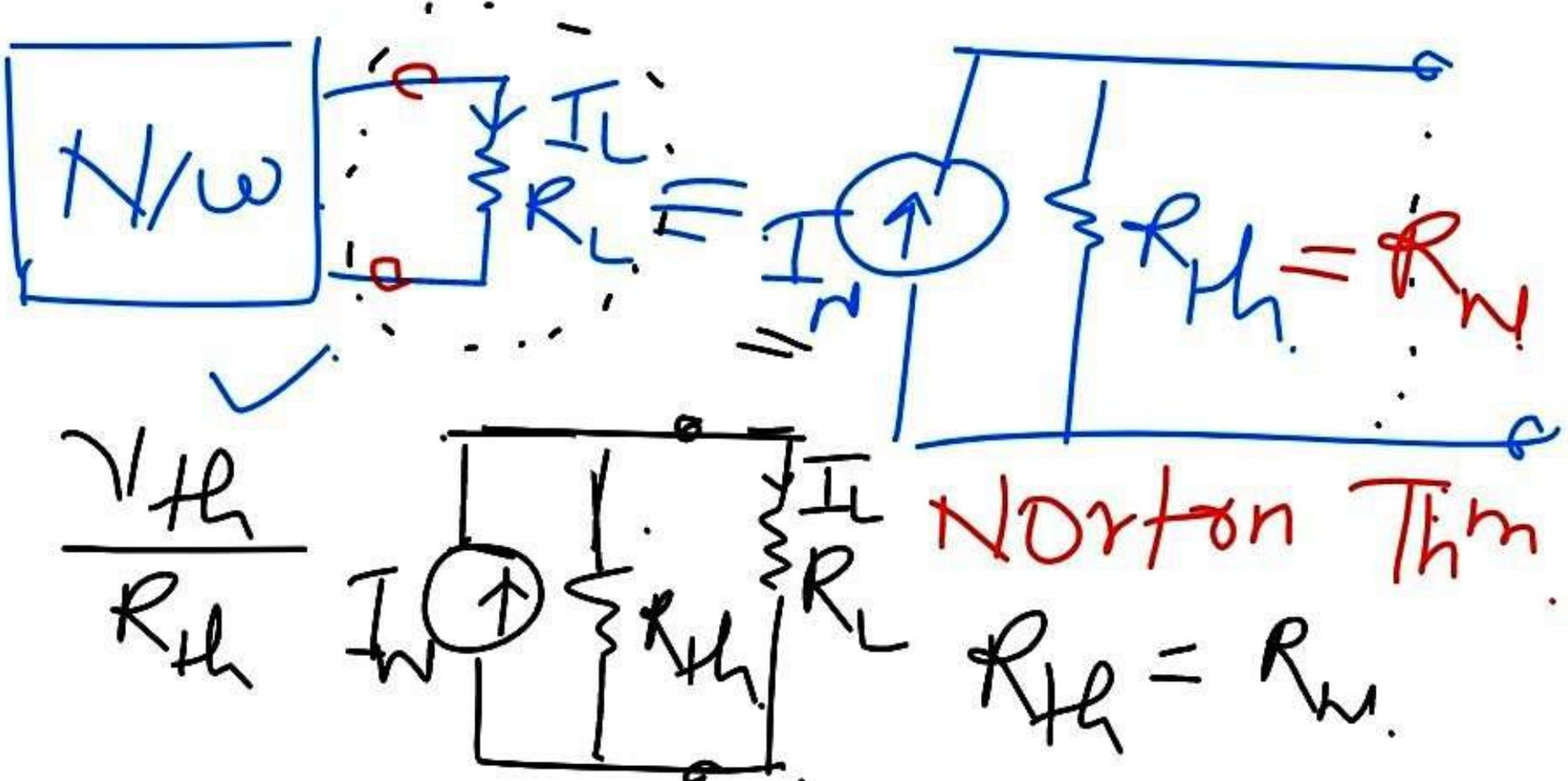



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$V_{th} \xrightarrow{+/-} .$$

All are Independent source

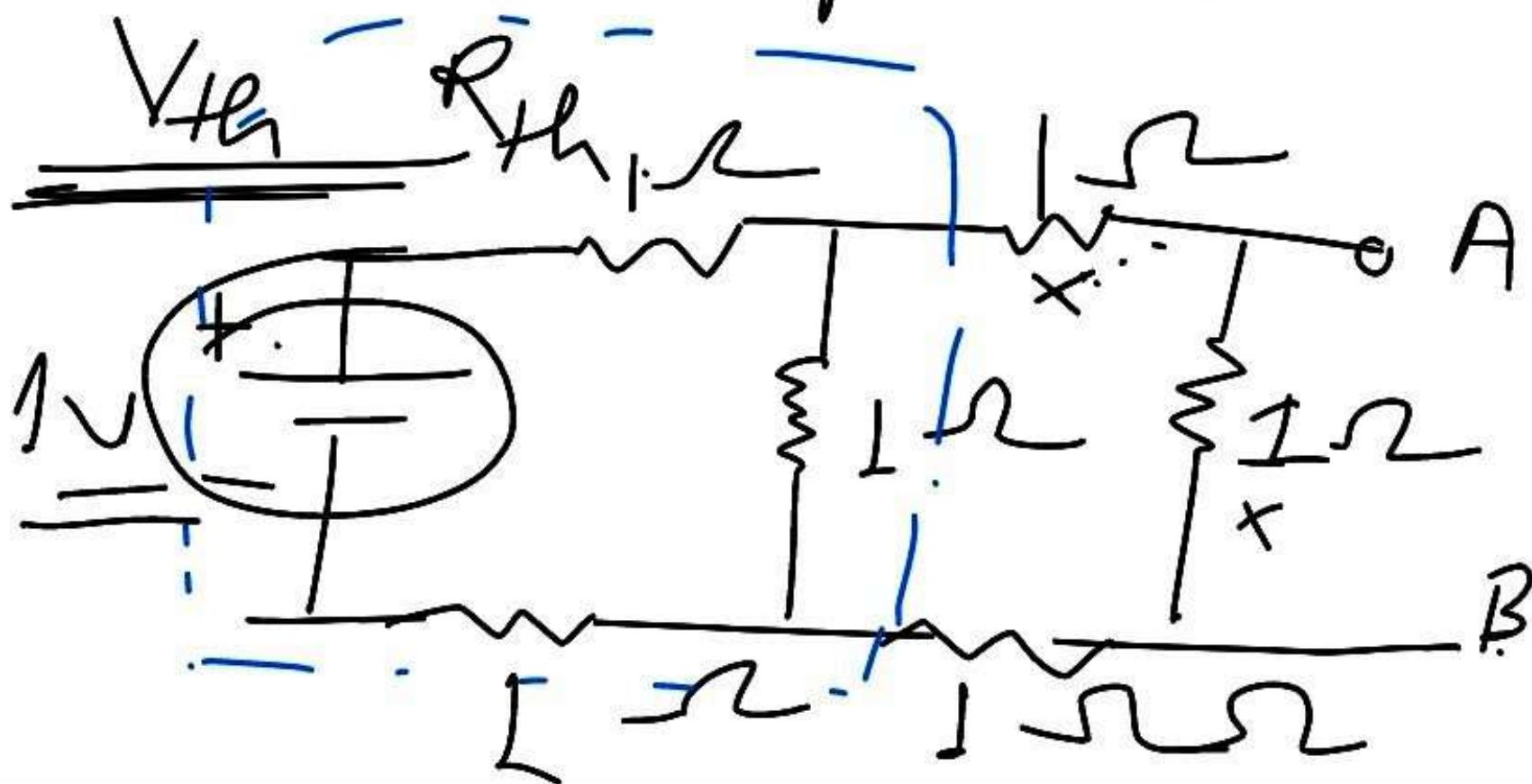


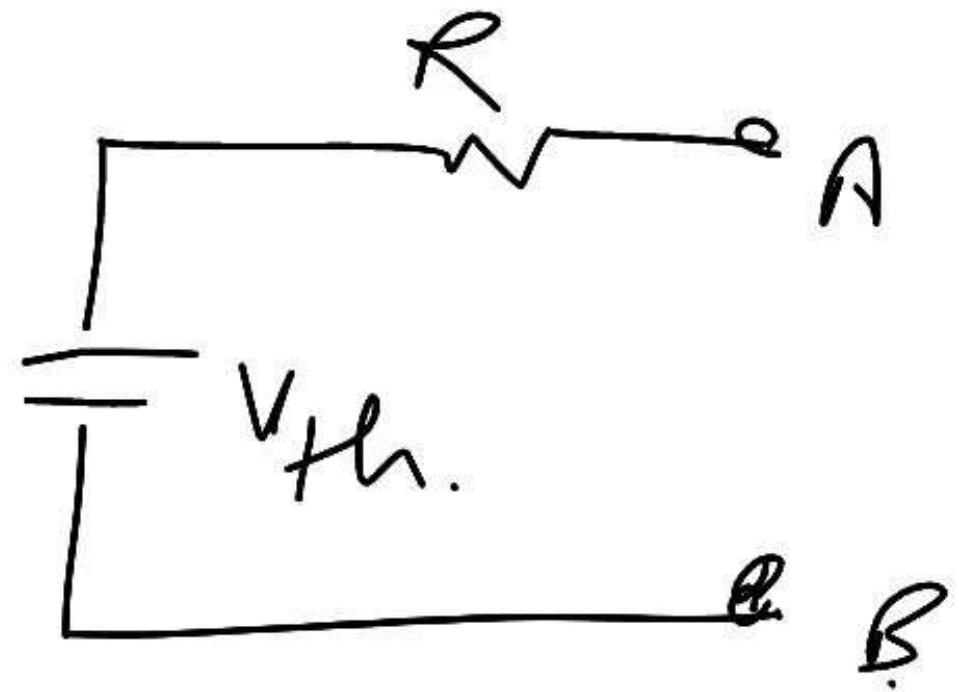

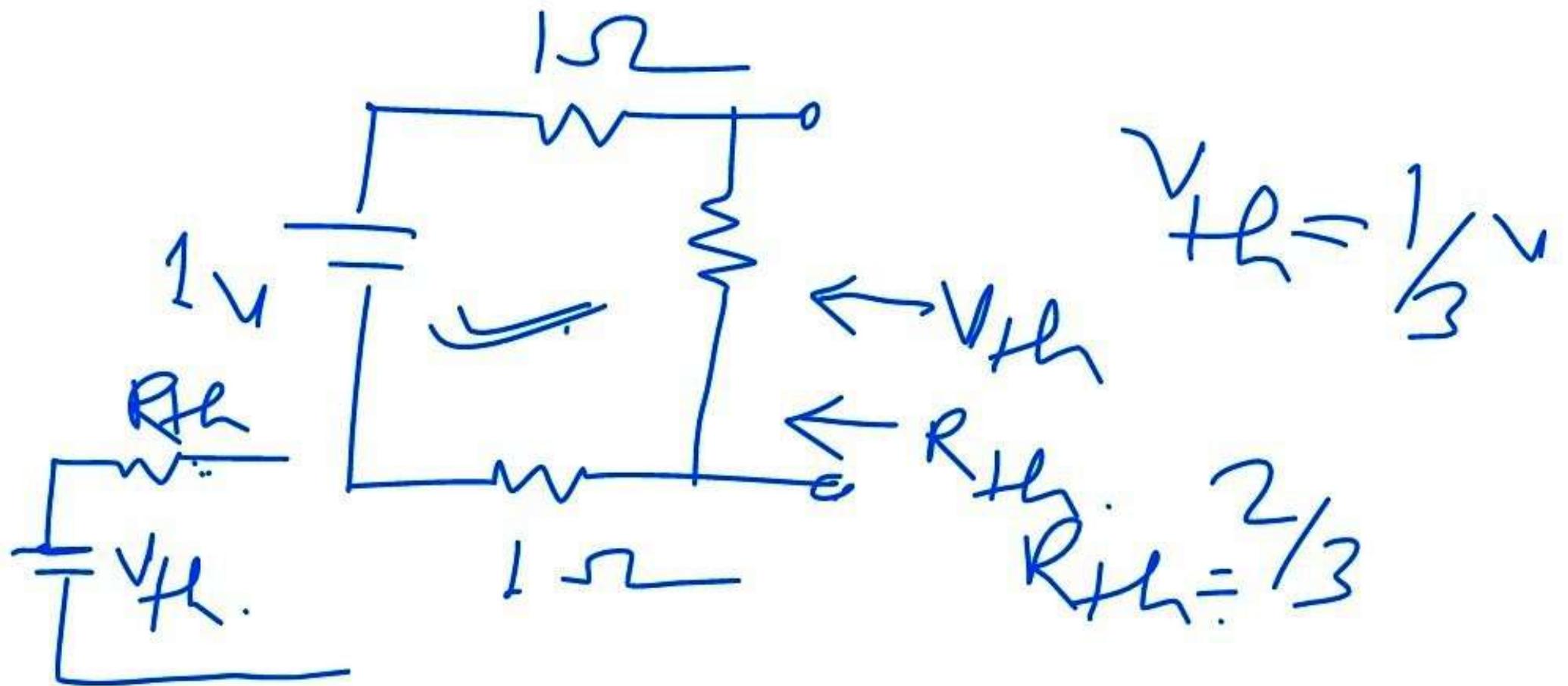

② At least one independent
& one dependent source.

- ① V_{th}
- ② I_{sc}
- ③ R_{th}

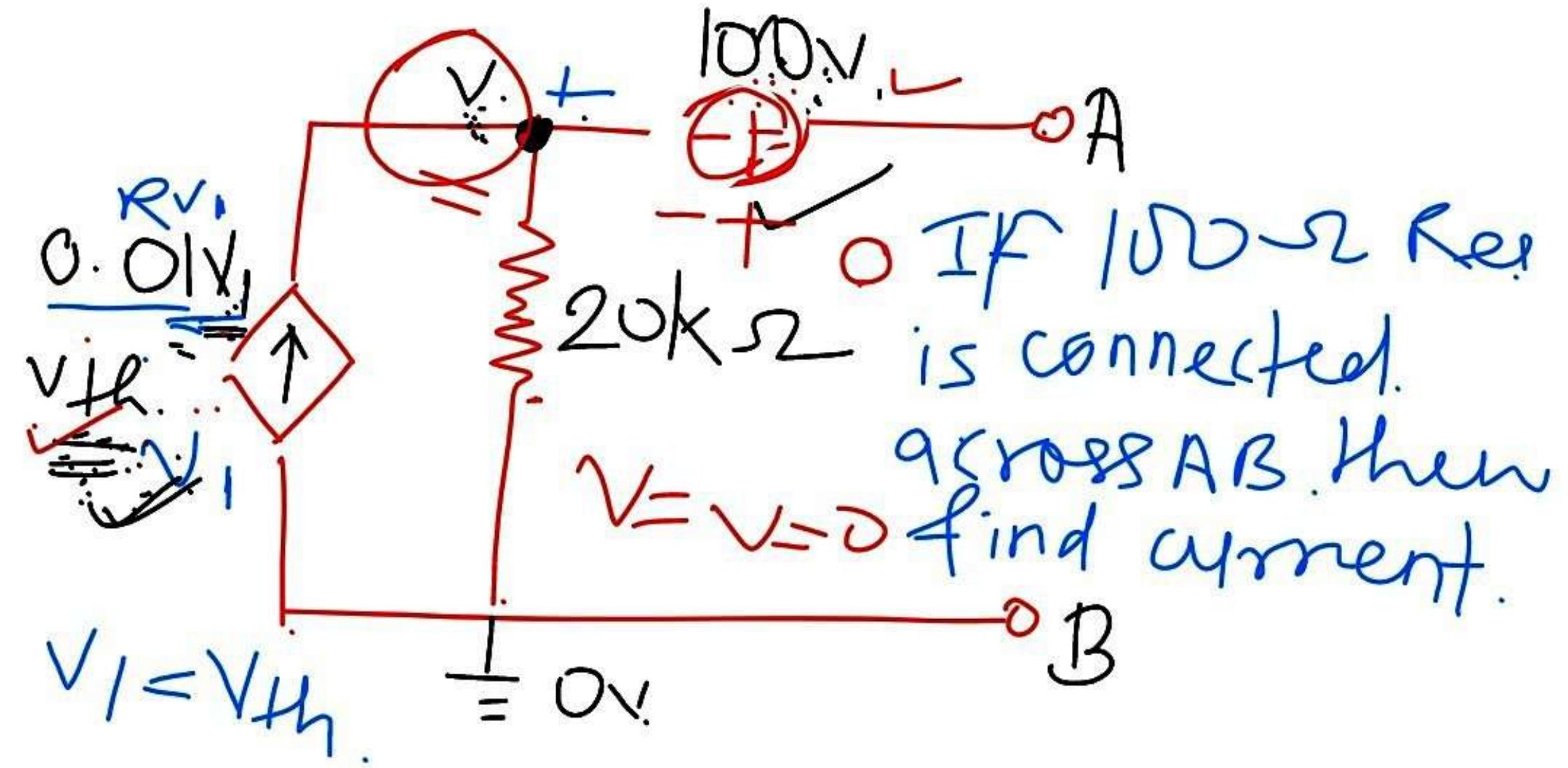



Assume $x_1 = V_{th}$. —①

By $KXL \Rightarrow V + 100 - x_1 = 0$

$$V + 100 - V_{th} = 0$$

$$\boxed{V = V_{th} - 100}$$

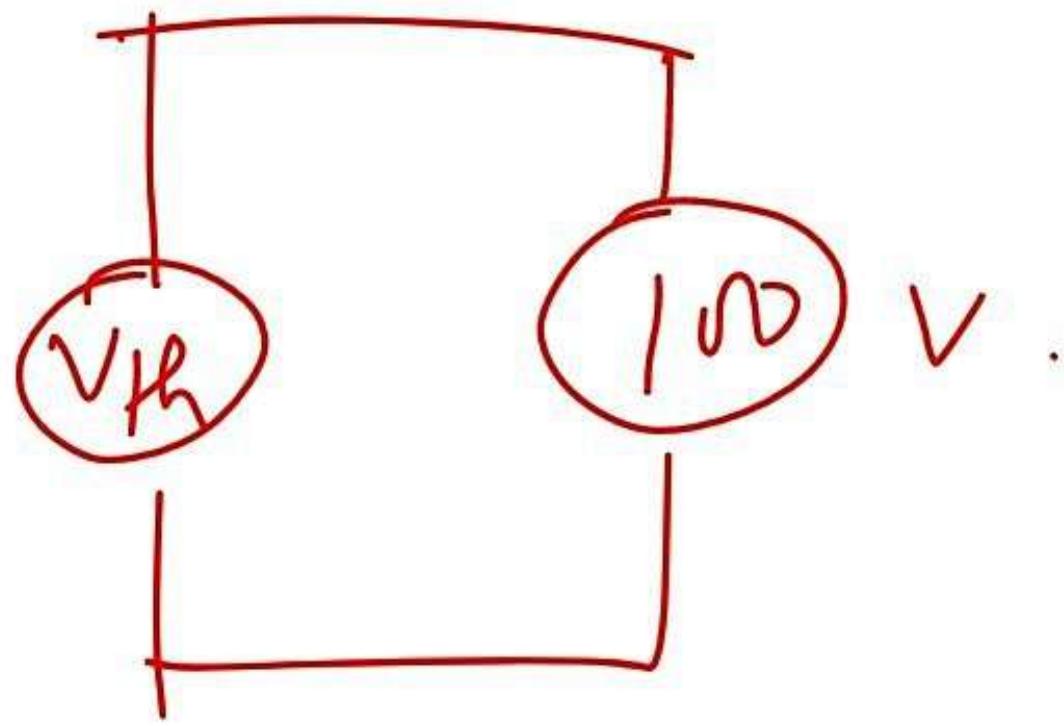

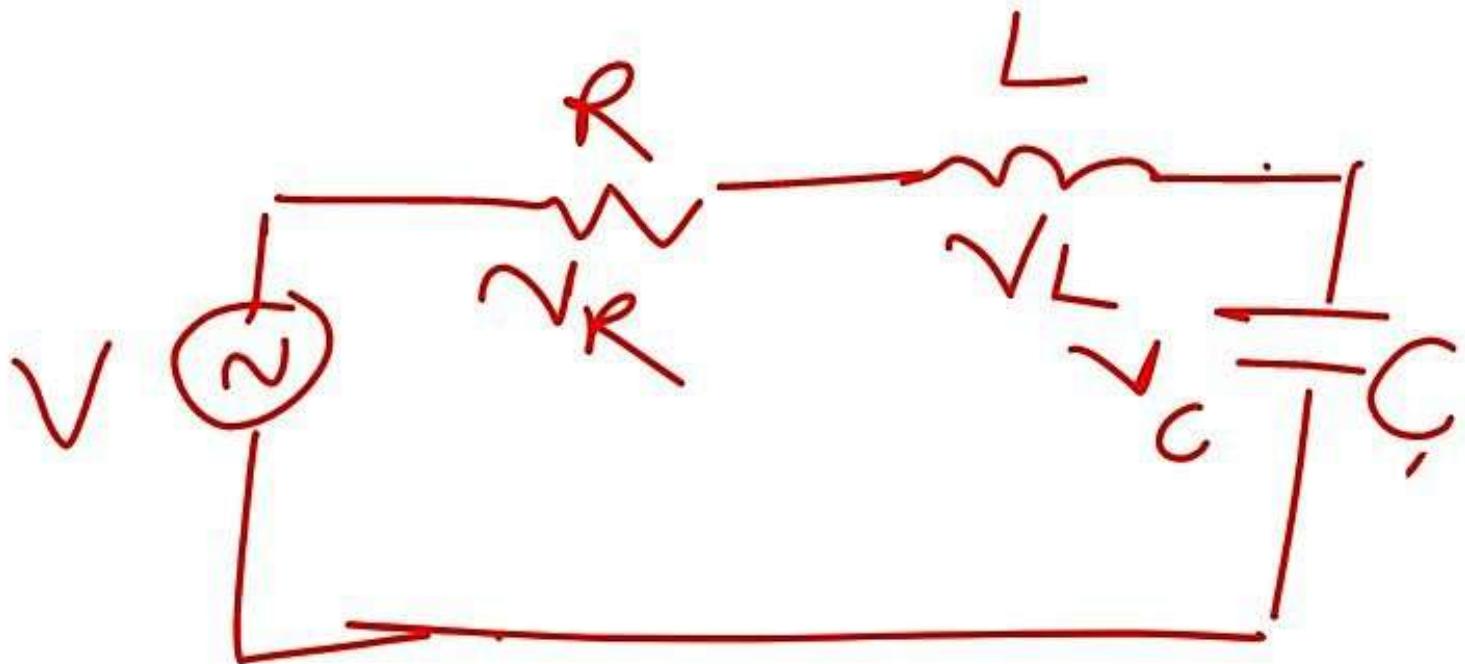


$$V = V_R + V_L + V_C$$

Nodal

$$= 0.01v_1 + \frac{v}{20k} + 0 = 0$$

$$-200v_1 + v = 0$$
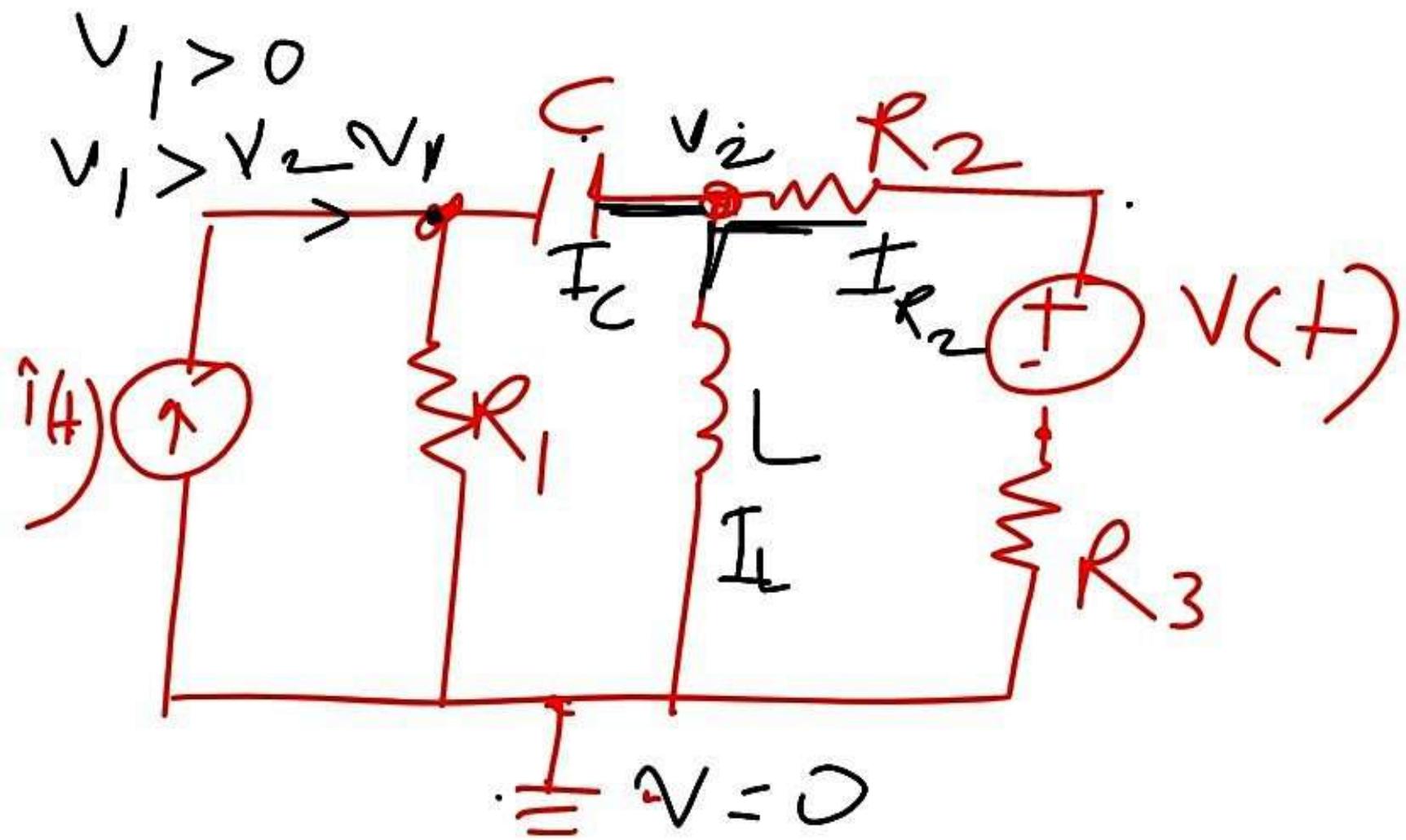
$$-200v_1 + \frac{v}{20k} - 100 = 0$$
$$\frac{v}{20k} - 100 = 0$$




$$-200V_1 + V_1 - 100 = 0$$

$$-199V_1 = 100$$

$$V_1 = \frac{100}{-199} = V_{th}$$

- 502.5mV

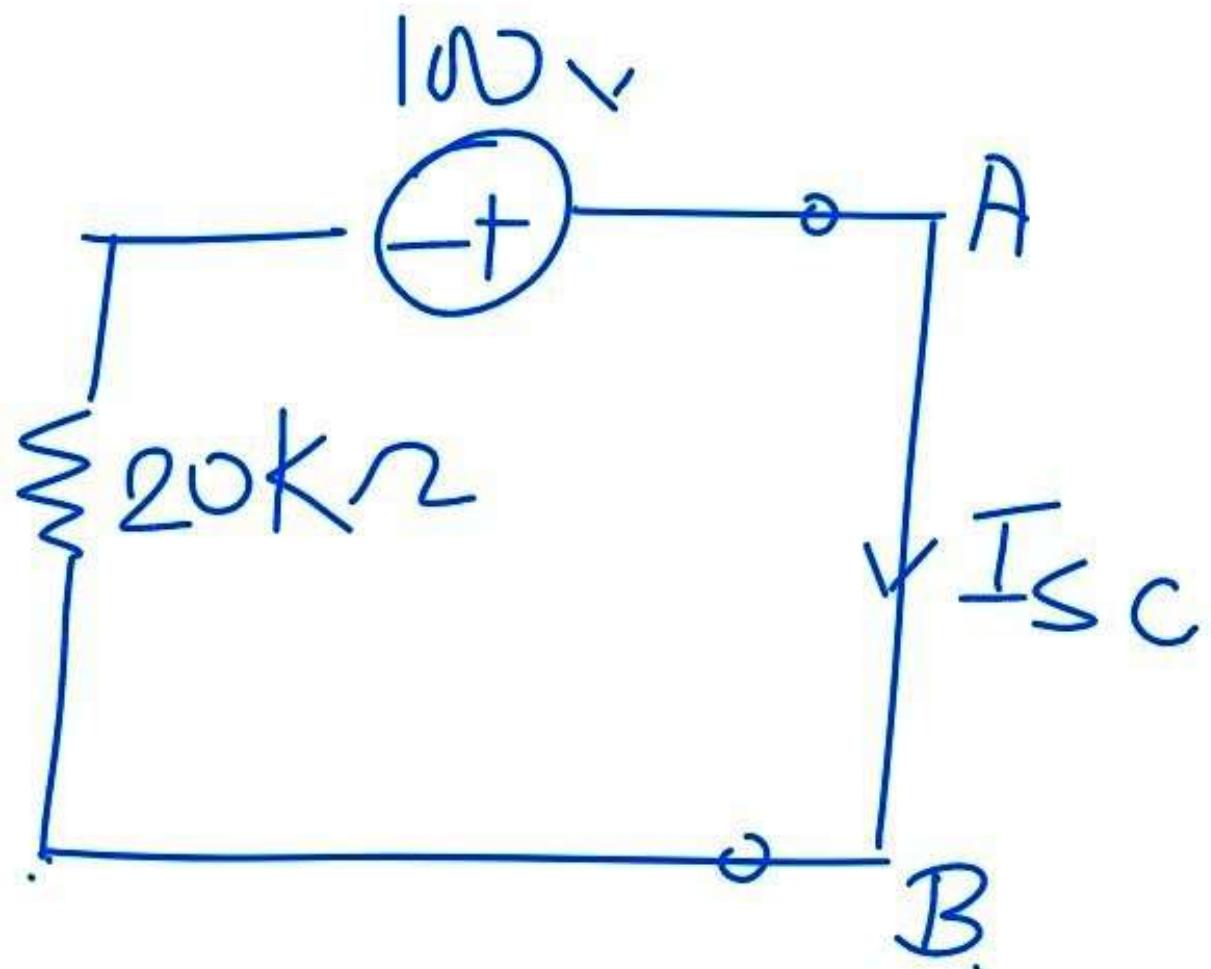

$$V_i = 0$$

$$\text{By KVL} = 100 - 20 \times 10^3 I_{SC}$$

$$I_{SC} = 5 \text{ mA}$$

$$R_{th} = \frac{V_{th}}{I_{SC}} = \frac{-5.02 \cdot 5 \text{ mV}}{5 \text{ mA}}$$

$$R_{th} = -100.5 \Omega$$

The presence of dependent sources in the network makes R_{th} sometimes to have a negative value.


Note

→ All are dependent
sources. (Depat N/ω)

$\checkmark V_{th} = 0$ $\checkmark I_{sc} = 0$


$R_{th} \neq 0$

$I_L = 0 \text{ Amp.}$

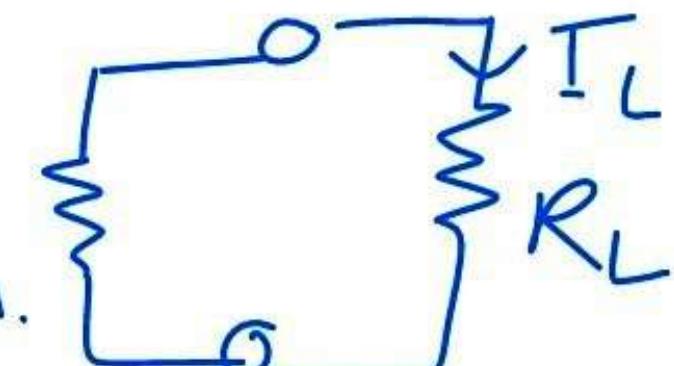

- Maximum power Transfer
- Theorem

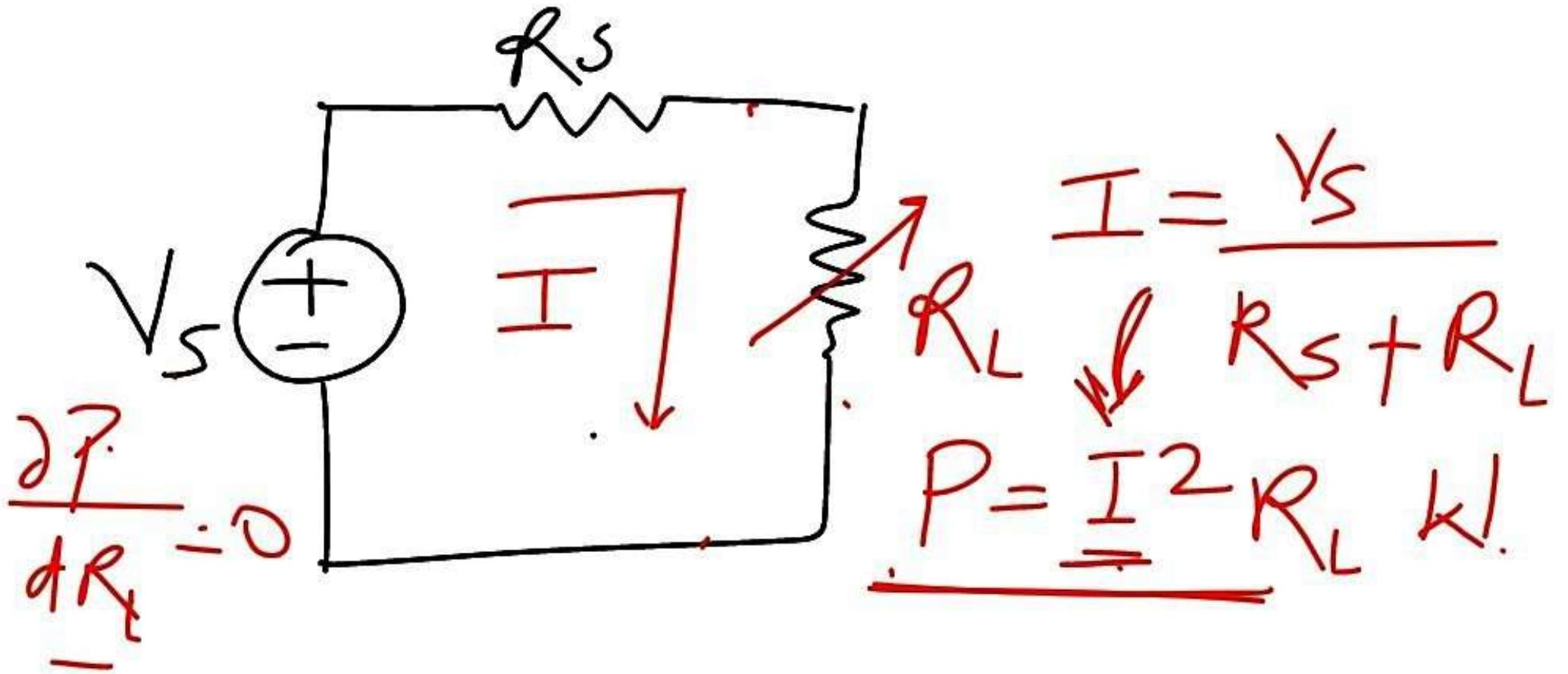① Under Variable Load
 $\Rightarrow R_s$ and R_L




$$P = I^2 R_L \Rightarrow I = \frac{V_s}{R_s + R_L}$$

$$P = \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2}$$

$$R_L = 0 \rightarrow$$

$$R_L = \infty \rightarrow$$

$$P_{\min}$$

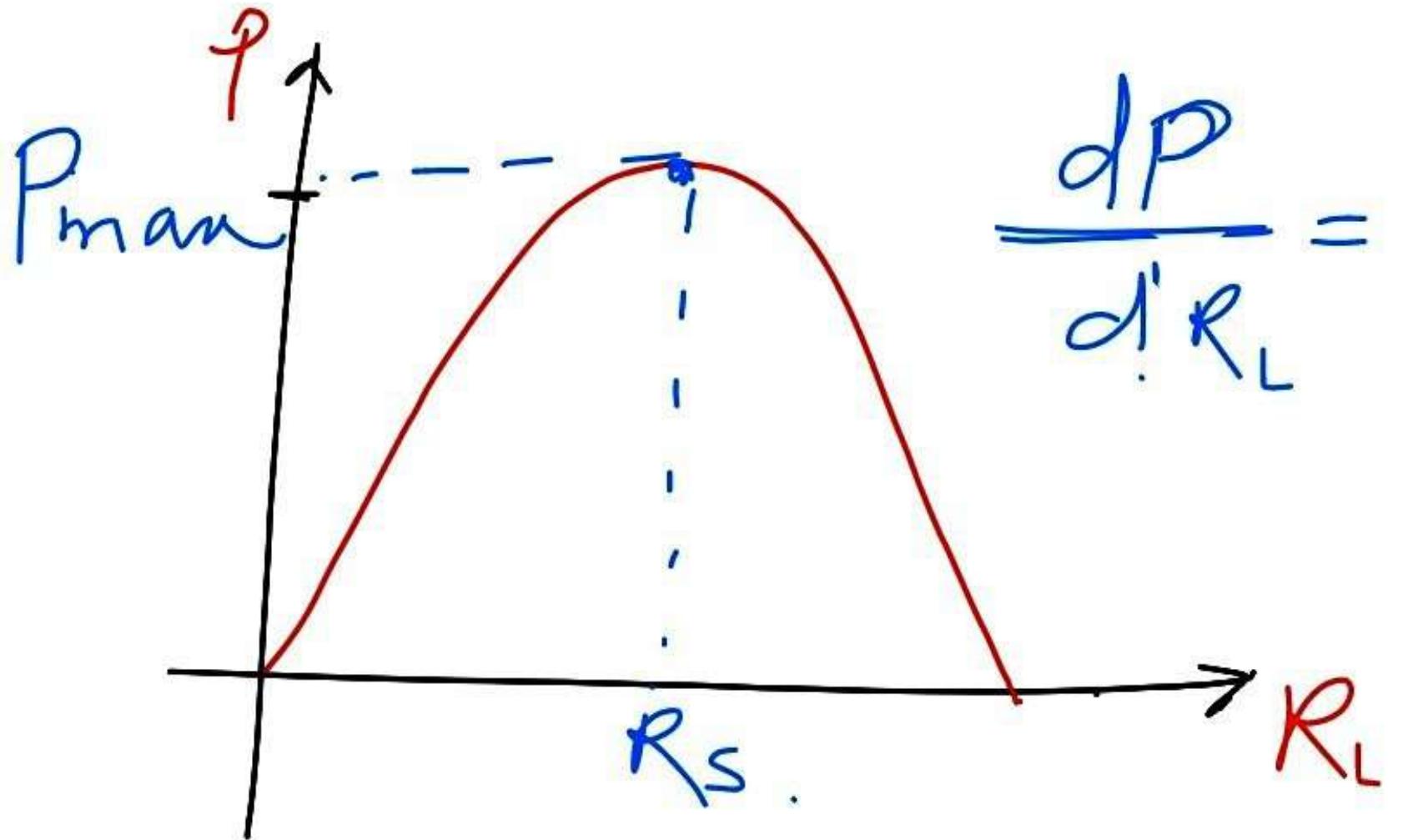

$$\frac{dP}{dR_L} = 0$$

$$\frac{dP}{dR_L} = \frac{\sqrt{s}(R_S + R_L)^2 \cdot 1 - R_L \cdot 2(R_S + R_L)}{(R_S + R_L)^2} \cdot \sqrt{s^2}$$

$\Rightarrow \frac{\sqrt{s^2} [(R_S + R_L)^2 \cdot 1 - R_L \cdot 2(R_S + R_L)]}{(R_S + R_L)^2}$

$$\frac{Vs^2 \left[(R_s + R_L)^2 \cdot 1 - R_L^2 (R_s + R_L) \right]}{(R_s + R_L)^2} = 0$$

$$\Rightarrow Vs^2 \left[(R_s + R_L)^2 \cdot 1 - R_L^2 (R_s + R_L) \right] = 0$$

$$(R_s + R_L)^2 - R_L \cdot 2(R_s + R_L)$$

$$(R_s + R_L)^2 = R_L \cdot 2(R_s + R_L)$$

$$R_s + R_L = 2R_L$$

$$R_s = 2R_L - R_L \Rightarrow \boxed{R_s = R_L \cdot 2}$$

$$P_{\text{max}} = P \Big|_{R_s = R_L}$$

$$= \frac{V_s^2 R_L}{(R_s + R_L)^2}$$

\Rightarrow

$$P = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$

$$\Big|_{R_s = R_L}$$

$$\frac{V_s^2 R_s}{(R_s + R_s)^2}$$
$$= \frac{V_s^2 R_s}{4 R_s^2} =$$

$$\frac{\underline{V_s^2}}{\underline{4R_s}} \text{ Watt.}$$

$$P_{max} = \frac{V_s^2}{4R} \text{ Watt}$$

useful power

$$P_{det} = P_{abs} \leftarrow \begin{matrix} \text{Tellegen's} \\ \text{Thm.} \end{matrix}$$

$$\begin{aligned}
 \underline{\underline{P_T}} &= \underline{\underline{I^2 R_S + I^2 R_L}} \quad | \quad R_L = R_S \\
 &= \frac{\underline{\underline{V_S^2}}}{4R_S} + \frac{\underline{\underline{V_S^2}}}{4R_L} \quad \underline{\underline{\text{Total power}}} \\
 &= \frac{\underline{\underline{2V_S^2}}}{4R_S} = \underline{\underline{\frac{1}{2} \frac{V_S^2}{R_S}}} \quad \text{or.}
 \end{aligned}$$


$$\frac{V_s^2}{2R_L} \text{ Watt} = \frac{V_s^2}{2R_S}$$

$$\eta = \frac{\text{Used forward power}}{\text{Total power}}$$

$$\frac{\gamma_s^2}{4R_s} = \frac{1}{2} = 0.5$$
$$\frac{\gamma_s^2}{2R_s} \because \eta = 50\%$$

The efficiency of maximum power transfer is almost 50%.

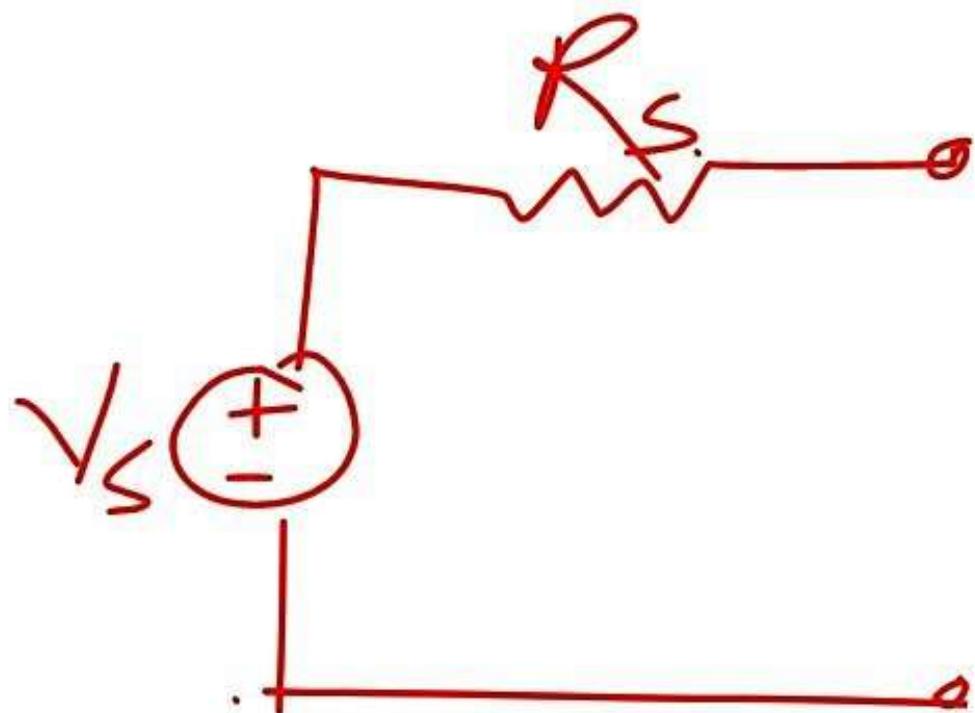$E_n \Rightarrow$ A practical DC source
when short circuited supplies
current of 2.5 Amps if can
provide a power of 80 Watt
to a 20 ohm load. Determine
the open ckt. voltage & R_L for MPT.



$$\begin{aligned}
 & R_L = 20 \Omega \\
 & \frac{V_s}{R_s} = 2.5 \text{ Amp} \\
 & P_{20\Omega} = 80 \text{ Watt} \\
 & I_{20\Omega}^2 R = 80
 \end{aligned}$$

$$I_{R=20}^L (20) = 80 \text{ Watt}$$

$$I_{R=20}^L = \frac{80}{20} = 4$$

$$\frac{\sqrt{s}}{R_s + R_L}$$

$$\underline{I}_{R=20} = \underline{2A} = \frac{\chi_s}{R_s + 20} \Rightarrow \textcircled{2}$$

$$\frac{V_s}{R_s} = 2.5 \quad \text{and} \quad \frac{V_s}{R_s + 20} = 2A$$

$R_s + 20$

$$\left\{ \begin{array}{l} V_s = 2.5 R_s \\ V_s = 2(R_s + 20) \end{array} \right.$$

$$2.5 R_s = 2 R_s + 40$$

$$2.5R_S = 2R_S + 40$$

$$2.5R_S - 2R_S = 40$$

$$\therefore 0.5R_S = 40$$

$$R_S = \frac{40}{0.5}$$


$$R_S = 80 \Omega \quad \checkmark$$

$$\frac{V_S}{R_S} = 2.5$$

$$\frac{V_S}{80} = 2.5$$

$$V_S = 2.5 \times 80$$

$$V_S = 200 \text{ V}$$

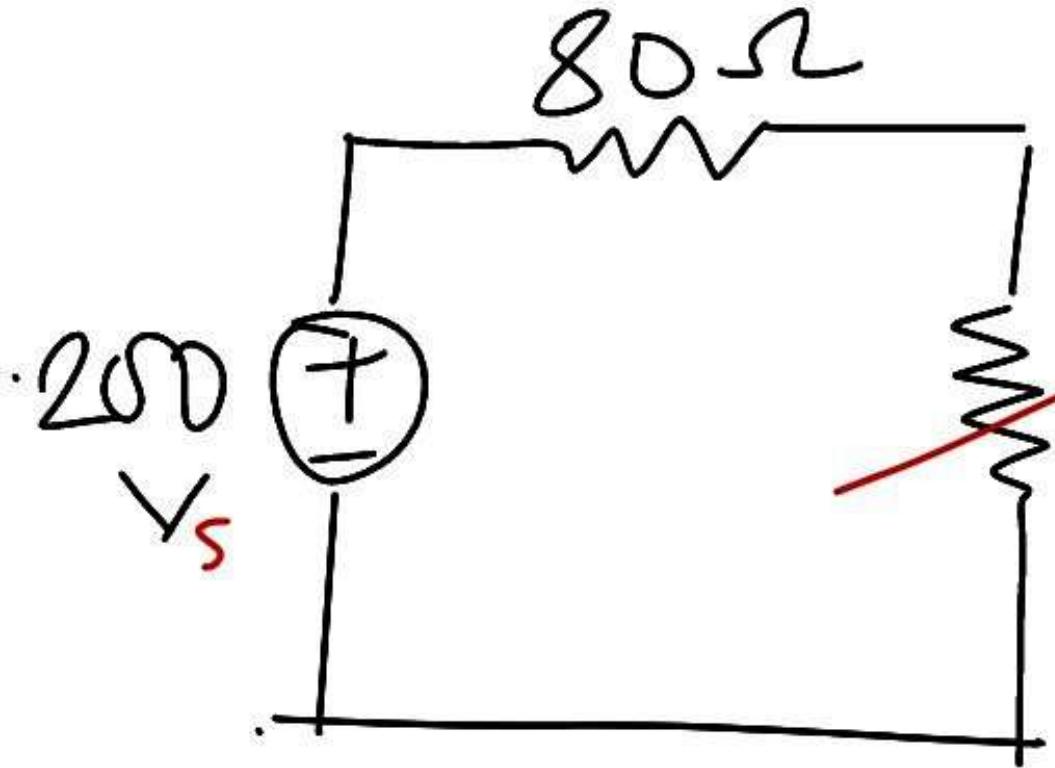


$R_L = R_S$
 $= 80 \Omega$ for MPT

$$P_{\text{max}} = \frac{\gamma s^2}{4R_s}$$

$$= \frac{(200)^2}{4 \times 80}$$

$$P_{\text{max}} = \frac{40000}{320} = \underline{\underline{125 \text{W}}}$$

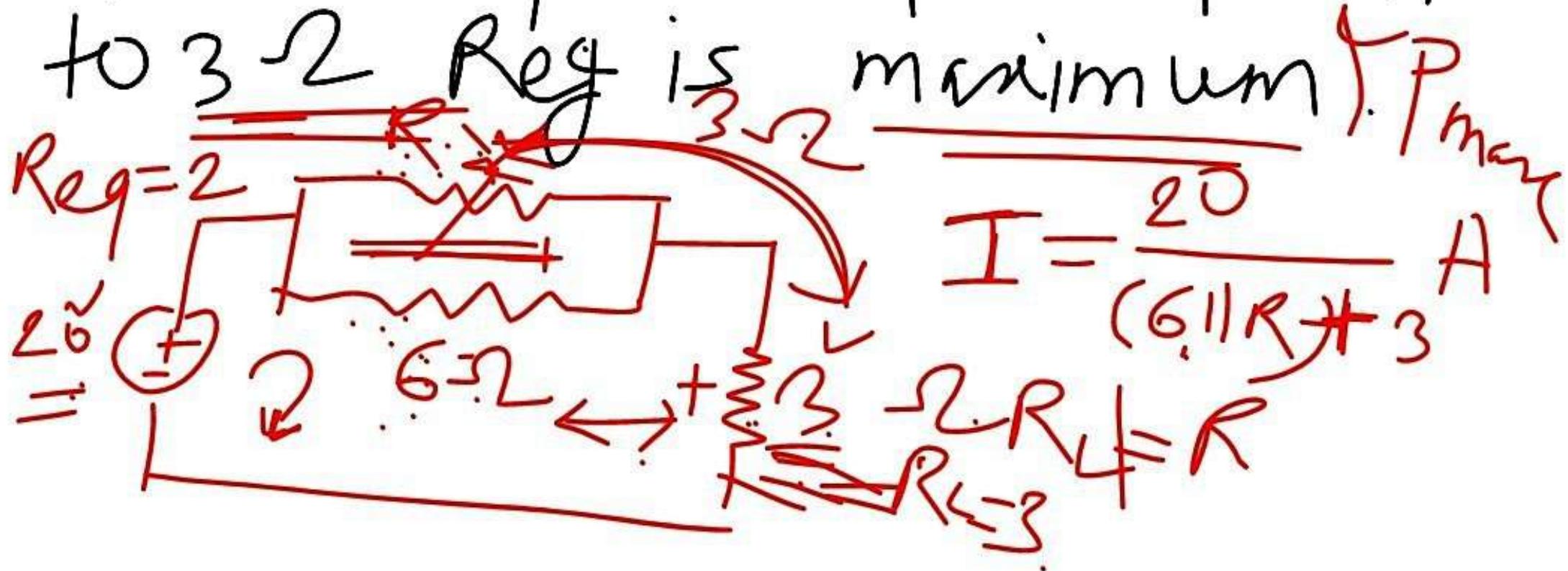② Determine the value of R at which power transferred to 3Ω Reg is maximum P_{max}



$$P_{3\text{m}} = I_{3\text{m}}^2 R_{3\text{m}}$$

$$\begin{aligned} P_{3\text{m}} &= I_{3\text{m}}^2 \cdot 3 \\ &= \left(\frac{20}{R_{\text{eq}} + 3} \right) A \\ &= \end{aligned}$$

$$\begin{aligned} R_{\text{eq}} &= 6 \parallel R \\ &\quad 6 \parallel 3 \\ &= \frac{6 \times 3}{6 + 3} = \frac{18}{9} \\ &= 2 \Omega \end{aligned}$$

$$R = 3\Omega$$


$$R_{eq} = 2\Omega$$

$$I$$

$$R_e$$

$$I = \frac{V}{R}$$

6113

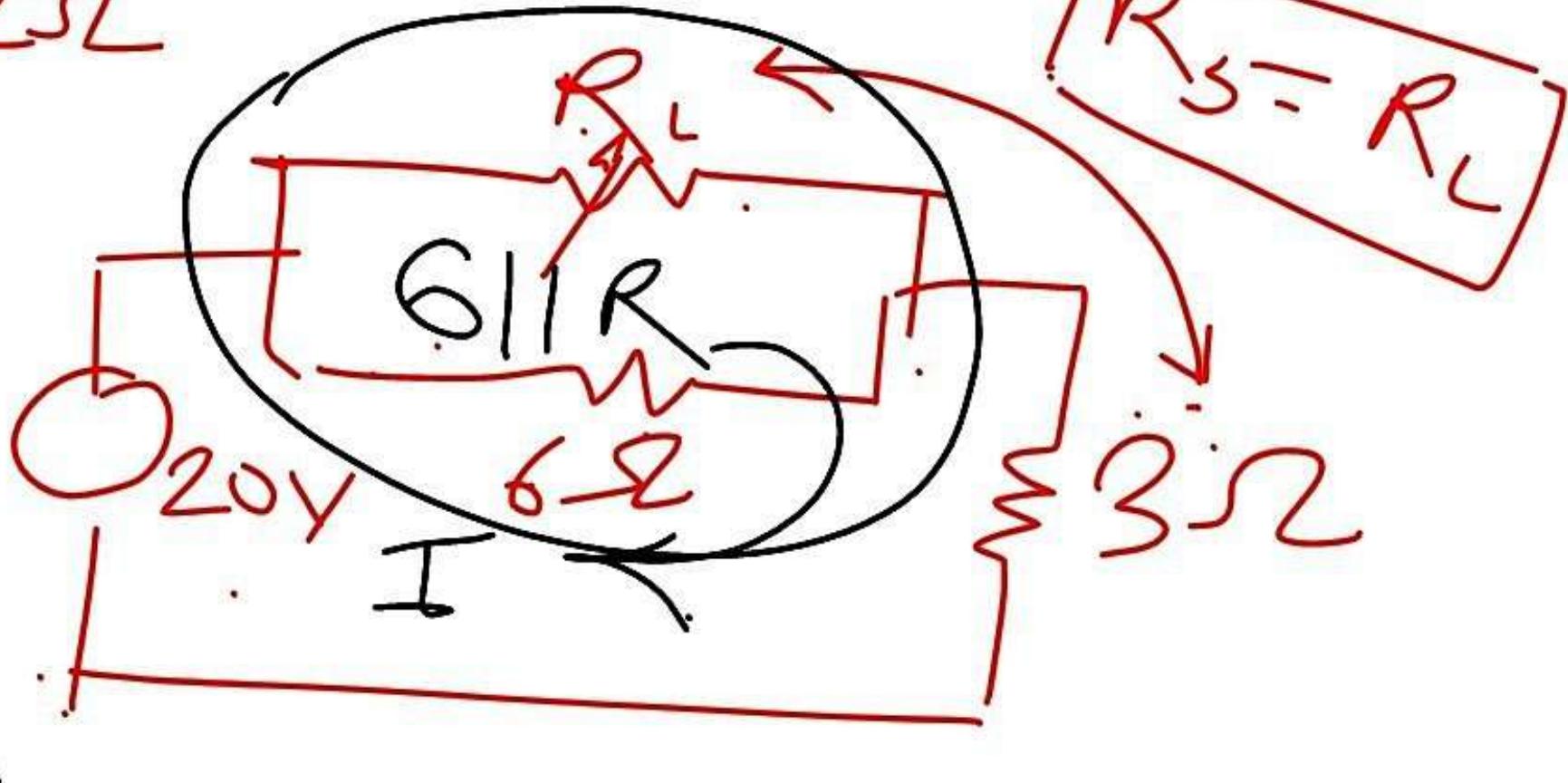

$$I = \frac{V}{R_s + R} \quad R = R_{eq}$$


$$= \frac{V}{3 + (6 || R)}$$

Iman = 4 Amper

$$\therefore \frac{V}{2+3} = \frac{20}{5} = \frac{I^2 R}{4^2 \times 3} = 48 N.$$

$$I = \frac{V_s}{R_{st} + R_L}$$

$$= \frac{20}{3+3} = \frac{20}{6} = 2 \text{ A}$$

$$= \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \text{ A}$$

$$\frac{R_{st}}{3+6} = \frac{R_{st}}{9} = \frac{2}{9} = \frac{2}{9} \text{ A}$$

$$\frac{R_L}{6+6} = \frac{6}{12} = \frac{1}{2} \text{ A}$$


$$R_{st} = 3 + 3 = 6 \Omega$$

$$R_L = 6 \Omega$$

$$R_{in} = 3 \parallel 6 = 2 \Omega$$

$$R_{out} = 6 \parallel 6 = 3 \Omega$$

$$V_o = 2 \times 18 = 36 \text{ V}$$

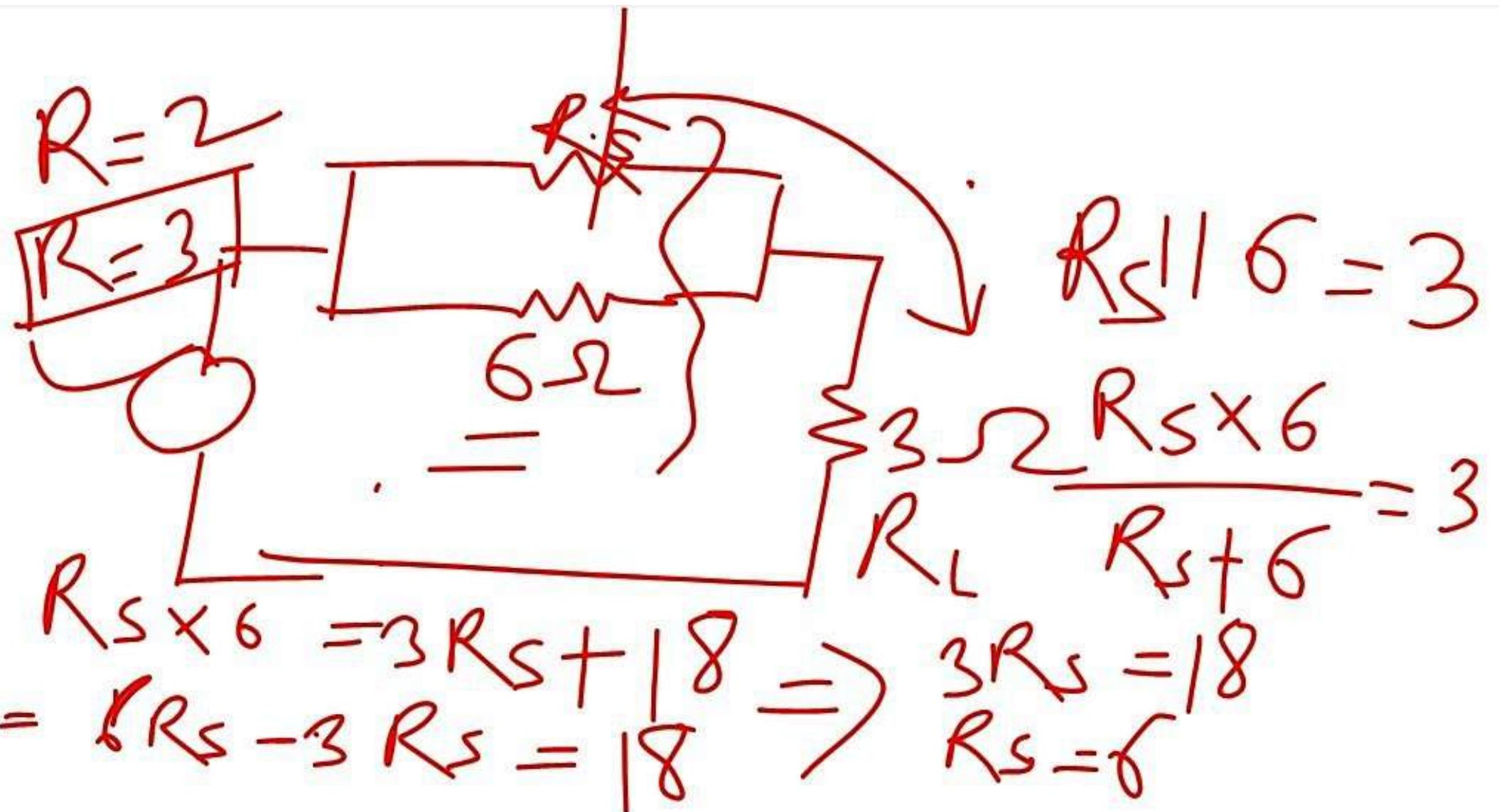

$$r_s^2 [(R_s + R_L)^2 + (X_s + X_L)^2] = 0$$

$$\frac{dP}{dX_L} = 0 \quad R_L \cdot 2(X_L + X_S)$$

$$\frac{[(R_s + R_L)^2 + (X_s + X_L)^2]^2}{X_L} = 0$$

$$R_E \geq (x_s + x_L) = 0$$

$$\therefore x_s + x_L = 0$$

$$P_{\max} = P \Big|_{x_s + x_L = 0}$$

$$\textcircled{1} \quad \underline{R_L} = \sqrt{R_s^2 + (x_s + x_L)^2} \quad \Omega$$

$$\textcircled{2} \quad \underline{x_s + x_L} = 0$$

③ Both R_L & X_L are varied
simultaneously.

$$\underline{R_L} = \sqrt{\underline{R_s}^2 + (\underline{x_s} + \underline{x_L})^2}$$
$$\underline{x_s} + \underline{x_L} = 0$$

case valid at a time.


$$R_L = R_S$$

$$X_L = -X_S$$

$$Z_L = Z_S^*$$

Pmax | $Z_S \neq X_L$
 $R_L = R_S =$
 $X_L = -X_S$
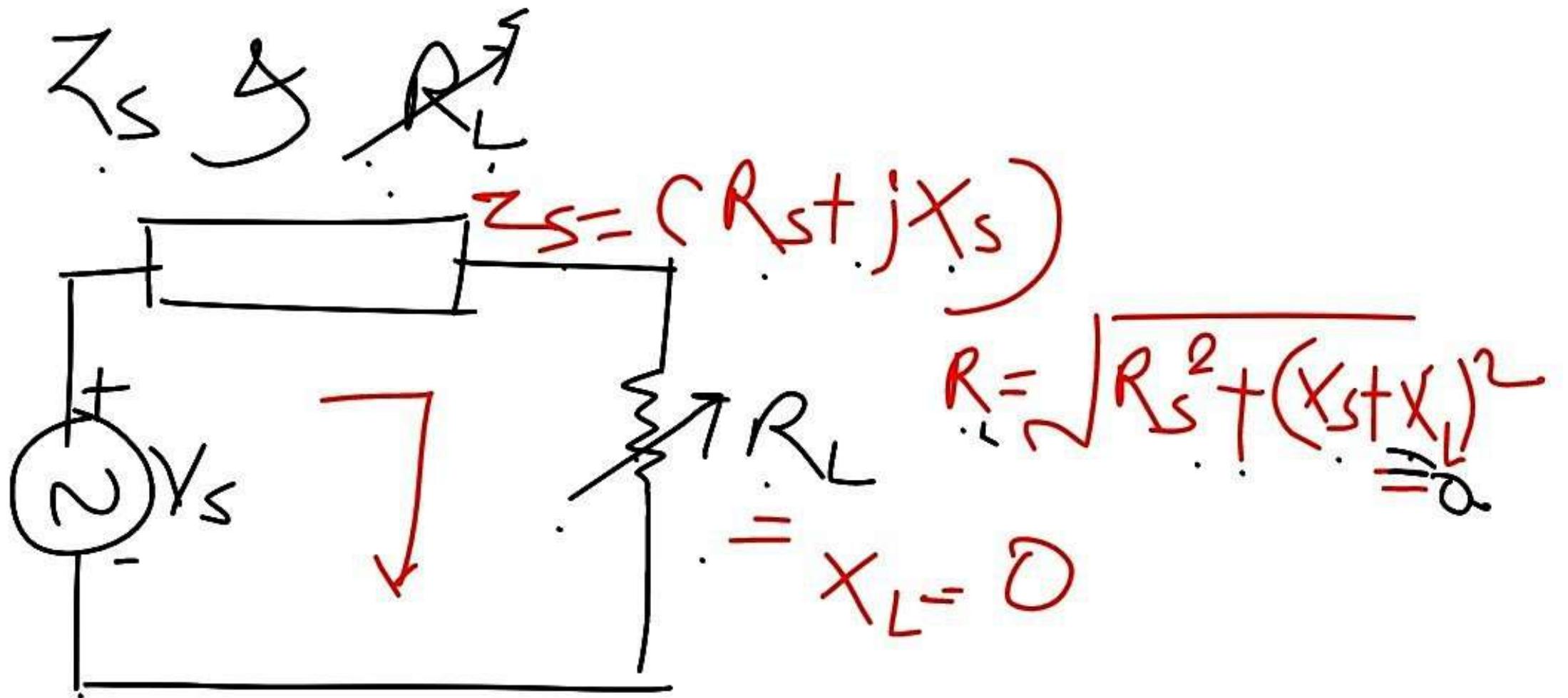
$$= \frac{V_S^2}{4R_E} = \frac{V_S^2}{4R_S}$$




$$R = \sqrt{R_s^2 + X_s^2} \quad -2$$

$$R_L = |R_s + jX_s| \quad | \checkmark$$

$$\boxed{R_L = |Z_s|}$$

$$P_{\text{max}} \mid R_L = |Z_s|$$

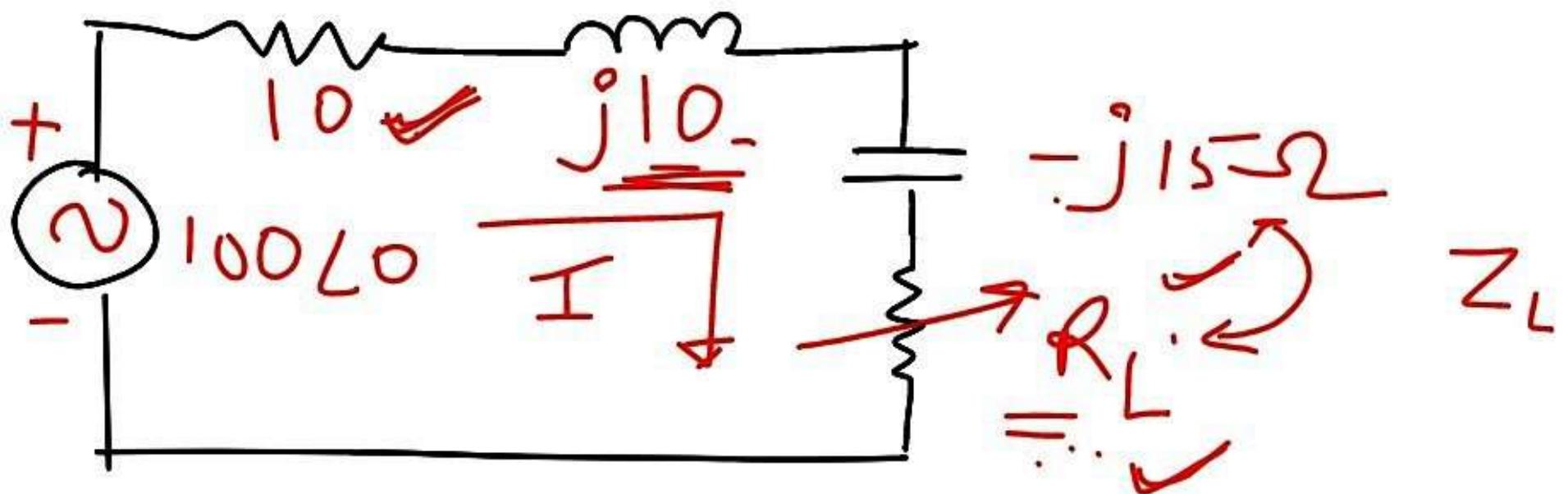
Q. Determine the max power transfer to R_L




$$\begin{aligned} Z_L &= (R_L - j|S|) \\ &= R_L + j(-|S|) \\ &= R_L + jx_L \quad |_{x_L = -|S|} \\ R_L &= \sqrt{R_S^2 + (x_L + x_S)^2} \end{aligned}$$

① klahan Z_S & Z_L .
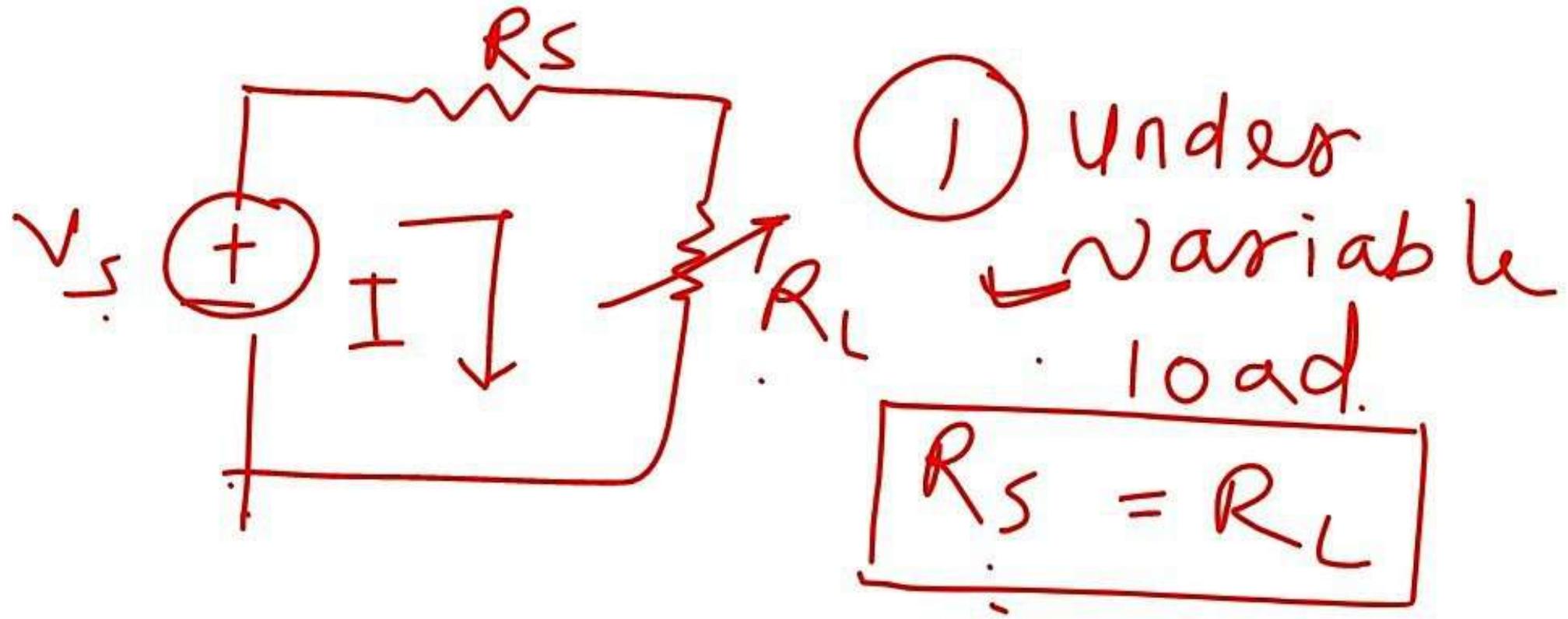
$$P = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} W.$$



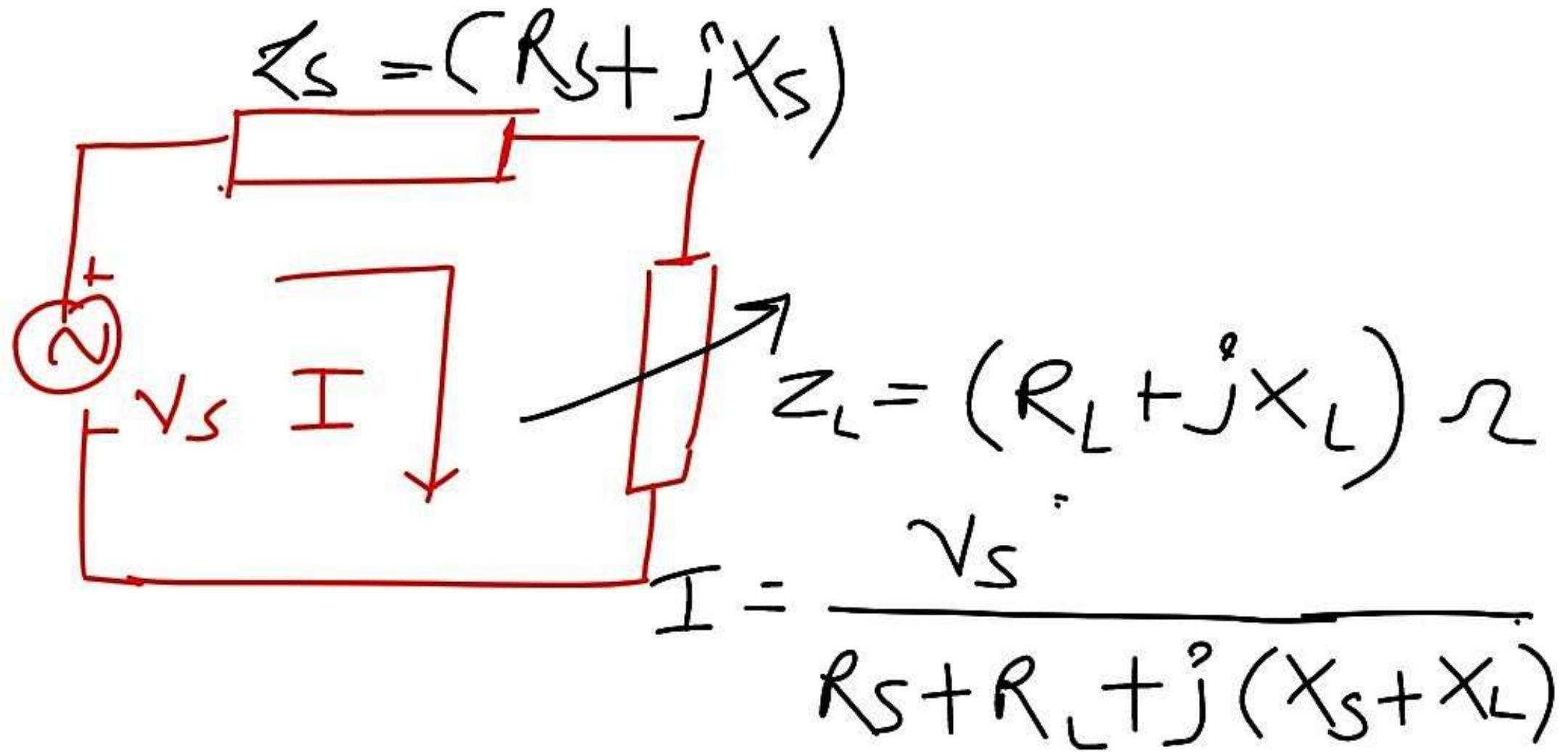

$$P = I^2 R_L$$

$$P = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \text{ Watt}$$

$$\boxed{\frac{dP}{dR_L} = 0}$$

for MPT
 R_L is variable

R_L is variable.

$$R_L = \sqrt{R_s^2 + (x_s + x_L)^2} \Omega$$

$$P_{max} = P |$$

$$R_L = \sqrt{R_s^2 + (x_s + x_L)^2}$$

$X_L \Rightarrow$ is variable.

$$\frac{dP}{dX_L} = 0$$

$$X_S + X_L = 0$$

$P_{max} | P_{at} X_S + X_L = 0$

R_L & x_L are varying.

$$\boxed{Z_L = Z_s^*}$$

$$R_L = R_s \text{ & } x_L = -x_s.$$

$$\begin{array}{c} P_{\max} \\ | \\ \text{at} \end{array} \quad R_L = R_s$$

$$R_L = \sqrt{R_s^2 + (X_S + X_L)^2}$$

$$X_S + X_L = 0$$

$$Z_L = Z_S^*$$


$$R_L = R_S$$

$$X_S = -X_L$$

$$Z_L = R_L + jX_L = R_S - jX_S$$

$$\begin{aligned} X_L &= \underline{X_S} \\ R_L &= R_S \end{aligned} \quad \left. \right\}$$
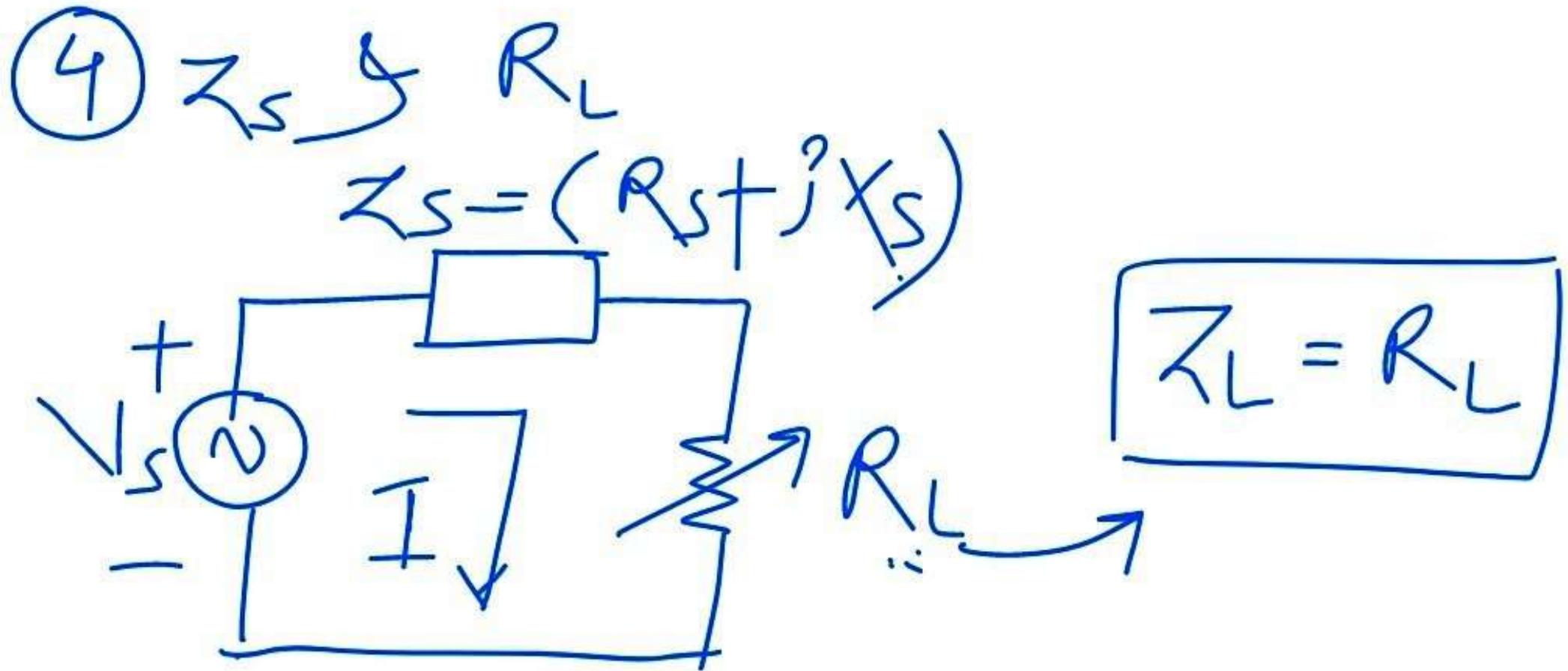
$$\frac{\underline{V_S}^2}{4R_L} = \frac{\underline{V_S}^2}{4R_S} \text{ Watt.}$$




$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$$

At $X_L = 0$

$$R_L = \sqrt{R_s^2 + X_s^2} \Omega$$

$$R_L = |R_s + jX_s| \Rightarrow R_L = |Z_s|$$

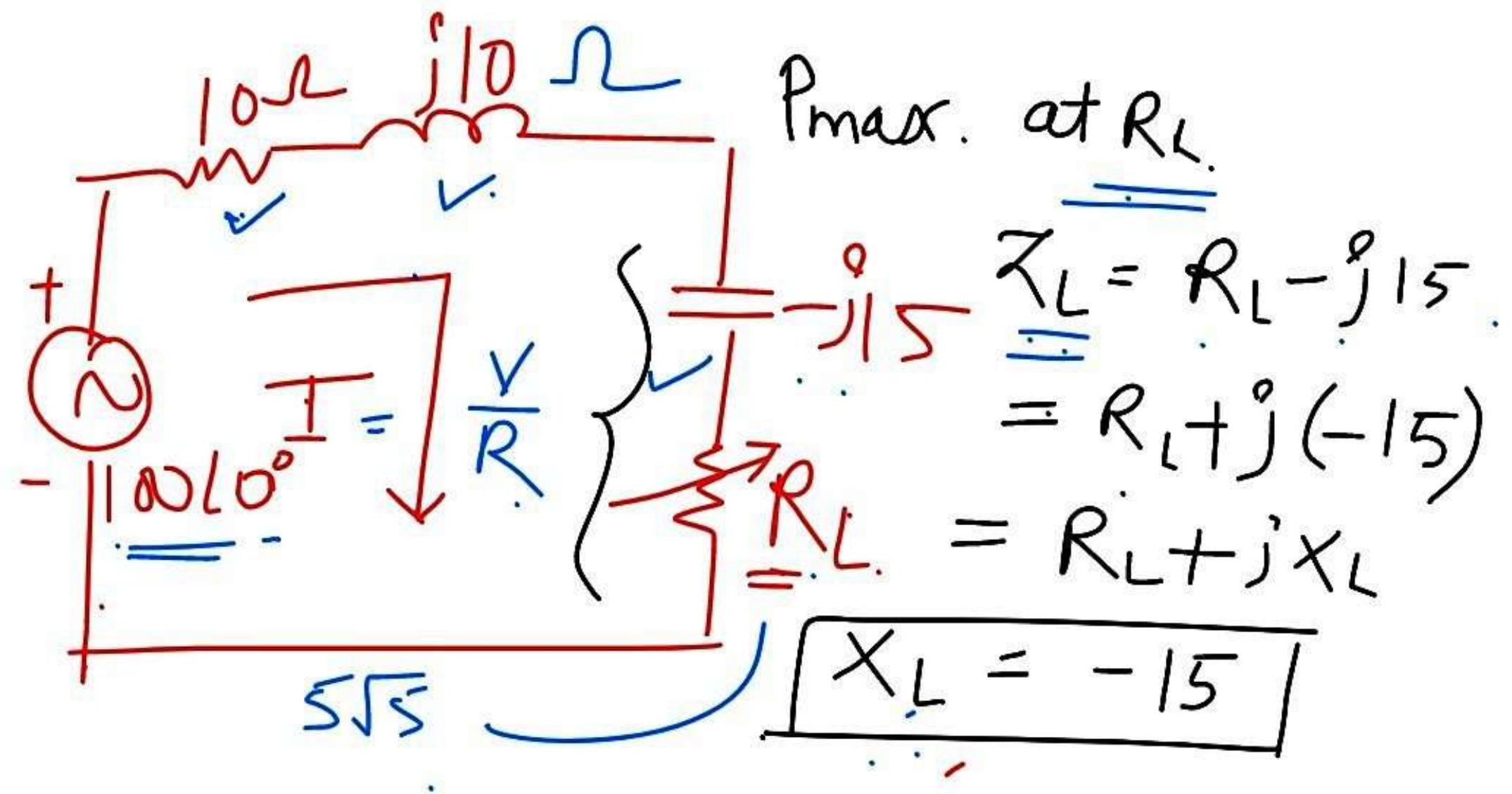

for MPT

$$R_L = \sqrt{R_s^2 + (X_L + \underline{X_s})^2}$$

$$= \sqrt{10^2 + (-15 + 10)^2}$$

$$= \sqrt{10^2 + (-5)^2} = 5\sqrt{5} \Omega$$


$$I = \frac{100\angle 0}{10 + j10 - j15 + 5\sqrt{5}} \Rightarrow \frac{100\angle 0}{10 + 5\sqrt{5} - j5}$$

$$P_{max} = I^2 R_L$$

$$P_{max} = \left| \frac{100\angle 0}{21 + 18 - j5} \right|^2 \cdot 5\sqrt{5}$$

$$P_{\text{mag}} = \underline{\underline{236 \text{ Watt}}}$$

$$= 4.59 \angle 13.28$$

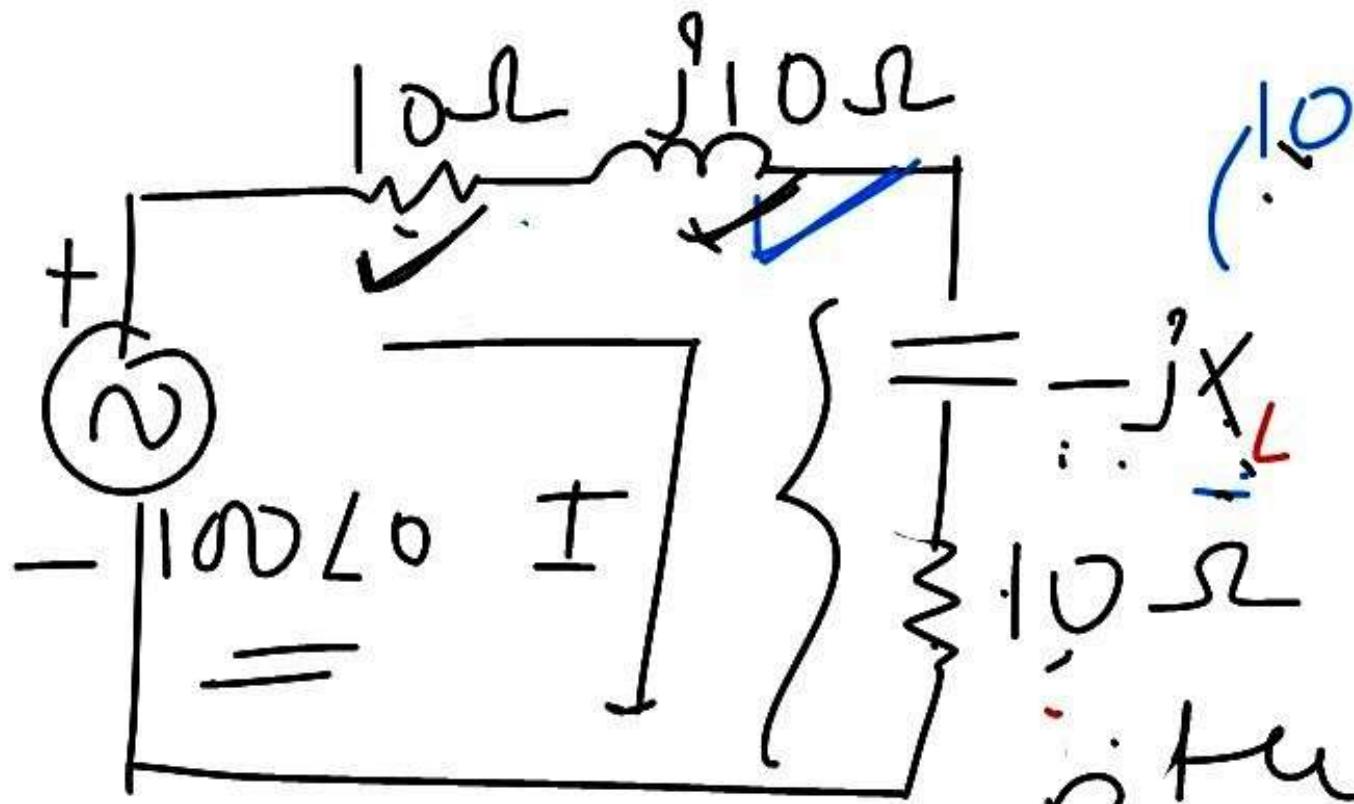

Determine
the value
of X_L

for which power
transfer to $\underline{R_L}$ load resistor is
max.

$$\begin{aligned}
 Z_L &= 10 - jX_L \\
 &= 10 + j(-X_L) \\
 &= R_L + jX_L \quad \Omega
 \end{aligned}$$

for MPT $\frac{X_S + X_L = 0}{10 - X_L = 0}$

$$X_L = 10$$

$$I = \frac{100 \angle 0^\circ}{10 + j10 - j10 + 10}$$

$$= \frac{100 \angle 0^\circ}{20}$$


$$I = 5 \angle 0^\circ$$

$$P_{\max} = |I|^2 \cdot R_L$$

$$= (5)^2 \times 10$$

$$P_{\max} = 250 \text{ Watt}$$

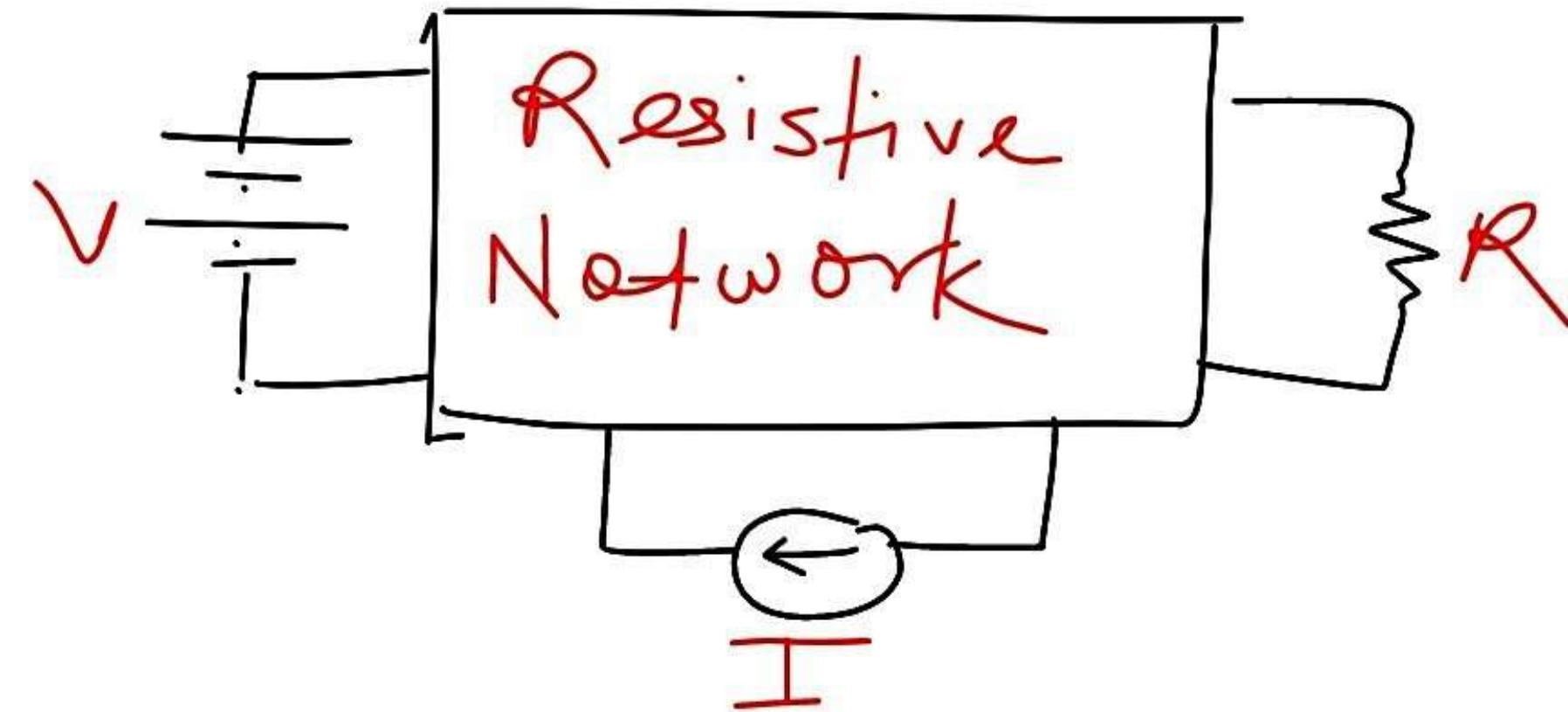A particular resistor R dissipates a power of $4W$ when V alone is active. The same resistor R dissipates a power of $9W$ when I alone is active. The max & min power dissipated by R when both sources are active.



$$P = I_1^2 R \text{ (When } V \text{ is active)}$$

$$P = I_1^2 R$$

$$I_1 = \frac{2}{\sqrt{R}}$$

When I is active.

$$I_2^2 R = 9$$

$$I_2 = \frac{3}{\sqrt{R}}$$

when both } $I_1 + I_2$ or
active . } $I_1 - I_2$

$$P = (I_1 + I_2)^2 R$$


$$= \left(\frac{2}{\sqrt{R}} + \frac{3}{\sqrt{R}} \right)^2 R$$

$$= \left(\frac{5}{(\sqrt{R})} \right)^2 R \Rightarrow 25 \text{ Watt}$$


$$P = (I_1 - I_2)^2 R$$

$$= \left(\frac{2}{\sqrt{R}} - \frac{3}{\sqrt{R}} \right)^2 R .$$
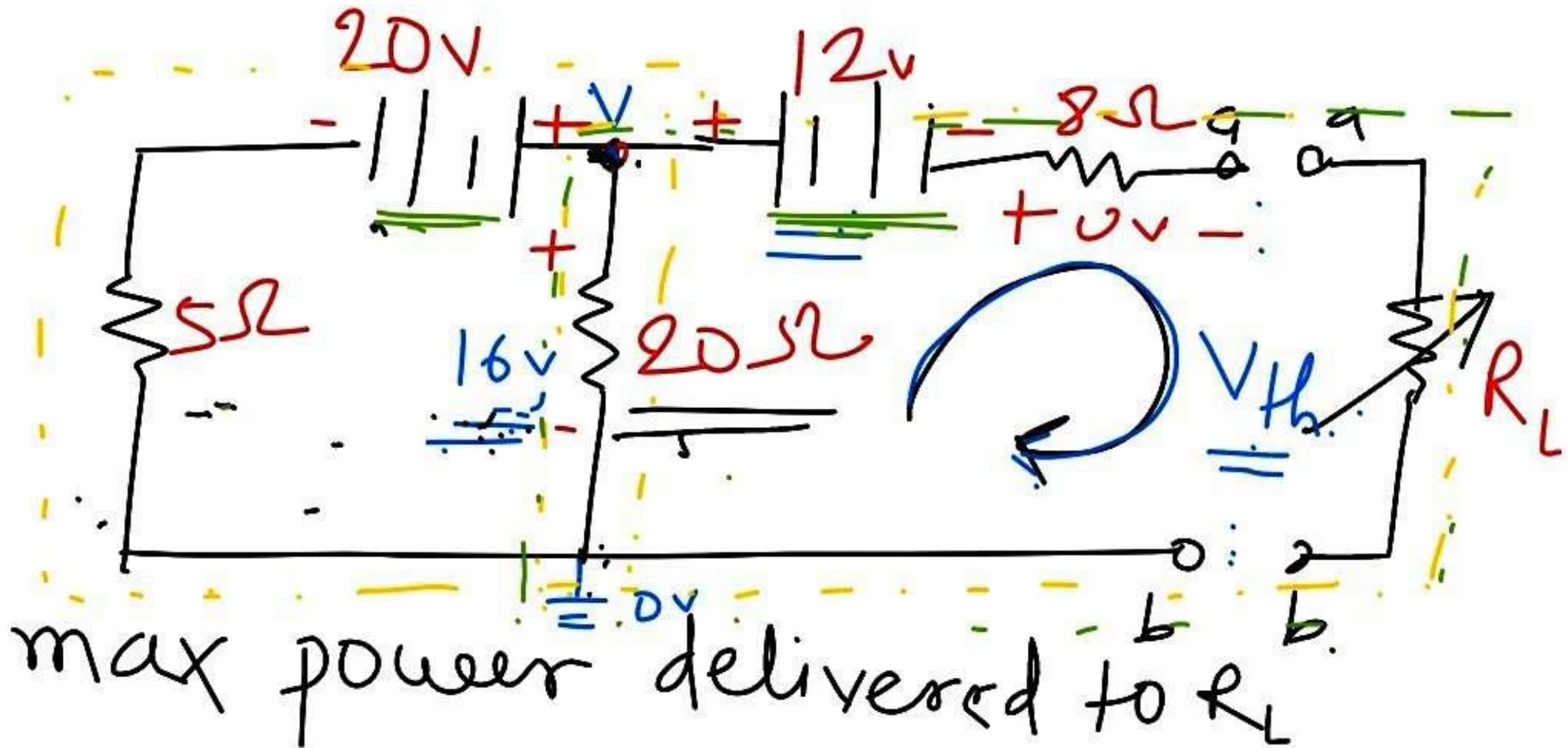
$$= \left(\frac{-1}{\sqrt{R}} \right)^2 \cdot R = 1 \text{ Watt} .$$



By Nodal

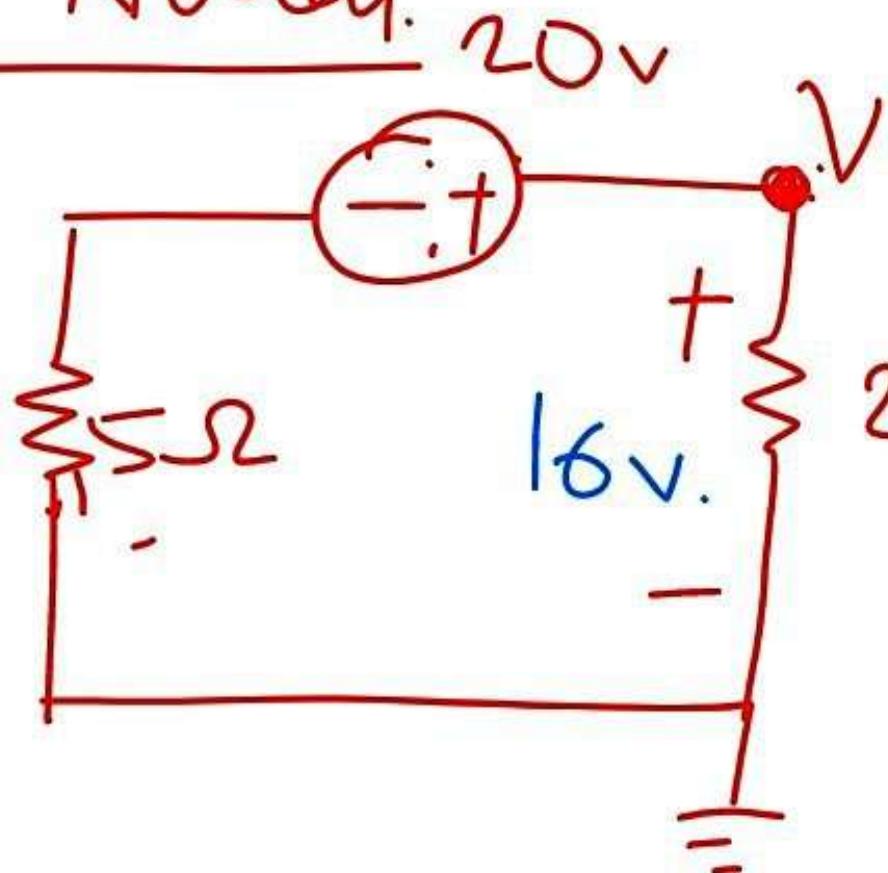

$$\frac{V}{5} - \frac{20}{5} + \frac{V}{20}$$

$$20\Omega = 0$$

$$\frac{4V - 80 + V}{20} = 0$$

$$5v - 80 = 0$$


$$5v = 80$$


$$\boxed{v = 16 \text{ V}}$$

By KVL.

$$16v - 12 - V_{th} = 0$$

$$\boxed{V_{th} = 4 \text{ V}}$$

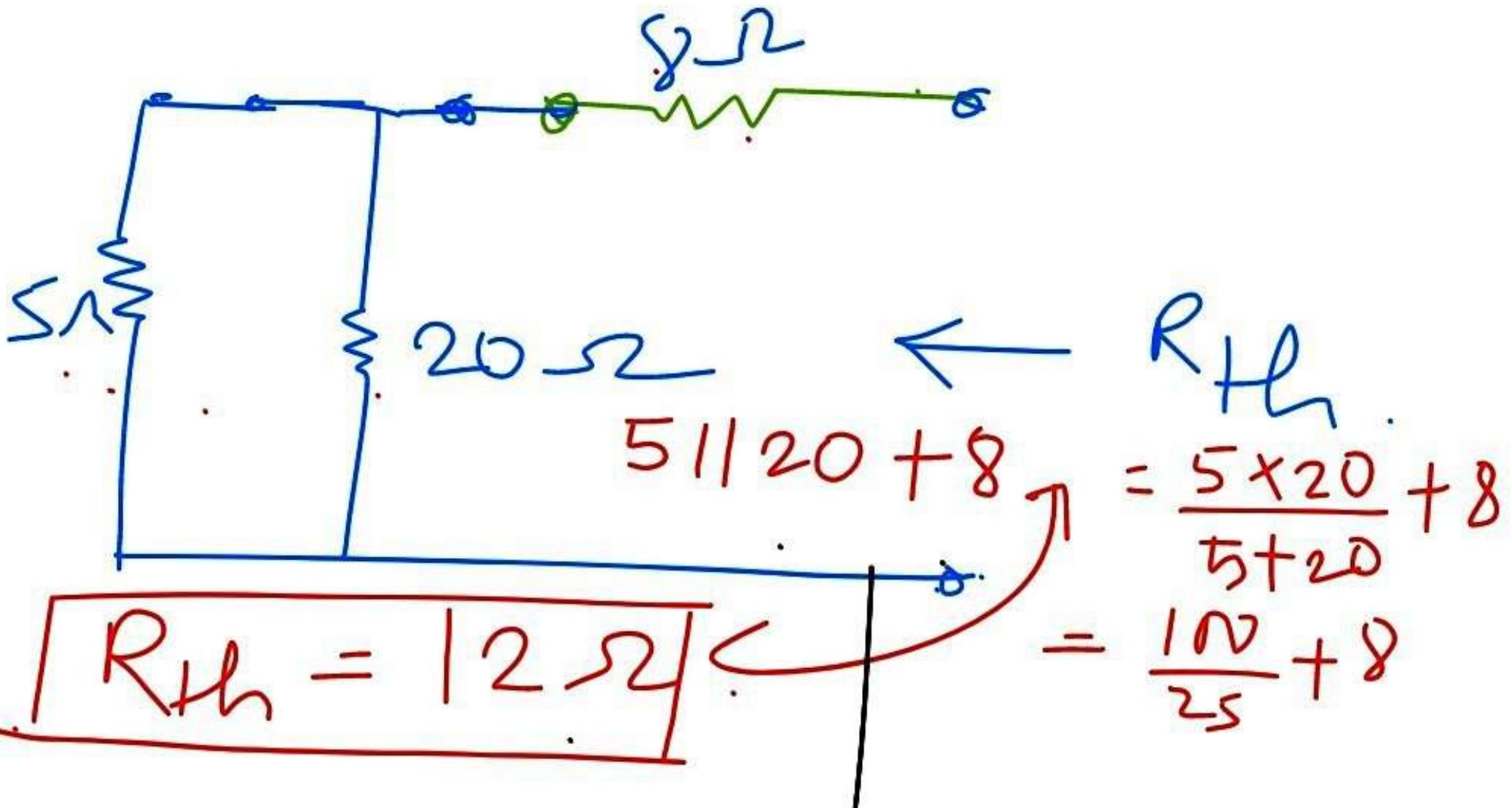

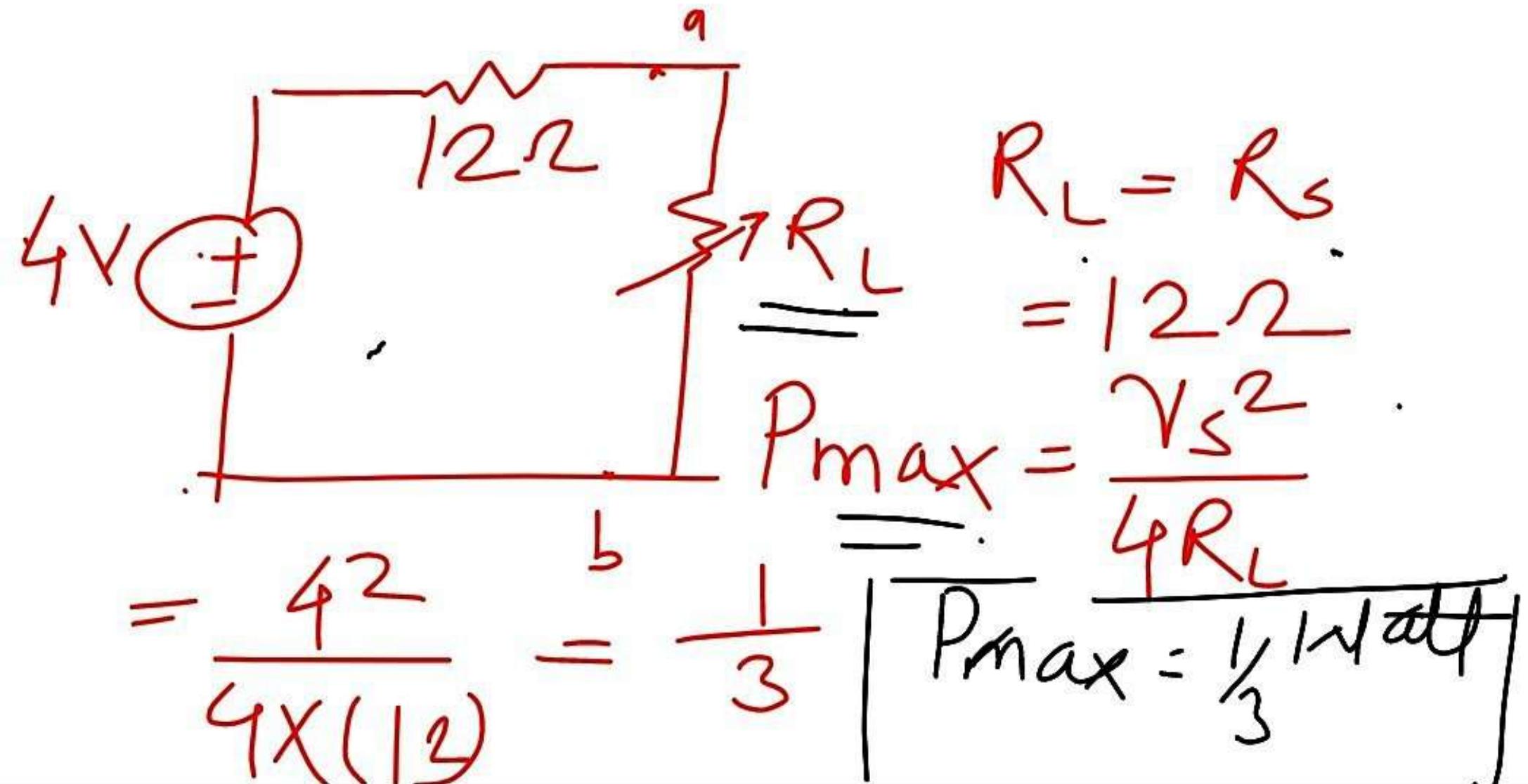

Circuit Theorems

Superposition Theorem :-

Definition :-


- In a linear network with several independent sources, the response in a particular branch when all the sources are acting simultaneously is equal to the linear sum of individual responses calculated by taking one independent source at a time.
- All the ideal voltage sources are eliminated from the network by shorting the sources, all the ideal current sources are eliminated from the network by opening the sources and do not disturb the dependent sources present in the network.

Properties:-

- This theorem is applicable only to linear networks i.e. the networks with R, L, C transformer and linear controlled sources as elements.
- The presence of dependent sources makes the network an active and hence SPT is used for both active as well as passive networks.

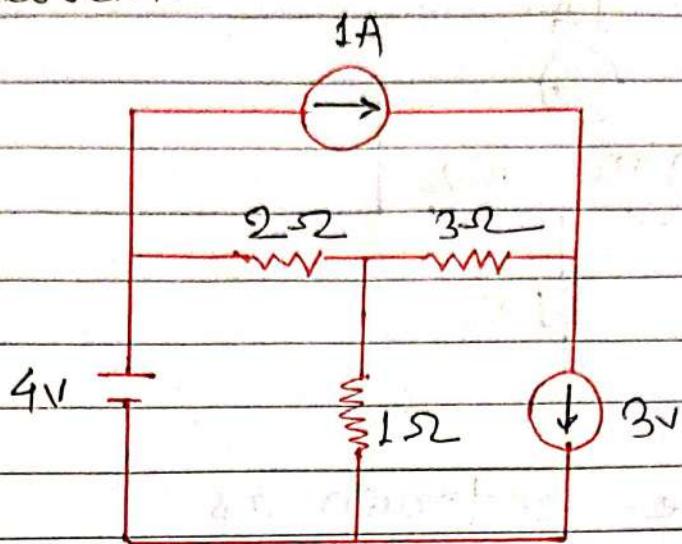
Example :-

Find the current in the 1Ω resistor using superposition theorem.



Step I :-


When the $4V$ source is acting alone.

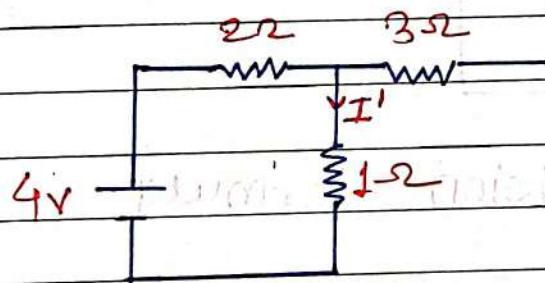

$$I' = \frac{4}{2+1} = 1.33 \text{ Ampere } (\downarrow)$$

Step II :-


By current division formula

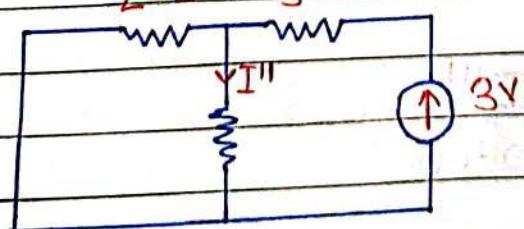


$$I'' = 3 \times \frac{2}{1+2} = 2 \text{ Amp } (\uparrow)$$

Step III

When the 1-ampere source is acting alone

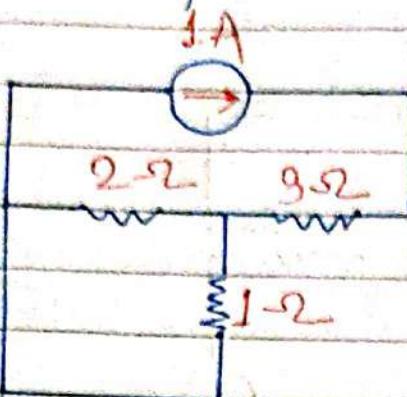

Circuit can be redrawn as

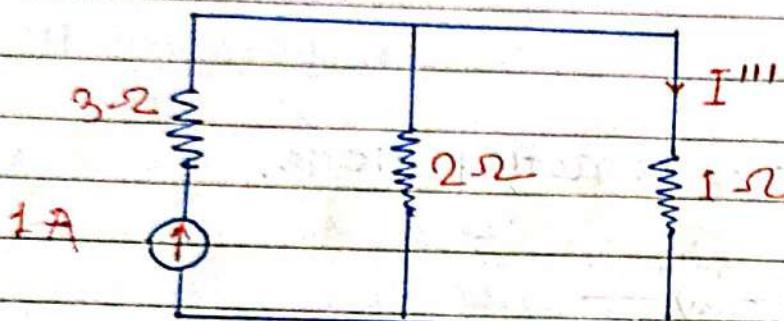

By current - division formula


$$I''' = \frac{1 \times 2}{2+1} = 0.66 \text{ Amp } (\downarrow)$$

Step IV


By superposition theorem

$$\begin{aligned} I &= I' + I'' + I''' \\ &= 1.33 + 2 + 0.66 \\ &= 4 \text{ Amp } (+) \end{aligned}$$

② Determine I

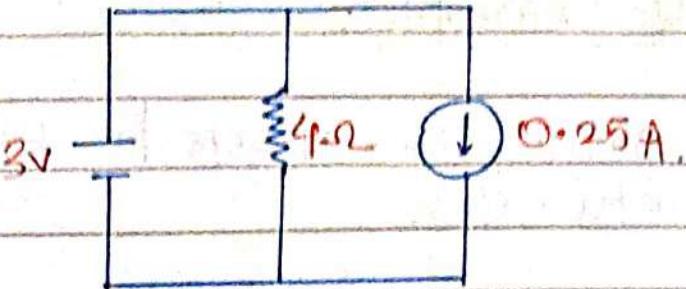


By KCL :-

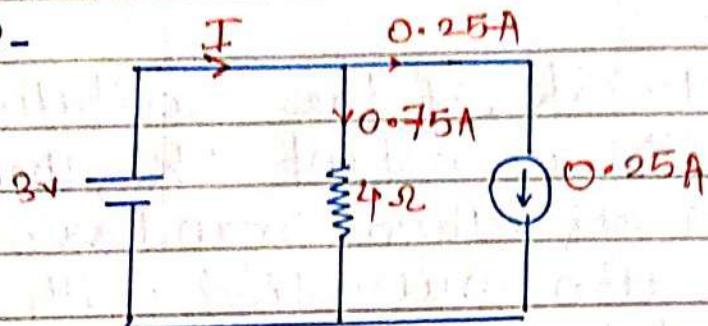


$$\text{By KCL} \Rightarrow -I + 0.75 + 0.25 = 0$$

$$\therefore \underline{I = 1.0 \text{ Amp.}}$$

By Superposition Theorem :-

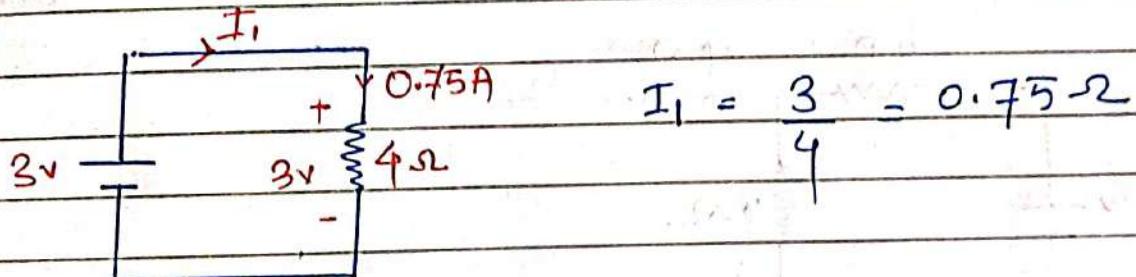

$$I_1 = \frac{3}{4} = 0.75 \text{ A}$$

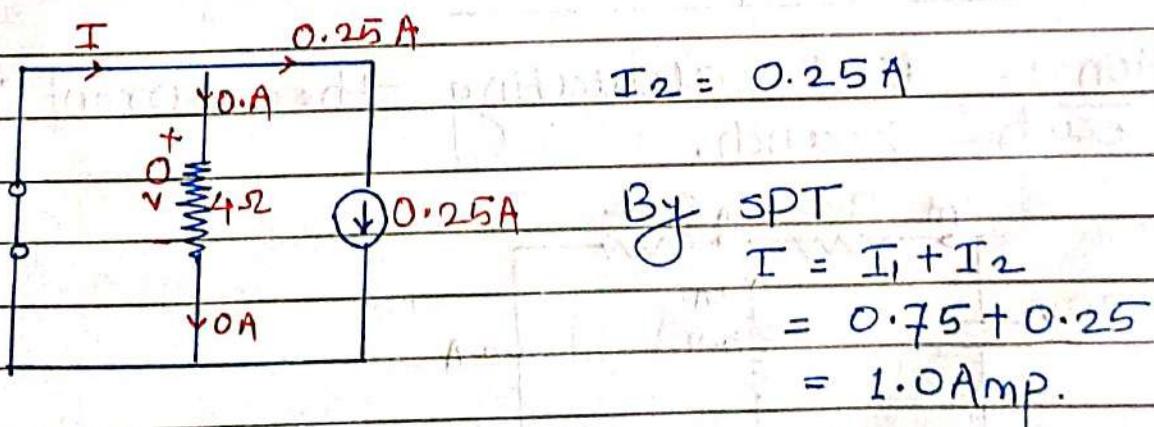

By SPT

$$I = I_1 + I_2$$

$$= 0.75 + 0.25$$

$$= 1.0 \text{ Amp.}$$

$$\underline{I = 1 \text{ Amp.}}$$

Homogeneity Principle:-


It is the principle obeyed by all the linear networks.

Definition:-


In a linear network, if the excitation is multiplied with a constant 'K', then the responses in all other branches of the network are also multiplied with the same constant K.

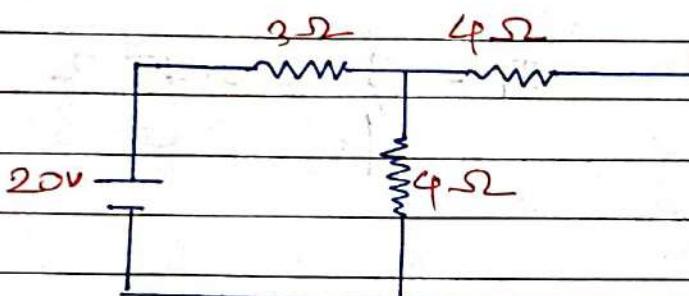Example:-


Find all branch currents if source voltage is increased to 60 volts in the circuit below.



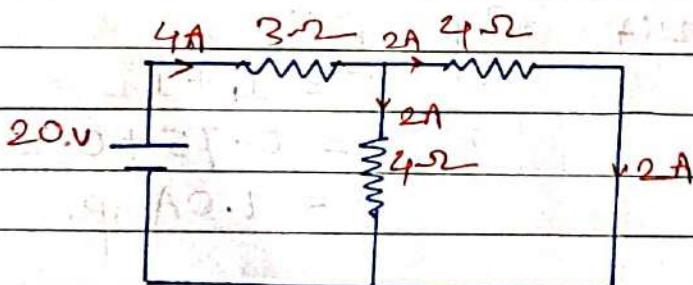Solution :- first calculating the current in each branch.



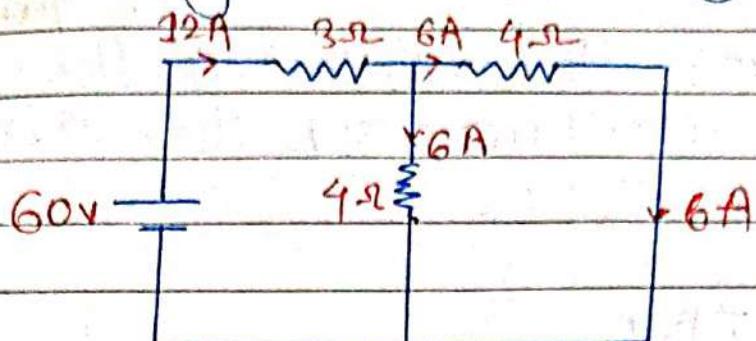
So here, the excitation is multiplied by '3' and hence the responses are also proportionally multiplied by '3'.



Note:-

When multiple sources are present superposition theorem to be applied first and later Homogeneity principle. i.e. Whenever Homogeneity principle is to be applied always ensure only one source in the network.

2) Determine I when $V_1 = 10V$ & $V_2 = -20V$.

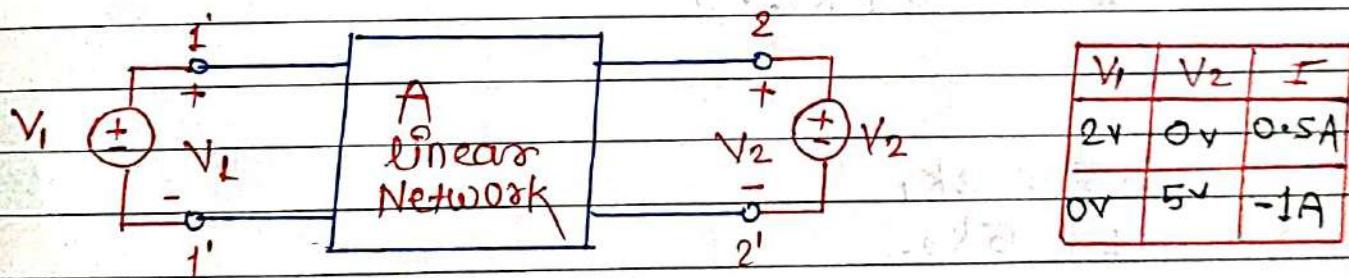

Method 1

- When $V_1 = 2V$ alone then the current is 0.5A (Given)
 - When $V_1 = 10V$ alone then current $I_1 = 5 \times 0.5$
- $I_1 = 2.5 \text{ Amp}$
- (Required)

When $V_2 = 5V$ alone then the current is $-1A$ (Given)

When $V_2 = -20V$ alone the current $I_2 = -4 \times (-1)$

$$I_2 = 4 \text{ Amp}$$

(Required)

By superposition theorem, when the both sources acting simultaneously the overall current $I = I_1 + I_2$

$$= 2.5 + 4$$

$$= 6.5 \text{ Amp.}$$

Method (2)

By superposition theorem,

$$I = I_1 + I_2$$

$$I = k_1 V_1 + k_2 V_2 \quad (\text{By homogeneity})$$

$$0.5 = k_1 \times 2 + 0$$

$$-1 = 0 + k_2 \cdot 5$$

$$0.5 = 2k_1$$

$$\& -1 = 5k_2$$

$$I = \left(\frac{V_1}{4} - \frac{V_2}{5} \right) \text{ Amp.}$$

$$= \left[\frac{10}{4} - \left(-\frac{20}{5} \right) \right]$$

$$= \left(\frac{10}{4} + \frac{20}{5} \right)$$

$$= \frac{50 + 80}{20}$$


$$= \frac{130}{20}$$

$$= 6.5 \text{ Amp.}$$

Thevenin's & Norton's Theorem :-

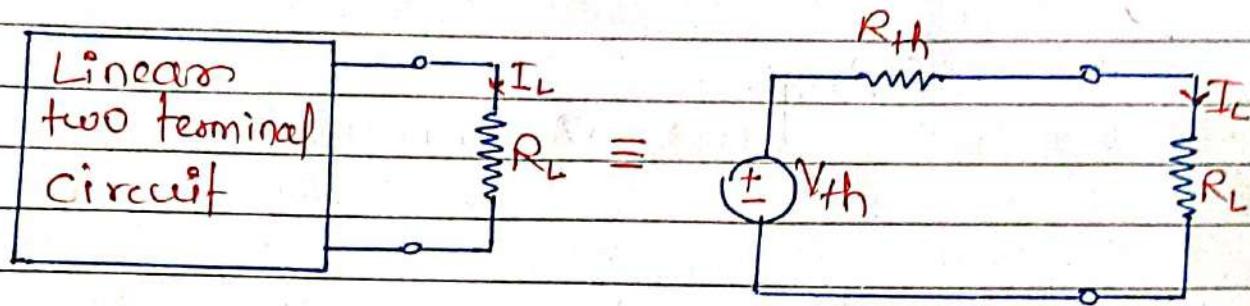
(1) Thevenin's Theorem :-

Thevenin's theorem states that a linear two terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{th} in series with a resistor R_{th} , where V_{th} is the open circuit voltage at the load terminals and R_{th} is the input or equivalent resistance at the load terminals when the independent sources are turned off. i.e. killed.



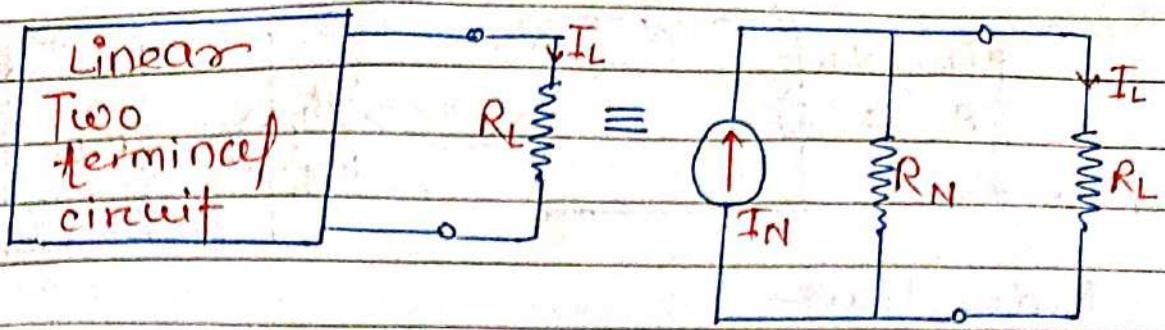(2) Norton's Theorem :-


Norton's theorem states that a linear two terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N , where I_N is the short circuit current through the load terminals and R_N is the input or equivalent resistance at the load terminals when the independent sources are turned off. i.e. killed.




Properties :-

- These theorems are applicable only for linear networks i.e. networks with R , L , C transformer and linear controlled sources as elements.
- Presence of dependent sources makes the network active and hence these theorems are used for both active as well as passive networks.

Procedure :-

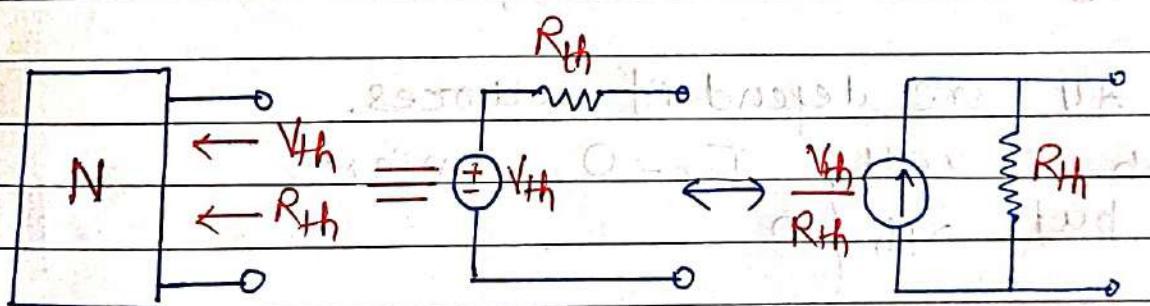

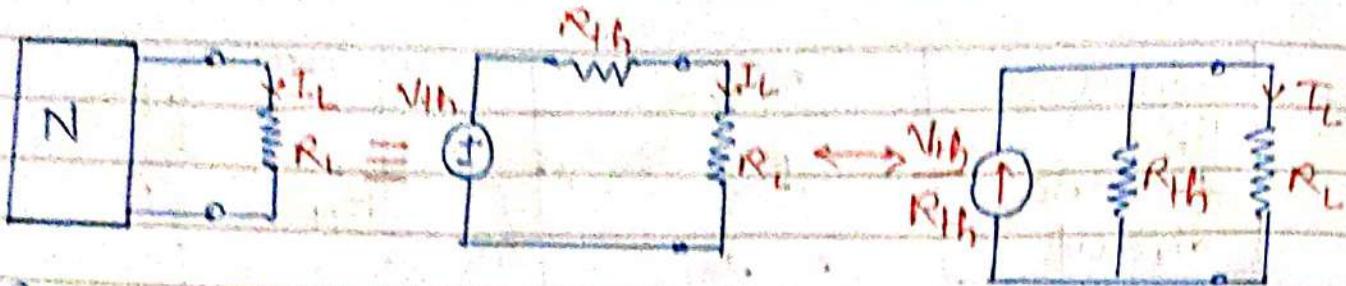

By Ohm's law

$$I_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right) \text{ Amp.}$$

$$I_L = \frac{\frac{V_{Th}}{R_{Th}} \cdot R_{Th}}{R_{Th} + R_L} = \left(\frac{V_{Th}}{R_{Th} + R_L} \right) \text{ Amp.}$$

Cases in Thévenin Theorem (Norton's theorem)
based on sources.


Case 1 :- (All are independent sources) : V_{Th} , R_{Th}

Case 2 :- (Atleast one independent and one dependent sources) : V_{Th} , I_{Sc}

$$R_{Th} = \frac{V_{Th}}{I_{Sc}} \Rightarrow I_{Sc} = \frac{V_{Th}}{R_{Th}} = I_N$$

Case 3 :- All are dependent sources.

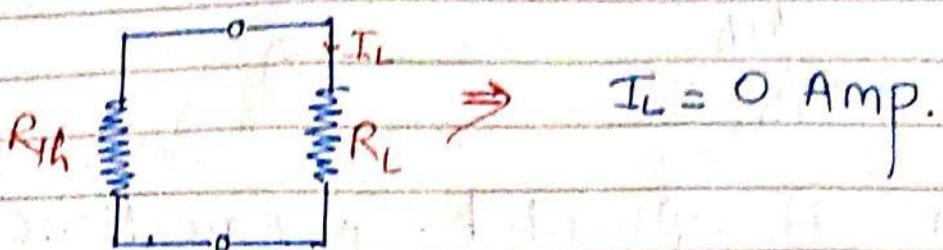$V_{Th} = 0$ Volt, $I_{Sc} = 0$ Amperes
but $R_{Th} \neq 0$




i.e. Thévenin's equivalent = Norton's Equivalent.

Q. ① Network N contains several resistances & DC sources. The current $I = 3 \text{ Amp}$ & 1.5 Amp . when $R = 0\ \Omega$ and $2\ \Omega$ respectively. Determine I when $R = 1\ \Omega$.

Sol:- (case 1 :- All are independent sources, so called passive Networks)


By Thévenin :-

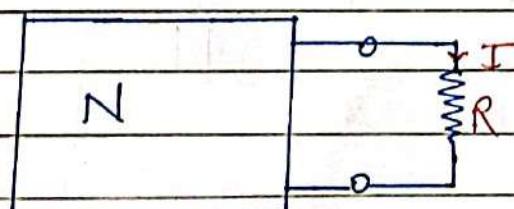Any network with any number of elements with respect to load element can be written as a 3 element network.



$$R_{Th} = 2\ \Omega$$

$$I = \frac{V_{Th}}{R_{Th} + R}$$

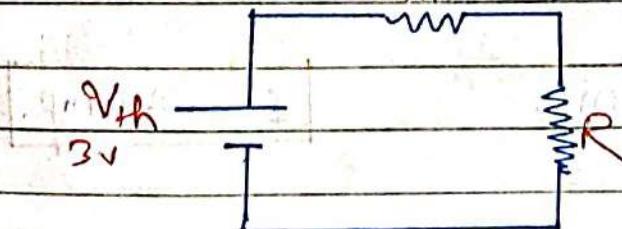

$$3 = \frac{V_{Th}}{R_{Th}}$$

— ①

$$1.5 = \frac{V_{th}}{R_{th} + 2} \quad \textcircled{2}$$

Equation $\textcircled{1}$ divided by Equation $\textcircled{2}$

$$\frac{3}{1.5} = \frac{R_{th} + 2}{R_{th}}$$

$$2 = 1 + \frac{2}{R_{th}}$$

$$\therefore 2 - 1 = \frac{2}{R_{th}}$$

$$1 = \frac{2}{R_{th}}$$

$$R_{th} = 2 \Omega$$

from eqn $\textcircled{1}$

$$3 = \frac{V_{th}}{2}$$


$$V_{th} = 6V$$

$$I = \frac{6}{2 + 1} = 2 \text{ Amp.}$$

$$I = 2 \text{ Amp.}$$

Method (2) By Norton Theorem :-

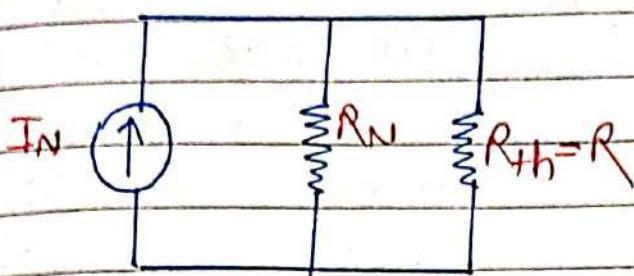Any network with any number of elements with respect to a load element can be written as a 3 element network by,



$$I = \frac{I_N \cdot R_N}{R + R_N}$$

$$3 = \frac{I_N \cdot R_N}{0 + R_N} \quad \text{--- (1)}$$

$$1.5 = \frac{I_N \cdot R_N}{2 + R_N} \quad \text{--- (2)}$$

eqn (1) divided by equation (2)

$$\frac{3}{1.5} = \frac{I_N \cdot R_N}{0 + R_N}$$

$$\frac{I_N \cdot R_N}{2 + R_N}$$

$$2 = \frac{2 + R_N}{R_N}$$

$$2 = \frac{2}{R_N} + 1$$

$$2 - I = \frac{2}{R_N}$$

$$R_N = \frac{2}{1}$$

$$R_N = 2 \Omega$$


Now

$$3 = \frac{I_N \cdot R_N}{R_N}$$

$$I_N = \frac{3 R_N}{R_N}$$

$$I_N = \frac{3 \times 2}{2}$$

$$I_N = 3 \text{ Amp}$$

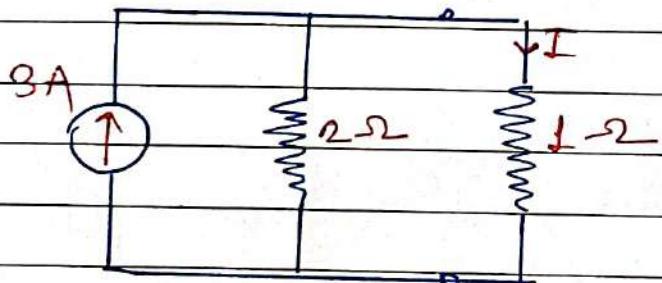

$$I = \frac{3 \times 2}{2+2} = \frac{6}{3}$$


$$I = 2 \text{ Amp.}$$

Observation :- Both I_N & R_N are independent of the load magnitude (value)


Q(2) An ideal voltage and current sources are connected in parallel. This combination will have.

- (a) Both Thevenin and Norton's equivalents
- (b) Thevenin's but not Norton's (Option b)
- (c) Norton's but Not Thevenin
- (d) Neither Thevenin Nor Norton's


→

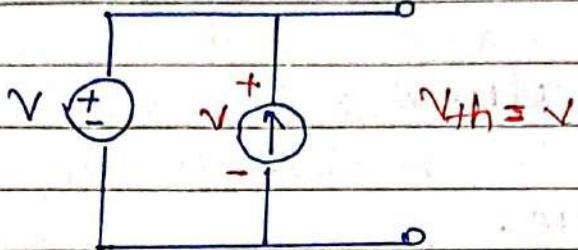

① Kill the sources

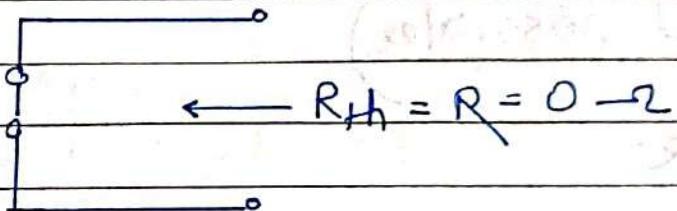

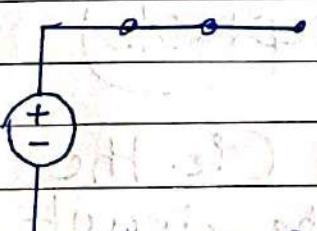Entire network is in series with R_{th} .




An ideal voltage source
(w.r.t. to load)

Note:- As discussed in source transformation if it is impossible to convert an ideal voltage source into its equivalent current source. Hence Norton's equivalent does not exist.

Reason :-

By direct Norton's Approach

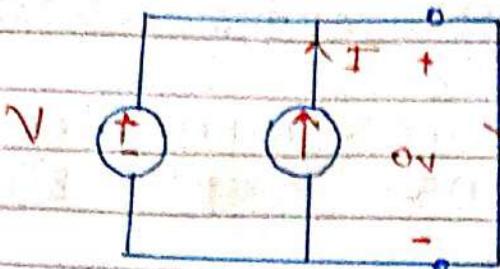

By KCL

$$I_{sc} = I + \text{Any value}$$

$$= \text{Any value}$$

(Any value for metal or conductor is not possible)

(OR)


By KVL,

$$V - 0 = 0$$

$$V = 0 \quad (\text{Not acceptable})$$

Since the violation of KVL (i.e. the conservation of energy) in the circuit, the physical connection is not possible. i.e. the circuit does not exist. Hence it is impossible to evaluate I_{sc} so, Norton's equivalent does not exist.

When both the sources are in series.

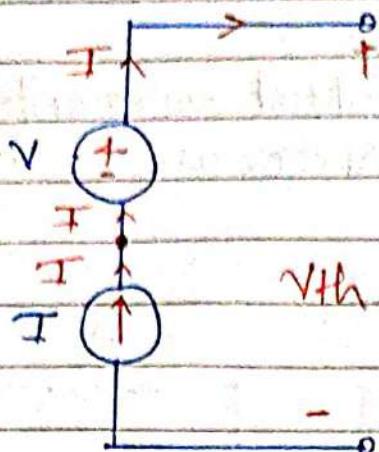



By KVL,


$V_{th} = V + \text{Any value}$
Any value for metal
(NOT acceptable)

(OR)

Here we cannot open the load for V_{th} since the violation of KCL at the node in the circuit & hence it is impossible to evaluate V_{th} . So, Thevenin's equivalent does not exist.



By Direct Norton's approach:

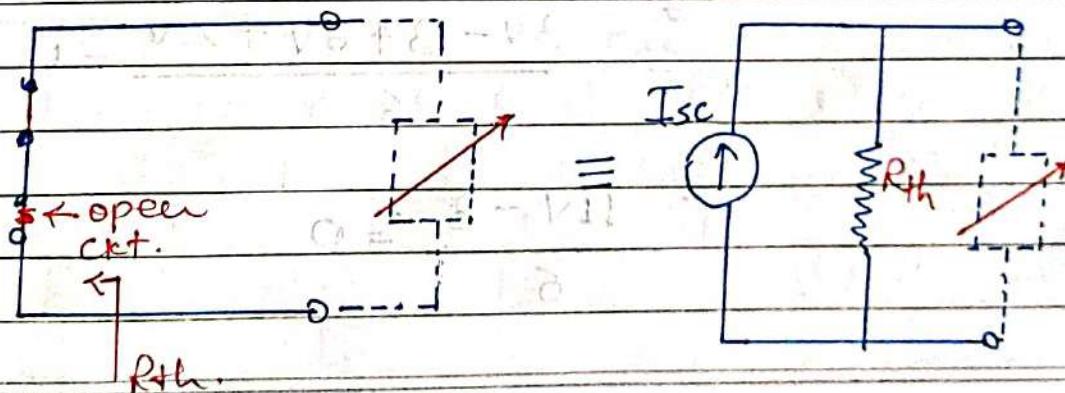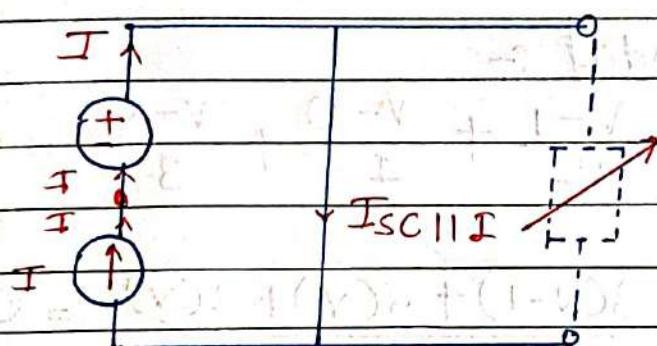

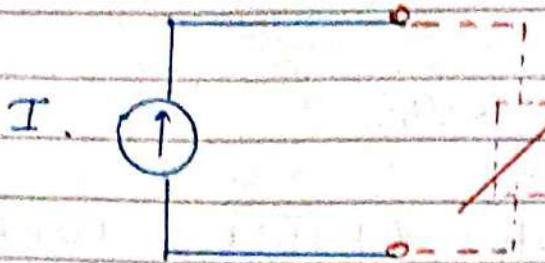


~~An ideal current source w. r. to load.~~

Q. 3

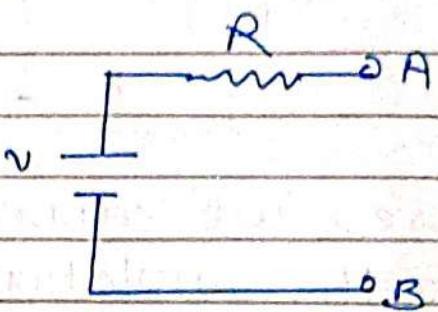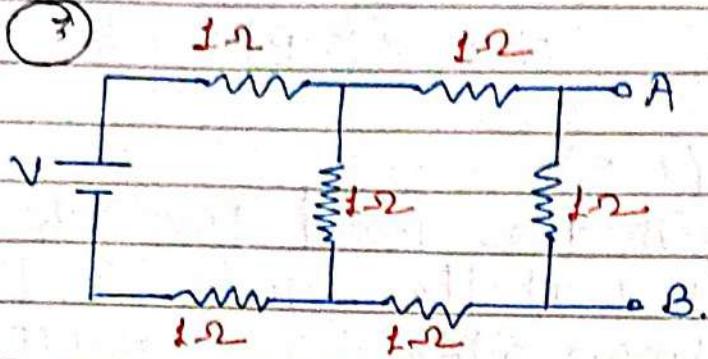

find V_{th} & R_{th} .

By Nodal Analysis \Rightarrow

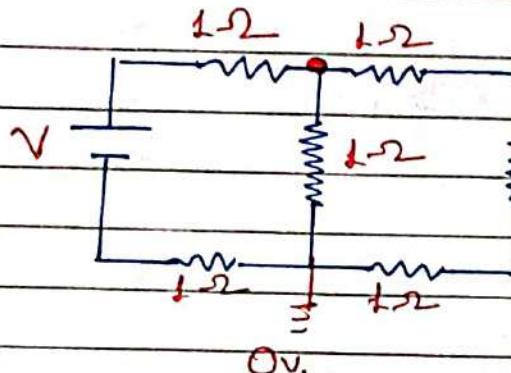

Nodal =

$$\frac{V-1}{2} + \frac{V-0}{1} + \frac{V-0}{3} = 0$$

$$= \frac{3(V-1) + 6(V) + 2(V)}{6} = 0$$


$$= \frac{3V - 3 + 6V + 2V}{6} = 0$$

$$= \frac{11V - 3}{6} = 0$$

$$11V - 3 = 0$$

$$11V = 3$$

$$V = \frac{3}{11} V$$

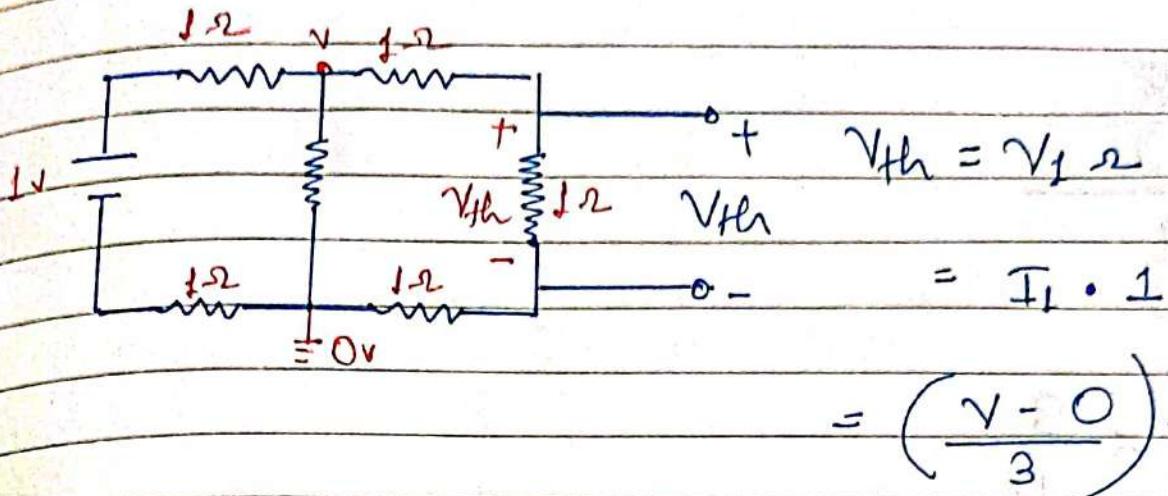


$$= \frac{V}{3}$$

$$\left(\because V = \frac{3}{11} V \right)$$

$$= \frac{3}{11} \cdot \frac{1}{3} V$$

$$V_{th} = \frac{1}{11} V$$

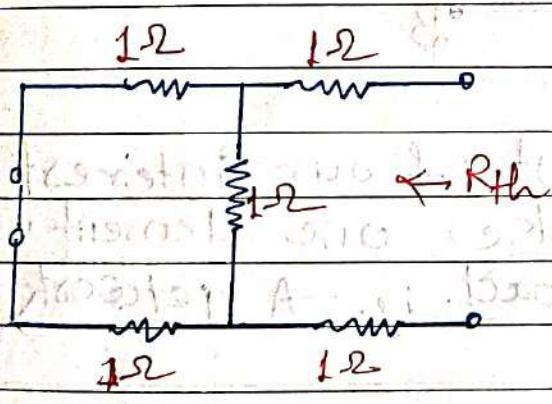

$$R_{th} = 11 \left(1 + \frac{2 \times 1}{2+1} + 1 \right)$$

$$= 11 \left(1 + \frac{2}{3} + 1 \right)$$

$$= 11 \left(\frac{8}{3} \right)$$

$$1 \times \frac{8}{3}$$

$$1 + \frac{8}{3}$$


$$\frac{8}{3}$$

$$\frac{11}{3}$$


$$= \frac{8}{3} \times \frac{3}{11}$$

$$R_{th} = \frac{8}{11} \Omega$$

Method (2) By Thevenin Theorem

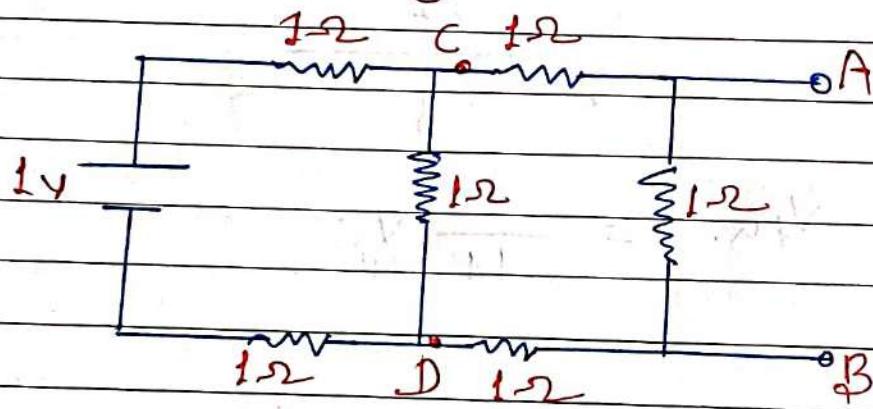

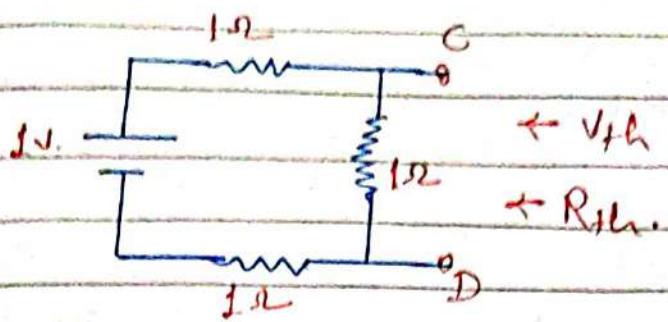Note:- Generally the element of our interest is a load. We can take one element or group of elements as a load. i.e. - A network can be a load.




$$V_{th} = \frac{1}{3} \times 1$$

$$= \frac{1}{3} \text{ V.}$$

$$R_{th} = 1 \parallel 2$$

$$= \frac{1 \times 2}{1 + 2}$$

$$= \frac{2}{3} \Omega$$

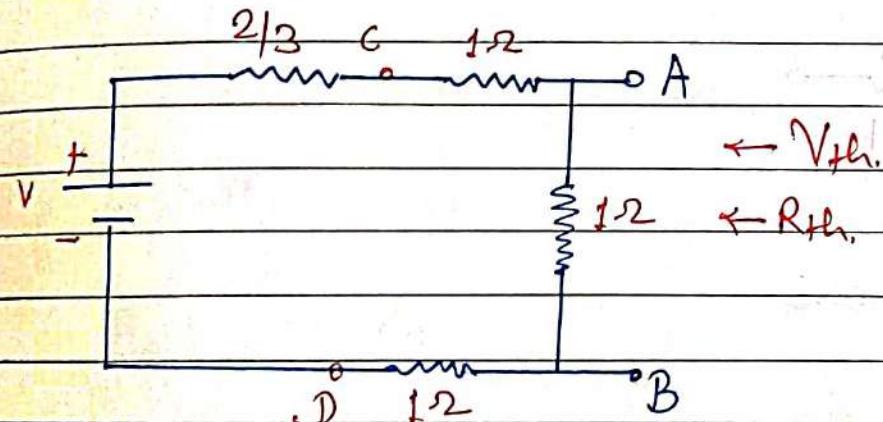

$$V_{th} = \left(\frac{1/3}{2/3 + 1 + 1 + 1} \right) \cdot 1$$

$$= \frac{1}{3}$$

$$\frac{2/3 + 3}{2/3 + 3}$$

$$= \frac{1}{3} \times \frac{3}{4} = \frac{1}{4} \text{ V}$$


$$R_{Th} = 11 \left(1 + \frac{2}{3} + 1 \right)$$

$$= 11 \left| \frac{8}{3} \right.$$

$$= \frac{1 \times 8/3}{1 + 8/3}$$


$$= \frac{8/3}{11/3}$$

$$R_{Th} = \frac{8}{11} \Omega$$

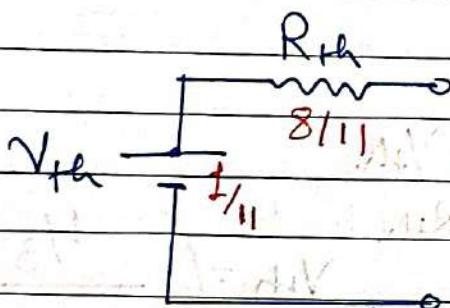


Case 2 :- (Atleast one dependent (Inside) and Independent (Outside) sources so called Active Network.)

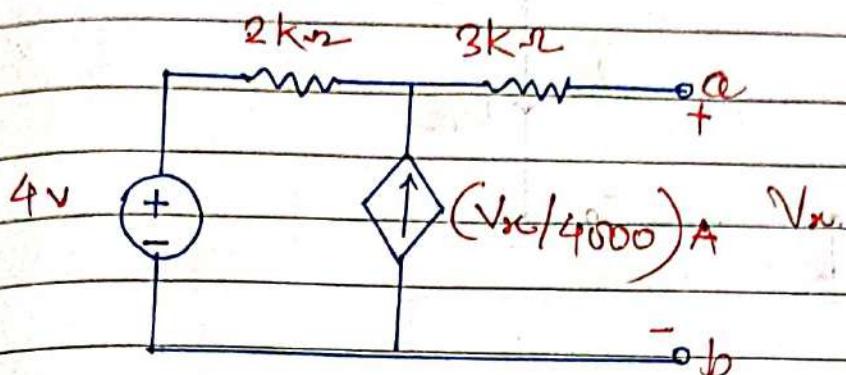Q(1) Determine the Thevenin's & Norton's equivalent across.



Soln :-

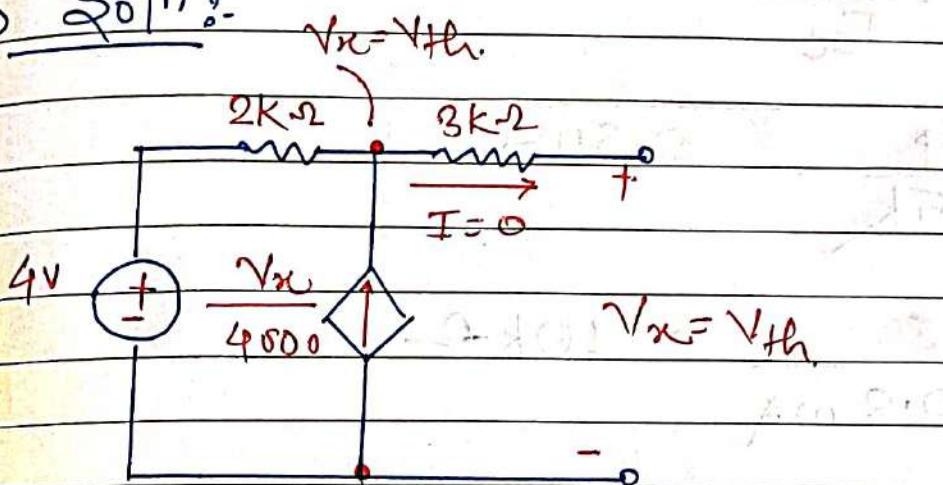


Assume $V_x = V_{th}$

By Nodal \Rightarrow

$$\frac{V_x - 4}{2k} - \frac{V_x}{4000} = 0$$

$$\frac{V_n}{2k} - \frac{2}{1k} = \frac{V_n}{4000}$$


$$V_n = 8V = V_{th}$$

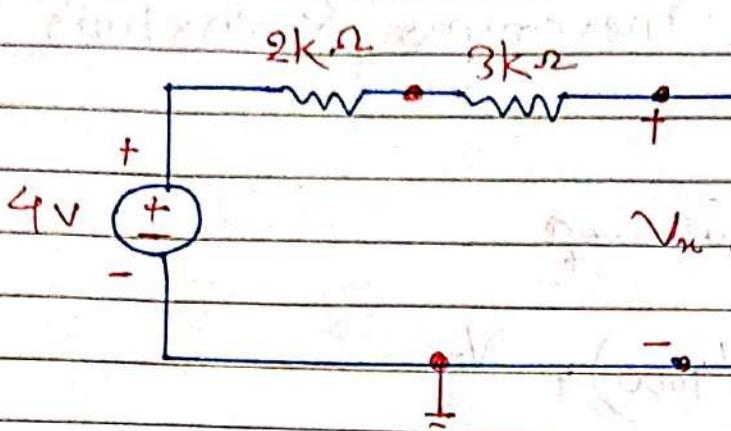


$$R_{th} = \frac{V_{th}}{I_{sc}}$$

$$I_{sc} = \frac{4}{5k} = 0.8 \text{ mA}$$

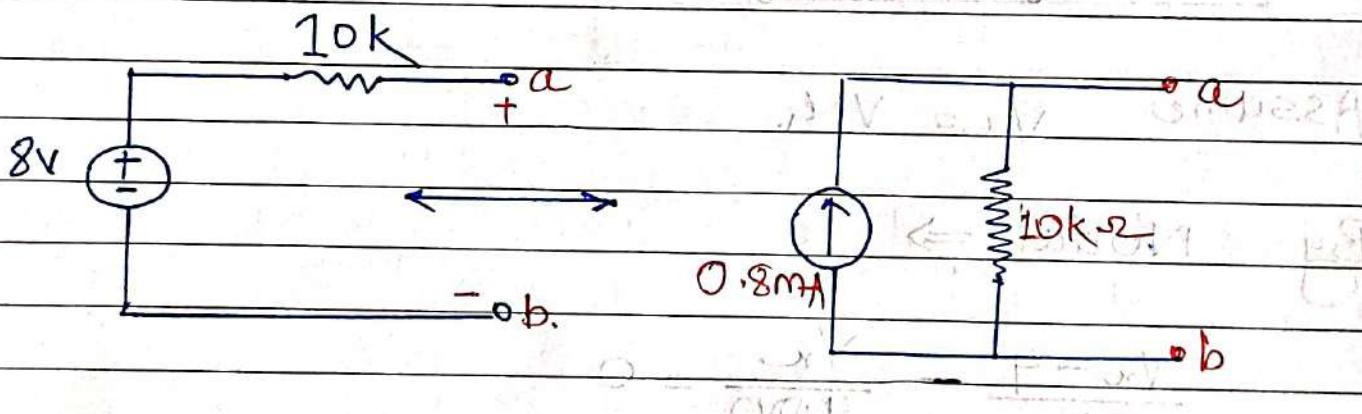
$$R_{th} = \frac{8}{0.8 \text{ mA}} = 10k\Omega$$



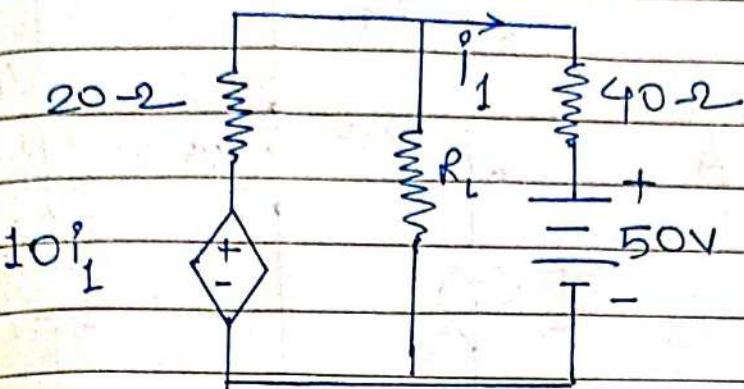Q. Consider the following circuit and determine Thevenin's and Norton's equivalent across R_L .



Sol. :-

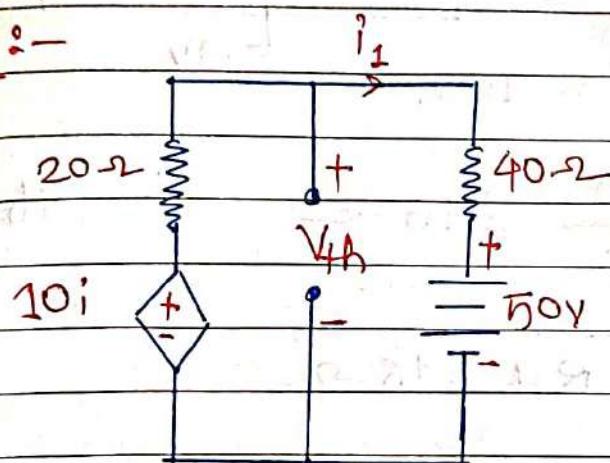

By Nodal \Rightarrow

$$\frac{V_{th}}{20} - \frac{10i_1}{20} + \frac{V_{th}}{40} - \frac{50}{40} = 0$$

$$\frac{2V_{th} - 20i_1 + V_{th} - 50}{40} = 0$$

$$3V_{th} - 20i_1 - 50 = 0$$

$$3V_{th} = 20i_1 + 50$$

By KVL,

$$10i_1 - 20i_2 - 40i_3 - 50 = 0$$

$$i_1 = -1 \text{ A.}$$


$$i_2 = -\frac{50}{40} = -\frac{5}{4} \text{ A.}$$

$$I_{sc} = \frac{5}{8} \text{ Amp}$$

$$\text{and } V_{th} = \frac{50 - 20}{3} = 10 \text{ V.}$$

$$\therefore R_{th} = \frac{10}{\frac{5}{8}} = \frac{80}{5} = 16 \Omega$$

$$V_o i_1 = -\frac{5}{4}$$

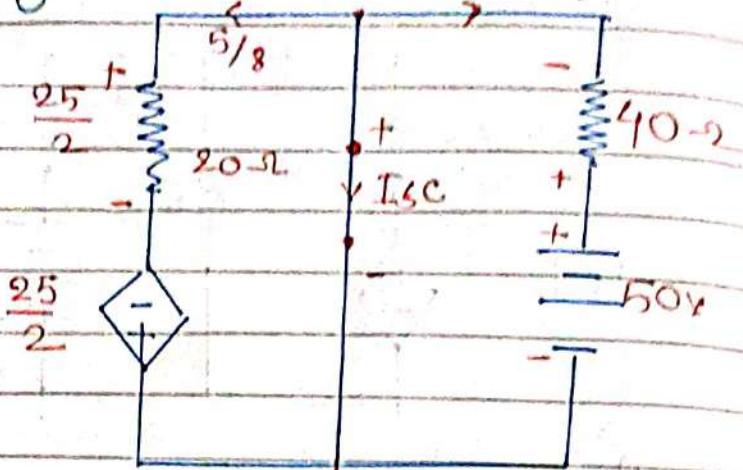


$$R_{th} = \frac{V_{th}}{I_{sc}}$$


$$\therefore V_{th} = 10 \text{ V and } R_{th} = 16 \Omega$$

Note:- Here, even though the load terminals are shorted, The controlled variable is non zero hence dependent source magnitude is non zero.

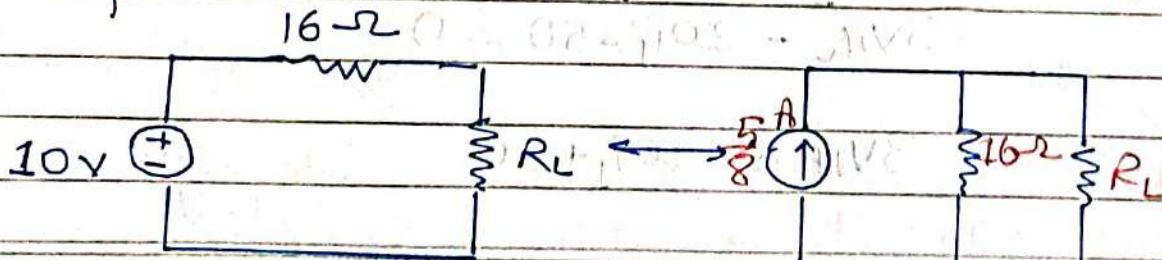To flow a current through the short circuit (ie zero impedance path) As well as ideal current source, There is no need of Potential difference (ie. Height difference) across the terminals. It is required only for the passive R, L, C.




Q. Consider the following circuit.

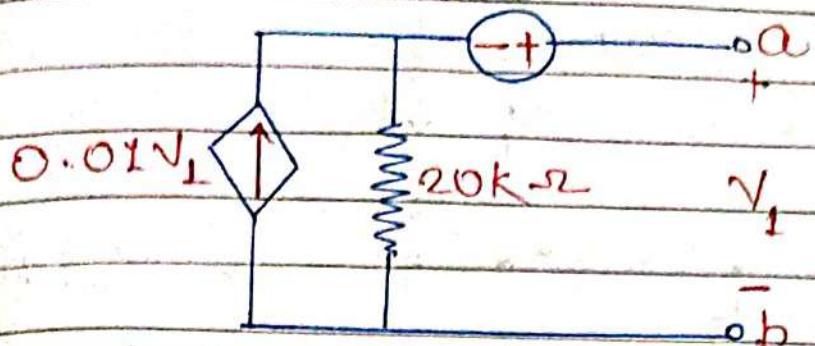

If a 100Ω resistor is connected across a, b , then determine current through it by using Thvenin's Theorem.

Soln:-

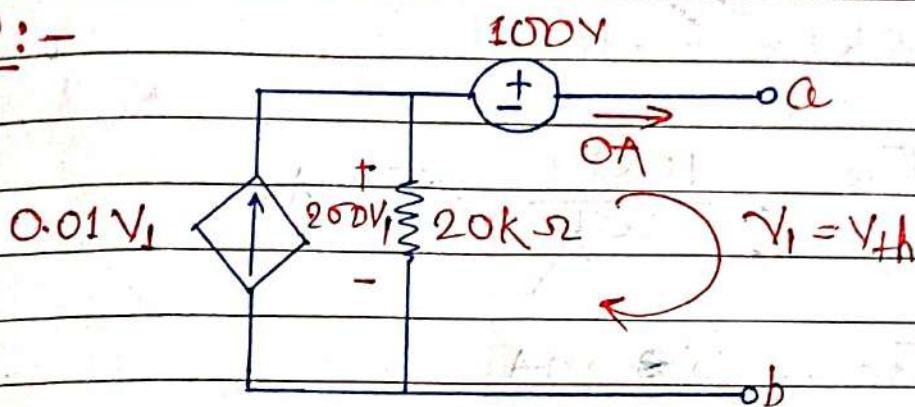


Assume $V_1 = V_{th}$

By KVL

$$200V_1 + 100 - V_1 = 0$$

$$199V_1 + 100 = 0$$
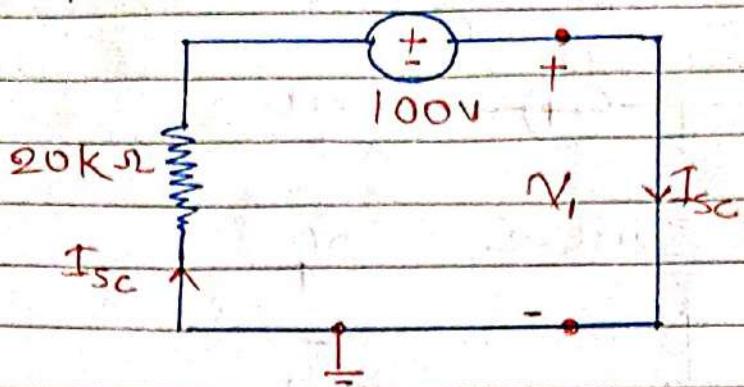
$$\therefore V_1 = \frac{-100}{199} = -502.5 \text{ mV}$$



By KVL

$$-20kI_{sc} + 100 = 0$$

$$-20kI_{sc} = -100$$

$$I_{sc} = \frac{100}{20k} = 5 \text{ mA}$$

$$I_{sc} = 5 \text{ mA}$$

$$R_{th} = \left| \frac{V_{th}}{I_{sc}} \right| = \frac{-502.5 \text{ mV}}{5 \text{ mA}} = \frac{-502.5 \text{ mV}}{5 \times 10^{-3}} = 100.5 \Omega$$


$$= |-100.5 \Omega| = 100.5 \Omega$$

$$R_{th} = 100.5 \Omega$$

$$100.5 \Omega$$

So,

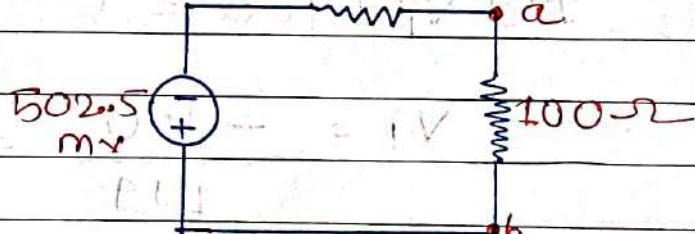
$$I_{100} = \frac{502.5 \text{ mV}}{200.5} = 2.5 \text{ mA}$$



Note:- Presence of dependent sources in the network makes R_{th} sometimes, to have a negative value.


Case 3 :- All are dependent sources, so called Dead Networks.

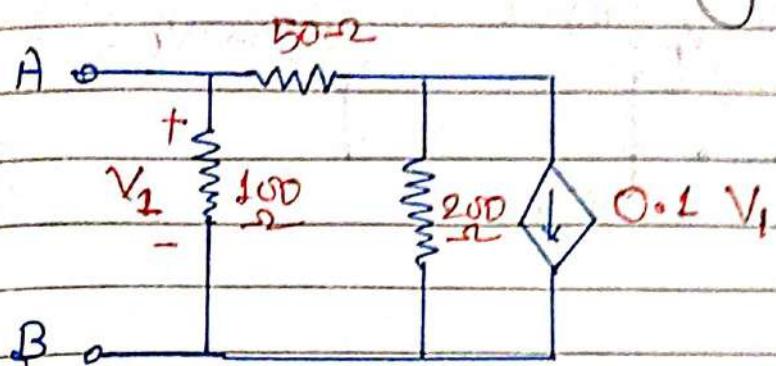Q. Determine Thevenin's and Norton's equivalent across AB of the following Networks.




The above ~~AB~~ network is a dead network, so we need to energize it with "V".
The ~~dead network~~ behavior is a load resistor behavior.

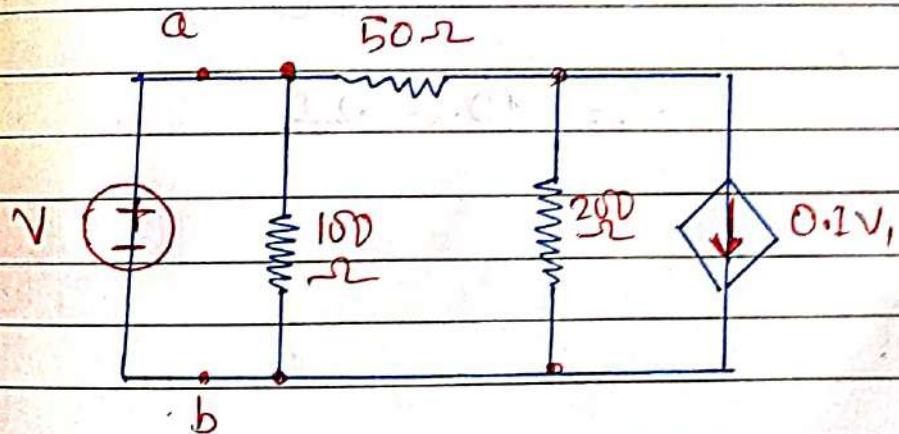Note:- Here we can apply source transformation for dependent source. As controlled variable is outside.



$V = V_1$


On doing source transformation

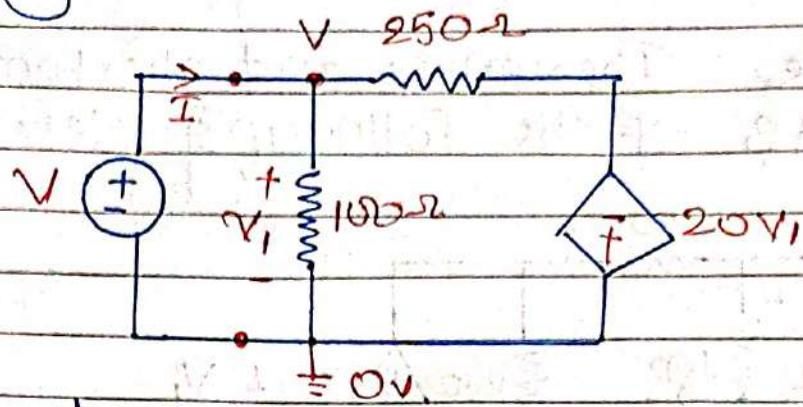

By Nodal \Rightarrow


$$-I + \frac{V}{150} + \left(\frac{V + 20I}{250} \right) = 0$$
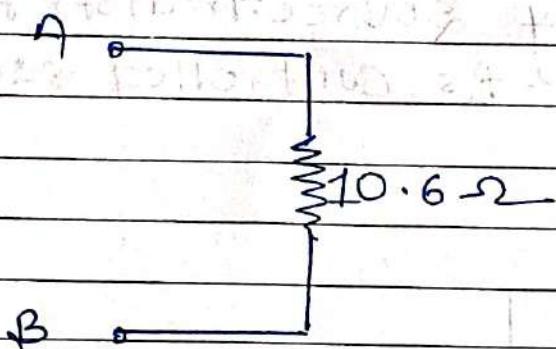
$$\frac{V_1}{I} = R_{TH} = R_N = \frac{1}{150} + \frac{2}{250}$$




$$= \frac{100 \times 250}{2350}$$


$$= 10.6\Omega$$

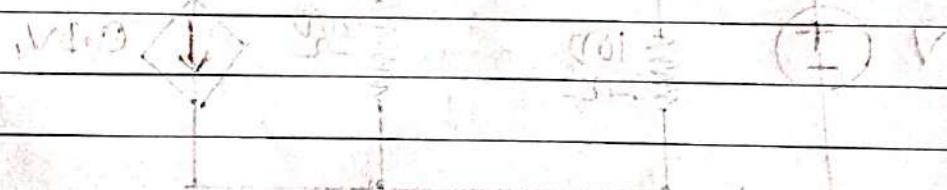

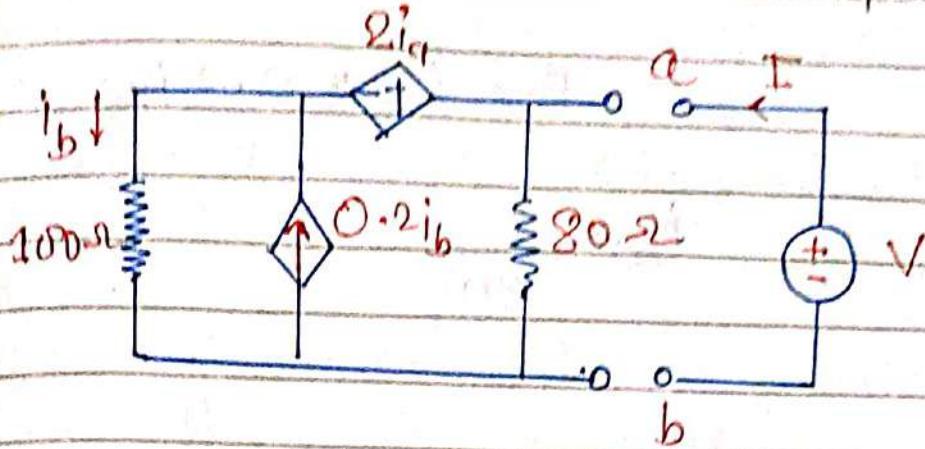Q. For the circuit shown in figure, determine the Thevenin and Norton's equivalent.



Soln :-

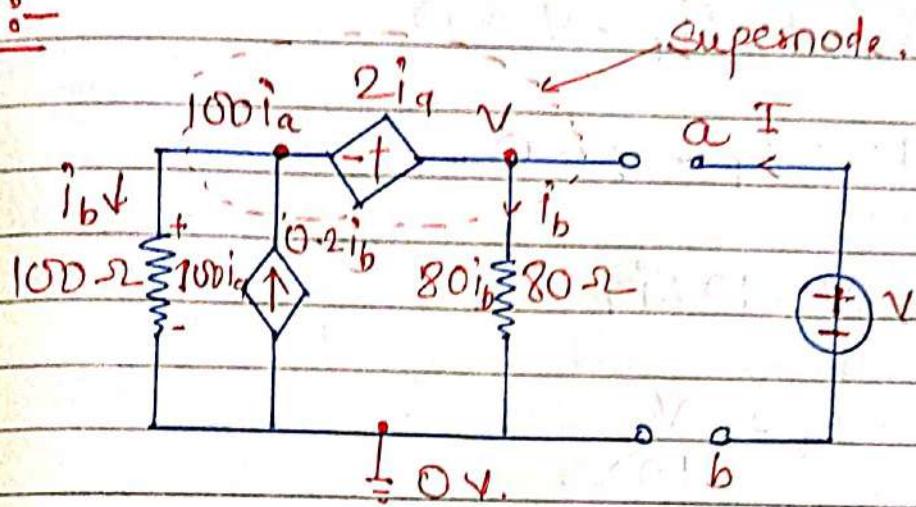

Note:- Here we cannot apply source transformation for dependent source as the controlled variable is inside. Hence supernode procedure is followed here for the dependent source. It is also to note that dependent source also behaves like independent source in the presence of atleast one external independent source.

Supernode Equation = $i_a - 0.2i_b + i_b - I = 0$

$$I = i_a + 0.8i_b$$

$$i_b = \frac{V}{80}$$

By KVL

$$100i_a + 2i_a - V = 0$$

$$102i_a - V = 0$$

$$V = 102i_a$$

$$i_a = \frac{V}{102}$$

$$I = \frac{V}{102} + 0.8 \times \frac{V}{80}$$

$$\frac{V}{I} = R_{th} = R_N = \frac{1}{\frac{1}{102} + \frac{1}{100}}$$


$$= \frac{100 \times 102}{202}$$
$$= 50.5 \Omega$$

Maximum Power Transfer Theorem (MPPT)

- This theorem is applicable only for linear networks i.e. the networks (with R, L, C , transformer and linear controlled sources as elements).
- The presence of dependent sources makes the network active and hence, MPPT is used for both active as well as passive networks.
- This theorem is applicable only when load is variable; otherwise (i.e. load is fixed) choose the minimum internal impedance of the source, which results in maximum current through the fixed load and hence, a maximum power dissipation across the load.

Under Variable Load conditions

① R_s & R_L

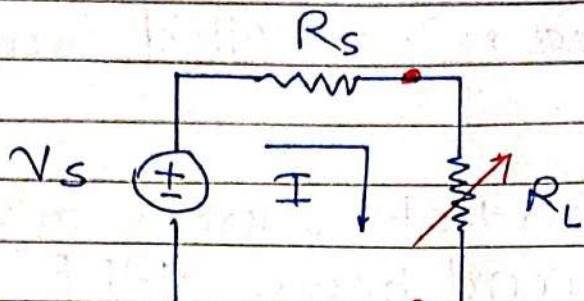


$$I = \frac{V_s}{R_s + R_L}$$

$$P = I^2 R_L \text{ Watt}$$

$$= R_L I \cdot I$$
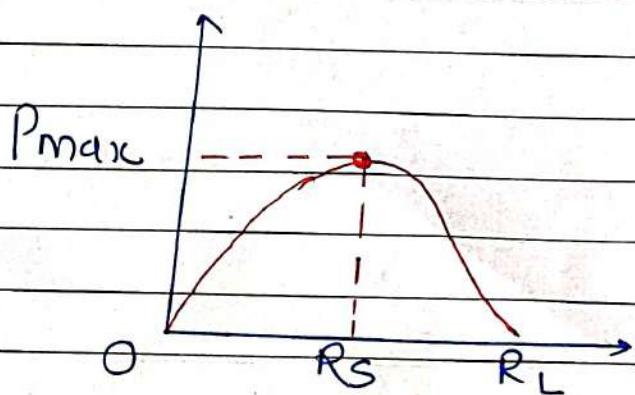
$$P = \frac{V_s^2 R_L}{(R_s + R_L)^2} \text{ Watt}$$



$$\frac{dP}{dR_L} = \frac{Vs^2 [(R_s + R_L)^2 \cdot 1 - R_L \cdot 2(R_s + R_L)]}{[(R_s + R_L)^2]^2}$$

for MPT $\rightarrow \frac{dP}{dR_L} = 0$

$$\frac{Vs^2 [(R_s + R_L)^2 \cdot 1 - R_L \cdot 2(R_s + R_L)]}{[(R_s + R_L)^2]^2} = 0$$

$$Vs^2 [(R_s + R_L)^2 \cdot 1 - R_L \cdot 2(R_s + R_L)] = 0$$

$$\therefore (R_s + R_L)^2 - R_L \cdot 2(R_s + R_L) = 0$$

$$(R_s + R_L)^2 = R_L \cdot 2(R_s + R_L)$$

$$R_s + R_L = 2R_L$$

$$R_s = 2R_L - R_L$$

$$R_s = R_L - 2$$

$$P_{max} = P_{RL=R_s} = \frac{Vs^2}{4R_L} \text{ Watt} = \frac{Vs^2}{4R_s} \text{ Watt}$$

$P_{\text{delivered}} = P_{\text{absorbed}}$ (By Tellegen's Theorem)

$$= I^2 R_s + I^2 R_L \quad | \\ R_L = R_s$$

$$= \frac{V_s^2}{2R_L} \text{ Watt} = \frac{V_s^2}{2R_s} \text{ Watt.}$$

$$\eta = \frac{\text{Useful Power}}{\text{Total Power}}$$

$$= \frac{\frac{V_s^2}{2R_L}}{\frac{V_s^2}{R_s}}$$

$$\frac{R_s}{2R_L}$$

$$= \frac{1}{2}$$


$$= 0.5$$

$$\therefore \eta = 50\%$$

Qo the efficiency of maximum power transfer theorem is atmost 50%.

② Z_s and Z_L

$$\text{Z}_s = (R_s + jX_s) \Omega$$

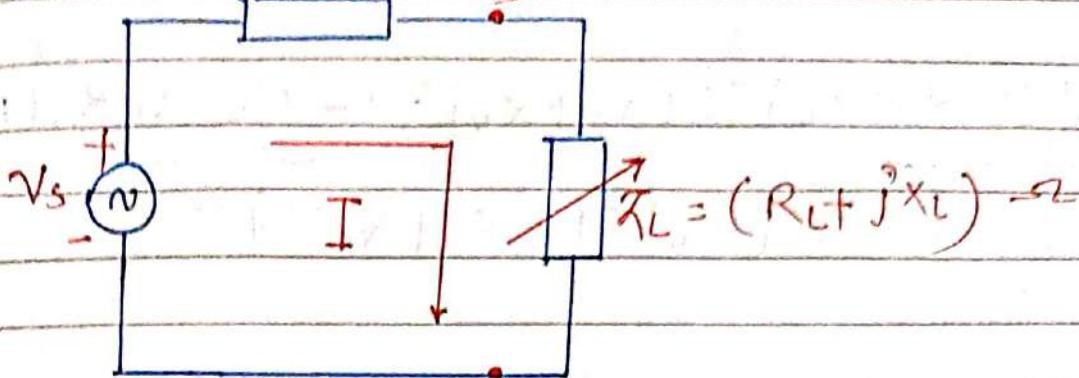

$$I = \frac{V_s}{R_s + R_L + j(X_s + X_L)}$$

$$|I| = \frac{|V_s|}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$P = |I|^2 \cdot R_L \text{ Watt}$$

$$P = \frac{|V_s|^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \text{ Watt}$$

③ Only ' R_L ' is variable :-

$$\frac{dP}{dR_L} = \frac{|V_s|^2 [(R_s + R_L)^2 + (X_s + X_L)^2] \cdot I - R_L \cdot 2(R_s + R_L)]}{[(R_s + R_L)^2 + (X_s + X_L)^2]^2}$$

For MPT $\frac{dP}{dR_L} = 0$

$$\frac{\gamma_s^2 [(R_{st} + R_L)^2 + (x_{st} + x_L)^2 \cdot 1 - R_L \cdot 2(R_{st} + R_L)]}{[(R_{st} + R_L)^2 + (x_{st} + x_L)^2]^2} = 0$$

$$\gamma_s^2 [(R_{st} + R_L)^2 + (x_{st} + x_L)^2 \cdot 1 - R_L \cdot 2(R_{st} + R_L)] = 0$$

$$\Rightarrow [(R_{st} + R_L)^2 + (x_{st} + x_L)^2 - R_L \cdot 2(R_{st} + R_L)] = 0$$

$$\Rightarrow R_{st}^2 + R_L^2 + 2R_{st} \cdot R_L + (x_{st} + x_L)^2 = R_L \cdot 2R_{st} + 2R_L^2$$

$$\Rightarrow R_{st}^2 + R_L^2 + (x_{st} + x_L)^2 = 2R_L^2$$

$$R_{st}^2 + (x_{st} + x_L)^2 = 2R_L^2 - R_L^2$$

$$R_{st}^2 + (x_{st} + x_L)^2 = R_L^2$$

$$\therefore R_L = \sqrt{R_{st}^2 + (x_{st} + x_L)^2} \Omega$$

$$P_{max} = P$$

$$R_L = \sqrt{R_{st}^2 + (x_{st} + x_L)^2}$$

(b) Only X_L is variable

$$\frac{dP}{dX_L} = \frac{V_s^2 [(R_s + R_L)^2 + (X_s + X_L)^2] \cdot 0 - R_L^2 (X_s + X_L)]}{[(R_s + R_L)^2 + (X_s + X_L)^2]^2}$$

for MPT $\frac{dP}{dX_L} = 0$

$$\frac{V_s^2 [(R_s + R_L)^2 + (X_s + X_L)^2] \cdot 0 - R_L^2 (X_s + X_L)}{[(R_s + R_L)^2 + (X_s + X_L)^2]^2} = 0$$

\Rightarrow

$$V_s^2 [(R_s + R_L)^2 + (X_s + X_L)^2] \cdot 0 - R_L^2 (X_s + X_L) = 0$$

$$\{(R_s + R_L)^2 + (X_s + X_L)^2\} \cdot 0 - R_L^2 (X_s + X_L) = 0$$
$$- R_L^2 (X_s + X_L) = 0$$

$$\therefore \boxed{X_s + X_L = 0}$$

$$P_{max} = P|$$

$$X_s + X_L = 0$$

(c) Both R_L & X_L are varied simultaneously

In this case, both the conditions

$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$$

$$\text{&} \quad X_s + X_L = 0$$

valid at time

$$\Rightarrow R_L = R_s \\ -X_s = X_L \Rightarrow X_L = -X_s.$$

$$\text{So, } Z_L = R_L + jX_L$$

$$= R_L - jX_s$$

$$Z_L = Z_s^* \quad \text{or} \quad |Z_L| = \sqrt{R_L^2 + X_s^2}$$


$$P_{\max} = P \Big|_{R_L = R_s}$$

$$X_L = -X_s$$

$$= \frac{V_s^2}{4R_L} \quad \text{Watt} = \frac{V_s^2}{4R_s} \quad \text{Watt}$$

(B) Z_s and R_L

$$Z_s = (R_s + jX_s) \Omega$$

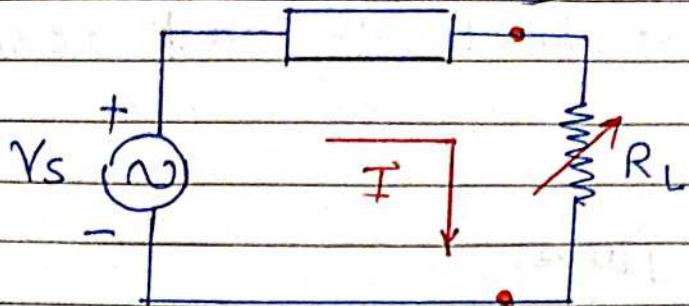

If is special case of (a) $X_L = 0$

i.e. $Z_L = R_L$ only when $X_L = 0$
so for MPT

$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2} \Big|_{X_L=0}$$

$$\boxed{R_L = \sqrt{R_s^2 + X_s^2}} \Omega$$

$$R_L = |R_s + jX_s|$$


$$\boxed{R_L = |Z_s| \Omega}$$

$$P_{max} = P \Big|_{R_L = \sqrt{R_s^2 + X_s^2}}$$

$\therefore \eta < 50\%$ (Nearest to 50%)

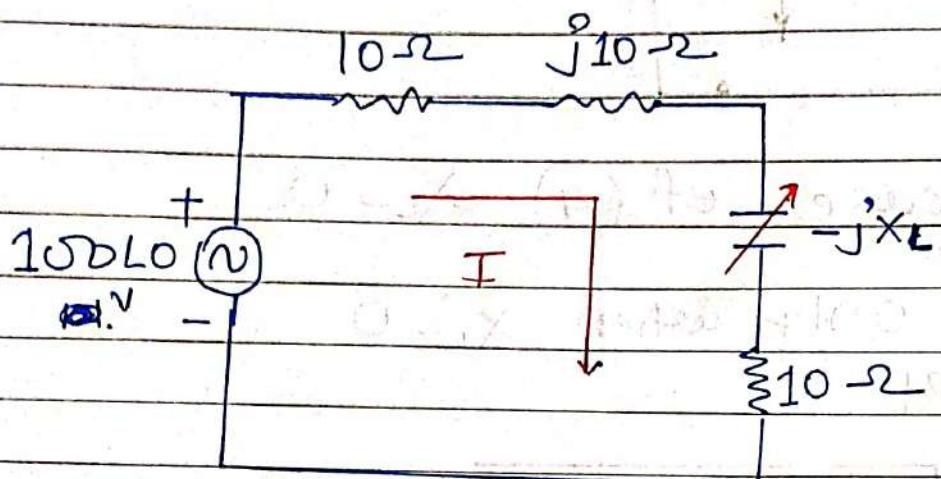Problems based on MPTT :-

Q. Determine the value of X_L at which power transfer to $10\ \Omega$ load resistor is maximum.



$$\Rightarrow Z_L = 10 - jX_L$$

$$= 10 + j(-X_L)$$

$$= R_L + j(X_L) \ \Omega$$

For MPTT

$$X_S + X_L = 0$$

$$10 - X_L = 0$$


$$X_L = 10$$

$$I = \frac{100\text{Lo}^\circ}{10 + j10 - j10 + 10} = 5\text{Lo}^\circ \text{ Amp.}$$

$$P_{\max} = |I|^2 R_L$$

$$= 5^2 \times 10 \\ = 250 \text{ Watt.}$$

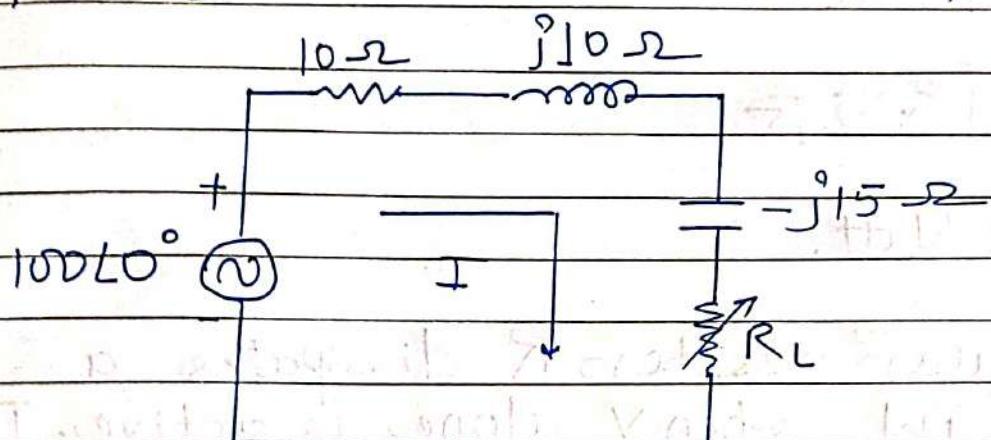Q. Determine the maximum power transfer to R_L



$$\Rightarrow Z_L = (R_L - j15) \Omega \\ = R_L + j(-15)$$

$$R_L + jX_L \quad \text{where } X_L = -15$$

for MPTT

$$R_L = \sqrt{R_s^2 + (X_L + X_S)^2}$$

$$= \sqrt{10^2 + (10 - 15)^2}$$

$$= 5\sqrt{5} \Omega$$

$$I = 100 \angle 0^\circ$$


$$\frac{10 + j10 - j15 + 5\sqrt{5}}{10 + j10 - j15 + 5\sqrt{5}}$$

$$P_{max} = |I|^2 R_L$$

$$= |I|^2 \times 5\sqrt{5}$$

$$= 236 \text{ Watts.}$$

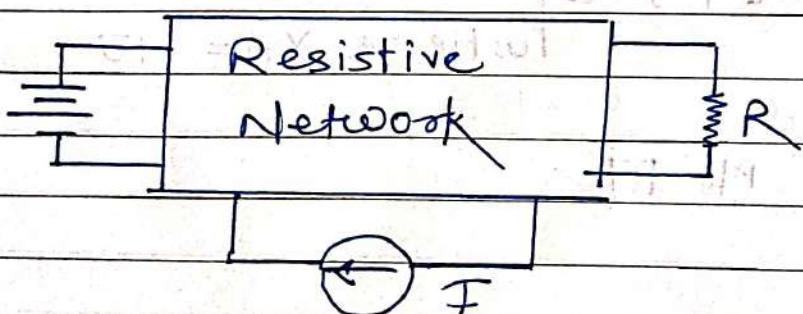Q. A particular resistor R dissipates a power of 4W when V alone is active. The same resistor R dissipates a power of 9 Watts when I alone is active. The maximum and minimum powers dissipated by R when both sources are active simultaneously will be



→ When only V is active

$$I_1^2 R = 4$$

$$I_1 = \frac{2}{\sqrt{R}}$$

When only I is active

$$I_2^2 R = 9$$

$$I_2 = \frac{3}{\sqrt{R}}$$


When both are active

$$I_{\text{total}} = I_1 + I_2 \quad \text{OR} \quad I_1 - I_2$$


$$P = (I_1 + I_2)^2 R = \left(\frac{3}{\sqrt{R}} + \frac{2}{\sqrt{R}} \right)^2 R = 25 \text{ Watt}$$

$$P = (I_1 - I_2)^2 R = \left(\frac{2}{\sqrt{R}} - \frac{3}{\sqrt{R}} \right)^2 R = 1 \text{ Watt}$$

Q. consider the following circuit

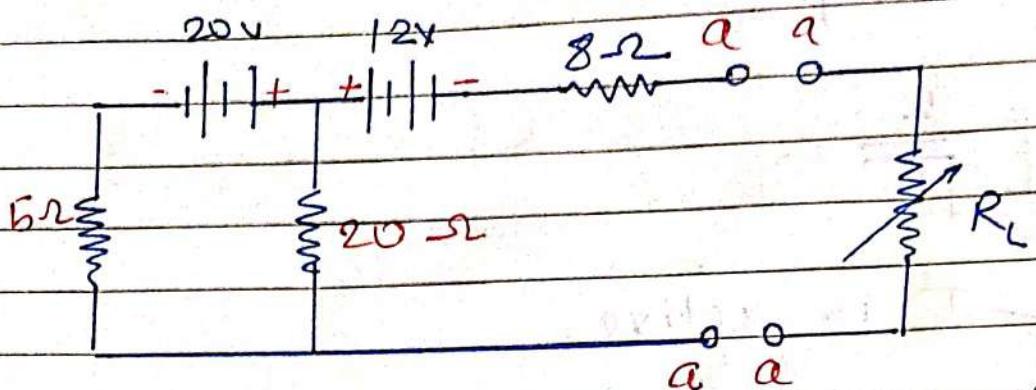

The maximum power delivered to 'R_L' is

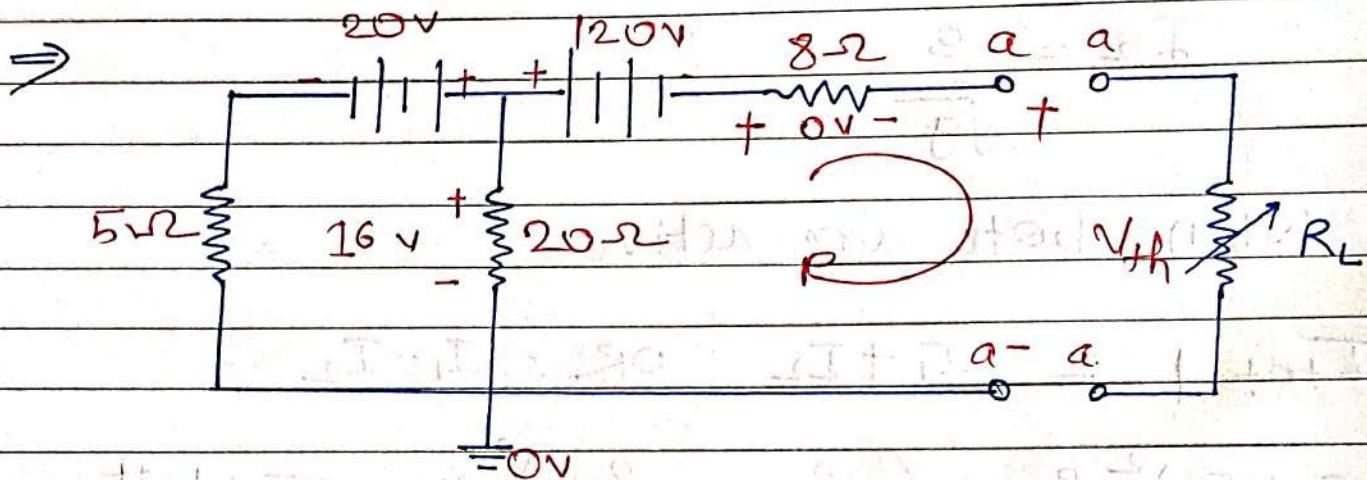

By Nodal

$$\frac{V}{5} - \frac{20}{5} + \frac{V}{20} = 0$$

$$\frac{4V - 80 + V}{20} = 0$$

$$5V - 80 = 0$$


$$V = \frac{80}{5} \Rightarrow 16V.$$

By KVL \Rightarrow

$$15 - 12 - V_{Th} = 0$$

$$V_{Th} = 4V.$$

R_{Th} :-

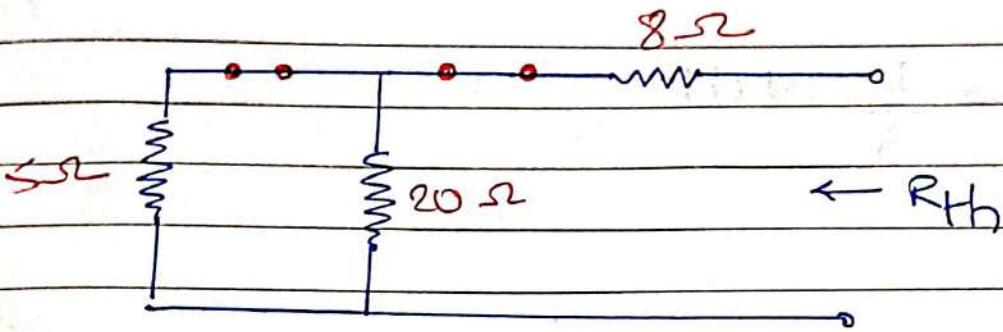


$$R_{Th} = (20 \parallel 5) + 8$$

$$= \frac{20 \times 5}{20+5} + 8$$

$$= 4 + 8$$

$$R_{Th} = 12\Omega$$

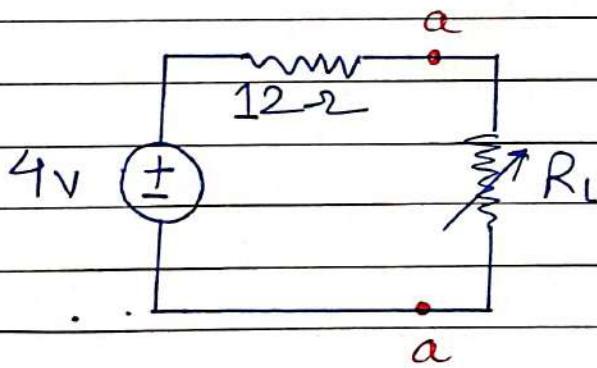

For maximum power transfer

$$R_L = R_s = 12 \Omega$$

$$P_{\max} = \frac{V_s^2}{4R_L} = \frac{4^2}{4(12)} = \frac{16}{48} = \frac{1}{3}$$

$$P_{\max} = \frac{1}{3} \text{ Watt}$$

Graph Theory :-

William Thomas
(1917 - 2002)


Tutte.

Introduction

Graph theory is geometrical representation of given electrical Network.

→ We are replacing all passive
elements by line segments
(Branches or edges)

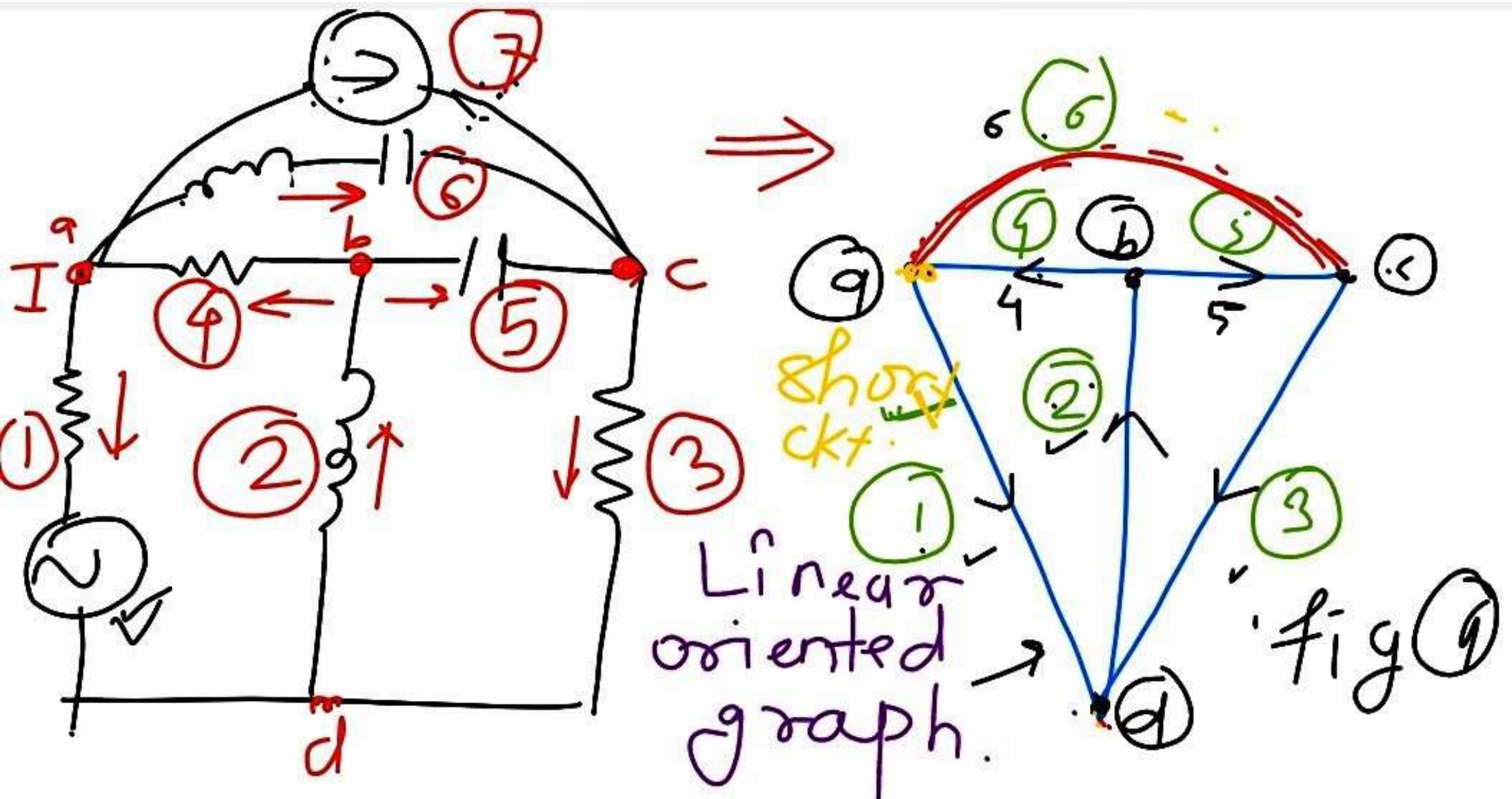- Ideal voltage sources
are replaced by short circuits
- ↳ Ideal current sources
are replaced by open circuit.




Observation

- ① Graph branches are less than or equal to the network branch.
- ② No. of nodes or vertices = 4
- ③ No. of edges or branches = 6

Complete Graph or Standard graph

Defⁿ.:- In a complete graph between any pair of nodes, only one branch is connected for all the combinations.


standard graph

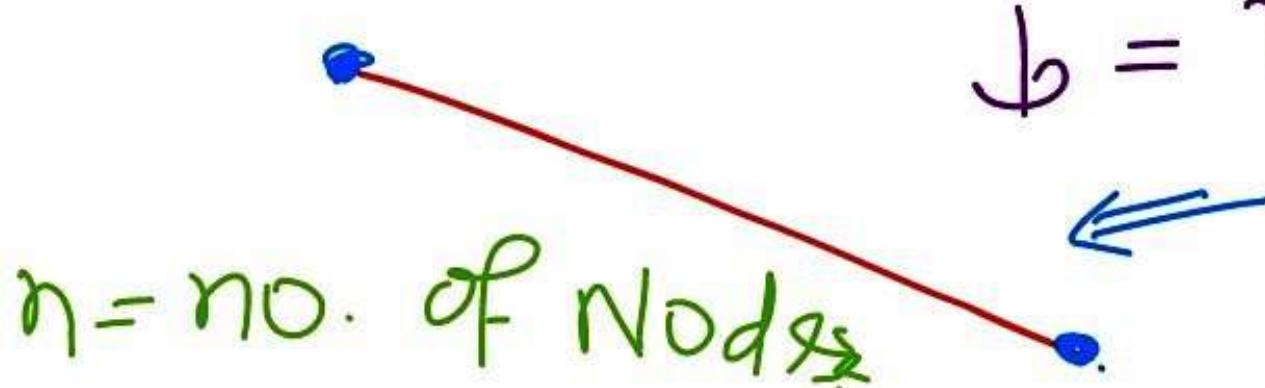


n = no. of Nodes

$$b = nC_2 = \frac{n(n-1)}{2}$$
$$= \frac{2(2-1)}{2}$$
$$= 1$$

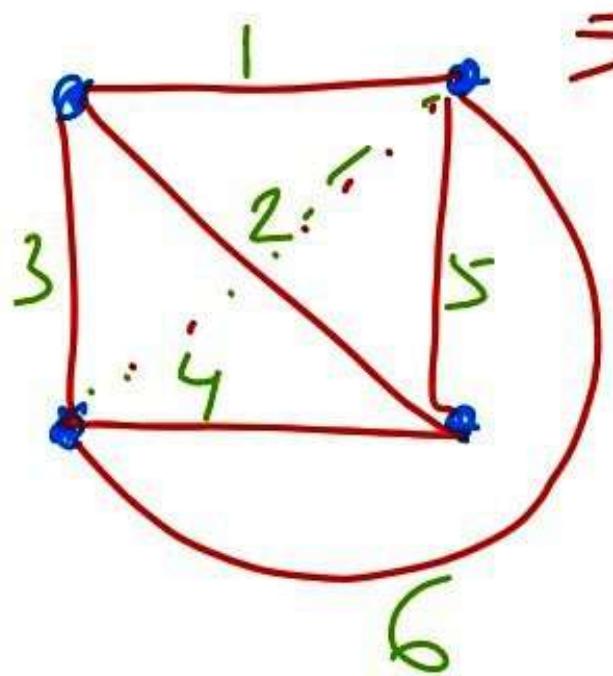
The minimum no. of edges
to make a graph complete with
 n nodes is nC_2



$$\Rightarrow \frac{4(4-1)}{2} = 6$$

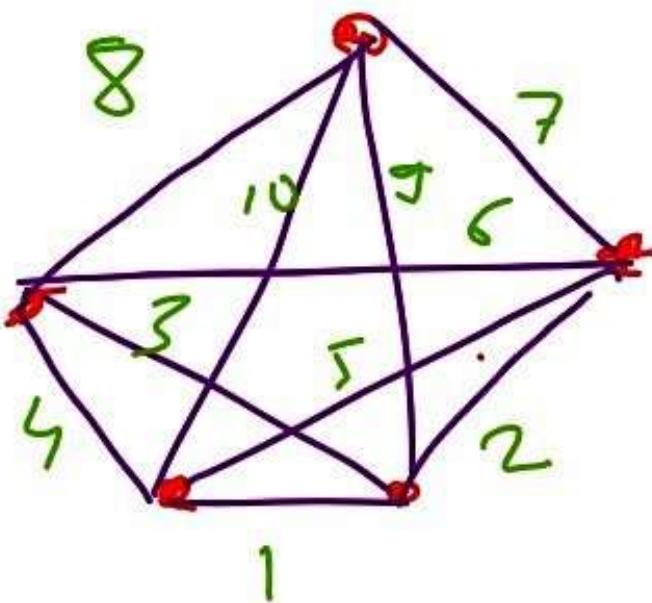

$$\Rightarrow \frac{5(5-1)}{2} = 10$$

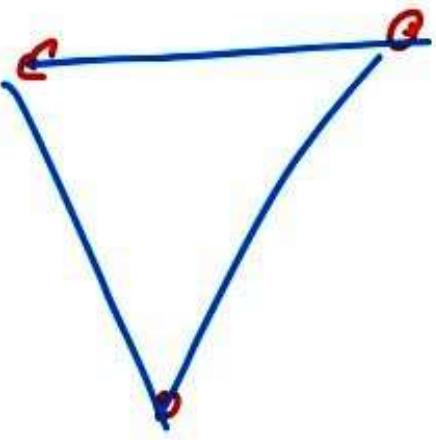

$$\frac{3(3-1)}{2} = 3.$$

for the given graph (fig 9)


$$n=4$$

$$\frac{4(4-1)}{2} = 6$$

Connected Graph


In connected graph, all the nodes are connected by atleast one branch. otherwise it is said to be unconnected.

fig. b

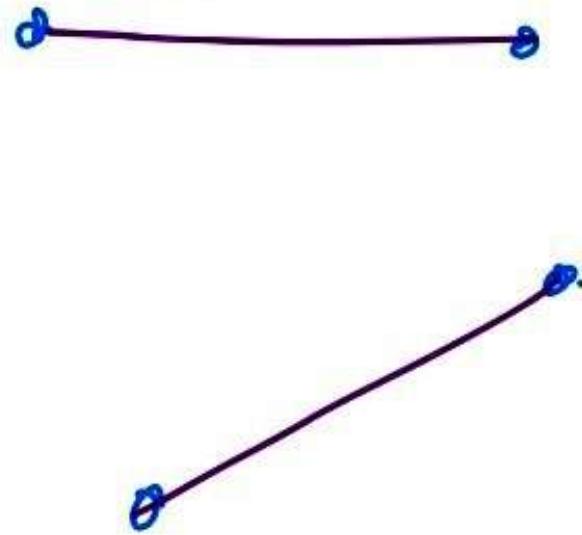


Connected graph.

fig c

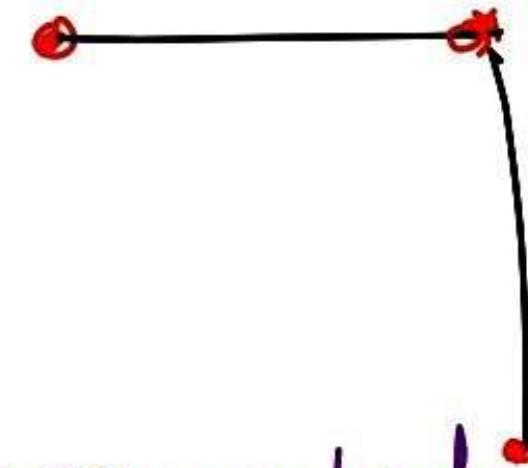

Unconnected
Graph.

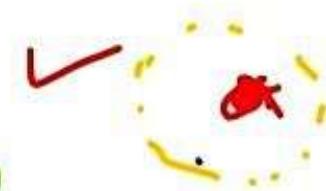


free
Node
or
Isolated
Node.

Sub graph



It is the graph with less number of branches (at least one branch) as compared to original graph.

Tree of Graph

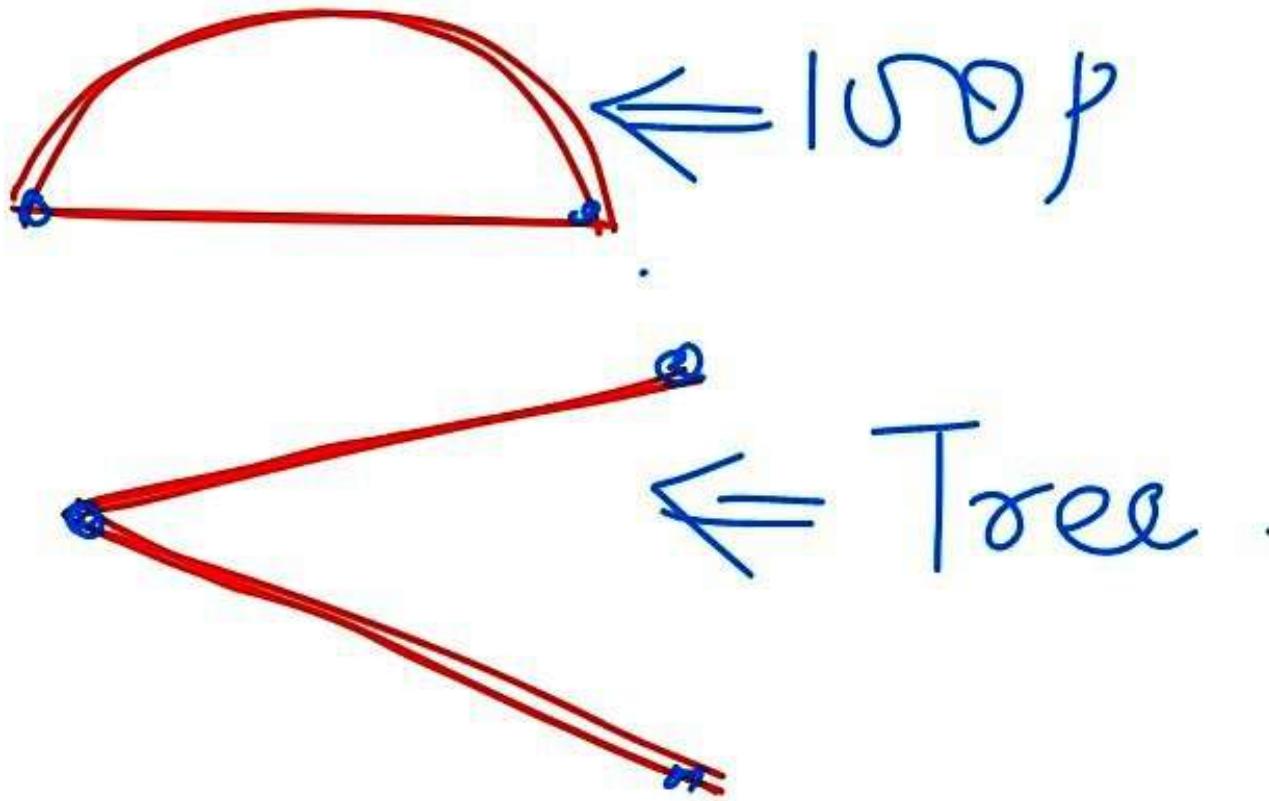Def'n:- Tree is a connected subgraph, which connects all the nodes without any closed loop.



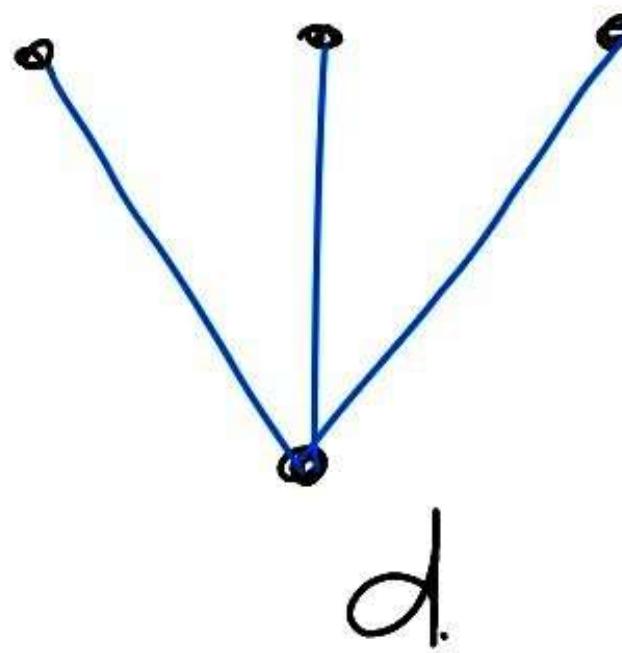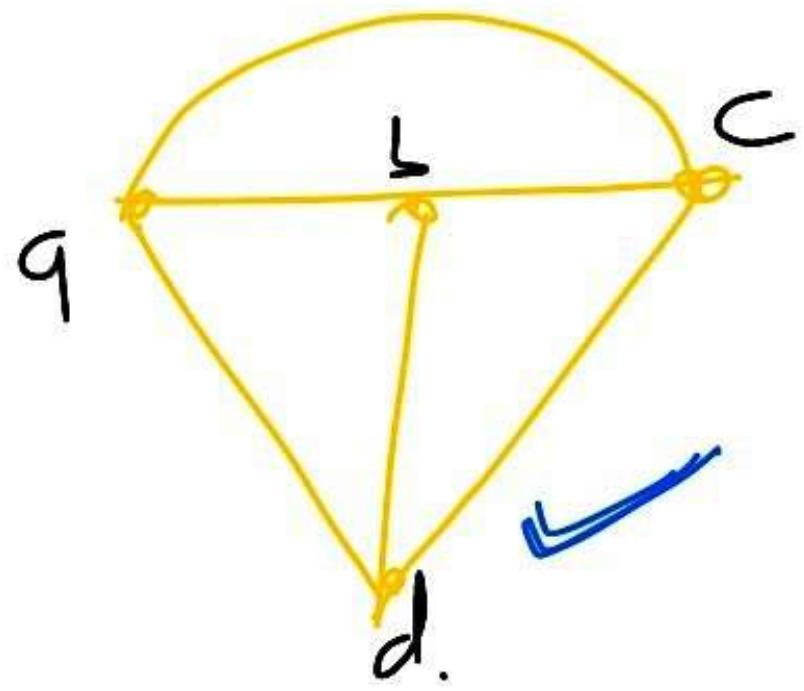- ⇒ No. of tree branches of any graph = $(n - l)$
- ⇒ Tree branches are called twigs.
- ⇒ for present graph ($4 - 1 = 3$)
Tree branches.
- ref fig ⑨



→ The no. of possible trees
of a complete graph with
 n nodes is $n^{(n-2)}$

Present graph

$$4^{(4-2)} = \underline{16}$$

$$\underline{n}$$

Possible Trees

Co-tree or the complimented Tree

Defn: It is a tree formed with all the removed branches from the original graph in order to construct a tree.



⇒ Co-tree branches are called links or chords.

⇒ No. of links

$$L = b - (n-1) \Rightarrow b - n + 1$$

$b \Rightarrow$ Branches. $L = 6 - 4 + 1$

$n \Rightarrow$ Nodes. $= 3$ links

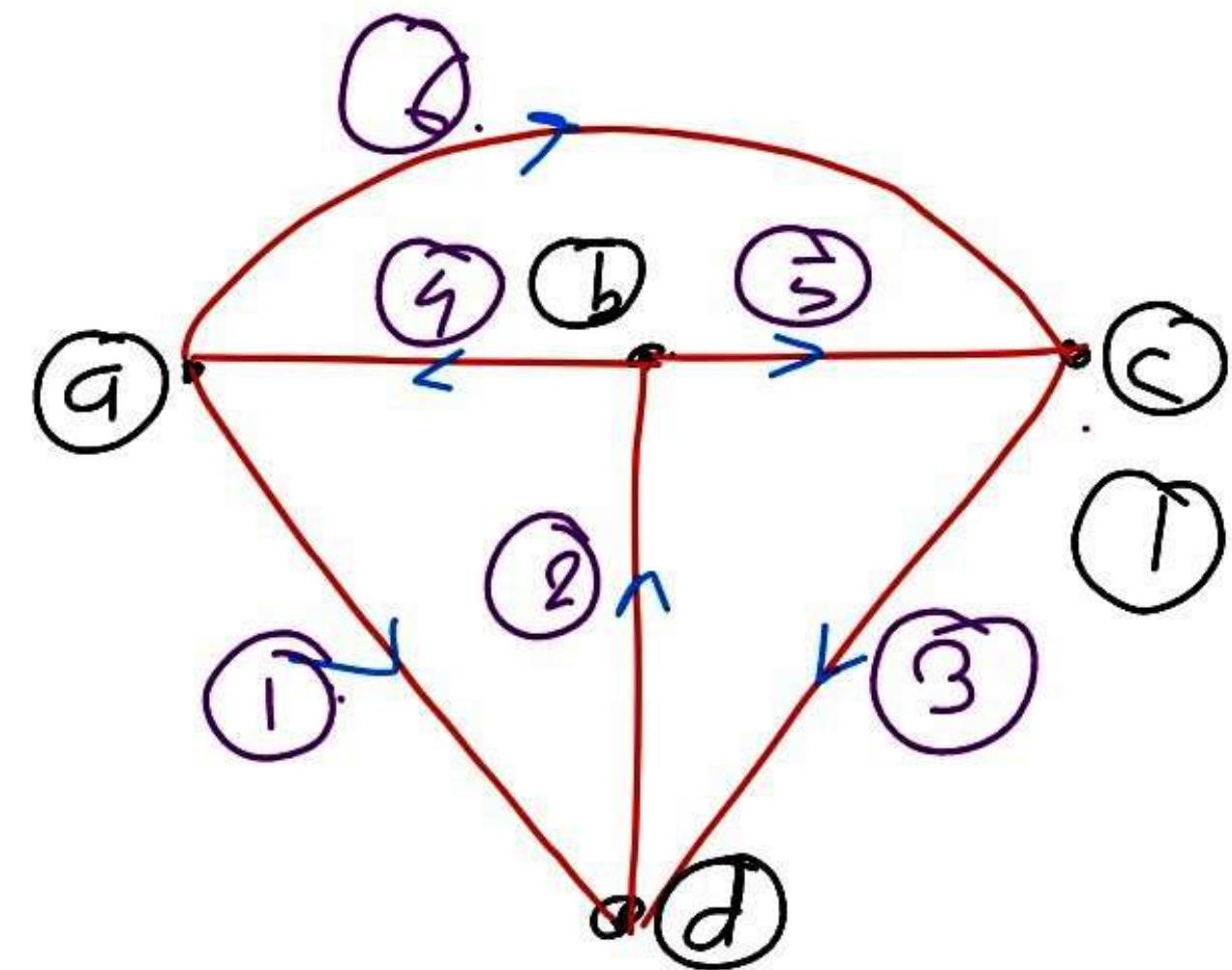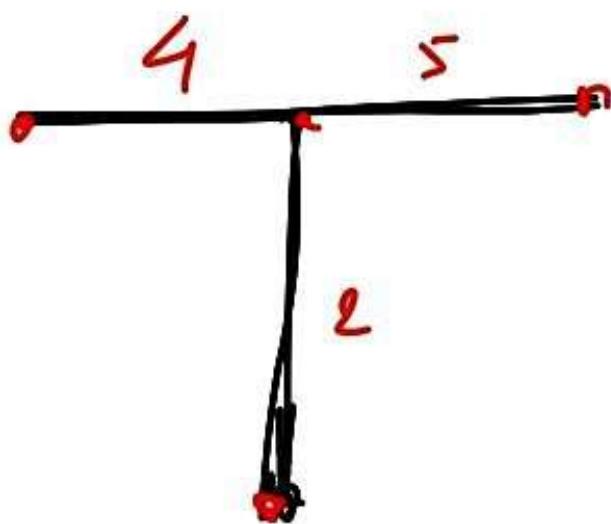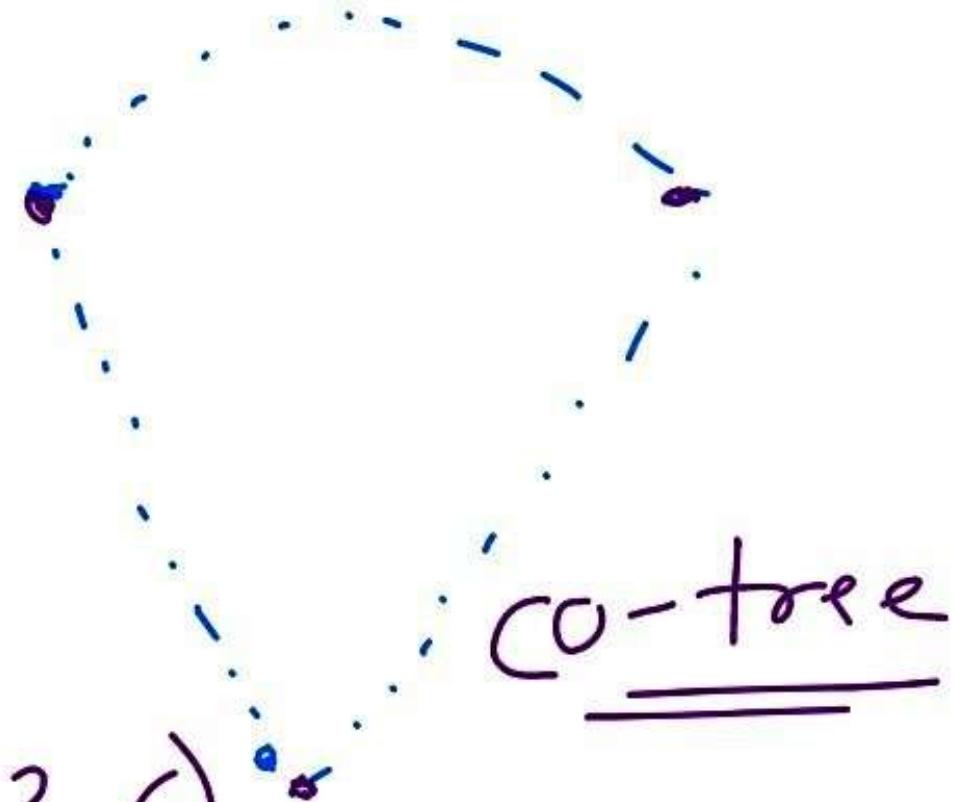

 $T(2, 4, 5)$.


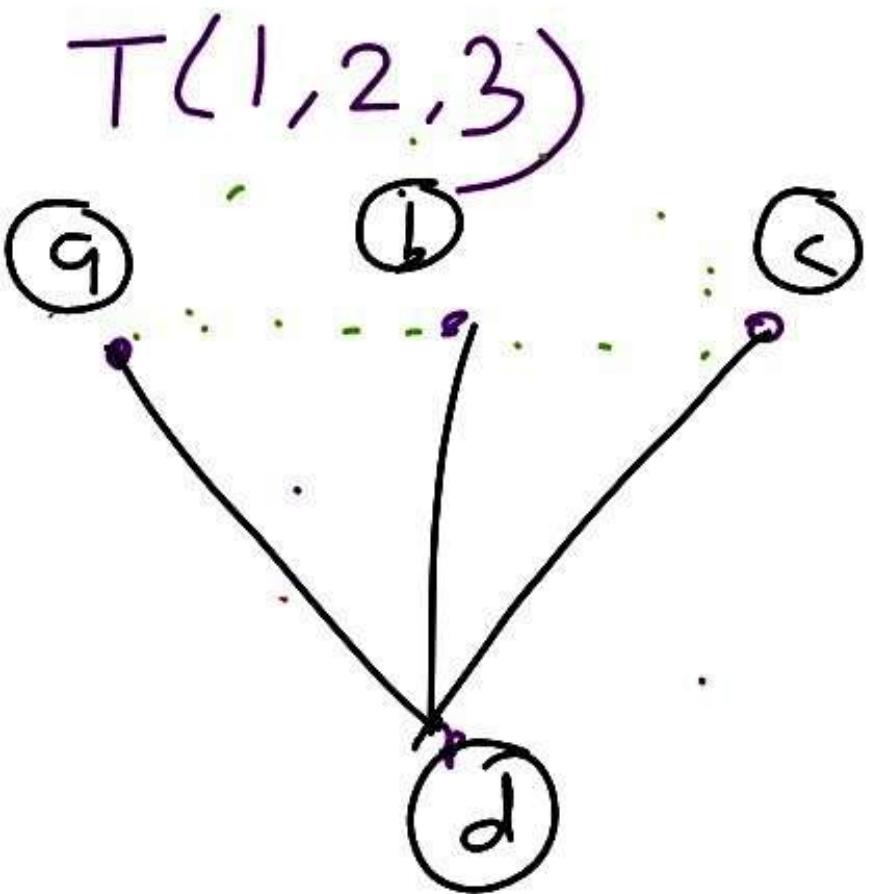
$T(2, 4, 5)$



Tree of
graph.


$L(1, 3, 6)$







$L(4, 5, 6)$
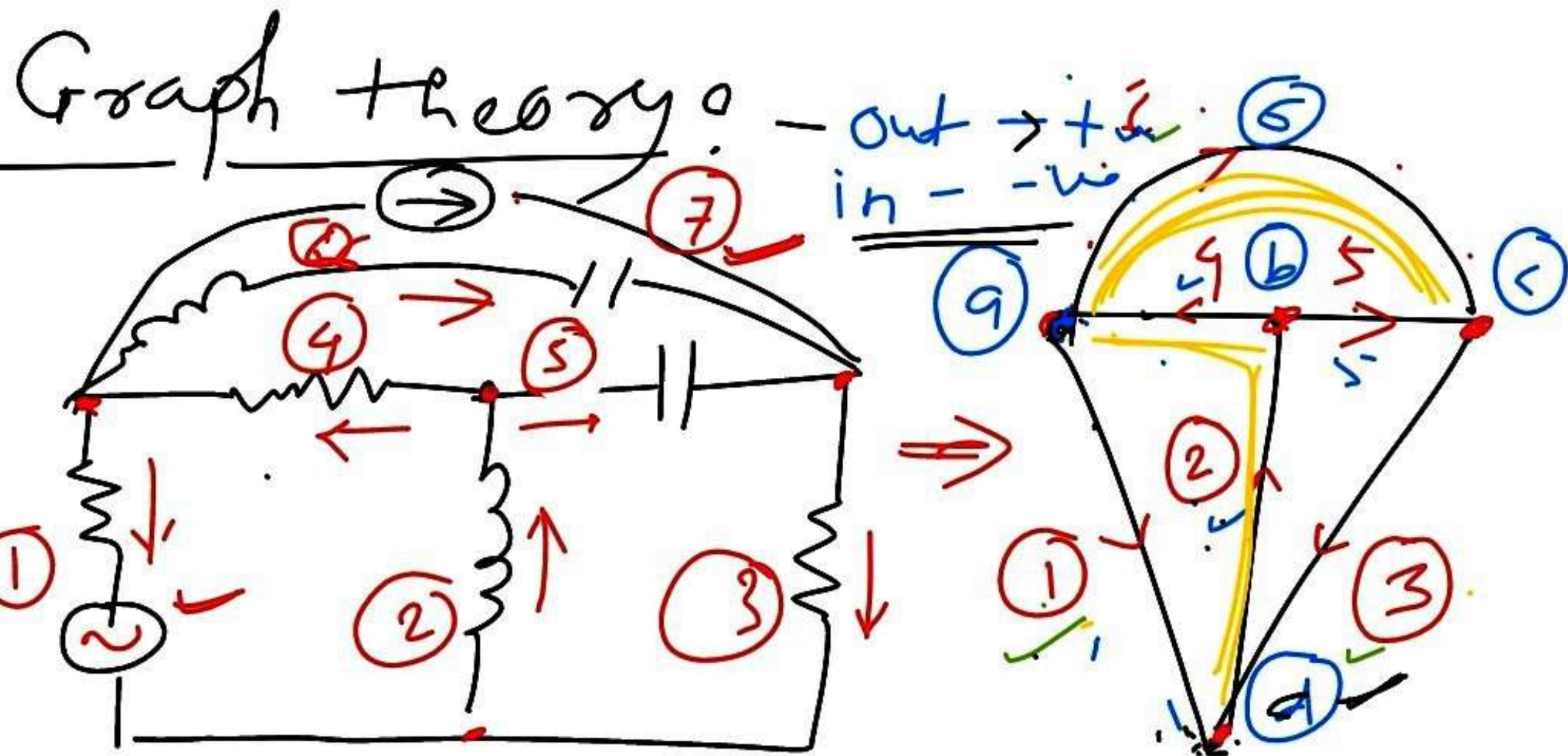
```
graph LR; i((i)) --- o((o)); o --- a((a)); a --- m((m)); m --- n((n))
```



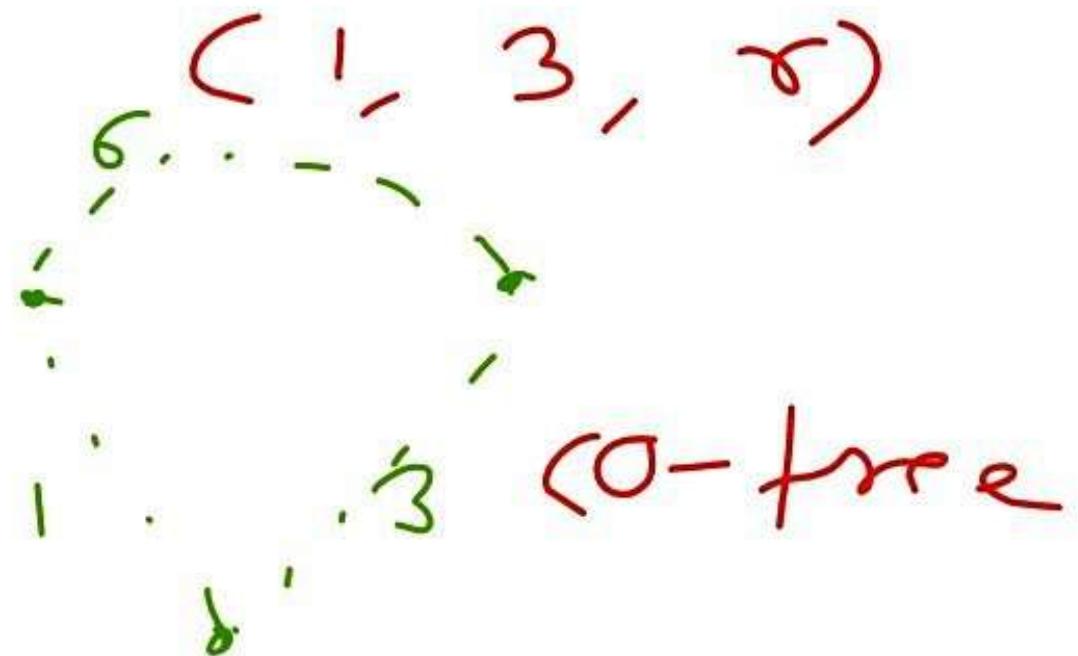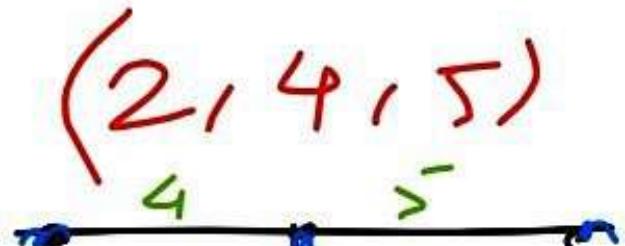

obs. - Tree + co-tree \Rightarrow
original graph.

Incidence Matrix (A_I)

Let us take the branch

current $i_1, i_2, i_3, \dots, i_6$
for the branches 1, 2, 3, ..., 6
respectively.

Writing the KCL eqⁿ at each node.

(a) I \Rightarrow $i_1 - i_4 + i_6 = 0$

(b) II \Rightarrow $-i_2 + i_4 + i_5 = 0$

(c) III \Rightarrow $i_3 - i_5 - i_6 = 0$


(d) IV \Rightarrow $-i_1 + i_2 - i_3 = 0$

$$\begin{array}{c}
 \text{I} \\
 \text{II} \\
 \text{III} \\
 \text{IV}
 \end{array}
 \left[\begin{array}{cccccc}
 1 & 2 & 3 & 4 & 5 & 6 \\
 1 & 0 & 0 & -1 & 0 & 1 \\
 0 & -1 & 0 & 1 & 1 & 0 \\
 0 & 0 & 1 & 0 & -1 & -1 \\
 -1 & 1 & -1 & 0 & 0 & 0
 \end{array} \right]_{4 \times 6} = \left[\begin{array}{c}
 i_1 \\
 i_2 \\
 i_3 \\
 i_4 \\
 i_5
 \end{array} \right]_{5 \times 1} = \left[\begin{array}{c}
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{array} \right]_{5 \times 1}$$

\Downarrow $A\vec{x}$
 $n \times b =$
 (6×1)
 $b \times 1$

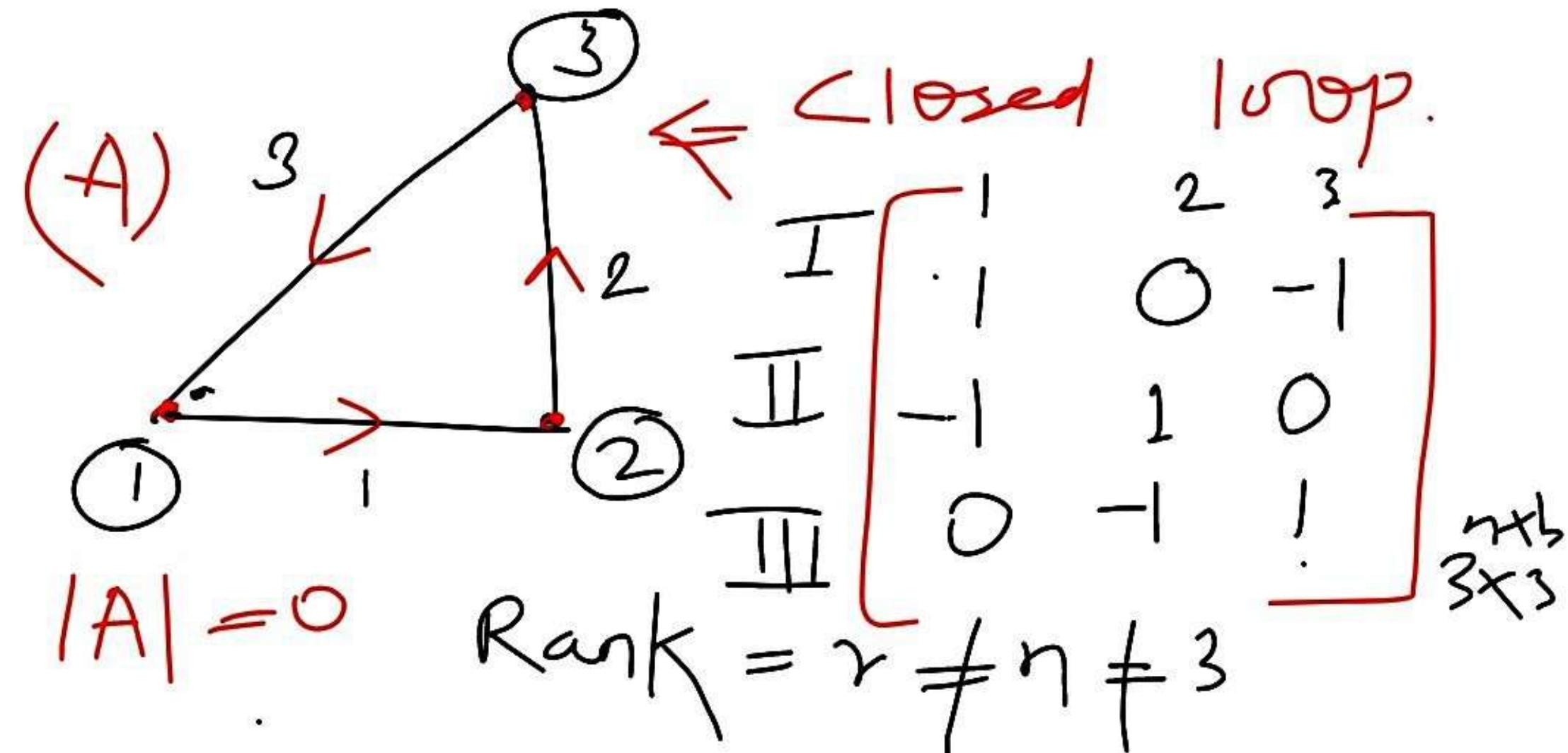- 1) The order of incidence matrix
 $(n \times b) \Rightarrow (4 \times 6)$
- 2) The rank of incidence matrix
is equal to the rank of graph.
 $= (n - 1) \Rightarrow (4 - 1) = 3$.


③ The determinant of the complete incidence matrix of closed loop is always equal zero.



Rank of this matrix = $r = n - 1$

$$= 3 - 1 = 2$$

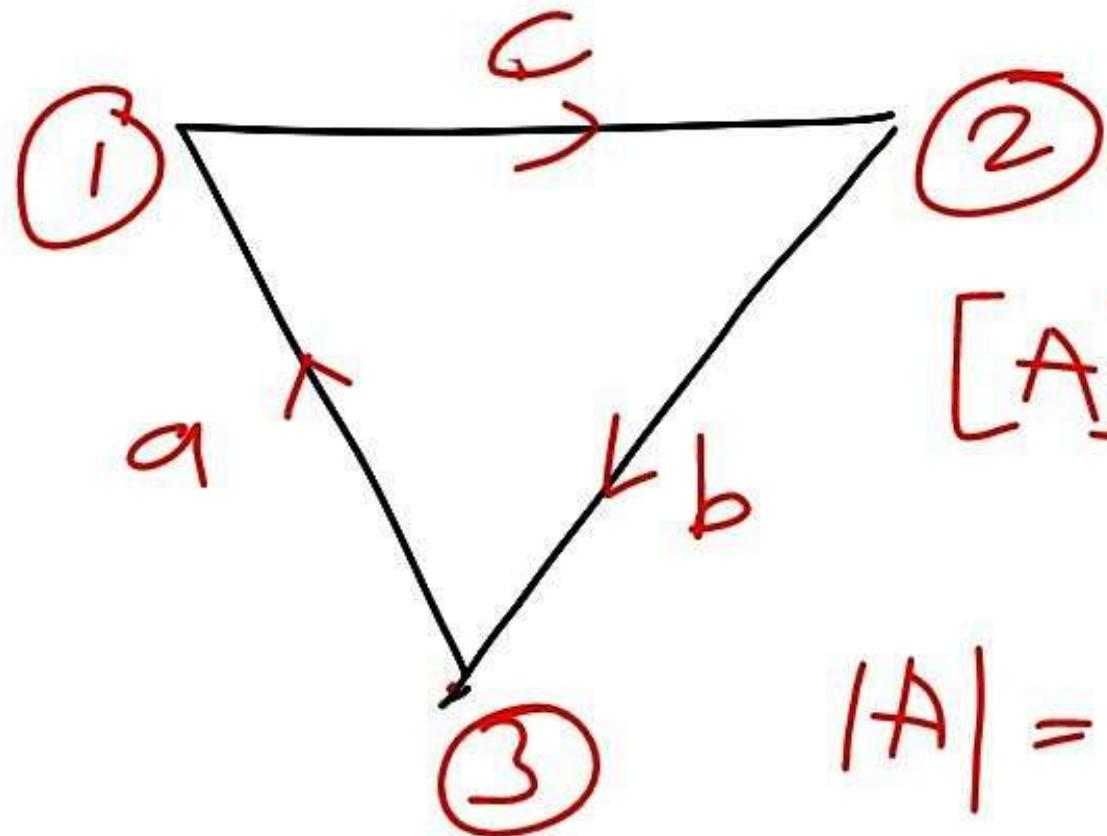\Rightarrow Incidence matrix of a closed loop graph is of $n \times n$



$$[A] = \begin{bmatrix} -1 & 0 & 1 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \end{bmatrix}$$

$$|A| = 0$$

Tie-set matrix :-

(fundamental loop matrix
or fundamental circuit
matrix)

Defⁿ: It is a closed path which contains only one link together with any number of twings (tree branches).

Let us take the branch voltages $v_1, v_2, v_3, \dots, v_6$ for the branches 1, 2, ..., 6 resp. of loops or cuts or tie set.


Minimum no. of loop or mesh eqn required to solve the n/w.


Steps.

① Select a tree.

$T(2, 4, 6)$ ✓

$L(1, 3, 5)$.


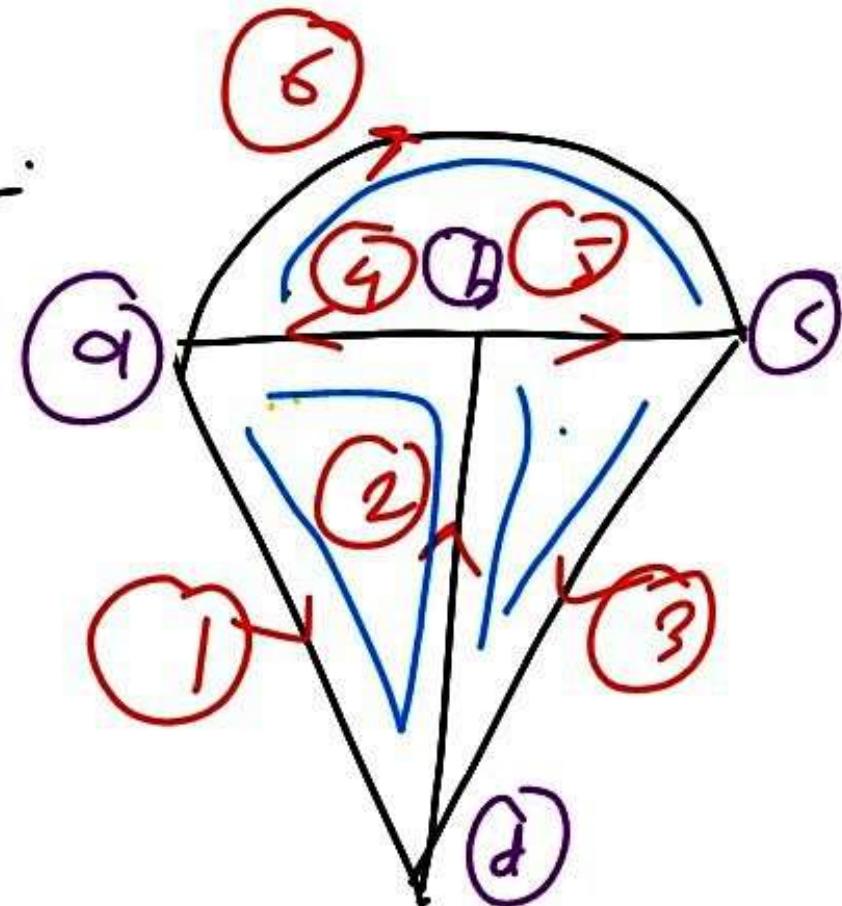


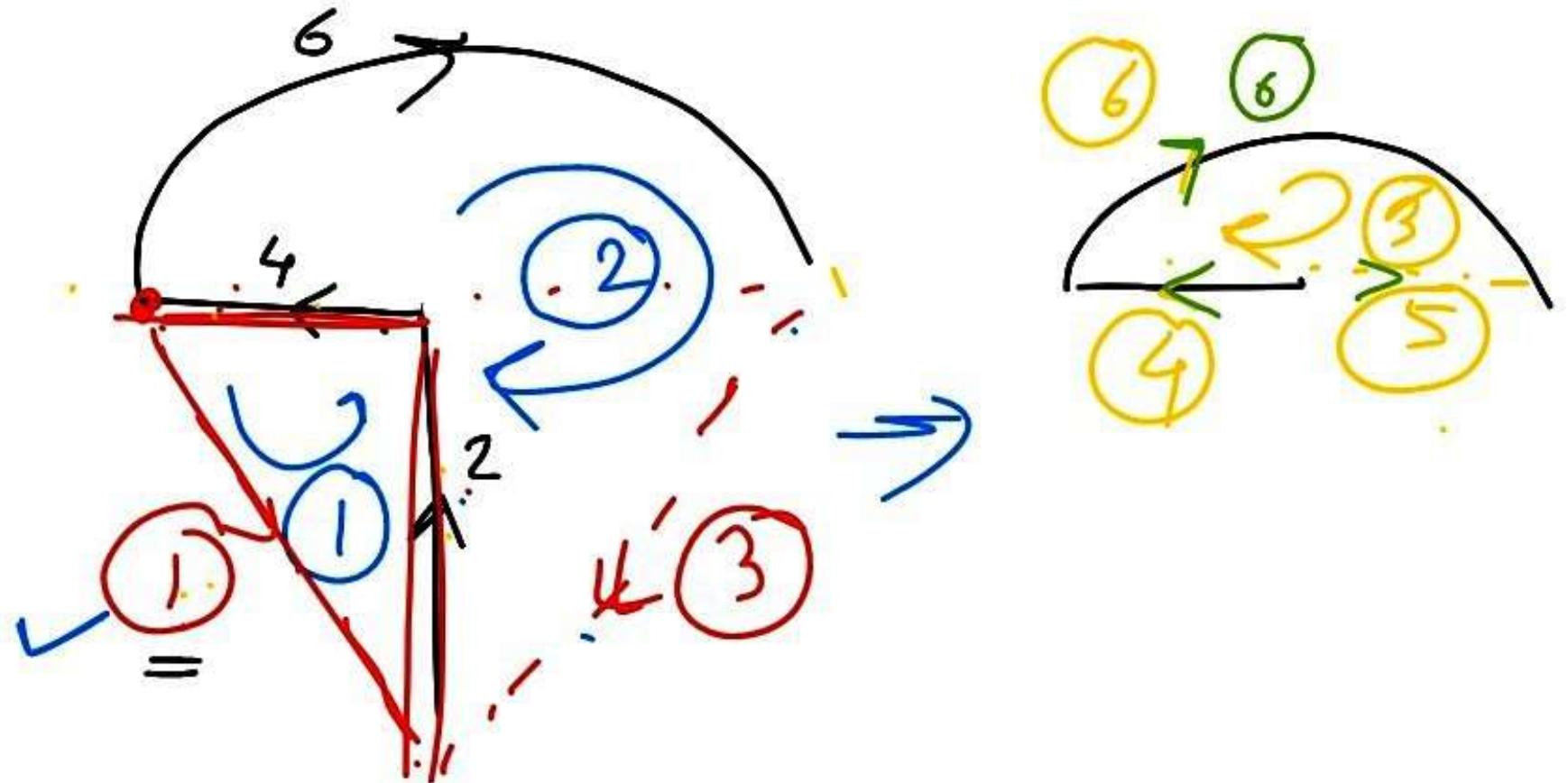


$$f_1 \Rightarrow v_1 + v_2 + v_4 = 0$$

$$f_2 \Rightarrow v_2 + v_3 + v_4 + v_6 = 0$$

$$f_3 \Rightarrow \dots$$

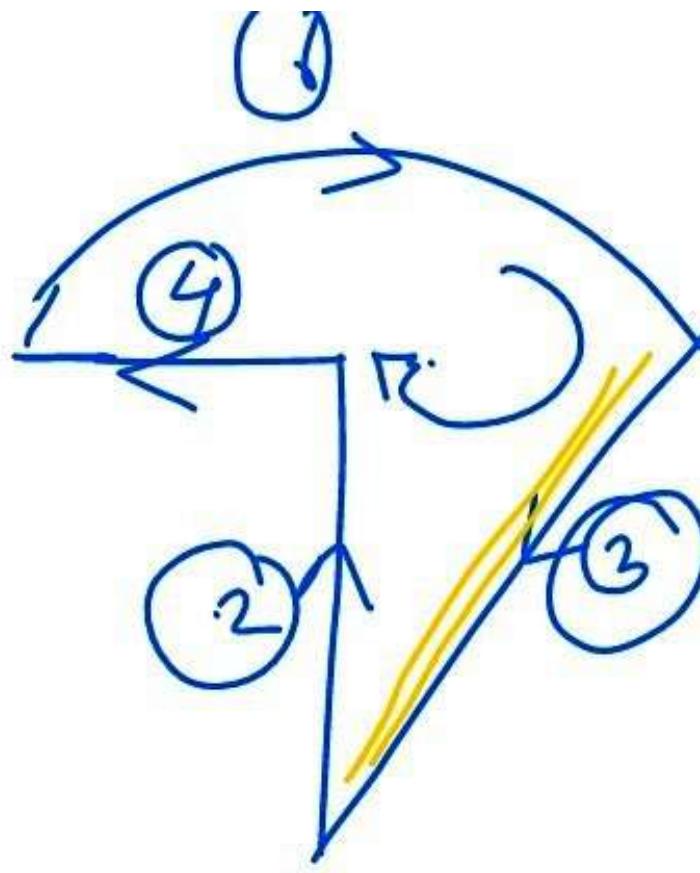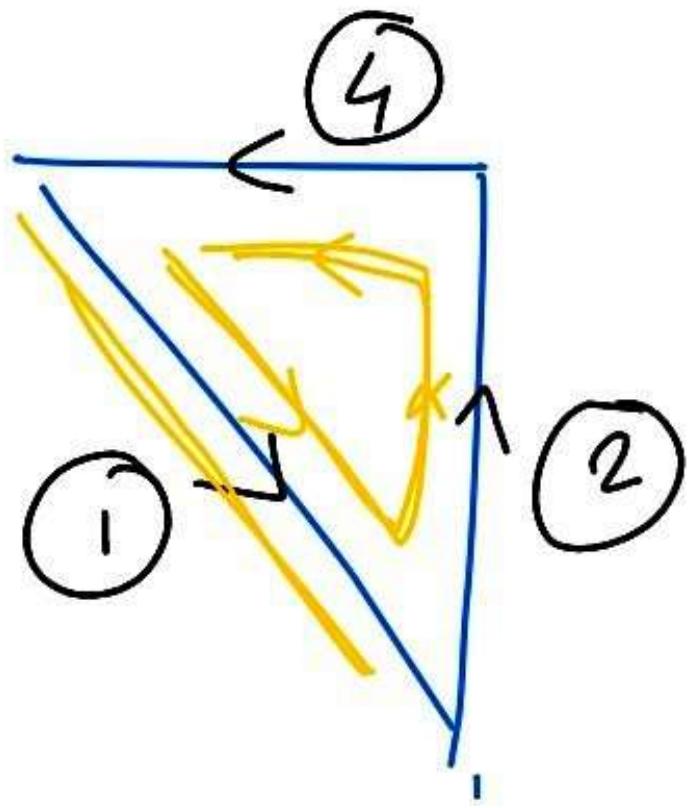

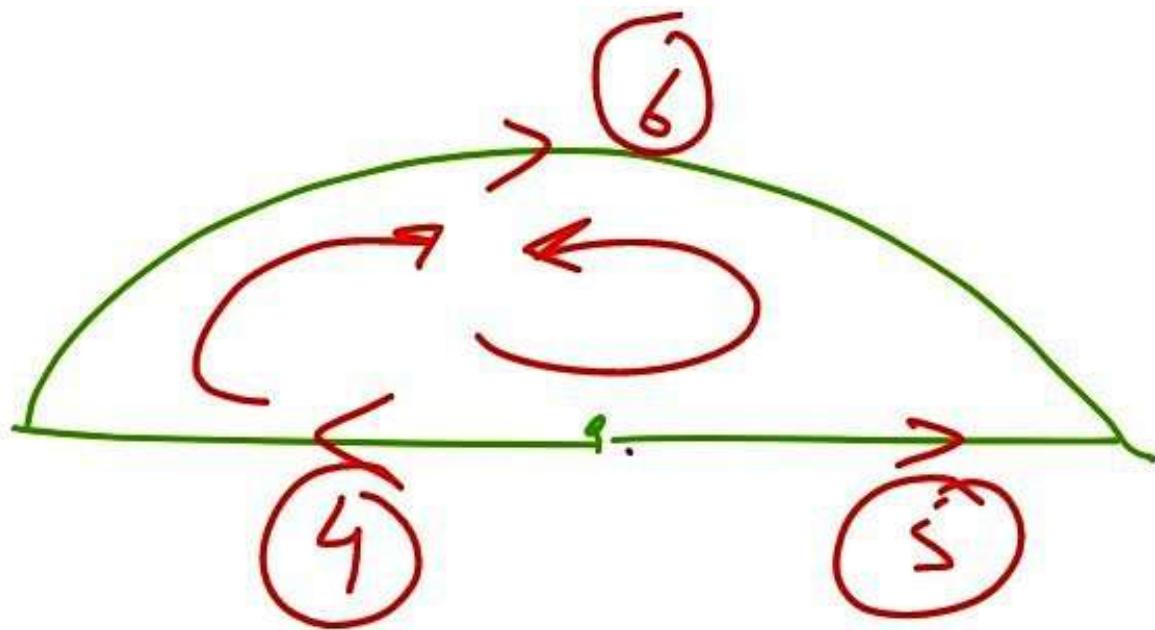

$$V_5 - V_4 - V_6 = 0$$

... -

Tie set matrix (B_r)

$$\begin{array}{l} f_1 \checkmark \\ f_2 \checkmark \\ f_3 \checkmark \end{array} \left[\begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & \leftarrow \\ 1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 1 & 0 & 1 \\ 0 & 0 & 0 & -1 & 1 & -1 \end{array} \right] = 3 \times 6 \quad \left[\begin{array}{c} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{array} \right]_{x1} = \left[\begin{array}{c} 0 \\ 0 \\ 0 \end{array} \right]_{(3 \times 1)}$$

$(b-n+1) \times b \Rightarrow$

$$(b-n+1) \Rightarrow \text{Rank of Tie set matrix}$$
$$6-4+1 = 3.$$

② No. of f-loop = $b-n+1$


③ For complete graph there
are $n^{(n-2)}$ f-loop matrices.

Construct the correct graph
of Network shown below.

$$VS \Rightarrow SC$$


$$CS \Rightarrow OP$$




4 ✓
6 ✓
3 ✓


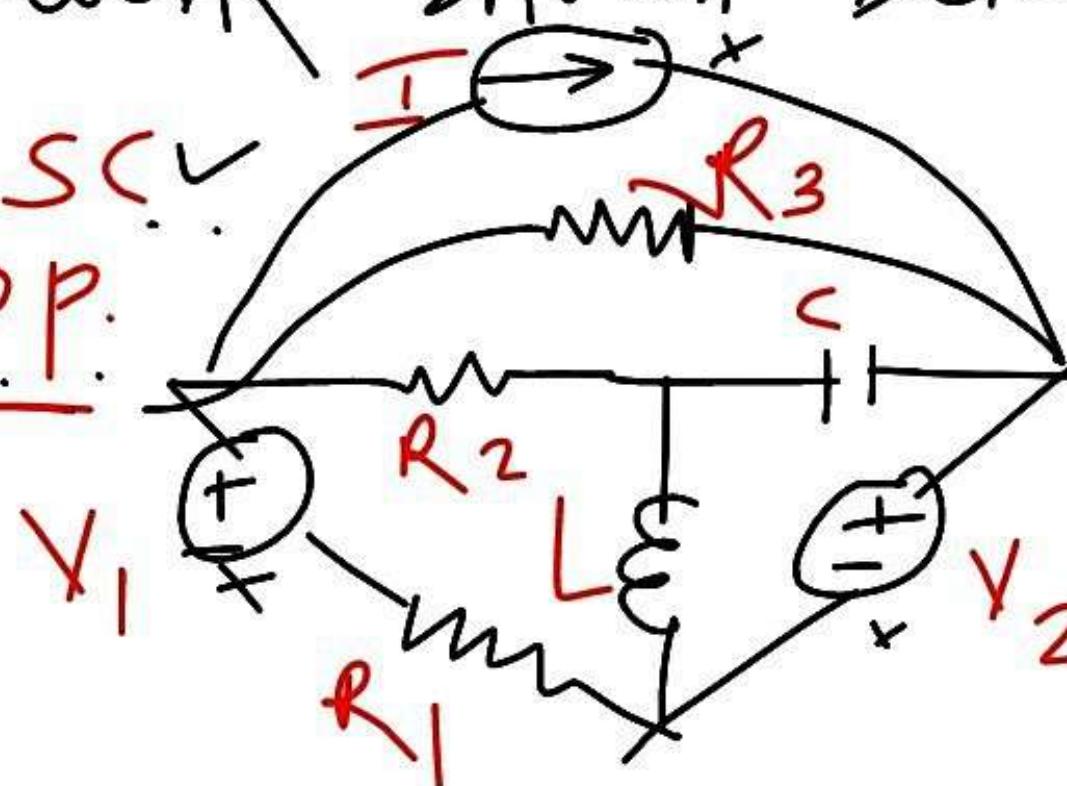



No. of
Nodes = ?

Branches = 7
Independent
Sources = 3

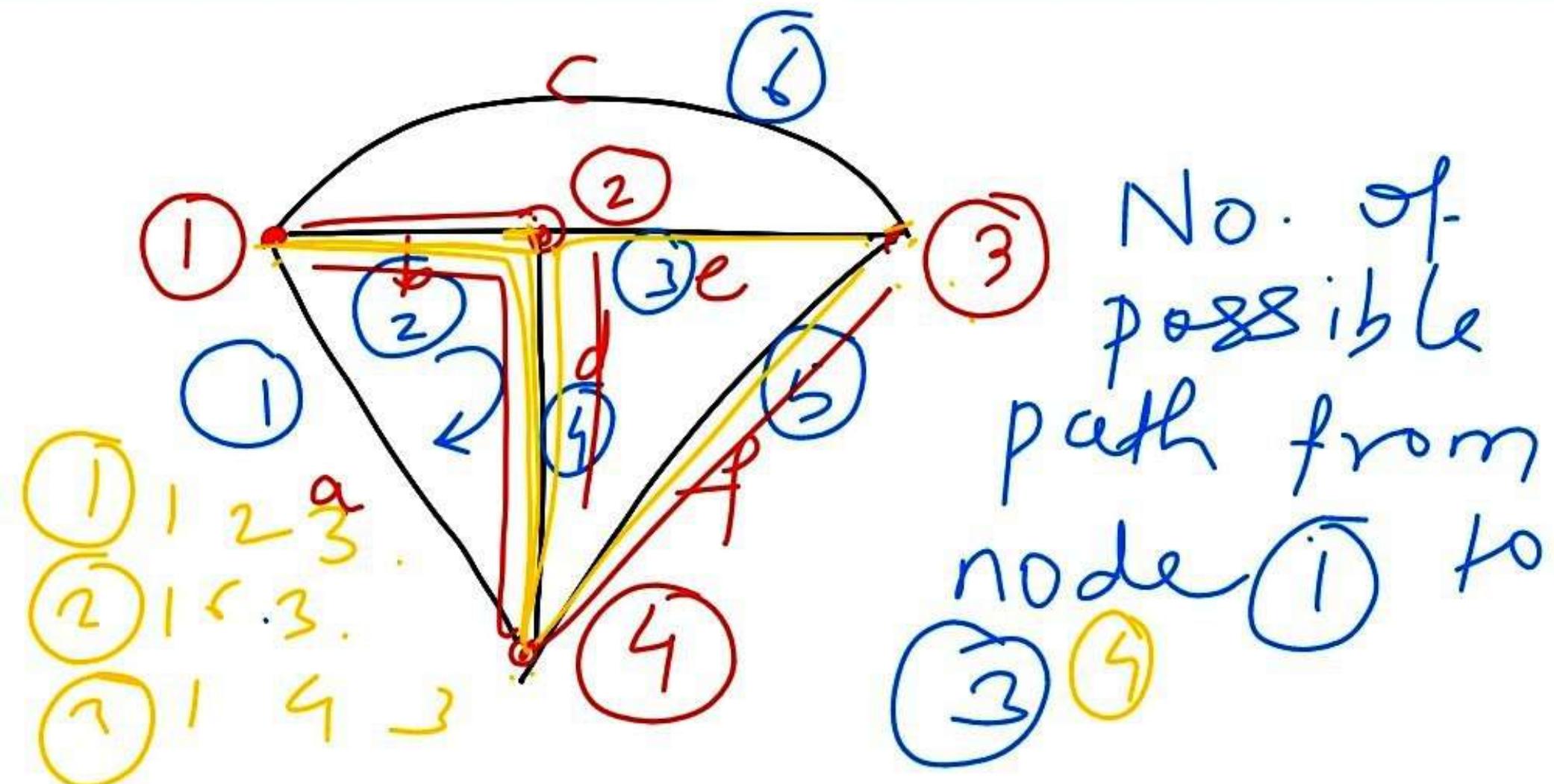

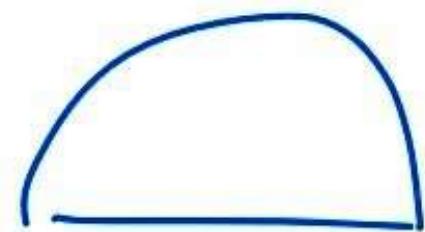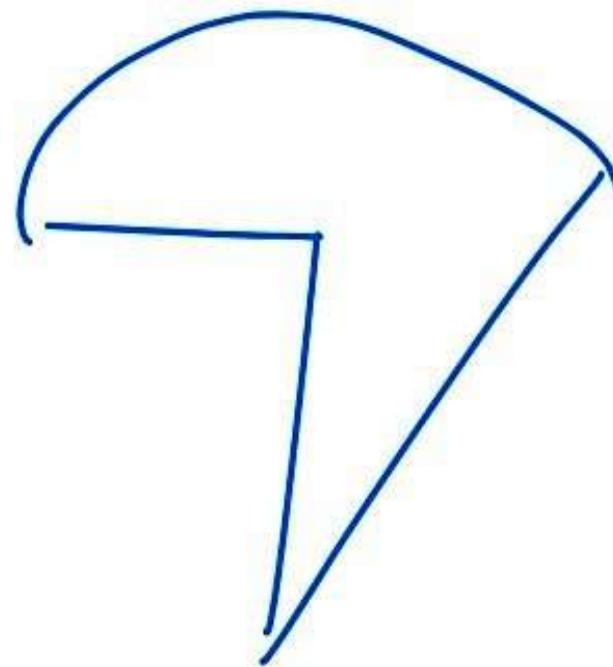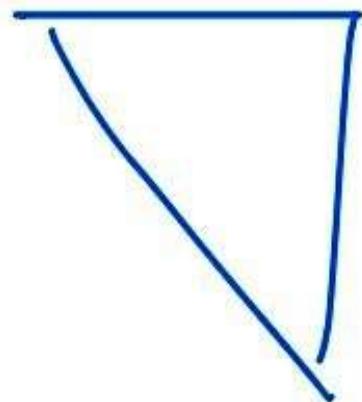

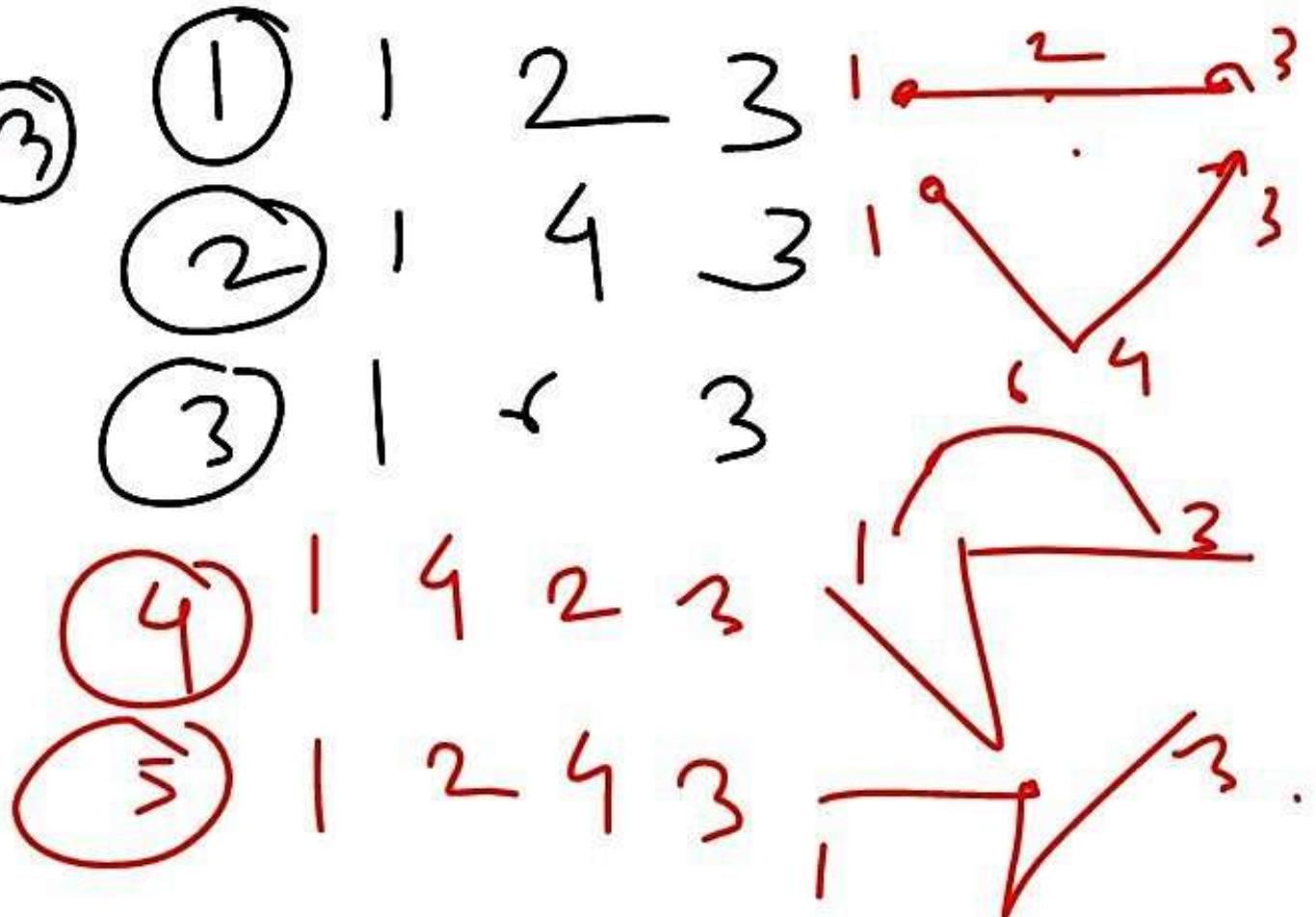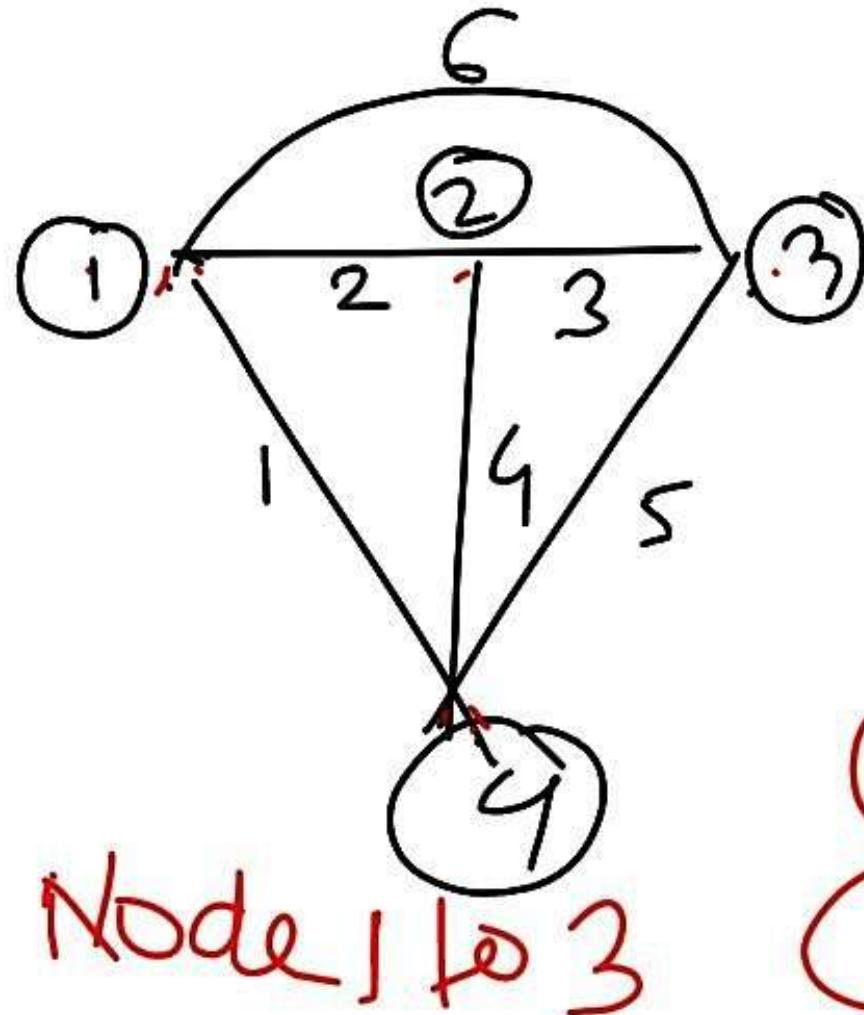

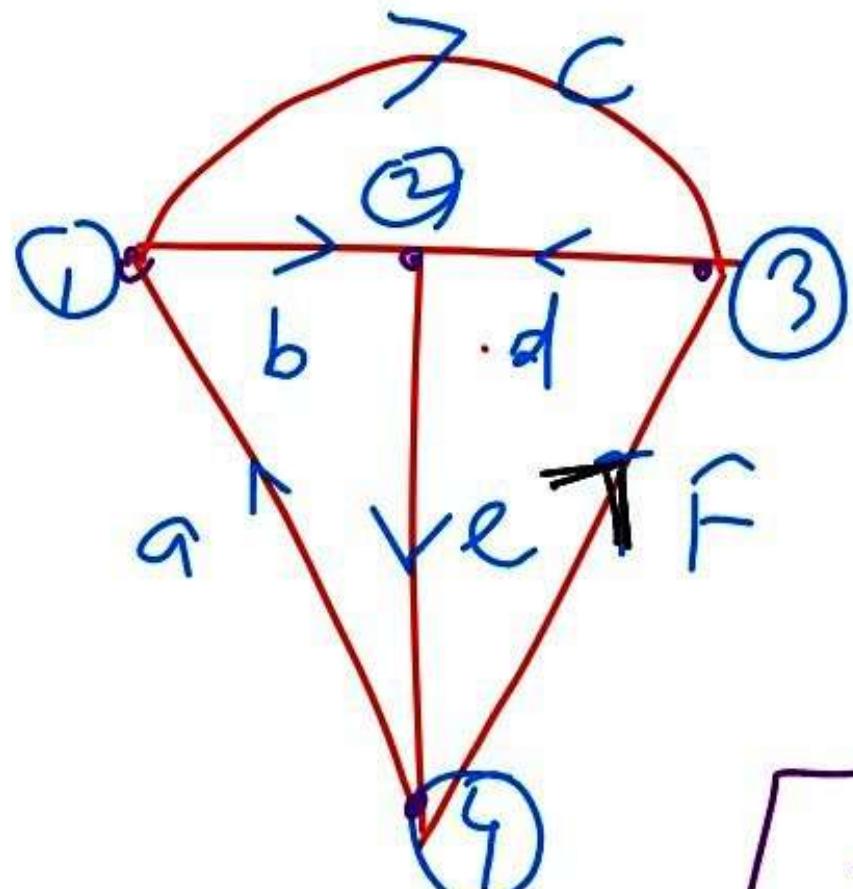

Construct the complete incidence matrix for the oriented graph.

$[A]$

$$[A] = \begin{pmatrix} a & b & c & d & e & f \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & -1 \\ 1 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 0 & 0 & 1 & 0 \end{pmatrix} \quad 4 \times 6$$


(1) (2) (3) (4)

Construct a oriented graph of a Network where Incidence matrix is given as

$$\begin{array}{c} \text{a} \\ \text{b} \\ \text{c} \\ \text{d} \\ \text{e} \\ \text{f} \end{array} \quad \begin{bmatrix} 1 & 1 & 0 & 0 & -1 & 0 \\ 2 & 0 & -1 & -1 & 0 & 0 \\ 3 & 0 & 0 & 1 & -1 & 1 \\ 4 & -1 & 0 & 0 & 1 & 0 \end{bmatrix}$$

No. of nodes - 4

No. of branches = 6

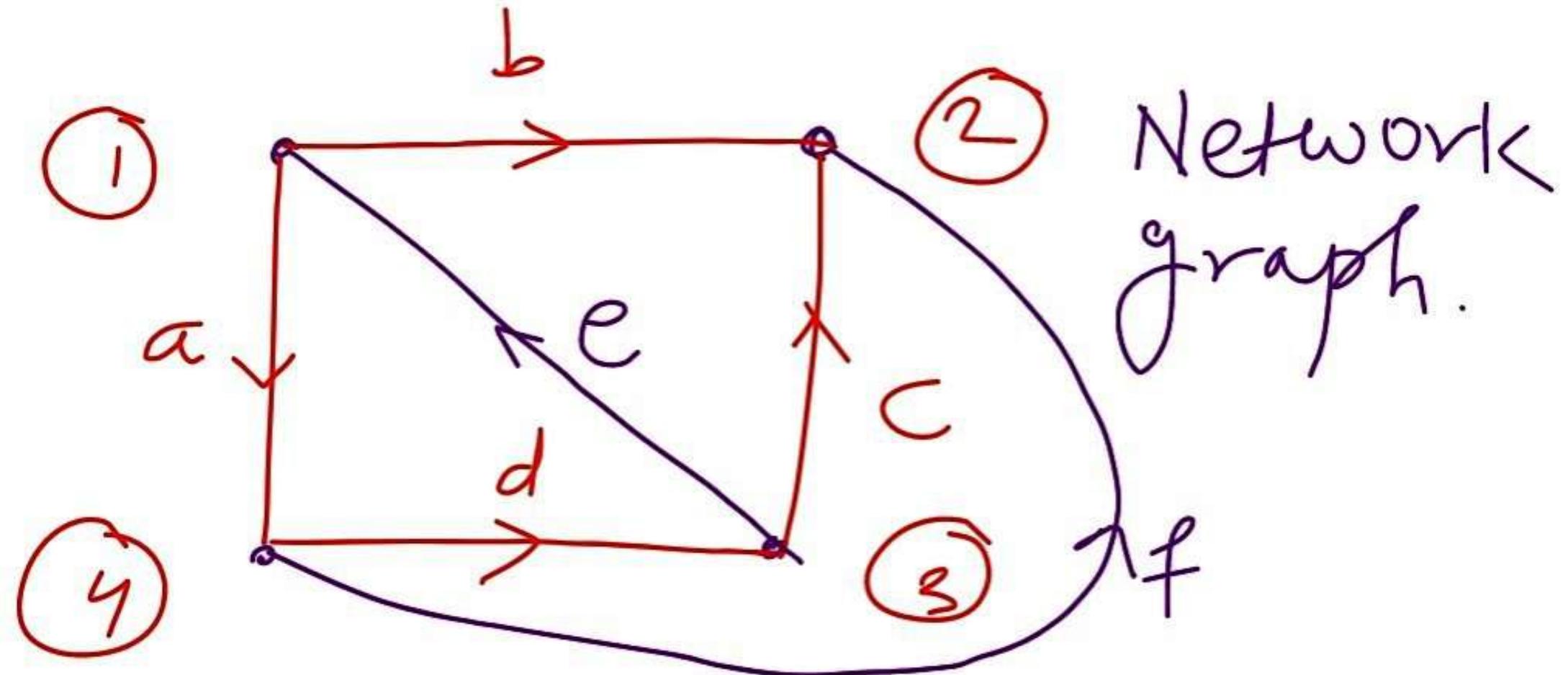

A graph of an electrical net
has 4 Nodes & 7 branches.
The no. of links 1, with
respect to chosen tree
would be.

$$\Rightarrow 4 \Rightarrow b - (n - 1) = 4$$

A N/w. has 8 Nodes
5 independent loops

No. of branches = ?

$\Rightarrow 12$

$$\checkmark l = b - (n - 1) \Rightarrow \boxed{b = 12}$$

$s = b - 7$


→ 6 Nodes & 9 Branch


Independent loops = 1

$$l = b - (n - 1) =$$


$$9 - (6 - 1) \underset{=} \Rightarrow 4$$
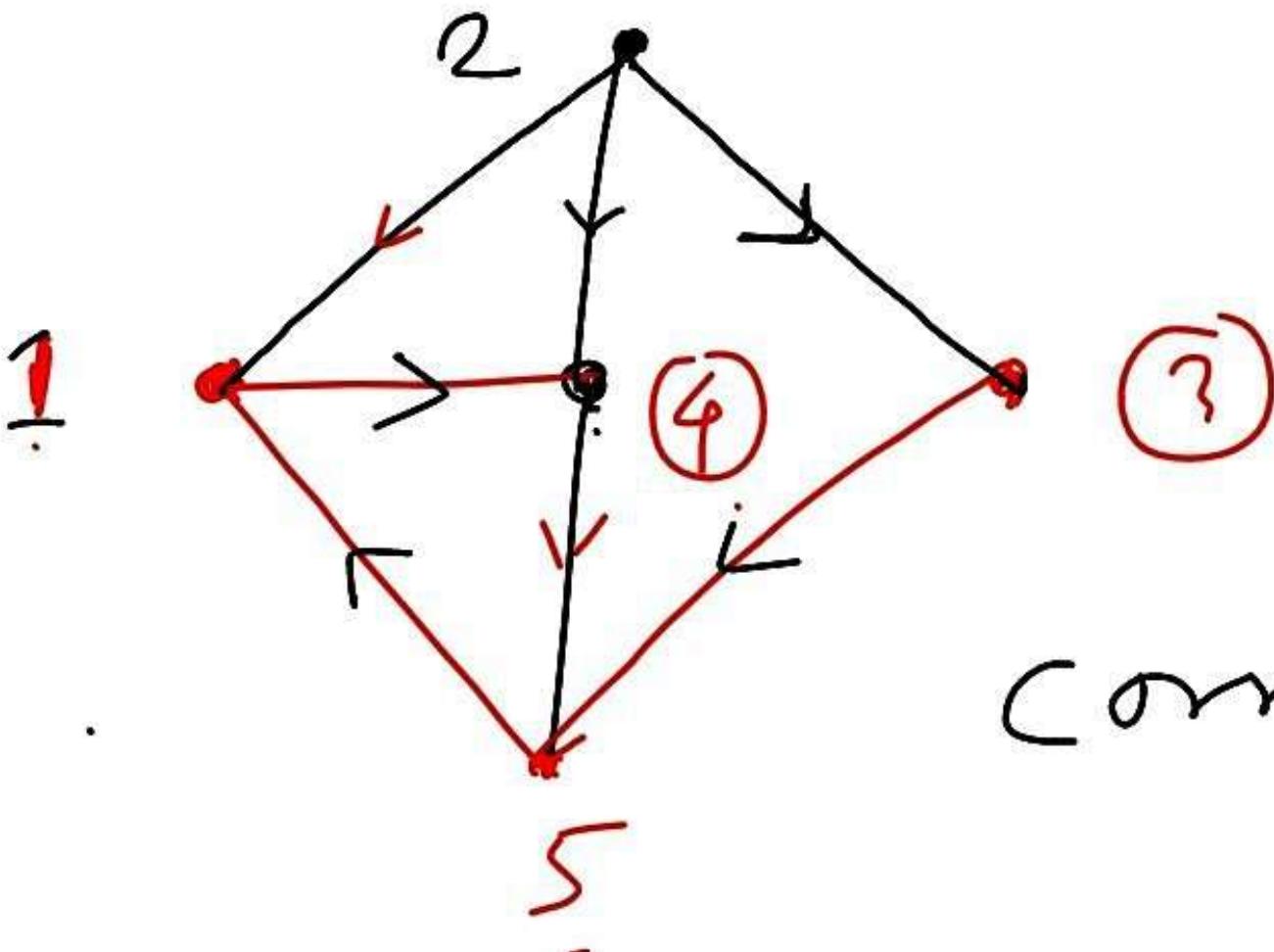
$$A = \begin{bmatrix} -1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & -1 & 0 \\ 1 & -1 & -1 & 0 & 0 & 0 & 0 \end{bmatrix},$$



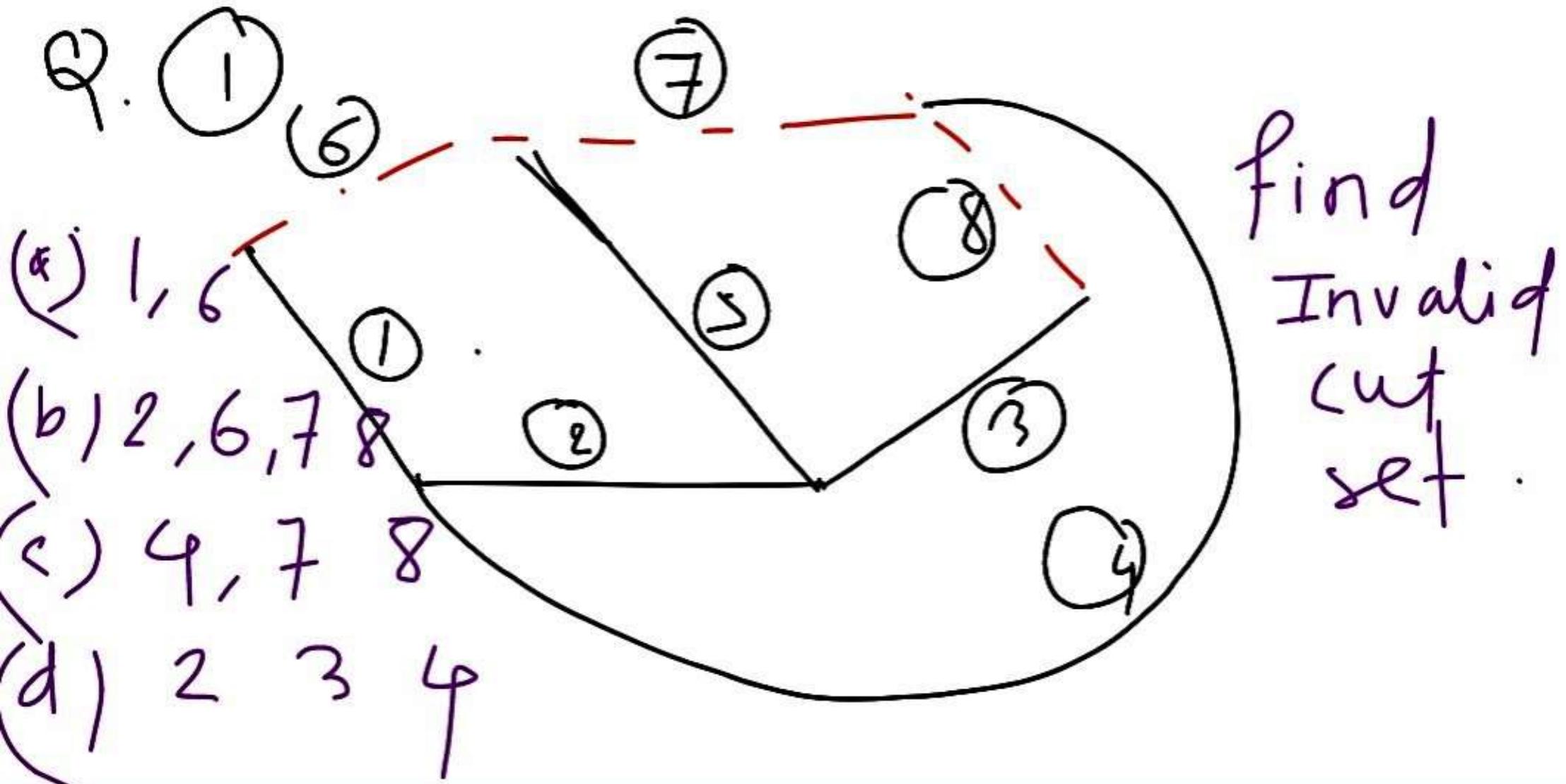

- (a) 6
- (b) 5
- (c) 4
- (d) 3

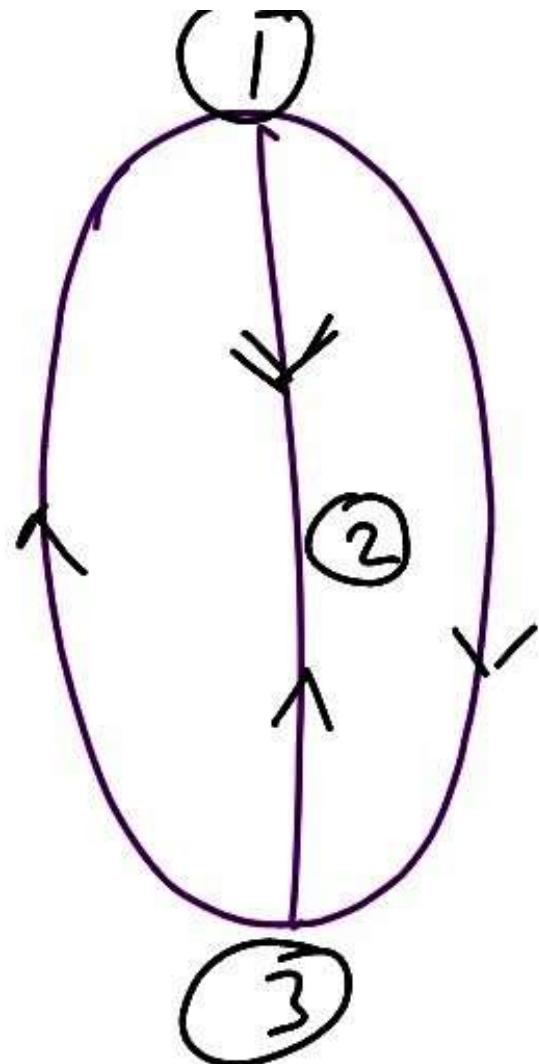

for the graph shown. find the no of possible tree.

Q. ③) A network graph
consist of 17 branches &
10 nodes. Determine the no.
of eqn required to solve
the corresponding Network

Gauss elimination Method

Consider A system . egn.

$$I_1 - 2 I_2 = 1$$

$$3 I_1 + 2 I_2 = 11$$

1st step \Rightarrow Write eqn in matrix form.

$$\begin{bmatrix} 1 & -2 \\ \underline{\underline{3}} & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$AX = B \quad 4 \times 4$$

$$C = A : B \quad R_2 \xrightarrow{R_2 - 3R_1}$$

$$\begin{array}{c} R_1 \\ R_2 \end{array} \left[\begin{array}{cc|c} 1 & -2 & 1 \\ 3 & 2 & \end{array} \right] \xrightarrow{\text{---}} \Rightarrow \begin{bmatrix} x & y \\ 0 & z \end{bmatrix}$$

→ convert this into upper triangular matrix.

Elementary row transformation
for upper triangular matrix.

$$R_2 \longrightarrow R_2 - 3R_1$$

$$\left[\begin{array}{ccc|c} 1 & -2 & | & 1 \\ 0 & 8 & | & 8 \\ \hline & & | & \end{array} \right]$$

$$I_1 - 2I_2 = 1$$

$$8I_2 = 8$$

$$\boxed{I_2 = 1}$$

& $I_1 - 2(1) = 1 \Rightarrow \boxed{I_1 = 3}$

$$x - 2y + 3z = 9$$

$$-x + 3y = -4$$

$$2x - 5y + 5z = 17$$

$$C = A : B.$$

$$\begin{array}{l} R_1 \\ \hline R_2 \\ \hline R_3 \end{array} \left[\begin{array}{ccc|c} 1 & -2 & 3 & 9 \\ -1 & 3 & 0 & -4 \\ 2 & -5 & 5 & 17 \end{array} \right] \quad A \quad \dots$$

$$\left[\begin{array}{ccc|c} 1 & -2 & 3 & 9 \\ 1 & 3 & 0 & -4 \\ 2 & -5 & 5 & 17 \end{array} \right]$$

$$R_2 \rightarrow R_2 + R_1$$

$$\left[\begin{array}{ccc|c} 1 & -2 & 3 & 9 \\ 0 & 1 & 3 & 5 \\ 2 & -5 & 5 & 17 \end{array} \right] \xrightarrow{R_3 - 2R_1} \Rightarrow$$

$$R_3 \rightarrow R_3 - 2R_1$$

$$\left[\begin{array}{ccc|c} 1 & -2 & 3 & 9 \\ 0 & 1 & 3 & 5 \\ 0 & -1 & -1 & -1 \end{array} \right]$$

$$\underline{R_3 \rightarrow R_3 + R_2}$$

$$\left[\begin{array}{ccc|c} 1 & -2 & 3 & 9 \\ 0 & 1 & 3 & 5 \\ 0 & 0 & 2 & 4 \end{array} \right]$$

$$x - 2y + 3z = 9$$

$$y + 3z = 5 \Rightarrow$$

$$2z = 4$$

$$\boxed{z = 2}$$


$$y + 3(2) = 5$$

$$\boxed{y = -1}$$

$$x - 2(-1) + 3 \times 2$$

$$= 9$$

$$= \boxed{x = 1}$$

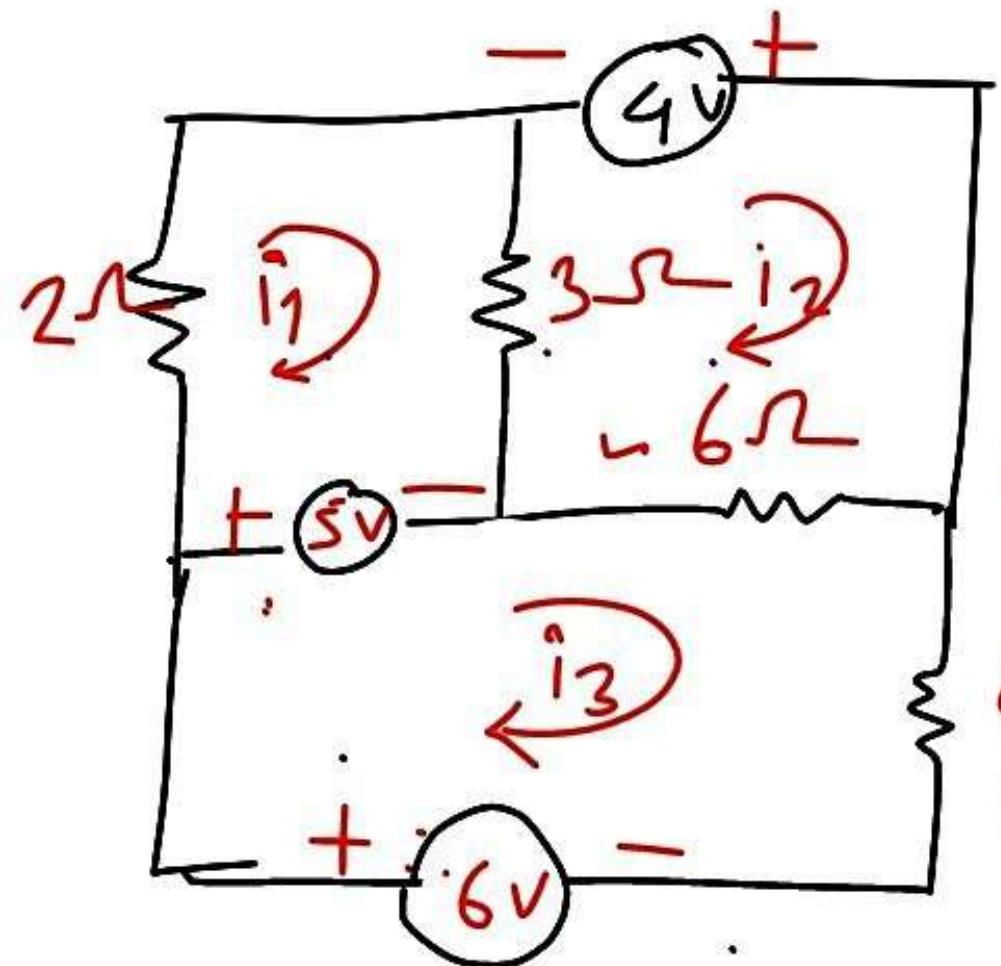

$$\begin{aligned}
 & \text{Loop 1:} \\
 & 2i_1 + 3(i_1 - i_2) = 5 \\
 & \Rightarrow 2i_1 + 3i_1 - 3i_2 = 5 \\
 & 5i_1 - 3i_2 = 5 \\
 & \text{Loop 3:} \\
 & 4i_2 = 5i_1 - 3i_2 = 5 \\
 & \text{---} \quad \textcircled{1}
 \end{aligned}$$

Loop. ②

$$6(\dot{i}_2 - \dot{i}_3) + 3(\dot{i}_2 - \dot{i}_1) = 4$$

$$6\dot{i}_2 - 6\dot{i}_3 + 3\dot{i}_2 - 3\dot{i}_1 = 4$$

$$-3\dot{i}_1 + 9\dot{i}_2 - 6\dot{i}_3 = 4 \quad \text{---} \textcircled{2}$$

Loop ③


$$\Rightarrow 6(i_3 - i_2) + 4i_3 = 6 - 5$$

$$6i_3 - 6i_2 + 4i_3 = 1$$

$$= -6i_2 + 10i_3 = 1 \quad \text{--- } ③$$

$$\left[\begin{array}{ccc} 5 & -3 & 0 \\ -3 & 9 & -6 \\ 0 & -6 & 10 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \end{array} \right] = \left[\begin{array}{c} 5 \\ 4 \\ 1 \end{array} \right]$$

$$\left[\begin{array}{ccc|c} 5 & -3 & 0 & 5 \\ -3 & 9 & -6 & 4 \\ 0 & -6 & 10 & 1 \end{array} \right]$$

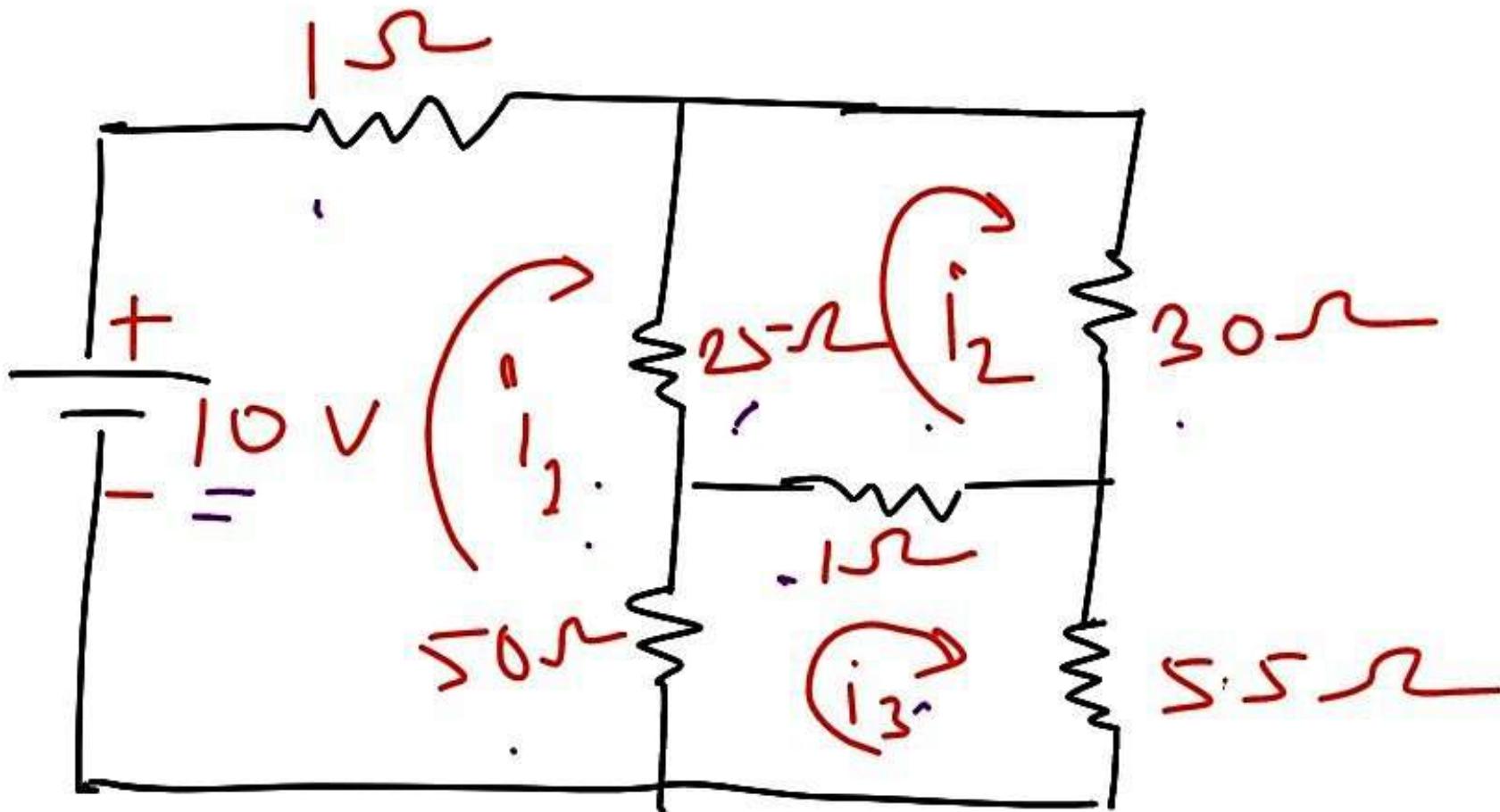

Imp P. ①

$$10\dot{i}_1 + 25(i_1 - \dot{i}_2) + 50(i_1 - \dot{i}_3) = 10$$

$$\dot{i}_1 + 25i_1 - 25\dot{i}_2 + 50i_1 - 50\dot{i}_3 = 10$$

$$\Rightarrow 76\dot{i}_1 - 25\dot{i}_2 - 50\dot{i}_3 = 10$$

— ①

Loop ②

$$\rightarrow 25(i_2 - i_1) + 30i_2 + i_1(i_2 - i_3) = 0$$

$$\rightarrow 25i_2 - 25i_1 + 30i_2 + i_2 - i_3 = 0$$

$$\rightarrow -25i_1 + 56i_2 - 1i_3 = 0$$

— ②

Loop ③

$$50(i_3 - i_1) + 1(i_3 - i_2) + 55i_3 = 0$$

$$\rightarrow 50i_3 - 50i_1 + i_3 - i_2 + 55i_3 = 0$$

$$\rightarrow -50i_1 - i_2 + 106i_3 = 0$$

— ③

$$\left[\begin{array}{ccc|c} 76 & -25 & -50 & \\ -25 & 56 & -1 & \\ -50 & -1 & 106 & \end{array} \right] = \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \end{array} \right] = \left[\begin{array}{c} 10 \\ 0 \\ 0 \end{array} \right]$$

$$\left[\begin{array}{ccc|c} 76 & -25 & -50 & 10 \\ -25 & 56 & -1 & 0 \\ -50 & -1 & 106 & 0 \end{array} \right]$$


$$Q_1 \text{ Ans} \Rightarrow i_1 = 3\frac{4}{15}, \quad i_2 = 1\frac{9}{9}$$
$$i_3 = 4\frac{1}{30}$$

$$Q_2. \text{ Ans} \Rightarrow i_1 = 0.245$$
$$i_2 = 0.111$$
$$i_3 = 0.117$$

Time & frequency response of circuits

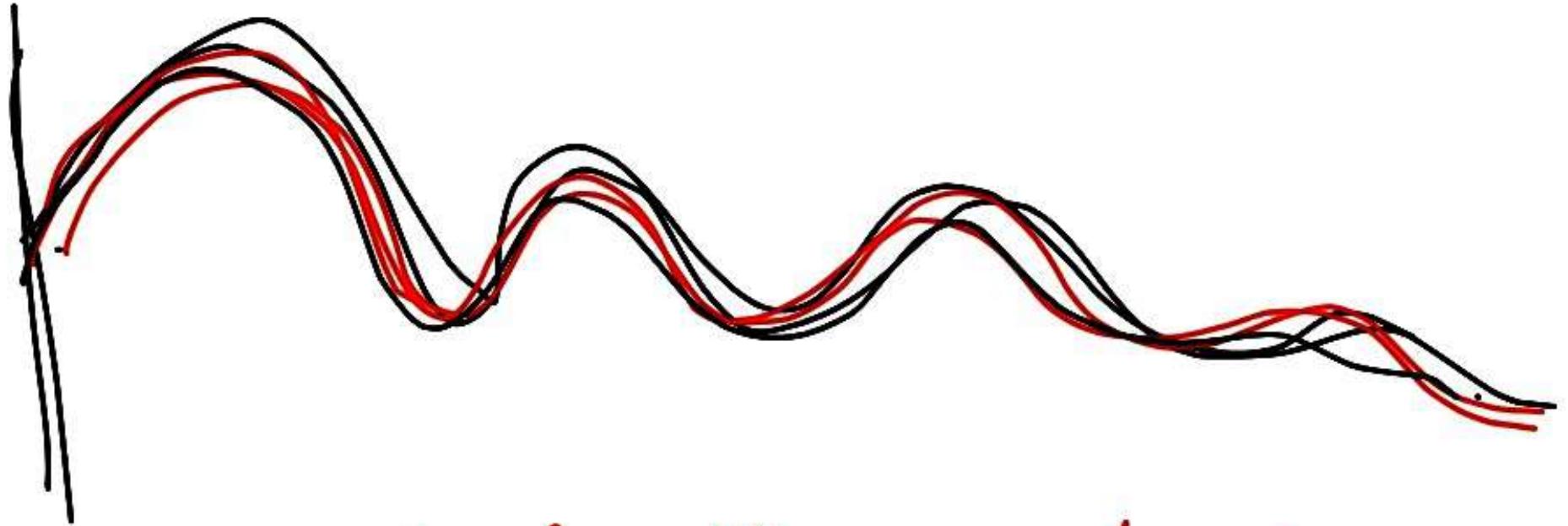- 1) first & second order differential eqn
- 2) Transient & steady state response


- ③ Transfer function.
- ④ Concept of poles & zeros.
- ⑤ Frequency response.



Transient in the system
because of presence of $L - C$

Energy stored in memory element
cannot change instantaneously.
ie within zero time.
due to the integration of
energy variables i_L & V_C

LSC will oppose sudden
changes.

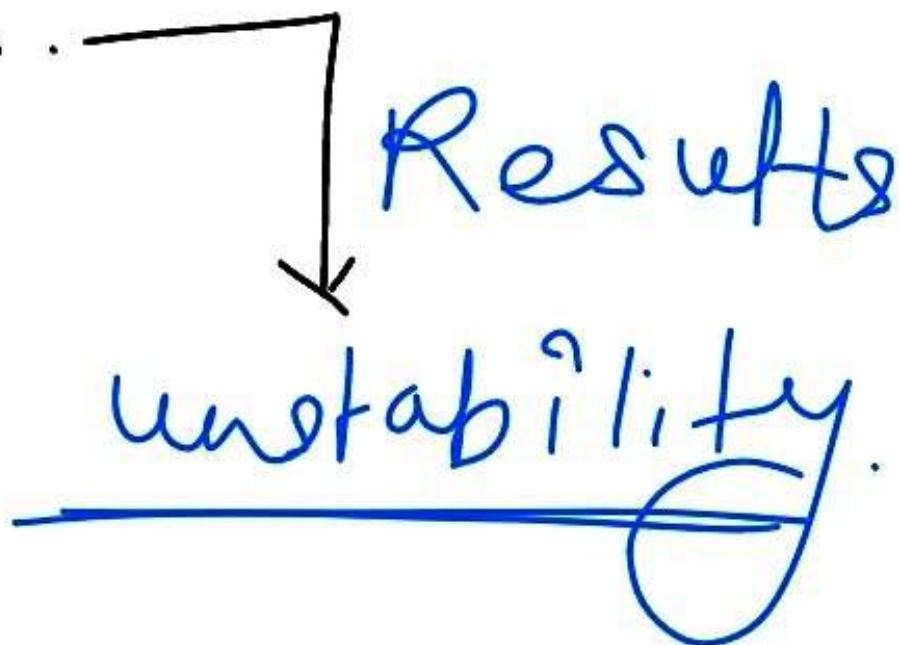

When the network
consist of only resistance
(memory less element) no
transient occurs in system.

$$V = iR \quad \& \quad i = \frac{V}{R}$$

Transient effects are more severe for DC as compared to AC. The transient free condition is possible to only for AC excitations. (At zero crossing of $\sin \omega t$)

Laplace transform :-

$$R \xrightarrow{LT} R_S$$

$$L \xrightarrow{LT} sL - i$$

$$C \xrightarrow{LT} \frac{1}{sC} -$$

$$V(t) \xrightarrow{LT} V(s)$$

$$\underline{i(t)} \xrightarrow{LT} I(s)$$

$$\underline{\dot{s}(t)} \xrightarrow{LT} 1$$

$$\underline{u(t)} \xrightarrow{LT} 1/s$$

$$K\underline{u(t)} \xrightarrow{LT} K/s$$

$$R(t) \xrightarrow{LT} \frac{1}{s+2}$$

$$P(t) \xrightarrow{LT} \frac{1}{s+3}$$

$$= e^{-at} u(t) \xrightarrow{LT} \frac{1}{s+a}$$

$$\downarrow$$
$$e^{-3t} u(t) \xrightarrow{LT} \frac{1}{s+3} \leftarrow \text{Ans}$$

$$\frac{V(s)}{I(s)} = Z(s) \text{ - } \Omega$$

$$V(s) = Z(s) \cdot I(s)$$

$$I(s) = \frac{V(s)}{Z(s)}$$

$$\frac{I(s)}{V(s)} = Y(s) \text{ - } \text{mho}$$

$$V(s) = \frac{I(s)}{Y(s)}$$

$$I(s) = Y(s) \cdot V(s)$$

$\zeta(s)$

$R \approx \infty$

$s_L \approx$

$\frac{1}{s_C} \approx$

$\gamma(s)$

$\frac{1}{R} \approx$


$\frac{1}{s_L} \approx$

$s_C \approx$

Note :-

Impedance ($Z(s)$) will be
in series.

Admittance in parallel.
we can add.

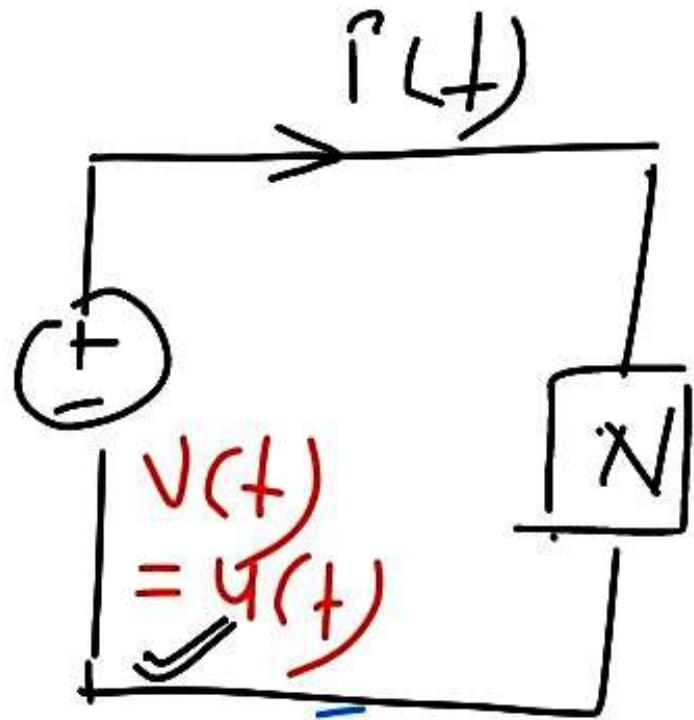

Network N contains
only two elements
& response to the

$i(t) = e^{-3t}$ unit step excitation
elements $u(t)$ Determine the
elements & their connect

System
Transfer

function =

Response LT

Excitation LT

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \frac{1}{Z(s)}$$

Admittance (mho)


$$\frac{I(s)}{V(s)} = \frac{\frac{1}{s+3}}{\frac{1}{s}} = \frac{s}{s+3} \Rightarrow Y(s)$$

$$I(t) = e^{-3t} u(t) \xrightarrow{LT} I(s) = \frac{1}{s+3}$$


$$\underline{V(t)} = \underline{u(t)} \xrightarrow{LT} V(s) = \frac{1}{s}$$

$$\frac{Z(s)}{Y(s)} = \frac{1}{s+3}$$
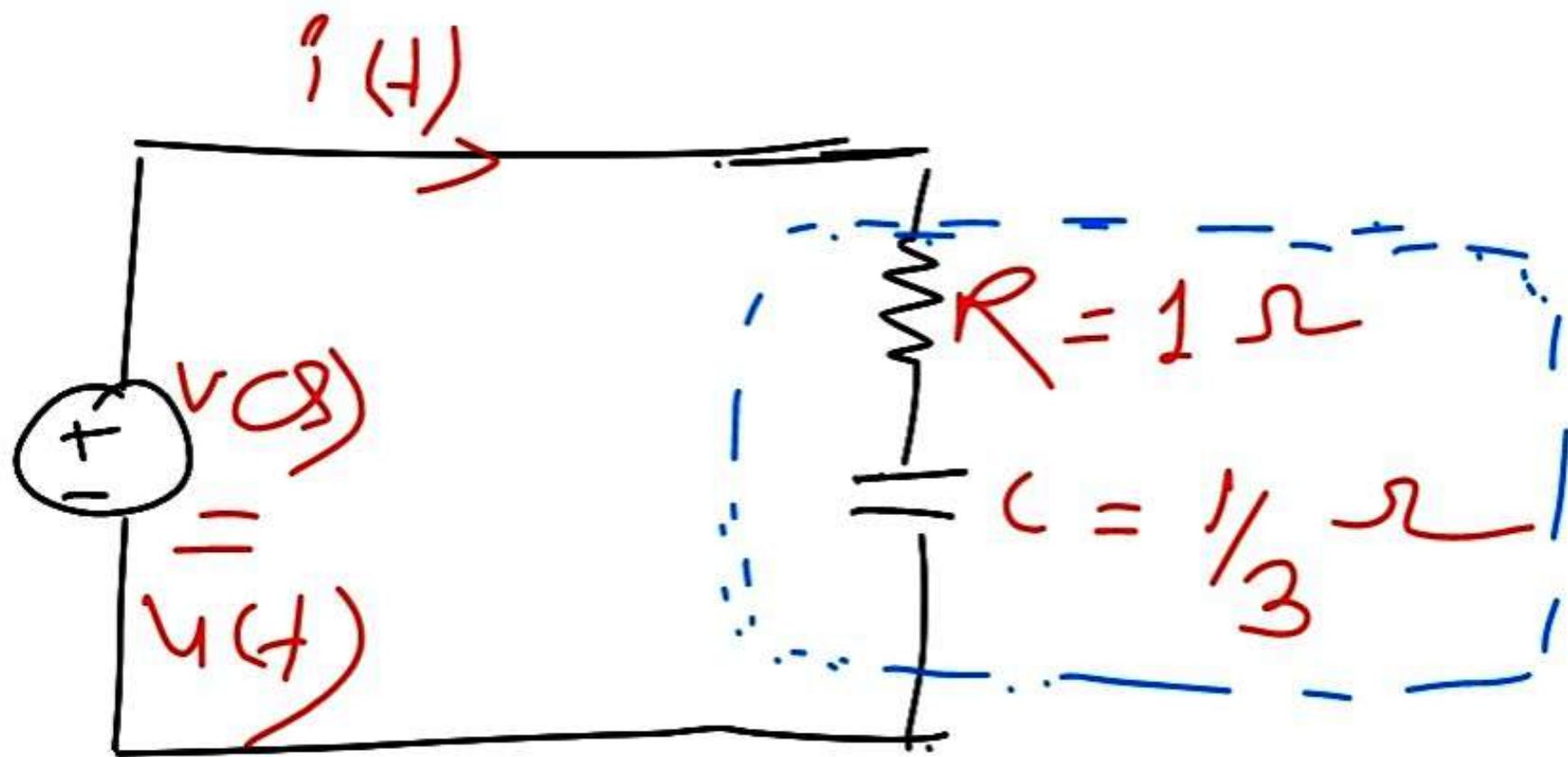
$$\begin{aligned} &= \frac{1 + \frac{3}{s}}{s + \frac{1}{3}} \\ &= R + \frac{1}{sC} \end{aligned}$$



$$i(t) = e^{-t} - e^{-(-t-z)}$$

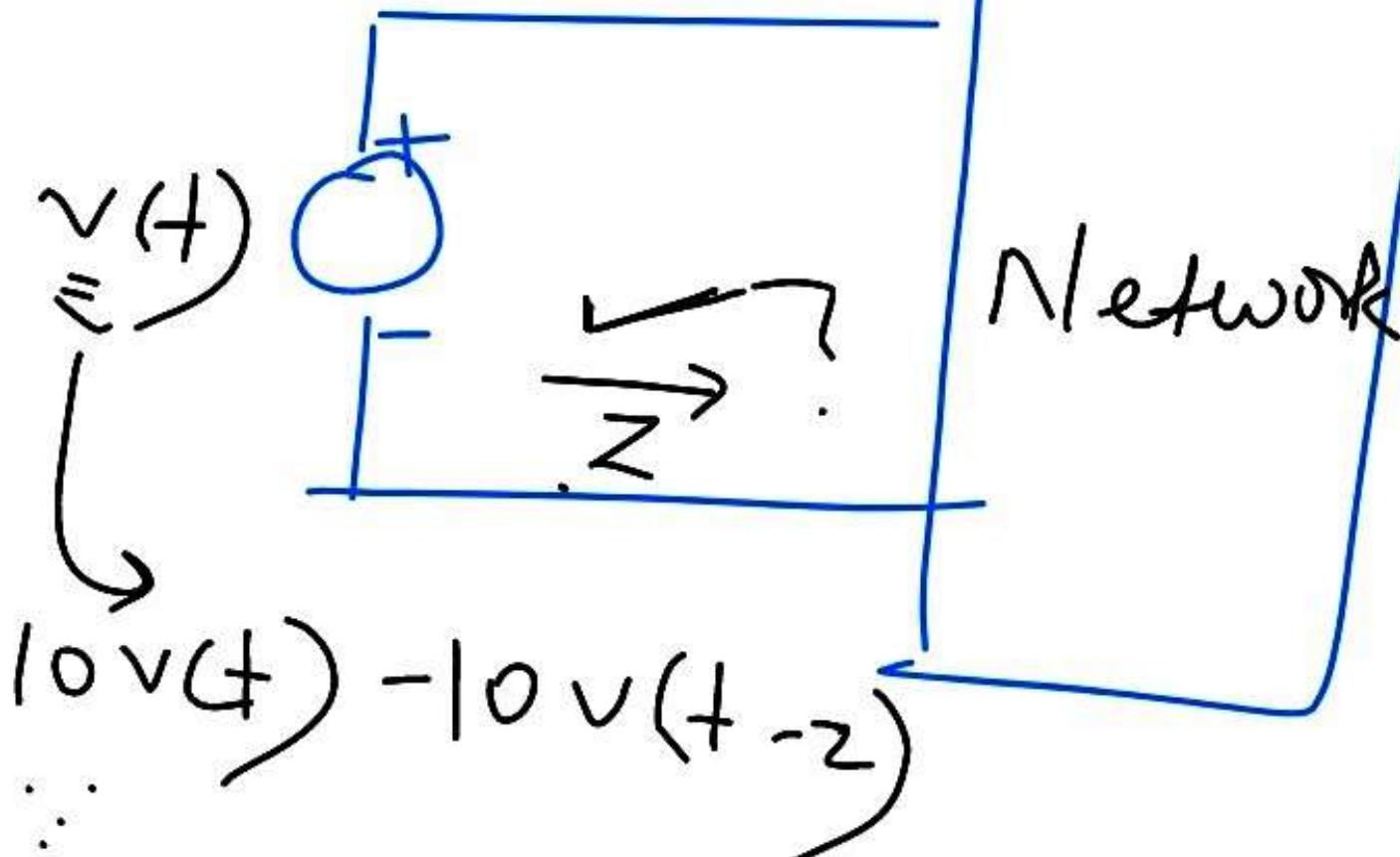

find out
the Z of
N/w. using
LT.

$$v(t) = 10v_<(t) - 10v_{(t-2)}$$

1st step

evaluate the LT of

$$v(t)$$

$$v(t) = 10U(t) - 10U(t-2)$$

$$v(s) = \frac{10}{s} - \frac{10}{s}e^{-2s}$$

$$= \frac{10}{s} (1 - e^{-2s})$$

Current $i(t) = e^{-t} - e^{-(t-2)}$

$$i(0) = \frac{1}{s+1} - \frac{1}{s+1} \cdot e^{-2s} = \frac{1 - e^{-2s}}{s+1}$$

$$Z(s) = \frac{V(s)}{I(s)}$$

$$= \frac{10}{s} (1 - e^{-2s})$$
$$\frac{1 - e^{-2s}}{s+1} \Rightarrow \frac{\frac{10}{s} (1 - e^{-2s})}{s+1}$$

*



$$\begin{aligned}
 &= \frac{10/s}{1/s+1} = 10 \cdot \frac{s+1}{s} \\
 &= 10(1 + \frac{1/s}{s}) \\
 &\stackrel{*}{=} 10 + \frac{1}{\frac{10}{s}}
 \end{aligned}$$

We know that Laplace transform
of R i.e. value is unchanged.
S LT of capacitor $\frac{1}{sC}$

$$Z(s) = R + \frac{1}{sC} \Rightarrow \begin{array}{l} R = 10\Omega \\ C = 1/10 \end{array}$$


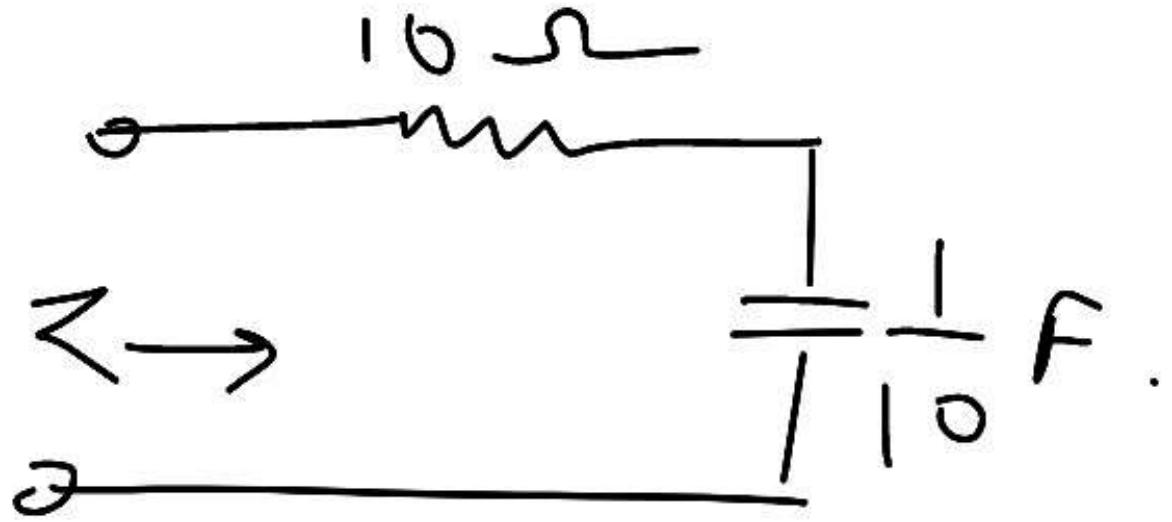



fig: - Impedance of the Y_ω

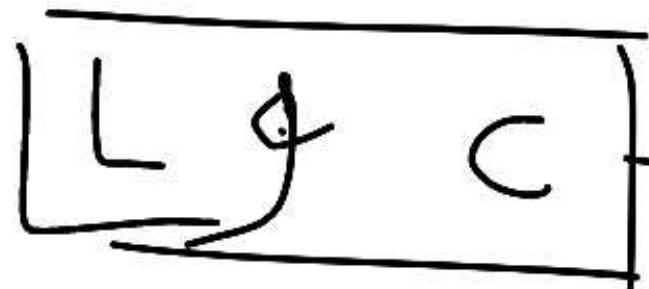


\rightarrow Memory element.

$\equiv R \rightarrow$ Memoryless element.

$$V = R_i^o \quad i = V_o / R$$

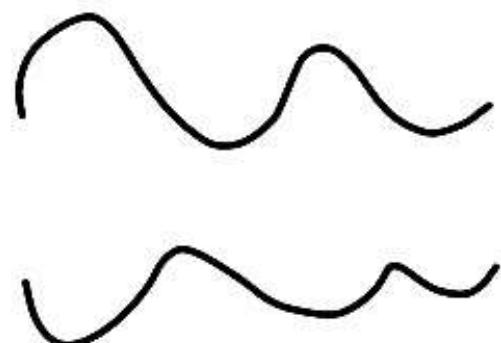

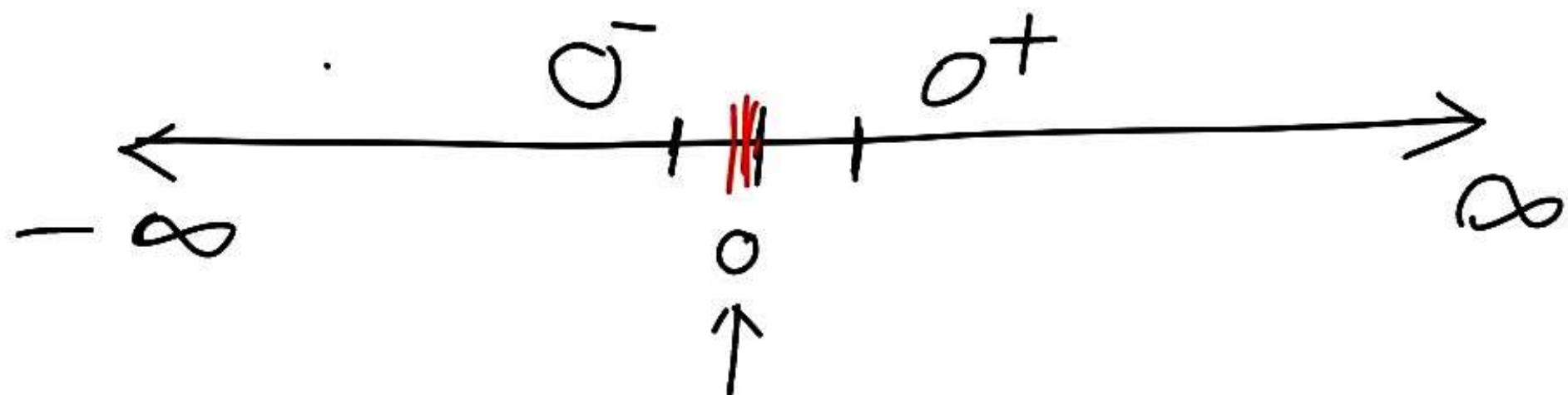Behaviour of L & C elements
at $t = 0$ and at $t = \infty$




$$\cancel{t=0^+} \Rightarrow \cancel{s=\infty} \Rightarrow z_L = \infty \checkmark$$

$$z_C = 0 \Rightarrow c = s.c$$

~~$$z_L = sL$$~~

~~$$z_C = \frac{1}{sc}$$~~
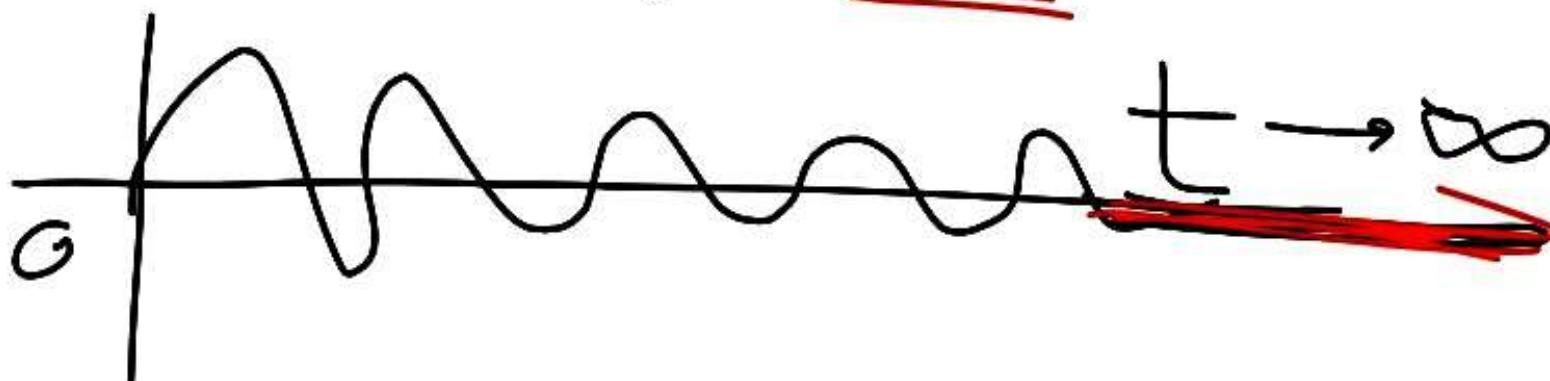
$$\begin{aligned} \underline{\underline{t \rightarrow \infty}} \Rightarrow \zeta = 0 &\Rightarrow \\ \underline{\underline{\zeta_L \rightarrow 0}} \Rightarrow L \rightarrow \underline{\underline{SC}} & \\ \underline{\underline{\zeta_C \rightarrow \infty}} \Rightarrow C \rightarrow \underline{\underline{OC}} & \\ \text{Graph: } & \end{aligned}$$


In long time after the switching action ($t \rightarrow \infty$) is steady state

In steady state \rightarrow Inductor (L)

$\Rightarrow SC$

Capacitor (C)
 $\Rightarrow OC$.

DC source is connected to N/w for long time. The n/w. is said to be in Steady state when the energy stored in N/w is max.

↳ constant. So, the energy stored in memory element will be max

↳ constant.

$$i_L' = \frac{1}{2} L i_L^2 = \text{Max \& constant}$$

$i_L \Rightarrow \text{Max \& constant}$

Inductor will behave
as current source in
steady state

$$V_L = L \frac{di_L}{dt} \Rightarrow V_L \geq 0 \quad L = \infty .$$

$$\frac{1}{2} C V_C^2 \Rightarrow \text{Max } & \text{constant}$$

$$V_C \Rightarrow \text{Max } & \text{constant}$$

Capacitor will act as constant voltage source in steady state.


Note :- Discussion is valid only
for DC excitations / source
→


AC excitations

L & C are changing



store
emerging

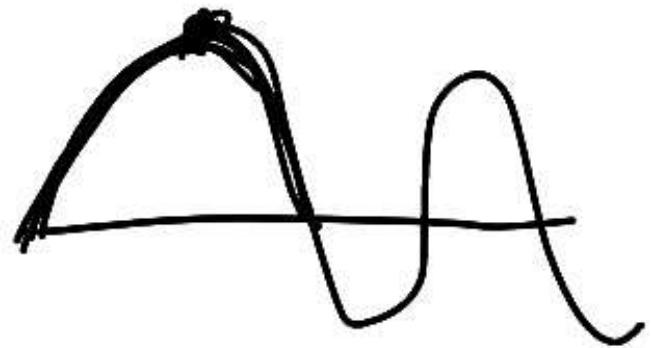

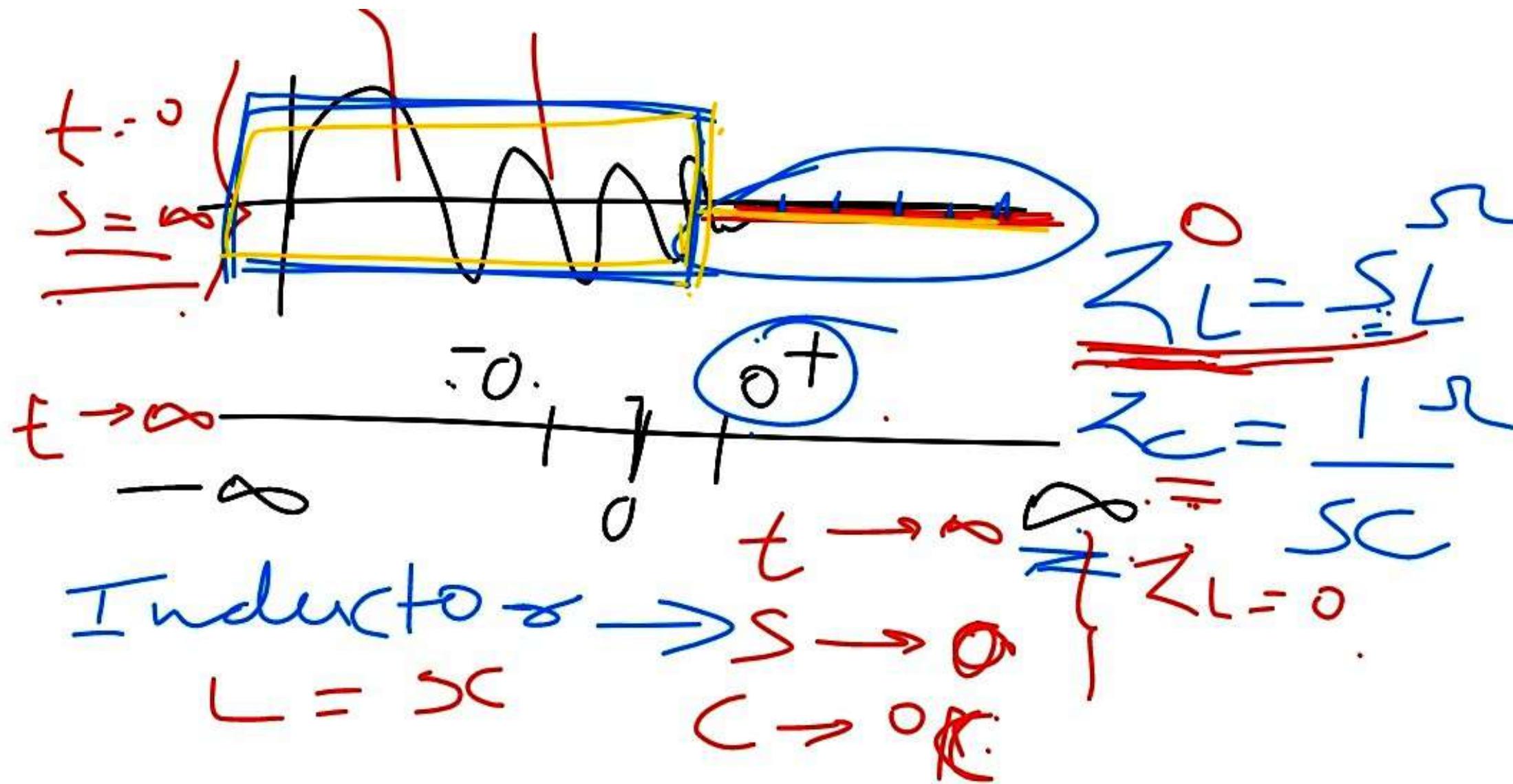

AC excitations

- ① for AC, during positive half of time period both L & C are changing state.

② During the negative slope of time period they (L, C) are discharging
(Delivering the energy)

Blind Approach ($s=j\omega$)

In steady state

$$\underline{Z}_L = j\omega L \quad \& \quad \underline{Z}_C = \frac{1}{j\omega C}$$

$\underline{Z}_L = sL$

Blind Approach ($s=j\omega$)

In steady state

$$Z_L = j\omega L \quad \& \quad Z_C = \frac{1}{j\omega C}$$

\therefore

$$Z_L = sL$$

for $\underline{\underline{A}}^C$ $\omega \neq 0$
 $\zeta_L \neq 0$

$$\zeta_L = j\omega L \text{ or}$$

$$\zeta_C = \frac{j}{j\omega_C} \quad (\zeta_C \neq \infty)$$

The impedances are finite
and hence L & C elements
are always present for

AC excitation.

$$Z_L = j\omega L \quad Z_L \neq 0$$

$$Z_C = \frac{1}{j\omega C} \quad Z_C \neq \infty$$

For DC

only in steady state $\omega = 0$


$$Z_L = j\omega L = 0 \quad L = SC$$

$$Z_C = \frac{1}{j\omega_C} = \infty \quad C \rightarrow OC$$

No inductor, capacitor operations
in steady state. for DC excitations.
i.e. $\underline{L \& C}$ elements will die
for dc excitations.

($\underline{L \& C}$ elements will experience
a deep sleep)

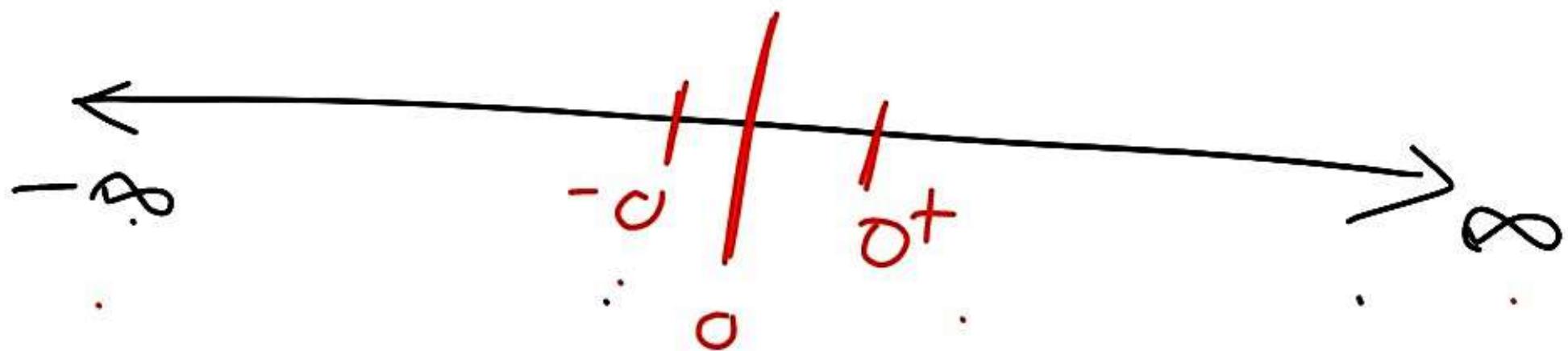Inductor current at $t = 0^-$ and
at $t = 0^+$ instants



$$\begin{aligned}
 L \Rightarrow i_L(t) &= \frac{1}{L} \int_0^t v_L(t) dt \\
 &= \frac{1}{L} \int_{-\infty}^{0^-} v_L(t) dt \xrightarrow{-\Delta} + \frac{1}{L} \int_0^t v_L(t) dt \\
 &= i_L(0^-) + \frac{1}{L} \int_{-\sigma}^{t^+} v_L(t) dt
 \end{aligned}$$

$$\text{At } t=0^+ \Rightarrow i_L(0^+)$$
$$= i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v_L$$

$$t = 0^- \quad L \Rightarrow i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t') dt$$


$$\Rightarrow \frac{1}{L} \int_{-\infty}^{0^-} v_L(t) dt + \frac{1}{L} \int_{0^-}^t v_L(t') dt$$

$$\Rightarrow i_L(0^-) + \frac{1}{L} \int_{0^-}^t v_L(t') dt$$

At $t = 0^+$

$$A \leftarrow 0^+$$
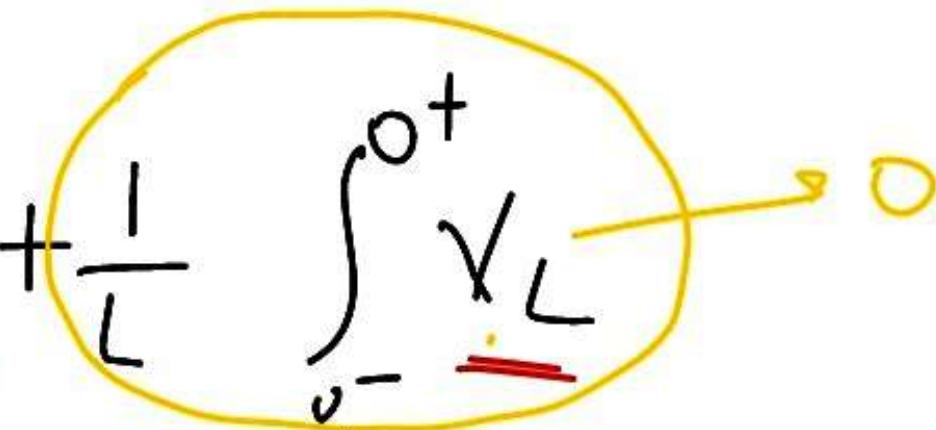
$$\underline{i_L(0^+)} = \underline{i_L(0^-)} + \frac{1}{L}$$



$$i_L(0^+) = i_L(0^-) \text{ Amp.}$$

$$E(0^+) = E(0^-) \rightarrow \text{Joule}$$


$$\frac{1}{\delta(+)} \boxed{N(+)} = \underline{\delta(+)} / \int \delta(+) = 1$$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{-\infty}^{0^-} \underline{\delta(+)} dt$$

$$i_L(0) = i_L(0^-) + \frac{1}{L}$$

$$E_L(0^+) > E_L(0^-)$$

amp ✓

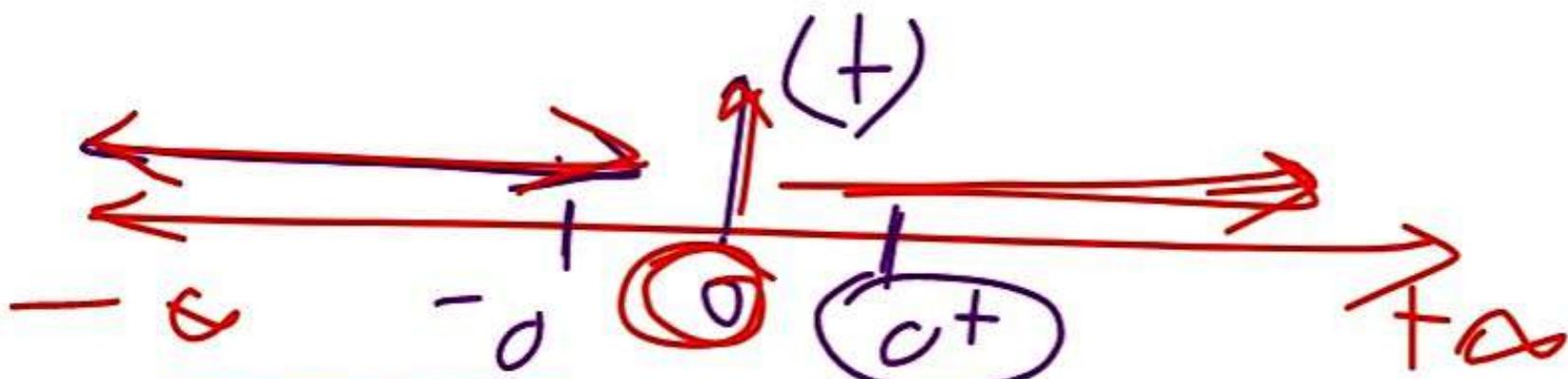


$$V_L(t) = \delta(t) = 0 \text{ for } -\alpha \leq t \leq \delta$$

~~$V_L(t) = \delta(t) = 0 \text{ for } -\alpha \leq t \leq \delta$~~

$$i_L(0^+) = \frac{-1}{t}$$
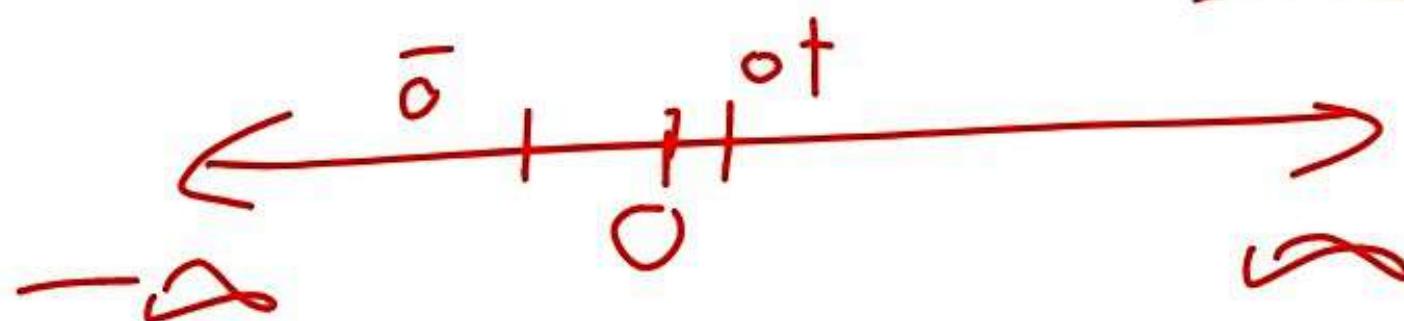
$$t=0 \Rightarrow L = \underline{\partial C} \quad C = \underline{S \cdot C}$$



$$t \rightarrow \infty \quad L = S \cdot C \quad C = O \cdot C$$

Blint Approach

In steady state $\Im_L = j\omega_0 \Omega$

$$\Im_C = \frac{1}{j\omega_0} \Omega$$

Blind Approach

In steady state $\Im_L = j\omega \parallel \Im_C$

$$\Im_C = \frac{1}{j\omega} \parallel$$

for AC $\omega \neq 0$

$$Z_L = j\omega L \neq 0$$

$$Z_C = \frac{1}{j\omega C} \neq \infty$$

L & C elements
always present
& they are busy.

DC \Rightarrow


$$\omega = \underline{\underline{0}}$$

$$Z_L = \underline{\underline{0}} \rightarrow L \Rightarrow SC$$

$$Z_C = \infty$$

$$C \rightarrow O.C$$

L & C elements will
dies for DC

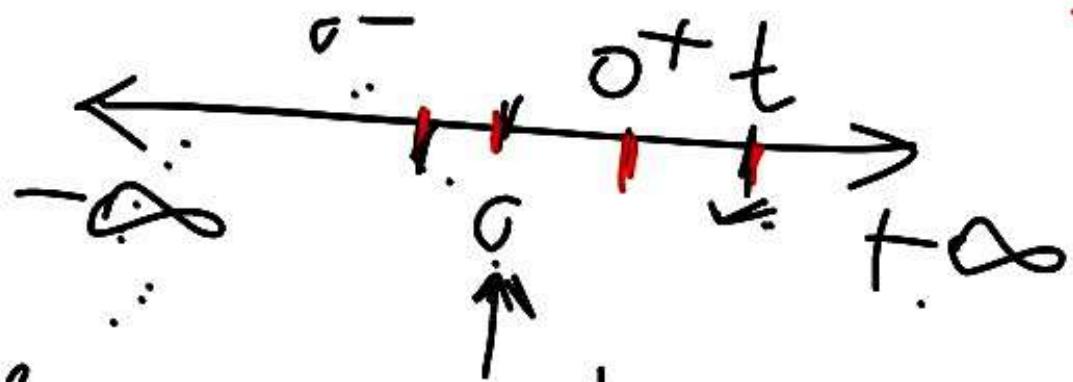

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$

$$= \frac{1}{L} \int_{-\infty}^{0^-} v_L(\tau) d\tau + \frac{1}{L} \int_{0^-}^t v_L(\tau) d\tau$$

at $t = 0^+$


The inductor
current &
capacitor voltage

$$i_L(0^-) + \frac{1}{L} \int_{0^-}^t v_L(t) dt \quad \underline{\text{obs}}$$

At $t = 0^+$ \Rightarrow

$i_L(0^+) = I_L(0^-)$ Amp. (Inductor current cannot change within 0 time)

$$E_L(0^+) = E_L(0^-) J$$

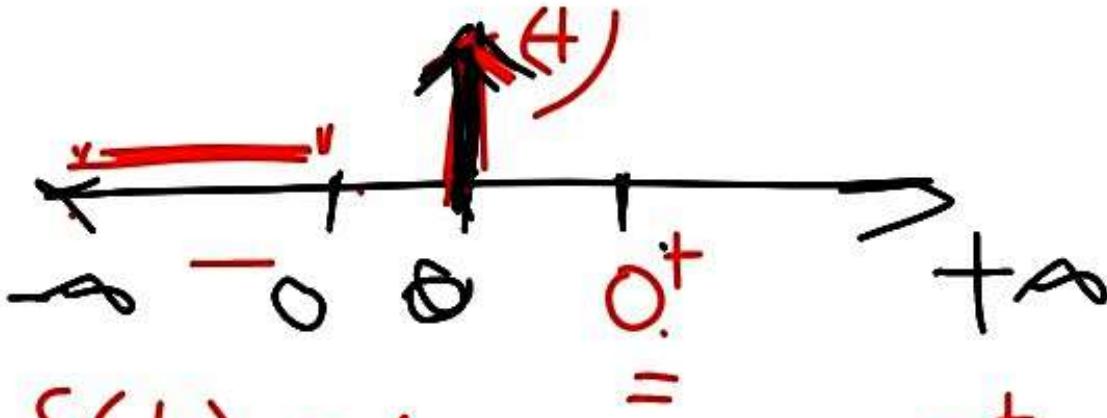


$$V_L(t) = \underline{\delta(t)} \quad -\infty \leq t < 0^+$$

$$\underline{\delta(t)} = 1$$

$$i_L(0^+) = \frac{1}{L} \int_{-\infty}^{0^+} V_L(t) dt$$

$$i_L(0^+) = \frac{1}{L}$$

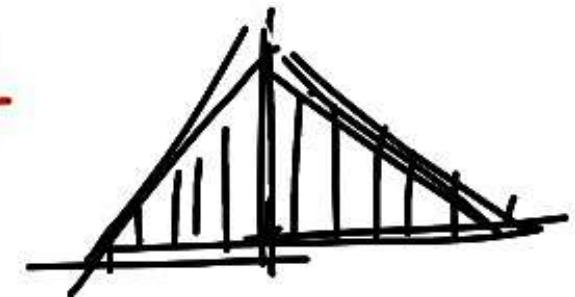

$$E_L(0^-) = 0 \text{ J} \cdot \text{v}$$

$$E_L(0^+) = \frac{1}{2} L \dot{i}^2 (0^+)$$


$$= \frac{1}{2} \times L \times \frac{1}{L^2}$$

$$\boxed{E_L(0^+) > E_L(0^-)}$$

$$E_L(0^+) = \frac{1}{2L}$$

$$\stackrel{!}{=} V_c(t) = \frac{1}{C} \int_{-\infty}^t i_c dt$$


At 0^-

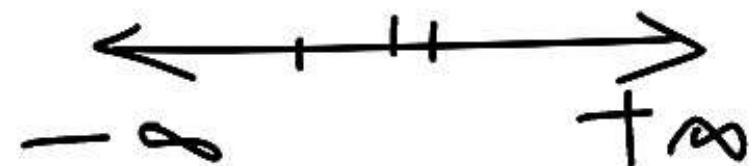

$$V_c(0^+) = V_c(0^-)$$

$$E_c(0^+) = E_c(0^-)$$

for Impulse

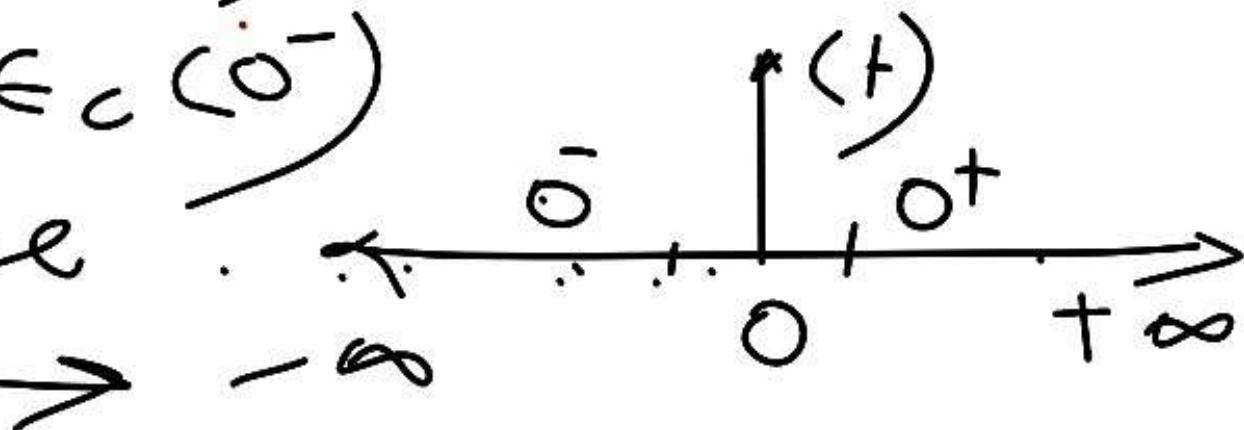

$$i_c = SC(+)$$

$$V_C(0^+) = \frac{1}{C} \times V$$


$$\overline{i_L} = \frac{1}{L}$$

$$E_C(0^+) = \frac{1}{2} C V^2 (0^+) \quad \frac{1}{2L}$$

$$= \frac{1}{2} \times C \times \frac{1}{L^2} \quad \frac{1}{2C}$$

$$E_C(0^+) = \frac{1}{2C}$$

Equivalent circuit

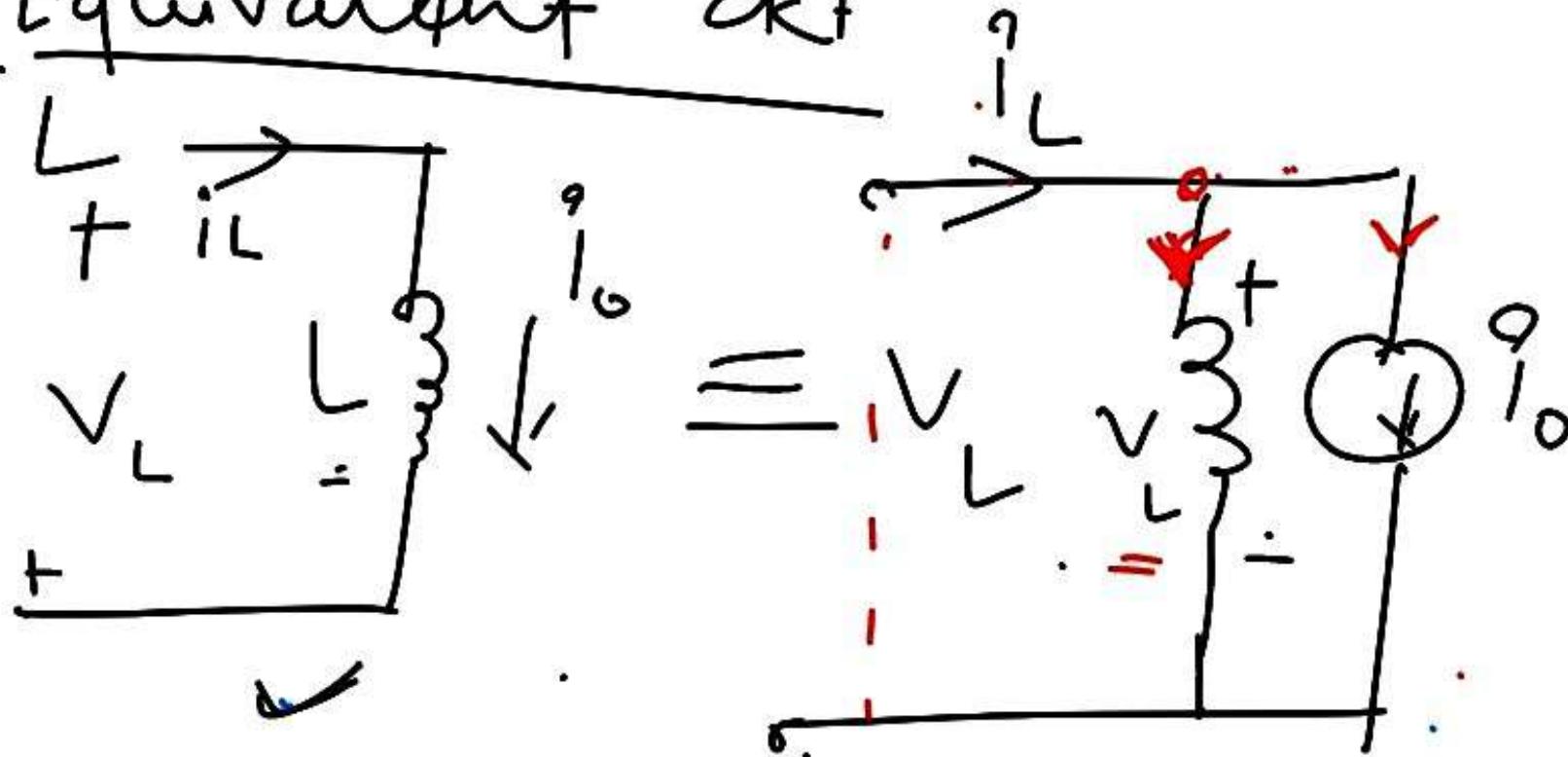

$$i_L = \frac{1}{L} \int_{-\infty}^t v_L(dt)$$

$$\boxed{i_L = i_L(0) + \frac{1}{L} \int v_L dt}$$

$$i_L(0) = i_0$$


Proof

By KCL :-

$$-i_L + I_L + i_o$$

$$= -i_L + \frac{1}{L} \int v_L(dt) + i_o = 0$$
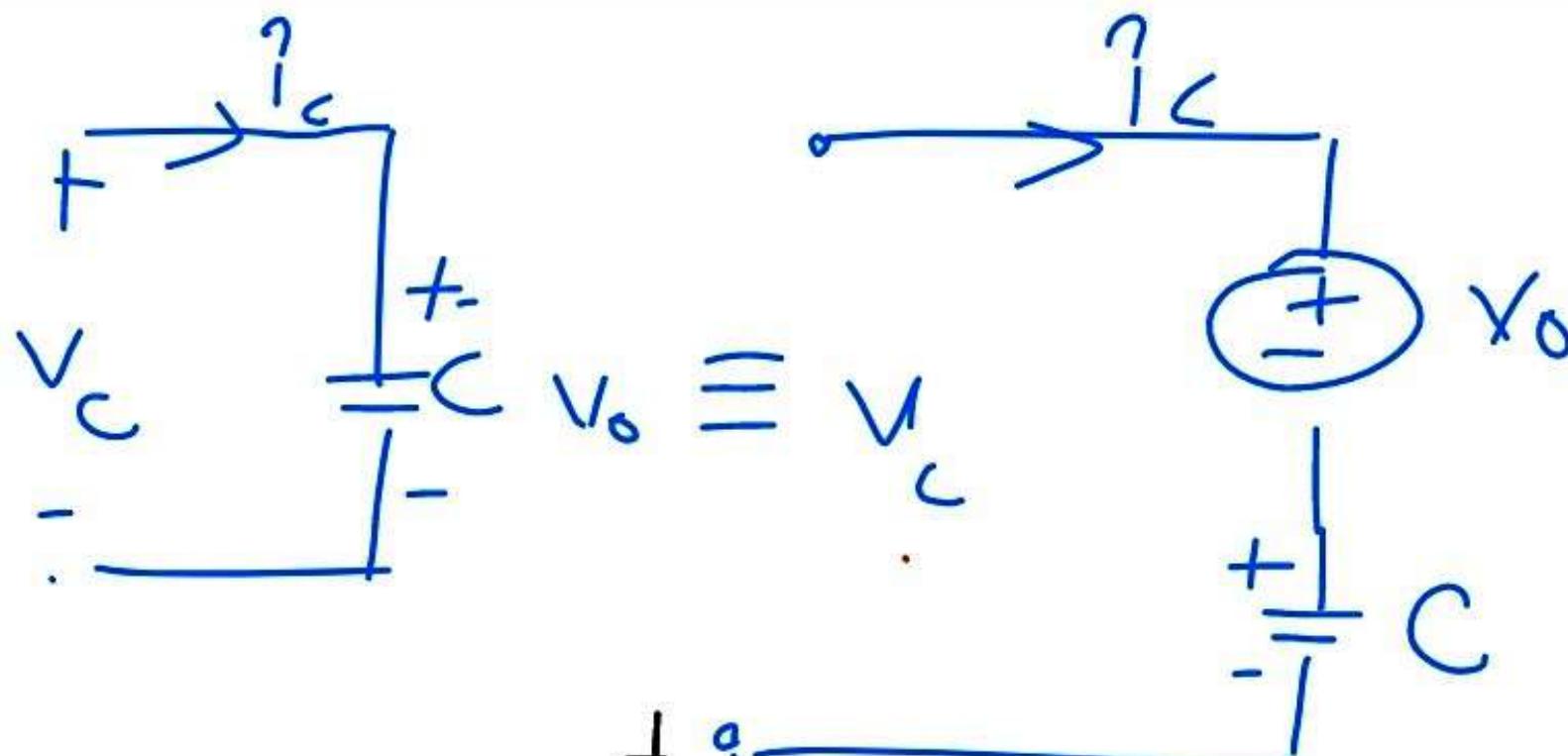
$$\Rightarrow i_L = \frac{1}{L} \int v_L(dt) + i_o \quad \checkmark$$



$$V_C = \frac{1}{C} \int_{-\infty}^t i_C dt \Rightarrow V_C(0) + \frac{1}{C} \int_0^t i_C dt$$

$$V_C = V_0 + \frac{1}{C} \int i_C dt =$$

Proof

By KVL :-

$$V_C - V_0 - \frac{1}{C} \int_{t_0}^t i_C dt = 0$$

$$V_C = V_0 + \frac{1}{C} \int_{t_0}^t i_C dt =$$


Classification of Transient

- 1) DC Transient ✓
- 2) AC Transient

① DC Transient

① Source free ckt ?

(Without independent sources)

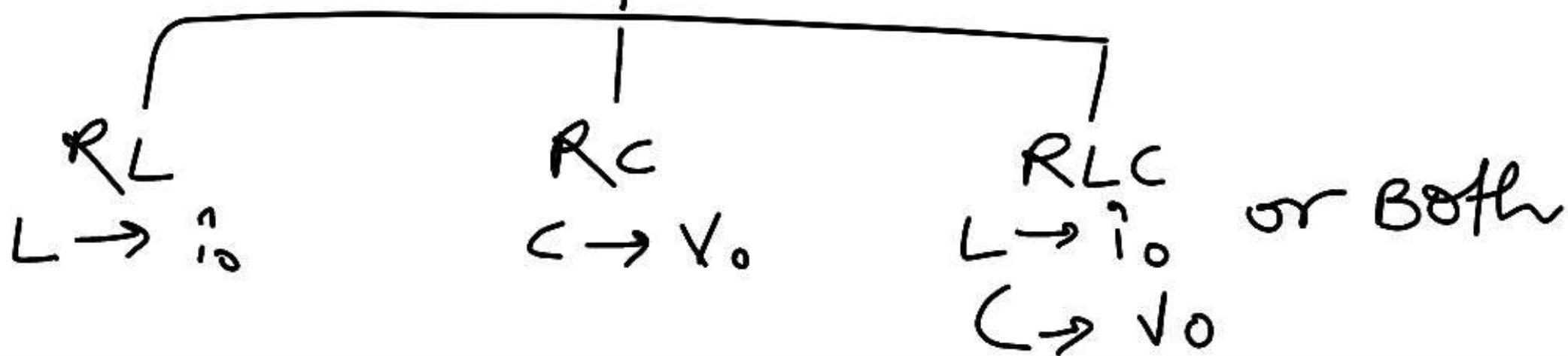

In all source free ckt, stored energies in the memory elements are maximum at $(t=0)$ (initially). These stored energies will be delivered to memoryless element in exponentially decayed manner. Hence the energy $\text{at } t \rightarrow \infty$ is zero.

Classification Transients

DC AC

Source free circuit: (Without independent source)


$R \rightarrow L \rightarrow i_o$ $RC \rightarrow C \rightarrow V_o$ $RLC \rightarrow$ Both.

Properties:-

$t = 0 \Rightarrow$ Energy max.

$t \rightarrow \infty$ \Rightarrow steady state \rightarrow Energy = 0
LC Transfer R

Source free RL circuit-

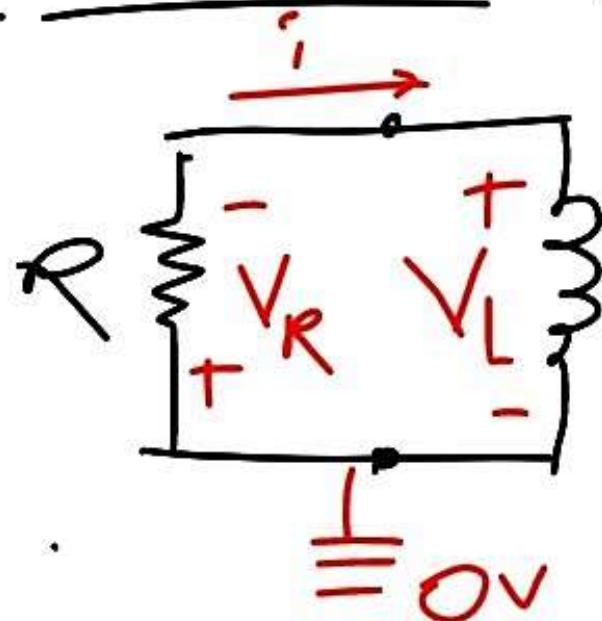

for $t \geq 0$
I₀ By KVL

$$v_R - v_L = 0$$

$$- Ri - L \frac{di}{dt} = 0$$

$$Ri + L \frac{di}{dt} = 0 \quad \xrightarrow{\text{Divide by } L}$$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

Let $D = \frac{d}{dt}$ $\Rightarrow \left(D + \frac{R}{L}\right) i = 0$

$$D + \frac{R}{L} \Rightarrow \text{characteristic eqn.}$$

$$D = -\frac{R}{L}$$

Here $s \in D = \frac{d}{dt}$


It is like $s = \alpha$


$$\alpha = -\frac{R}{L}$$

$i(t) = K e^{\alpha t}$, for $0 \leq t \leq \infty$

$$i(t) = K e^{-R/L t} \text{ for } 0 \leq t < \infty$$

$$i(t) = K e^{-R/L t} \text{ Amp.}$$

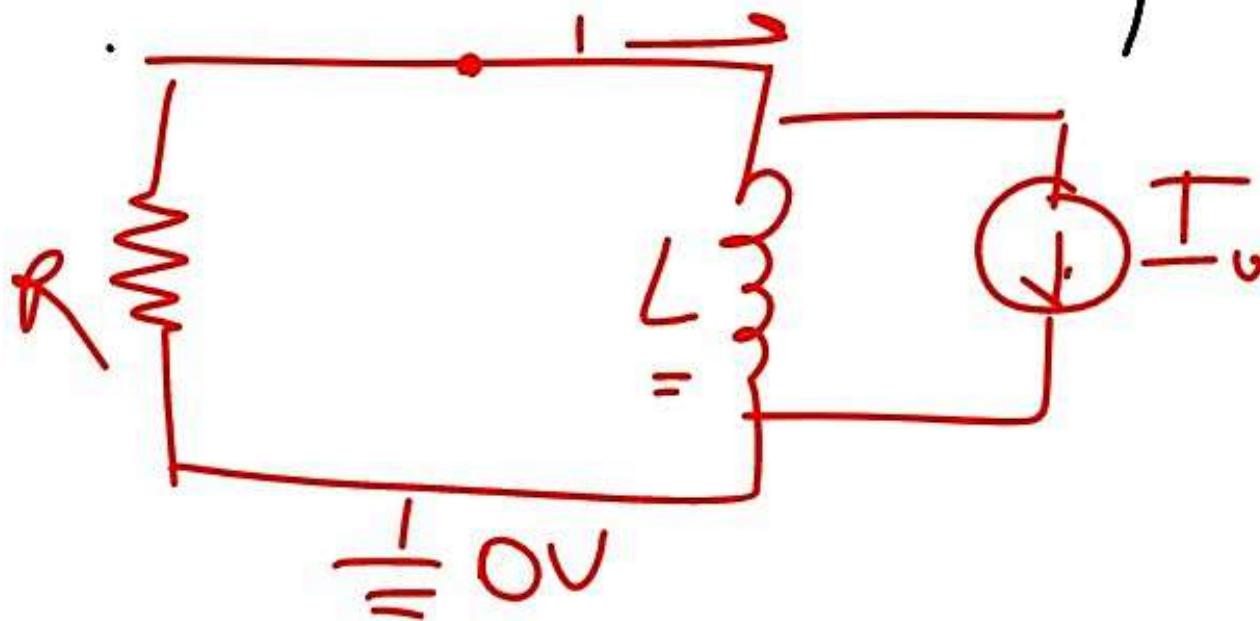

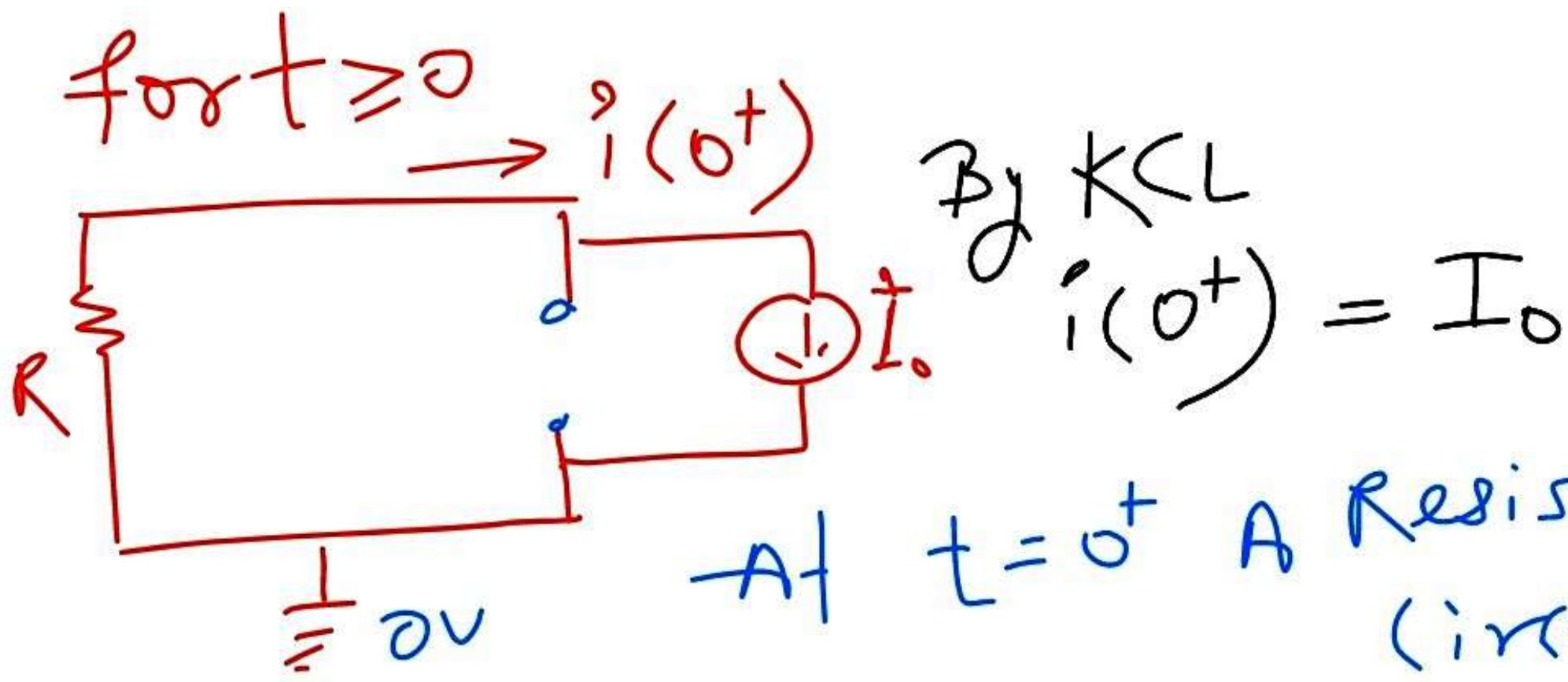

At $t = 0^+$ A Resistive circuit.

$$t = 0^+$$

$$Z_L = \infty$$

$$Z_C = \frac{1}{sc}$$

$$s \rightarrow \infty \quad Z_L = \infty$$

$$L \rightarrow 0.C$$

$$Z_C = 0 = sc$$

$$A \quad t=0^+$$

$$i(0^+) = K e^{-\sigma}$$

$$i(0^+) = K = I_0$$


$$i(t) = I_0 e^{-R/X_L t} \quad 0 \leq t \leq \infty$$

$$i(t) = I_0 e^{-t/\tau} \text{ Amp.}$$

$\tau = \frac{L}{R}$ Sec. = Time constant
of the circuit.

$$i(t) = I_0 e^{-R_L t}$$
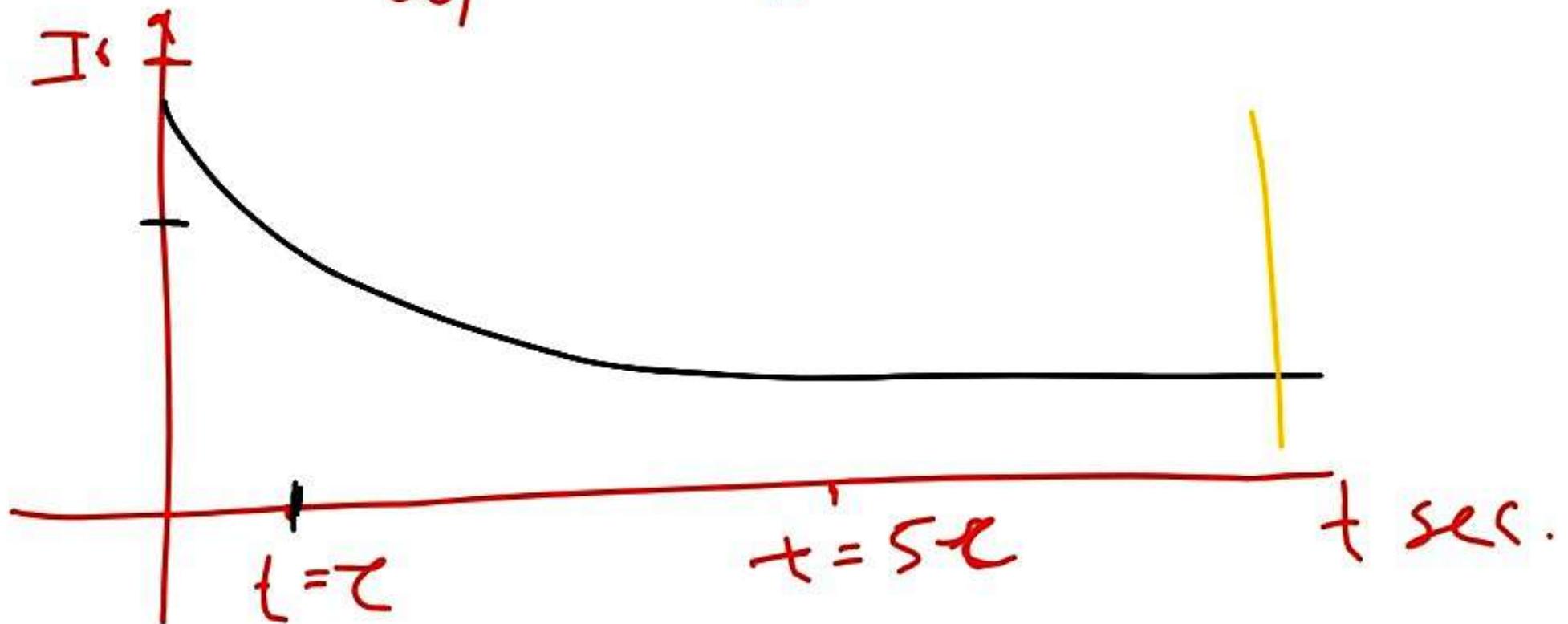
$$V_L(t) = L \frac{di}{dt}(t) \Rightarrow \text{Ohms Law}.$$



$$i(t) = I_0 e^{-t/\tau}$$

$$\text{At } t = \tau$$


$$i(t) = I_0 e^{-1}$$

$$i(t) = \frac{I_0}{e} = \underline{\underline{0.368 I_0}}$$


$$i(t) = I_0 e^{-t/c}$$

$$\underline{t = 5c}$$
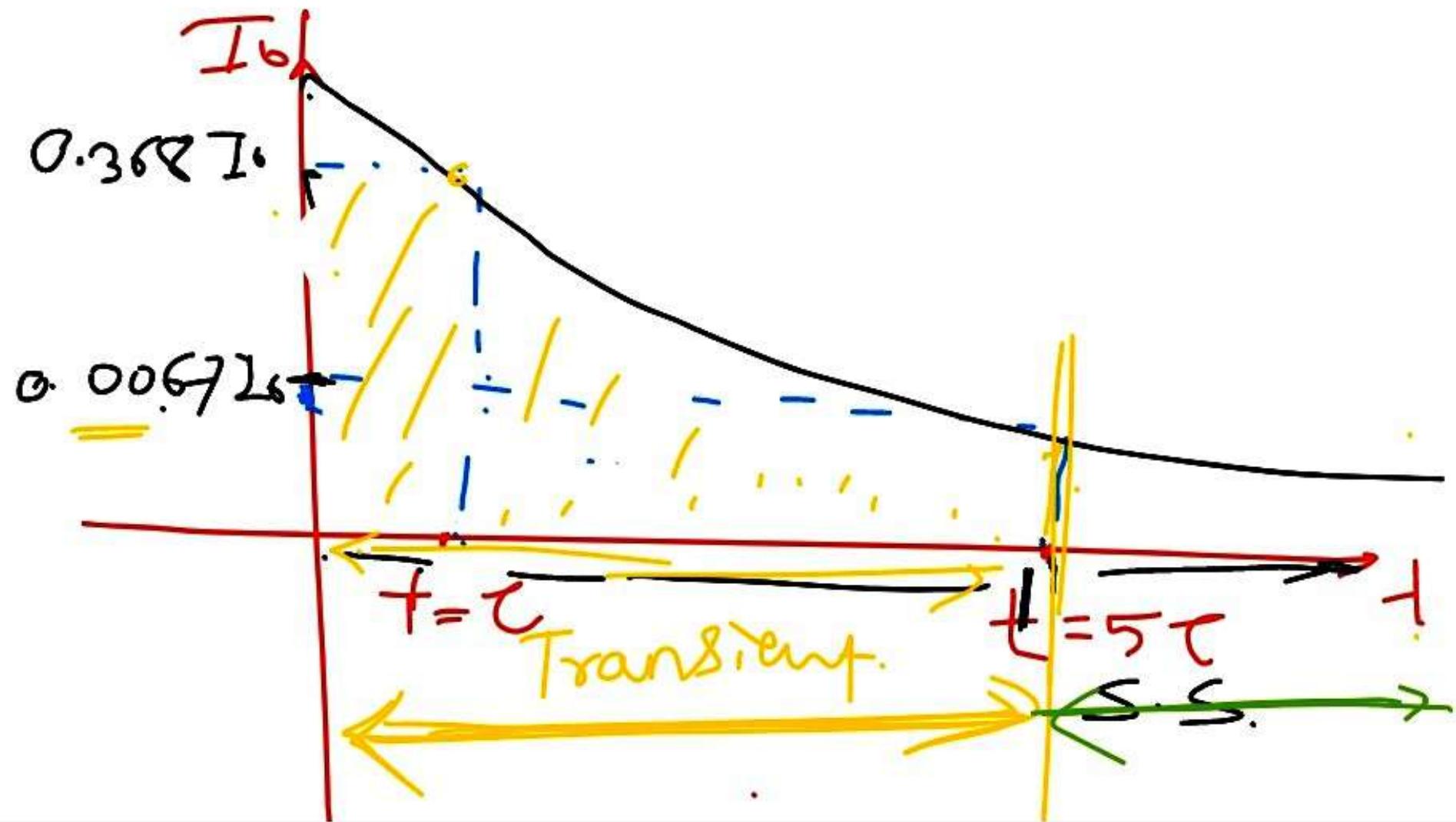
$$i(t) = \frac{I_0}{e^{\frac{t}{c}}} = 0.0067 \quad I_0 \approx 0$$



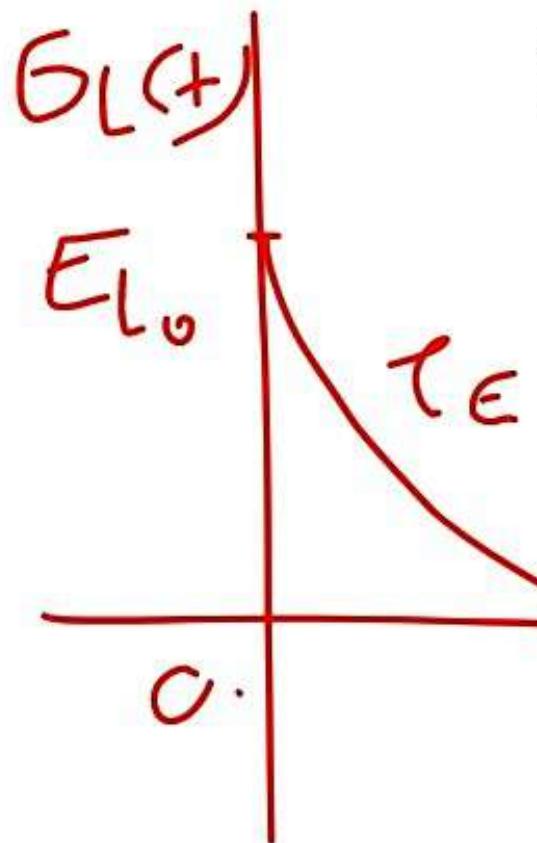
$$\begin{aligned}
 E_L(t) &= \frac{1}{2} L i^2(t) \text{ Joule} \\
 &= \frac{1}{2} L \left(I_0 e^{-t/\tau_E} \right)^2 \quad \tau_E = \frac{L}{2R} \\
 &= \frac{1}{2} L I_0^2 \cdot e^{-2t/\tau_E} \quad \boxed{\tau_E = \frac{\tau_i}{2}} \\
 &= E_{L_0} \cdot e^{-t/\tau_E} \text{ Joule}
 \end{aligned}$$



Observe: The energy decay is 2 times faster than current decay.
+ use).

Source free RC circuit :-

for $t \geq 0$

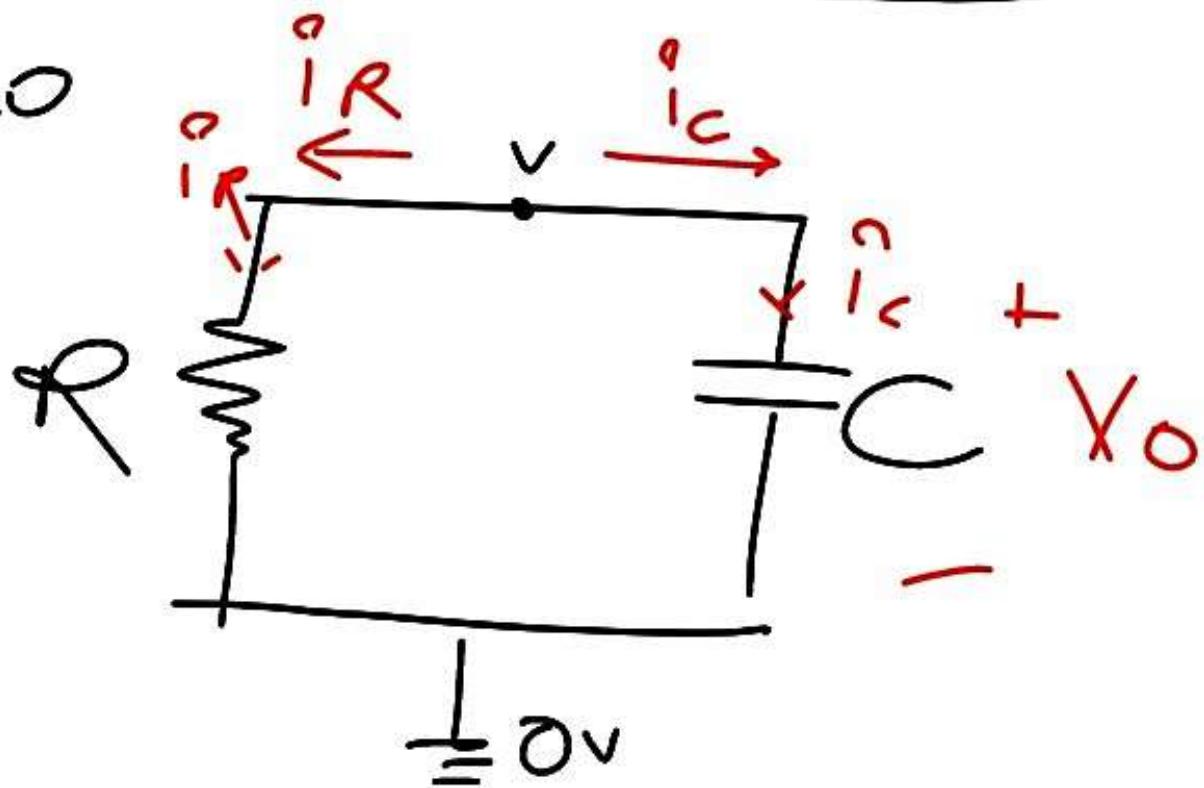

By KCL

$$\left(\frac{d}{dt} + \frac{1}{RC} \right) v = 0$$

$$i_R + i_C = 0$$


$$\frac{d}{dt} = D$$


$$\frac{v}{R} + C \frac{dv}{dt} = 0 \Rightarrow \frac{dv}{dt} + \frac{v}{RC} = 0$$

$$\left(D + \frac{1}{RC} \right) v = 0$$

$$s = \alpha$$
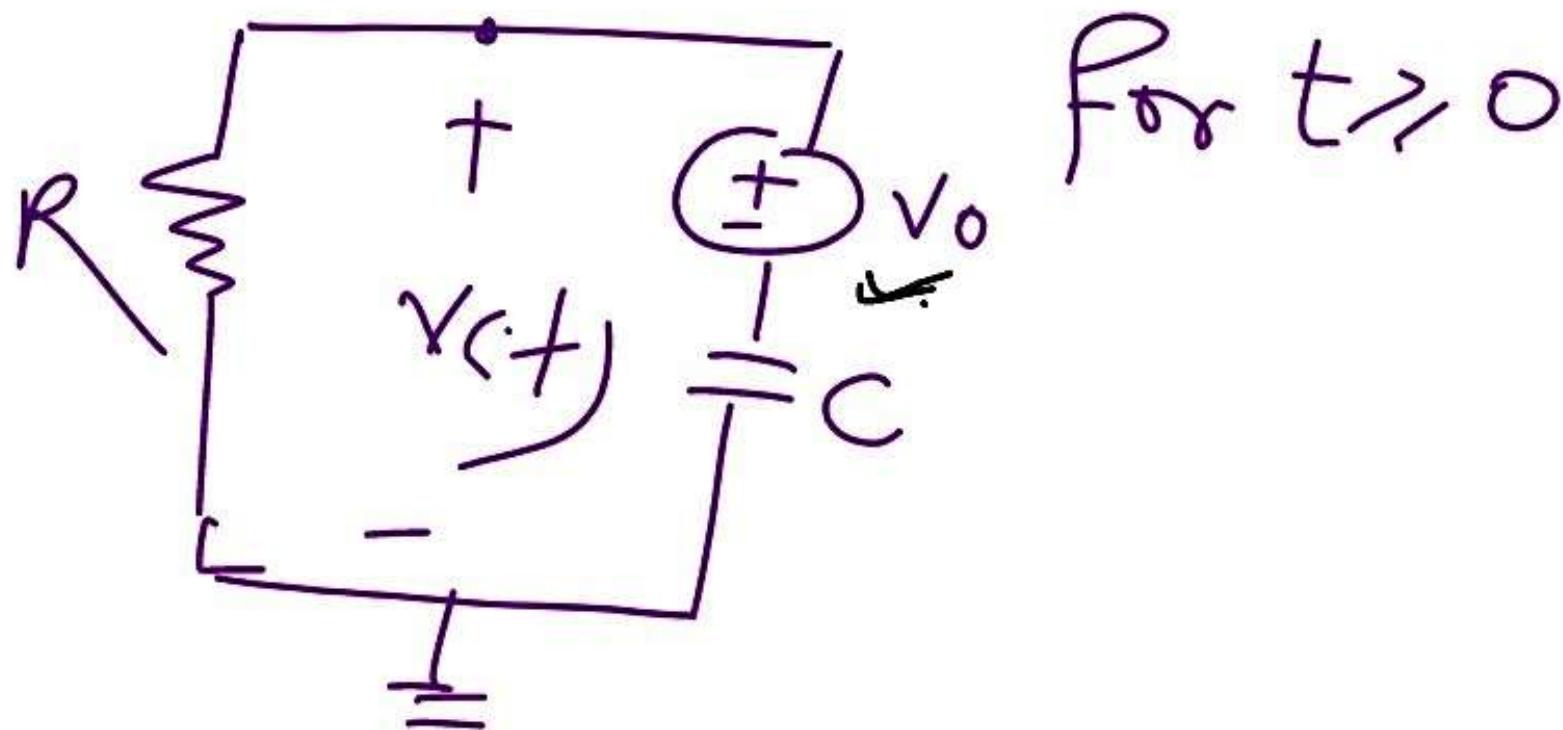
$$v(t) = K e^{-t/R_C} \text{ volt. } 0 \leq t \leq \infty$$



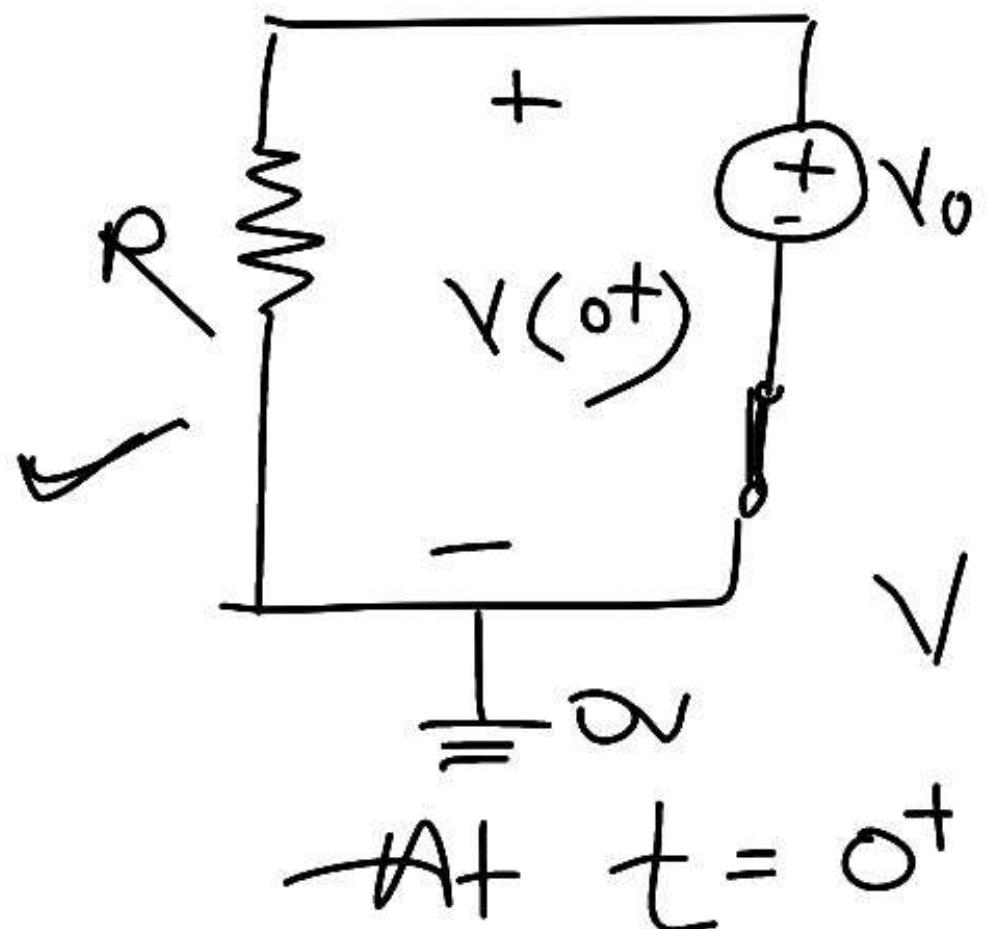

At $t = 0^+$,

\rightarrow A resistive ckt.

$$V(0^+) = V_0 \rightarrow k$$

At $t = 0^+$

$$V(0^+) = k e^0$$

$$V = V_0 = V(0^+)$$

$$V(t) = V_0 e^{-t/R_C} \quad \tau = R_C \text{ sec.}$$

$$V(t) = V_0 e^{-t/\tau} \quad 0 \leq t \leq \infty$$


$$V(t) = V_0 e^{-t/\tau}$$

① for $t = \underline{\tau}$

$$V(t) = \frac{V_0}{e} = \underline{0.368 V_0}$$

② for $t = \underline{5\tau}$
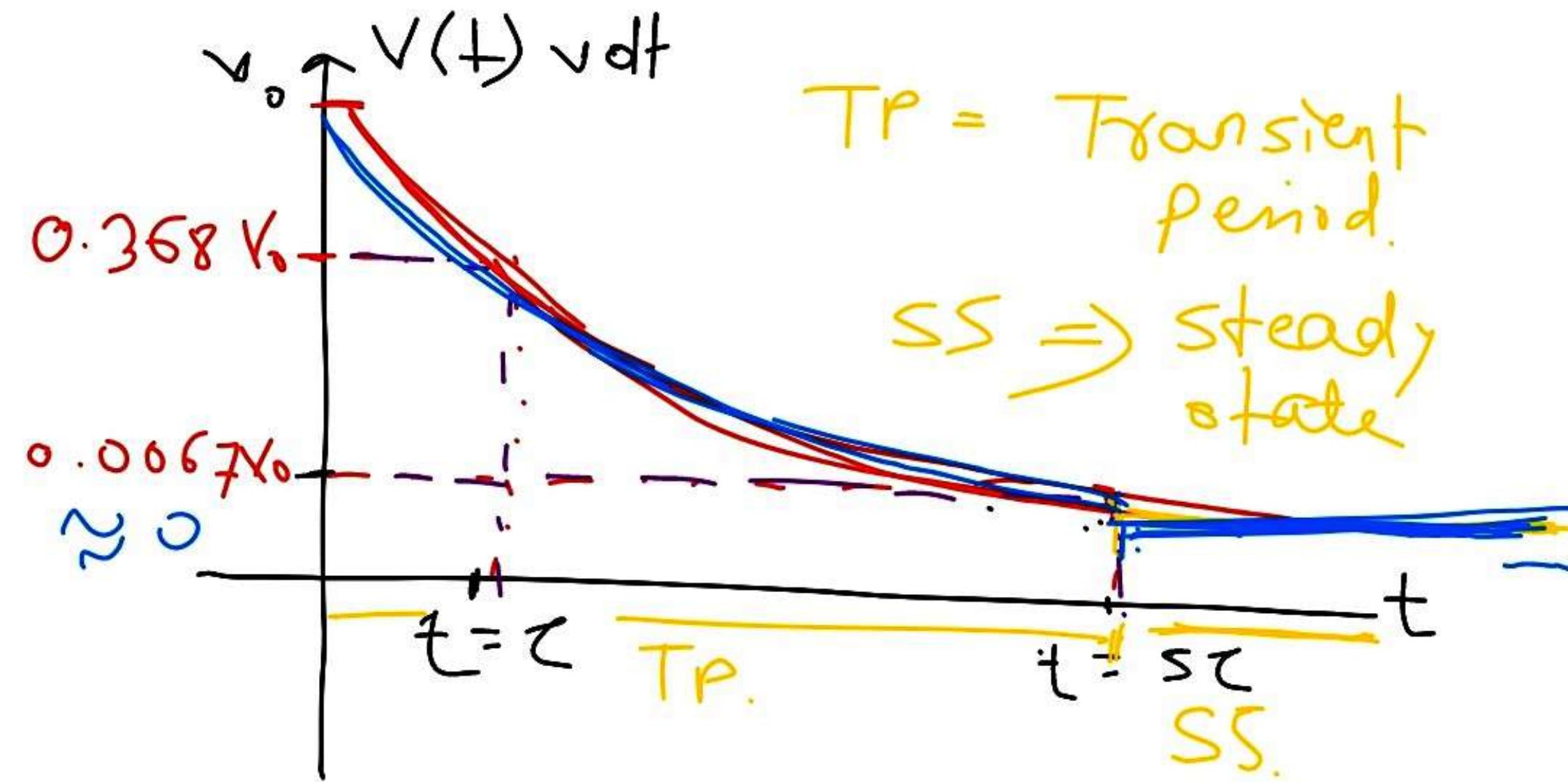
$$V(t) = \frac{V_0}{e^5} = \underline{0.0067 V_0}$$



$$E_C(t) = \frac{1}{2} C V^2(t) \quad \text{Take}$$

$$= \frac{1}{2} C (V_0 e^{-t/\tau})^2$$

$$(a^m)^n = a^{mn}$$

$$= \frac{1}{2} C V_0^2 e^{-2t/\tau}$$

$$= E_{Co} e^{-2t/\tau_v}$$

$$E_C(t) = E_{C_0} e^{-2t/\tau_E}$$

$$\tau_E = \frac{\tau_V}{2}$$

$$E_C(t) = E_{C_0} e^{-t/\tau_E} \text{ Joule}$$

$$\tau_E = \frac{RC}{2} \text{ sec.}$$

Here the energy decay
is 2 times faster than
voltage decay.

$$\tau_i = \tau_v = \frac{L}{R} = R_C \checkmark$$

$$\frac{L}{CR^2} = 1 \Rightarrow \text{unitless.}$$

$$\frac{CR^2}{L} = 1 \Rightarrow \text{unitless.} \checkmark$$


$$CR^2 = L \Rightarrow \text{Henry.}$$

$$C = \frac{L}{R^2} = \text{farad.}$$

$$\frac{L}{RC} = R = \text{Ohm.}$$

$$\frac{L}{C} = R^2 = \text{Ohm}^2$$

$$\sqrt{\frac{L}{C}} = R = \text{ohm}$$

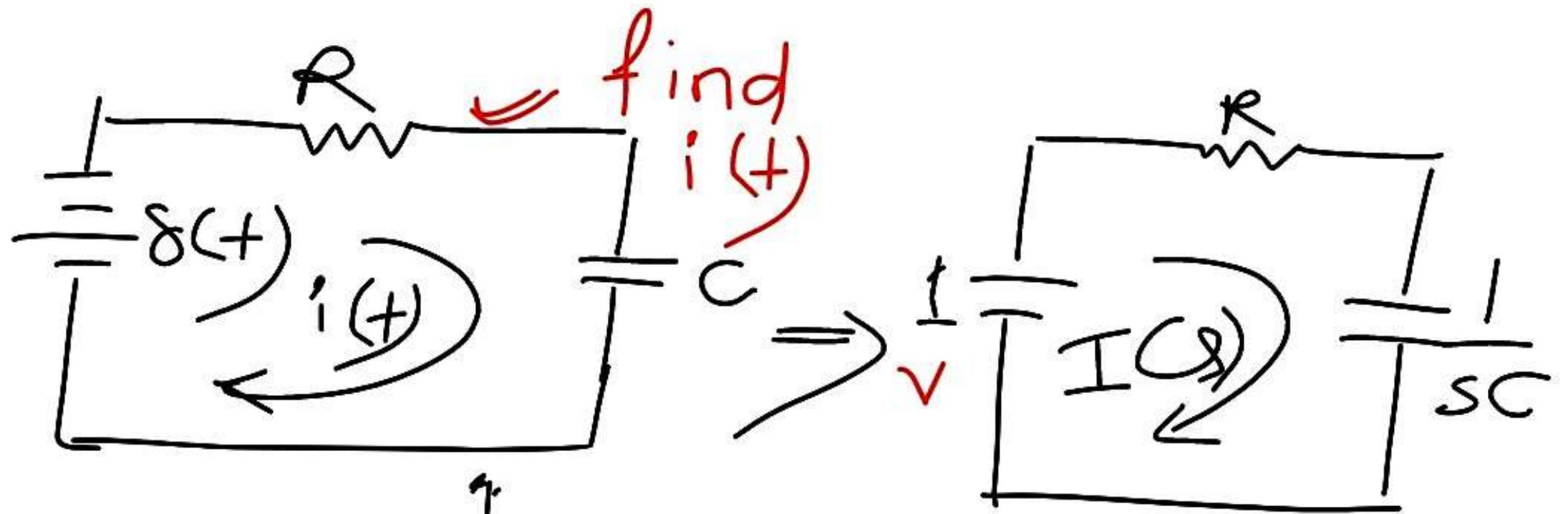

$$I(s) = \frac{1}{R + \frac{1}{sC} + L} = \frac{sC}{sRC + 1}$$

$$I(s) = \frac{V}{R}$$

Divide Num. & Den. by R_C .


$$I(s) = \frac{sC}{s + \frac{1}{R_C}} \Rightarrow \frac{s/R}{s + \frac{1}{R_C}}$$

$$I(s) = \frac{1}{R} \left(\frac{s + \frac{1}{R_C} - \frac{1}{R_C}}{s + \frac{1}{R_C}} \right)$$


$$I(s) = \frac{1}{R} \left(1 - \frac{1/R_C}{s + 1/R_C} \right)$$

$$i(t) = \frac{1}{R} \left(s(t) - \frac{1}{R_C} e^{-t/R_C} \right)$$

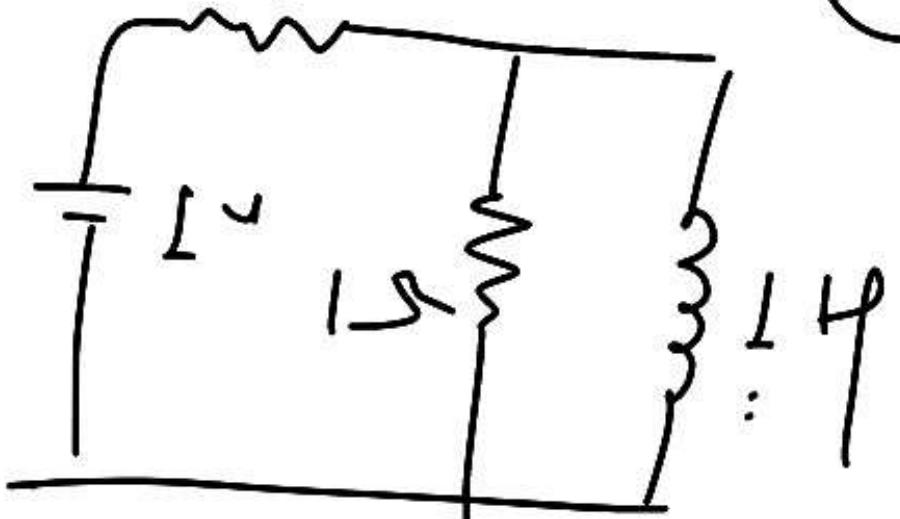Determine the time
for following circuit constants




$$T = \frac{1}{R_{eq}}$$

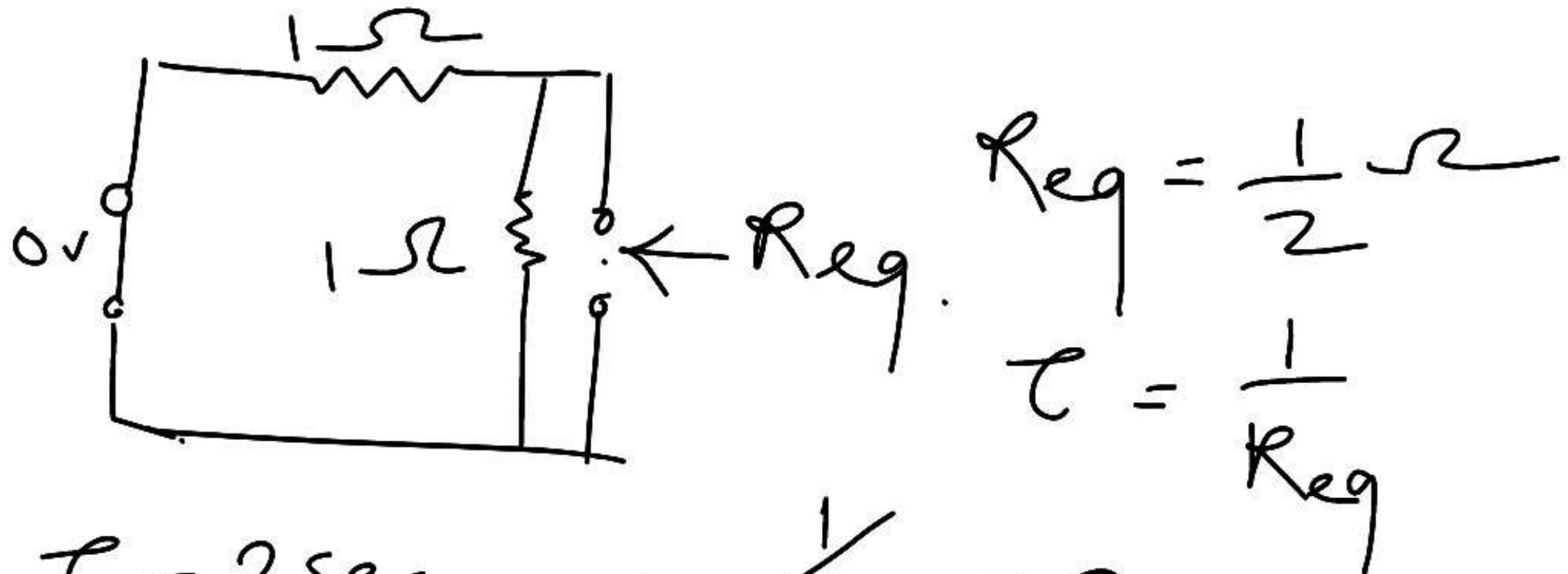

$$\tau = 2 \text{ sec.} = \frac{1}{\frac{1}{2}} = 2$$

$$R_{eq} = \frac{1}{2} \text{ ohm}$$

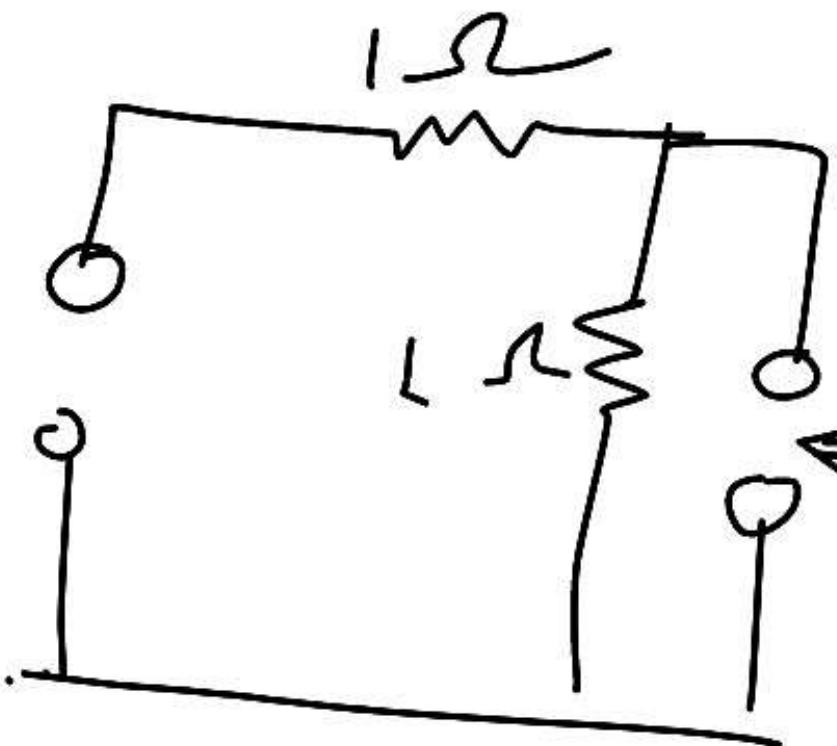


$$\boxed{\tau = 1}$$

$$R_{eq} = 1 \Omega$$

$$\tau = \frac{1}{R_{eq}}$$

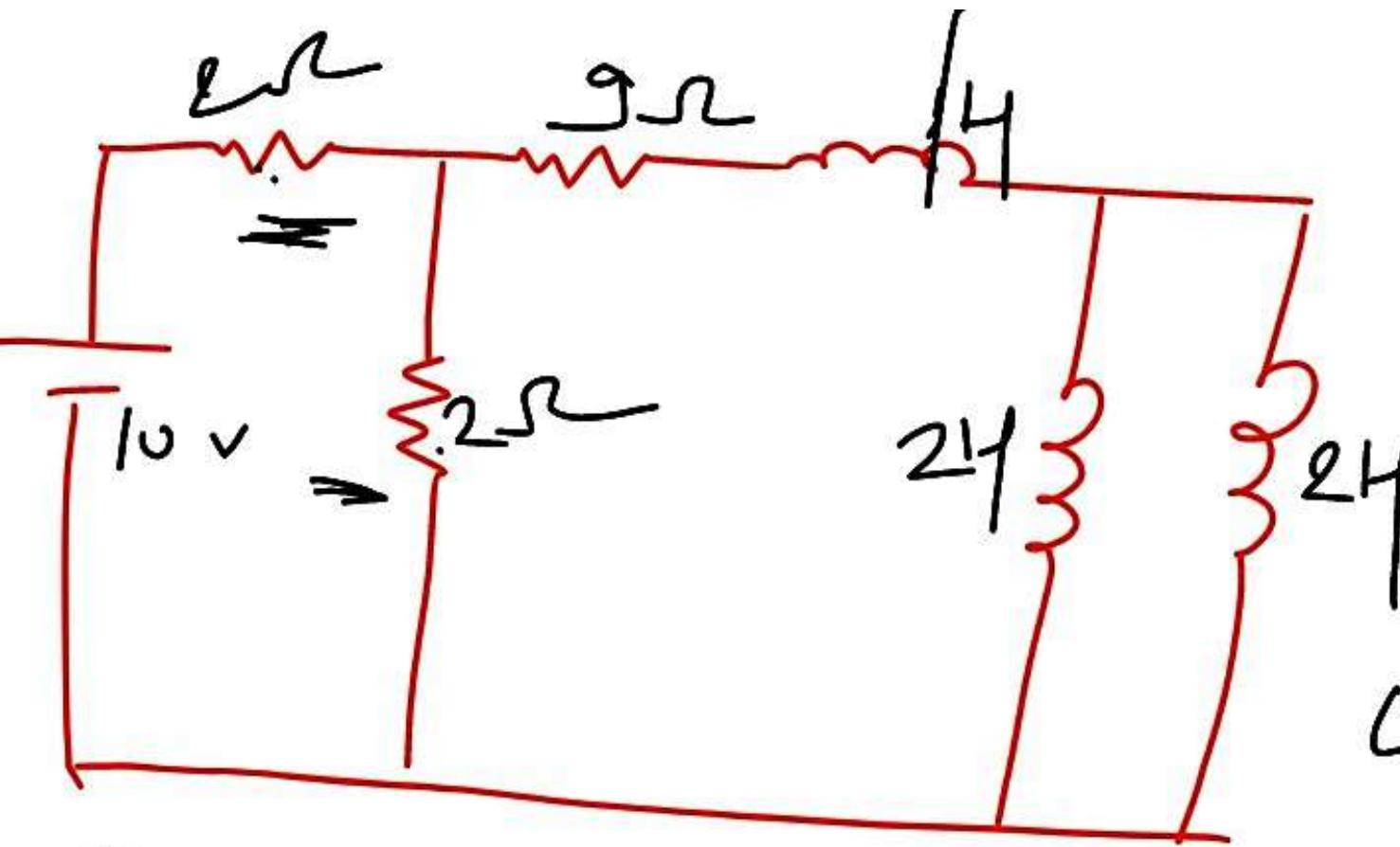
Obs:- Here R_{eq} is the equivalent resistance experienced by the source current connected across the open inductor load terminals after eliminating internal independent source.



$$L_{eq} = \frac{1 + 2 \parallel 2}{1 + \frac{2 \times 2}{2+2}}$$


$$L_{eq} = 1$$

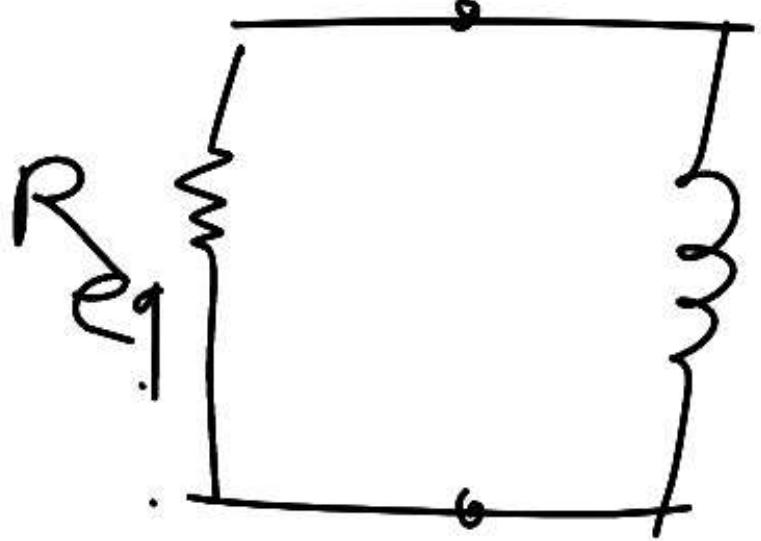
$$R_{eq} = 9 + 2 \parallel 2 \Rightarrow 9 + \frac{2 \times 2}{2+2} = 10$$



$$\tau = \frac{L_{eq}}{R_{eq}}$$
$$\tau = \frac{2}{10}$$
$$= \tau = 0.25 \text{ sec.}$$

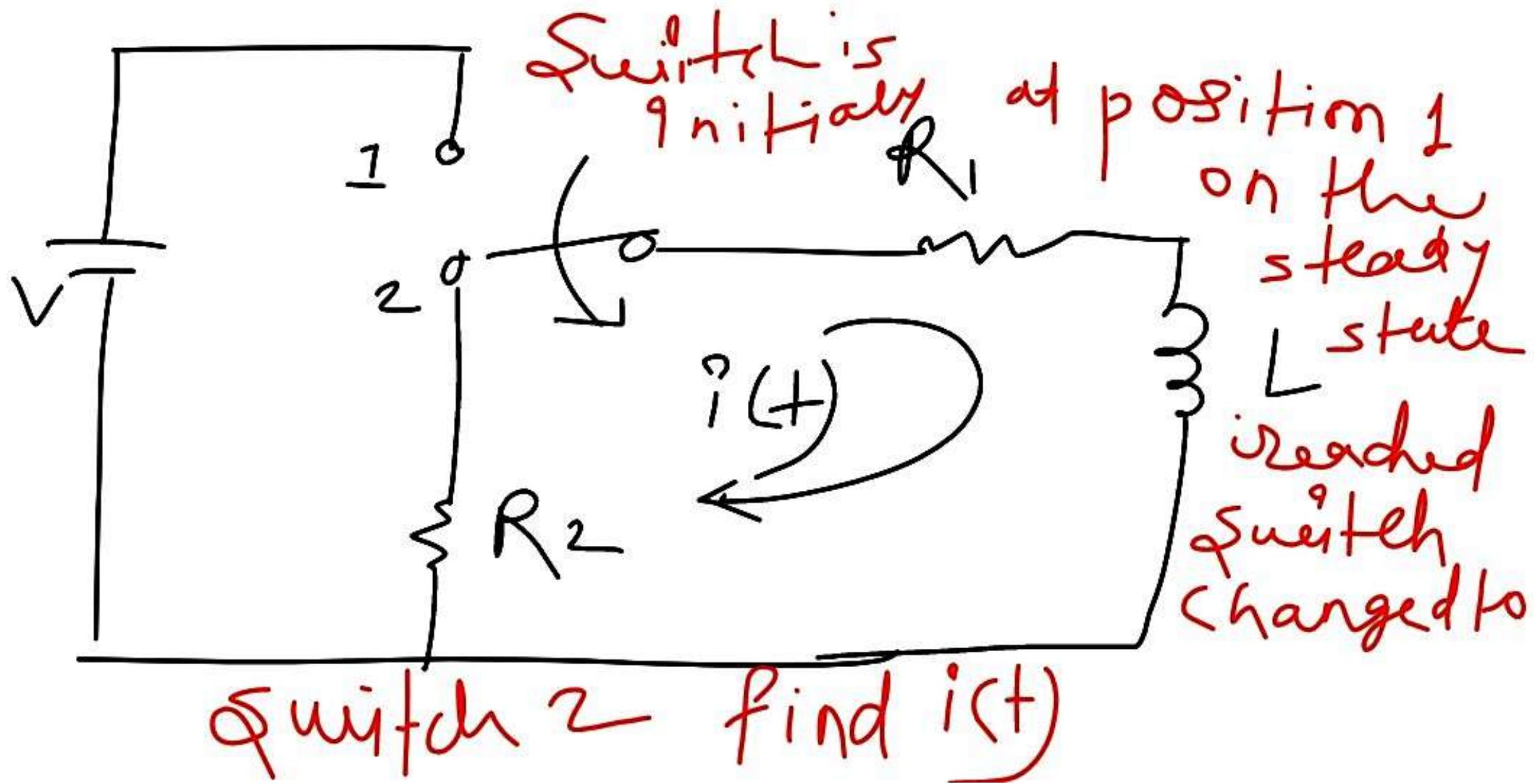Note When Resistor & inductor
are not separable, then circuit
will have multiple time
constants & the Laplace
transform approach (LTA)
is used to evaluate the
constants.



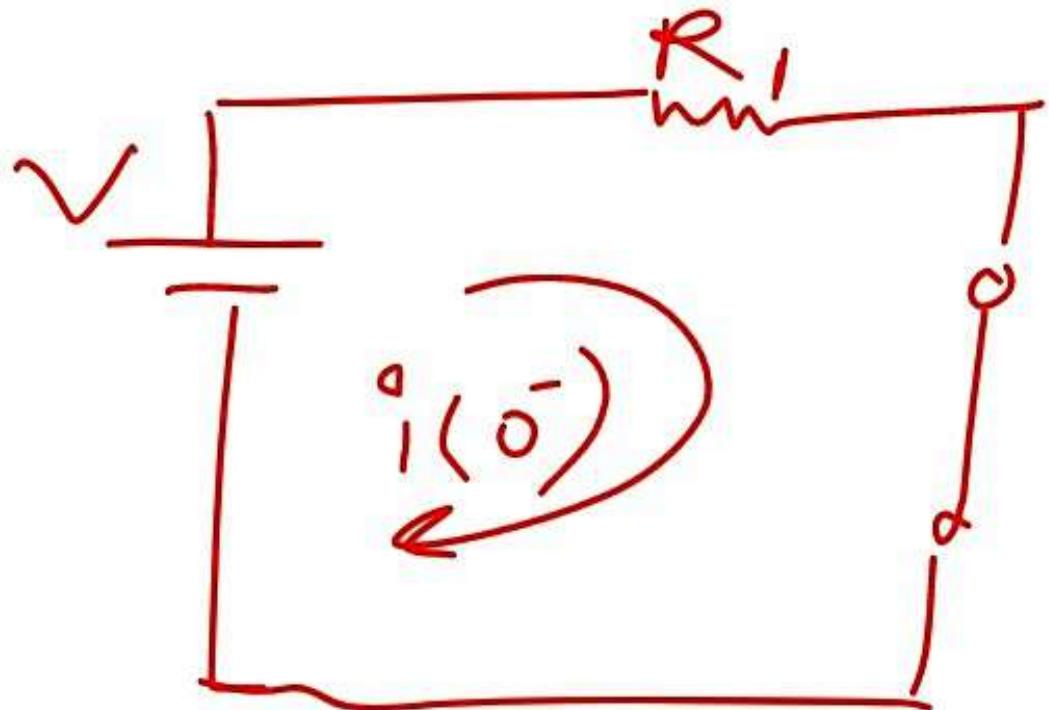


$$i(0^-) = \frac{V}{R_L}$$

At $t = 0^-$

Nw. attained.
ss. Hence
L acts as SC.

Since inductor does not allow sudden change.

$$i(0^+) = \frac{V}{R}$$

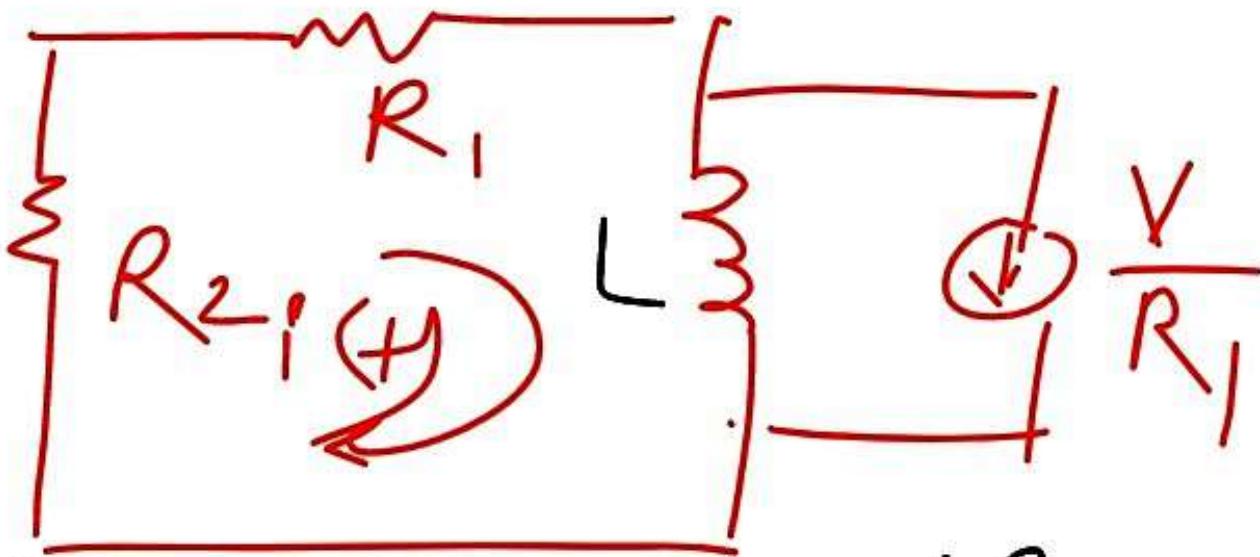

$$(R_1 + R_2)i + L \frac{di}{dt} = 0 \Rightarrow$$

$$\frac{di}{dt} + \left(\frac{R_1 + R_2}{L} \right) i = 0$$

$$i(t) = k e^{-\left(\frac{R_1 + R_2}{L}\right)t}$$

$$\text{At } t=0, i(0) = \frac{k}{R} = k$$

$$i(+)=\frac{V}{R_1} e^{-\left(\frac{R_1+R_2}{L}\right)t}$$

[The capacitor in the circuit as shown below is initially charged to 12 volt with s_1 & s_2 open]. s_1 is closed at $t = 0$ while s_2 is closed at $t = 3$. The waveform of capacitor current will be:


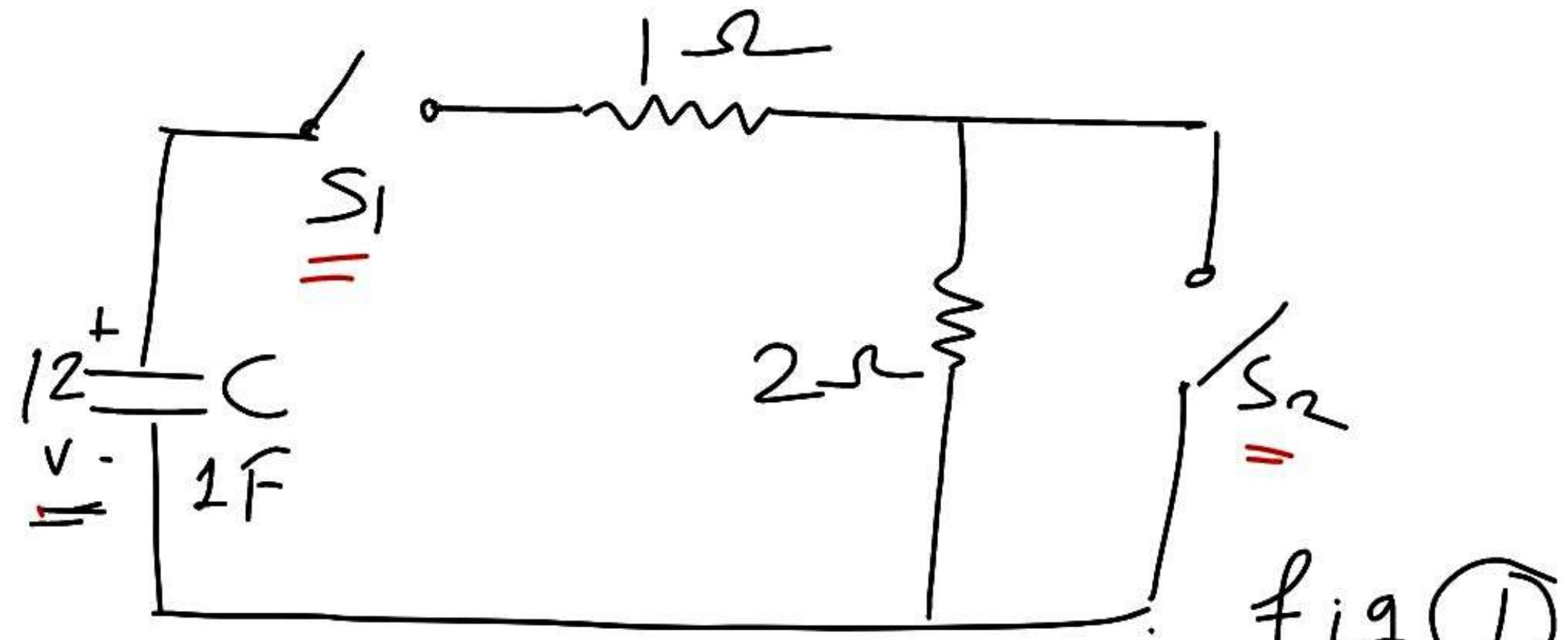


fig ①

for. $0 < \underline{t} < 3$

for S_1 closed & S_2 closed.

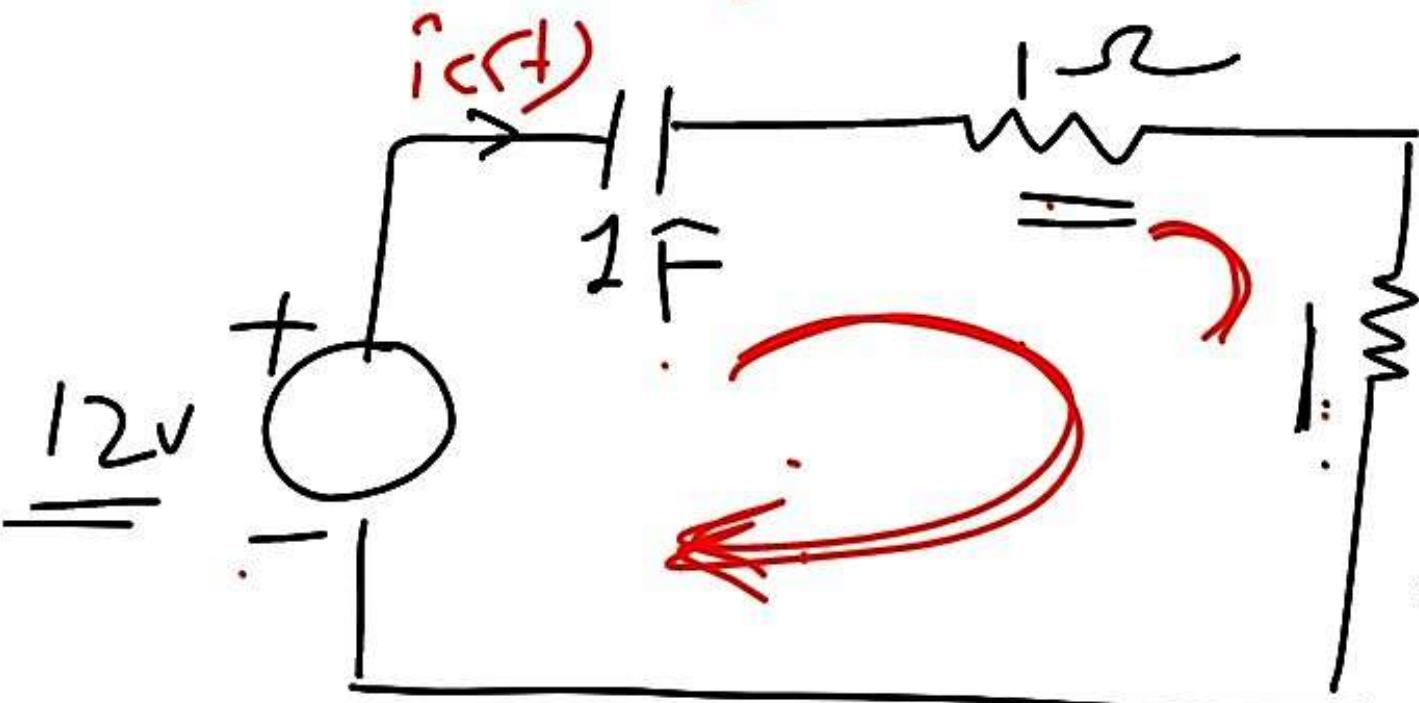

$$i_C(0+) = \frac{12}{3}$$

$$= 4 \text{ Amperes}$$

$$\underline{\underline{L}} = R C = 3 \times 1$$
$$= 3 \text{ seconds}$$


$0 < t < 3$ fig ②

$$i(t) = 4 e^{-t/3} \quad i(0) = 4 = K$$

$$i(3) = 4 e^{-1} \quad (\text{At } t=3) = \\ = 1.47 \quad \checkmark$$

$$V_C(3) = V_C(3^+) = i(5) \cdot R \\ = 4 e^{-1} \times 3 = 4 \cdot 4$$

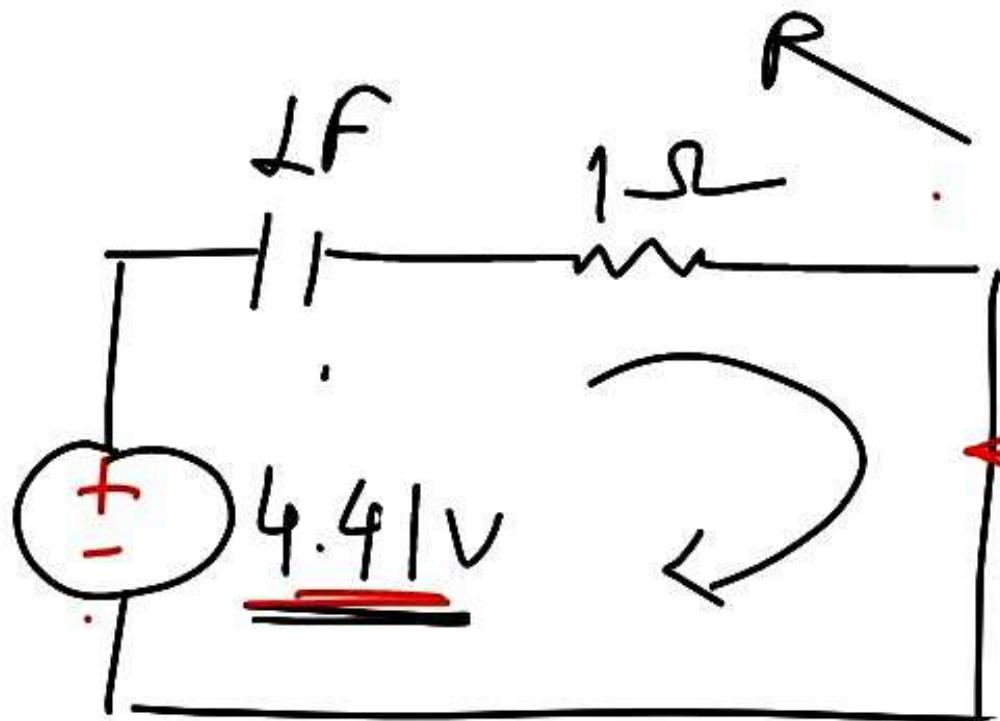
$$\overset{?}{i_c(3^+)} = \frac{v_c(3^+)}{R} = \frac{4.41}{1} = \underline{\underline{4.41}}$$



$c < t < 3$

$for 3 < t < \infty$

$$\overset{?}{i_c(\infty)} = 0$$

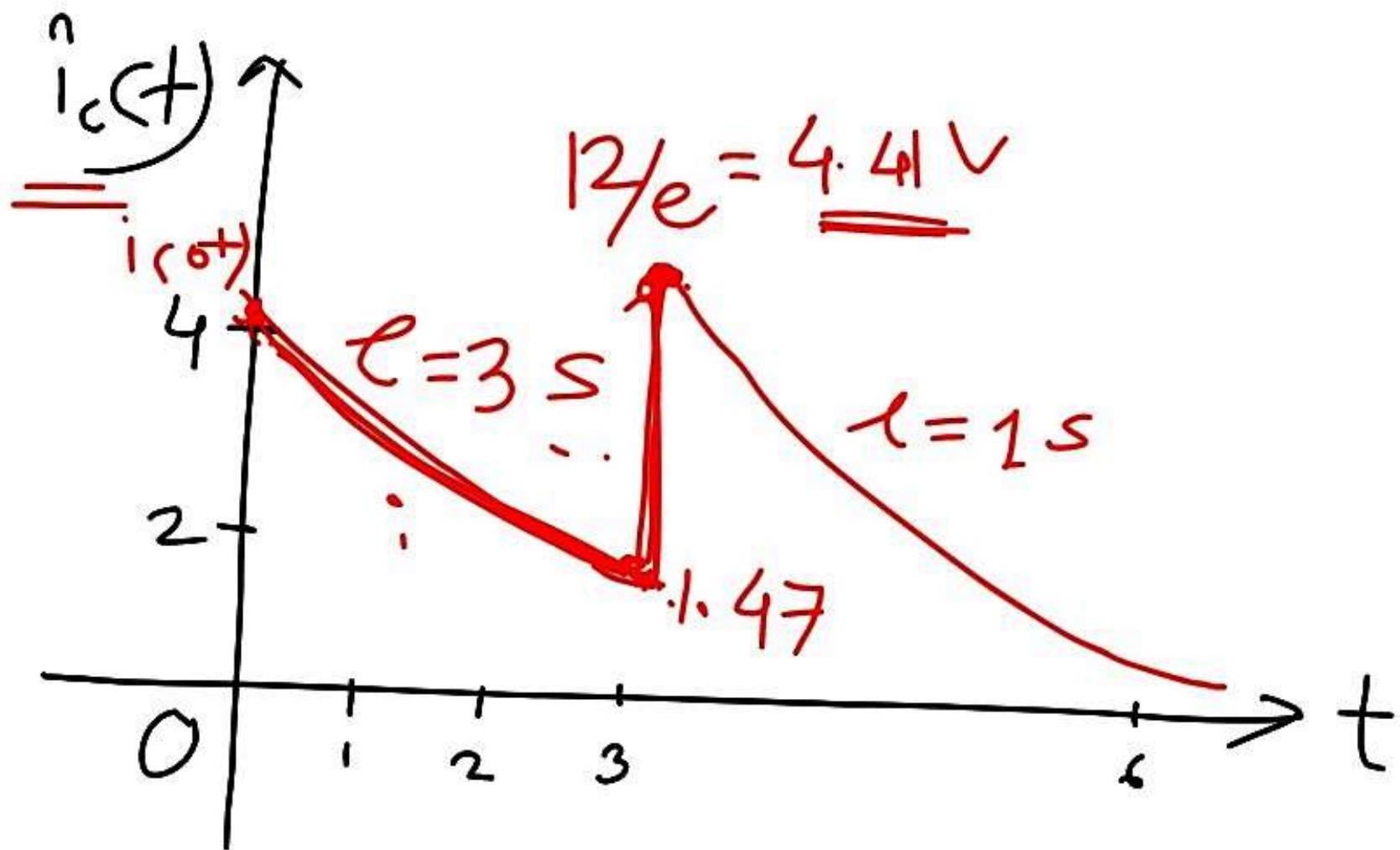

With source circuit & using
Laplace Transform Analysis.


Behaviour of inductor & capacitor
with sources initial ($t = 0^+$)
& final ($t \rightarrow \infty$)


At $t = 0^+$ $\Rightarrow L = 0C \Rightarrow C = \infty$

At $t \rightarrow \infty \Rightarrow L = \infty C \Rightarrow C = 0C$

L & C elements will lose their significance & hence the circuit nature is resistive.

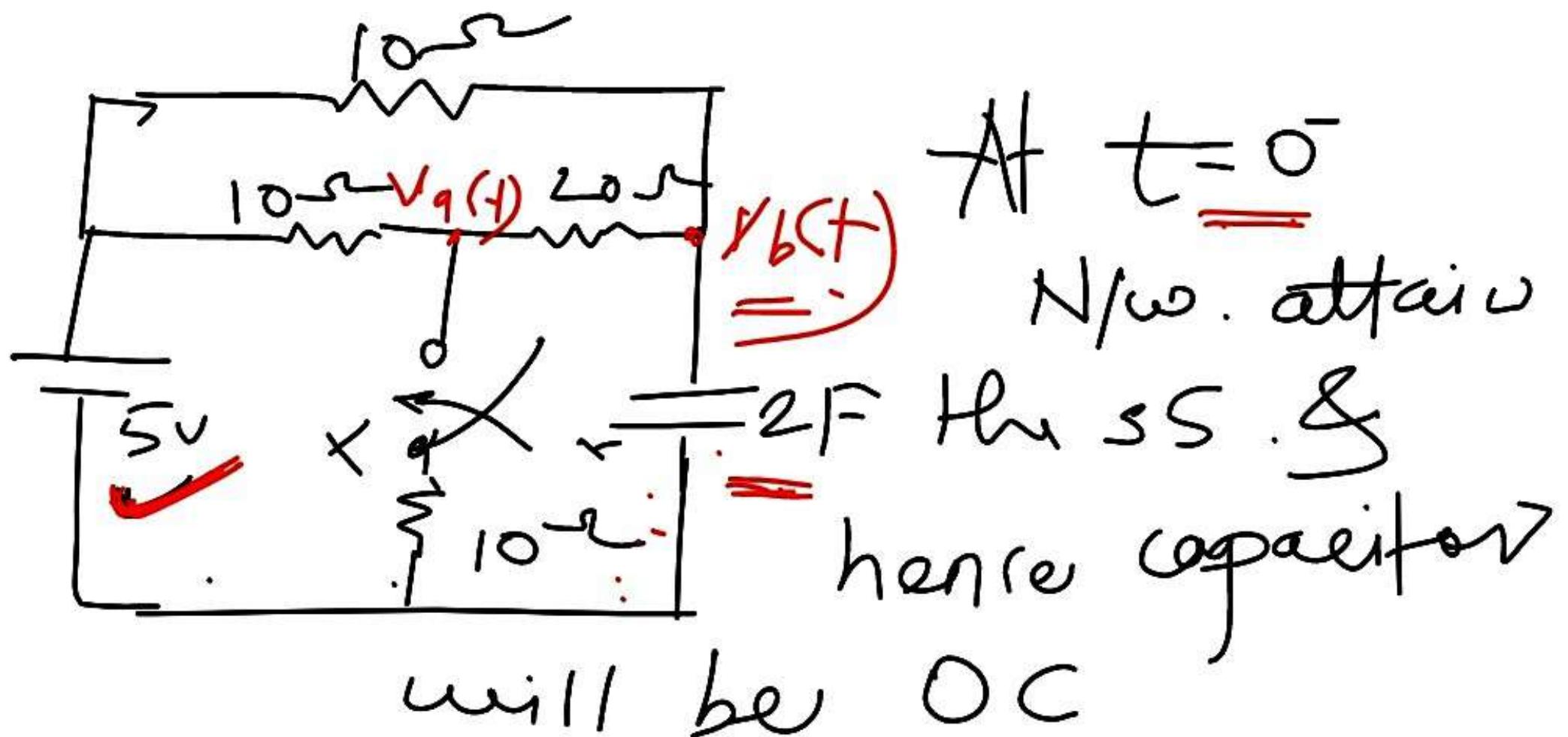
In a NW. which is a steady state
is reached with switch open
At $t = 0$, switch is closed. Determine
 $x_q(0^-)$ $v_a(0^+)$ & $v_b(0^+)$ &
 $v_b(0^-)$



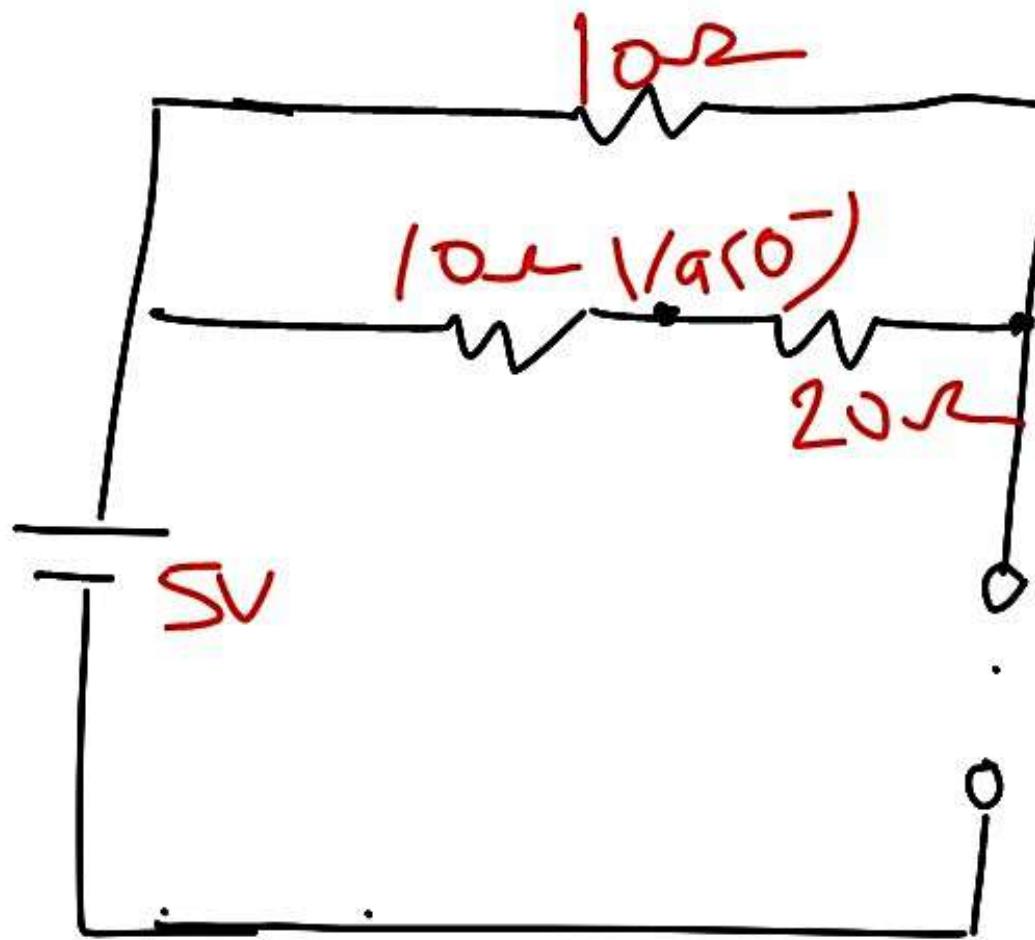

$$V_a(0^-) = 5V$$

$$\underline{V_b(0^-)} = 5V$$

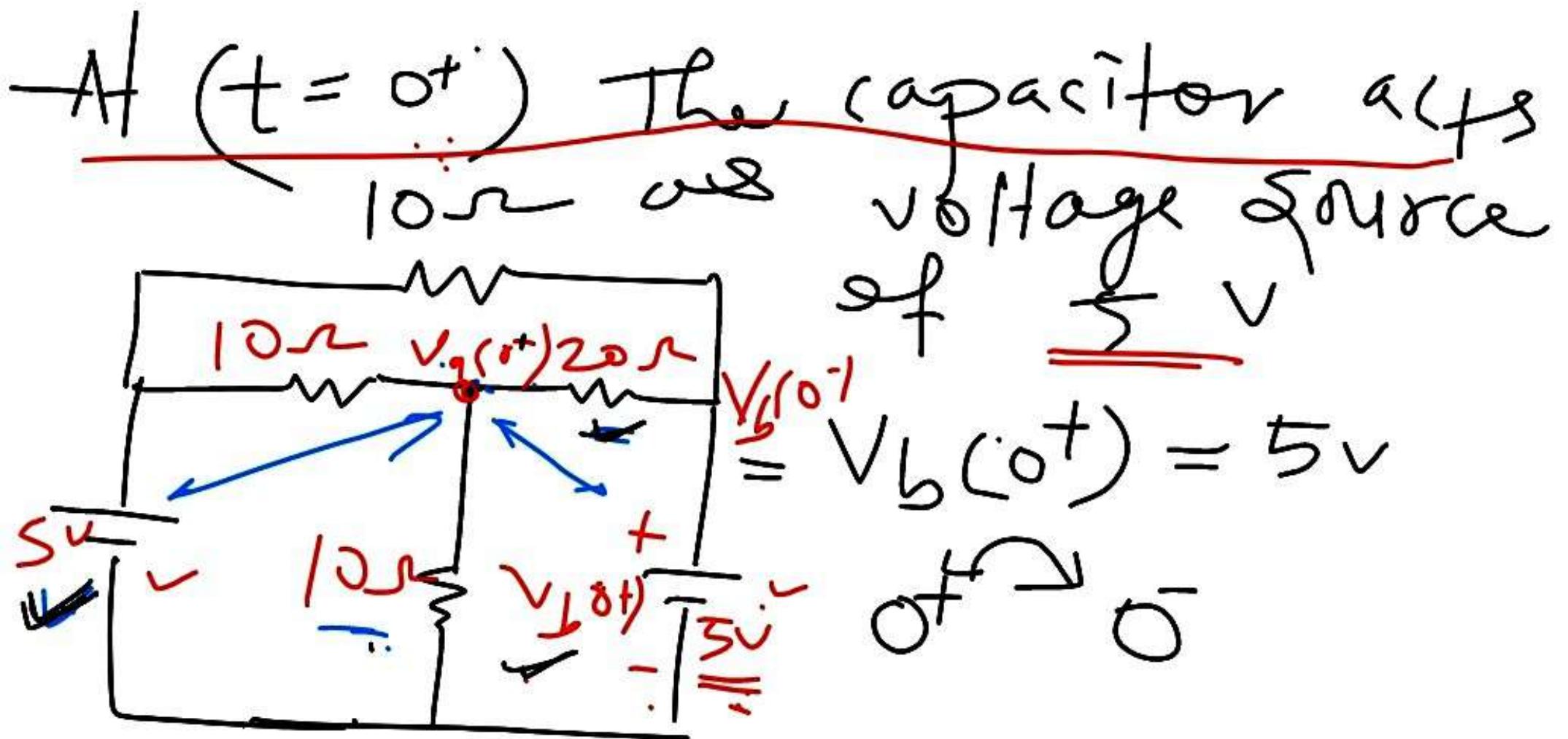

find $V_q(0^+)$

writing KCL eqn at $t = 0^+$

$$\frac{V_q(0^+) - 5}{10} + \frac{V_q(0^+)}{10} + \frac{V_q(0^+) - 5}{20} = 0$$

$$V_q(0^+) = \frac{2V_q(0^+) - 10 + 2V_q(0^+) + V_q(0^+) - 5}{20}$$


$$\frac{V_a(0^+) - 15}{20} = 0$$

$$| V_a(0^+) = \frac{15}{5} = 3 \text{ volt} |$$

- C ← 0⁺

AC Transients :-

① Series RL circuit :-

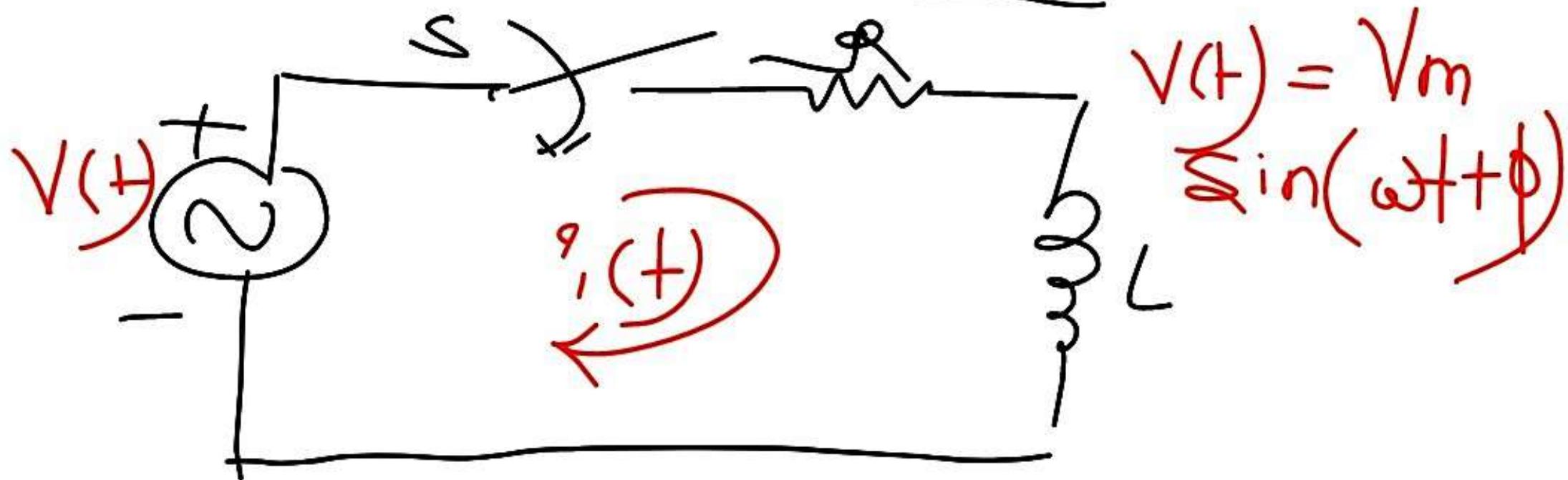

$$i(t) = i_{tr}(t) + i_{ss}(t)$$

$i_{tr}(t) \Rightarrow$ Transient ✓ Natural Response


$i_{ss}(t) \Rightarrow$ steady state. ✓ forced response.

$$i(t) = K e^{-t/\tau} + i_{ss}(t)$$

$$= [K e^{-R/L t}] + i_{ss}(t) \checkmark$$

*
Transient
Response

↓
steady
response.

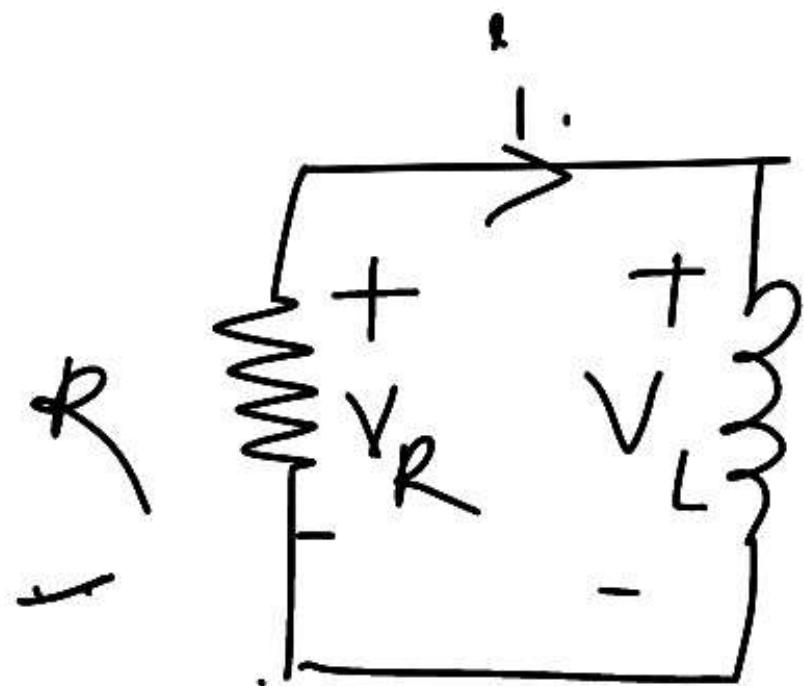

By KVL

$$-V_R - V_L = 0$$


$$\Rightarrow \frac{di}{dt} + \frac{R}{L}i - Ri = 0$$


Let

$$\dot{\phi} = \frac{1}{L} \Rightarrow \left(D + \frac{R}{L} \right) i = 0$$

$$\dot{\phi} = -\frac{R}{L} \quad S = \alpha \\ i(t) = k e^{\alpha t} \quad \text{for } 0 \leq t \leq \infty$$
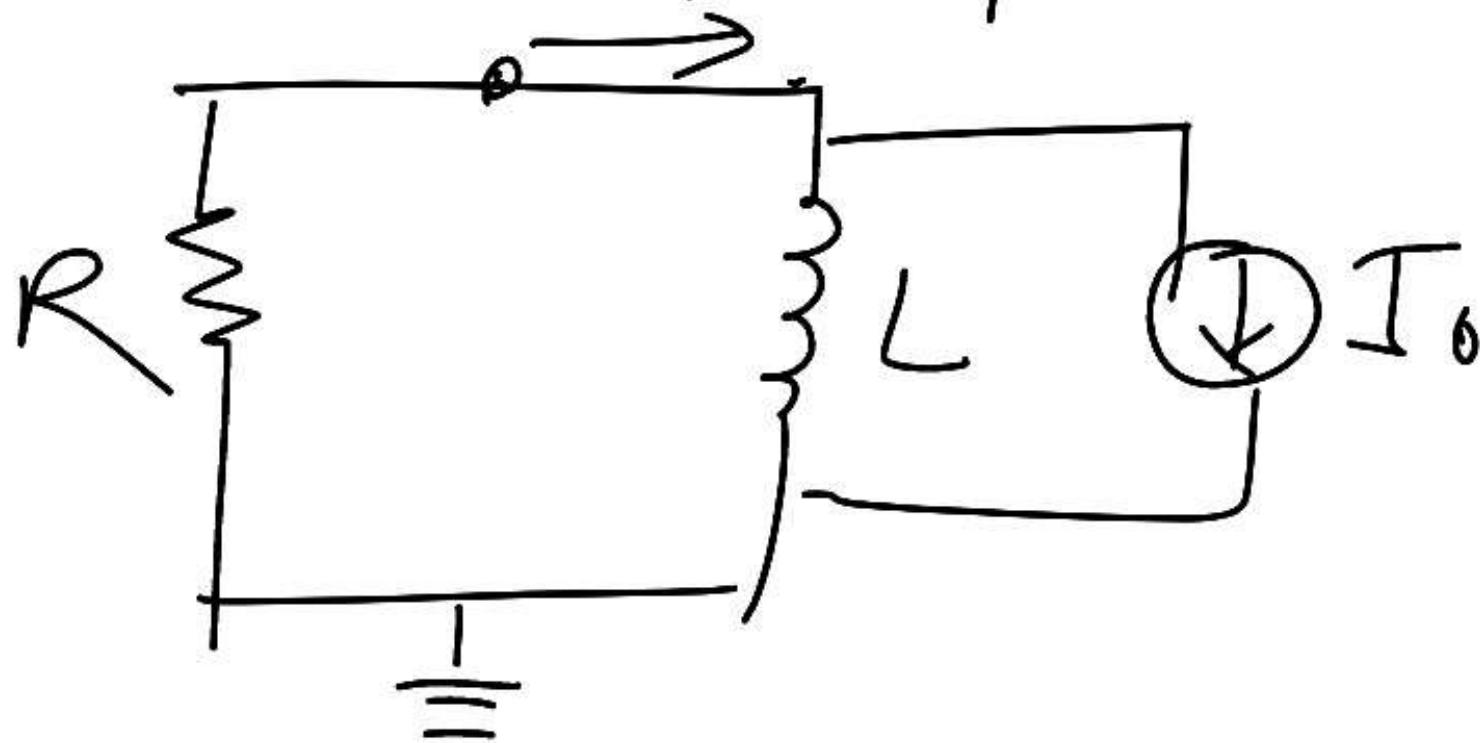
$$= k e^{-R_L t} \text{ Amp for } 0 \leq t \leq \infty$$



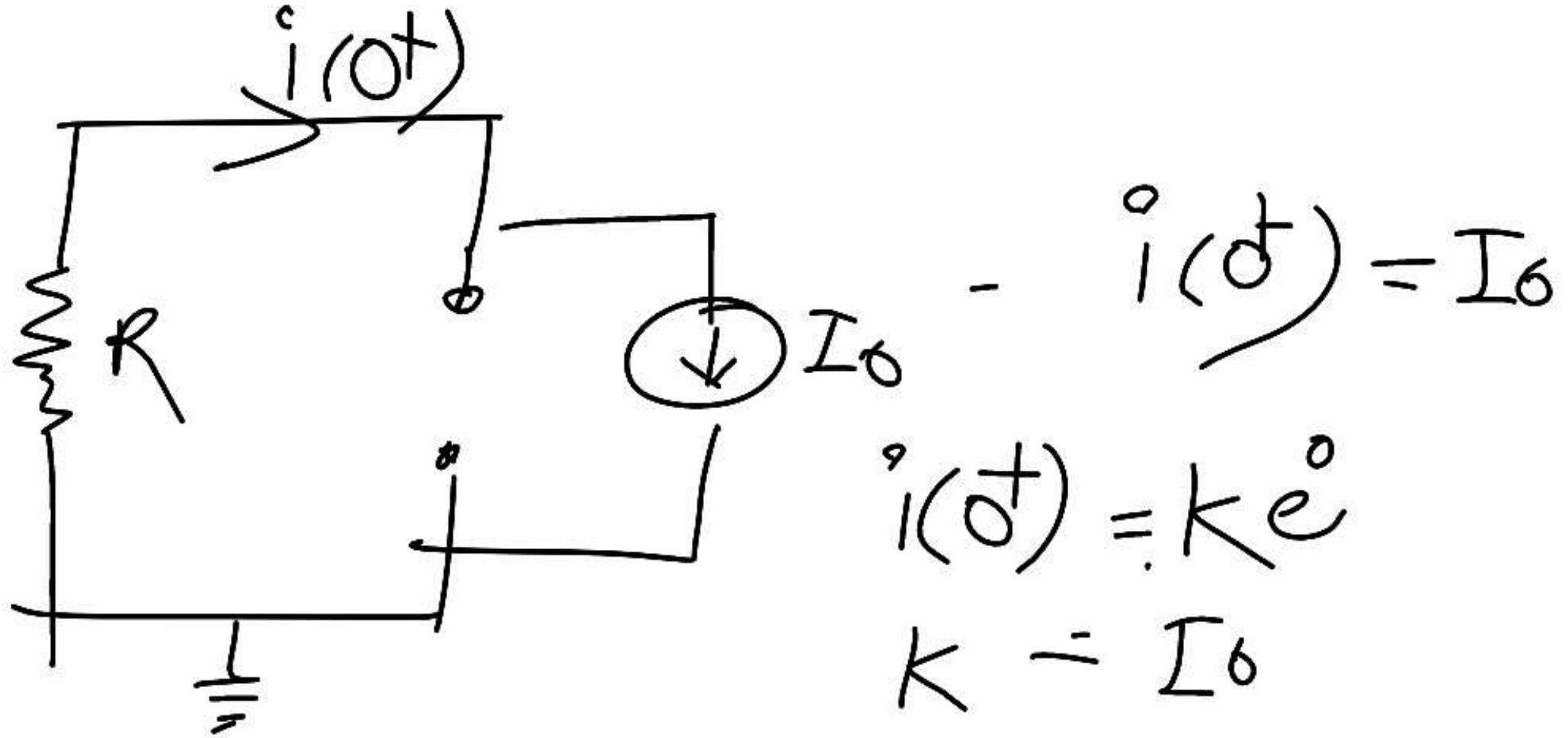


$$i(0^+) = k e^{-\sigma} = I_0$$

$$I(t) = I_0 e^{-R/L t}$$


$$i(t) = I_0 e^{-t/\tau}$$

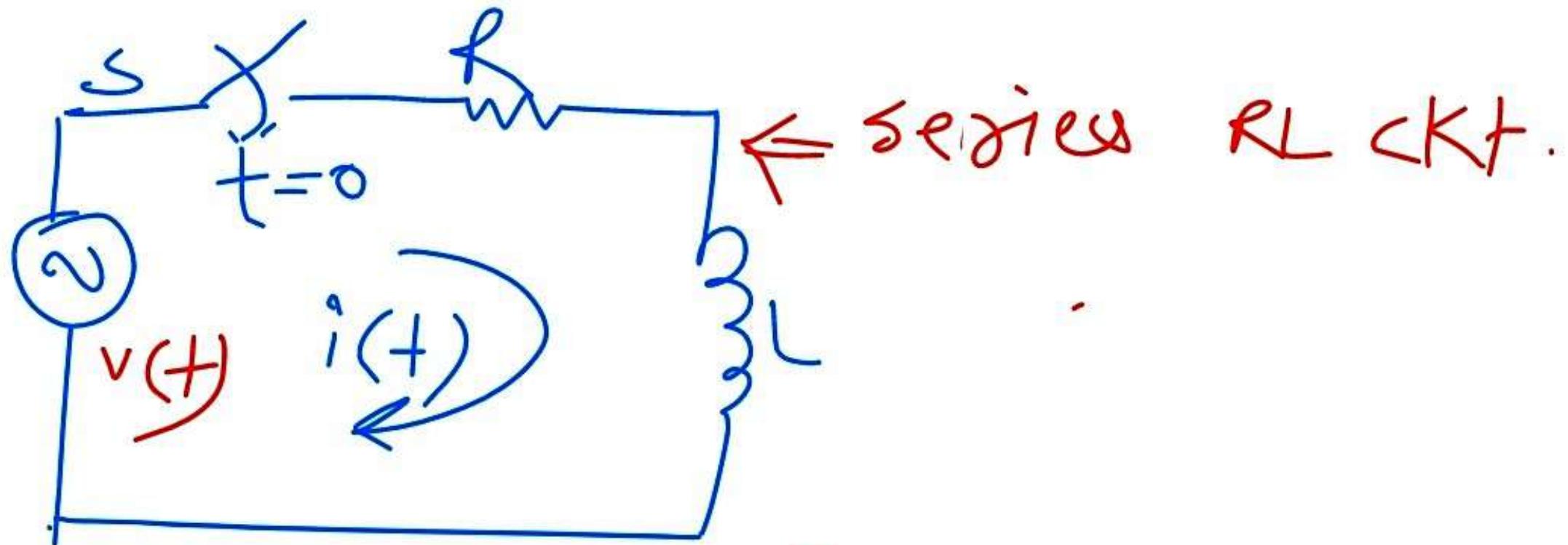
$$\tau = L/R \Rightarrow \text{Time constant}$$



$$i(t) = \underline{i_{tr}(t)} + i_{ss}(t)$$

$$i_r(t) = k_e^{-t/\tau}$$

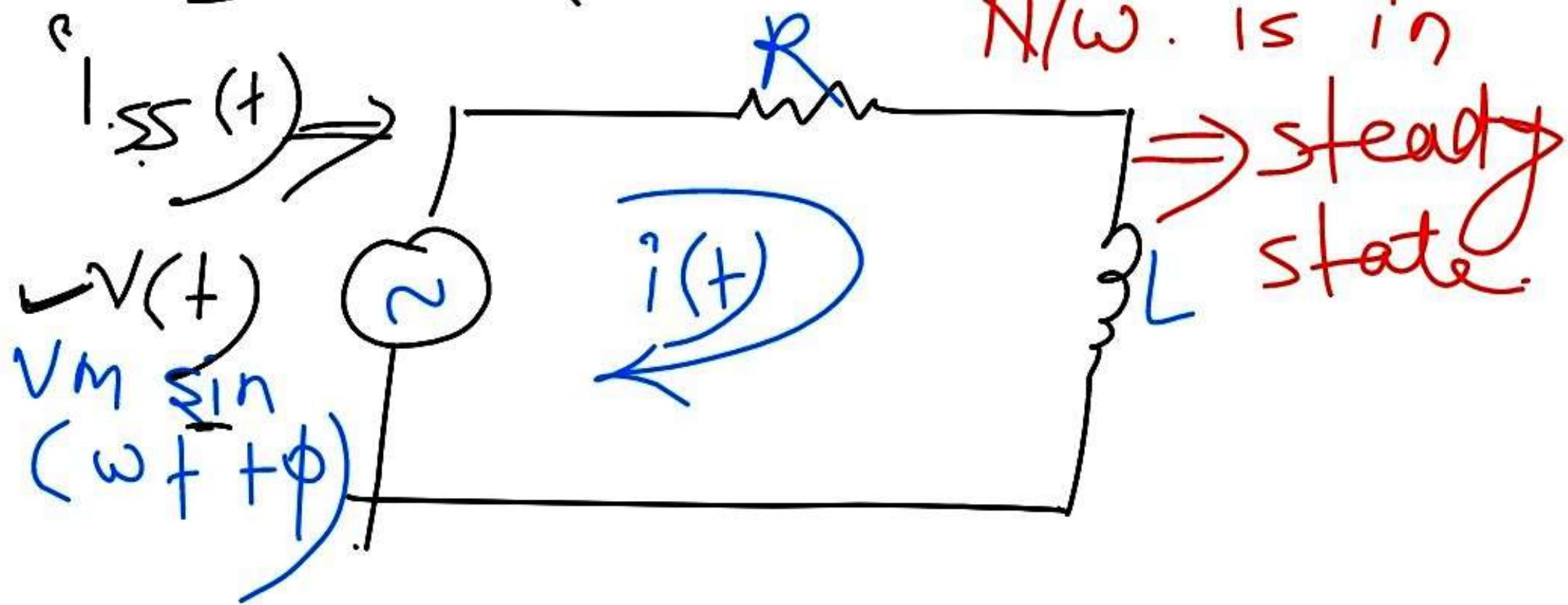

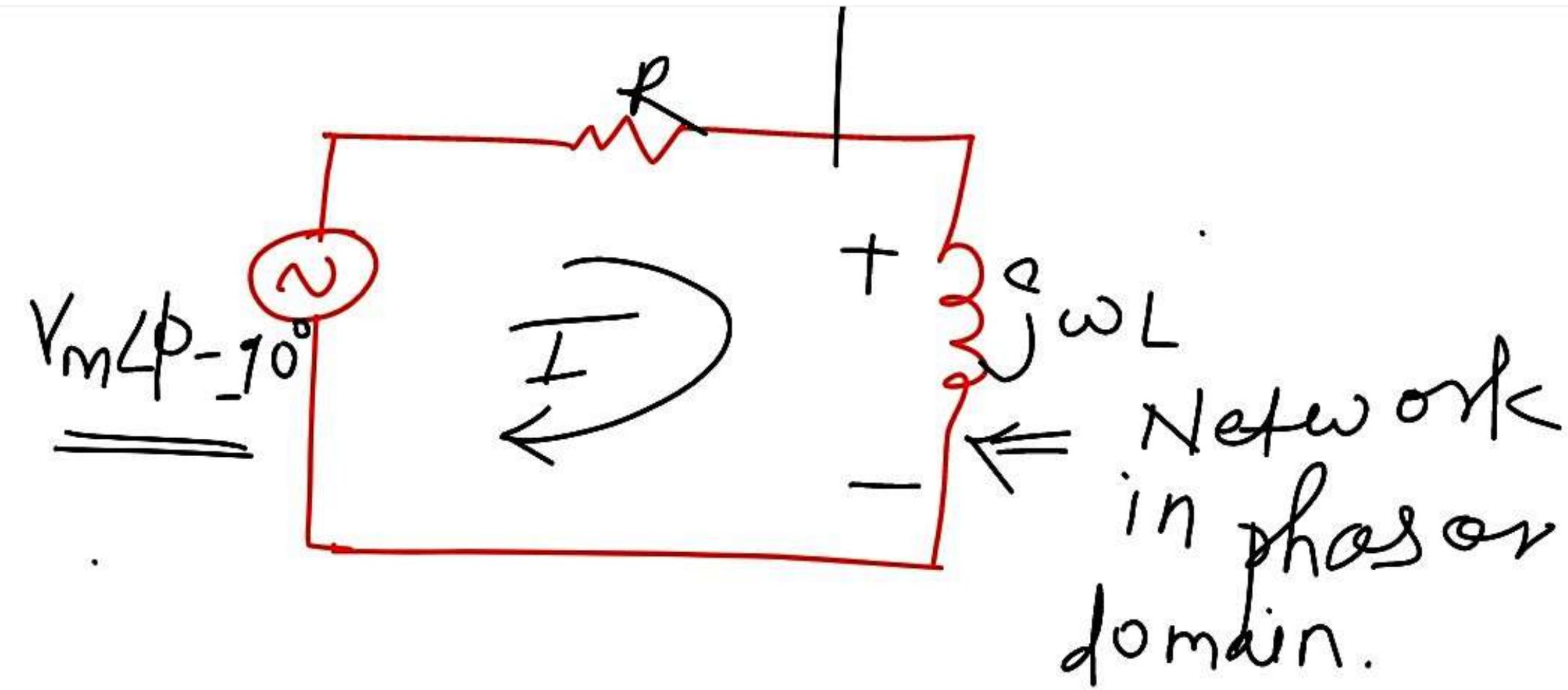

$$V(t) = V_m \cos(\omega t + \phi)$$

$$V = V_m e^{j\phi} \leftarrow \text{exponential.}$$

$$= V_m \angle \phi \leftarrow \text{Polar}$$

$$= V_m (\cos \phi + j \sin \phi)$$

Rectangular.

$$i(t) = I_m \cos(\omega t + \theta)$$


$$I \Rightarrow I_m e^{j\theta} \Rightarrow \text{polar.}$$

$$= I_m e^{j\theta} \Rightarrow \text{Exponential.}$$

$$= \overline{I_m} (\cos \theta + j \sin \theta) \Rightarrow \text{Rect.}$$

$$\begin{aligned}
 i(t) &= 10 \sin(2t + 30^\circ) \text{ Amp.} \\
 &= 10 \cos(2t + 30^\circ - 90^\circ) \text{ Amp} \\
 &= 10 \cos(2t - 60^\circ) \text{ Amp.}
 \end{aligned}$$
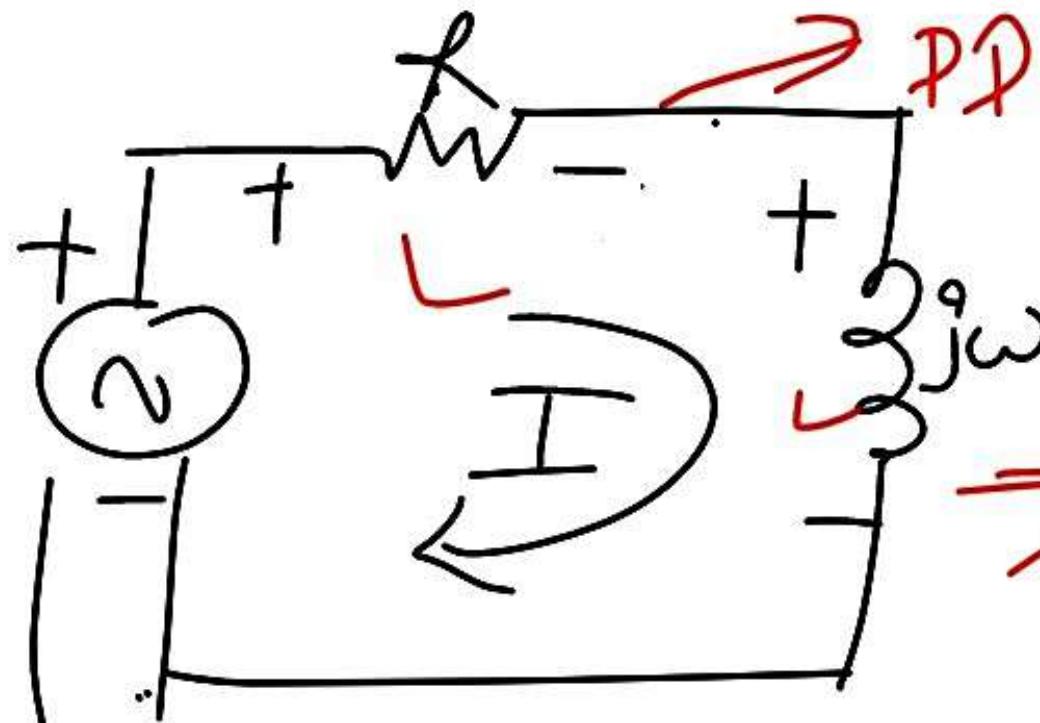
$$\begin{aligned}
 I &= 10 \angle -60^\circ \xrightarrow{\text{P}} 10(\cos 60^\circ - j \sin 60^\circ) \\
 &= 10 e^{-j 60^\circ} \xrightarrow{\text{E}} \text{Rect.}
 \end{aligned}$$



$$\underline{V_m \angle \phi - 90^\circ}$$

By KVL in PD.

$$V_m \angle \phi - 90^\circ - RI - j\omega LI = 0$$

By KVL

$$V_m \angle \phi - 90^\circ - RI - j\omega LI = 0$$

$$\begin{aligned} V_m \angle \phi - 90^\circ &= RI + j\omega LI \\ &= I(R + j\omega L) \end{aligned}$$

$$\therefore I = \frac{V_m \angle \phi - 90^\circ}{R + j\omega L} \Rightarrow$$

$$I = \frac{\sqrt{m} \angle \phi - 90^\circ}{\sqrt{R^2 + (\omega L)^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$I = \frac{\sqrt{m}}{\sqrt{R^2 + (\omega L)^2}} \angle \phi - \tan^{-1}\left(\frac{\omega L}{R}\right) - 90^\circ$$

$$= \alpha < \beta.$$

$$\alpha = \frac{\sqrt{m}}{\sqrt{R^2 + (\omega L)^2}}$$

$$\beta = \phi - \tan^{-1} \frac{\omega L}{R} - 90^\circ$$

$$q e^{j\beta}$$

$$\begin{aligned} i(\theta) &= R P \cdot [I \cdot e^{j\omega t}] \\ &= \alpha \cos(\omega t + \beta) \\ &= \alpha \cos\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} - 90^\circ\right) \end{aligned}$$

$$\begin{aligned}V(t) &= V_m \cos(\omega t + \phi), \\&= \text{Real part} [V_m e^{j(\omega t + \phi)}] \\&= \text{Real part} [\underline{V_m e^{j\phi}} \cdot e^{j\omega t}] \\&= \text{Real part} [\underline{\underline{V}} \cdot e^{j\omega t}]\end{aligned}$$

$$\frac{V_m}{\sqrt{R^2 + (\omega_L)^2}} \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$

Amp.

$$\Rightarrow i_{ss}(t)$$

$$t-D \leftrightarrow P \cdot D$$

$$i(t) \leftrightarrow I =$$

$$v(t) \leftrightarrow V$$

$$R \leftrightarrow R$$

$$L \leftrightarrow j\omega L \quad (\zeta = j\omega)$$

$$C \not\leftrightarrow \frac{1}{j\omega} C$$

$$V_t = V_m \sin(\omega t + \phi)$$

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \frac{1}{Z(s)} = \frac{1}{R + sL}$$

$s = j\omega$

$$H(j\omega) = \frac{1}{R + j\omega L}$$

Method ② By LTA.

$$V(+)= \underline{V_m \sin(\omega t + \phi)}$$

$$(s = j\omega)$$

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \underline{\frac{1}{Z(s)}} = \underline{\frac{1}{R+SL}}$$

$$Y = IR \Rightarrow \underline{\underline{\frac{Y}{I}}} = Z \quad \frac{Y(s)}{I(s)} = Z(s)$$

$$H(j\omega) = \underline{Y(j\omega)} = \frac{1}{Z(j\omega)} = \frac{1}{R + j\omega L}$$


$$V = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \angle -\tan^{-1} \frac{\omega L}{R}$$


$$I(s) = \underline{H(s)} \cdot \underline{Y(s)}$$


$$i(t) = \frac{I}{\sqrt{R^2 + (\omega L)^2}} I_m \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$


A hand-drawn diagram consisting of a horizontal line segment and a vertical line segment meeting at a right angle. The horizontal line has a small gap in the middle, through which a curved arrow points from left to right, representing the current $i_{ss}(t)$. To the right of this gap, the word "Amp." is written in red.

$$i(t) = i_{ss}(t)$$

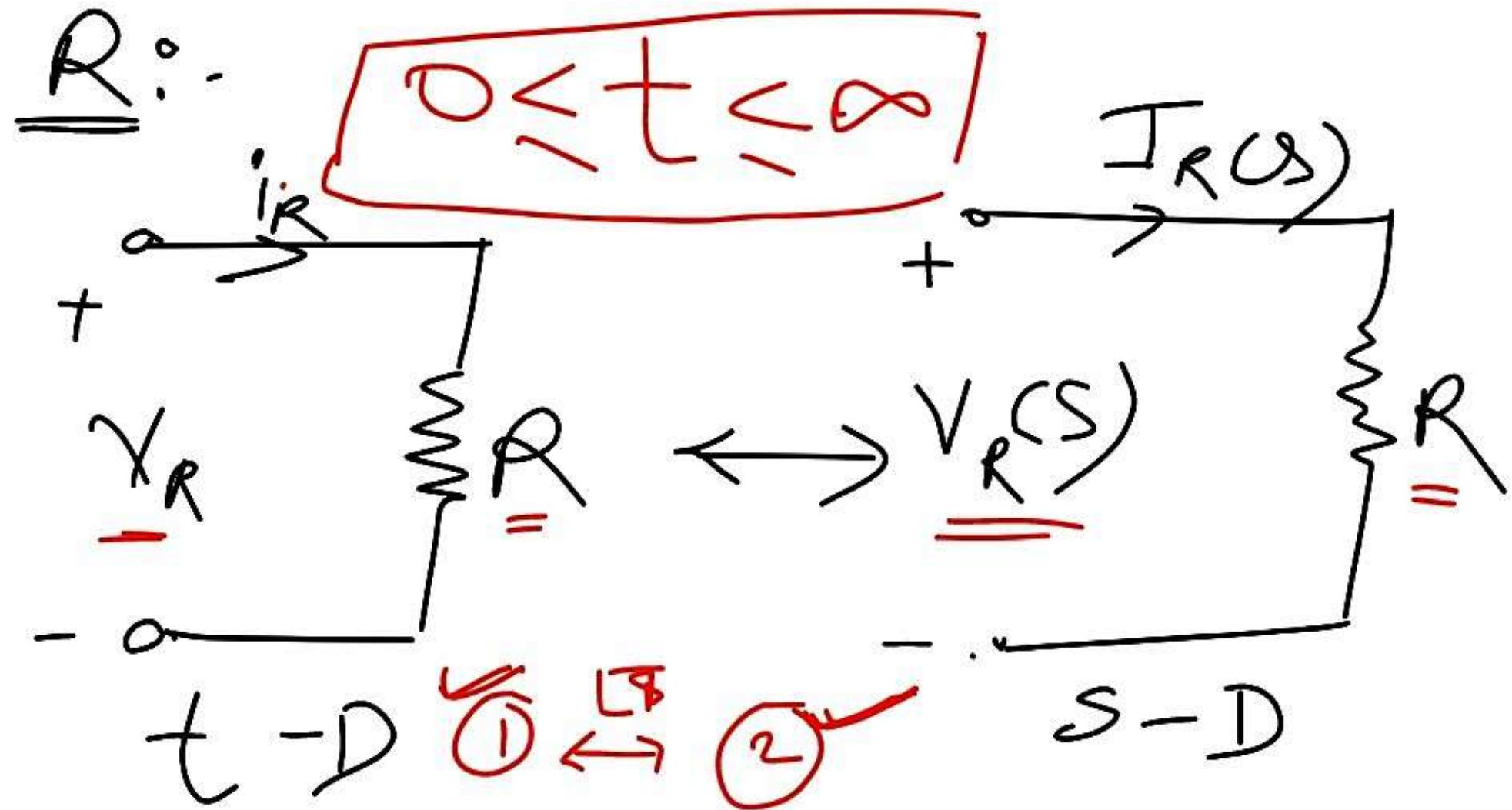

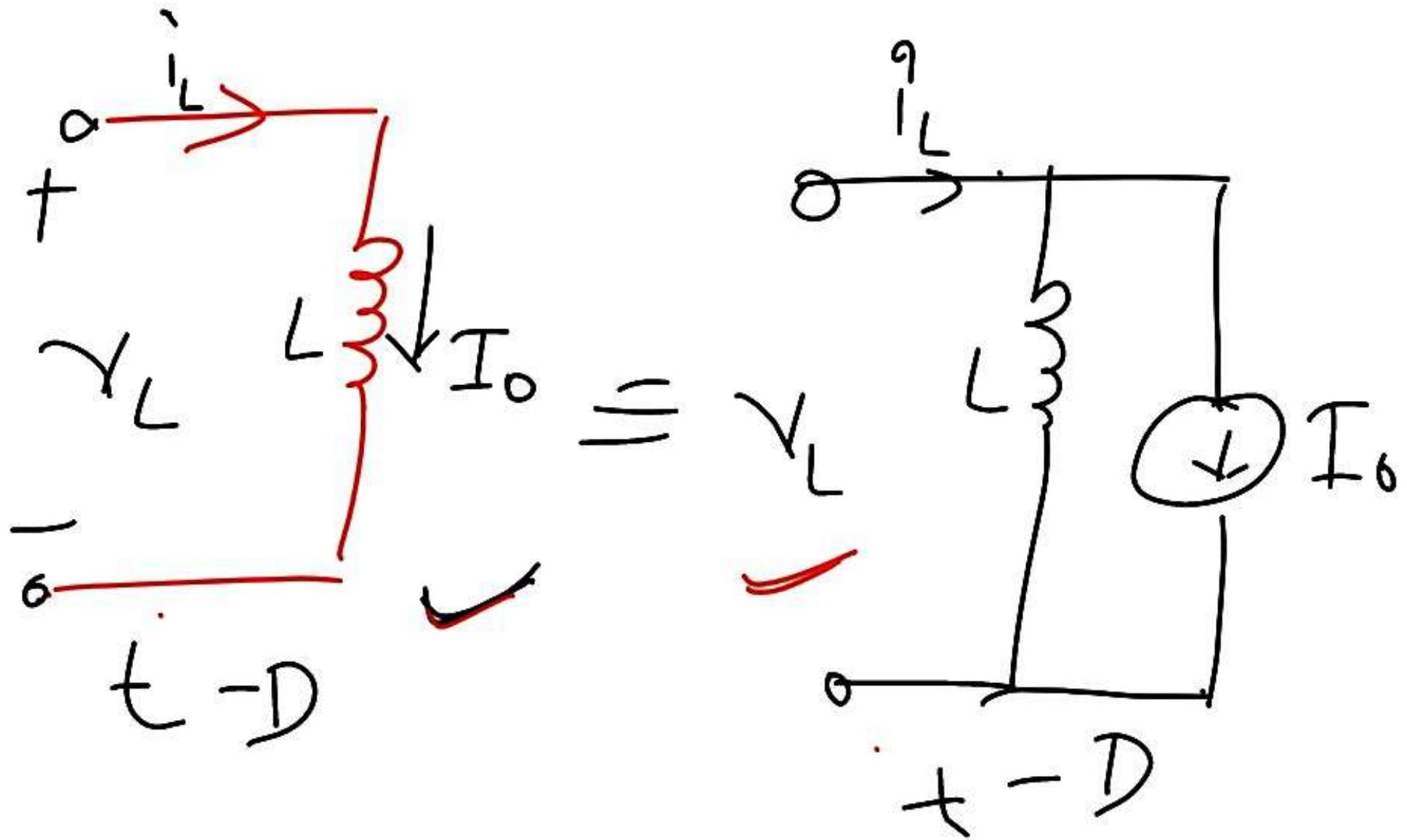

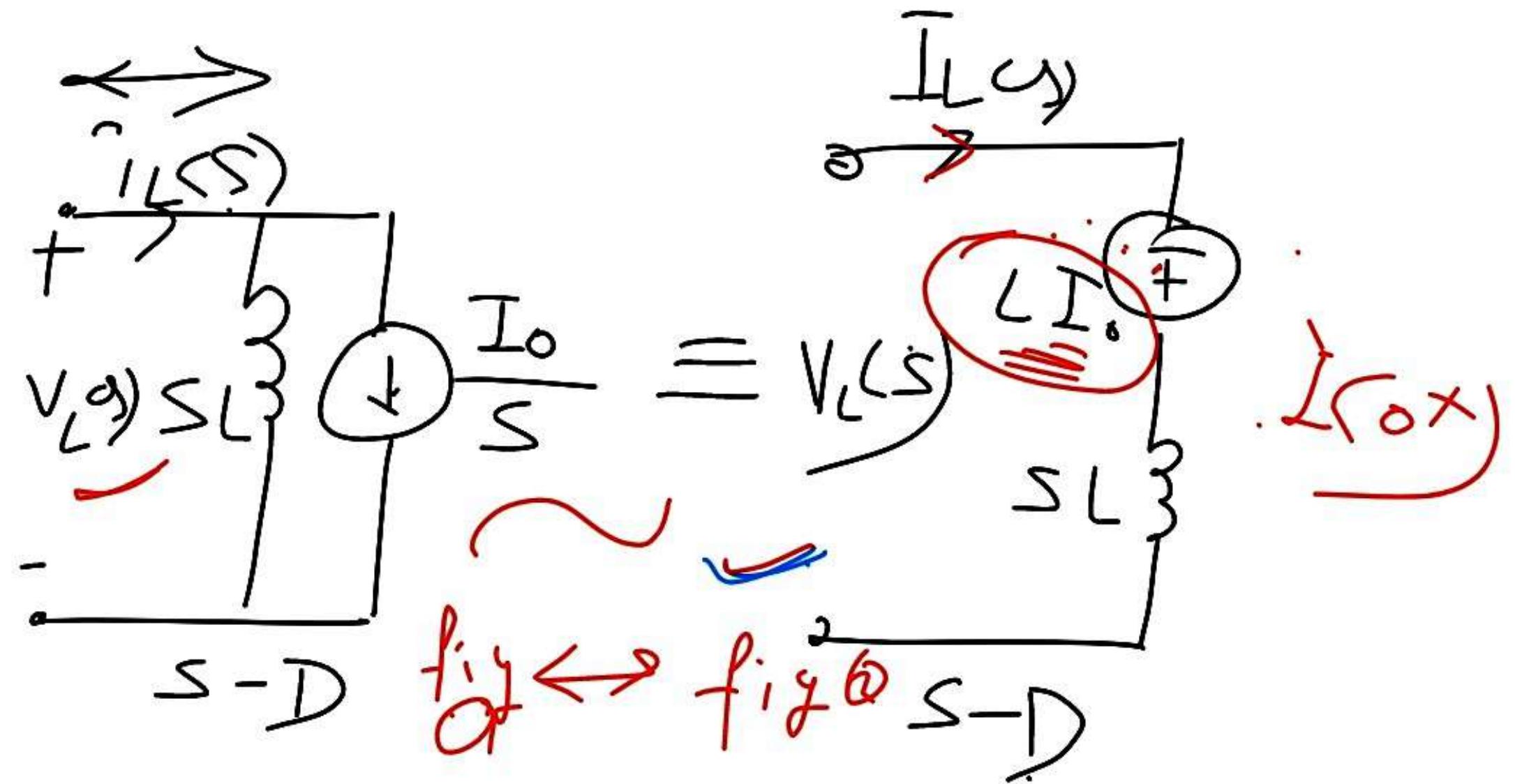

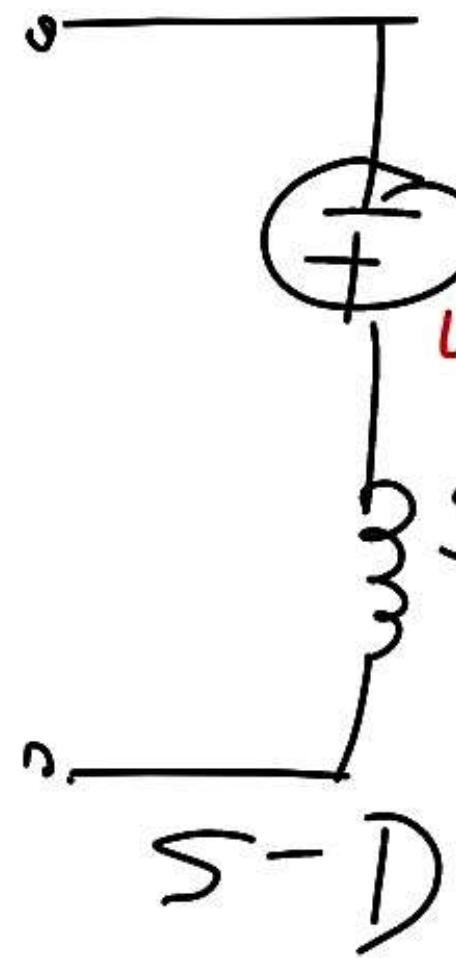


N/Cs. represents the
equivalent of
inductor in Laplace
domain determine
initial current through
it.


Since $L I_0 = 6$ volt.


$$L = \frac{V}{I}$$

$$\boxed{I_0 = 12 \text{ Amp.}}$$
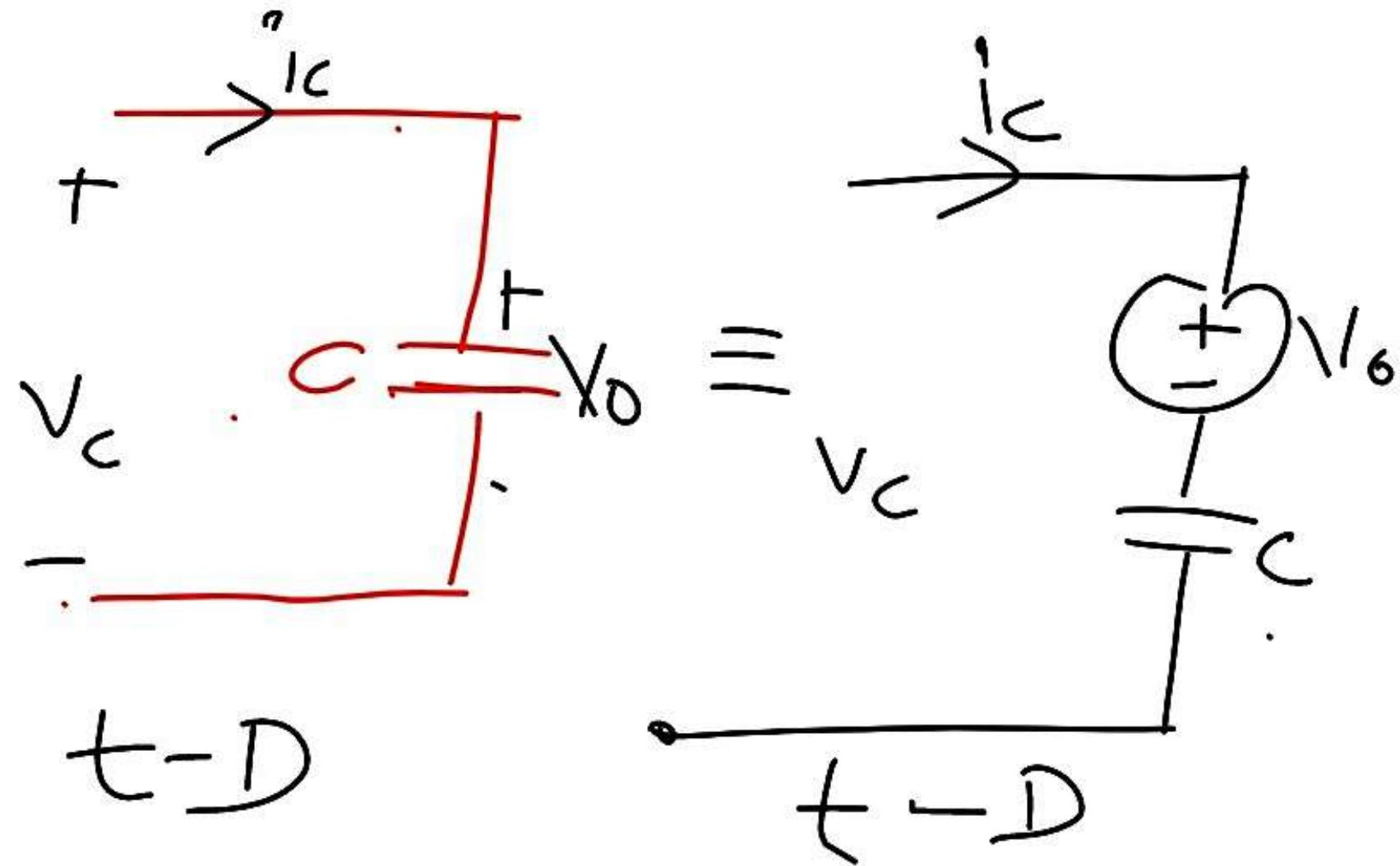
$$I_0 = \frac{6}{L} = \frac{6}{\frac{1}{2}} = 12 \text{ Amp.}$$




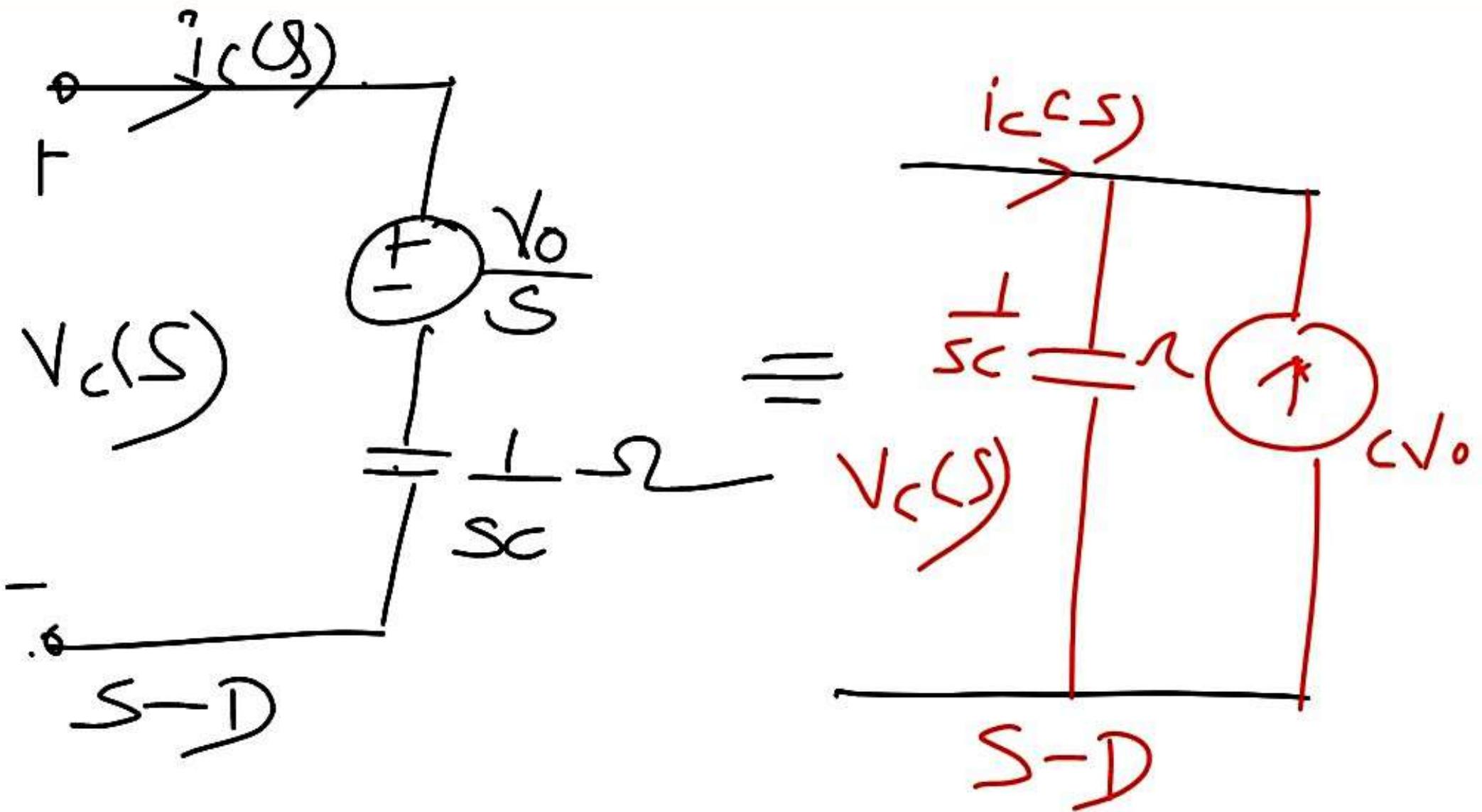

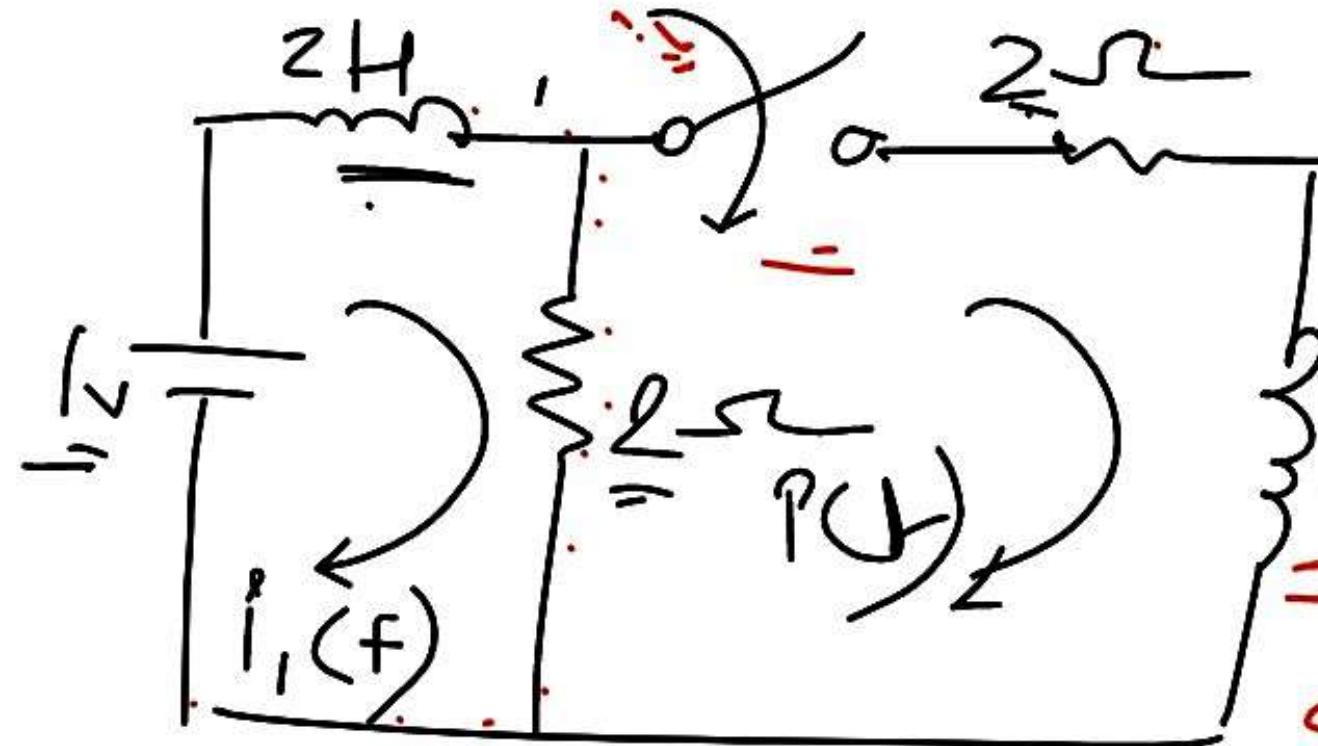

In the N/w
switch is
closed at
 $t=0$, the
ss being reached
before $t=0$. Determine current through
inductor 3H

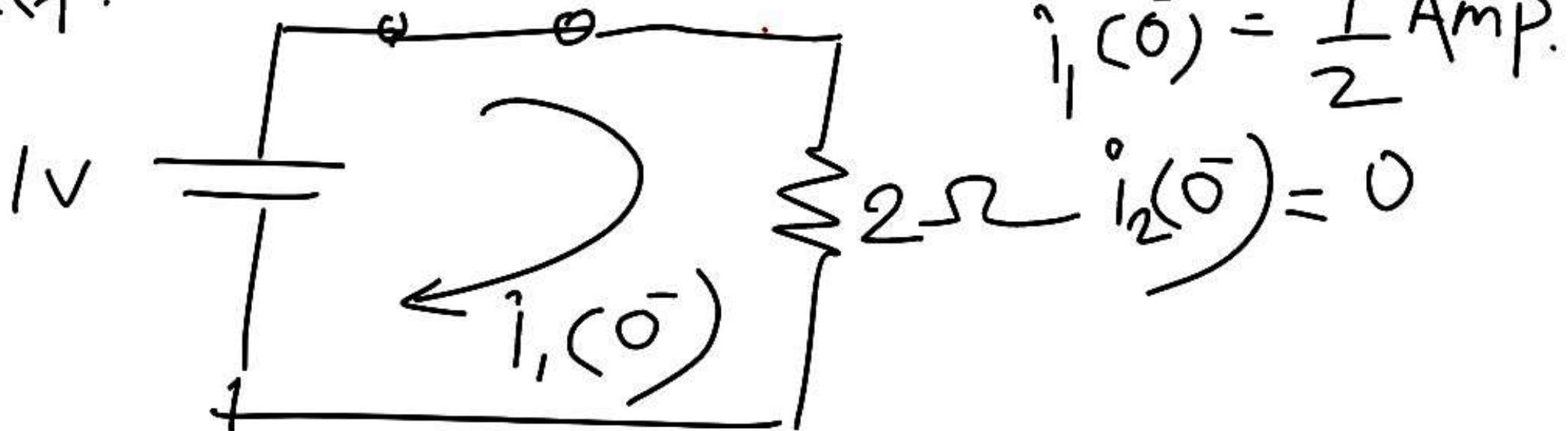At $t=0^-$, ss condition is reached
Hence, inductor of 2H will
act.




Since the current through
the inductor cannot change
instantaneously.

$$\underline{i_1(0^+)} = \frac{1}{2} \text{ Amp}$$

$$i_2(0^+) = 0 \text{ Amp}.$$

für $t > 0$

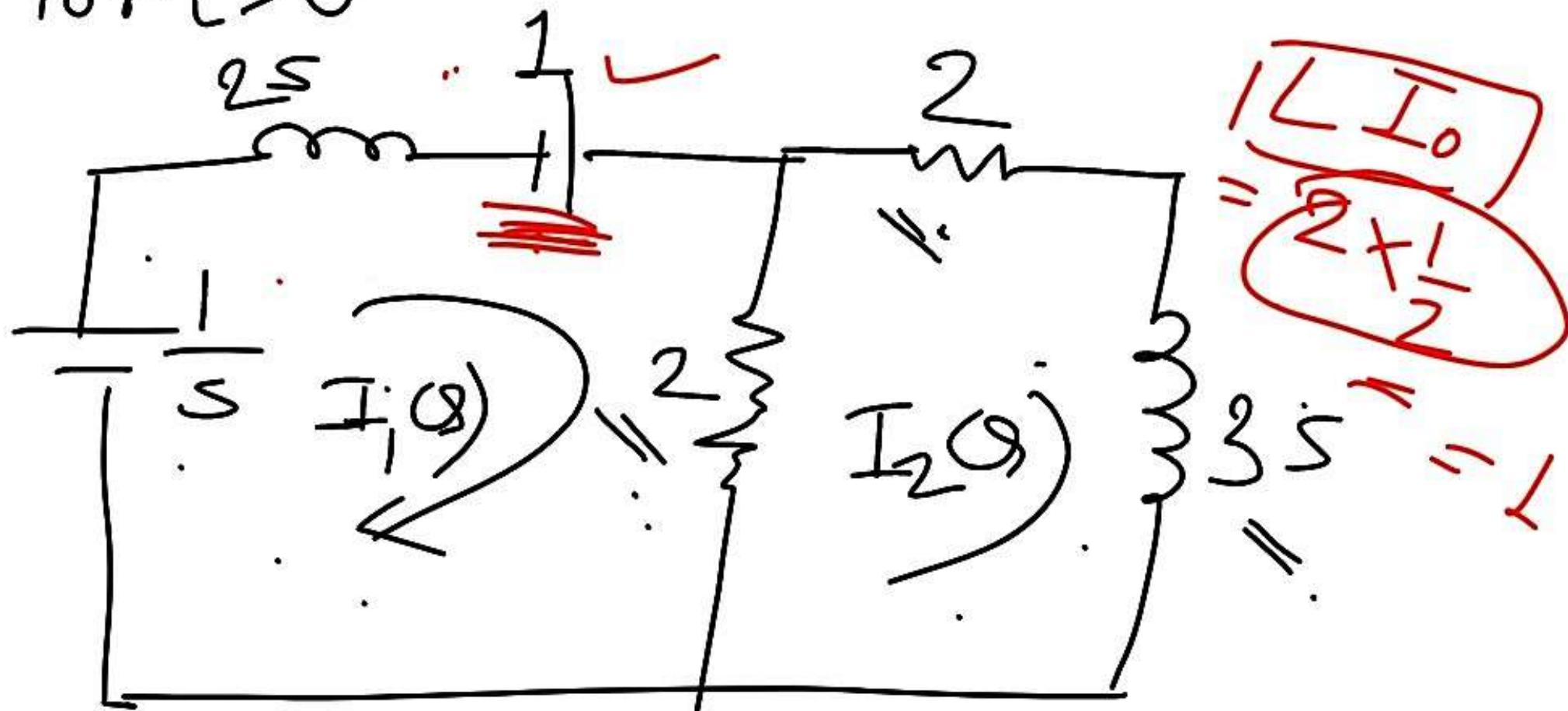

$$\frac{1}{S} - 2SI_1(S) + 1 - 2(I_1(S) - I_2(S)) =$$

$$\Rightarrow \underline{(2+2S)I_1(S)} - 2I_2(S) = 1 + \frac{1}{S}$$

(1)

Apply KVL to mesh ②

$$-2(I_2(s) - I_1(s)) - 2I_2(s) - 3sI_2(s) = 0$$
$$\Rightarrow -2I_1(s) + (4 + 3s)I_2(s) = 0 \quad \text{---} ②$$

Cramer's rule

$$ax + by = e$$

$$cx + dy = f$$

$$x = \frac{\begin{vmatrix} e & b \\ f & d \end{vmatrix}}{\begin{vmatrix} a & b \\ c & d \end{vmatrix}}$$

$$y = \frac{\begin{vmatrix} a & e \\ c & f \end{vmatrix}}{\begin{vmatrix} a & b \\ c & d \end{vmatrix}}$$

$$I_2(s) = \frac{\begin{vmatrix} 2+2s & 1+s \\ -2 & 0 \end{vmatrix}}{\begin{vmatrix} 2+2s & -2 \\ -2 & 4+3s \end{vmatrix}} \Rightarrow$$

By
Cramer's
rule.

$$\frac{2}{s}(s+1)$$

$$\frac{(2s+2)(4+3s)-4}{(2s+2)(4+3s)} \Rightarrow$$

$$\Rightarrow \frac{s+1}{s(2s^2+7s+2)} = \frac{s+1}{s \left(s + \frac{1}{3}\right)(s+2)}$$

$$= \frac{\frac{1}{3}(s+1)}{s(s+2)\left(s+\frac{1}{3}\right)}$$

By Partial fraction

$$I_2(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+\frac{1}{3}}$$

$$A = \frac{1}{3}(s+1) \\ \cdot \frac{(s+2)(s+\frac{1}{3})}{|_{s=0}}$$

$$A = \frac{1}{2}$$

$$\frac{B = \frac{1}{3}(s+1)}{s(s+\frac{1}{3})}$$

$$B = -\frac{1}{10}$$

$$c = \frac{1}{3}(s+1)$$

$$\frac{s(s+2)}{s} = -\frac{2}{5}$$


$$s = -\frac{1}{3}$$

$$I_2(s) = \frac{1}{2s} - \frac{1}{10(s+2)} - \frac{2}{5(s+\frac{1}{3})}$$

Taking Inverse Laplace T.

$$i_2(t) = \frac{1}{2} - \frac{1}{10} e^{-2t} - \frac{2}{5} e^{-(\frac{1}{3})t}$$

for $t > 0$

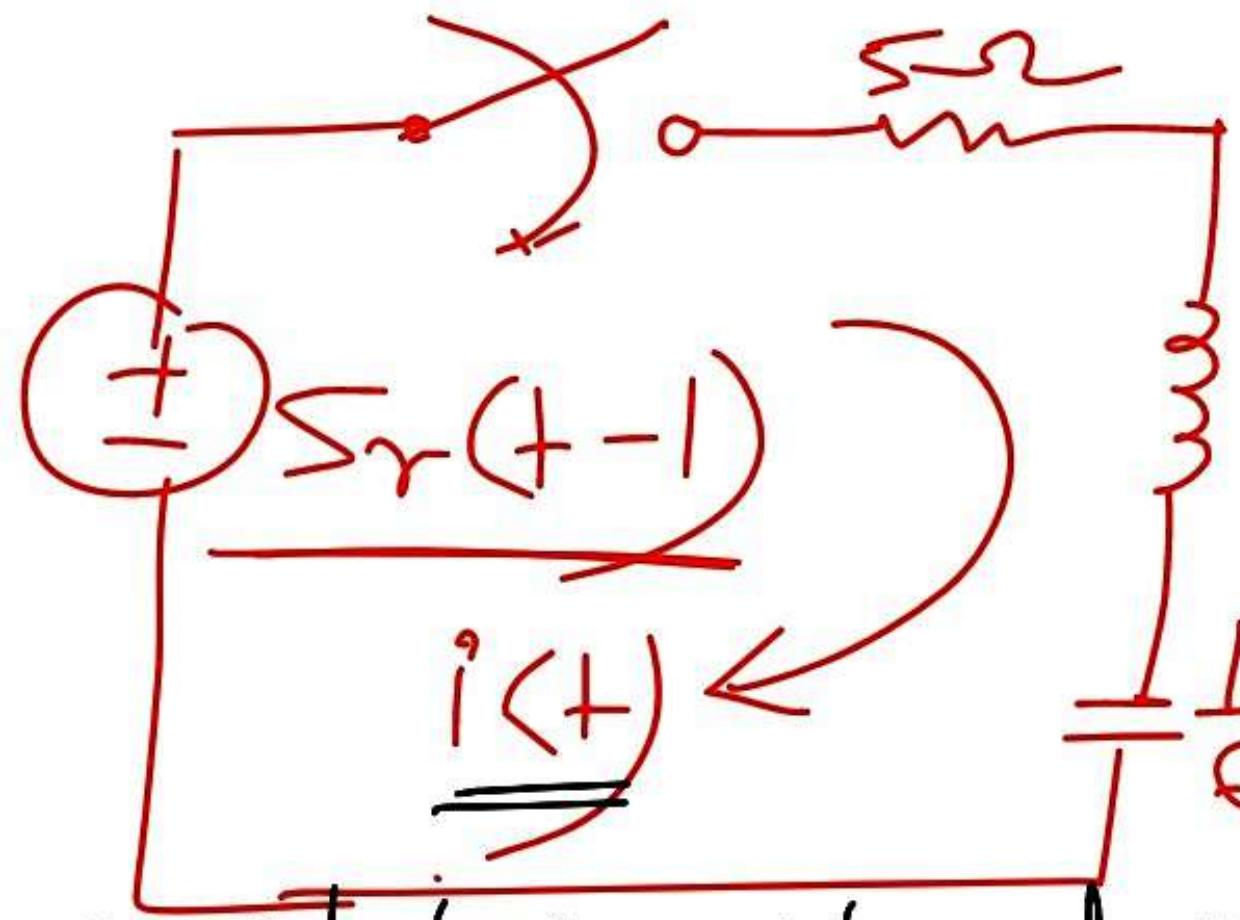


switch is closed at $t = 0$ o initial condition.

In N/C.

Determine
= the current
 $i(t)$ when
the with
initial
condition.

Transformed \mathcal{N}/ω .

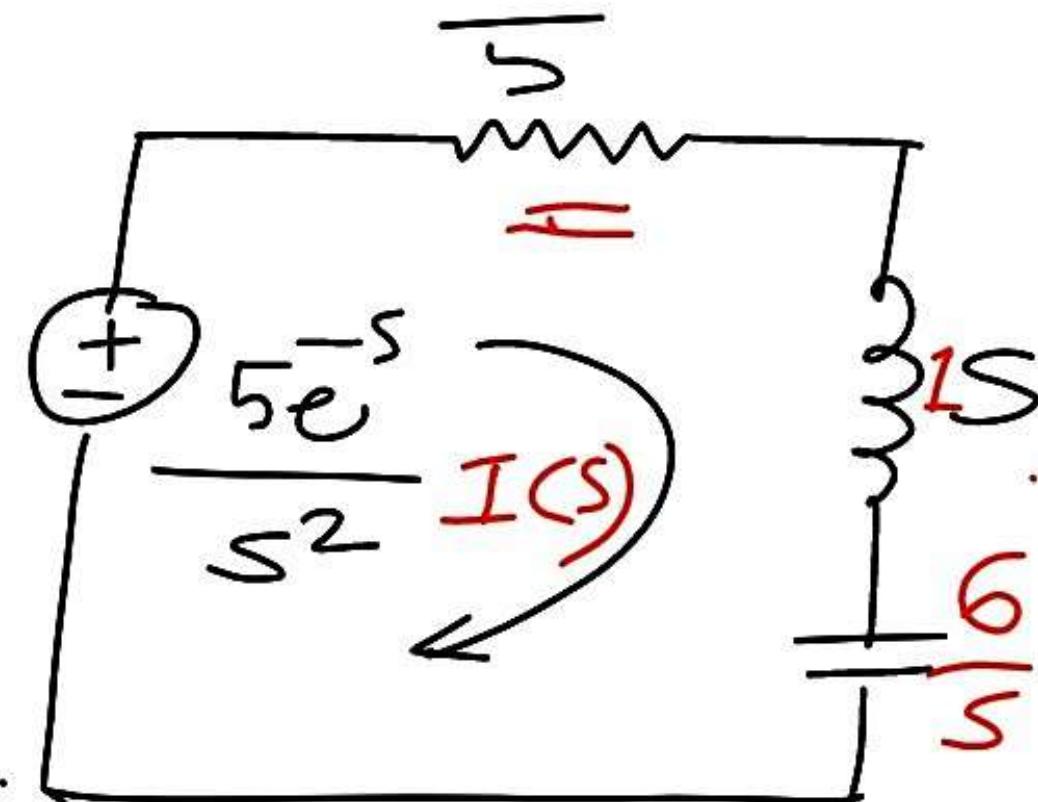

$$\begin{aligned} \overline{\underline{5e^{(-s)}}} &\xrightleftharpoons{LT} \underline{5e^{-s}} \\ \underline{\underline{\omega}} & \xrightleftharpoons{LT} \underline{\underline{\frac{1}{s^2}}} \\ \underline{\underline{\omega}} & \xrightleftharpoons{LT} \underline{\underline{\frac{1}{s^2}}} \end{aligned}$$

→ Apply KVL to mesh for $t > 0$

$$\frac{5e^{-s}}{s^2} = 5I(0) + sI(s) + \frac{6}{s} I(s)$$

$$I(s) = \frac{5e^{-s}}{s(s^2+5s+6)} = \frac{5e^{-s}}{s(s+3)(s+2)}$$

By Partial fraction expansion

$$\frac{1}{s(s+3)(s+2)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+2}$$

By solving

$$A = \frac{1}{(s+3)(s+2)} \Big|_{s=0} = \frac{1}{6}$$

$$B = \frac{1}{s(s+2)} \Big|_{s=-3} = \frac{1}{3}$$

$$C = \frac{1}{s(s+3)} \Big|_{s=-2} = -\frac{1}{2}$$

$$I(s) = 5 \bar{e}^{-s} \left[\frac{1}{6s} + \frac{1}{3(s+3)} - \frac{1}{2(s+2)} \right]$$

$$\frac{5e^{-s}}{s} + \frac{5e^{-s}}{s+3} - \frac{5e^{-s}}{s+2}$$

Taking inverse LT

$$\underline{i(t)} = \frac{5}{6} u(t-1) + \frac{5}{3} e^{-3(t-1)} u(t-1) \\ - \frac{5}{2} e^{-2(t-1)} u(t-1) \quad \text{for } t > 0$$

$$u(t) = \frac{1}{s}$$
$$r(t) = \frac{1}{s^2}$$

$$\delta(t) = 1$$
$$p(t) = \frac{1}{s^3}$$

$$s \xrightarrow{\text{ILT}} t$$

Phasor Representation:

- A phasor is a complex No. that represents amplitude & phase of a sinusoid. It is defined only for the sinusoidal signals.



⇒ All sinusoidal signals
are converted into
cosinoids by subtracting
 90° from phase

- ⇒ A phasor may be expressed in exponential form, polar form, rectangular form.
- ⇒ phasor has magnitude & direction. it behaves as vector

$$\underline{V(t)} = V_m \cos(\omega t + \phi)$$

$$= \text{Real part} [V_m e^{j(\omega t + \phi)}]$$

$$= \text{Real part} [V_m \cdot e^{j\omega t} \cdot e^{j\phi}]$$

$$= \text{Real part} [V e^{j\omega t}]$$

$V = V_m e^{j\phi}$ \Rightarrow Exponential form
of phasor representation

$= V_m \angle \phi$ \Rightarrow Polar form of
the phasor
representation.

$$V_m(\cos\phi + j\sin\phi) \Rightarrow$$

Rectangular form of
phasor representation.

Note :- The add. or. sub. of two phasors are generally carried out only in rectangular form. whereas a division multiplication of phasors are carried out either in polar or exponential form.

$$i(t) = I_m \cos(\omega t + \theta)$$

$$I = I_m \angle \theta \Rightarrow \text{polar}$$

$$= I_m e^{j\theta} \Rightarrow \text{exp.}$$

$$= I_m (\cos \theta + j \sin \theta) \Rightarrow \text{Rect.}$$

$$\underline{V(+)} = \underline{10} \cos(2t + 30^\circ) \text{ volt.}$$

$$V = \underline{10} \angle 30^\circ \rightarrow \text{polar.}$$

$$= 10 e^{j30^\circ} \Rightarrow \text{expo.}$$

$$= 10 (\cos 30^\circ + j \sin 30^\circ) \Rightarrow$$

$$= 10 \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) \xrightarrow{\text{Rect. Phasor}} R.$$

$$\begin{aligned} i(t) &= 10 \sin(2t + 30^\circ) \text{ Amp.} \\ \Rightarrow i(t) &= 10 \cos(2t + 30^\circ - 90^\circ) \text{ Amp.} \\ \Rightarrow i(t) &= 10 \cos(2t - 60^\circ) \\ I &= 10 \angle -60^\circ \text{ polar.} \\ &= 10 e^{-j60^\circ} \text{ exp.} \end{aligned}$$

$$10(\cos 60^\circ - j \sin 60^\circ)$$

$$= 10\left(\frac{1}{2} - j \frac{\sqrt{3}}{2}\right)$$

\rightarrow phasor representation

$\checkmark V(t) = 10 \sin(2t + 30^\circ)$ volt.

$= 10 \cos(2t + 30^\circ - 90^\circ)$

$$V = 10 \angle 85^\circ (2t - 60^\circ)$$

$$V = 10 \angle -60^\circ \xrightarrow{\text{polar}}$$

$$= 10 e^{-j60^\circ} \Rightarrow \text{expo.}$$

$$V = 10 (\cos 60^\circ - j \sin 60^\circ) \xrightarrow{\text{Rect.}}$$

$$= 10 \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right) \Rightarrow \begin{matrix} \text{phasor} \\ \text{representation} \end{matrix}$$

$$\frac{V}{I} = Z$$

$$\frac{I}{V} = Y$$

$$V = ZI$$


$$I = \frac{V}{Z}$$

$$Y = \frac{1}{Z}$$

$$I = VY$$

$$V = \frac{I}{Y}$$

$$R = \frac{V}{I} = Y$$

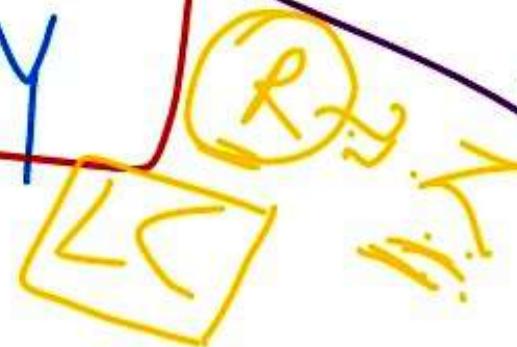

Ohm
mho

$$t - D \longleftrightarrow P \cdot D$$

$$i(+)\longleftrightarrow I$$

$$\sqrt{C(+)}\longleftrightarrow V$$

$$R \longleftrightarrow R \Omega$$


$$L \longleftrightarrow j\omega L \Omega \quad (\text{where } j\omega = s)$$
$$= \frac{1}{j\omega_C} \Omega$$

Note:-

Analysis of AC in steady state
is generally carried out in
phasor domain i.e. KCL, KVL,
Ohm's Law, Nodal mesh, ST,
are written only in phasor
domain.

AC Transients

① Series RL ckt.

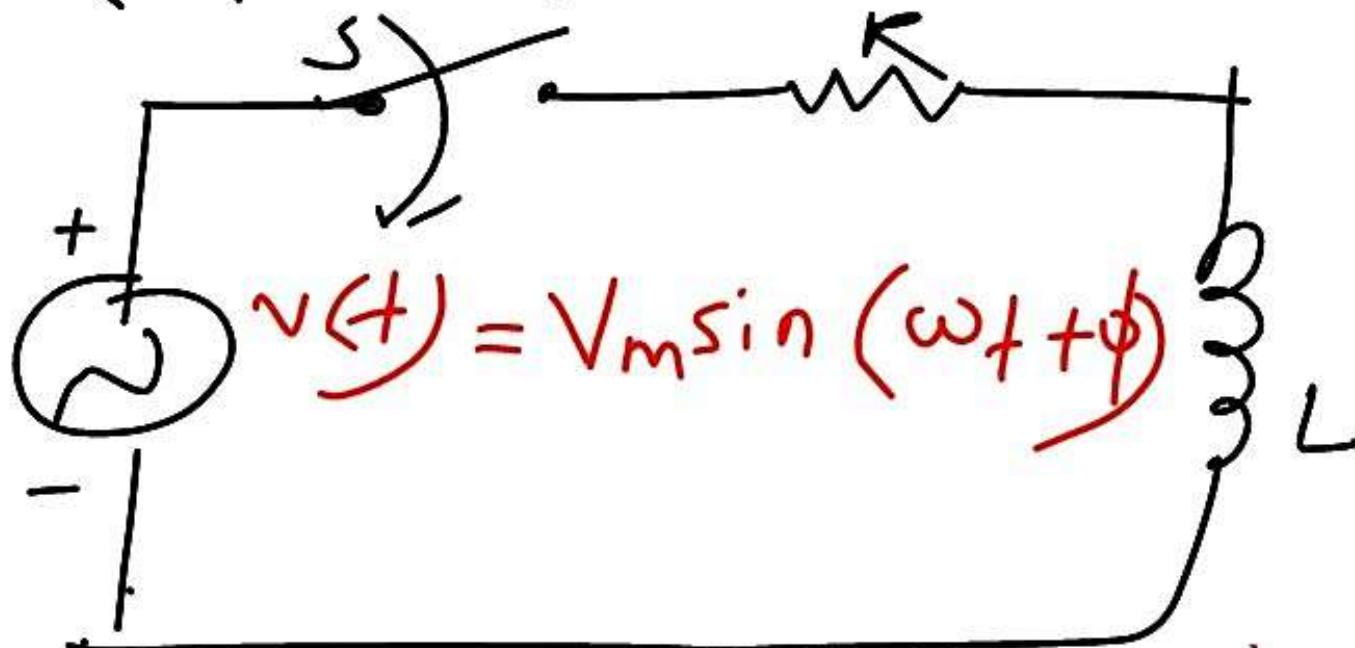

Complex situation
= Complex function +
Particular Integration.

CS = CF + PI
= Natural + Forced
Response. Response


Phasors


→ phasor is a complex number that represent amplitude & phase of sinusoid.

$$V(t) = V_m \cos(\omega t + \phi)$$

AC transients :-

1) Series RL circuit :-

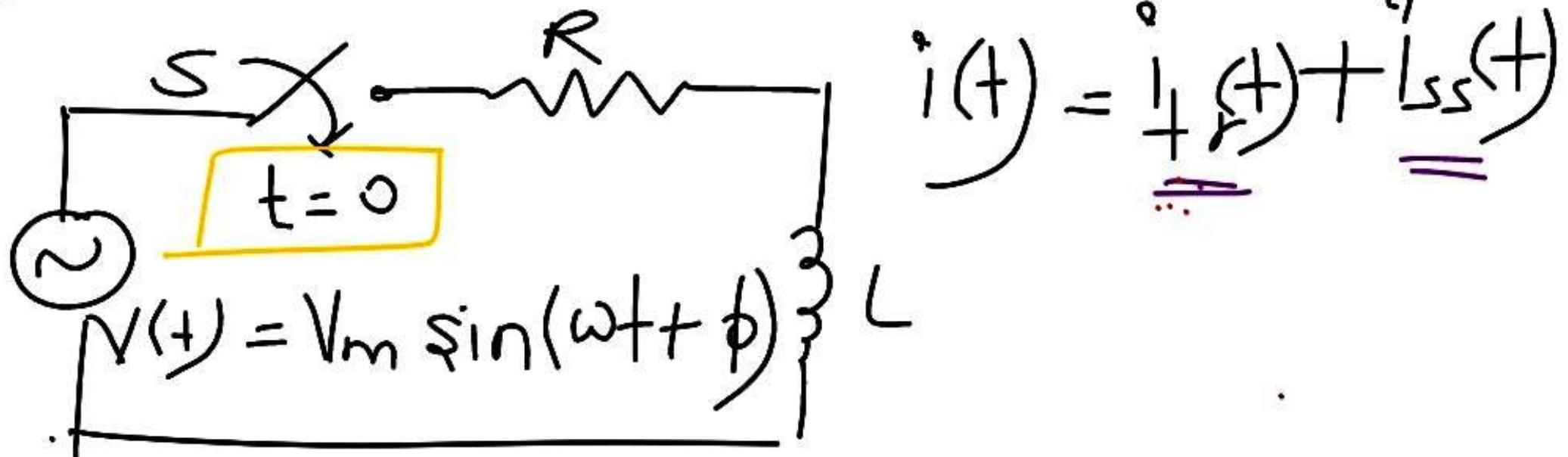


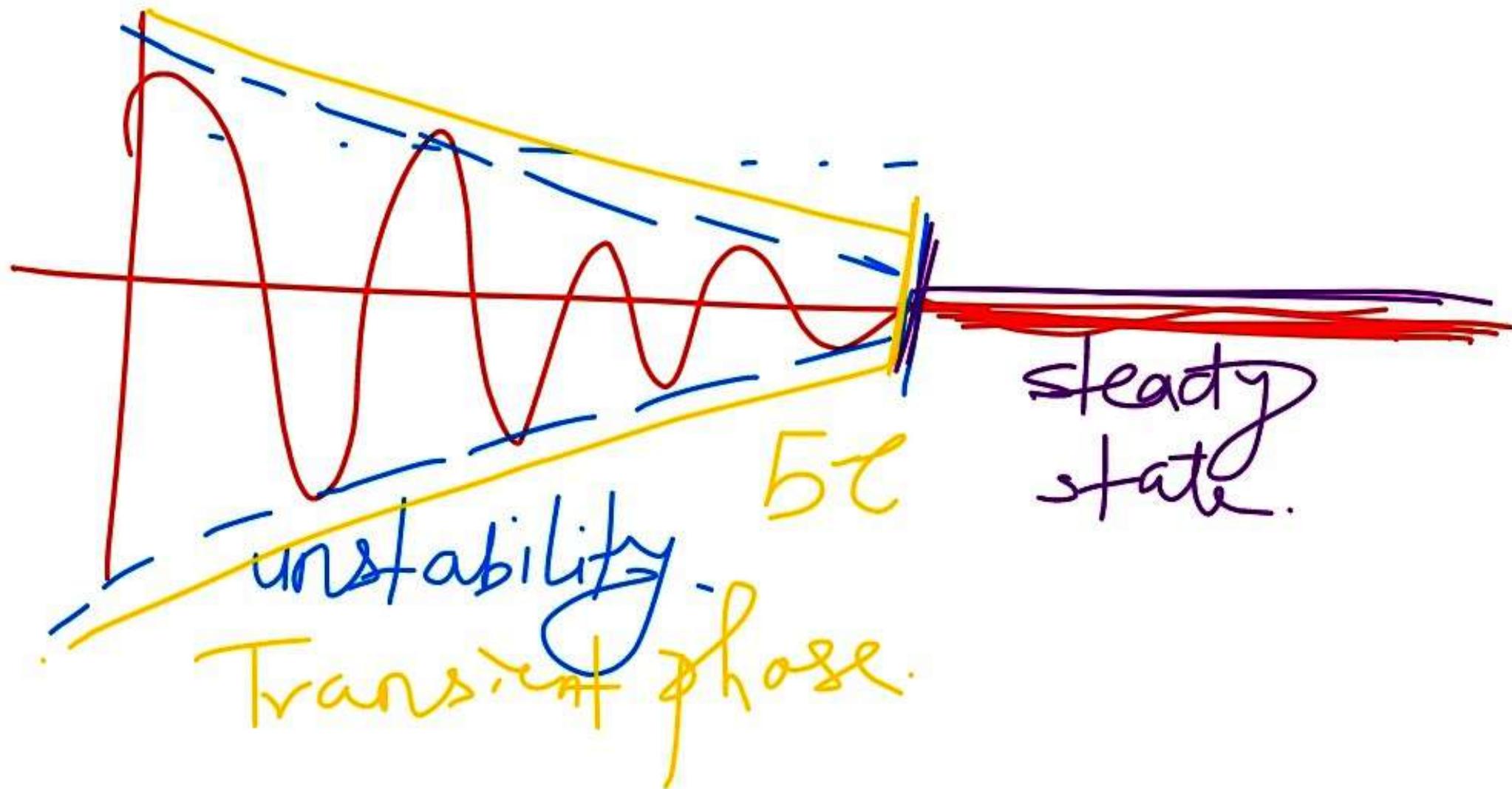

$$i(t) = i_{tr}(t) + i_{ss}(t)$$

$$\downarrow$$
$$i_{tr}(t) = k e^{-t/\tau}$$

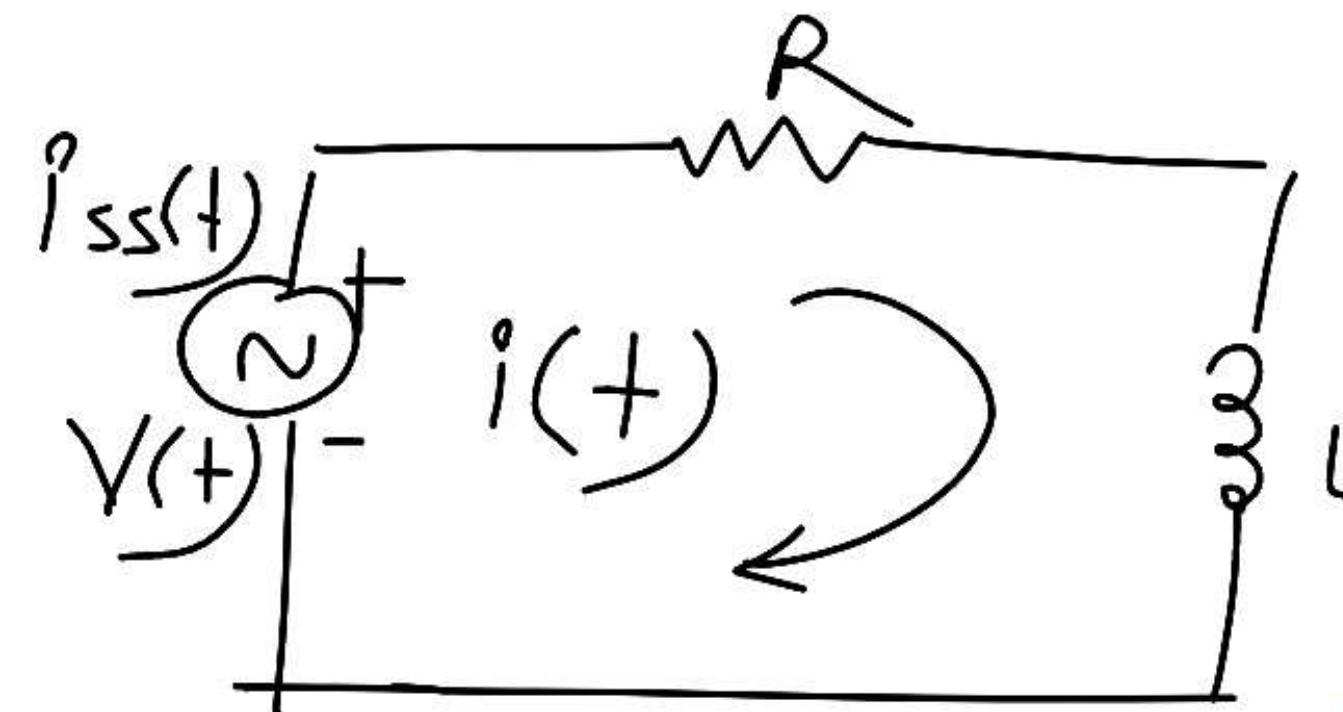
$$= k - \frac{R}{L} t$$
$$\boxed{i_{ss}(t) = ?}$$



$\frac{N}{\omega} \cdot i_{in}$
steady state

$$V(+) = V_m \sin(\omega t + \phi)$$

By phasor Approach

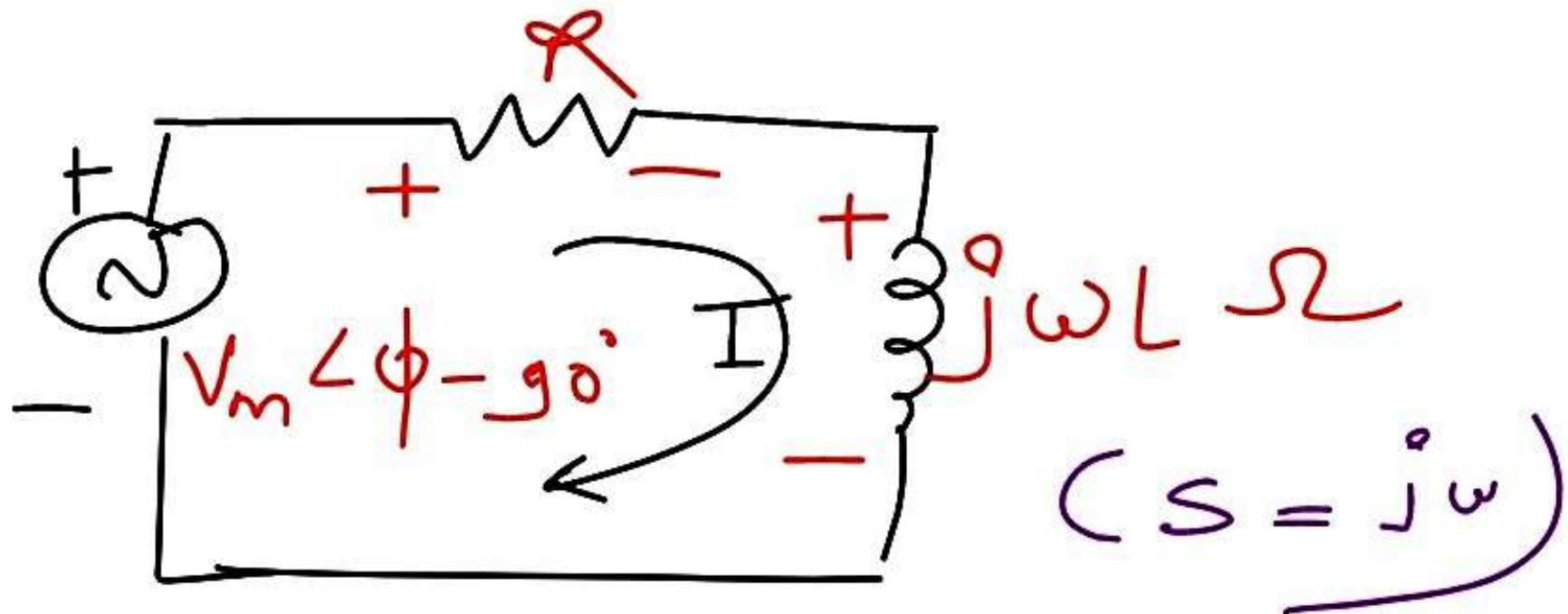

By KVL in P-D

$$V_m \angle \phi - 90^\circ - RI - j\omega L I = 0$$

$$V_m \angle \phi - 90^\circ = RI + j\omega L I = 0 \\ = I(R + j\omega L)$$

$$I = \frac{V_m \angle \phi - 90^\circ}{R + j\omega L}$$

$$I = \frac{V_m L \phi - 90^\circ}{\sqrt{R^2 + (\omega L)^2}} \angle -\tan^{-1} \frac{\omega L}{R}$$

$$I = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \angle \phi - \tan^{-1} \frac{\omega L}{R} - 90^\circ$$

$\alpha < \beta \Rightarrow \alpha e^{j\beta}$.

$$i(t) = \text{Real part} [I e^{j\omega t}] \text{ Amp.}$$

$$= \alpha \cos(\omega t + \beta)$$

$$= \alpha \cos\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} - \gamma_0\right)$$

$$= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t + \phi - \tan^{-1} \frac{\omega L - \gamma_0}{R}\right)$$

$$\frac{\frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin \left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} \right)}{Amp.} = P_{ss}(t)$$

$$t \rightarrow D \xrightarrow{\quad} D - D$$

$$i(t) \rightarrow I$$

$$\vee(t) \rightarrow \vee$$

$$\neg R \leftrightarrow R$$

$$c \leftrightarrow \frac{1}{j\omega_c}$$

Method (2) By LTA

$$V(t) = V_m \sin(\omega t + \phi)$$

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \frac{1}{Z(s)} = \frac{1}{R + sL}$$

$$s \rightarrow j\omega$$

$$H(j\omega) = \frac{1}{R + j\omega L}$$

$$\frac{1}{\sqrt{R^2 + (\omega L)^2}} e^{-j \tan^{-1} \frac{\omega L}{R}}$$

$$I(s) = H(s) \cdot V(s)$$

$$i(t) = \frac{1}{\sqrt{R^2 + (\omega L)^2}} V_m \sin \left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} \right)$$

$I_{ss}(t)$

$$I(+)=i_{tr}(+) + i_{ss}(+)$$

$$= L e^{-R_L t} + \frac{V_m}{\sqrt{R^2 + (\omega_L)^2}} \sin(\omega_L t + \phi - \tan^{-1} \frac{\omega L}{R})$$

$$i(0^-) = i(0^+) \Rightarrow \underline{OA}$$

$$t=0$$

$$\theta = \dot{\theta}_0 + \frac{\sqrt{m}}{\sqrt{R^2 + (\omega L)^2}} \sin\left(\phi + \theta_0 - \tan^{-1}\frac{\omega L}{R}\right)$$

$$K = \frac{-\sqrt{m}}{\sqrt{R^2 + (\omega L)^2}} \sin\left(\phi - \tan^{-1}\frac{\omega L}{R}\right)$$

0

As. $k < 0 \Rightarrow k \ll 1$,

Transient effects are less
severe for A.C.

Suppose $\phi - \tan^{-1} \frac{\omega L}{R} = 0$

$$K = 0$$

$$i_r(t) = 0 \Rightarrow i(t) = i_{ss}(t)$$

i.e. A transient free response

ζ_0 , condition for transient free response at $t=0$

$$\phi - \tan^{-1} \frac{\omega L}{R} = 0 \quad | \begin{array}{l} (\omega t + \phi) \\ + = 0 \end{array}$$
$$\therefore \boxed{\phi = \tan^{-1} \frac{\omega L}{R}} \Rightarrow = \frac{\tan^{-1} \omega L}{L}$$


Note: If the total phase of excitation at the time of switching is equal to $\tan^{-1} \left(\frac{\omega L}{R} \right)$ then no transient will result at the time of switching for sinusoidal excitation.

⇒ If the switch is closed at $t = t_0$, then condition for transient-free response at $t = t_0 \Rightarrow$

$$\boxed{\omega t + \phi = \tan^{-1} \frac{\omega L}{R}}$$

AC Transient :-

Parallel RL circuit :-

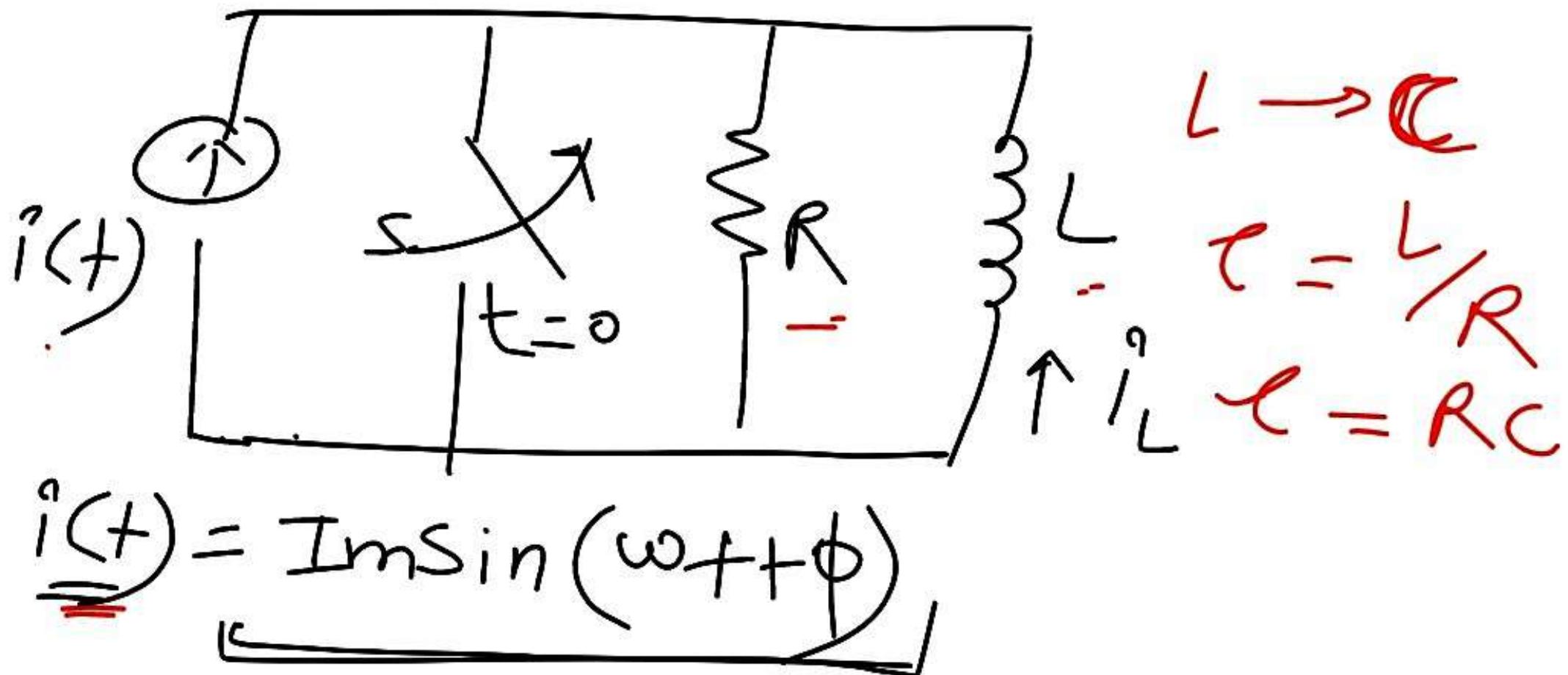

$i_{Lss}(t)$ by LTA

$$\frac{\underline{I}_{L(s)}}{\underline{I}(s)} = H(s) = \left(\frac{\text{Desired LT}}{\text{Excitation LT}} \right)$$

$$I_L(s) = \frac{I(s) \cdot R}{R + sL}$$

(By current division in S Domain)

$$\frac{I_L(s)}{I(s)} = \frac{R}{R + sL}$$

Tf. H(s)

$$H(s) = \frac{R}{R+SL}$$

$$H(j\omega) = \frac{R}{R+j\omega L} \Rightarrow \frac{1}{1+\frac{j\omega L}{R}}$$

$$\Rightarrow \sqrt{\frac{1}{1+\left(\frac{\omega L}{R}\right)^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$i_L(t) = \underbrace{i_{Lr}(t)}_{\text{initial}} + i_{Lss}(t)$$

$$= K e^{-Rt} + \frac{Im}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \sin(\omega t - \tan^{-1} \frac{\omega L}{R})$$

t=0

$$i_L(\omega^-) = i_L(\omega^+) = 0 \quad t=0$$

$$K = \frac{-Im}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \sin\left(\phi - \tan^{-1} \frac{\omega L}{R}\right)$$

$\nwarrow \quad \nwarrow 1$

Suppose $\phi - \tan^{-1} \frac{\omega L}{R} = 0$

$K = 0 \Rightarrow i_{tr}(t) = 0$

$$i_L(t) = i_{Lss}(t)$$

\Rightarrow Transient free response

$$\phi - \tan^{-1} \left(\frac{\omega L}{R} \right) = 0$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) \quad \text{at } t = 0$$

$$\omega t_0 + \phi = \tan^{-1} \frac{\omega L}{R} \quad \text{at } t = t_0$$

If $i(t) = \underline{I_m} \cos(\omega t + \phi)$ then

$$\phi = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2} \quad \text{at } t = 0$$

$$\omega t_0 + \phi = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2}$$

at $t = t_0$

Note:- Transient free condition
is not possible for network
with both the energy
storing elements ie RLC.
Network.

$$i(t) = i_{tr}(t) + i_{ss}(t)$$

$$S_1 S_2 = \alpha + j\beta$$

$$i_L(0^+)$$

$$V_L(0^+)$$

$K_1 \neq K_2 \Rightarrow$

$$D \cdot e^{\alpha t} \left(\overset{<}{K_1} \cos \beta t + \overset{>}{K_2} \sin \beta t \right) + i_{ss}(t)$$

Obs \rightarrow Transfer free ($\pm \omega$ value)
in R_L & R_C ckt with AC excitation
will depend on the source freq(ω)
initial phase ϕ , ckt constant.
 (R, L, C) & on nature of excitation
(Sine or cosine)

But Not on the maximum
value of the excitation .

(V_m or I_m)

$$1) L(K) = \frac{K}{s}$$
$$2) L(e^{at}) = \frac{1}{s-a}$$
$$3) L(e^{-at}) = \frac{1}{s+a}$$

$$4) L(\sin at) \\ = \frac{a}{s^2 + a^2}$$

$$5) L(\cos at) = \frac{s}{s^2 + a^2} \quad s > 0$$

$$6) L(\sinh at) = \frac{a}{s^2 - a^2} \quad s > |a|$$


$$7) L(\cosh at) = \frac{s}{s^2 - a^2} \quad s > |a|$$

$$(8) \quad L(t^n) = \frac{\Gamma n + 1}{s^{n+1}} =$$


$$\frac{n!}{s^{n+1}} \quad \text{when } n \in \mathbb{N} \}$$

$n > -1$

AC circuit Analysis :-

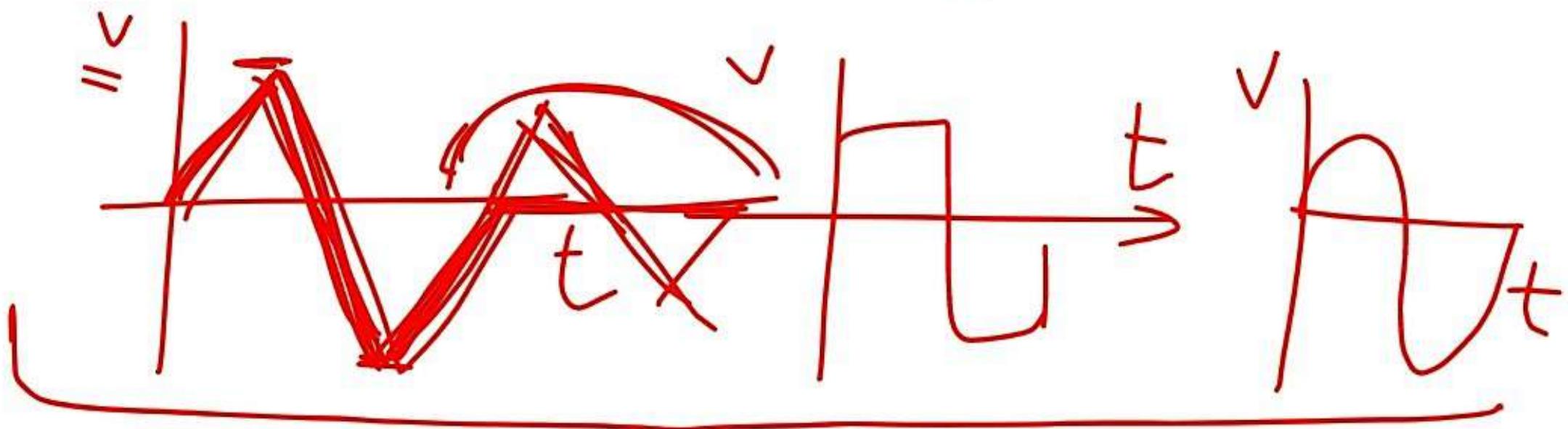
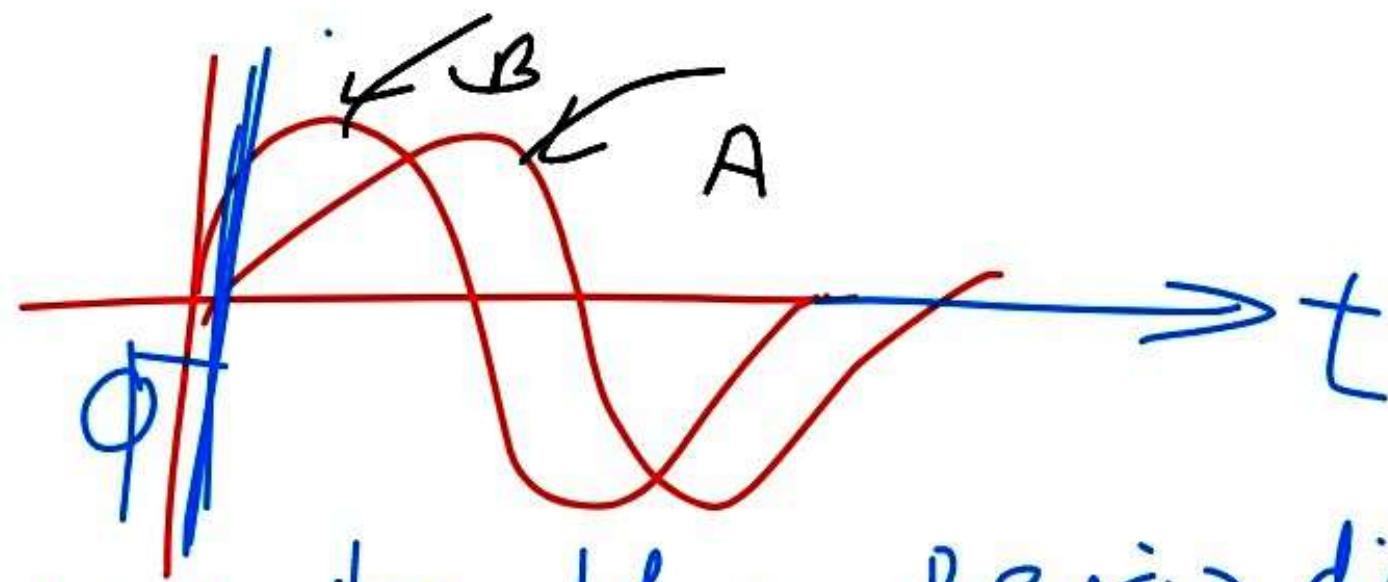
$$\begin{aligned}V &= V_m \sin \theta \\&= V_m \sin \omega t \\&= V_m \sin 2\pi f t \\&= V_m \sin \frac{2\pi}{T} t\end{aligned}$$



$x(t)$ be the periodic
signal of period T

$$x(t \pm T) = x(t)$$

Avg value = DC value

$$\text{Avg} = x_{DC} = \frac{1}{T} \int_0^T x(t) dt$$

= Area of signal over 1 period
Period.

Transient Circuit Analysis

Laplace Transform Application for solving
Steady state AC circuits

$f(t)$	$F(s)$	$f(t)$	$F(s)$
$i(t)$	$I(s)$	$\delta(t)$	1
$v(t)$	$V(s)$	$u(t)$	$1/s$
R	R	$\tau(t)$	$1/s^2$
L	sL	$p(t)$	$1/s^3$
C	$1/sL$	$e^{-at}u(t)$	$1/s+a$
	sC	$Ku(t)$	K/s

$$\frac{V(s)}{I(s)} = Z(s) \Omega$$

$$\Rightarrow V(s) = Z(s) \cdot I(s) \Rightarrow I(s) = \frac{V(s)}{Z(s)}$$

$$\frac{I(s)}{V(s)} = Y(s) \rightarrow \Rightarrow V(s) = \frac{I(s)}{Y(s)}$$

$$\Rightarrow I(s) = Y(s) \cdot V(s)$$

$$Y(s) = \frac{1}{Z(s)} \Omega$$

$Z(s)$	$Y(s)$
$R \Omega$	$1/R \Omega$
$sL \Omega$	$1/sL \Omega$
$sC \Omega$	$1/sC \Omega$

We can add impedances in series and admittances in parallel.

Ex. ① Find out the Laplace transform of the shifted gate pulse shown below.

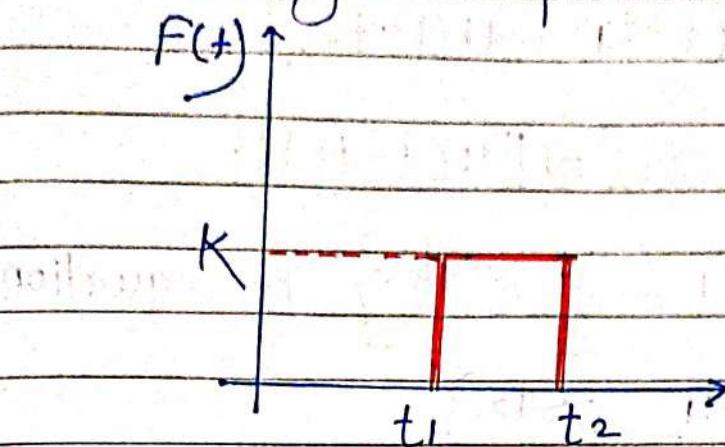


fig. A shifted gate function.

→ This shifted gate function can be synthesized with the help of two step functions as follows.

$$KU(t-t_1)$$

$$K$$

$$t_1$$

fig ① - A step function starting at t_1

$$0$$

$$t_2$$

Fig ② - A step function starting at t_2

$$-K$$

$$KU(t-t_2)$$

$$K[U(t-t_1) - U(t-t_2)]$$

$$0$$

$$t_1$$

$$t_2$$

fig. A gate pulse obtained by subtracting signal of Fig ① & ②

The above waveform shows that the gate pulse can be represented as

$$f(t) = k [U(t-t_1) - U(t-t_2)]$$

$$\mathcal{L}[f(t)] = \mathcal{L}\{k[U(t-t_1) - U(t-t_2)]\}$$


$$= k \{ \mathcal{L}[U(t-t_1)] - \mathcal{L}[U(t-t_2)] \}$$

$$= k \left\{ \frac{1}{s} e^{-st_1} - \frac{1}{s} e^{-st_2} \right\} \text{ By equation}$$

$$= \frac{k}{s} (e^{-st_1} - e^{-st_2})$$

Ex. (2) Figure shows an impedances whose voltage and current are as shown.

$$i(t) = e^{-t} - e^{-(t-2)}$$

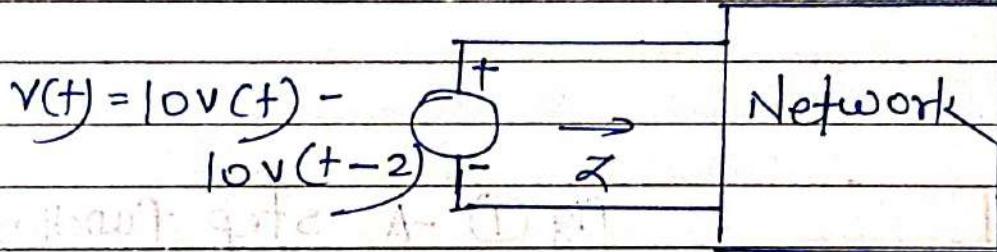

Find out the impedance α of the network using Laplace transform method.

→ Let us first evaluate the Laplace transform of $v(t)$ & $i(t)$

$$v(t) = 10 u(t) - 10 u(t-2)$$

By using Laplace transform of above eqn we get.

$$V(s) = 10 \frac{1}{s} - 10 \frac{1}{s} e^{-2s}$$

$$= \frac{10}{s} (1 - e^{-2s})$$

The current is given as
 $i(t) = e^t - e^{-(t-2)}$

Taking Laplace-transform of above eqn,

$$I(s) = \frac{1}{s+1} - \frac{1}{s+1} e^{-2s} = \frac{1 - e^{-2s}}{s+1}$$

The driving point impedance $Z(s)$ is given as

$$Z(s) = \frac{V(s)}{I(s)}$$

$$= \frac{\frac{10}{s} (1 - e^{-2s})}{\frac{1 - e^{-2s}}{s+1}} = 10 \frac{s+1}{s}$$

$$= 10 \left(1 + \frac{1}{s} \right)$$

$$= 10 + \frac{10}{s}$$

$$10 + \frac{1}{\frac{1}{10} s}$$

We know that Laplace transform of R is the value is unchanged and Laplace transform of capacitor is $\frac{1}{sc}$. Thus, the above impedance appears to be series connection of resistor and capacitor i.e.

$$Z(s) = R + \frac{1}{sc}$$

$$R = 10 \Omega \text{ and}$$

$$C = \frac{1}{10} \text{ Farad}$$

\therefore The circuit will be:


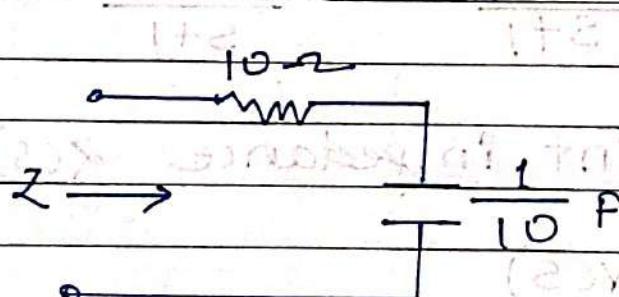


Fig: Impedance of Network.

Introduction to Transient Analysis :-

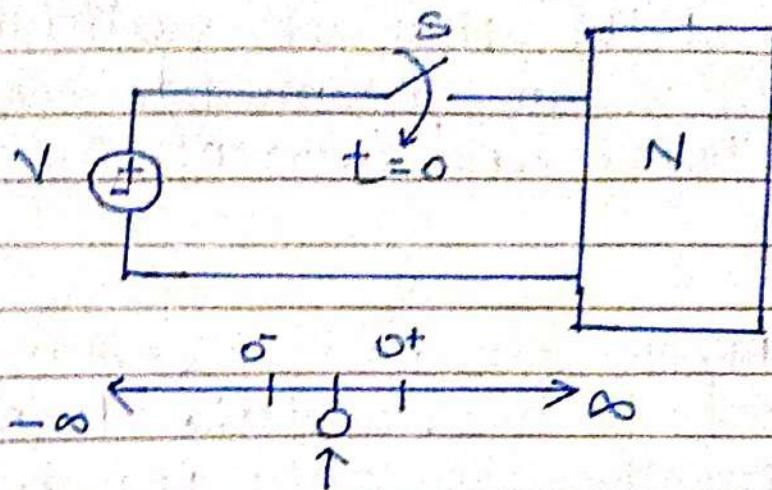

$$0^- = -0.000\dots 01$$

$$0^+ = +0.000\dots 01$$

$$0^+ - 0^- = 0.000\dots 02 \\ = 0.0$$

i.e. within zero time.

Introduction :-


→ Transient in the system is because of the presence of energy storing elements called the inductor & the capacitor.

→ Since the energy stored in a memory element cannot change instantaneously i.e. within zero time. (due to integrations of energy variables i_L and v_C). L & C elements will oppose sudden changes in the system, which results in instability of the system due to severe oscillations.

→ When the network consists of only resistances (a memoryless system), no transient occurs in the system at the time of switching, since the resistor can accommodate any amount of voltages and currents ($V = RI$ or $I = V/R$)

→ The transient effects are more severe for d.c. as compared to a.c. and the transient free condition is possible to only for a.c. excitations (at zero crossings of sine or cosine)

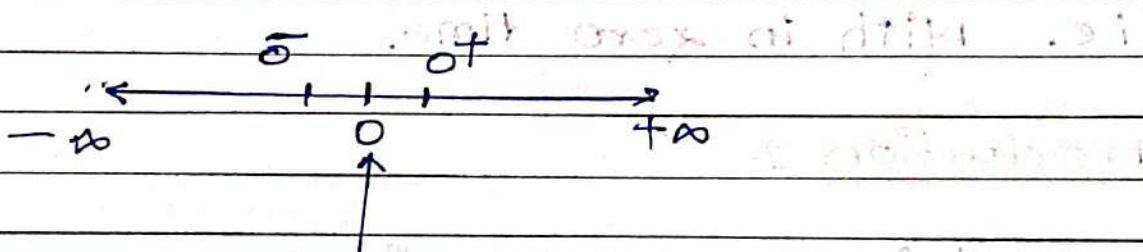Behaviour of L and C elements at $t=0^+$ and as $t \rightarrow \infty$ instants



will be discussed at instants of transient
 $Z_L = sL$ ~~and~~ ~~inductance increases with time~~

$\zeta_C = 1/sC$ ~~and~~ ~~capacitance decreases with time~~

$t = 0^+ \rightarrow s = \infty \rightarrow Z_L \rightarrow 0$ - open circuit

and $\zeta_C = 0 \rightarrow 1/C \rightarrow \infty$ - short circuit

$\zeta_C = 0 \rightarrow 1/C \rightarrow \infty$ - short circuit means no voltage across capacitor (isolate source) ~~high voltage~~

$t \rightarrow \infty \rightarrow s \rightarrow 0 \Rightarrow Z_L \rightarrow 0$ - $L \rightarrow SC$

equilibrium charge at $Z_C \rightarrow \infty$ $C \rightarrow 0$ - $C \rightarrow 0$

→ A long time after the quenching action ($t \rightarrow \infty$) is the steady state. In steady state, the inductor behaviour is a short circuit behaviour and the capacitor behaviour is an open circuit behaviour.

Steady state OR Drunken state ;

Whenever an independent DC source is connected to the network for a long time, (i.e. ideally infinite amount of time and practically up to 5 time constants), then the network is said to be in steady state. In steady state, the energy stored in the network is maximum and constant. So, energy stored in the memory elements is maximum and constant.

$$\text{i.e. } \frac{1}{2} L i_L^2 = \text{Maximum \& constant.}$$

$$\Rightarrow i_L = \text{Maximum \& constant}$$

So, inductor will act as a constant current source in steady state

$$\text{since } V_L = L \cdot \frac{di_L}{dt} \Rightarrow V_L \rightarrow 0 \Rightarrow L \rightarrow \text{sc.}$$

$$\text{Similarly } \frac{1}{2} C v_C^2 = \text{maximum \& constant}$$

$$\Rightarrow v_C = \text{Maximum \& constant}$$

so, capacitor will acts as a constant voltage source in steady state.

Since $i_c = C \frac{d}{dt} V_c \rightarrow i_c \rightarrow 0 \Rightarrow C \rightarrow 0$

Observation :

The above discussion is valid only for dc excitations / sources.

What about AC excitations / sources ?

→ for AC, during the positive slope of the period, both L & C elements are charging [i.e. storing the energy] and during the negative slope of the period, they are discharging [i.e. delivering the energy]. So, the net energy observed over the period is zero. And hence, L & C elements are always present for a.c. excitations / sources.

Blind Approach :

→ In steady state, $Z_L = j\omega L \rightarrow \underline{Z_L}$

$$Z_C = \frac{1}{j\omega C} \rightarrow \underline{Z_C}$$

→ for AC, $\omega \neq 0$ and hence $\underline{Z_L} = j\omega L (\neq 0)$ and $\underline{Z_C} = \frac{1}{j\omega C} (\neq 0)$ i.e. The impedances

are finite and hence, L and C elements are always present for a.c. excitations/sources.


→ for dc. $\omega=0$ and hence

$$Z_L = 0 \Omega \Rightarrow L \rightarrow \text{sc.}$$

$$Z_C = \infty \Omega \Rightarrow C \rightarrow \text{o.c.}$$

i.e. The L & C elements will die for dc. excitations/sources in steady state.

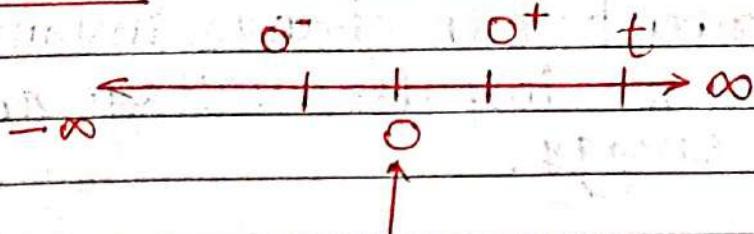Inductor current at $t=0^-$ and at $t=0^+$ instants



$$L: i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t) dt$$

$$= \frac{1}{L} \int_{-\infty}^{0^-} v_L(t) dt + \frac{1}{L} \int_{0^-}^t v_L(t) dt$$

$$= i_L(0^-) + \frac{1}{L} \int_{0^-}^t v_L(t) dt.$$

$$\text{At } t=0^+ \Rightarrow i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_0^{0^+} v_L = 0 \cdot dt$$

$$i_L(0^+) = i_L(0^-) \text{ Amperes}$$

$$E_L(0^+) = E_L(0^-) \text{ Joule}$$

So, inductor current cannot change instantaneous
i.e. with zero time for all the practical excitations.
Similarly the energy.


$$\text{If } V_L(t) = \delta(t), \text{ then } i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{-\infty}^{0^+} \delta(t) dt$$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \text{ Ampere}$$

$$E_L(0^+) > E_L(0^-) \text{ Joule.}$$

So, inductor current can change instantaneous
i.e. within zero time for impulse voltage across
it. Similarly the energy.

More Specifically for Impulse:

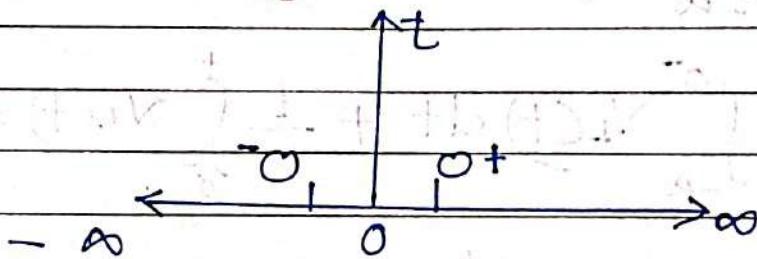

$$V_L(t) = \delta(t) = 0 \quad \text{for } -\infty \leq t < 0^-$$

$$\Rightarrow i_L(0^-) = \frac{1}{L} \int_{-\infty}^{0^-} V_L(t) \cdot dt = 0 \text{ Ampere}$$

$$i_L(0^+) = 1 \text{ Ampere.}$$

$$\text{So, } E_L(0^+) = \frac{1}{2L} \text{ Joule. } E_L(0^-) = 0 \text{ J.}$$

$$E_L(0^+) = \frac{1}{2} L i_L^{0^2}(0^+)$$

$$= \frac{1}{2} L \left(\frac{1}{L}\right)^2$$

Capacitor Voltages at $t=0^-$ & at $t=0^+$
instants:-

$$\text{C: } V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C \cdot dt$$

$$= V_C(0^-) + \frac{1}{C} \int_{0^-}^t i_C \cdot dt$$

$$\text{At } t=0^+ \Rightarrow V_C(0^+) = V_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C \cdot dt$$

$$V_C(0^+) = V_C(0^-) \text{ volt.}$$

for all practical inputs

$$E_C(0^+) = E_C(0^-) \text{ Joule.}$$

More specially for impulse :-

$$i_C = \delta(t) = 0 \text{ for } -\infty \leq t < 0^+$$

$$V_C(0^-) = \frac{1}{C} \int_{-\infty}^{0^-} i_C \cdot dt = 0 \text{ volt.}$$

$$V_c(0^+) = \frac{1}{C} \text{ volt.}$$

$$\text{So } E_c(0^-) = 0 \text{ J} \text{ & } E_c(0^+)$$


$$= \frac{1}{2} C V_c^2(0^+)$$

$$= \frac{1}{2} C \cdot \left(\frac{1}{C}\right)^2$$

$$E_c(0^+) = \frac{1}{2C} \text{ Joule.}$$

Equivalent Circuits :-

L :-

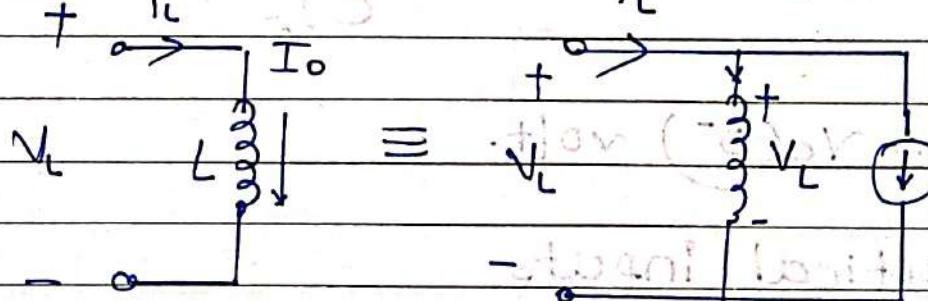

$$i_L = \frac{1}{L} \int_{-\infty}^t V_L dt$$

$$i_L = i_L(0) + \frac{1}{L} \int_0^t V_L dt \quad | \quad i_L(0) = I_0$$


Proof 2:

By KCL,

$$\rightarrow -i_L + \frac{1}{L} \int_0^t v_L dt + I_0 = 0$$

$$\rightarrow i_L = I_0 + \frac{1}{L} \int_0^t v_L dt$$

C :

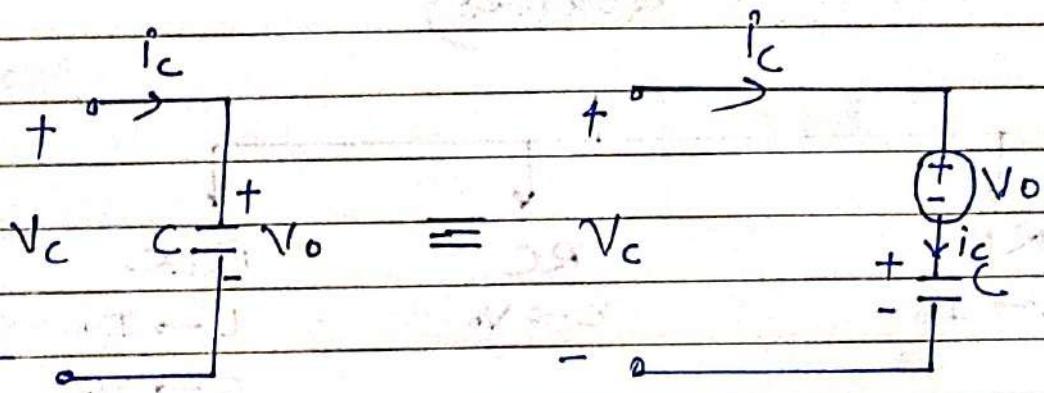

$$V_C = \frac{1}{C} \int_0^t i_C dt$$

$$V_{C(t)} = V_{C(0)} + \frac{1}{C} \int_0^t i_C dt \quad | V_{C(0)} = V_0$$

Proof 3:

$$\text{By KVL} \quad V_C - V_0 - \frac{1}{C} \int_0^t i_C dt = 0$$


$$V_C = V_0 + \frac{1}{C} \int_0^t i_C dt$$

Classification of Transient

- ① DC Transient
- ② AC Transient


DC Transient :-

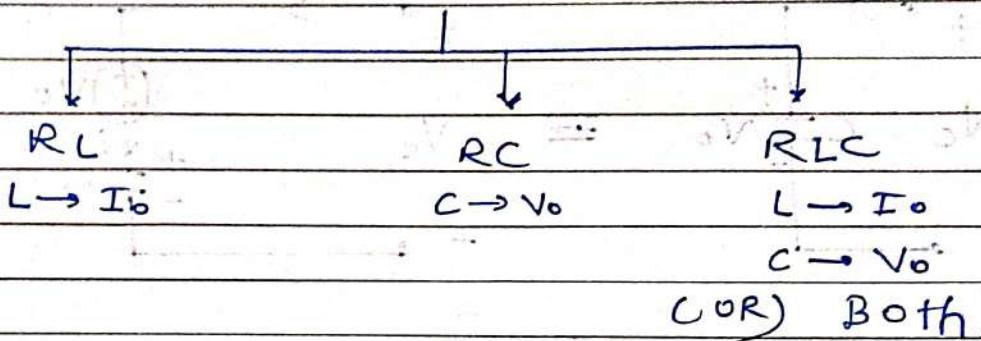- ① Source Free circuit (without independent sources)



Property :- In all the source free circuits, stored energies in the memory elements are maximum at $t=0$ and as a function of time, these stored energies will be delivered to the memoryless resistances in an exponentially decayed manner and hence, the energy present in the network at steady state ($t \rightarrow \infty$) is zero.

source free RL circuit :-

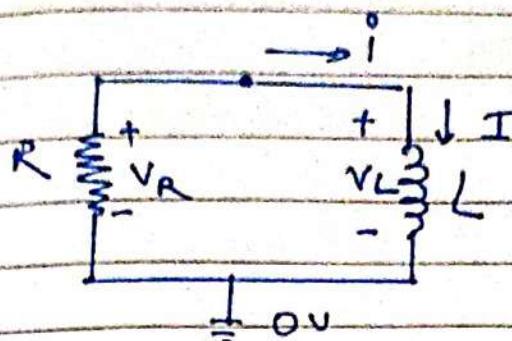

For $t \geq 0$

By KVL

$$-V_R - V_L = 0$$

$$\therefore R \cdot i - L \cdot \frac{di}{dt} = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

Let


$$D = \frac{d}{dt} \Rightarrow \left[D + \frac{R}{L} \right] i = 0$$

characteristic equation $D + \frac{R}{L} = 0$


If it is like $s = q$

$$i(t) = K e^{at} \quad \text{for } 0 \leq t \leq \infty$$
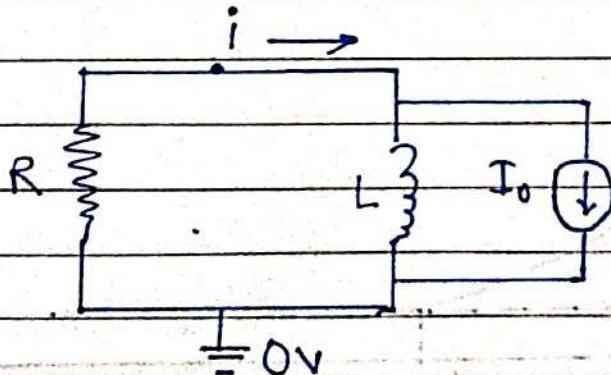
$$= K e^{-\frac{R}{L}t} \quad \text{A for } 0 \leq t \leq \infty$$



for $t \geq 0$

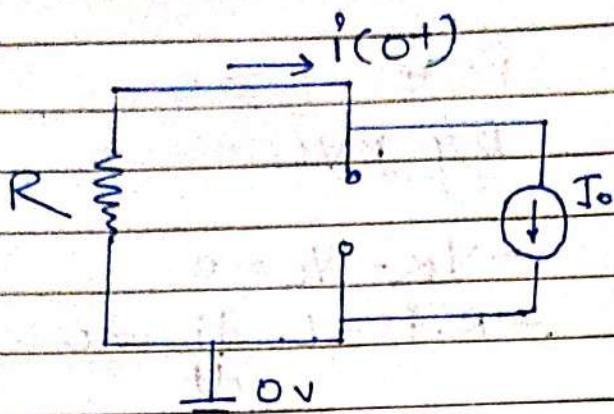


At $t = 0^+$: A resistive circuit

$$\begin{aligned} \text{By KCL} \Rightarrow -i(0^+) + I_0 &= 0 \\ \Rightarrow i(0^+) &= I_0 \end{aligned}$$

$$\begin{aligned} \text{So } t = 0^+ \Rightarrow i(0^+) &= k e^{-0} \Rightarrow k = i(0^+) = I_0 \\ \Rightarrow i(t) &= I_0 e^{-\frac{Rt}{L}} \text{ Ampere, for } 0 \leq t \leq \infty \end{aligned}$$

$\Rightarrow \tau = \frac{L}{R}$ seconds = Time constant
of the circuit
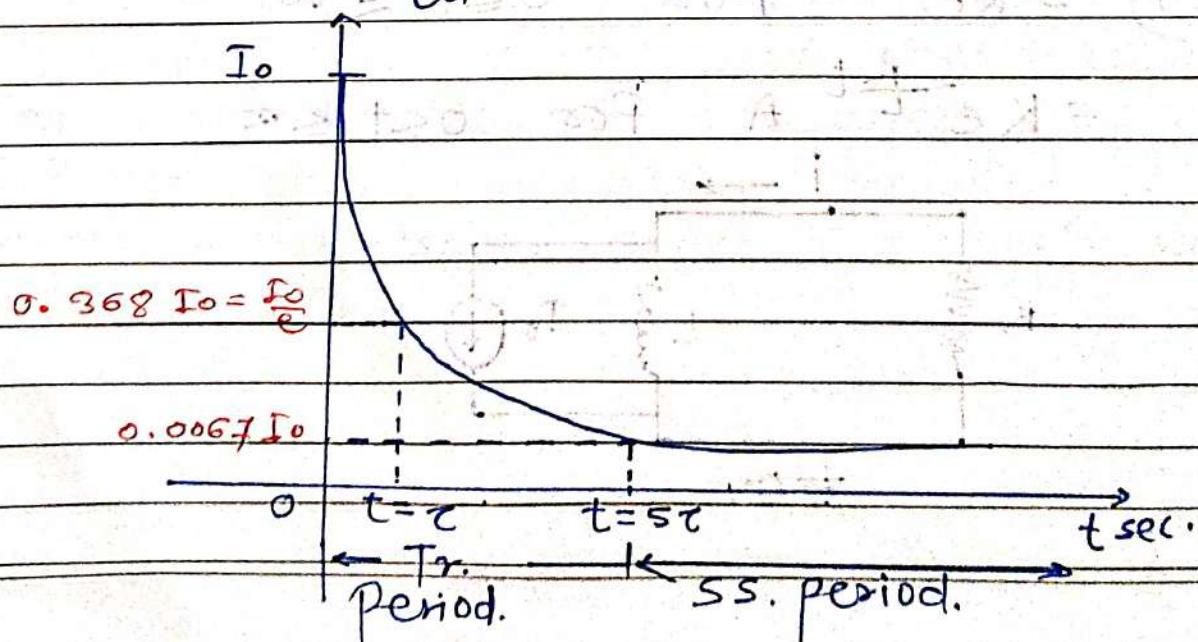
$$v_L(t) = L \frac{di(t)}{dt} \text{ By Ohm's law}$$




At $t = 5\tau_i$,

$$i(t) = I_0 e^{-t/\tau_i} = \frac{I_0}{e^5} = 0.0067 I_0 \approx 0.0$$

$$E_L(t) = \frac{1}{2} L i^2(t) \text{ Joule} = \frac{1}{2} L \left[I_0 e^{-t/\tau_i} \right]^2$$

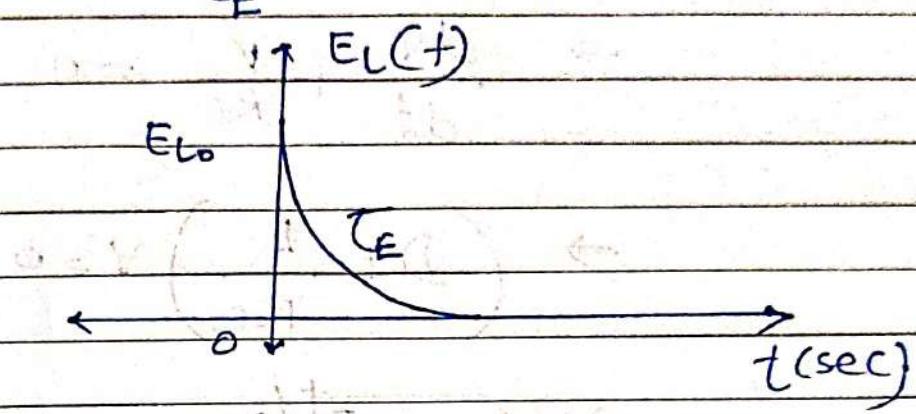
$$= E_{L_0} \frac{e^{-t/\tau_F}}{\tau_F} \text{ Joule} \quad \text{for } 0 \leq t \leq \infty$$



$$\tau_F = \frac{\tau_i}{2} = \frac{L}{2R} \text{ sec.}$$

So the energy is 2 times faster than the current decay.


Source Free RC circuit

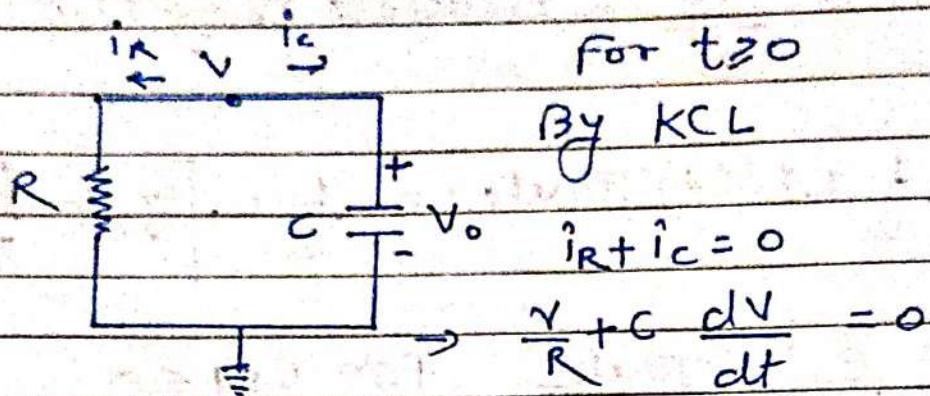


$$\rightarrow \frac{dV}{dt} + \frac{V}{RC} = 0$$

$$\rightarrow \left(D + \frac{1}{RC} \right) V = 0$$
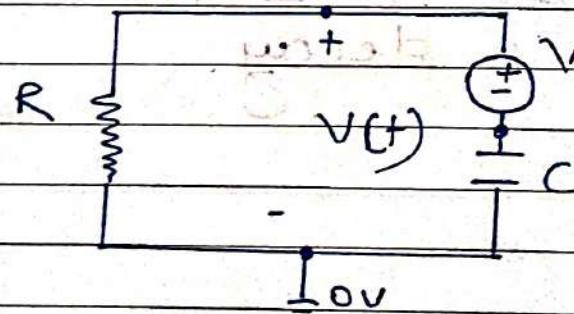
$$\Rightarrow V(t) = k e^{-t/RC} \text{ volt for } 0 \leq t < \infty$$



for $t \geq 0$

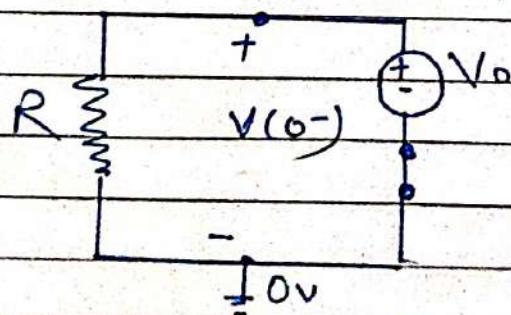

At $t = 0^+$; A resistive circuit


$$\text{so, } t = 0^+ \Rightarrow V(0^+) = V_0 \quad \rightarrow V(0^+) = k e^0 \Rightarrow k = V(0^+) = V_0$$

$$V(t) = V_0 e^{-\frac{t}{RC}} \quad V \text{ for } 0 \leq t < \infty$$

$$V(t) = V_0 e^{t/RC} \quad V \text{ for } 0 < t \leq \infty$$

$\tau = RC$ = Sec. = Time constant of the circuit

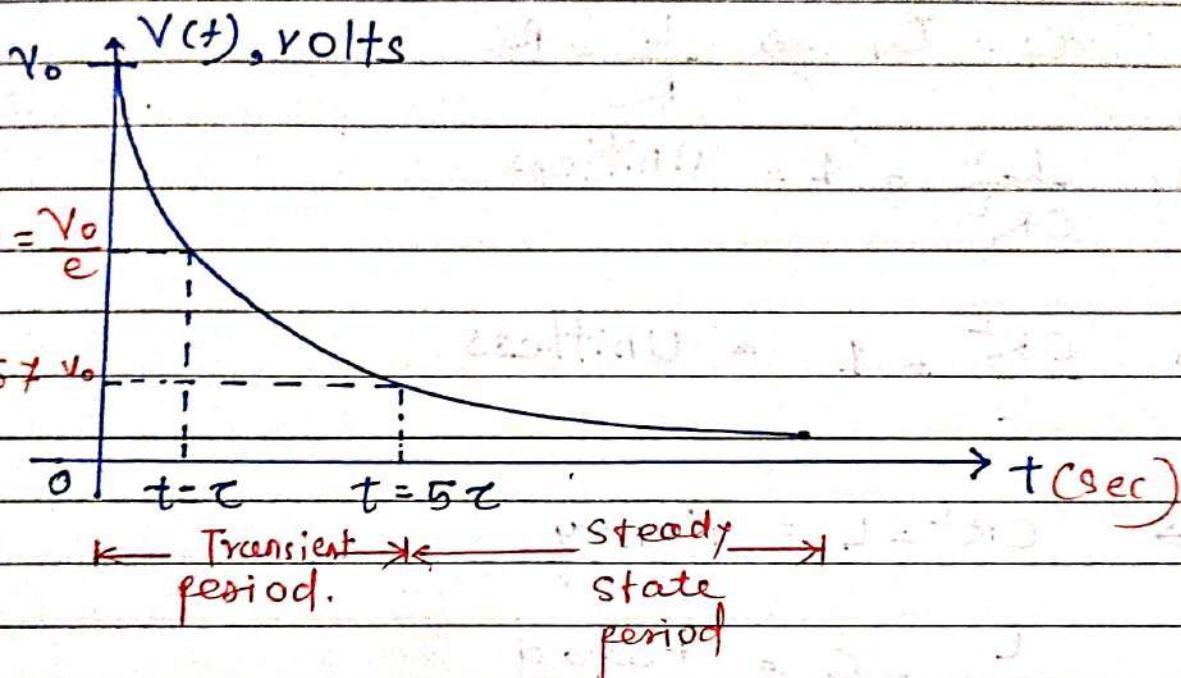
$$i_c = C \frac{dV(t)}{dt} \quad \text{By Ohm's law}$$



$$\text{At } t = 5\tau, V(t) = V_0 e^{-5} = \frac{I_0}{e^5} = 0.0067 V_0 \approx 0.0$$

$$E_c(t) = \frac{1}{2} C V^2(t) \text{ Joule} = \frac{1}{2} C \left(V_0 e^{-t/\tau} \right)^2$$
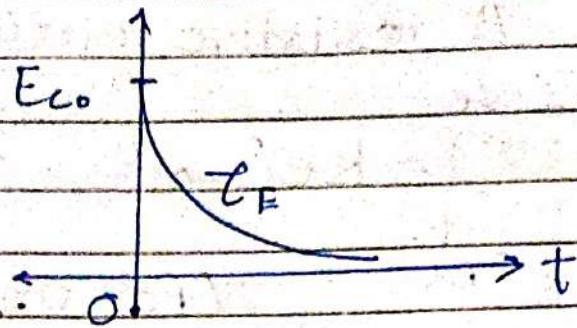
$$= E_c e^{-t/\tau} \text{ Joule for } 0 \leq t < \infty$$



$$T_E = \frac{T_v}{2} = \frac{RC}{2} \text{ sec.}$$

So the energy decay is 2 times faster than the voltage decay.

→ Second = second

$$T_i = T_v \Rightarrow \frac{L}{R} = RC$$

$$\rightarrow \frac{L}{CR^2} = 1 = \text{Unitless}$$

$$\rightarrow \frac{CR^2}{L} = 1 = \text{Unitless}$$

$$\rightarrow CR^2 = L = \text{Henry}$$



$$\rightarrow \frac{L}{R^2} = C = \text{Farad}$$

$$\rightarrow \frac{L}{RC} = R = \text{Ohm}$$

$$\rightarrow \frac{L}{C} = R^2 = \text{Ohm}^2$$

$$\rightarrow \sqrt{\frac{L}{C}} = R^2 = \text{Ohm.}$$

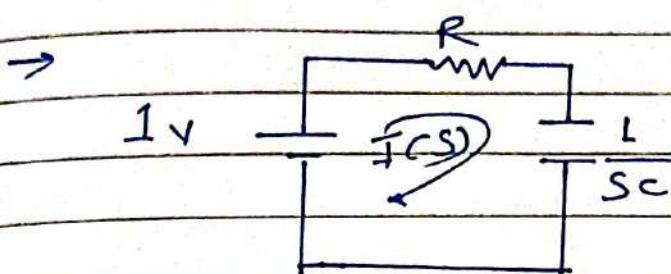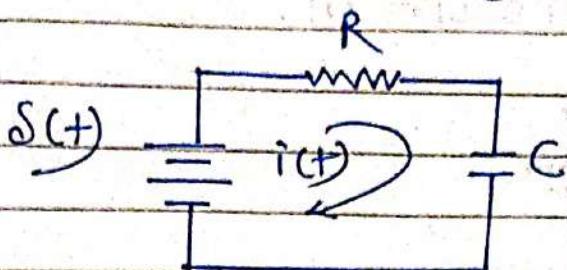Example 3:- The circuit shown below, find $i(t)$ if the impulse voltage is applied to the circuit



$$I_{CS} = \frac{1}{R + \frac{1}{sC}} = \frac{sC}{sRC + 1}$$


$$I_{CS} = \frac{sC/R}{s + \frac{1}{RC}} = \frac{s/R}{s + 1/RC}$$

$$I_{CS} = \frac{1}{R} \left[\frac{s + \frac{1}{RC} - \frac{1}{RC}}{s + \frac{1}{RC}} \right]$$

$$= \frac{1}{R} \left[1 - \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \right] \Rightarrow i(t) = \frac{1}{R} \left[S(+) - \frac{1}{RC} e^{-\frac{t}{RC}} \right]$$

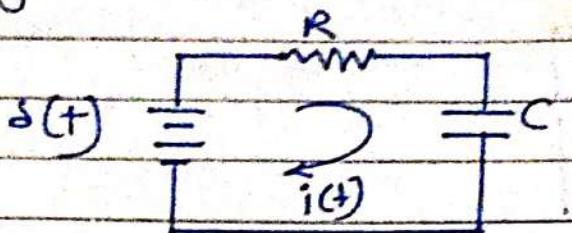Example:

The circuit is shown. Find $i(t)$ if the impulse voltage is applied to the circuit.




$$\rightarrow i.v \quad \frac{1}{R} i_{(s)} - \frac{1}{sc}$$


A circuit diagram for the impulse voltage source $s(t)$. It shows a rectangular loop with an arrow indicating current flow. Inside the loop, there is a circle with $i(s)$ written next to it, indicating the direction of current flow in the loop.

Example: In the network of Figure, the switch is initially at position 1. On the steady state having reached, the switch is changed to position 2. Find current $i(t)$

→

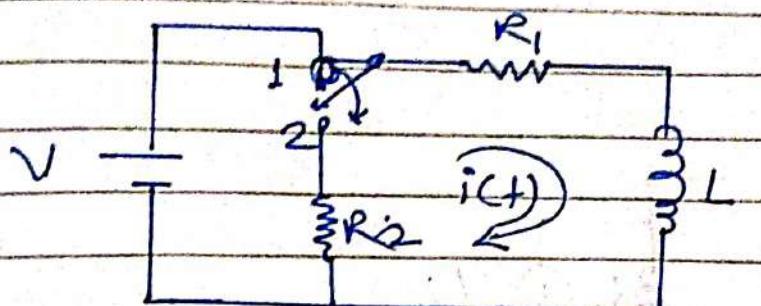

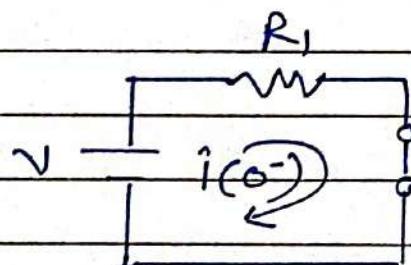At $t = 0^-$, the network has attained steady state condition. Hence, the inductor acts as a short circuit



$$i(0^-) = \frac{V}{R_1}$$

Since the inductor does not allow sudden change in current


$$i(0^+) = \frac{V}{R_1}$$

Writing KVL equation for $t > 0$

$$(R_1 + R_2) \cdot i + L \frac{di}{dt} = 0$$

$$\frac{di}{dt} + \frac{(R_1 + R_2)}{L} i = 0$$

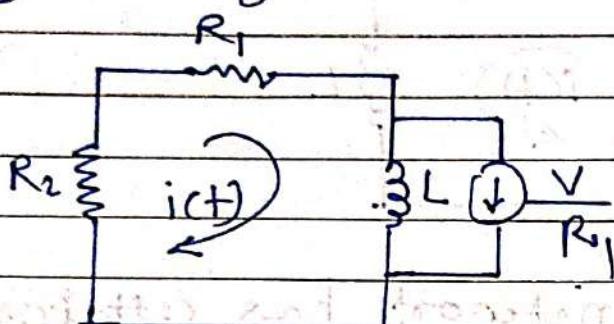The solution of this differential equation is given by



$$i(t) = k e^{-\left(\frac{R_1 + R_2}{L}\right)t}$$


$$\text{At } t=0, i(0) = \frac{V}{R_1}$$

$$\frac{V}{R_1} = k e^0 = k$$

$$i(t) = \frac{V}{R_1} e^{-\left(\frac{R_1 + R_2}{L}\right)t}$$

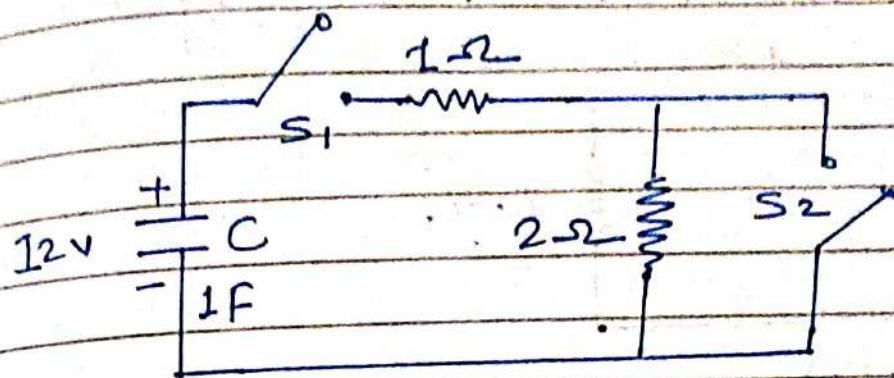Example 8

The capacitor in the circuit as shown below is initially charged to 12 volt with S_1 & S_2 open. S_1 is closed at $t=0$ while S_2 is closed at $t=3$. The waveform of the capacitor current is represented by



→ for $0 < t < 3$, the circuit is shown in fig.

$$i(0^+) = \frac{12}{3} = 4 \text{ Amp.}$$

$$\tau = RC = 1 \times 3 = 3 \text{ second}$$

$$i(t) = 4e^{-t/3}$$

$$i(3^-) = 4e^{-1} = 1.48$$

$$V_C(3^-) = 4e^{-1} \quad V_C(3^+) = 4e^{-1} \times 3 = 4.44$$

At $t=3$, S_2 is closed. 2Ω is short circuited. Current jumps to a higher value and then decays to zero quickly with a reduced time constant.

For $3 < t < \infty$ The circuit is shown in Fig ②

$$i_c(3+) = \frac{V_c(3+)}{1} = 4.44$$

$$i_c(\infty) = 0$$

$i_c(t)$ for $0 < t < \infty$ is shown in Fig ③

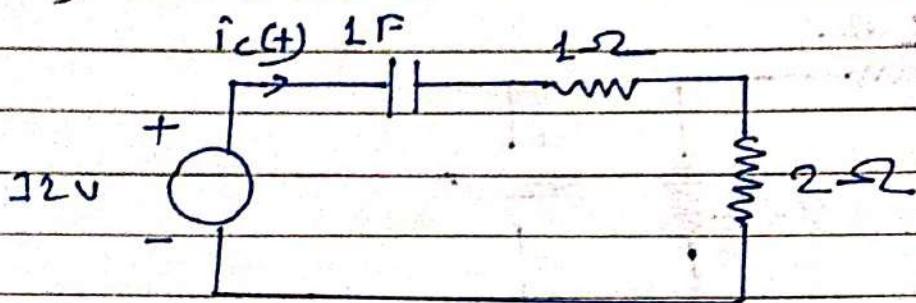


Fig ①

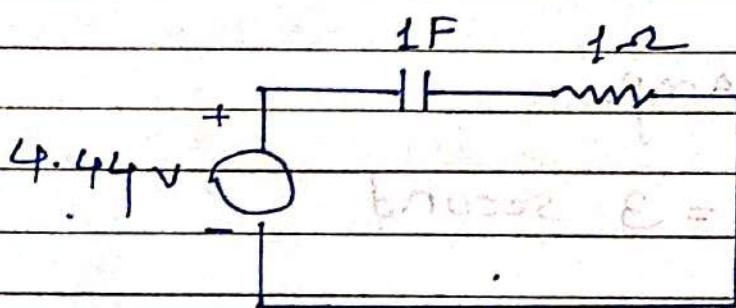


Fig ②

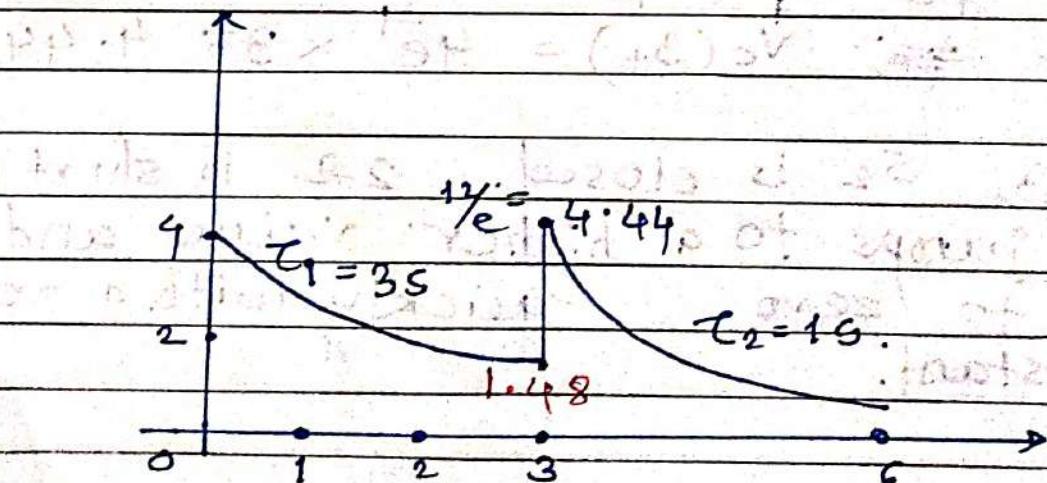


fig ③

Note :- With source circuits and using Laplace Transform Analysis

Behaviour of inductor and capacitor with sources, initial ($t=0^+$) and Final ($t \rightarrow \infty$) conditions


$$\text{At } t \rightarrow t=0^+ \Rightarrow L = 0C \Rightarrow C \approx SC.$$

$$\text{As } t \rightarrow t \rightarrow \infty \Rightarrow L = SC. \Rightarrow C = 0C.$$


Property :- At these two instant, L & C elements will lose their significance and hence the nature of the circuit is resistive

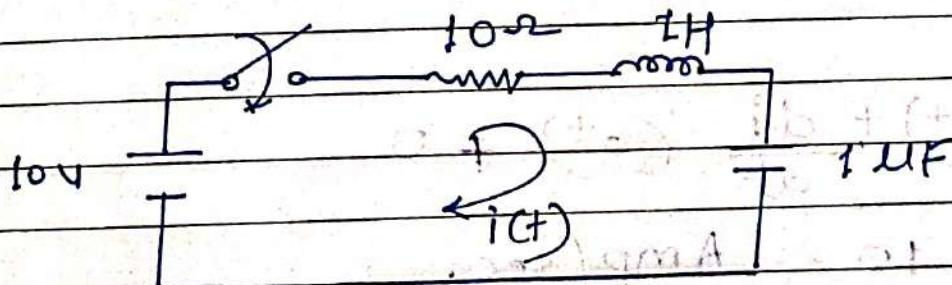Example :- In the network shown in figure the switch is closed. Assuming all initial conditions as zero

Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$.



Soln :-

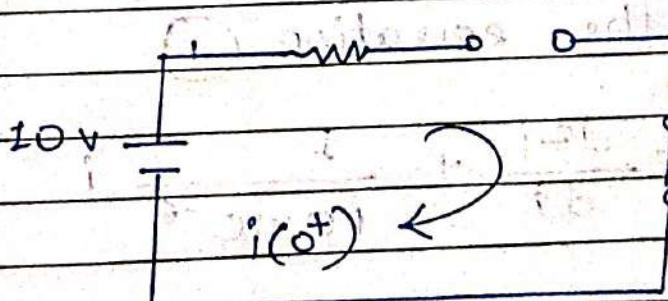

At $t=0^-$


$$i(0^-) = 0, V_c(0^-) = 0$$

At $t=0^+$, the inductor acts as an open circuit and the capacitor acts as a short circuit

$$i(0^+) = 0$$

$$V_c(0^+) = 0$$

Writing KVL equation For $t > 0$

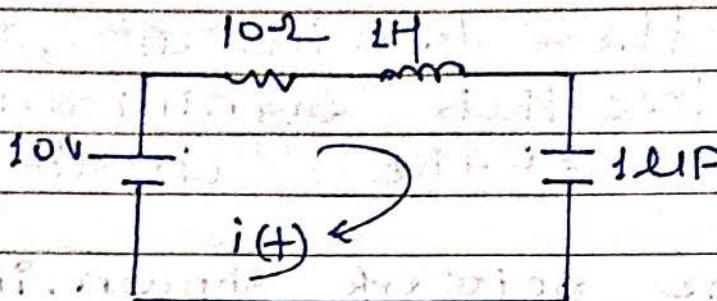

$$10 - 10i - 1 \cdot \frac{di}{dt} - \frac{1}{10 \times 10^{-6}} \int_0^t i dt = 0$$

$$10 = 10i + \frac{di}{dt} - \frac{1}{10 \times 10^{-6}} \int_0^t i dt \quad \text{--- (1)}$$

At $t=0^+$

$$10 = 10i(0^+) + \frac{di}{dt}(0^+) \neq 0$$

$$\frac{di}{dt}(0^+) = 10 \text{ Amp/sec.}$$

Differentiating the equation (1)


$$0 = 10 \frac{di}{dt} + \frac{d^2i}{dt^2} + \frac{1}{10 \times 10^{-6}} \cdot i$$

At $t=0^+$


$$0 = 10 \frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} + \frac{1}{10^{-5}} i(0^+)$$

$$\frac{d^2i(0^+)}{dt^2} = -10 \times 10 = -100 \text{ Amp/sec.}$$

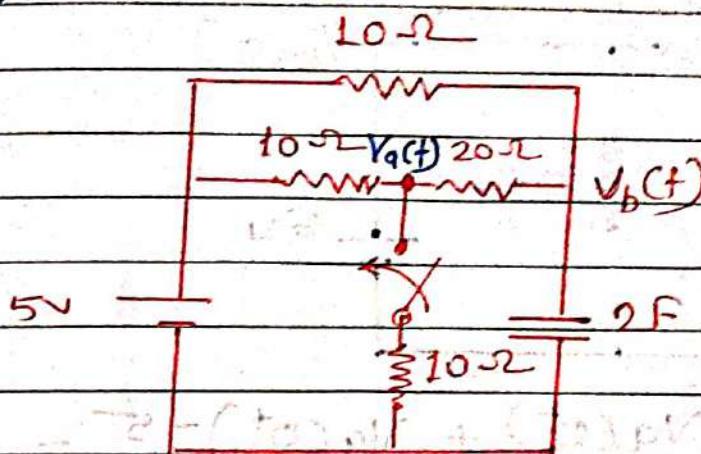Example:- In the accompanying fig. is shown a network in which a steady state is reached with switch open. At $t=0$, switch is closed. Determine $V_a(0^-)$, $V_a(0^+)$, $V_b(0^-)$ & $V_b(0^+)$



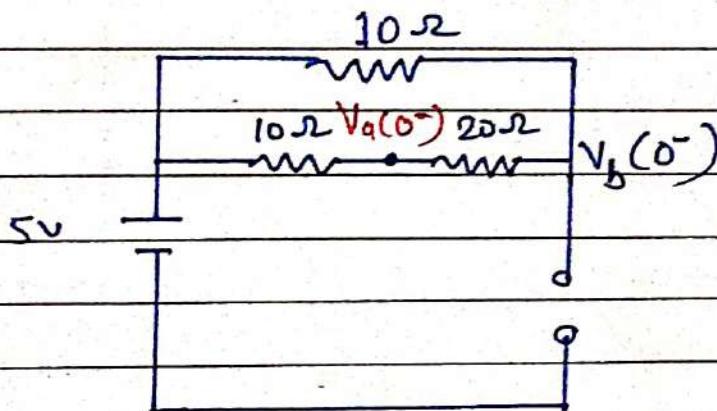At $t=0^-$, the network attains steady state condition. Hence, the capacitor acts as an open circuit.




$$V_a(0^-) = 5 \text{ volt.}$$

$$V_b(0^-) = 5 \text{ volt.}$$

At $t = 0^+$, the capacitor acts as a voltage source of 5 volt.

$$V_b(0^+) = 5 \text{ volt.}$$

Writing KCL equation at $t = 0^+$

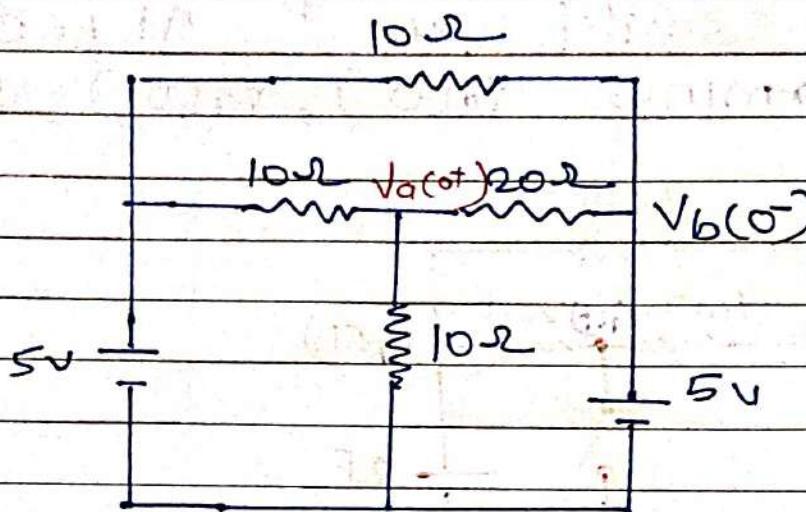


$$\frac{V_a(0^+) - 5}{10} + \frac{V_a(0^+)}{10} + \frac{V_a(0^+) - 5}{20} = 0$$

$$0.25V_a(0^+) = 0.75$$



$$V_a(0^+) = 3 \text{ volt.}$$

With sources, Laplace transforms approach
of solving transient problems for oscillos


R :-

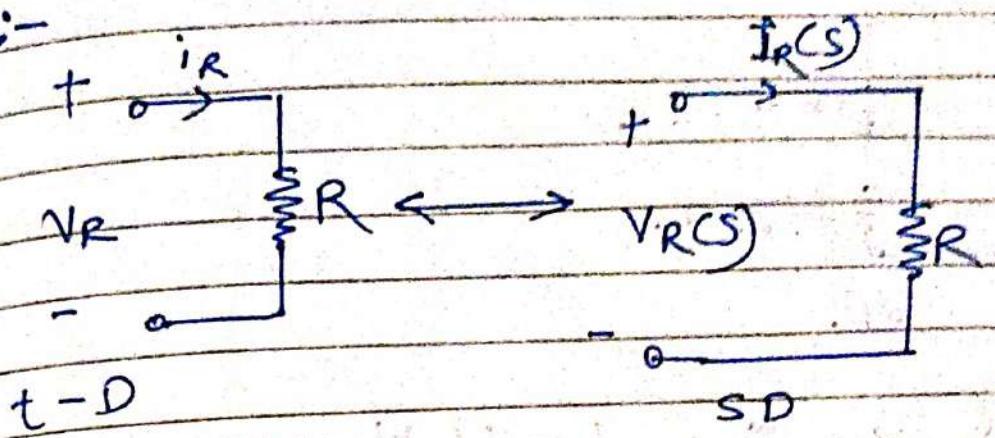

L :-

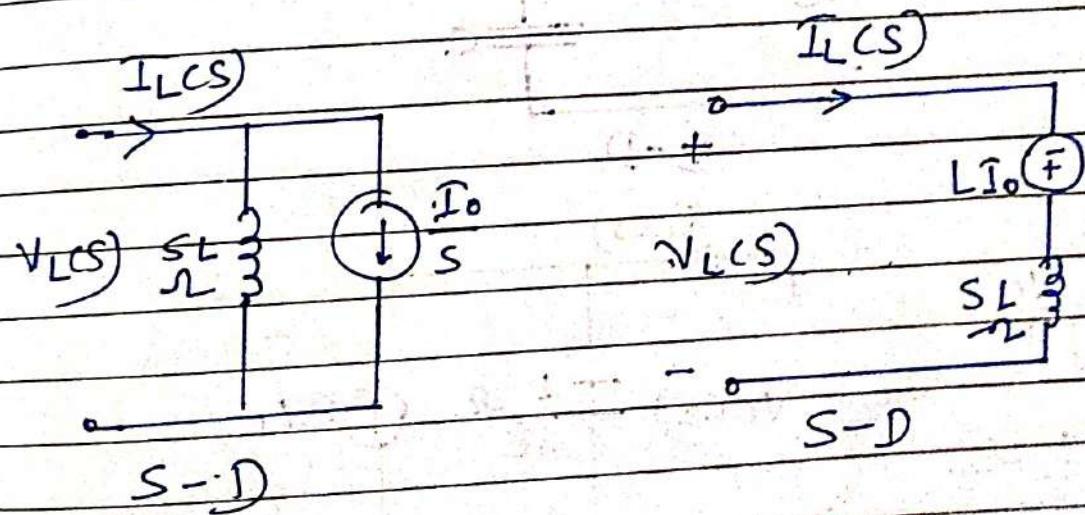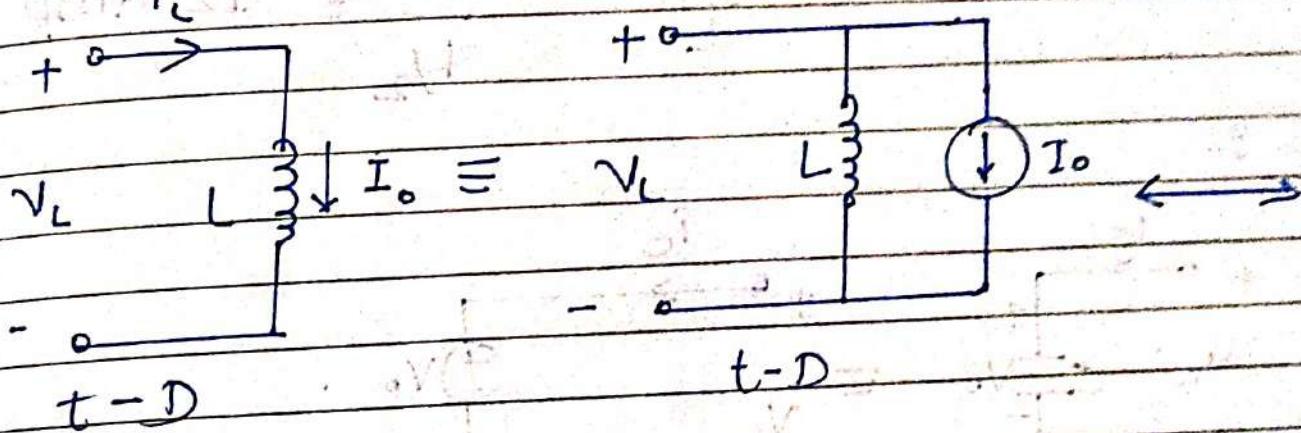

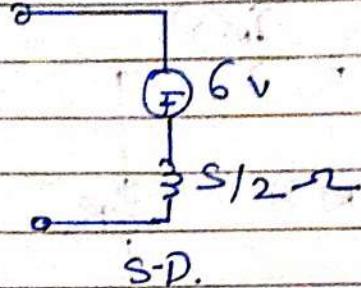
Example: The network below, represents the equivalent of an inductor in Laplace domain. Determine initial current through it




Since $LI_0 = 6 \text{ V}$ & $L = \frac{1}{2} \text{ Henry}$.

$$\text{So, } I_0 = \frac{6}{L} \Rightarrow \frac{6}{\frac{1}{2}} = 12 \text{ Amp}$$


C :-

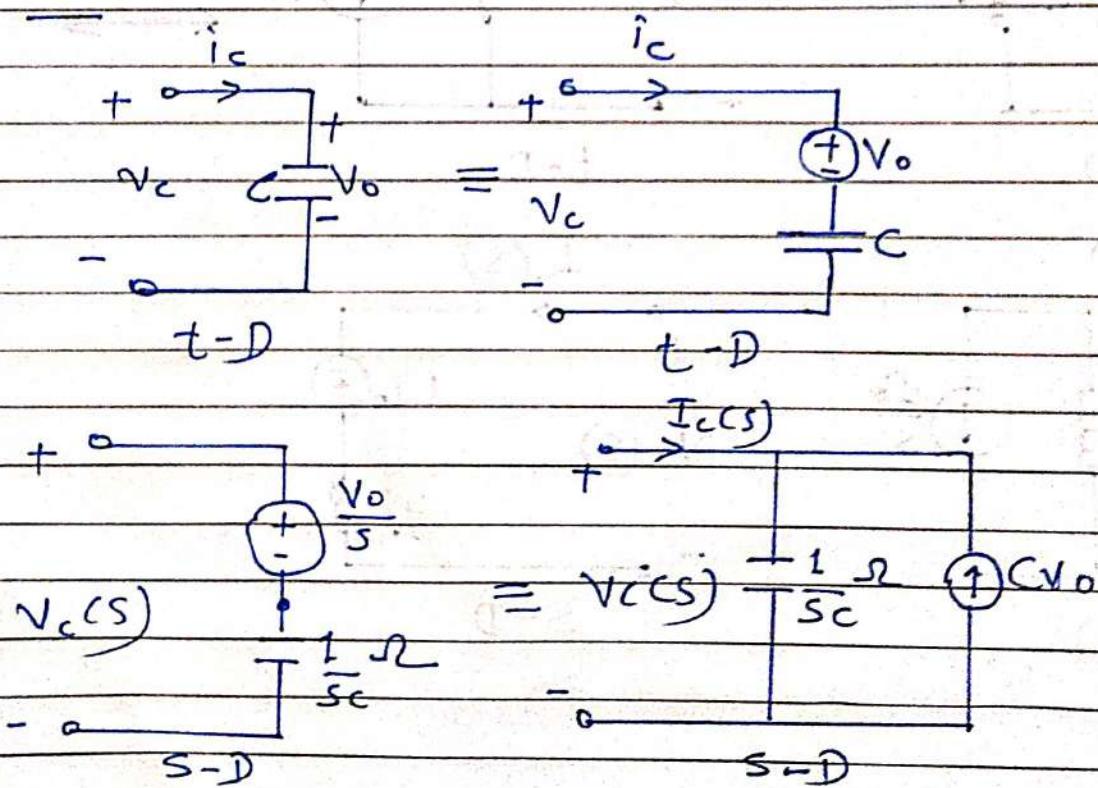

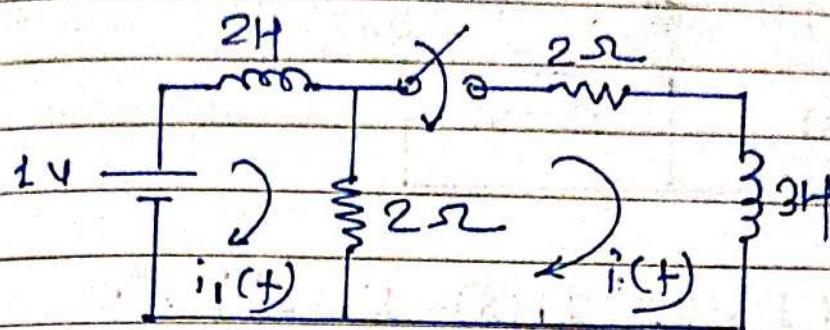Example: In the network shown, in Figure, the switch is closed at $t=0$, the steady state being reached before $t=0$. Determine current through inductor of 3 H .



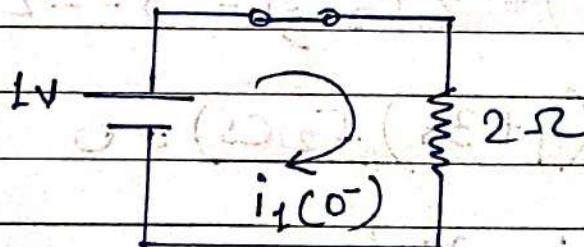→ At $t = 0^-$, steady state condition is reached. Hence, the inductor of 2 H acts as a short circuit.



$$i_1(0^-) = \frac{1}{2} \text{ Amp.}$$


$$i_2(0^-) = 0$$

since current through the inductor cannot change instantaneously

$$i_1(0^+) = \frac{1}{2} \text{ Amp.}$$

$$i_2(0^+) = 0$$

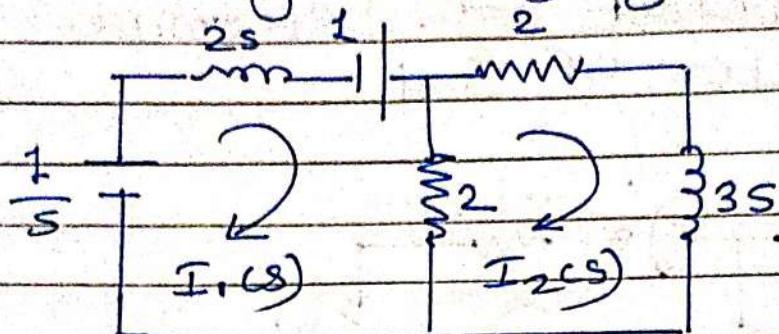For $t > 0$, the transformed network is shown in Fig. Applying KVL to Mesh 1



$$\frac{1}{s} - 2sI_1(s) + 1 - 2(I_1(s) - I_2(s)) = 0$$

$$(2+2s)I_1(s) - 2I_2(s) = 1 + \frac{1}{s}$$

Applying KVL to mesh 2

$$-2(I_2(s) - I_1(s)) - 2I_2(s) - 3sI_2(s) = 0$$

$$-2I_1(s) + (4+3s)I_2(s) = 0$$

By cramer's rule

$$I_2(s) = \frac{\begin{vmatrix} 1+s/s & 1 \\ -2 & 0 \end{vmatrix}}{\begin{vmatrix} 2+2s & 1+s/s \\ -2 & 0 \end{vmatrix}}$$

$$\frac{\begin{vmatrix} 2+2s & -2 \\ -2 & 4+3s \end{vmatrix}}{\begin{vmatrix} 2+2s & 1+s/s \\ -2 & 0 \end{vmatrix}}$$

$$= \frac{\frac{2}{s}(s+1)}{(2s+2)(4+3s)-4}$$

$$\frac{(2s+2)(4+3s)-4}{\frac{2}{s}(s+1)}$$

$$= \frac{s+1}{s(2s^2+7s+2)} = \frac{s+1}{3s(s+\frac{1}{3})(s+2)}$$

$$= \frac{\frac{1}{3}(s+1)}{s(s+2)(s+\frac{1}{3})}$$

By partial fraction expansion,

$$I_2(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+\frac{1}{3}}$$

$$A = \frac{\frac{1}{3}(s+1)}{(s+2)(s+\frac{1}{3})} \Big|_{s=0} = \frac{1}{2}$$

$$C = \frac{\frac{1}{3}(s+1)}{s(s+2)} \Big|_{s=-\frac{1}{3}} = -\frac{2}{5}$$

$$B = \frac{\frac{1}{3}(s+1)}{s(s+\frac{1}{3})} \Big|_{s=2} = -\frac{1}{10}$$


$$I_2(s) = \frac{1}{2s} - \frac{1}{10(s+2)} - \frac{2}{5(s+\frac{1}{3})}$$

Taking inverse Laplace transform


$$i_2(t) = \frac{1}{2} - \frac{1}{10} e^{-2t} - \frac{2}{5} e^{-(1/3)t} \text{ for } t > 0$$

~~Ex~~ example:-

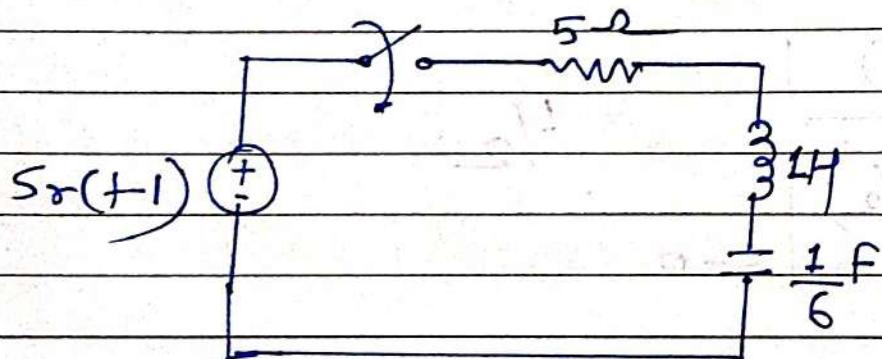For the network shown, determine the current $i(t)$ when the switch is closed at $t=0$ with zero initial conditions.



The transformed network is shown in fig.

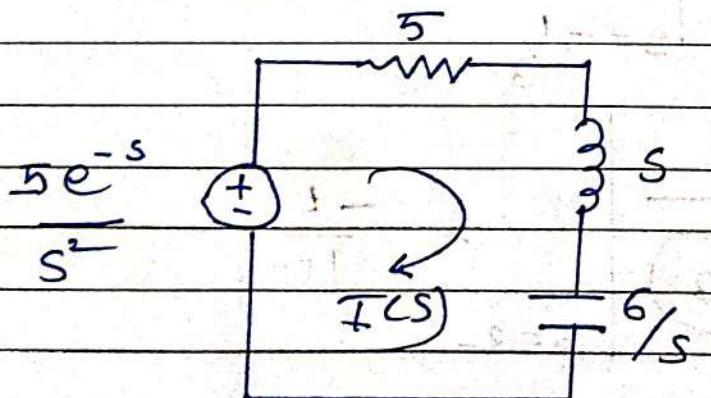

Applying KVL to the mesh for t > 0

$$\frac{5e^{-s}}{s^2} - 5I(s) - \frac{6}{s} I(s) = 0$$

$$5e^{-s} - 5I(s) + sI(s) + \frac{6}{s} I(s) = \frac{5e^{-s}}{s^2}$$

$$I(s) = \frac{5e^{-s}}{s(s^2 + 5s + 6)} = \frac{5e^{-s}}{s(s+3)(s+2)}$$

By partial fraction expansion

$$\frac{1}{s(s+3)(s+2)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+2}$$

$$A = \left. \frac{1}{(s+3)(s+2)} \right|_{s=0} = 1/6$$

$$B = \left. \frac{1}{s(s+2)} \right|_{s=-3} = 1/3$$

$$C = \left. \frac{1}{s(s+3)} \right|_{s=-2} = -1/2$$

$$I(s) = 5e^{-s} \left[\frac{1}{6s} + \frac{1}{3(s+3)} - \frac{1}{2(s+2)} \right]$$

$$= \frac{5e^{-s}}{6s} + \frac{5e^{-s}}{3(s+3)} - \frac{5e^{-s}}{2(s+2)}$$

Taking inverse Laplace transform

$$i(t) = \frac{5}{6} u(t-1) + \frac{5}{3} e^{-3(t-1)} u(t-1) - \frac{5}{2} e^{-2(t-1)} u(t-1)$$

Phasor Representation and its Importance in steady state AC circuit Analysis

A phasor is a complex number that represents amplitude and phase of a sinusoid. It is defined only for the sinusoidal signals. All sinusoidal signals are converted into cosinusoids by subtracting 90° from phase.

- As a complex quantity a phasor may be expressed in exponential form, polar form, rectangular form. Since phasor have magnitude & phase ("direction"), it behaves as a vector.

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \phi) \\ &= \text{Real part} [V_m e^{j(\omega t + \phi)}] \end{aligned}$$

$$= \text{Real part} [V_m e^{j\phi} \cdot e^{j\omega t}]$$

$$= \text{Real part} [V \cdot e^{j\omega t}]$$

$$v = V_m e^{j\phi} \rightarrow \text{Exponential form of phasor representation}$$

$$= V_m L \phi \rightarrow \text{Polar form of the phasor representation.}$$

$$= V_m (\cos \phi + j \sin \phi) \rightarrow \text{Rectangular form of phasor representation.}$$

$$i(t) = I_m \cos(\omega t + \theta)$$

$$I = I_m L \theta \rightarrow \text{Polar}$$

$$= I_m e^{j\theta} \rightarrow \text{Expo}$$

$$= I_m (\cos \theta + j \sin \theta) \rightarrow \text{Rect.}$$

eg. $v(t) = 10 \cos(2t + 30^\circ) \text{ volt.}$

$$v = 10 L 30^\circ \rightarrow \text{Polar}$$

$$= 10 e^{j30^\circ} \rightarrow \text{Expo}$$

$$= 10 (\cos 30^\circ + j \sin 30^\circ) \rightarrow \text{Rect}$$

$$= 10 \left[\frac{\sqrt{3}}{2} + j \frac{1}{2} \right] \text{ ie. phasor is}$$

a representation of complex number?

eg. $i(t) = 10 \sin(2t + 30^\circ) \text{ Ampere}$
 $= 10 \cos(2t + 30^\circ - 90^\circ) \text{ Ampere}$
 $= 10 \cos(2t - 60^\circ) \text{ Ampere}$

$$I = 10 L - 60^\circ.$$

$$\begin{aligned}
 &= 10e^{j60^\circ} \\
 &= 10(\cos 60^\circ - j\sin 60^\circ) \\
 &= 10 \left(\frac{1}{2} - j\frac{\sqrt{3}}{2} \right)
 \end{aligned}$$

$$\boxed{\frac{V}{I} = Z}$$

$$V = Z \cdot I \Rightarrow I = \frac{V}{Z}$$

$$\frac{I}{V} = Y$$

$$I = Y \cdot V \Rightarrow V = \underline{I}$$

$$\boxed{Y = \frac{1}{Z}}$$

$$t - p \leftrightarrow p - p$$

$$i(+)\leftrightarrow I$$

$$v(+)\leftrightarrow V$$

$$R \leftrightarrow R$$

$$L \leftrightarrow j\omega L \rightarrow C(s = j\omega)$$

$$C \leftrightarrow \frac{1}{j\omega C}$$


Note :-

- Analysis of AC in steady state is generally carried out in the phasor domain i.e. KCL, KVL, Ohm's Law, Nodal Mesh, and source transformation are written only in the phasor domain.
- Addition & subtraction operations of phasors are carried out only in the rectangular form, whereas division & multiplication operations of phasors are carried out either in polar or in exponential form..

AC Transient :-

Steady State Response and Transient response condition for RL, RC & RLC Circuits.

Series RL Circuit :-

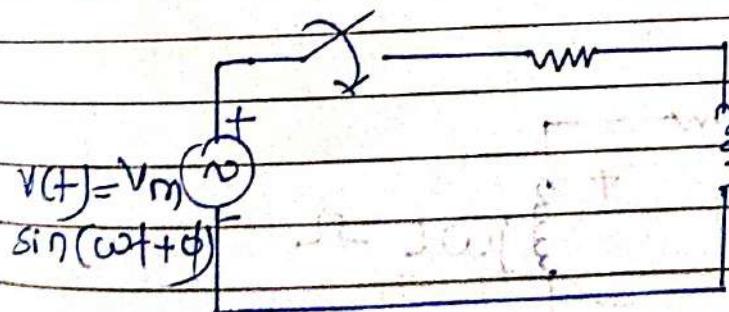

$$C.S = C.F + P.I$$

Complex situation =
complex function +
particular integration.

$i(t) =$ Natural + forced
response + response

→ Transient Response + Steady state response


⇒ Response upto 5τ + Response after 5τ

$$i(t) = i_{tr}(t) + i_{ss}(t)$$

$$i(t) = K e^{-t/\tau} + i_{ss}(t)$$

$$= K e^{-R/L t} + i_{ss}(t)$$


$i_{ss}(t)$

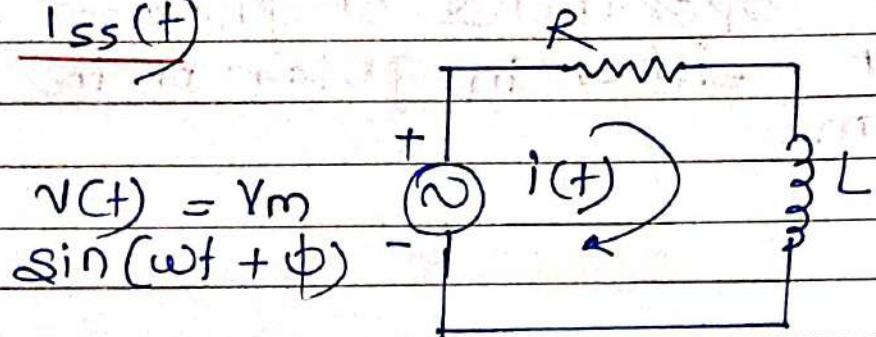

Network is in steady state

Method (1): By Phasor approach :-

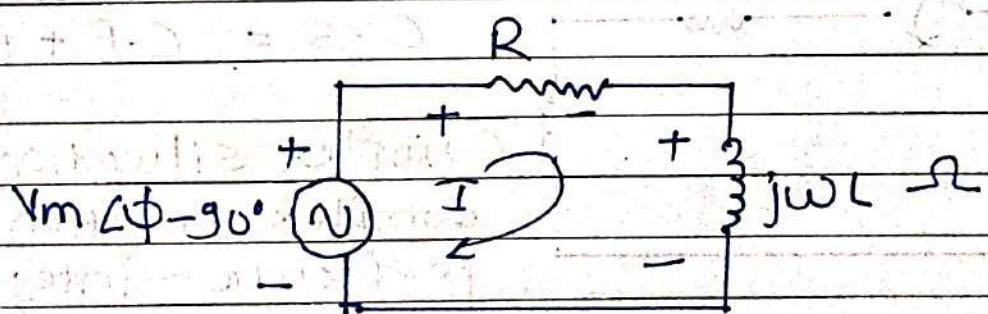Transform above network into phasor domain



Network is in P.D

$V = Z \cdot I$ / By Ohm's law in P.D.

By KVL in P.D

$$\Rightarrow V_m \angle \phi - 90^\circ - RI - j\omega L I = 0$$

$$I = \frac{V_m \angle \phi - 90^\circ}{R + j\omega L} = \frac{V_m \angle \phi - 90^\circ}{\sqrt{R^2 + (\omega L)^2}} e^{-j \tan^{-1}(\frac{\omega L}{R})}$$

$$\Rightarrow I = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \angle \phi - \tan^{-1}\left(\frac{\omega L}{R}\right) - 90^\circ$$

$$= \alpha \angle \beta = \alpha e^{j\beta}$$

$$i(t) = R \cdot P [I \cdot e^{j\omega t}] \text{ Amperes}$$

$$= \alpha \cos(\omega t + \beta)$$

$$= \alpha \cos(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} - 90^\circ)$$

$$= \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}) \text{ Amp}$$

$$= i_{ss}(t)$$

Method (2) : By L.T.A.

$$v(t) = V_m \sin(\omega t + \phi)$$

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \frac{1}{Z(s)} = \frac{1}{R + sL}$$

$$H(j\omega) = \frac{1}{R + j\omega L}$$

$$= \frac{1}{\sqrt{R^2 + (\omega L)^2}} \angle -j\arctan \frac{\omega L}{R}$$

$$\Rightarrow I(s) = H(s) \cdot V(s)$$

$$i(t) = \frac{1}{\sqrt{R^2 + (\omega L)^2}} V_m \sin\left(\omega t + \phi - \arctan \frac{\omega L}{R}\right) \text{Amp}$$

$$= i_{ss}(t)$$

$$i(t) = i_{tr}(t) + i_{ss}(t)$$

$$= K e^{-Rt/L} + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin\left(\omega t + \phi - \arctan \frac{\omega L}{R}\right)$$

$$i(0^-) = 0A = i(0^+)$$

$$\Rightarrow \theta = k e^{-\theta} + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\phi - \tan^{-1} \frac{\omega L}{R})$$

$$\Rightarrow k = \frac{-V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\phi - \tan^{-1} \frac{\omega L}{R}) \ll 1$$

As $k \ll 1$, the transient effects are less severe for AC.

$$v_L(t) = L \frac{di(t)}{dt} \quad \text{By Ohm's law.}$$

$$\text{Suppose } \phi - \tan^{-1} \frac{\omega L}{R} = 0 \Rightarrow k = 0$$

$$\Rightarrow i_{tr}(t) = 0 \rightarrow i(t) = i_{ss}(t)$$

i.e. A transient free response

So, condition for transient-free response at $t=0$ is

$$\boxed{\phi = \tan^{-1} \frac{\omega L}{R}}$$

$$\text{i.e. } \left. \omega t + \phi \right|_{t=0} = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

Note:

→ If the total phase of excitation at the time of switching is equal to $\tan^{-1} \left(\frac{\omega L}{R} \right)$ then no transient will result in the system at the time of switching for sinusoidal excitation.

→ IF the switch is closed at ~~t = 0~~, $t = t_0$ then the condition for the transient free response at $t = t_0$ is

$$\omega t_0 + \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

→ IF the excitation is $v(t) = V_m \cos(\omega t + \phi)$ then the sine is replaced by cosine in the steady state response and hence 'k' is a function of cosine.

→ Suppose $\phi - \tan^{-1} \frac{\omega L}{R} = \frac{\pi}{2}$

$$\Rightarrow k = 0 \Rightarrow i_{ss}(t) = 0$$

$$\Rightarrow i(t) = i_{ss}(t)$$

i.e. A transient-free response


$$\phi - \tan^{-1} \left(\frac{\omega L}{R} \right) + \frac{\pi}{2} \text{ at } t=0$$

$$\omega t_0 + \phi = \tan^{-1} \left(\frac{\omega L}{R} \right) + \frac{\pi}{2} \text{ at } t=t_0$$

In the above cases if 'L' is replaced by 'C' then $\tau = \frac{L}{R}$ should be replaced by

$$\tau = R C$$

Parallel RL Circuit :-

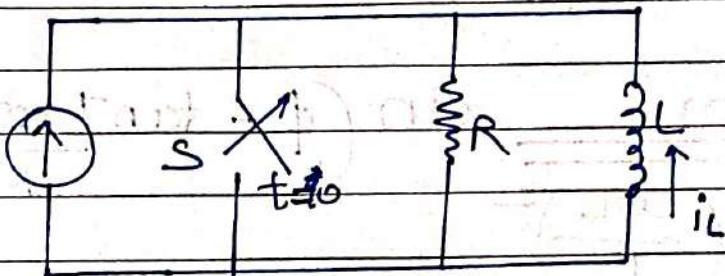

$i_{Lss}(t)$ by LTA :-

$$\frac{I_L(s)}{I(s)} = H(s) = \frac{\text{desired L.T}}{\text{'excitation LT'}}$$

$$I_L(s) = \frac{I(s) \cdot R}{R + sL}$$

(By current division in s-domain)

$$\frac{I_L(s)}{I(s)} = H(s) = \frac{R}{R + sL}$$

$$H(j\omega) = \frac{1}{1 + \frac{j\omega L}{R}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} e^{-j\arctan\left(\frac{\omega L}{R}\right)}$$

$$i_L(t) = i_{L_{tr}}(t) + i_{L_{ss}}(t)$$

$$= Ke^{-Ryt} + \frac{Im}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \sin(\omega t + \phi - \arctan\left(\frac{\omega L}{R}\right))$$

$$i_L(0^-) = 0 = i_L(0^+)$$

$$K = \frac{-Im}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \sin\left(\phi - \arctan\left(\frac{\omega L}{R}\right)\right) \ll 1$$

$$v_L(t) = L \frac{di_L(t)}{dt} \quad \text{By Ohm's Law}$$

$$\text{Suppose } \phi - \arctan\left(\frac{\omega L}{R}\right) = 0$$

$$\Rightarrow K = 0 \Rightarrow i_{L_{tr}}(t) = 0$$

$$\Rightarrow i_L(t) = i_{L_{ss}}(t)$$

i.e. A transient-free response.

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) \text{ at } t=0$$

$$\omega t_0 + \phi = \tan^{-1} \frac{\omega L}{R} \text{ at } t=t_0$$

(Same as series RL circuit)

If $i(t) = I_m \cos(\omega t + \phi)$, then

$$\phi = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2} \text{ at } t=0$$

$$\omega t_0 + \phi = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2} \text{ at } t=t_0$$

In the above cases if 'L' is replaced by 'C' - the $\tau = \frac{L}{R}$ should be replaced by

$$\tau = RC.$$

Note :- Transient free condition is not possible for network with both the energy storing elements. i.e. for RLC networks.

Reason :- $s_1, s_2 = \alpha \pm j\beta$

$$i(t) = i_{fr}(t) + i_{ss}(t)$$

$$= e^{\alpha t} (K_1 \cos \beta t + K_2 \sin \beta t) + i_{ss}(t)$$


Here by applying initial conditions $i_L(0^+)$ and $v_C(0^+)$, k_1 is a function of sine and k_2 is a function of cosine (vice versa), hence no time will satisfy both $k_1 = k_2 = 0$ simultaneously to zero and so the transient term is always present in the complete response.

Observation :-

So, -the transient -free time (to value) in R and RC circuits with AC excitations will depend on the source frequency (ω), its initial phase (ϕ), on the circuit constants (R, L, C) and on the nature of the excitation (sine or cosine), but not on the maximum value of -the excitation (V_m or I_m).

Practice Problem :-

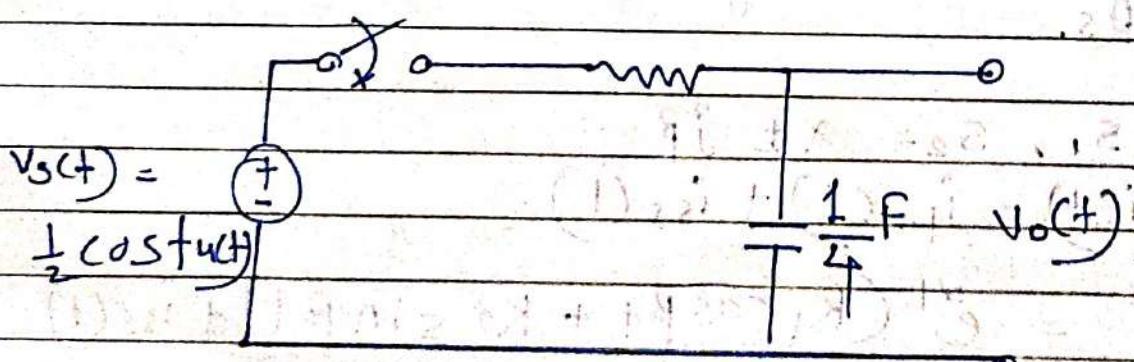For the network shown in fig find the response $v_o(t)$



Laplace transform of some elementary functions.

The direct application of the definition gives the following formulae.

$$\textcircled{1} \quad L\{k\} = \frac{k}{s} \quad s > 0$$

$$\textcircled{2} \quad L\{e^{at}\} = \frac{1}{s-a} \quad s > a$$

$$\textcircled{3} \quad L\{e^{-at}\} = \frac{1}{s+a} \quad s > -a$$

$$\textcircled{4} \quad L\{\sin at\} = \frac{a}{s^2 + a^2} \quad s > 0$$

$$\textcircled{5} \quad L\{\cos at\} = \frac{s}{s^2 + a^2} \quad s > 0$$

$$\textcircled{6} \quad L\{\sinh at\} = \frac{a}{s^2 - a^2} \quad s > |a|$$

$$\textcircled{7} \quad L\{\cosh at\} = \frac{s}{s^2 - a^2} \quad s > |a|$$


$$\textcircled{8} \quad L\{t^n\} = \frac{\Gamma(n+1)}{s^{n+1}} \quad (n > -1)$$

$\frac{n!}{s^{n+1}}$, where $n \in \mathbb{N}$
 $\frac{n^n}{s^{n+1}} \quad (n \notin \mathbb{Z})$

AC Circuit Analysis

Sinusoidal voltage signal.
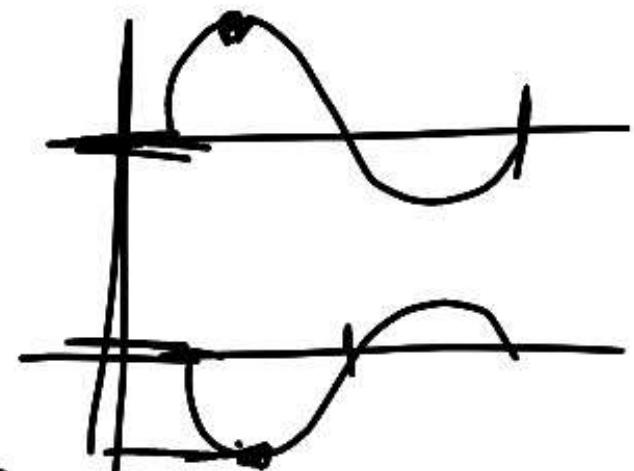
$$\begin{aligned}v &= V_m \sin \omega t \\&= V_m \sin \omega t \\&= V_m \sin 2\pi f t \\&= V_m \sin \frac{2\pi}{T} t\end{aligned}$$




Note: (+) sign. when used in connection with the phase difference denotes lead.

(-) sign means lag.

$$\begin{aligned}V_A &= V_m \sin \omega t \\V_B &= V_m \sin (\omega t + \phi)\end{aligned}\}$$

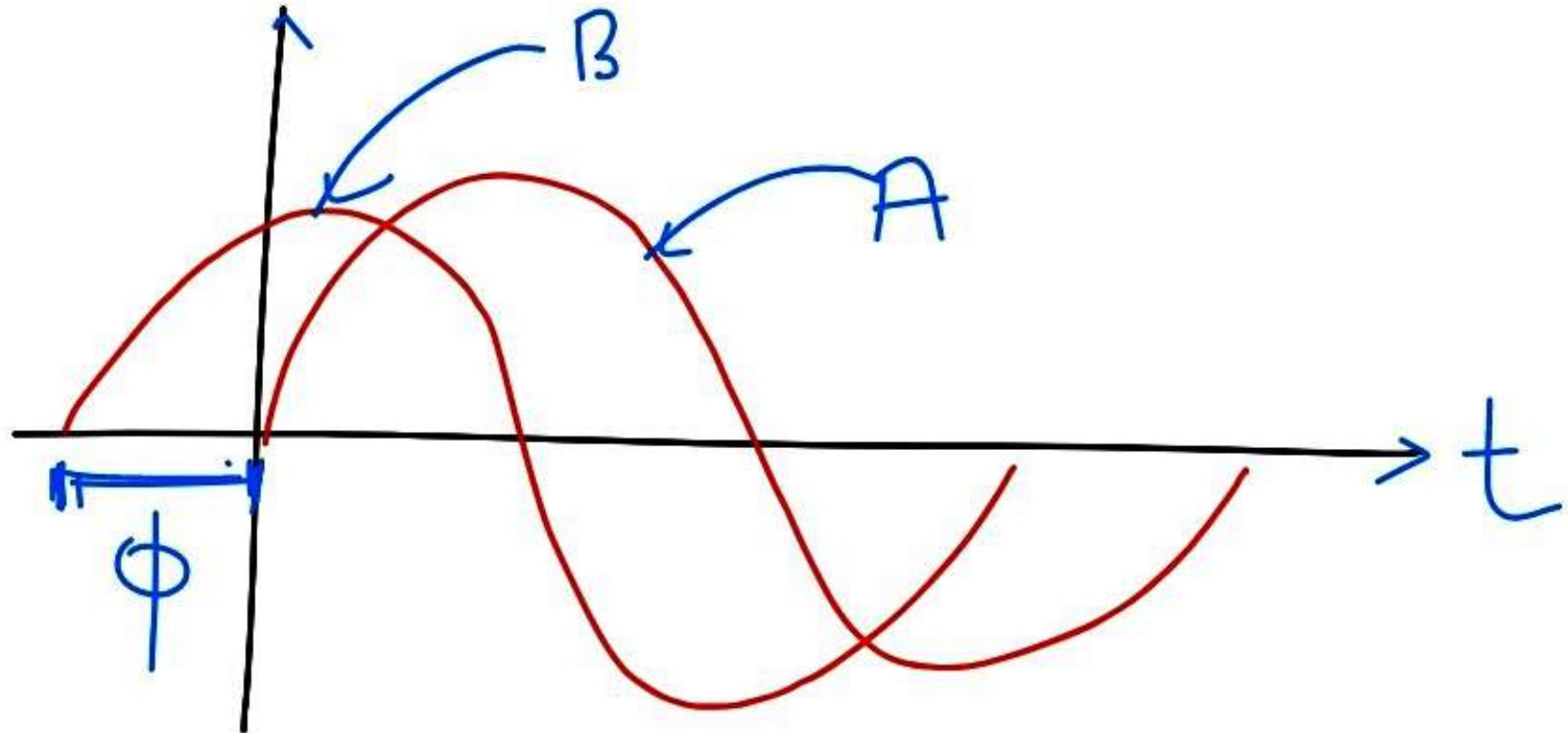\Rightarrow quantity β leads A
by a phase angle ϕ



Let $x(t)$ be the periodic signal
of period T .

then $x(t \pm T) = x(t)$

Average value = DC value.

$$x_{avg} = x_{dc} = \frac{1}{T} \int_0^T x(t) dt$$

= Area of the signal over one period

RMS value = $\bar{x}_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$


3) Peak Factor = $\frac{x(t)_{\max}}{x(t)_{\text{avg.}}}$

$$= \frac{x_{\max}}{x_{\text{Avg.}}}$$

$$(4) \underline{\text{form factor}} = \frac{x_{\text{rms}}}{x_{\text{avg}}}$$

Note:- The avg. is
Value of sine or cosine
function of any phase & freq.
is zero.

→ And its rms value

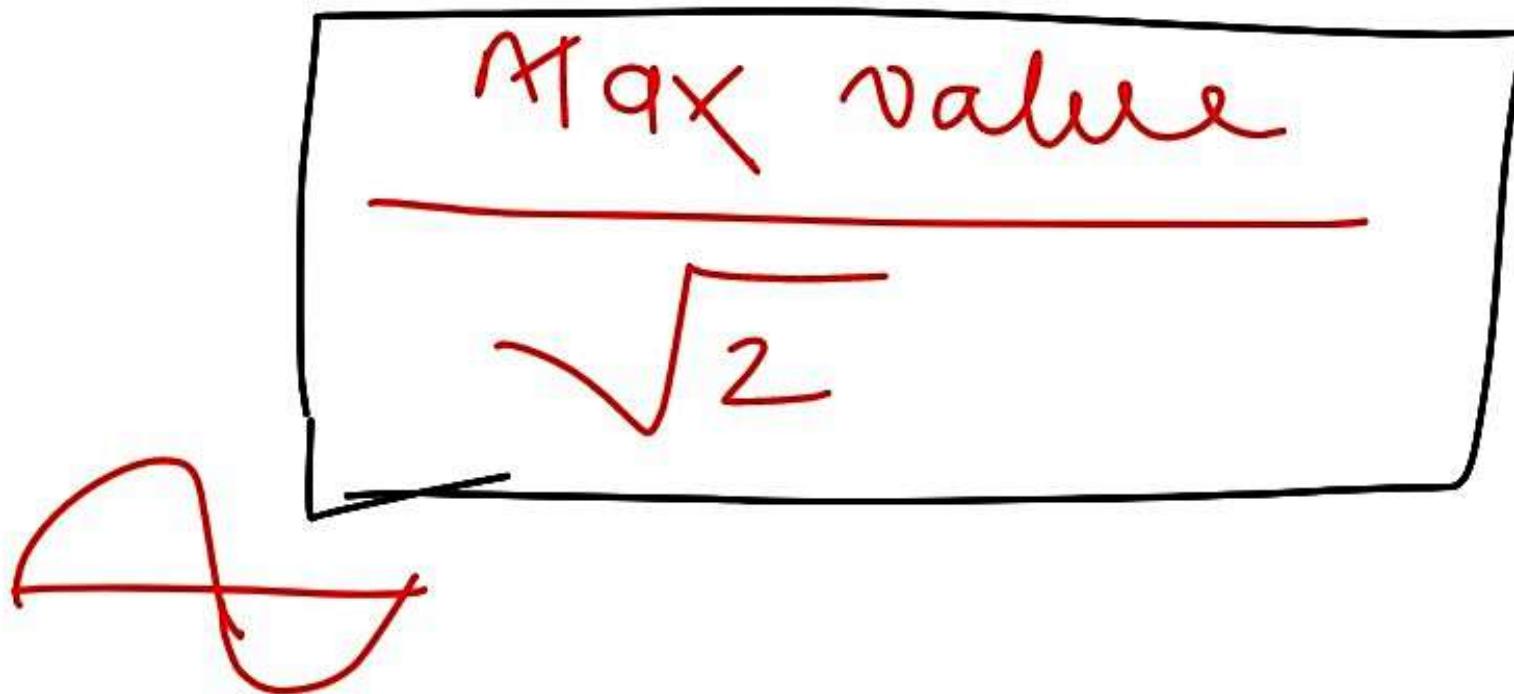


$$f(t) = a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t +$$

$$b_1 \sin \omega t +$$

$$f(t) b_2 \sin 2\omega t + \dots - \dots$$

Range value = $\sqrt{a_0^2 + \frac{1}{2}(a_1^2 + a_2^2 + b_1^2 + b_2^2)}$

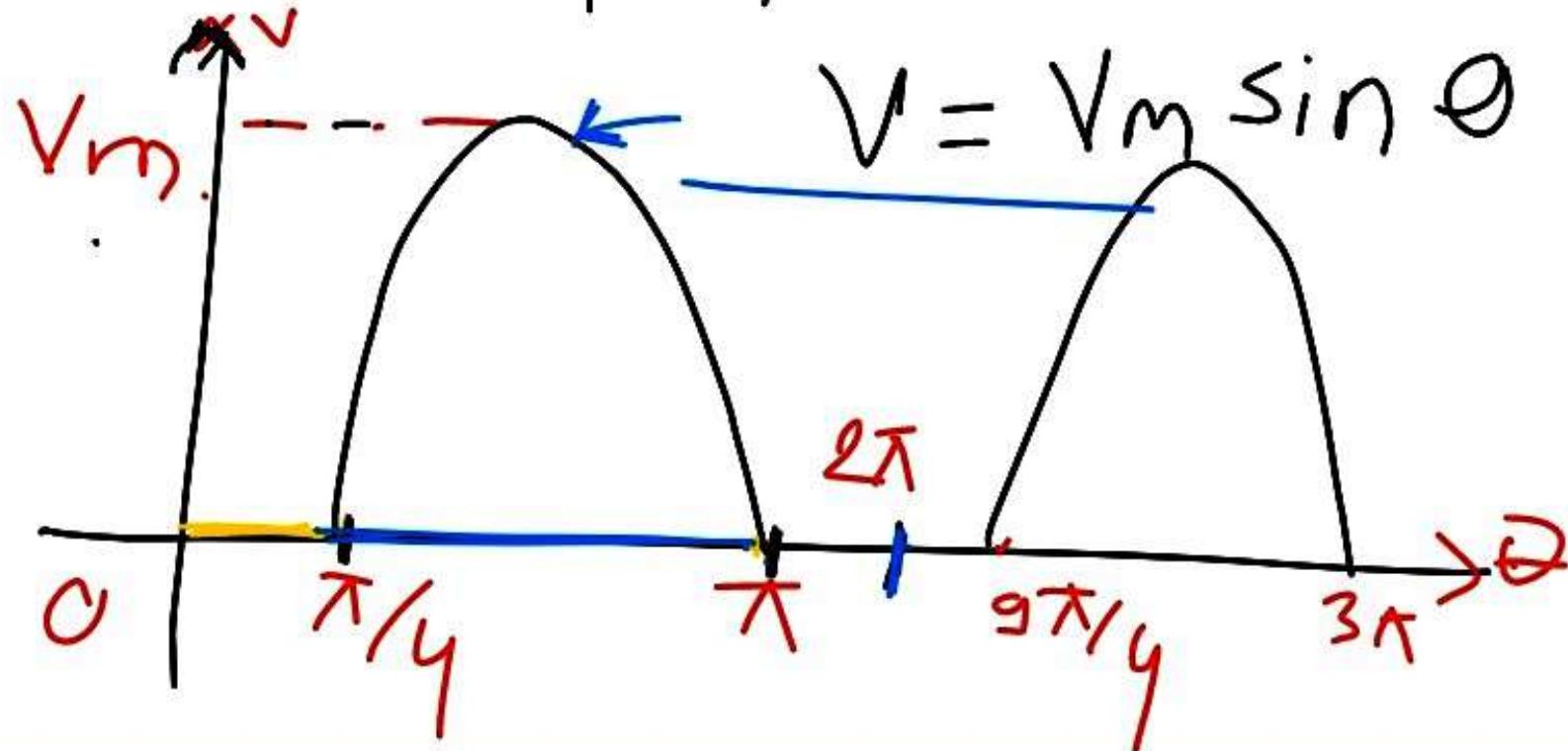Find the avg. value of sine
value of the waveform.



$$V = 0$$

$$= V_m \sin \theta$$

$$= \underline{0}$$

$$\underline{0} < \theta < \pi/4$$

$$\underline{\pi/4} < \theta < \pi$$

$$\pi < \theta < 2\pi$$

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V(\theta) d\theta \quad T = 2\pi$$
$$= \frac{1}{2\pi} \int_{\pi/4}^{\pi} V_m \sin \theta d\theta$$
$$= 4$$

$$\Rightarrow \frac{V_m}{2\pi} (-\cos \psi)^{\star} \pi/4$$

$$\Rightarrow \frac{3}{4} \cdot \frac{V_m}{2\pi}$$

$$\left| \begin{aligned} & \frac{V_m}{2\pi} \times (1 + 0.707) \\ & = 0.272 V_m \\ & \underline{\underline{Y_{avg}}} \end{aligned} \right.$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2(\theta) d\theta}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \theta d\theta}$$

=

$$\sqrt{\frac{V_m^2}{2\pi} \int_{\pi/4}^{\pi} \sin^2 \theta d\theta}$$


$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\pi/4}^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta}$$

$$\begin{aligned}
 & \sqrt{\frac{Nm^2}{2\pi} \left(\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right)^\star} \\
 &= \sqrt{\frac{Nm^2}{2\pi} \left(\frac{\pi}{2} - \frac{\sin 2\pi}{4} - \frac{\pi}{8} + \frac{\sin \pi}{4} \right)}
 \end{aligned}$$

$$\sqrt{0.227 V_m^2}$$

$$= 0.476 V_m.$$

$$\boxed{V_{rms} = 0.476 V_m.}$$

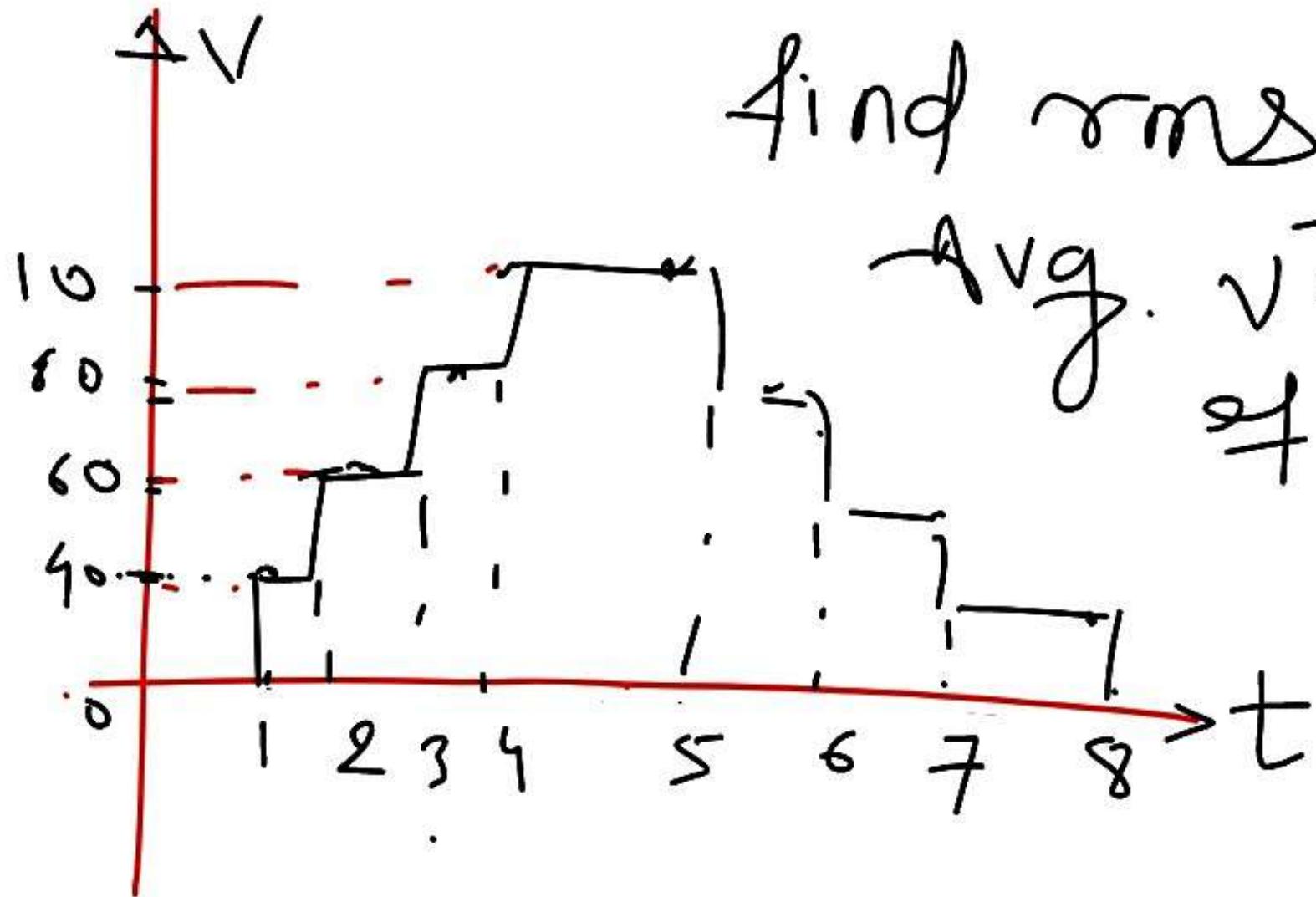

find rms &
Avg. value
of wave
form.


$$\bar{V}_{avg} = \frac{0 + 40 + 60 + 80 + 100 + 80 + 60 + 40}{8}$$

$\Rightarrow 57.5 \text{ V}$


$$V_{rms} = \sqrt{\frac{0^2 + 40^2 + 60^2 + 80^2 + 100^2 + 80^2 + 60^2 + 40^2}{8}}$$

$\Rightarrow 64.42 \text{ V}$

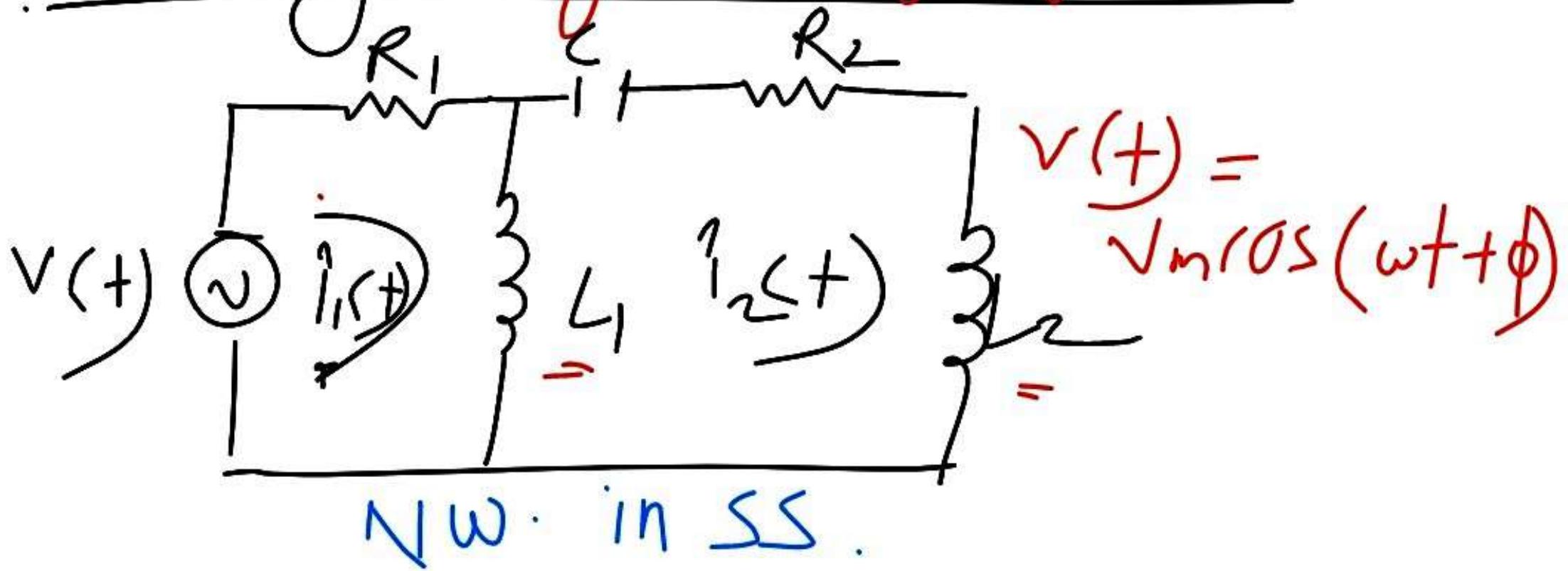(e) Sinusoidal Steady state
Analysis By using Phasor.



Transform \rightarrow phasor form

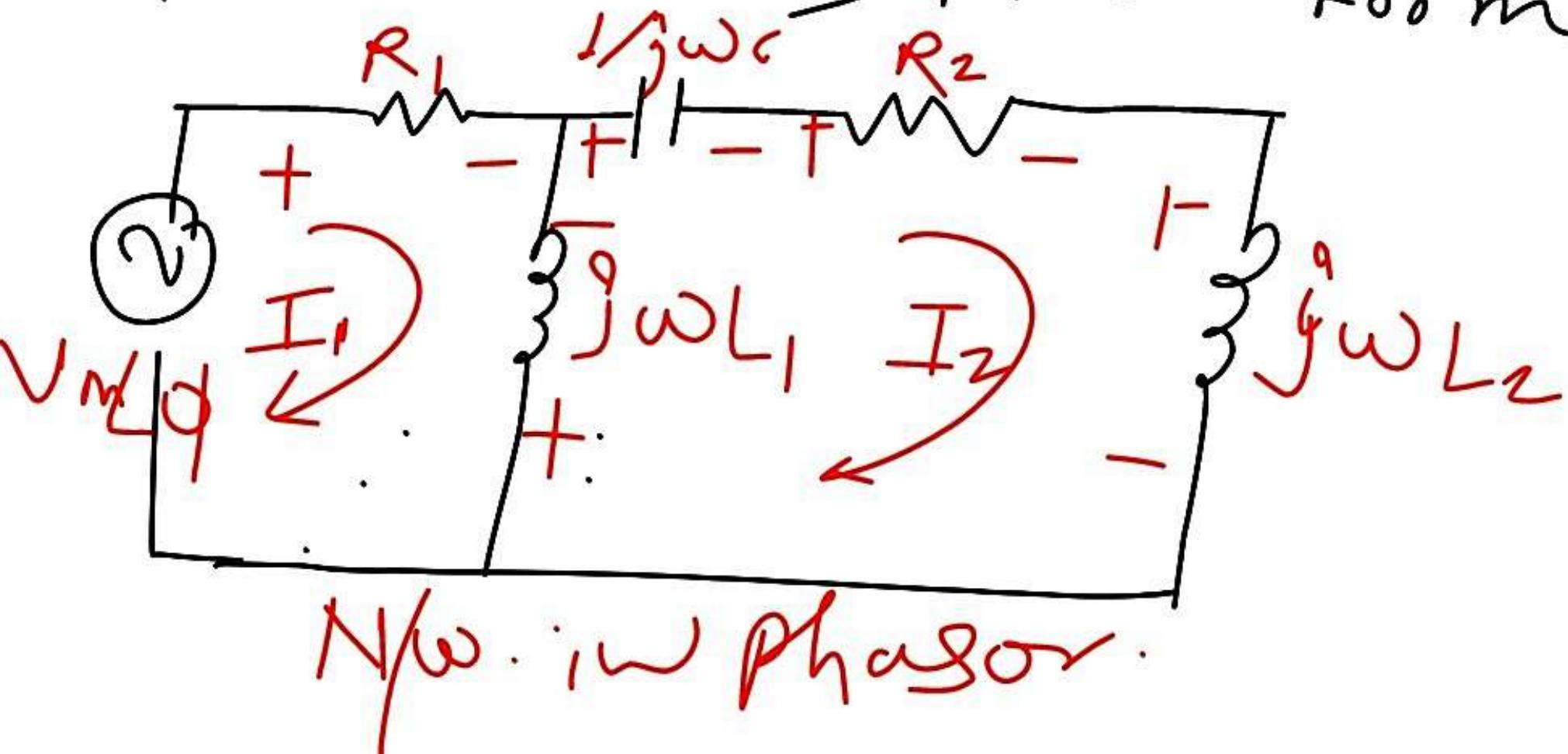

$$V = \angle I$$


By KVL

$$\Rightarrow V_m \angle \phi - R_1 I_1 - j \omega L (I_1 - I_2) = 0$$

$$\Rightarrow \frac{-1}{j \omega C} I_2 - R_2 I_2 - j \omega L_2 I_2 - j \omega L (I_2 - I_1) = 0$$

$$I_1 = \frac{\Delta I}{\Delta} \mid i_1(t) =$$
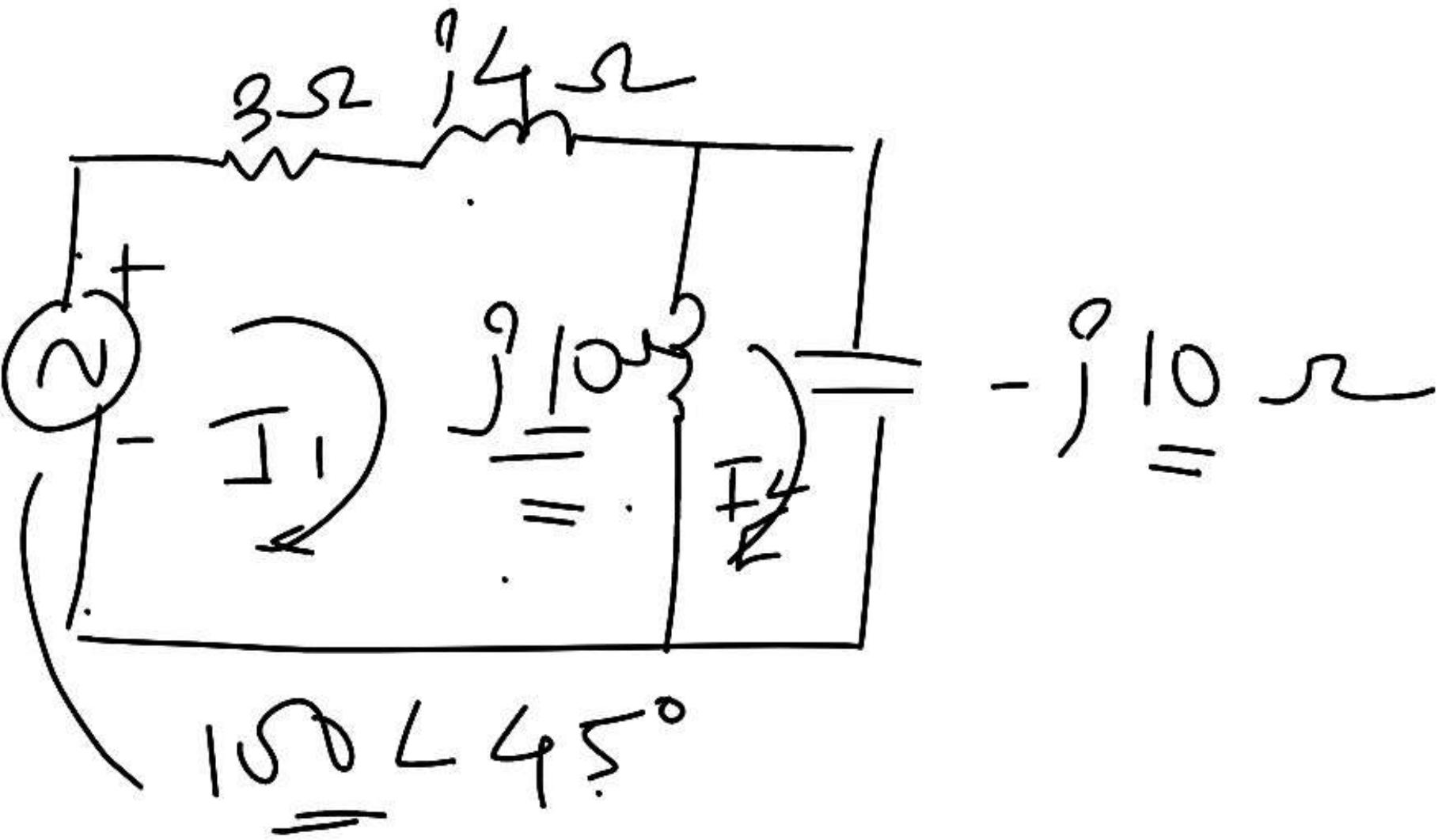
$$I_2 = \frac{\Delta I_2}{\Delta} \mid i_2(t)$$



\Rightarrow for mesh ①

$$\Rightarrow 100 \angle 45^\circ - (3 + j4) I_1 - j_{10}(I_1 - I_2)$$

$$(3 + j4) I_1 - j_{10} I_2 = 100 \angle 45^\circ$$

↙ - ①

Mesh ②

$$\Rightarrow -j10(I_2 - I_1) + j10I_2 = 0$$

$$j10I_1 = 0 \quad | \text{ substitute}$$

$$I_1 = 0$$

in ①

$$I_1 = 0$$

$$-j10I_2 = 100 \angle 45^\circ$$


$$I_2 = \frac{100 \angle 45}{10 \angle -90}$$

$$\boxed{I_2 = 10 \angle 135^\circ \text{ Amp.}}$$

AC Circuit Analysis

Sinusoidal voltage signal.
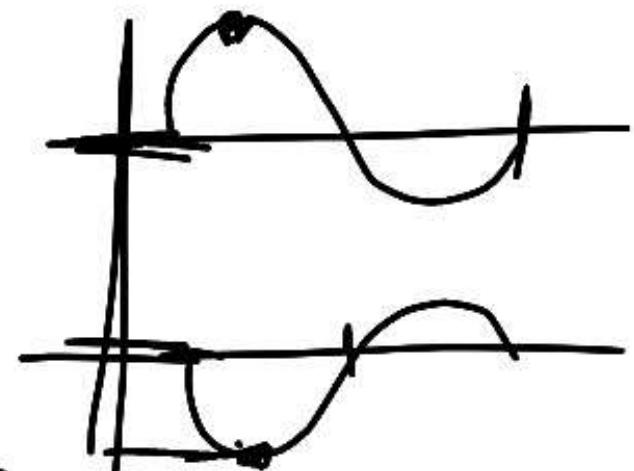
$$\begin{aligned}v &= V_m \sin \omega t \\&= V_m \sin \omega t \\&= V_m \sin 2\pi f t \\&= V_m \sin \frac{2\pi}{T} t\end{aligned}$$




Note: (+) sign when used in connection with the phase difference denotes lead.

(-) sign means lag.

$$\begin{aligned}V_A &= V_m \sin \omega t \\V_B &= V_m \sin (\omega t + \phi)\end{aligned}\}$$

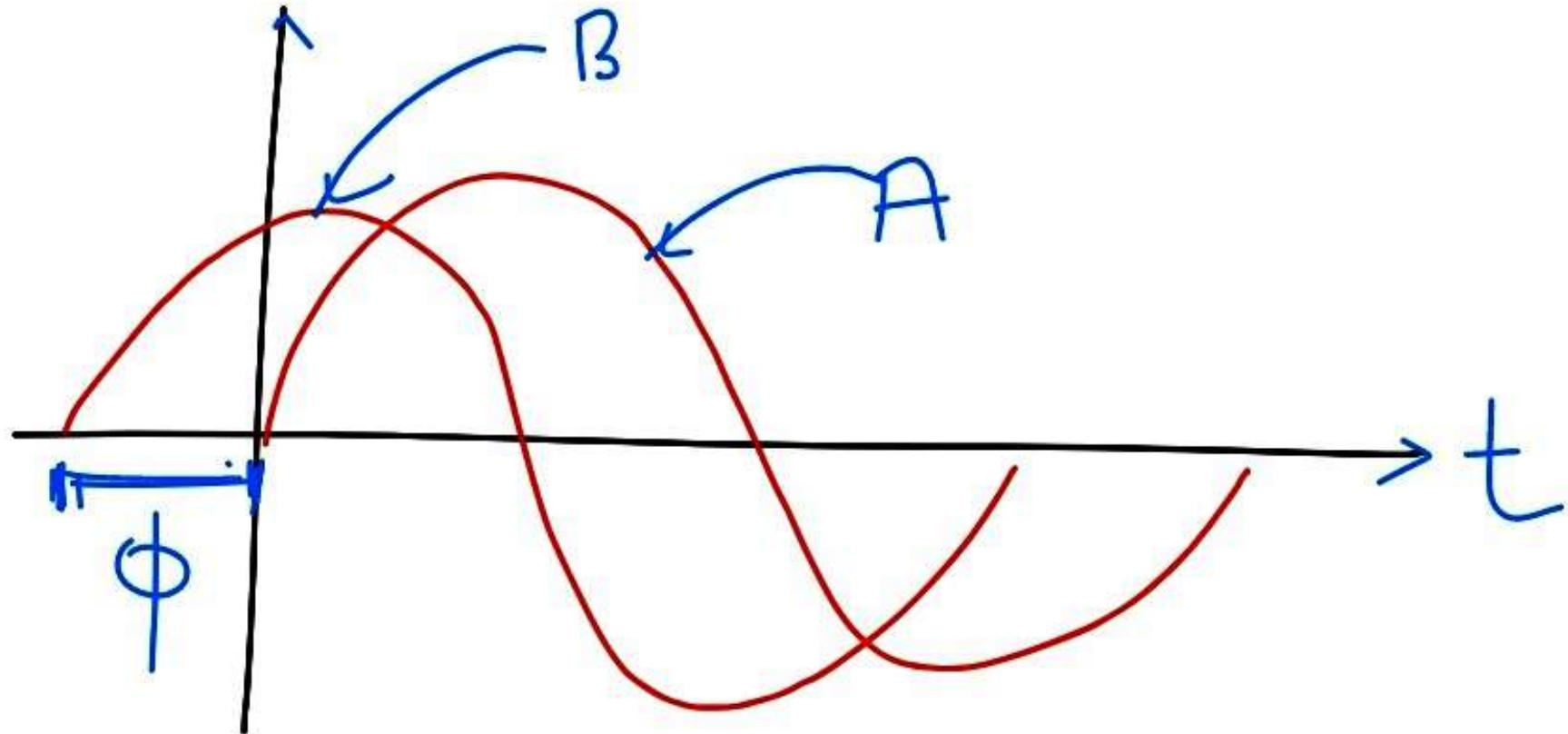\Rightarrow quantity β leads A
by a phase angle ϕ



Let $x(t)$ be the periodic signal
of period T .

then $x(t \pm T) = x(t)$

Average value = DC value.

$$x_{avg} = x_{dc} = \frac{1}{T} \int_0^T x(t) dt$$

= Area of the signal over one period

RMS value = $\bar{x}_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$


3) Peak Factor = $\frac{x(t)_{\max}}{x(t)_{\text{avg.}}}$

$$= \frac{x_{\max}}{x_{\text{Avg.}}}$$

$$(4) \underline{\text{form factor}} = \frac{x_{\text{rms}}}{x_{\text{avg}}}$$

Note:- The avg. is
Value of sine or cosine
function of any phase & freq.
is zero.

→ And its rms value

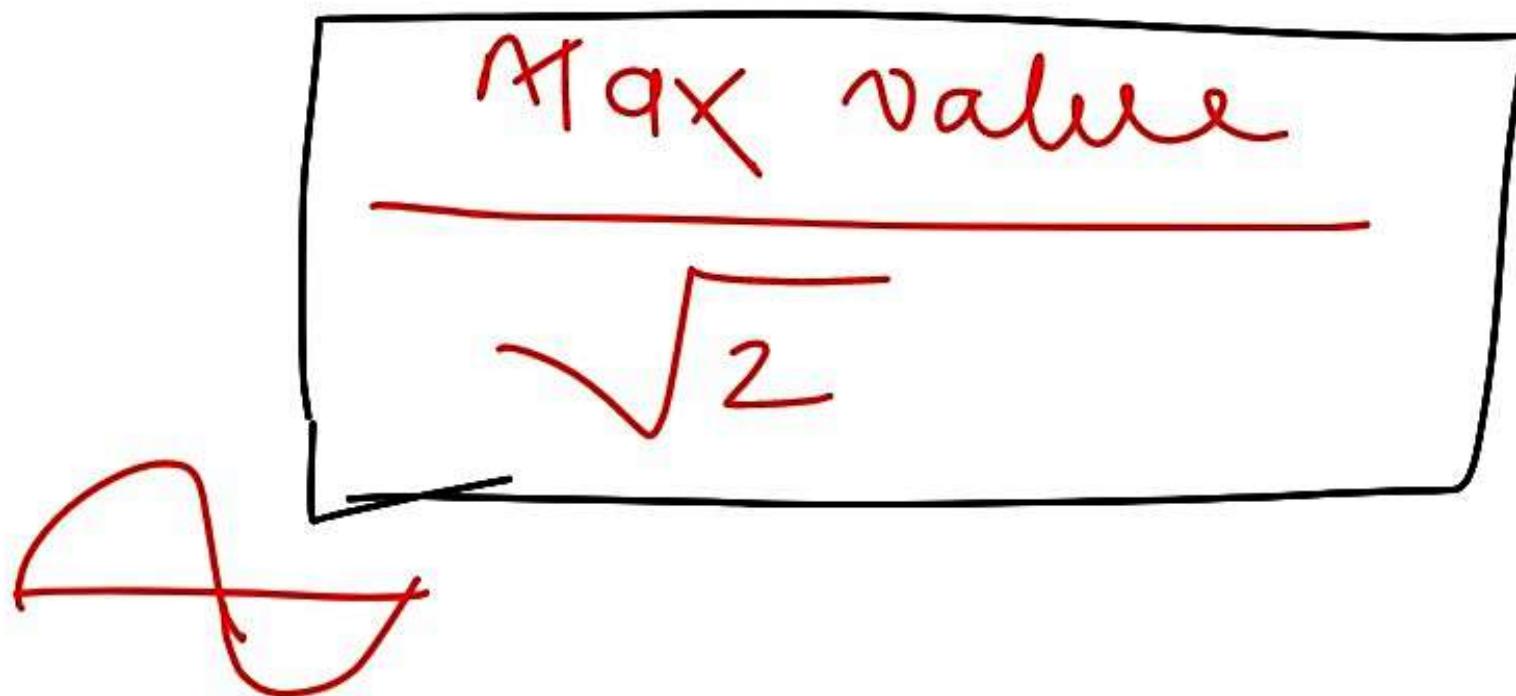


$$f(t) = a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t +$$

$$b_1 \sin \omega t +$$

$$f(t) \quad b_2 \sin 2\omega t + \dots - \dots$$

Range value = $\sqrt{a_0^2 + \frac{1}{2}(a_1^2 + a_2^2 + b_1^2 + b_2^2)}$

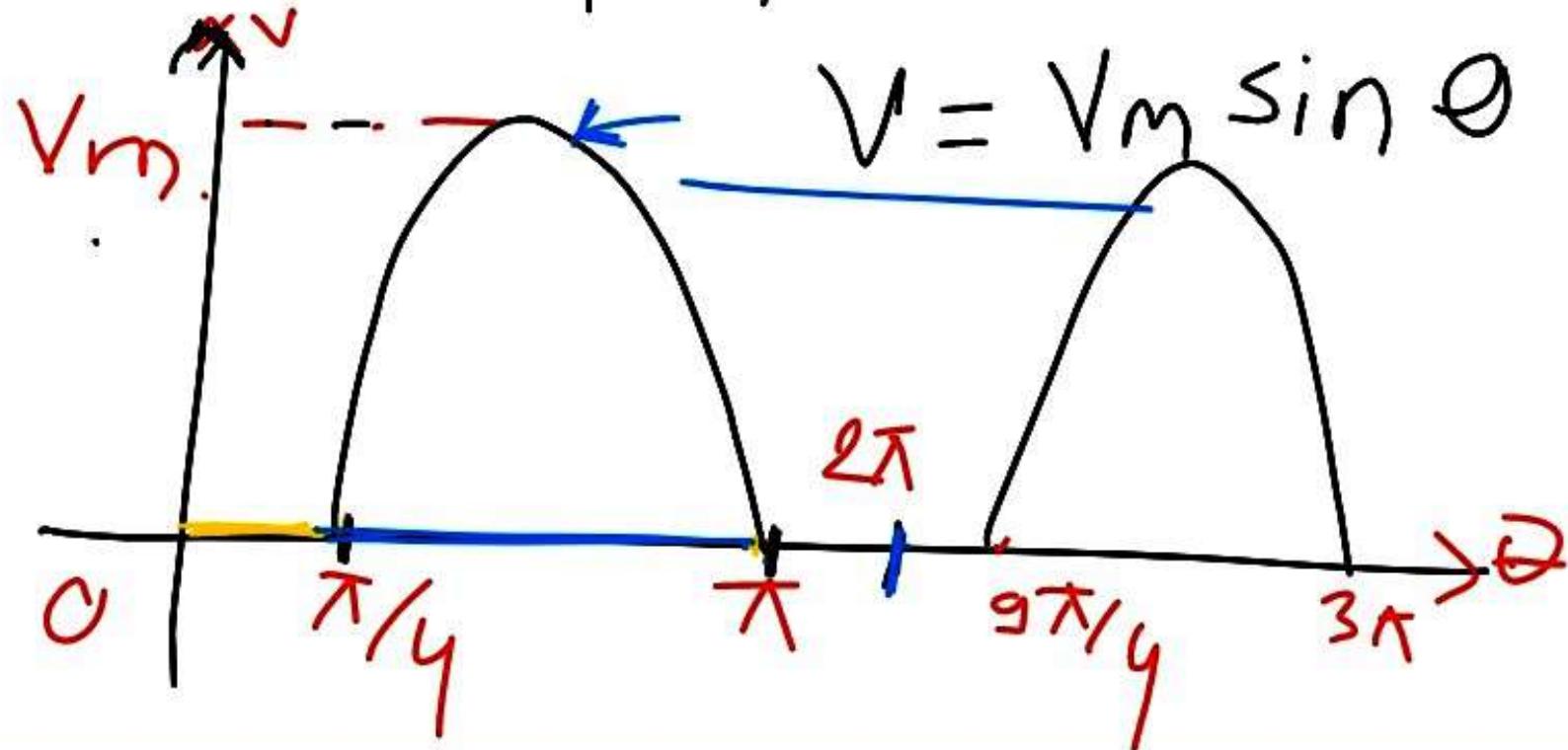Find the avg. value of sine value of the waveform.



$$V = 0$$

$$= V_m \sin \theta$$

$$= \underline{0}$$

$$\begin{array}{c} 0 < \theta < \pi/4 \\ \hline \pi/4 < \theta < \pi \\ \hline \pi < \theta < 2\pi \end{array}$$

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V(\theta) d\theta \quad T = 2\pi$$
$$= \frac{1}{2\pi} \int_{\pi/4}^{\pi} V_m \sin \theta d\theta$$
$$= 4$$

$$\Rightarrow \frac{V_m}{2\pi} (-\cos \psi)^{\star} \pi/4$$

$$\Rightarrow \frac{3}{4} \cdot \frac{V_m}{2\pi}$$

$$\left| \begin{aligned} & \frac{V_m}{2\pi} \times (1 + 0.707) \\ & = 0.272 V_m \\ & \underline{\underline{Y_{avg}}} \end{aligned} \right.$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2(\theta) d\theta}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \theta d\theta}$$

=

$$\sqrt{\frac{V_m^2}{2\pi} \int_{\pi/4}^{\pi} \sin^2 \theta d\theta}$$


$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\pi/4}^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta}$$

$$\begin{aligned}
 & \sqrt{\frac{Nm^2}{2\pi} \left(\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right)^\star} \\
 &= \sqrt{\frac{Nm^2}{2\pi} \left(\frac{\pi}{2} - \frac{\sin 2\pi}{4} - \frac{\pi}{8} + \frac{\sin \pi}{4} \right)}
 \end{aligned}$$

$$\sqrt{0.227 V_m^2}$$

$$= 0.476 V_m.$$

$$\boxed{V_{rms} = 0.476 V_m.}$$

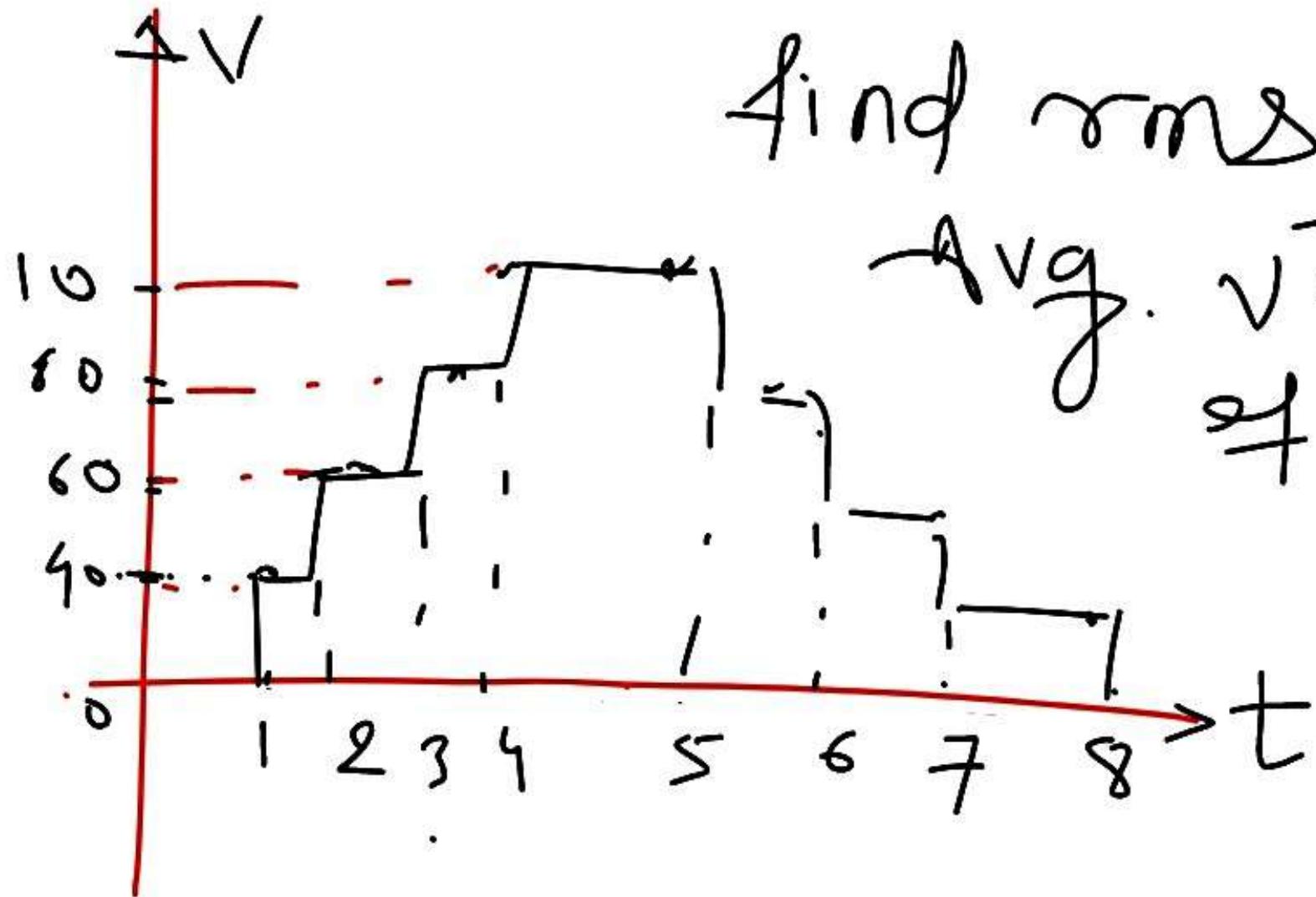

find rms &
Avg. value
of wave
form.


$$\bar{V}_{avg} = \frac{0 + 40 + 60 + 80 + 100 + 80 + 60 + 40}{8}$$

$$\Rightarrow \underline{57.5 \text{ V}}$$


$$V_{rms} = \sqrt{\frac{0^2 + 40^2 + 60^2 + 80^2 + 100^2 + 80^2 + 60^2 + 40^2}{8}}$$

$$\Rightarrow \underline{64.42 \text{ V}}$$

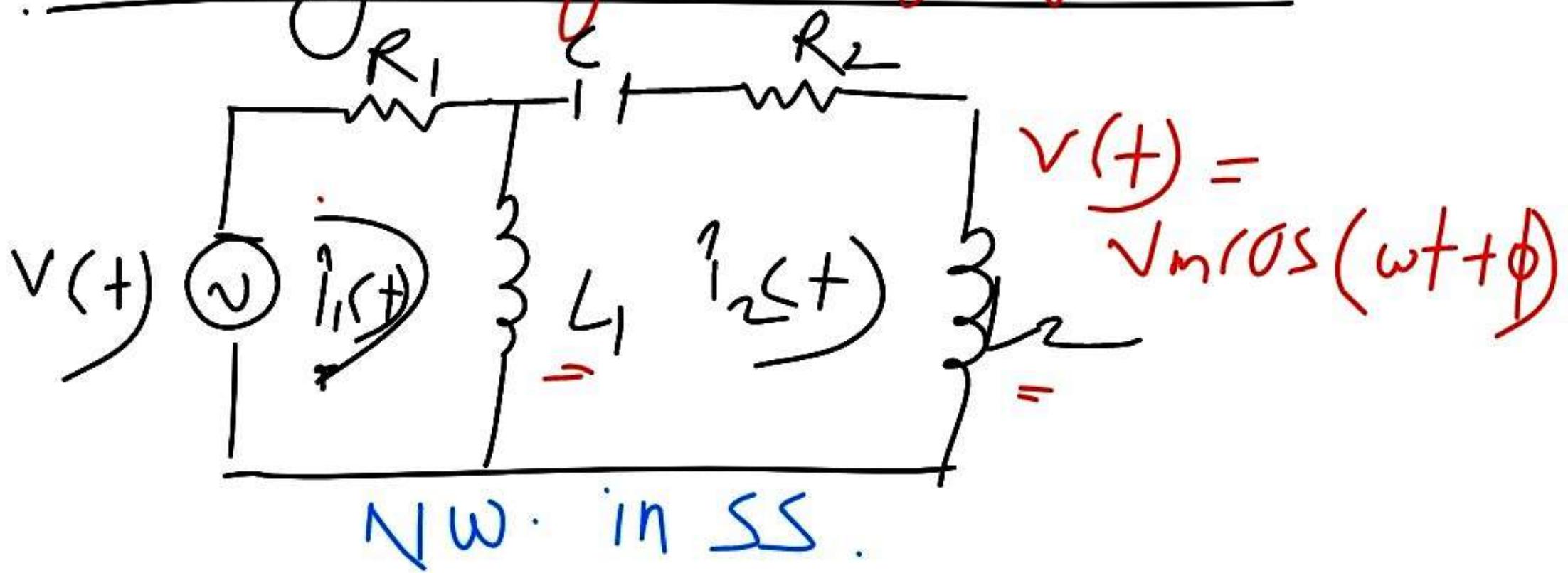(e) Sinusoidal Steady state
Analysis By using Phasor.



Transform \rightarrow phasor form

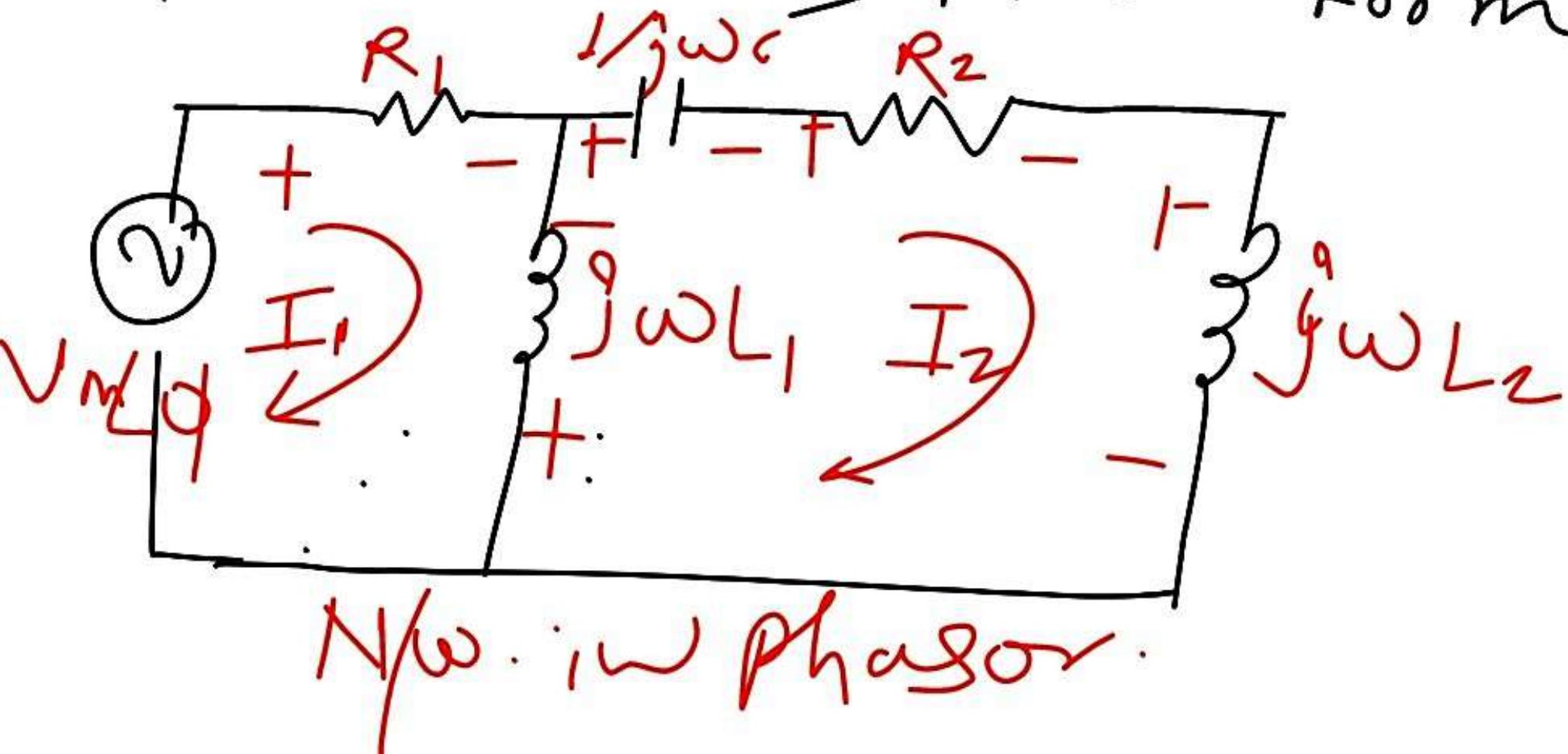

$$V = \angle I$$


By KVL

$$\Rightarrow V_m \angle \phi - R_1 I_1 - j \omega L (I_1 - I_2) = 0$$

$$\Rightarrow \frac{-1}{j \omega C} I_2 - R_2 I_2 - j \omega L_2 I_2 - j \omega L (I_2 - I_1) = 0$$

$$I_1 = \frac{\Delta I}{\Delta} \mid i_1(t) =$$
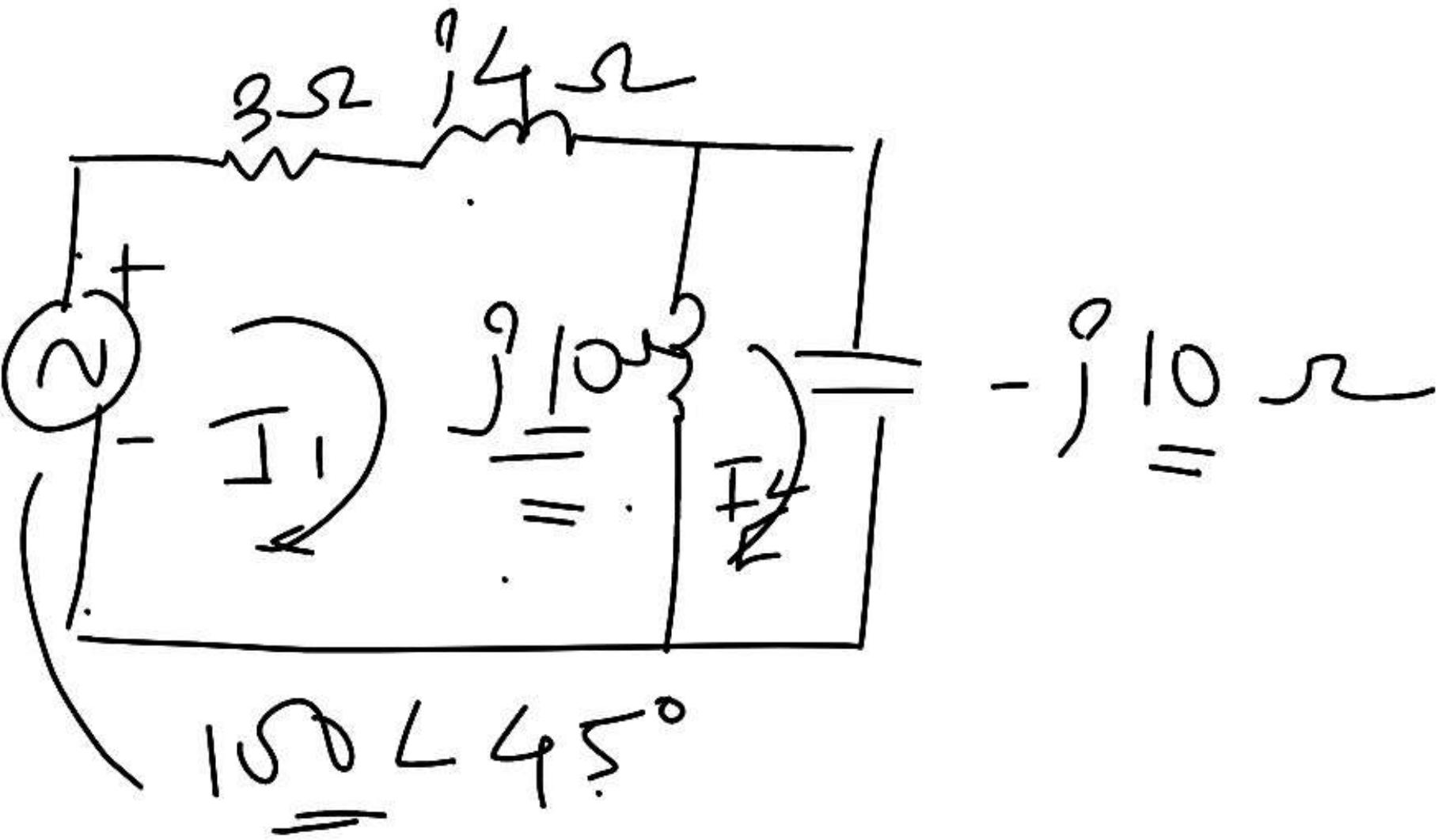
$$I_2 = \frac{\Delta I_2}{\Delta} \mid i_2(t)$$



\Rightarrow for mesh ①

$$\Rightarrow 100 \angle 45^\circ - (3 + j4) I_1 - j_{10}(I_1 - I_2)$$

$$(3 + j4) I_1 - j_{10} I_2 = 100 \angle 45^\circ$$

↙ - ①

Mesh ②

$$\Rightarrow -j10(I_2 - I_1) + j10I_2 = 0$$

$$j10I_1 = 0 \quad | \text{ substitute}$$

$$I_1 = 0$$

in ①


$$I_1 = 0$$


$$-j10I_2 = 100 \angle 45^\circ$$


$$I_2 = \frac{100 \angle 45}{10 \angle -90}$$

$$\boxed{I_2 = 10 \angle 135^\circ \text{ Amp.}}$$

Phasor for 11q RL ckt:

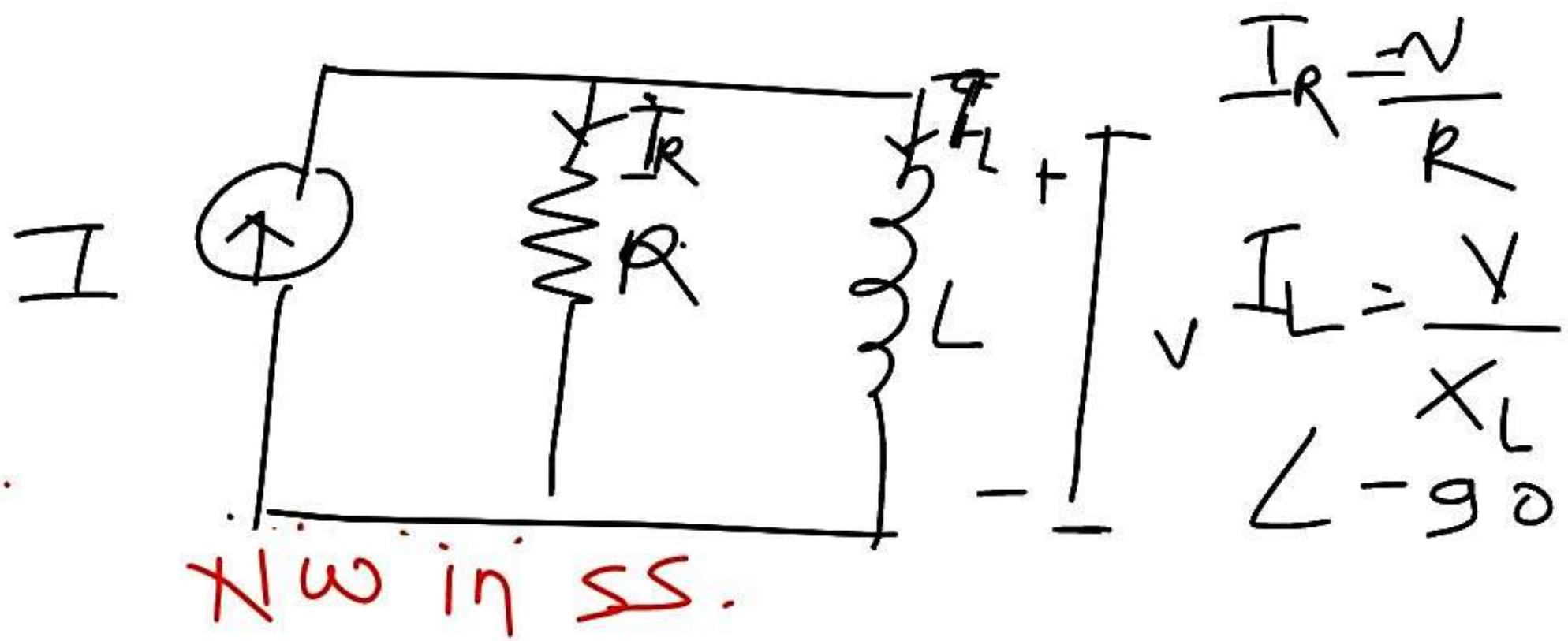

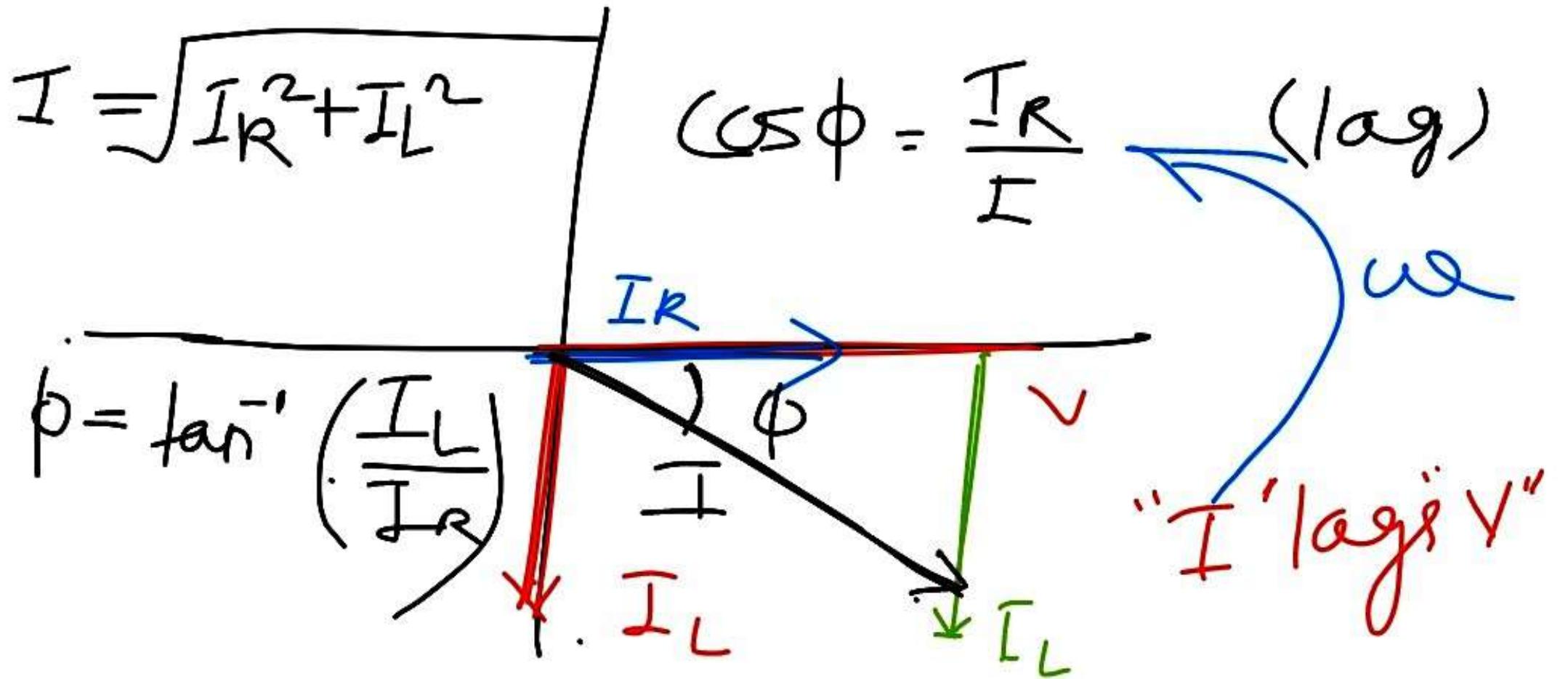

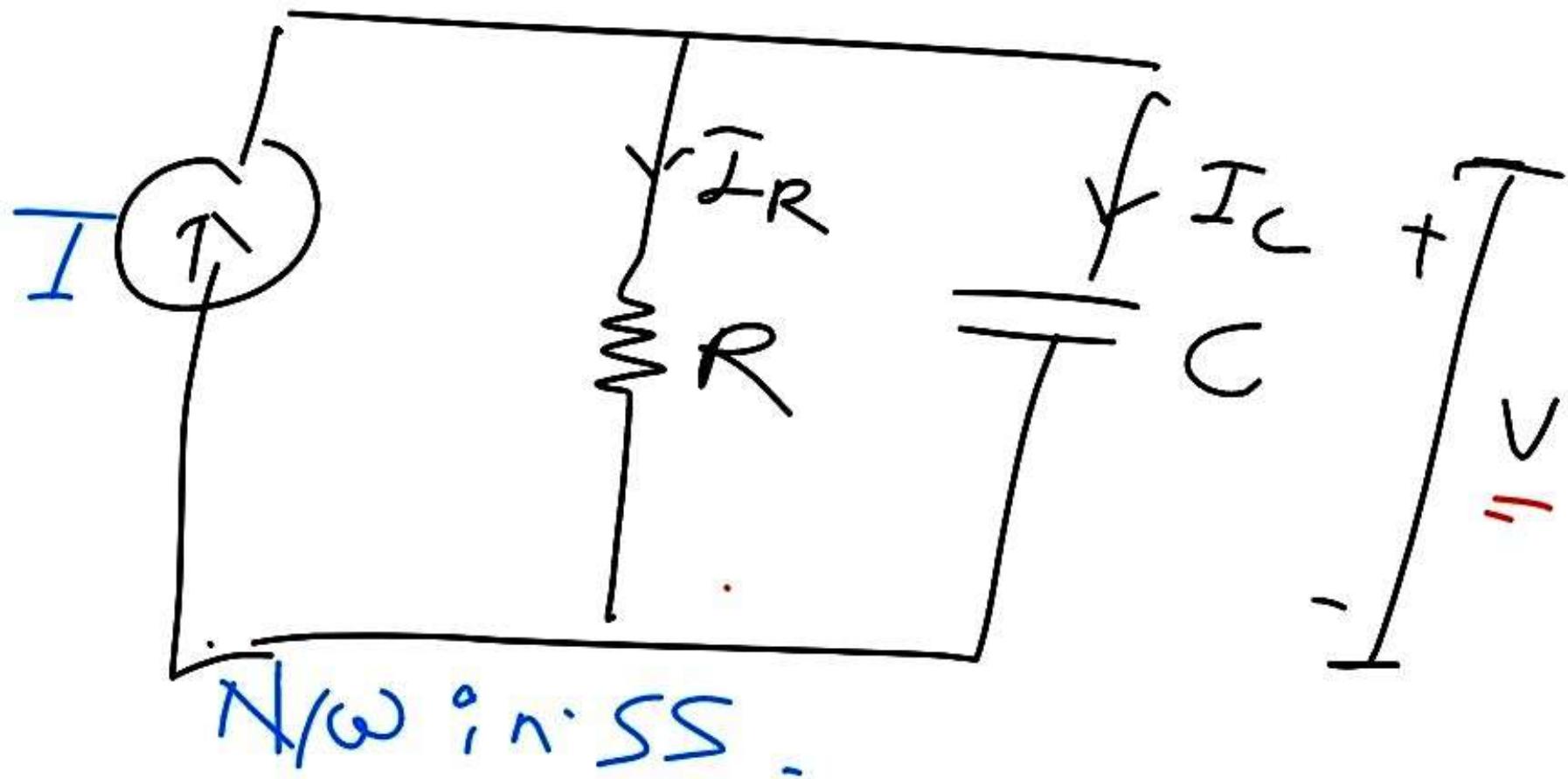


$$I_R = \frac{V}{R} \quad \text{and} \quad I_C = \frac{V}{X_C} \angle 90^\circ$$


$$I = \sqrt{I_R^2 + I_C^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C}{I_R} \right)$$

$$\cos \phi = \frac{I_R}{I}$$

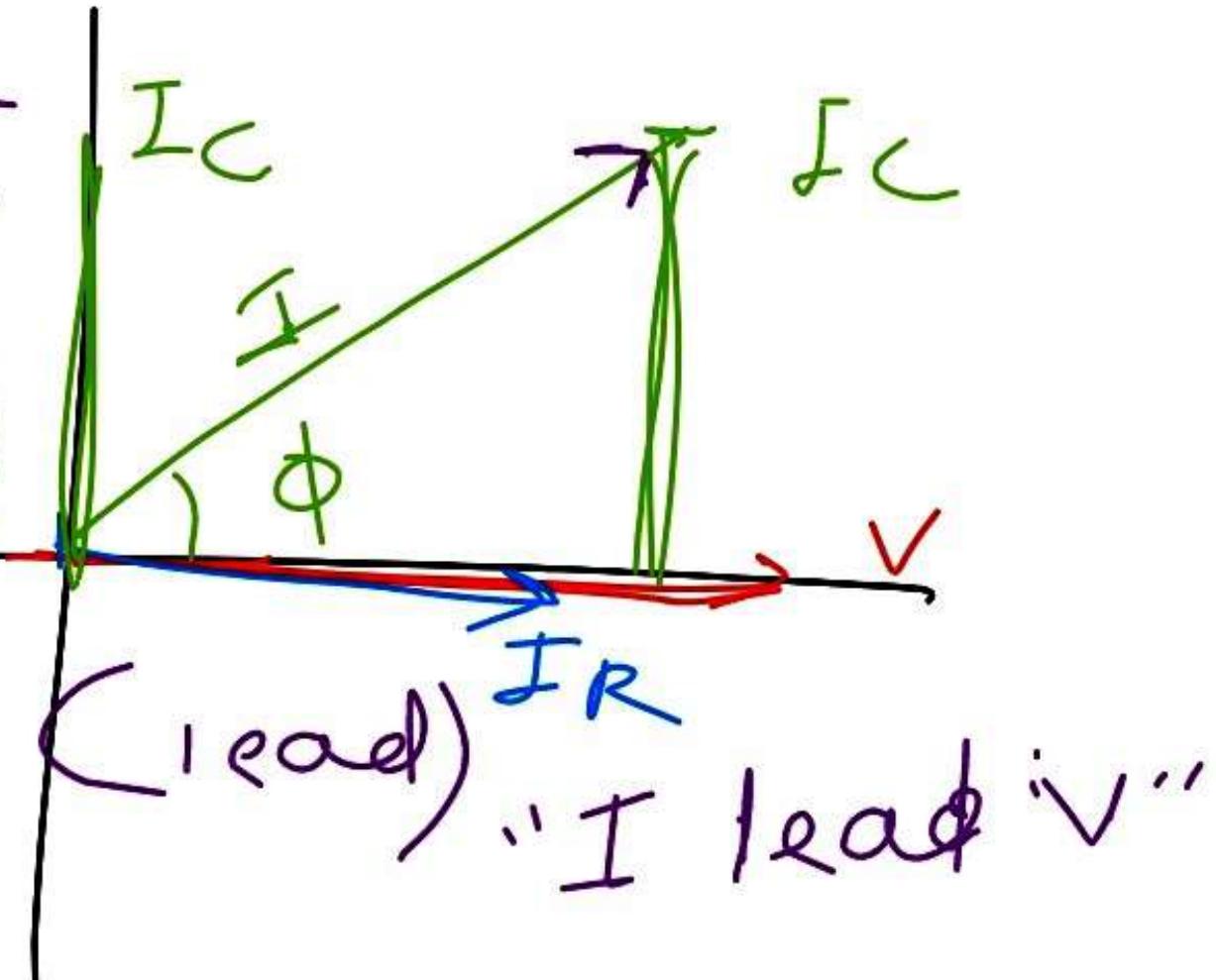

11 el RLC CKT.

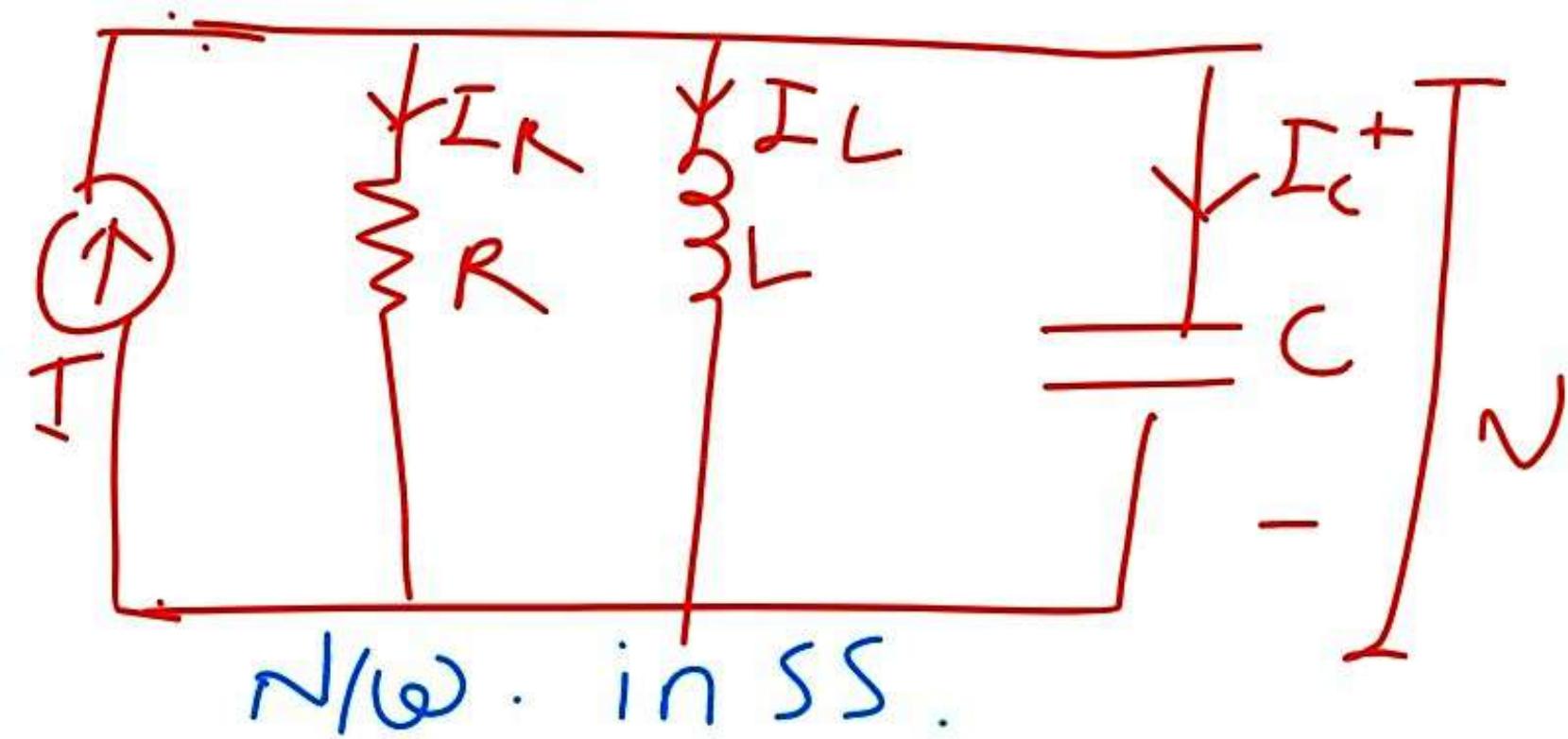

$$I_R = \frac{V}{R}$$


$$I_L = \frac{V}{X_L} \angle -90^\circ$$

$$I_C = \frac{V}{X_C} \angle 90^\circ$$

$$\textcircled{1} \quad I_C > I_L$$

I leads V .

$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$

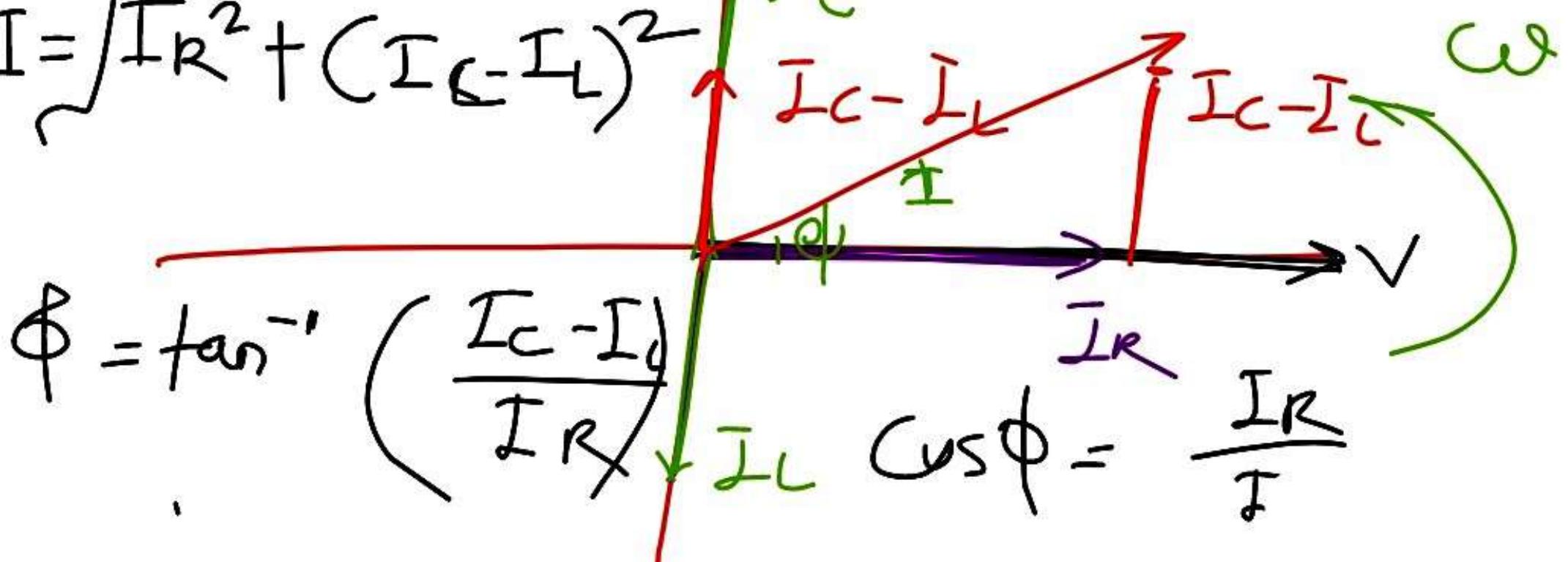

2) $I_L > I_C$

$$I = \sqrt{I_R^2 + (I_E - I_C)^2}$$

I_C

$$\cos \phi = \frac{I_R}{I}$$

I lags V !

$$\phi = \tan^{-1} \left(\frac{I_L - I_C}{I_R} \right)$$

$$\frac{I_L - I_C}{I_R}$$

$$\sqrt{I_L}$$

$$2\phi$$

$$I$$


$$I_R$$

$$V$$

$$I_L - I_C$$

$$I_L = I_C$$
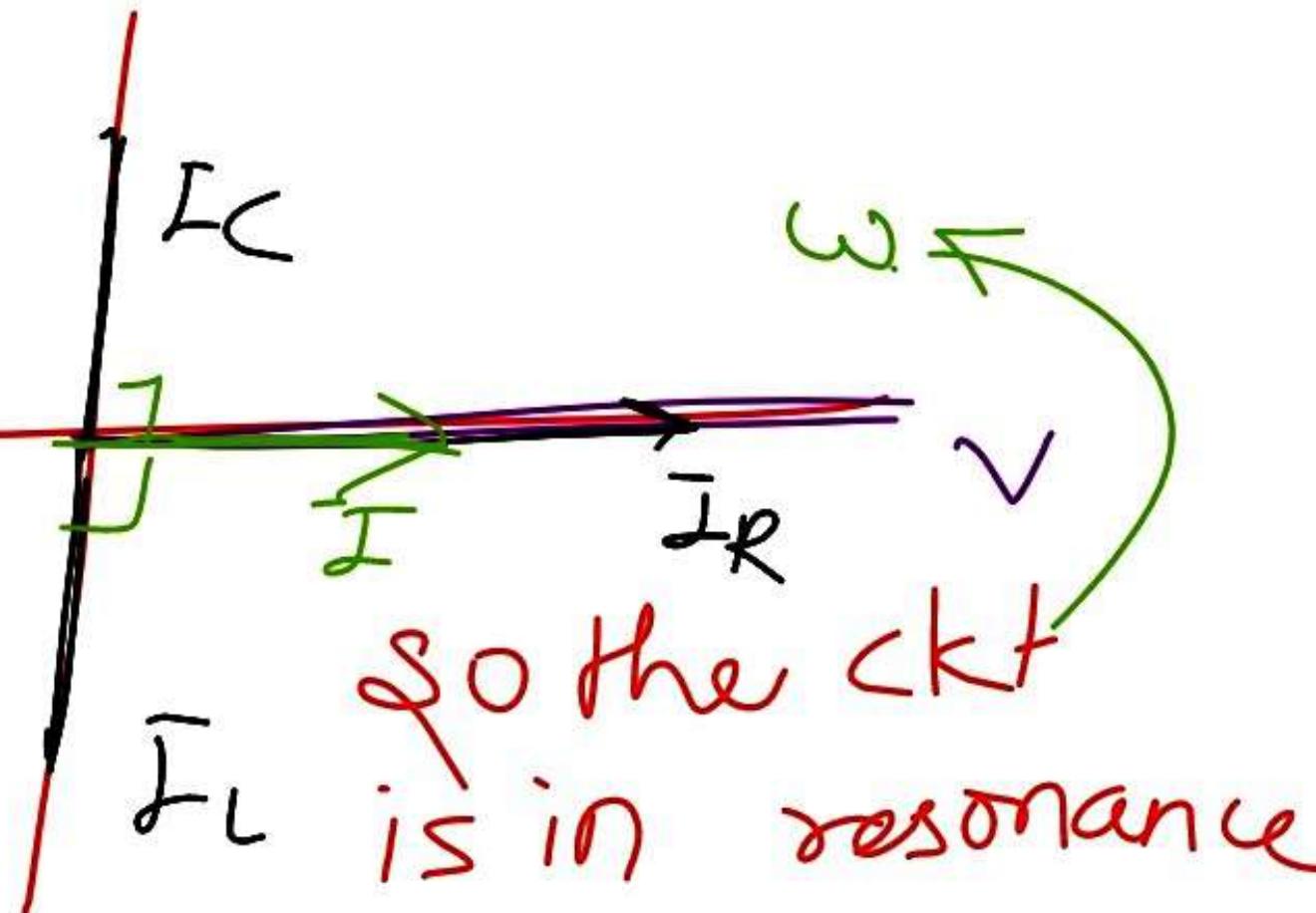
$$\begin{aligned} I_R &= I \\ \phi &= 0 \end{aligned}$$



Power Calculations in AC.

For DC circuit.

$$P_{DC} = VI = \frac{V^2}{R} = I^2 R$$

Power in any instant in AC
ckt is called instantaneous
power. & it is defined by

$$P = V_i$$

$$P = \frac{1}{T} \int_0^T v_i dt$$

$$P = \frac{1}{2\pi} \int_0^{2\pi} v_i dt$$

Avg power

Power in pure resistive ckt

$$v = V_m \sin \omega t$$

$$i = I_m \sin \omega t$$

$$P = vi$$

$$= V_m I_m \sin^2 \omega t$$

$$= \frac{1}{2} V_m I_m (1 - \cos^2 \omega t)$$

Active power is given by

$$\cdot P = \frac{1}{T} \int_0^T v_i dt$$

$$\frac{V_m I_m}{2T} \int_0^T (1 - \cos^2 \omega t) dt$$

$$= \frac{1}{2} V_m I_m \Rightarrow \left(\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \right)$$

$$\Rightarrow V_{rms} I_{rms} \text{ Watt.}$$

Note: Power Waveform is +ve throughout the cycle.

\Rightarrow As I & V are in phase.

⇒ power flows only in one direction.

⇒ It is consumed in R
↳ appears in the form of heat.

Powers in pure Inductive Ckt.

V leads I by 90° .

$$\Rightarrow V = V_m \sin(\omega t + 90^\circ)$$

$$I = I_m \sin \omega t$$

$$= P = VI$$

$$V_m I_m \sin(\omega t + 90^\circ) \sin \omega t$$

$$= \frac{1}{2} V_m I_m (2 \cos \omega t \sin \omega t)$$

$$= \boxed{\frac{1}{2} V_m I_m \sin 2\omega t}$$

$$P_L = -\frac{V_m I_m}{4\omega L} (\cos 4\omega t - \cos 0)$$

" $P_L = 0$ ✓

⇒ For pure Inductive ckt
the active power is zero.

Reactive Power

→ It is the power supplied to Reactance (Inductive or Capacitive)

Q.

$$Q_L = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$
$$= V_{rms} I_{rms}$$

$$V_L = V_{rms} = X_L I_L \quad |$$
$$Q_L = V_L I_L. \quad Q_L \Rightarrow \text{Rate of}$$
$$Q_L = I_L^2 X_L \quad \text{Change of}$$
$$Q_L = \frac{V_L^2}{X_L} \quad \text{reactive energy}$$

Let's Load & Source

Power in capacitive ckt

Voltage lag current by 90°

$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + 90^\circ)$$

$$P = VI$$

$$\frac{1}{2} V_m I_m \underline{2 \sin \omega t \sin(\omega t + 90^\circ)}$$

$$= \frac{1}{2} V_m I_m \sin 2\omega t$$

$$P_c \Rightarrow \frac{1}{T_0} \int_0^T p dt = \frac{V_m I_m}{2 T_0} \int_0^T \sin 2\omega t dt$$

Avg power \Rightarrow Active Power.

$$\frac{V_m I_m}{4 \pi f} (1 - 1) = 0$$

\Rightarrow In pure capacitive ckt
the active or Avg power
supplied over one complete cycle
is zero.

$$Q_C = \frac{V_C^2}{X_C} \quad \text{Or.} \quad I_C^2 X_C$$

Q_C is rate of change of power
reactive power both load &
source Q_C is taken as -ve.

Leading reaction

Powers in general series ckt

$$V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t - \phi)$$

ϕ is phase diff b/w V & I .

$\phi \Rightarrow -ve$. Current leads the V

$$P_{\text{inst}} \Rightarrow V_i$$

$$\Rightarrow V_m I_m \sin \omega t \sin(\omega t - \phi)$$

$$\Rightarrow \frac{1}{2} V_m I_m (2 \sin \omega t \sin$$

$$P_{\text{inst.}} = \frac{1}{2} V_m I_m (\cos \phi - \cos(\omega t - \phi))$$

Avg power


$$\Rightarrow P_L = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$= V_{rms} I_{rms} \cos \phi$$

$$P_I = \frac{1}{2T} \int_0^T \sin \omega t \, dt.$$

$$P = \text{Apparent Power} \times \cos \phi$$

$$Q = V_{rms} I_{rm} \sin \phi$$

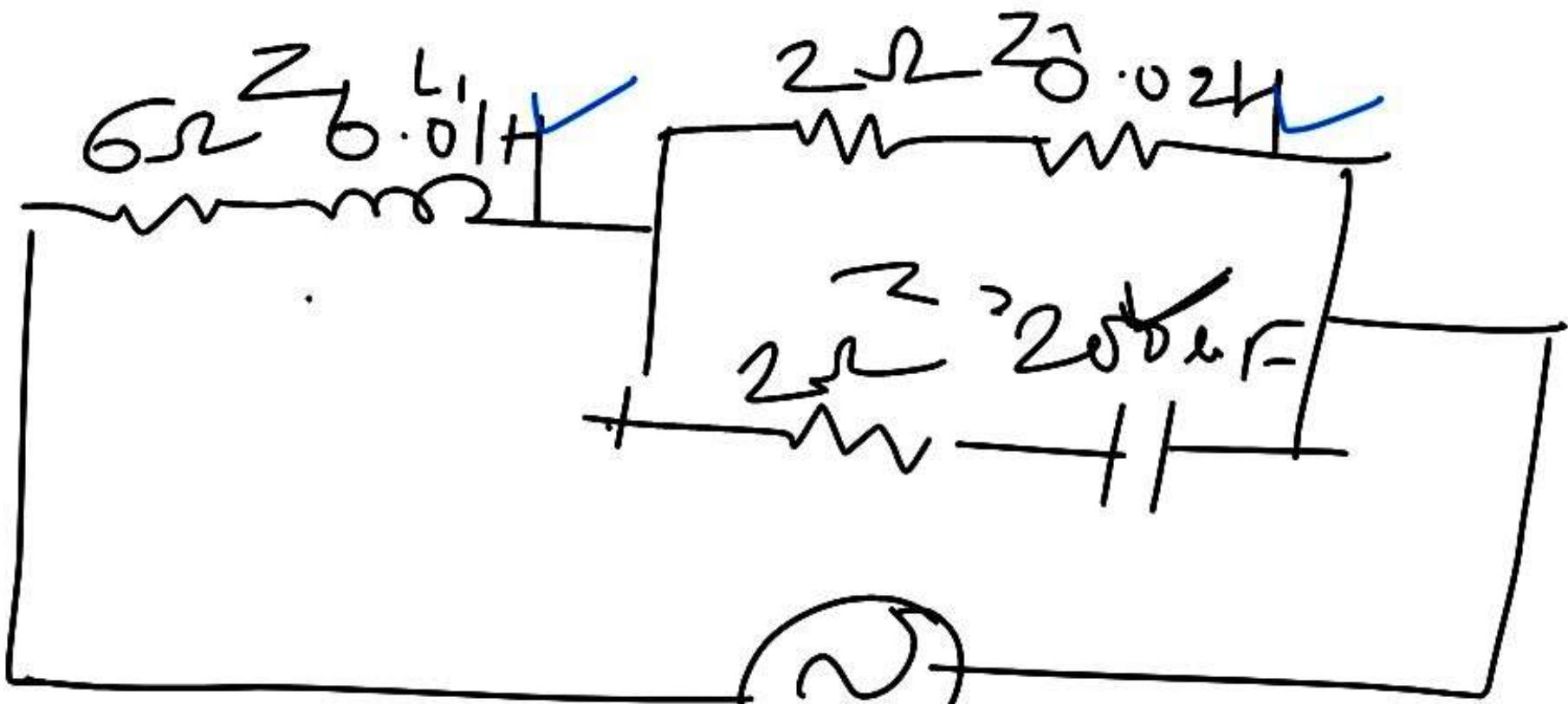

$I, P, PF / \underline{100V}, \underline{50Hz}$

$$X_{L1} = 2\pi \times 50 \times 0.01 = 3.14 \Omega$$

$$X_{L2} = 2\pi \times 50 \times 0.02 \Rightarrow 6.28 \Omega$$

$$X_C = \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}} = 15.92 \Omega$$

$$\left. \begin{array}{l} \bar{Z}_1 = R_1 + j\omega L \\ \bar{Z}_2 = R_2 + j\omega L \\ \bar{Z}_3 = R_3 - j\omega C \end{array} \right\} \quad \begin{array}{l} 6 + j3.14 \Omega \\ 4 + j6.28 \Omega \\ 2 - j15.9 \Omega \end{array}$$

$$\begin{aligned}
 \bar{z} &= z_1 + \frac{\bar{z}_2 \times \bar{z}_3}{\bar{z}_2 + \bar{z}_3} \\
 &= (6+j3.14) + \frac{(4+j6.28)(2-j15.92)}{(4+j6.28)+(2-j15.92)} \\
 &= 17.27 \angle 30.75^\circ
 \end{aligned}$$


$$I = \frac{\bar{V}}{Z} = \frac{100 \angle 0^\circ}{17.27 \angle 30.75^\circ}$$

$$= 5.79 \angle -30.75^\circ \text{ Amp.}$$

$$P = VI \cos \phi = 100 \times 5.79 \cos(30.75^\circ)$$

$$= \underline{497.94 \text{ W.}}$$
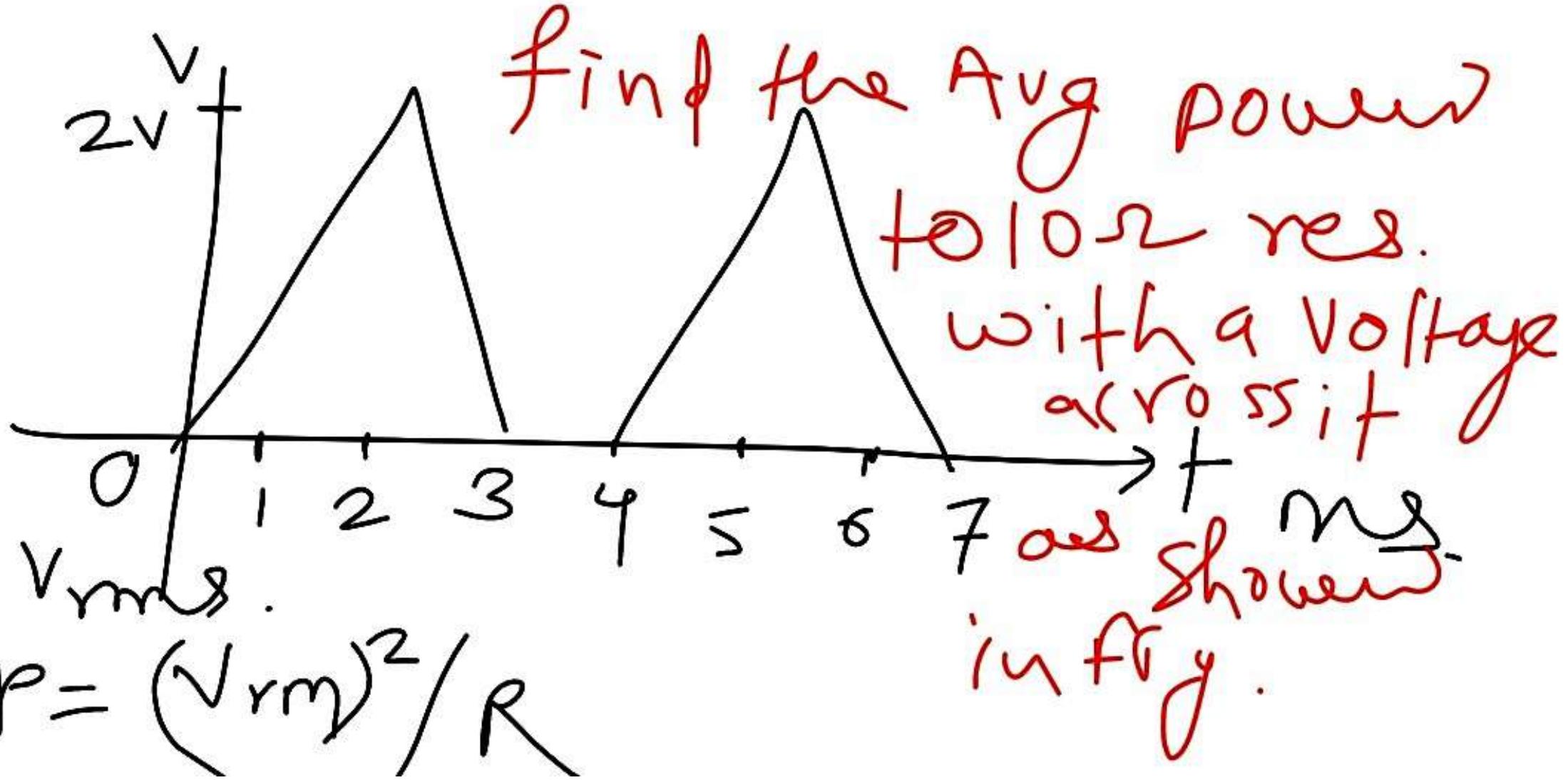
$$\text{PF} = \cos \phi = \cos(30.75^\circ) \\ = 0.86 \text{ (Tagging)}$$



Open circuit impedance parameter
(Z Parameters) → It represents
→ relation b/w voltage & current)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow$$

Matrix eqn.

$$V_1 = Z_{11} I_1 + Z_{12} \underline{I}_2 \leftarrow (I_2 = 0)$$

$$V_2 = Z_{21} \underline{I}_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \quad \begin{matrix} \rightarrow \text{Driving point} \\ \text{at port 1} \end{matrix}$$


$\checkmark \quad \underline{I}_2 = 0$

$$Z_h = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \Leftarrow \text{Transfer Impedance}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \Leftarrow \text{Transfer Impedance}$$

$$Z_{22} = \left| \frac{V_2}{I_2} \right| \Big|_{I_2=0} \quad \begin{matrix} \leftarrow \text{Driving point} \\ \text{Impedance at port 2.} \end{matrix}$$

$$Z_{12} = \left| \frac{V_1}{I_2} \right| \Big|_{I_1=0} \Rightarrow$$

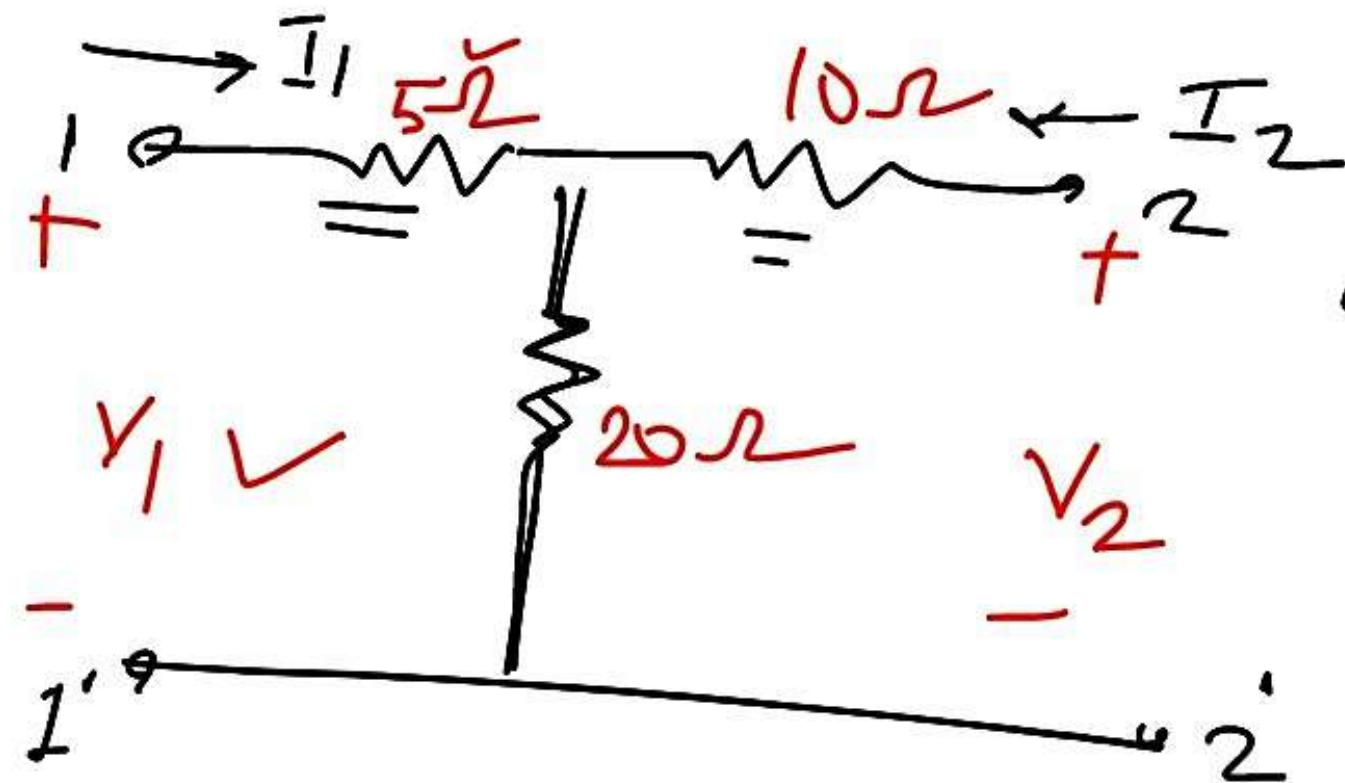


Determine
 the z
 parameters

→ Q When ($I_1 = 0$) ✓

Port 1 \Rightarrow OC.

$$\Rightarrow \text{By KVL} \Rightarrow 10I_2 + 20I_2 - V_2 = 0 \\ = 30I_2 - V_2 = 0$$
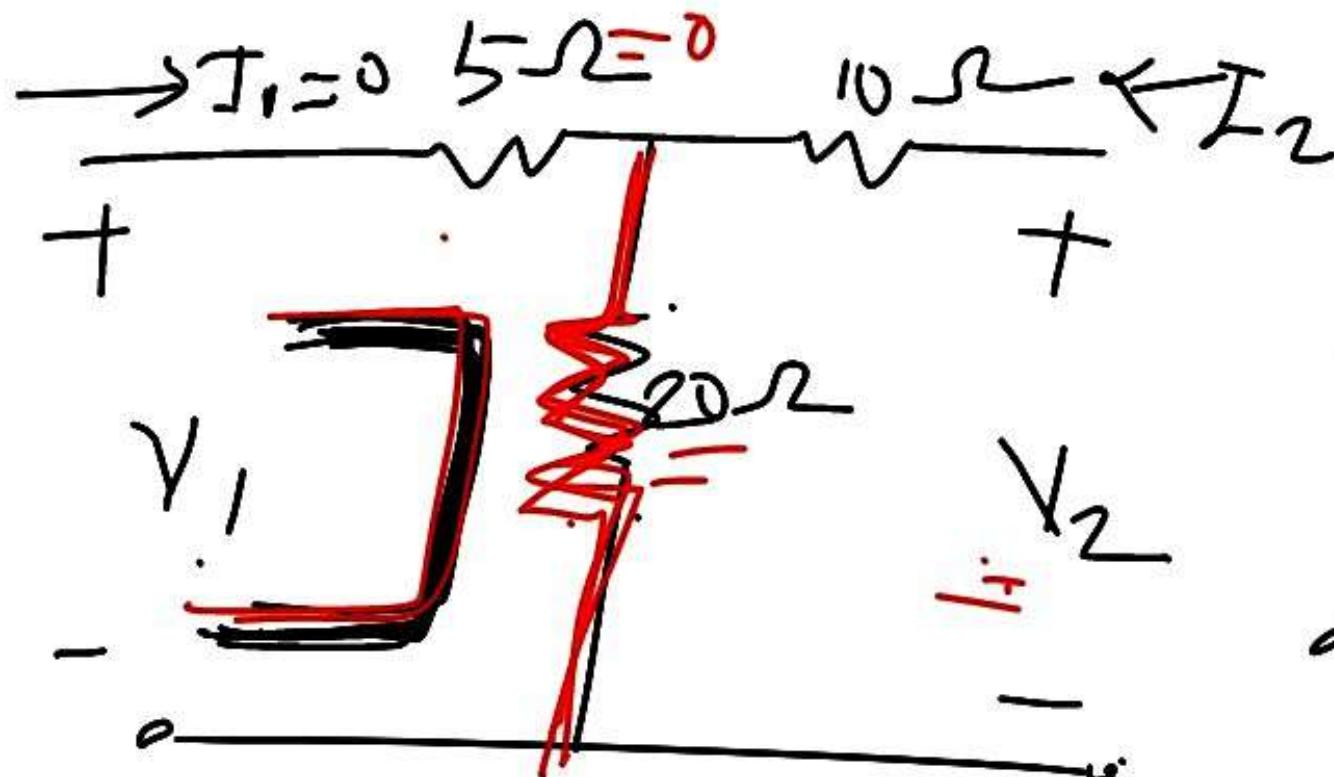
$$\therefore \frac{V_2}{I_2} = 30\Omega \Rightarrow z_{22} =$$



$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = 20 \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$V_2 = 20 I_1$$

$$V_1 = 20 I_2$$

Case ②

When $I_2 = 0 \Rightarrow$ Port 2 OC.

$$\rightarrow \text{KVL} \Rightarrow 5I_1 + 20I_1 - V_1 = 0$$

$$25I_1 - V_1 = 0$$

$$\left| \frac{V_1}{I_1} \right| = R_{11} = \underline{\underline{25\Omega}}$$

$$[Z] = \begin{bmatrix} 25 & 20 \\ 20 & 30 \end{bmatrix}$$

Short Circuit Admittance parameters

(Y parameters)

Relationship b/w current &
Admittance Matrix voltages.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\bar{I}_1 = V_{11}X_1 + V_{12}X_2$$

$$I_2 = V_{21}X_1 + V_{22}X_2$$


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

Driving point
admittance at
port 1.

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \Leftarrow \text{Transfer Admittance}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \Leftarrow \text{Transfer Admittance}$$


$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \Leftarrow \begin{array}{l} \text{Driving point} \\ \text{admittance at port 2} \end{array}$$

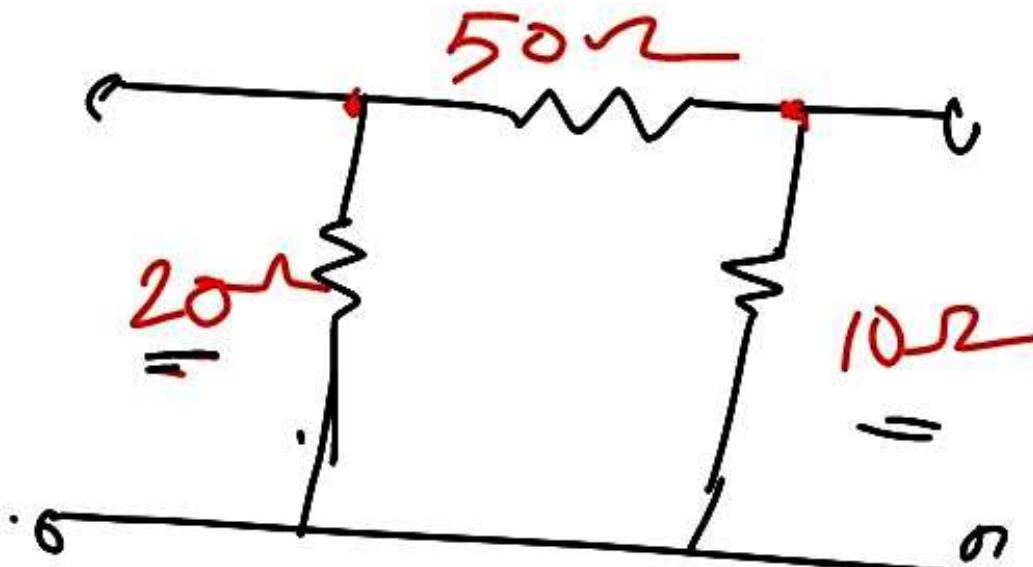

find the
Y parameters

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

① $V_1 = 0$ Port 1 S.C.

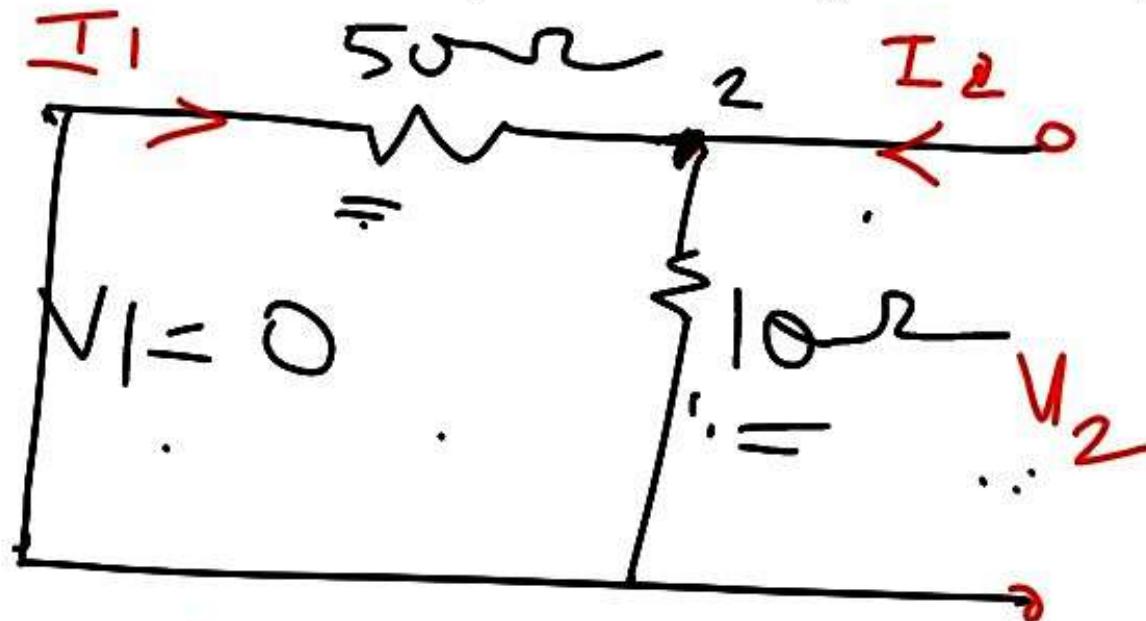

when $V_1 = 0$

By KCL

$$\frac{V_2 - V_1}{10} + \frac{V_2 - V_1}{50} = I_2$$

$$V_1 = 0$$

$$\frac{V_2 - 0}{10} + \frac{V_2 - 0}{50} = I_2$$

$$V_2 \left(\frac{1}{10} + \frac{1}{50} \right) = I_2$$


$$\therefore \frac{I_2}{V_2} = \frac{3}{25} \text{ or } = 0.12 - j$$

$$Y_{22} = 0.12 \text{ or}$$

$$I_1 = \frac{V_1 - V_2}{50} = \frac{0 - V_2}{50}$$

$$= J_{12} = \left| \frac{I_1}{V_2} \right| \quad V_1 = 0 = \frac{1}{50} = 0.02$$

$v_2 = 0$ ← Case 2

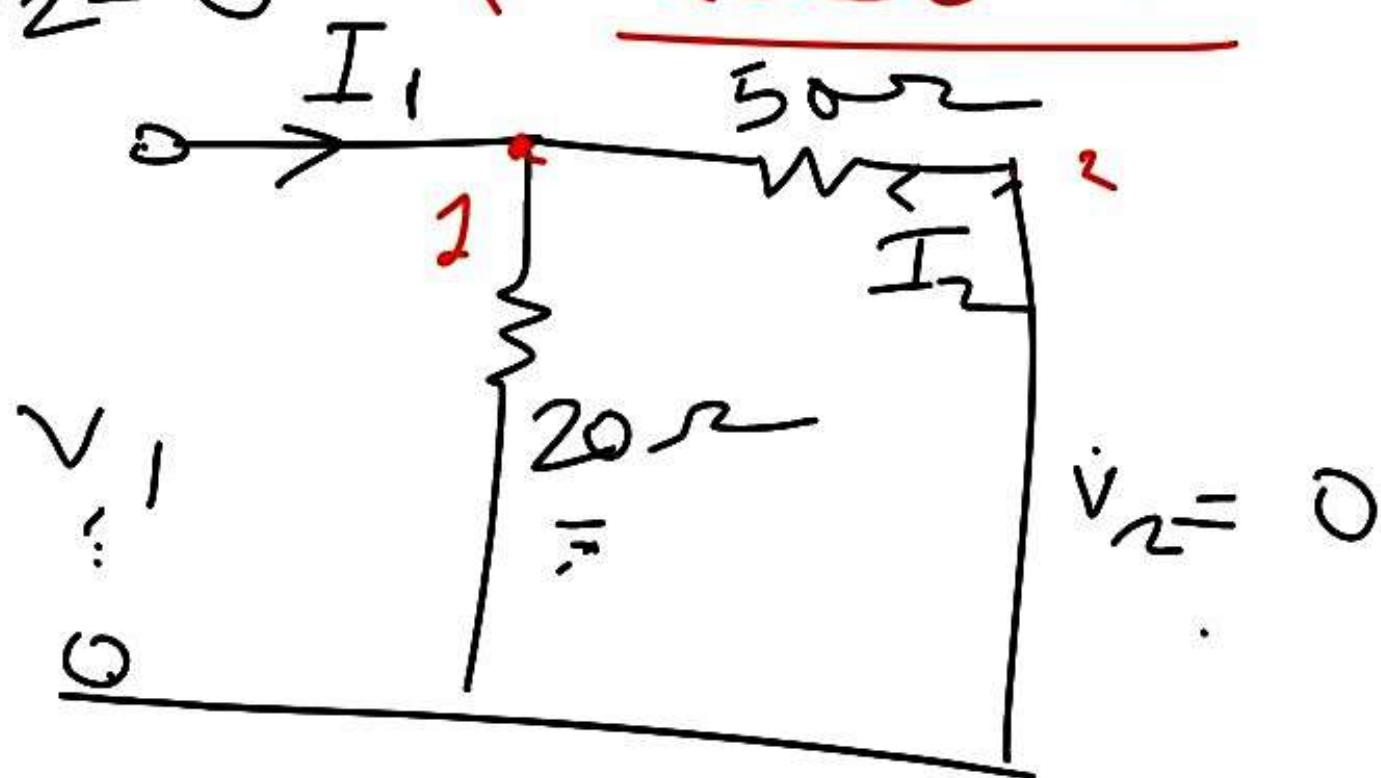

KCL at node 1.

$$\frac{V_1 - V_2}{20} + \frac{V_1 - V_2}{50} = I_1 \quad (V_2=0)$$

$$\frac{V_1 - 0}{20} + \frac{V_1 - 0}{50} = \bar{I}_1$$

$$Y_{11} = \left| \frac{I_1}{V_1} \right|_{V_2=0} \Rightarrow \frac{1}{20} + \frac{1}{50} = 0.07 \text{ v}$$

$$I_2 = \frac{V_2 - V_1}{50} \quad (V_2 = 0)$$

$$y_{21} = \left| \frac{I_2}{x_1} \right| = \frac{1}{50} = 0.02 \text{ v}$$

$y_2 = 0$

$$\begin{bmatrix} y_1 & y_2 \\ y_2 & y_1 \end{bmatrix} = \begin{bmatrix} 0.07 & 0.02 \\ 0.02 & 0.42 \end{bmatrix}$$

ABCD Parameters or Transmission

If gives relation b/w param
I/P quantities & O/P.
quantities in 2 port N/w.
(Thus it is voltage-current pair)

Transmission parameter Matrix

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$



$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \leftarrow \text{open ckt reverse voltage gain}$$

$$B = \left. \frac{V_1}{Z_2} \right|_{V_2=0} \leftarrow \begin{array}{l} \text{short ckt} \\ \text{transfer} \\ \text{impedance} \end{array}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

open ckt Transfer
admittance

$$\mathcal{D} = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$


← short ckt.
reverse current
gain

$$A = \left| \frac{V_1}{V_2} \right| \Big|_{I_2=0}$$

$$B = \left| -\frac{X_1}{Z_2} \right| \Big|_{V_2=0}$$

$$C = \left| \frac{Z_1}{V_2} \right| \Big|_{I_2=0}$$

$$D = \left| -\frac{Z_1}{Z_2} \right| \Big|_{V_2=0}$$

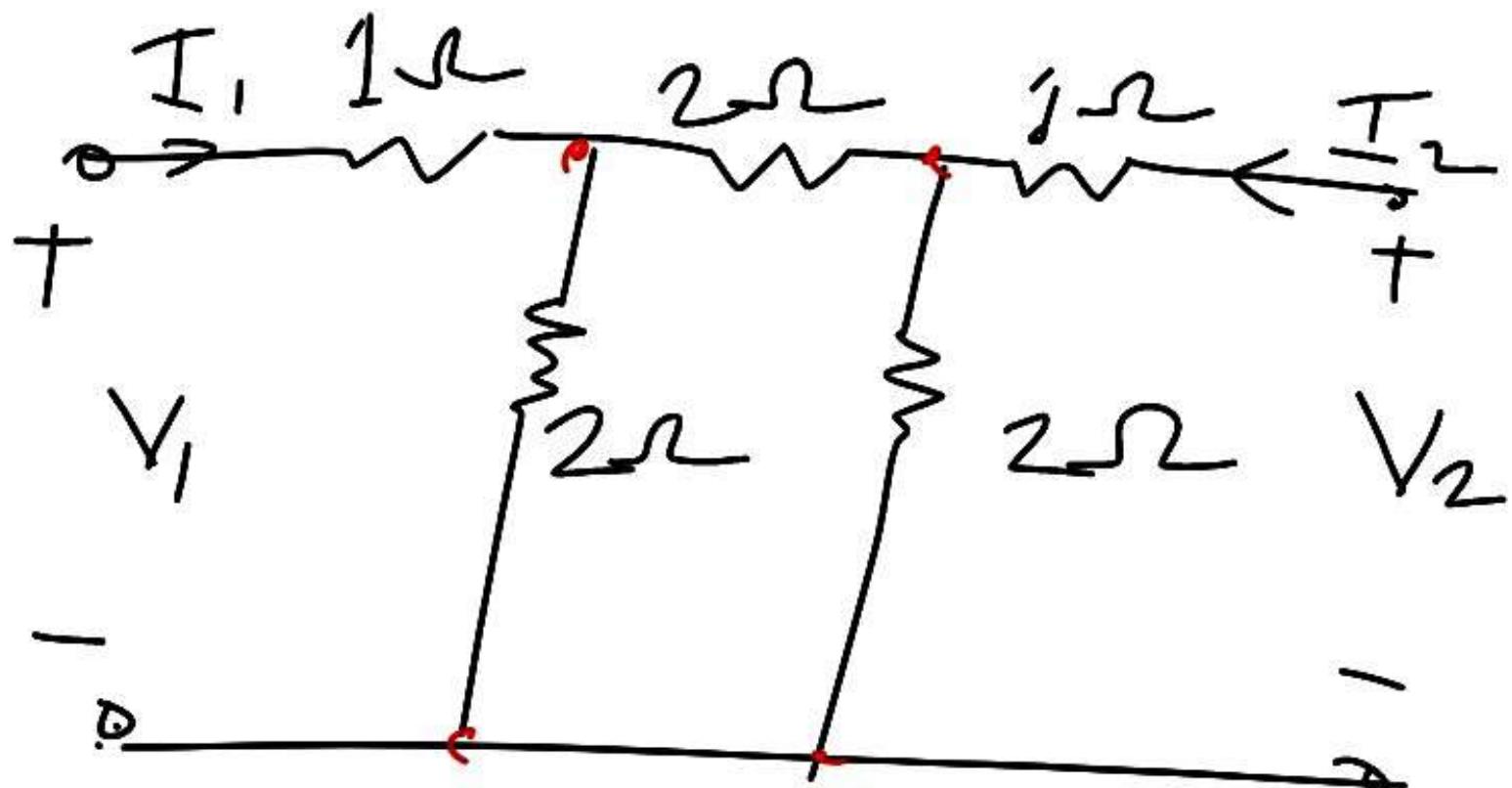

Find
 $A \ B \ C \ D$
 parameters

$$\frac{T N/\omega}{\cdot} \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} (Z_a + Z_b) I_1 +$$

$Z_c I_2 = V_2$

$$Z_c I_1 + (Z_b + Z_c) h = V_1$$

$$A = \frac{z_{11}}{z_{21}}$$

$$C = -\frac{1}{z_{12}}$$


$$B = \frac{-\Delta z}{z_{21}}$$

$$D = \frac{z_{22}}{z_{12}}$$

$$\begin{cases} y_{11} = \frac{z_{22}}{\Delta z} \\ y_{12} = y_{21} = -\frac{z_2}{\Delta z} \\ y_{22} = \frac{z_{11}}{\Delta z} \end{cases}$$

- Write KVL eqn.
- Find Z parameters.
- Give the relation betⁿ A B C D Z parameters & find A B C D.
- Give the relation betⁿ Y & Z parameters & find Y parameters

(2) π or delta N/w.

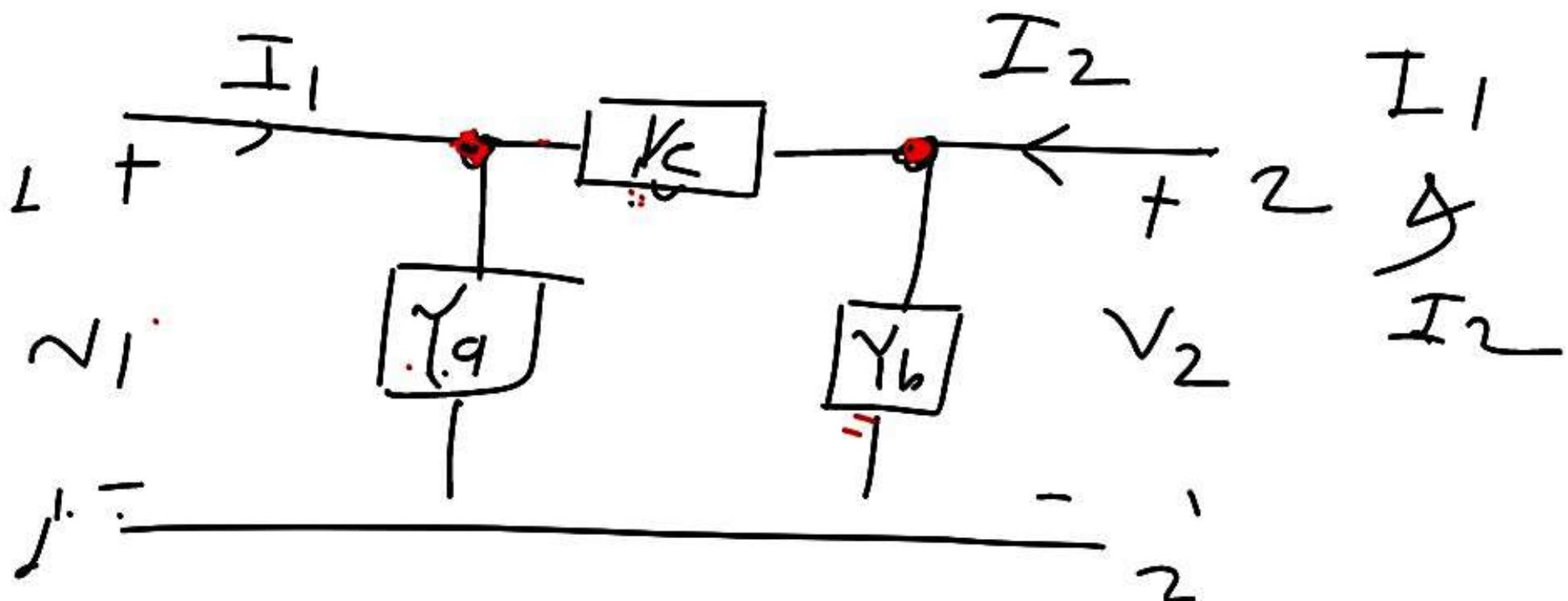

→ Write KCL eqn

→ find 4 parameters.

$$A = -\frac{y_{22}}{y_{21}} \quad B = -\frac{1}{y_{21}}$$

$$C = -\frac{\Delta Y}{y_{21}} \quad D = -\frac{y_{11}}{y_{21}}$$

$$\left[\begin{array}{cc} A & B \\ C & D \end{array} \right]$$

$$I_1 = (V_1 - V_2)Y_C + V_1 Y_A$$


$$\Rightarrow \underline{(Y_A + Y_C)V_1 - Y_C V_2 = I_1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

$$I_2 \Rightarrow V_2 Y_B + (V_2 - V_1)Y_C$$

$$\Rightarrow \underline{-Y_C V_1 + (Y_B + Y_C) V_2}$$

Ladder Network

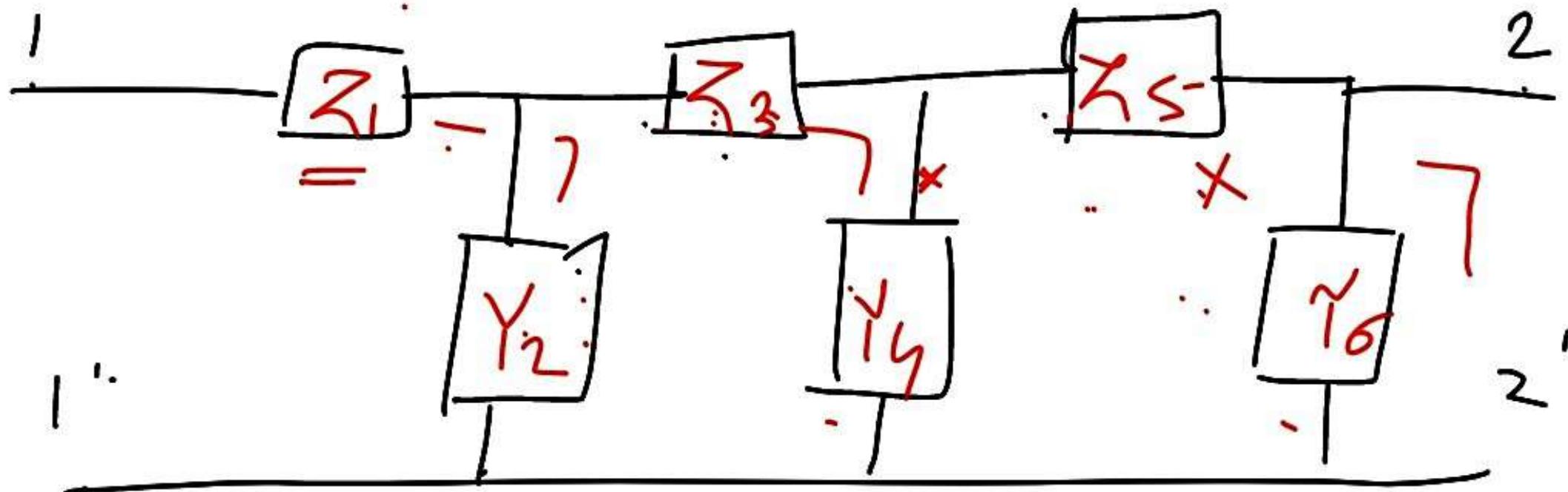



Driving Point Impedance at
port 1

$$Z_{11} = \frac{Z_1 + \frac{Y_2 + \frac{1}{Z_3 + \frac{Y_4 + \frac{1}{Z_5 + \frac{1}{Y_6}}}}}{\dots}}{\dots}$$

Continued fraction.

Lattice Network

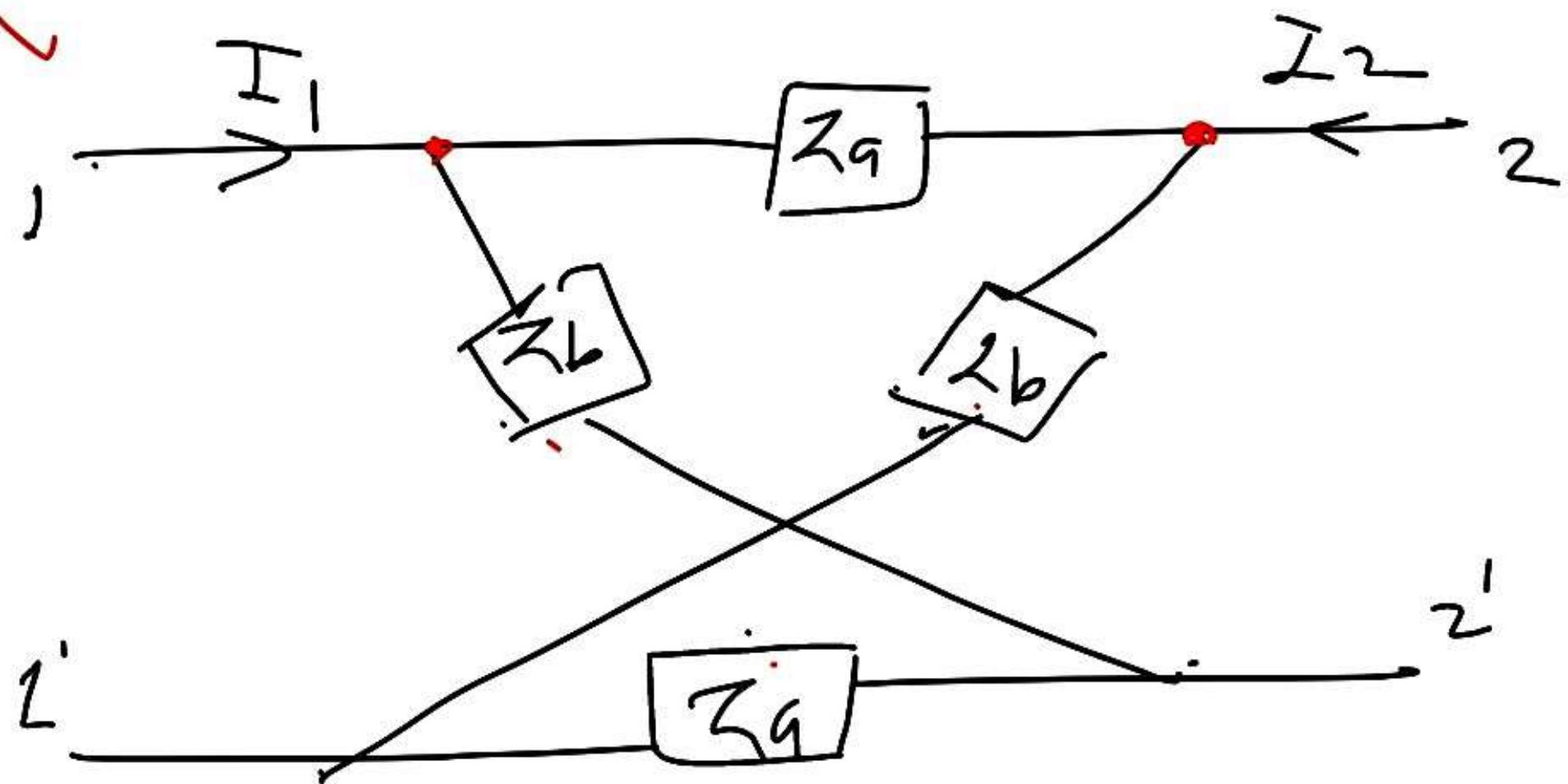

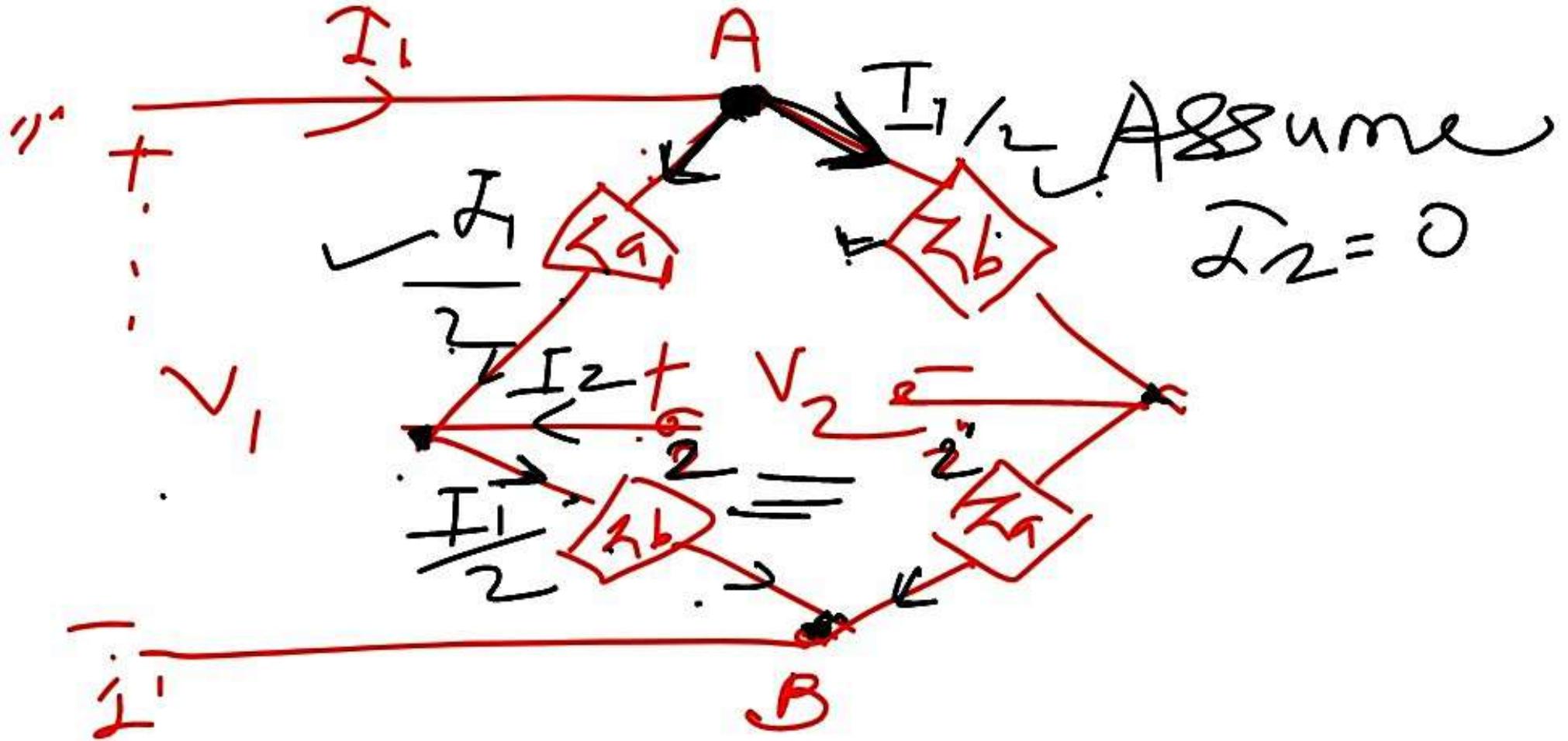

$$\frac{I_1}{2} Z_9 + V_2 = \frac{I_1}{2} Z_b$$

$$V_2 = \frac{I_1}{2} Z_b - \frac{I_1}{2} Z_9$$

$$V_2 = \frac{I_1}{2} (Z_b - Z_9)$$

$$V_1 = \frac{I_1}{2} Z_a + \frac{I_1}{2} Z_b$$


$$V_2 = \frac{I_1}{2} Z_b - \frac{I_1}{2} Z_a$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$\zeta_{12} = \zeta_{21} \Rightarrow \frac{\zeta_b - \zeta_g}{2}$$

$$\zeta_{11} = \zeta_{22} \Rightarrow \frac{\zeta_b + \zeta_g}{2}$$

Bridge TN/ue

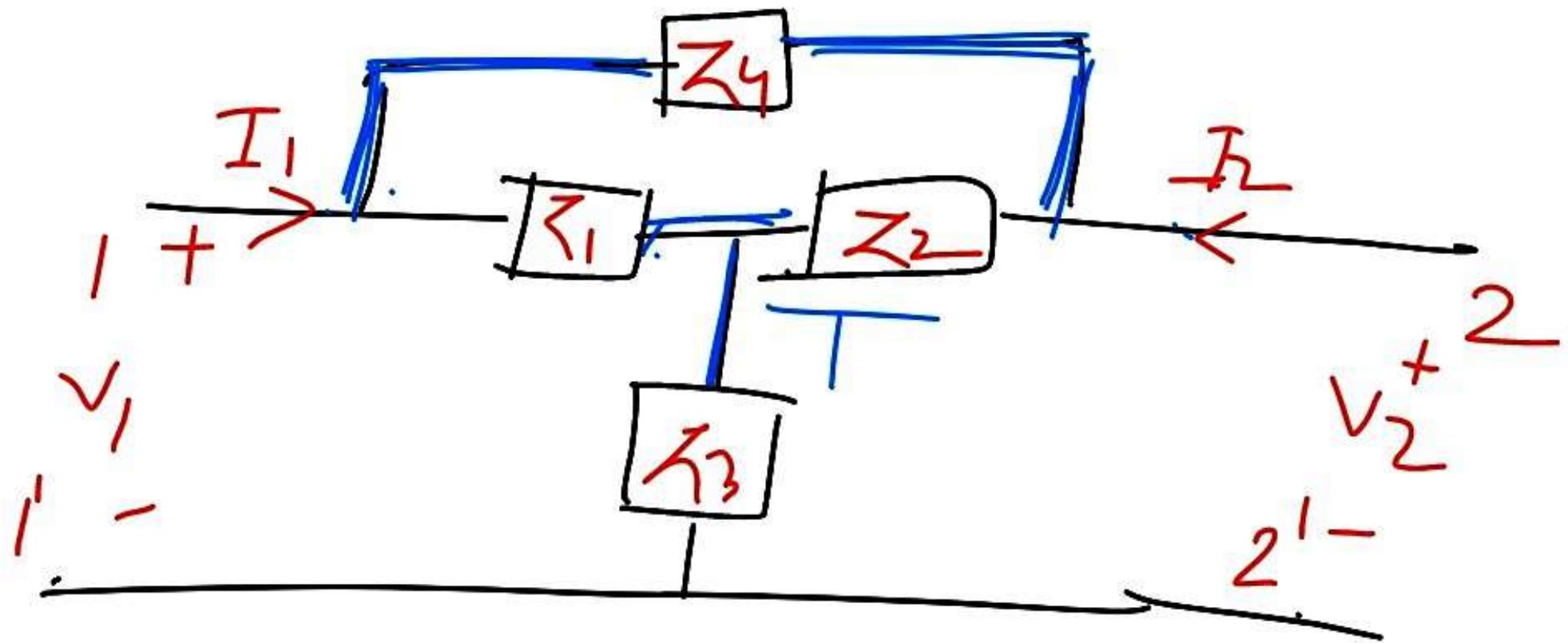

$$Y_{jk} = \frac{\Delta'_{jk}}{\Delta} \Rightarrow Y_{11} = \frac{\Delta''_{11}}{\Delta}$$

(Mesh)

$\Delta \rightarrow$ loop basis determinant

$\Delta'_{jk} \Rightarrow$ cofactor. (Output is shorted)


$$Z_{jk} = \frac{\Delta'_{kj}}{\Delta'}$$

(Node basis
relation)

Δ' = loop basis determinant

Δ'_{kj} => cofactor. (O/p is open
circuited)
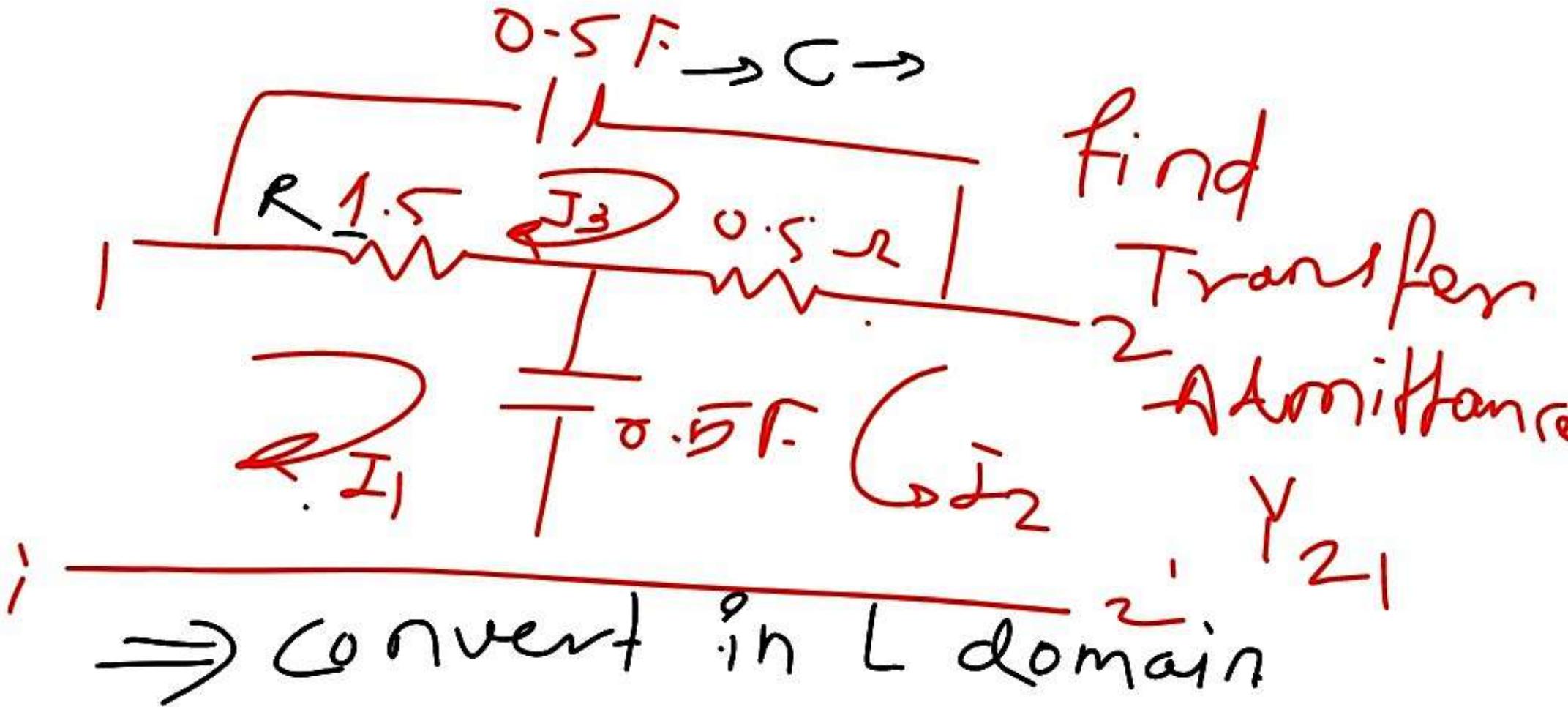
$$G_{21} = \frac{I_2}{I_1} = \frac{\Delta_{21}}{\Delta_{11}}$$



$$\left(\frac{1}{2} + \frac{2}{5} \right) I_1 + \frac{2}{5} I_2 - I_3 = V_1$$

$$\frac{2}{5} I_1 + \left(\frac{1}{2} + \frac{2}{5} \right) I_2 + \frac{1}{2} I_3 = V_2$$

$$-I_1 + \frac{1}{2} I_2 + \left(\frac{3}{2} + \frac{2}{5} \right) I_3 = 0$$


$$\Delta = \begin{pmatrix} \left(1 + \frac{\gamma}{S}\right) & \frac{2}{S} & -1 & \cdot \\ \frac{2}{S} \left(\frac{1}{2} + \frac{\gamma}{S}\right) & \frac{1}{2} & \cdot & \cdot \\ -1 & \frac{1}{2} & \left(\frac{3}{2} + \frac{\gamma}{S}\right) & \cdot \\ \cdot & \cdot & \cdot & \cdot \end{pmatrix} \cdot \begin{matrix} v_1 \\ v_2 \\ \vdots \\ 0 \end{matrix}$$

$\Delta|_2 \Rightarrow$

$\begin{pmatrix} -1 \\ -1 \end{pmatrix} + 2 \begin{bmatrix} \frac{\gamma}{S} & \frac{1}{2} \\ -1 & R \end{bmatrix}$

$$\Delta_{12} \Rightarrow (-1)^{k^2}$$

for series & shunt element

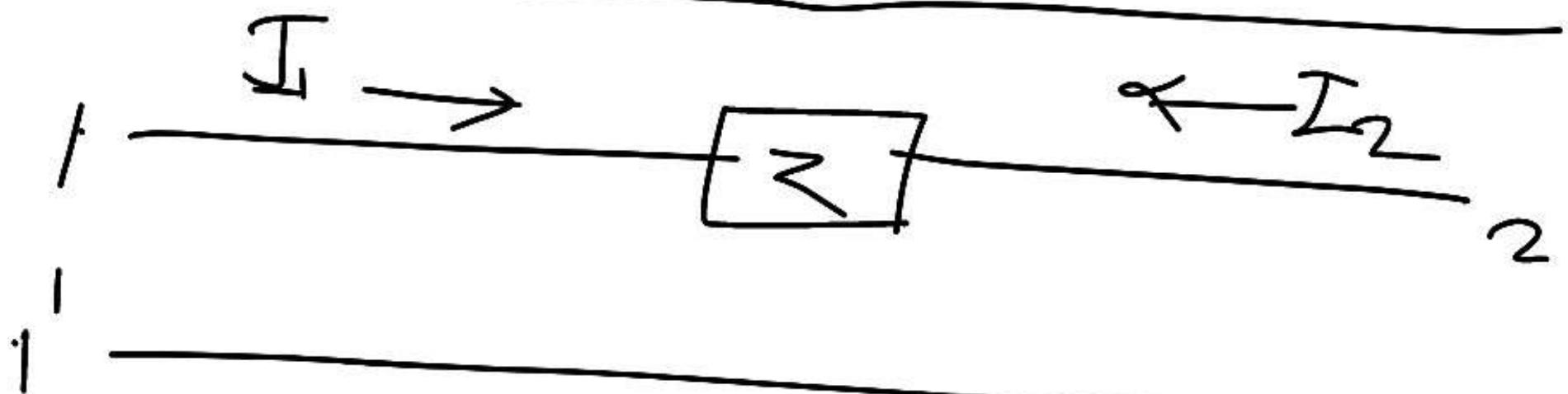


for series element ($I_1 = -I_2$)
Reciprocal & Symeon.

for series-element ($I_1 = -I_2$)
Z parameters are not defined.
 \because If $I_2 = 0$ then I_1 also
Zero.

$$[Y] = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

for shunt current $v_1 = v_2$

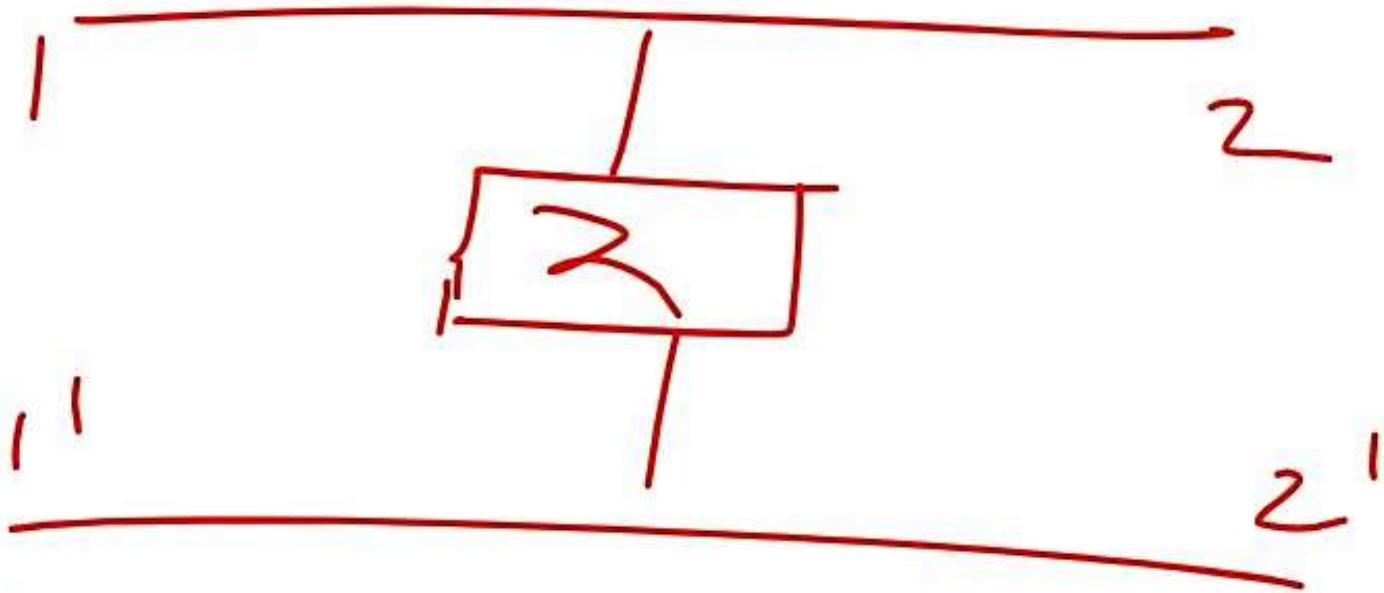


γ parameter will not define

$\therefore v_2 = 0$ then $v_1 = 0$

$$[Z] = \begin{bmatrix} z & z \\ z & z \end{bmatrix}$$

$$ABCD = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

Reciprocal & symmetric

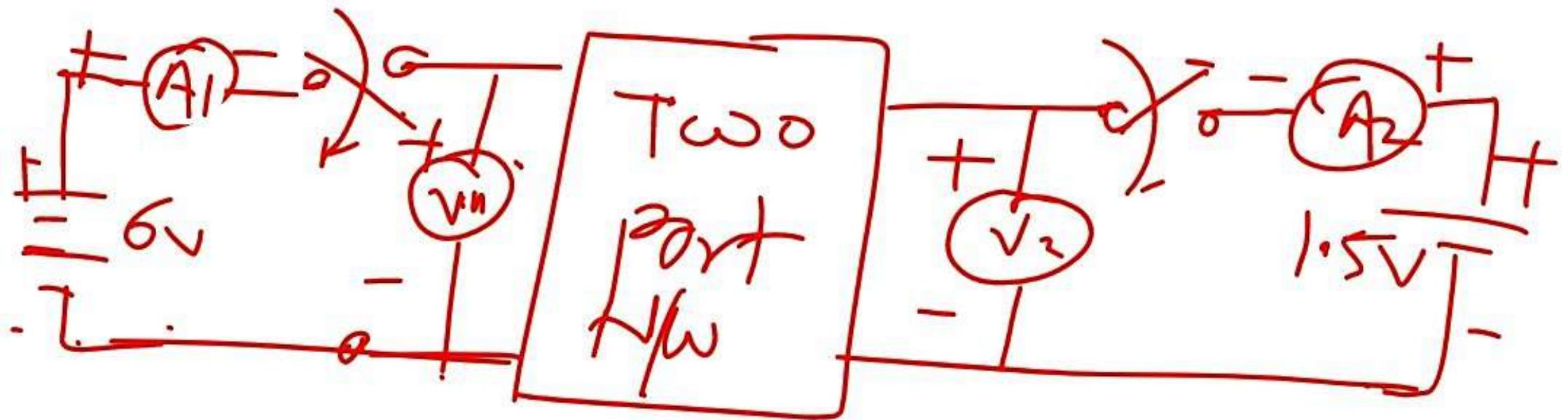

① $S_1 = \text{open}$.

$$A_1 = 0 A$$

$$V_2 = 1.5 V$$

$S_2 = \text{closed}$.

$$V_1 = 4.5 V$$

$$A_2 = 1 A$$

② S_1 closed

$$A_1 = 4 A$$

$$V_2 = 6 V$$

$S_2 = \text{open}$.

$$V_1 = 6 V$$

$$A_2 = 2 A$$


Z parameter matrix
 h parameter matrix } find.

Time And Frequency Response of circuit.

AC Circuit Analysis:

Average and RMS values of Periodic Signal

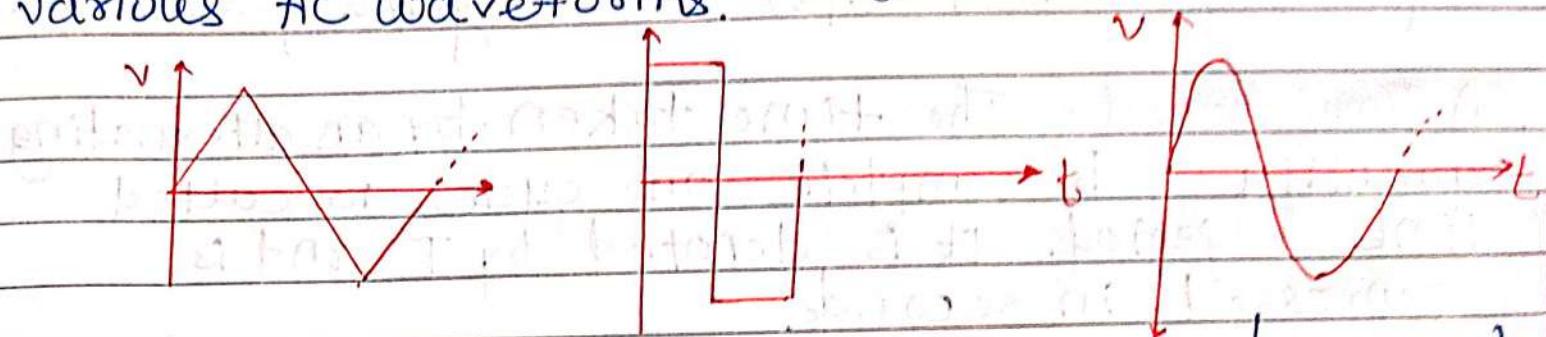An alternating waveform changes its magnitude and direction periodically. Fig. shows various AC waveforms.



Many times, alternating voltages and currents are represented by a sinusoidal waveforms. A sinusoidal voltage can be represented as

$$\begin{aligned}
 \text{Voltage } v &= V_m \sin \theta \\
 \text{Current } i &= I_m \sin \omega t \\
 &= V_m \sin 2\pi f t \\
 &= V_m \sin \frac{2\pi}{T} t
 \end{aligned}$$

Terms related with alternating Quantity :

① Waveform: A waveform is a graph in which the instantaneous value of any quantity is plotted against time. Fig. shows a few waveforms.

(2) Cycle :- One complete set of positive and negative values of an alternating quantity is termed as cycle.

(3) Frequency :- The number of cycles per second of an alternating quantity is known as frequency. It is denoted by f and is expressed in hertz (Hz) or cycles per second.

(4) Time period :- The time taken by an alternating quantity to complete one cycle is called time period. It is denoted by T and is expressed in seconds.

(5) Amplitude :- The maximum positive or negative value of an alternating quantity is called the amplitude.

(6) Phase :- The phase of an alternating quantity is the time that has elapsed since the quantity has last passed through zero point of reference.

(7) Phase difference :- This term is used to compare the phases of two alternating quantities. Two alternating quantities are said to be in phase when they reach

Their maximum and zero values at the same time.
Their maximum value may be different in magnitude.

A leading alternating quantity is one which reaches its maximum or zero value earlier as compared to the other quantity.


A lagging alternating quantity is one which attains its maximum or zero value later than the other quantity.

A plus (+) sign when used in connection with the phase difference denotes 'lead', whereas a minus (-) sign denotes 'lag'.

$$V_A = V_m \sin \omega t$$

$$V_B = V_m \sin(\omega t + \phi)$$

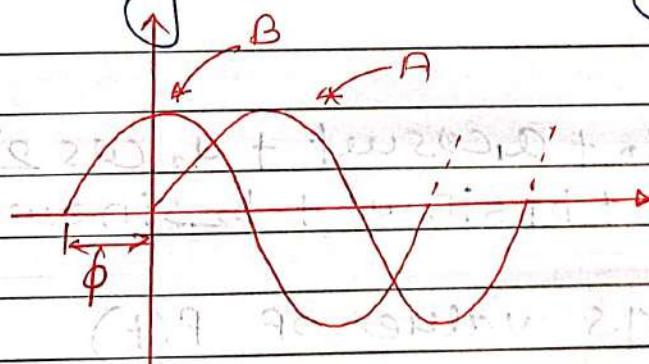Here, quantity B leads A by a phase angle ϕ



Let $x(t)$ be the periodic signal of period 'T'

$$\text{then } x(t \pm T) = x(t)$$

Average Value = DC value

$$X_{avg} = X_{dc} = \frac{1}{T} \int_0^T x(t) dt$$

Avg. or DC = Area of the signal over one period

Periodic

$$\text{RMS value} = X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$\text{Peak Factor} = \frac{x(t)_{\max}}{x(t)_{\text{avg}}} = \frac{x_{\max}}{x_{\text{avg}}}$$


→ The average and value of sine or cosine function of any phase and frequency is zero, and its rms value is Maximum value

$$\rightarrow \text{If } f(t) = a_0 + a_1 \cos wt + a_2 \cos 2wt + \dots + b_1 \sin wt + b_2 \sin 2wt + \dots$$

then the RMS value of $f(t)$

$$(f(t))_{\text{rms}} = \sqrt{a_0^2 + \frac{1}{2} (a_1^2 + a_2^2 + \dots + b_1^2 + b_2^2 + \dots)}$$

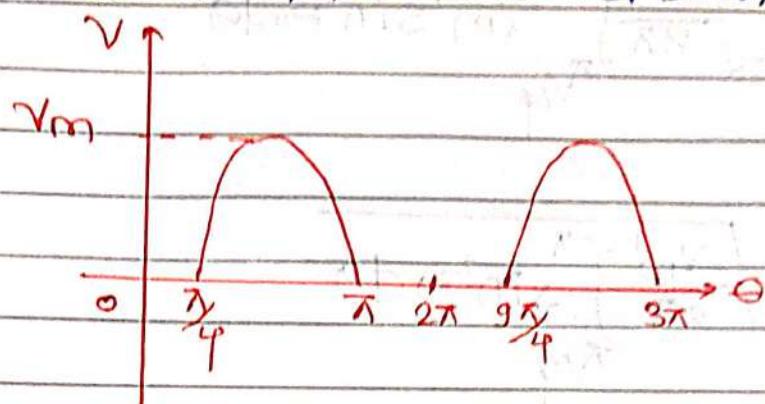Example :- Find the average value and rms value of the waveform shown in Fig.



$$\begin{aligned} V &= 0 & 0 < \theta < \pi/4 \\ &= V_m \sin \theta & \pi/4 < \theta < \pi \\ &= 0 & \pi < \theta < 2\pi \end{aligned}$$

$$\begin{aligned} V_{avg} &= \frac{1}{2\pi} \int_0^{2\pi} V(\theta) d\theta \\ &= \frac{1}{2\pi} \int_{\pi/4}^{\pi} V_m \sin \theta d\theta \\ &= \frac{V_m}{2\pi} \left[-\cos \theta \right]_{\pi/4}^{\pi} \\ &= \frac{V_m}{2\pi} (1 + 0.707) = 0.272 V_m. \end{aligned}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2(\theta) d\theta}$$

$$= \sqrt{\frac{1}{2\pi} \int_{\pi/4}^{\pi} v_m^2 \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{v_m^2}{2\pi} \int_{\pi/4}^{\pi} \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{v_m^2}{2\pi} \int_{\pi/4}^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta}$$


$$= \sqrt{\frac{v_m^2}{2\pi} \left(\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right) \Big|_{\pi/4}^{\pi}}$$

$$= \sqrt{\frac{v_m^2}{2\pi} \left(\frac{\pi}{2} - \frac{\sin 2\pi}{4} - \frac{\pi}{8} + \frac{\sin \pi/2}{4} \right)}$$

$$= \sqrt{0.227 v_m^2}$$

$$= 0.476 v_m$$

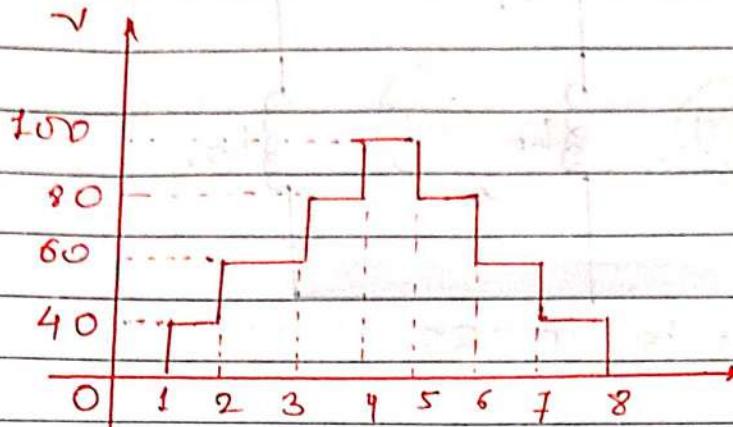Example :- Find -the rms and average value of the waveform shown in figure.



$$V_{avg} = \frac{0+40+60+80+100+80+60+40}{8}$$


$$V_{rms} = \sqrt{\frac{(0)^2 + (40)^2 + (60)^2 + (80)^2 + (100)^2 + (80)^2 + (60)^2 + (40)^2}{8}}$$

$$= 64.42 \text{ volt.}$$


Sinusoidal Steady State Analysis (S³A) by Using Phasors

Steady state indicates absence of transients. It is achieved practically after 5 time constants of switching action & analysis in steady state is generally carried out by using phasors.

Procedure :-

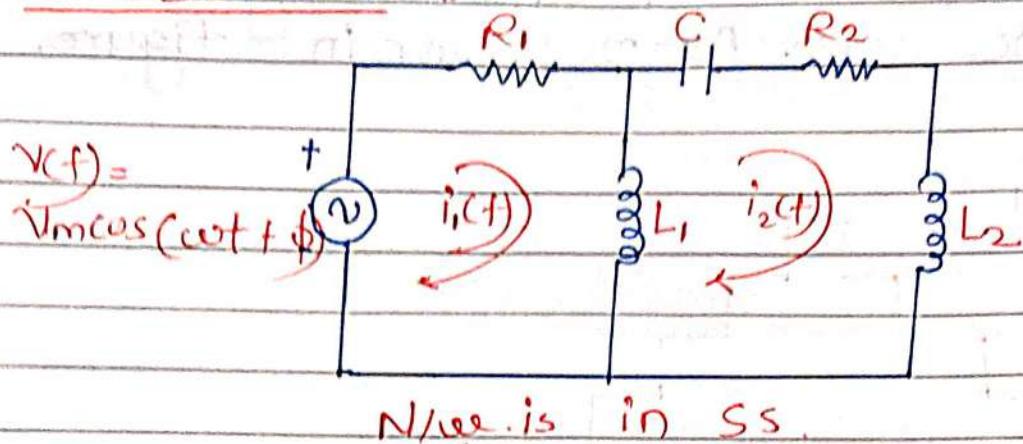

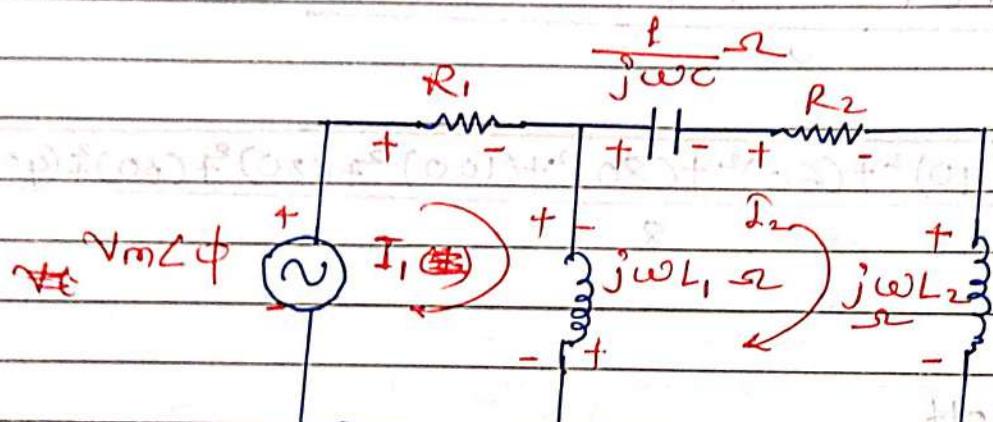Transform the above network into phasor domain.



$$V = \omega \cdot I$$

By KVL in Phasor domain

$$V_m L \phi - R_1 I_1 - j \omega L_1 (I_1 - I_2) = 0 \quad \text{--- (1)}$$

$$\frac{-1}{j \omega C} I_2 - R_2 I_2 - j \omega L_2 I_2 - j \omega L_1 (I_2 - I_1) = 0 \quad \text{--- (2)}$$


$$I_1 = \Delta_1$$

$\Delta \quad i_1(t) = \text{Real Part} [I_1 \cdot e^{j\omega t}] \text{ Amp.}$

Date _____
Page _____

$$I_2 = \frac{A_2}{\Delta} |_{i_2(t)} = \text{Real part} [I_2 \cdot e^{j\omega t}] \text{ Amp.}$$

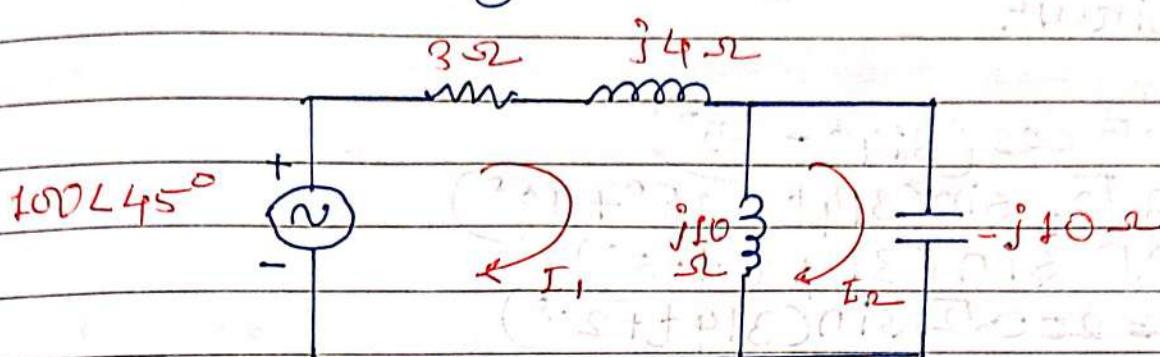Example :- Find mesh currents I_1 & I_2 in the network of figure.



Applying KVL to mesh 1:

$$100\angle 45^\circ - (3 + j4)I_1 - j10(I_1 - I_2) = 0$$

$$(3 + j14)I_1 - j10I_2 = 100\angle 45^\circ \quad \text{①}$$

Applying KVL to mesh 2:

$$-j10(I_2 - I_1) + j10(I_2) = 0$$

$$j10I_1 = 0$$

$$I_1 = 0$$

Substituting I_1 in eqn ① we get

$$-j10I_2 = 100\angle 45^\circ$$

$$I_2 = \frac{100\angle 45^\circ}{j10} = 10\angle 135^\circ \text{ Amp.}$$

Example:

A two element series circuit is connected across an ac source given by $e = 200\sqrt{2} \sin(314t + 20^\circ)$. The current in the circuit then is found to be $i = 10\sqrt{2} \cos(314t - 25^\circ)$. Determine the parameters of the circuit.

$$\rightarrow i = 10\sqrt{2} \cos(314t - 25^\circ) \\ = 10\sqrt{2} \sin(314t - 25^\circ + 90^\circ) \\ i = 10\sqrt{2} \sin(314t + 65^\circ)$$

$$\text{Also, } e = 200\sqrt{2} \sin(314t + 20^\circ)$$

Current lead emf by $(65^\circ - 20^\circ) = 45^\circ$.

Power Factor = $\cos 45^\circ = 0.707$ (leading)

Now,

$$Z = \frac{V_m}{I_m} = \frac{200\sqrt{2}}{10\sqrt{2}} = 20\Omega$$

$$R = Z \cos \phi = 20(0.707) = 14.14\Omega$$

$$X_C = Z \sin \phi = 20(0.707) = 14.14\Omega$$

$$X_C = \frac{1}{2\pi f C} = 14.14 \Rightarrow C = \frac{1}{2\pi f \times 14.14}$$


$$= \frac{1}{2 \times 3.14 \times 50 \times 14.14} = 2.2523 \times 10^{-4} F$$

$$= 225.23 \mu F$$



Phasor Diagram :-

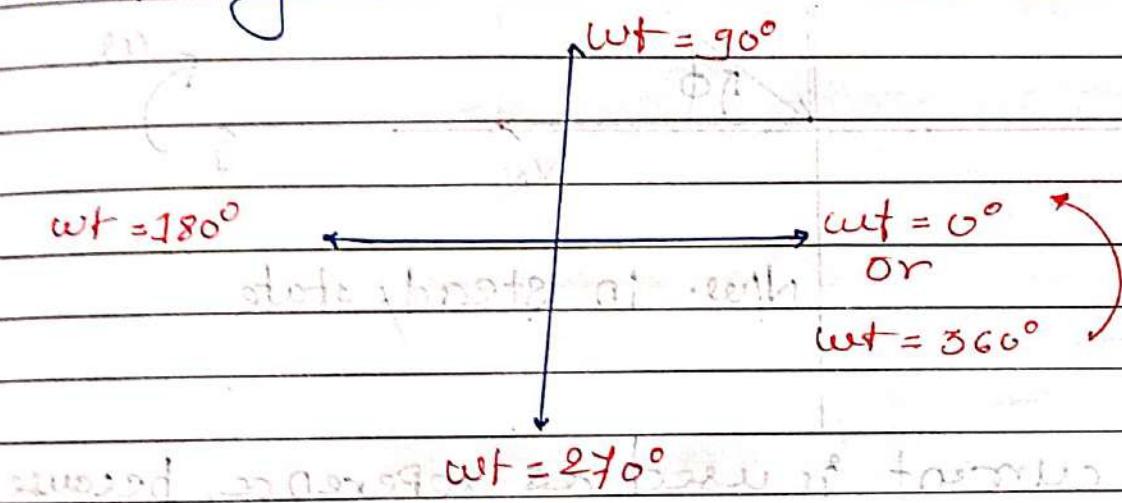- A graphical or pictorial representation of phasors is known as phasor diagram.
- Phasor diagram is a pictorial representation of all the phase voltages and their respective currents in a network.
- Phasor is a rotating vector, which rotates in the anti clockwise direction with angular frequency ' ω ' in the time domain



$$Z_R = R \angle 0^\circ = R \angle 0^\circ \Omega$$

$$Z_L = j\omega L \angle 90^\circ = jX_L \angle 90^\circ \Omega$$

where


$$X_L = \omega L$$

$$Z_C = \frac{1}{j\omega C} \angle -90^\circ = -j\frac{1}{\omega C} \Omega$$

$$= -jX_C = X_C \angle -90^\circ \Omega$$

$$\text{where } X_C = \frac{1}{\omega C}$$


Series RL circuit :-

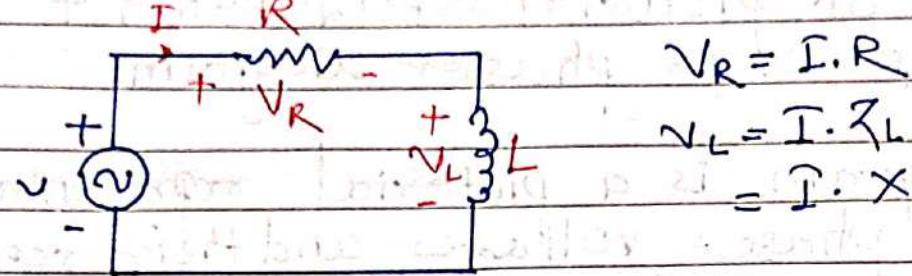

$$V_R = I \cdot R$$

$$V_L = I \cdot Z_L$$

$$= I \cdot X_L \quad 90^\circ$$

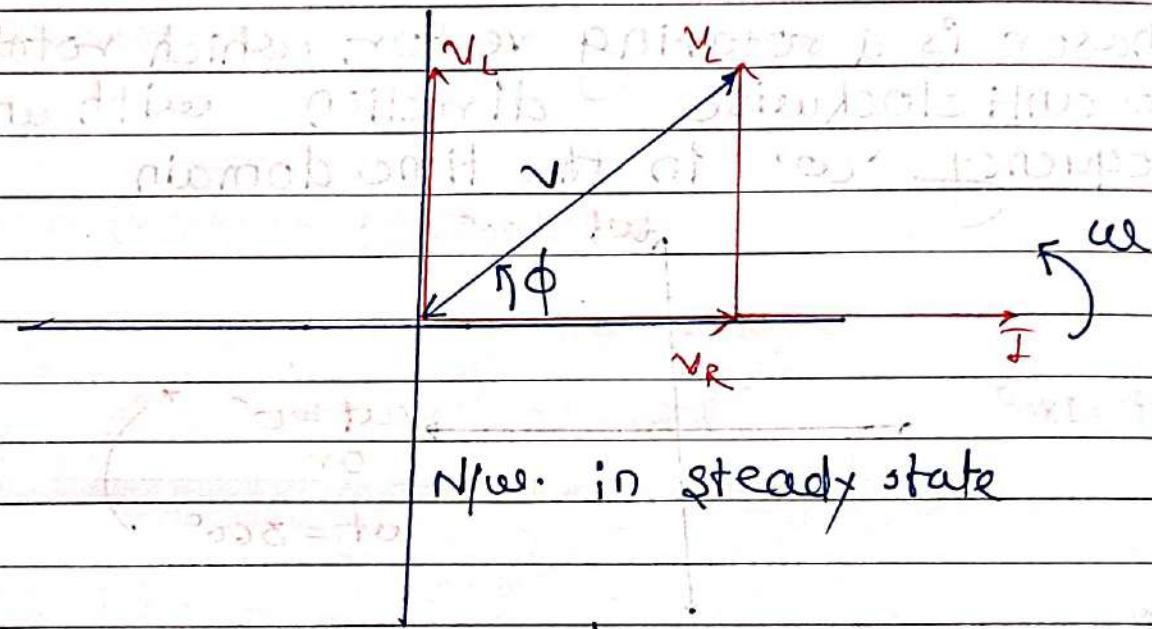

New. in steady state

In series current is used as reference, because it is same.


Current lags the voltage by 90° .

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right) = \text{Impedance Angle}$$

$$\cos \phi - \text{PF (Power factor)} = \frac{V_R}{V} \quad (\text{lag}) \text{ i.e. } I \text{ lags } V$$

series RC circuit :-

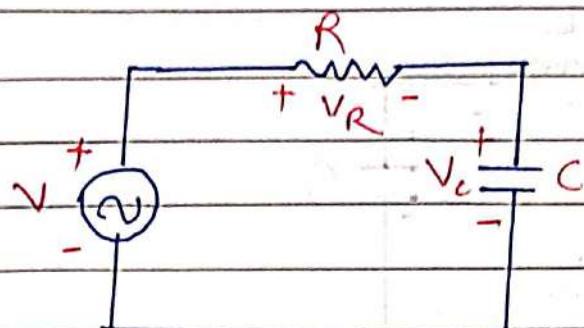


$$V_R = I \cdot R$$

$$V_C = I \cdot Z_C$$

$$= I \cdot X_C L - 90^\circ$$

Network in steady state

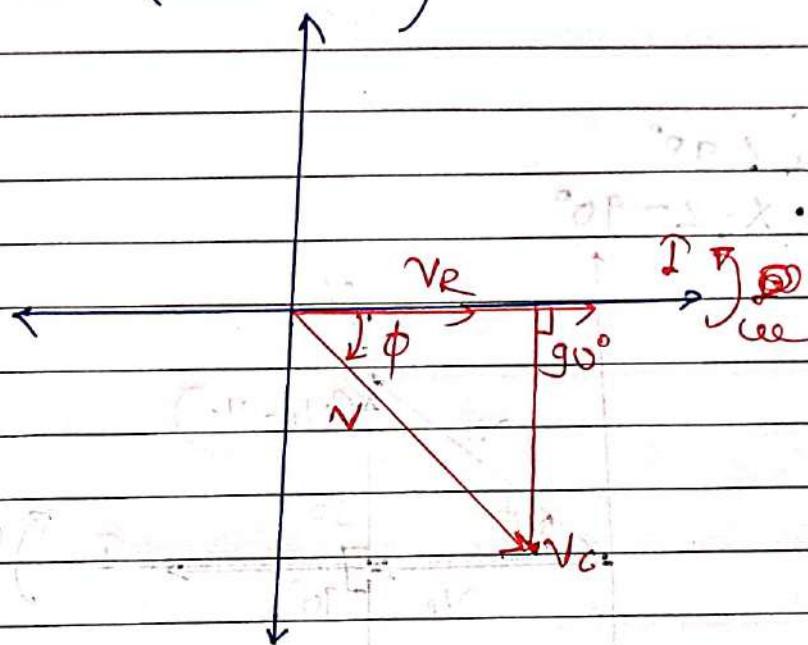


$$V = \sqrt{V_R^2 + V_C^2}$$

$$\phi = \tan^{-1} \left(\frac{V_C}{V_R} \right) = \text{Impedance Angle}$$

$$-90^\circ - \phi = \text{Admittance Angle}$$

i.e. "I" leads "V" by $90^\circ - \phi$

Series RLC circuit :-

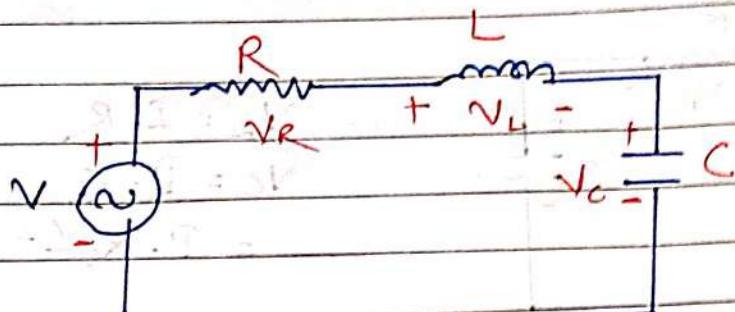


v/vs. in steady state.

$$VR = I \cdot R$$

$$VL = I \cdot X_L < 90^\circ$$

$$VC = I \cdot X_C < -90^\circ$$

① $VL > VC$

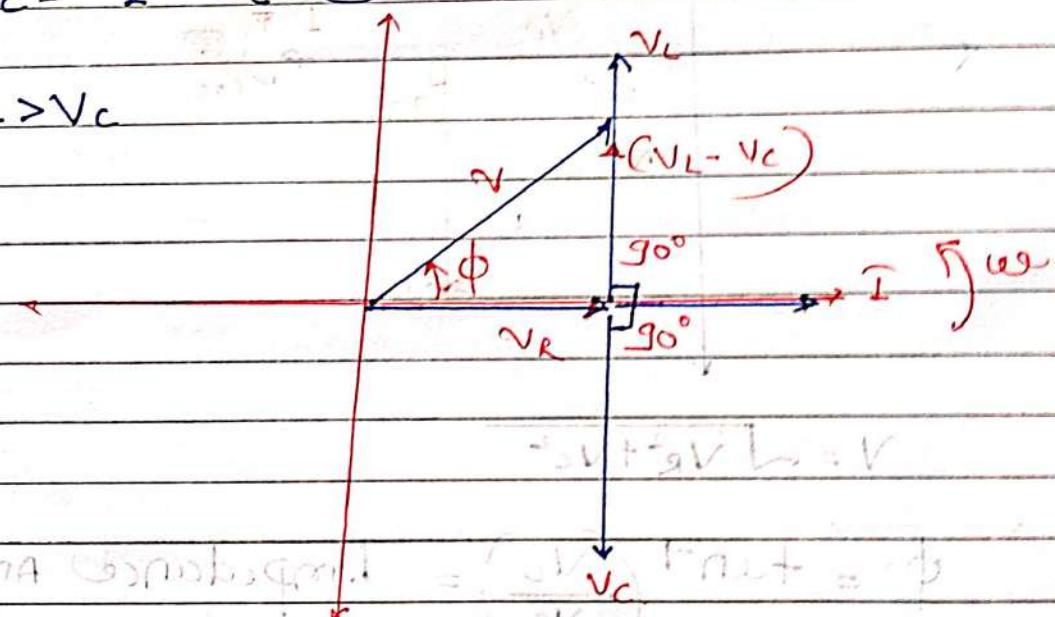

$$\text{Voltage } V_{eff} = \sqrt{VR^2 + (VL - VC)^2}$$


$$\phi = \tan^{-1} \left(\frac{VL - VC}{VR} \right)$$

= Impedance angle (i.e. "I" lags "V")

= Admittance Angle

$$\cos \phi = P.F. = \left(\frac{VR}{V} \right) \text{ (lag)}$$

② $V_C > V_L$

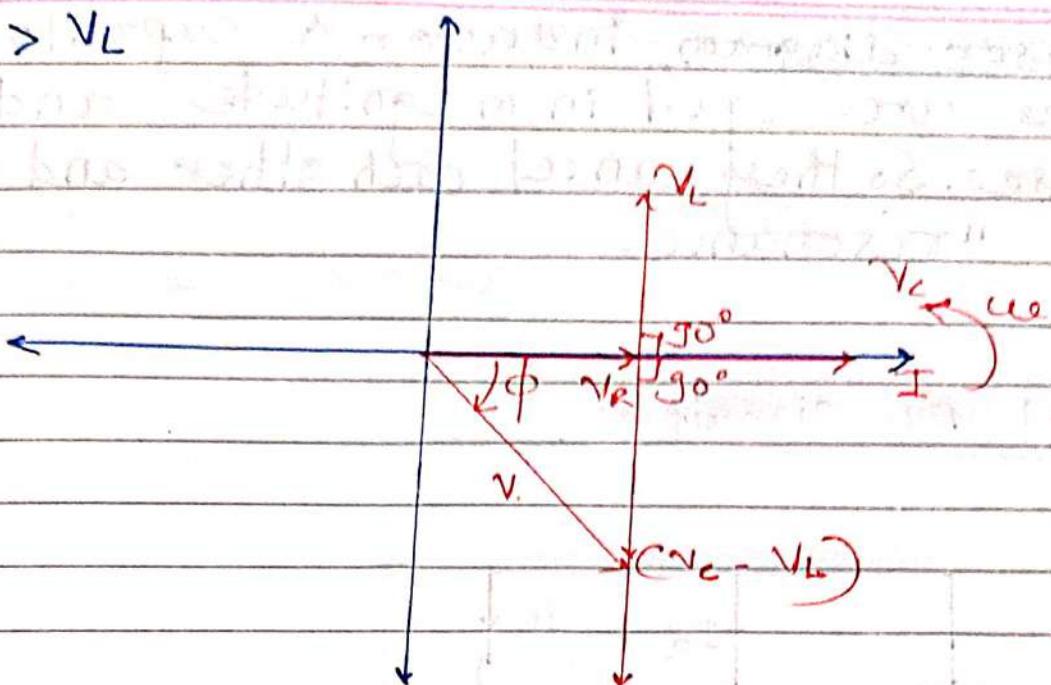

$$V = \sqrt{V_R^2 + (V_C - V_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{V_C - V_L}{V_R} \right)$$


= Impedance Angle

= Admittance Angle

$$\cos \phi = \text{Power factor} = \left(\frac{V_R}{V} \right) \quad (\text{lead})$$

"I" leads "V"


③ $V_L = V_C$

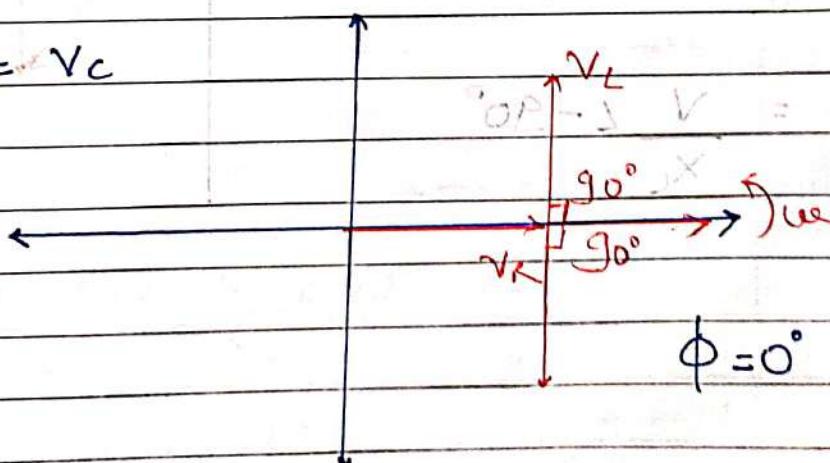

$\phi = 0^\circ \Rightarrow \text{unity power factor.}$

In phasor diagram, inductor & capacitor voltages are equal in magnitude and opposite in phase. So they cancel each other and this is called "resonance".

Parallel RL circuit :-

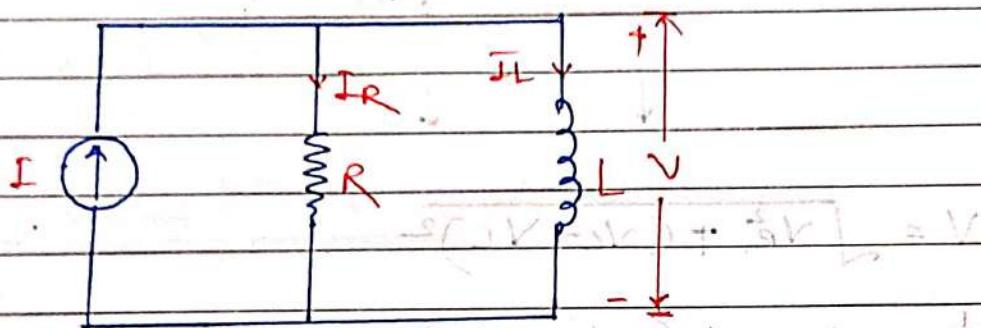


N/w. in steady state

$$I_R = \frac{V}{R}$$

$$I_L = \frac{V}{Z_L}$$
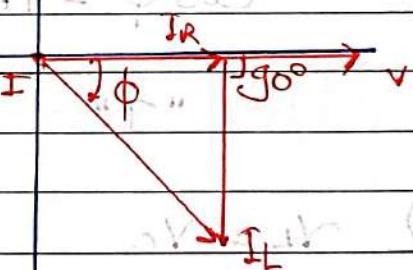
$$\Rightarrow I_L = \frac{V}{X_L} \angle -90^\circ$$




$$I = \sqrt{I_R^2 + I_L^2}$$

$\phi = \tan^{-1} \left(\frac{I_L}{I_R} \right)$ = Impedance Angle
 = Admittance Angle

$$\cos \phi = \text{P.F.} = \left(\frac{I_R}{I} \right) \text{ (lag)}$$

i.e. "I" lags "V"

Parallel RC circuit:

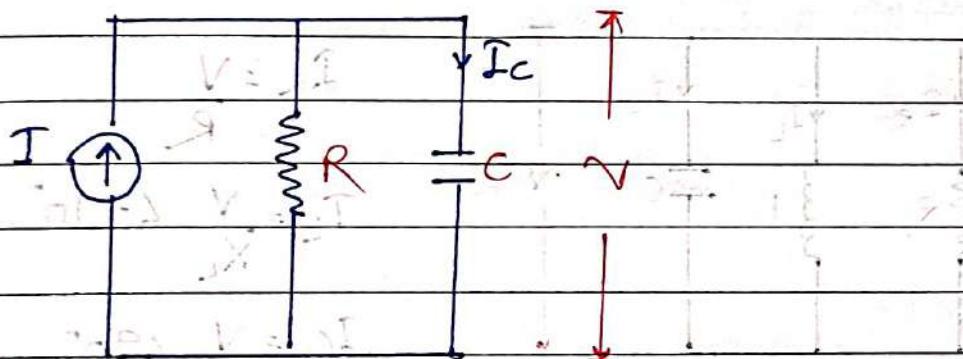


N/w is in steady state

$$I_R = \frac{V}{R}$$

$$I_C = \frac{V}{Z_C}$$
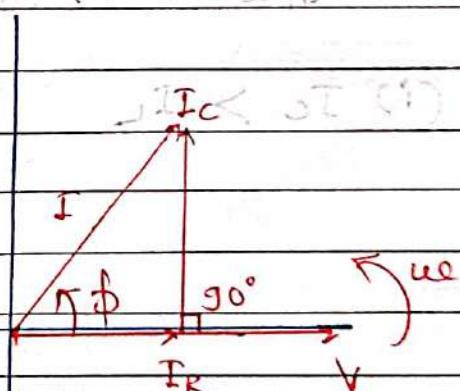
$$\Rightarrow I_C = \frac{V}{X_C} \angle 90^\circ$$



$$I = \sqrt{I_R^2 + I_C^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C}{I_R} \right) = \text{Impedance Angle}$$


$\hat{=}$ Admittance Angle

$$\cos \phi = \text{P.F.} = \left(\frac{I_R}{I} \right)$$


(lead)

i.e. "I" leads "V"

Parallel RLC circuit :-

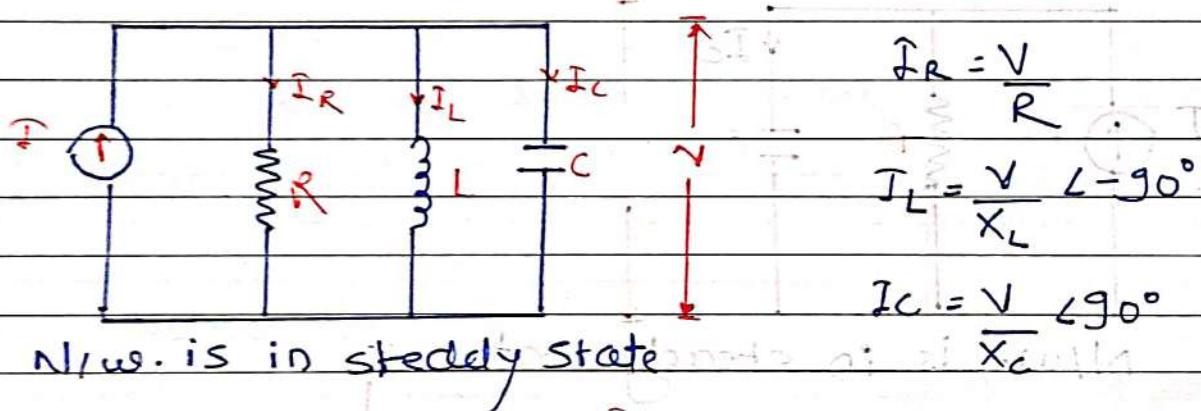

(i) $I_C > I_L$

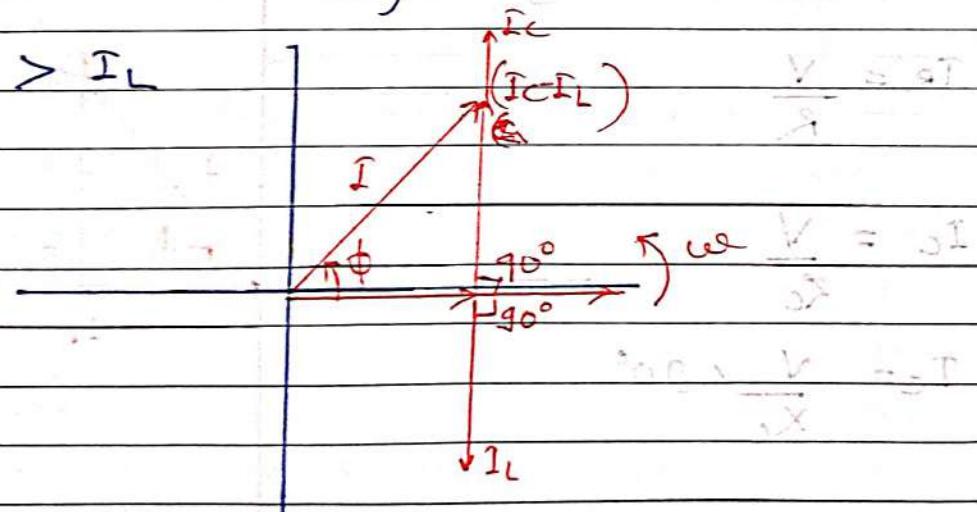


$$\Gamma = \sqrt{I_R^2 + (I_C - I_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C - I_L}{I_R} \right)$$


Γ = Impedance Angle
 ϕ = Admittance Angle

$$\cos \phi = \text{P.F.} = \left(\frac{I_R}{I} \right) \text{ (lead)}$$

(ii) $I_L > I_C$

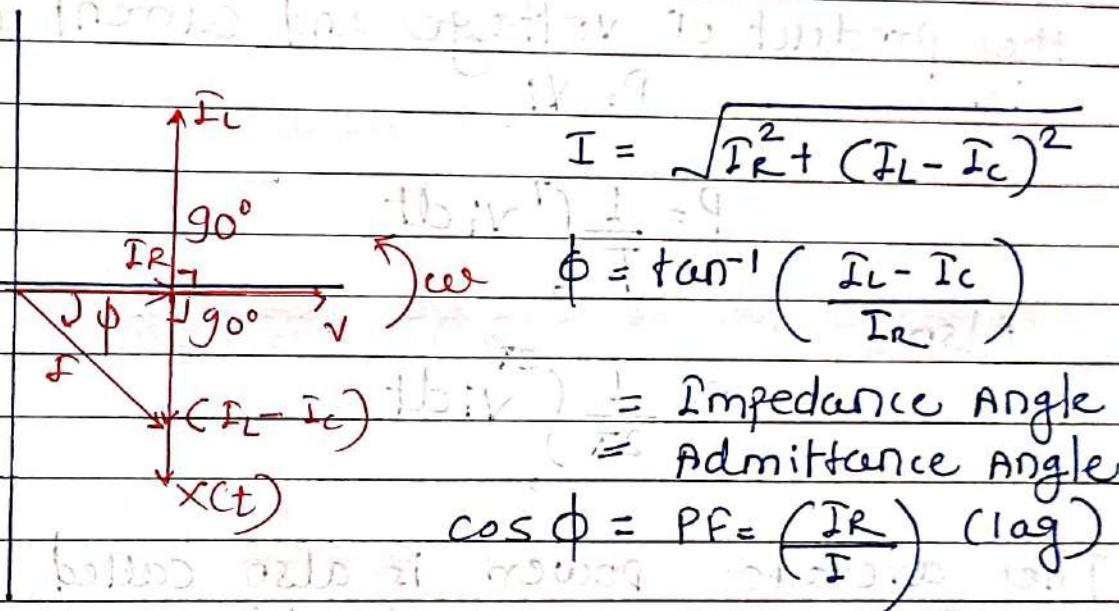

(iii) $I_L = I_C$

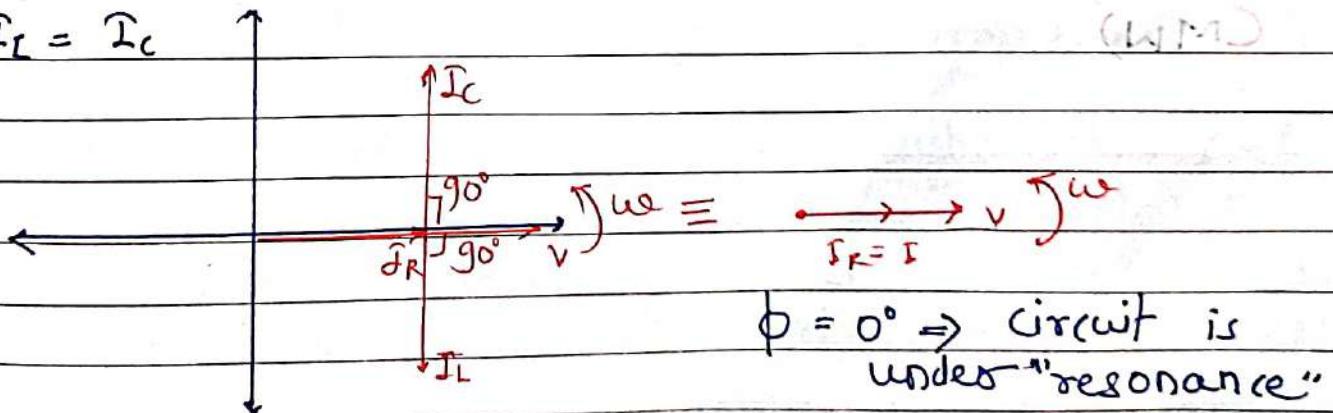

Power Calculations :-

Power relations in AC circuit:-

For a DC circuit, the power is given by

$$P_{DC} = VI = I^2 R = \frac{V^2}{R}$$

The power at any instant in an AC circuit is called instantaneous power. It is defined by the product of voltage and current at that instant.
i.e. $P = VI$

$$P = \frac{1}{T} \int_0^T V_i I_i dt$$

Also

$$P = \frac{1}{2\pi} \int_0^{2\pi} V_i I_i dt$$

The average power is also called the active power or true power and is measured in watts (W). The bigger units are kilowatts (kW) and megawatt (MW).

Power in Pure resistive circuits

The voltage and current in a pure resistive circuit are in phase and may be respectively represented by

$$v = V_m \sin \omega t$$

$$i = I_m \sin \omega t$$

The instantaneous power is given by

$$\begin{aligned} P &= vi \\ &= V_m I_m \sin^2 \omega t \\ &= \frac{1}{2} V_m I_m (1 - \cos 2\omega t) \end{aligned}$$

.. The active power is given by

$$\begin{aligned} P &= \frac{1}{T} \int_0^T vi dt = \frac{V_m I_m}{2T} \int_0^T (1 - \cos 2\omega t) dt \\ &= \frac{1}{2} V_m I_m \quad (\because \int_0^T \cos 2\omega t dt = 0) \\ &= \left(\frac{V_m}{\sqrt{2}} \right) \left(\frac{I_m}{\sqrt{2}} \right) = V_{rms} I_{rms} \text{ Watt.} \end{aligned}$$

The power waveform is positive throughout the cycle.
This is because voltage & current are in phase.

The power flows only in one direction. It is consumed in R & appears in the form of heat.

Power in pure Inductive Circuit

The voltage leads the current by 90° in a pure inductive circuit. Let the voltage and current at any instant be respectively represented by

$$v = V_m \sin(\omega t + 90^\circ) \text{ and } i = I_m \sin \omega t$$

The instantaneous power is given by

$$P = vi$$

$$= V_m I_m \sin(\omega t + 90^\circ) \sin \omega t$$

$$= \frac{1}{2} V_m I_m (2 \cos \omega t + \sin 2\omega t)$$

$$= \frac{1}{2} V_m I_m \sin 2\omega t$$

Active Power (OR) Average Power :-

$$P_L = \frac{1}{2T} \int_0^T V_m I_m \sin 2\omega t dt$$

$$= \frac{1}{2} V_m I_m \frac{1}{2\omega} (-\cos 2\omega t) \Big|_0^T$$

$$\therefore P_L = \frac{-V_m I_m}{4\omega T} (\cos 2\omega T - \cos 0)$$

$$\therefore P_L = \frac{-V_m I_m}{4\omega T} (\cos 4\pi - \cos 0)$$

$$\text{and } P_L = \frac{-V_m I_m (1-1)}{4\omega T} = 0$$

Therefore in a pure inductive circuit, the active power supplied over a complete cycle average power is zero.

Reactive Power:

The power supplied to a reactance (Inductive or capacitive) is termed reactive power. Unlike active power denoted by symbol P , the reactive power is denoted by symbol Q and given the name volt-amp-reactive (var). Let us now see how the reactive power is calculated.

The peak value of instantaneous power is given by

$$Q_L = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms}$$

for a pure inductive circuit

$$V_L = V_{rms} = X_L I_L$$

$$\therefore Q_L = (V_L I_L) \text{ mW} = T_{avg}$$

$$= I_L^2 X_L$$

$$\text{Also } Q_L = \frac{V_L^2}{X_L}$$

Here Q_L is rate of change of reactive energy between the load and the source.

By convention, Q_L is taken as positive and is called the lagging reactive power.

Power in Pure Capacitive Circuit

The voltage lags the current by 90° in a pure capacitive circuit. Let the voltage & current at any instant be represented by

$$v = V_m \sin \omega t \quad i = I_m \sin(\omega t + 90^\circ)$$

∴ The instantaneous power can be written as

$$P = vi = \frac{1}{2} V_m I_m \sin \omega t \sin(\omega t + 90^\circ)$$

$$= \frac{1}{2} V_m I_m \sin 2\omega t$$

Active power (or) Average Power

$$\begin{aligned} P_c &= \frac{1}{T} \int_0^T pdt = \frac{V_m I_m}{2T} \int_0^T \sin 2\omega t dt \\ &= -\frac{V_m I_m}{4\omega T} (\cos 2\omega t) \Big|_0^T \end{aligned}$$

$$\text{stands to zero} \Leftrightarrow -\frac{V_m I_m}{4\omega T} (1 - 1) = 0$$

Reactive Power

The peak value of instantaneous power can be written as

$$P_c = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms}$$

For a purely capacitive circuit

$$V_{rms} = V_c + j X_c I_c$$

$$\begin{aligned} Q_c &= V_c I_c \\ &= I_c^2 X_c \end{aligned}$$

OR $(Q_c = \frac{V_c^2}{X_c})$

Here Q_c is the rate of change of reactive power between the load & the source. By convention, Q_c is taken as negative & is called the leading reactive power.

Power in a general series circuit :-

For a passive ac circuit, let the voltage & current at any instant to be given by

$$v = V_m \sin \omega t$$

$$\text{& } i = I_m \sin(\omega t - \phi)$$

where ϕ is the phase difference between the voltage and the current. If ϕ is -ve, current leads the voltage.

The instantaneous power P is given by

$$P = vi$$

$$= V_m I_m \sin(\omega t - \phi)$$

$$= \frac{1}{2} V_m I_m (2 \sin \omega t \sin(\omega t - \phi))$$

$$\text{or } P = \frac{1}{2} V_m I_m (\cos \phi - \cos(2\omega t - \phi))$$

The average power P is given by

$$P_L = \frac{1}{2T} \int_0^T vi dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} (\cos \phi - \cos(2\omega t - \phi)) dt$$

$$= \frac{V_m I_m}{2T} \left[\int_0^T \cos \phi dt - \int_0^T \cos(2\omega t - \phi) dt \right]$$

$$\frac{V_m I_m}{2T} \times \cos\phi \times T \quad \left(\because \int_0^T \cos(2\omega t - \phi) dt = 0 \right)$$

$$\frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos\phi = V_{rms} I_{rms} \cos\phi$$

The product of V_{rms} & I_{rms} is called the apparent power and P is called the true or real power.

True Power = Apparent power $\times \cos\phi$

True (real) power = Apparent power \times Power factor
 That is, the product of rms values of voltage & current with the cosine of the angle between them (i.e. the power-factor) is called the real power or true power denoted by symbol P .

Reactive Power :-

We can now generalize our previous definition and state that the product of rms values of voltage & current with the sine of the angle between them is called the reactive power Q .

$$\therefore Q = V_{rms} I_{rms} \sin\phi$$


The reactive power is also called the wattless power or quadrature power. The table represents the different expressions of power in ac series circuits.



Circuit	Power factor	Real power	Reactive power	Apparent power
R	1	$V_{rms} I_{rms}$	0	$V_{rms} I_{rms}$
L	0	$V_{rms} I_{rms}$	$V_{rms} I_{rms} \text{ (lag)}$	$V_{rms} I_{rms}$
C	0	$V_{rms} I_{rms} \text{ (lead)}$	$V_{rms} I_{rms}$	$V_{rms} I_{rms}$
RL	$\cos \phi \text{ (lag)}$	$V_{rms} I_{rms} \cos \phi$	$V_{rms} I_{rms} \sin \phi$	$V_{rms} I_{rms}$
RC	$\cos \phi \text{ (lead)}$	$V_{rms} I_{rms} \cos \phi$	$V_{rms} I_{rms} \sin \phi$	$V_{rms} I_{rms}$
RLC	$\cos \phi \text{ (lead)}$	$V_{rms} I_{rms} \cos \phi$	$V_{rms} I_{rms} \sin \phi$	$V_{rms} I_{rms}$
	$\cos \phi = 1$ (in phase)	$V_{rms} I_{rms}$	0	$V_{rms} I_{rms}$

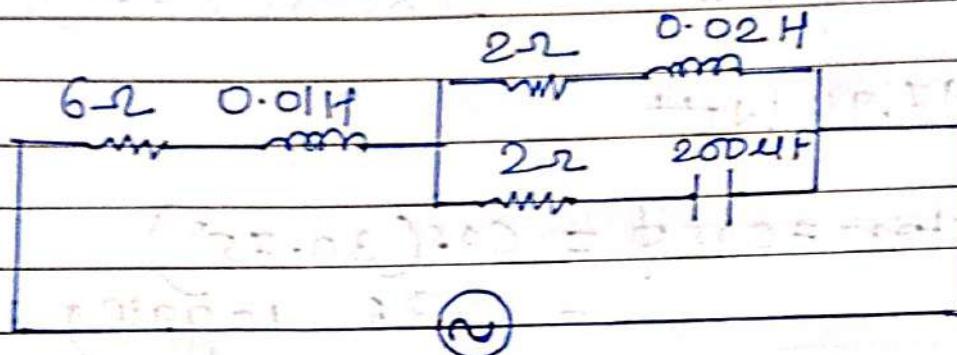Example :-

Determine the current in the circuit of fig. Also, find the power consumed as well as power factor.



200 V. 50Hz.

$$X_{L1} = 2\pi \times 50 \times 0.02 = 3.14 \Omega$$

$$X_{L2} = 2\pi \times 50 \times 0.01 = 3.14 \Omega$$

$$X_C = \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}} = 15.92 \Omega$$

$$\bar{Z}_1 = 6 + j3.14 \Omega$$

$$\bar{Z}_2 = 4 + j6.28 \Omega$$

$$\bar{Z}_3 = 2 - j15.92 \Omega$$

$$\bar{Z} = \bar{Z}_1 + \frac{\bar{Z}_2 \times \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3}$$

$$= (6 + j3.14) + \frac{(4 + j6.28)(2 - j15.92)}{(4 + j6.28) + (2 - j15.92)}$$

$$= 17.27 \angle 30.75^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{17.27 \angle 30.75^\circ}$$

$$= 5.792 \angle -30.75^\circ \text{ Amp.}$$


$$P = V I \cos \phi = 100 \times 5.79 \times \cos(30.75^\circ)$$

$$= 497.94 \text{ Watt}$$

Power factor = $\cos \phi = \cos(30.75^\circ)$
 $= 0.86$ lagging.

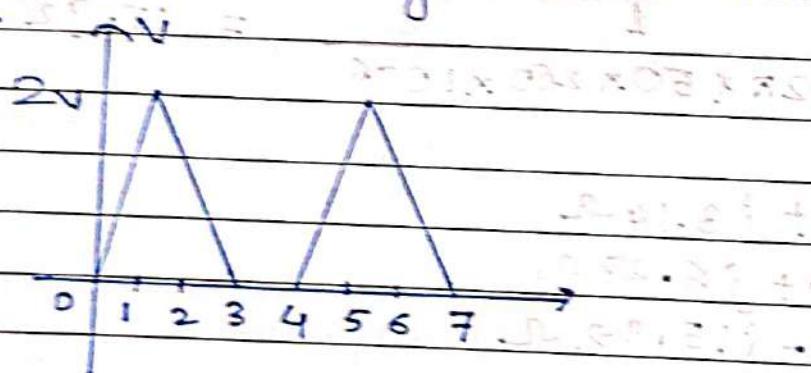Example :-

Find the average power delivered to a 10Ω resistor with a voltage across it as shown in the figure.



$$V_{rms} = \sqrt{\frac{1}{4} \int_0^4 (v)^2 dt}$$

$$= 2 \times \sqrt{\frac{1}{4} \int_0^{1.5} \left(\frac{3}{4}t\right)^2 dt}$$



$$\frac{1}{2} \int_0^{1.5} \frac{9}{16} t^2 dt$$

$$= \frac{1}{2} \times \frac{9}{16} \times \frac{t^3}{3} \Big|_0^{1.5}$$

$$V_{rms} = \frac{3}{2 \times 16} \times (1.5)^3 = 0.316$$

$$P = \frac{(V_{rms})^2}{R} = \frac{(0.316)^2}{10} = 100 \text{ milliwatt.}$$