

Module-I.

⇒ Frequency Response of an Amplifier.

* Objective of Module I: Determine the "speed limitations" of circuits.

* Preview:


→ Amplifier :- It is the term used to describe a circuit which increases its input signal, but not all amplifiers are the same as they classified according to their circuit configurations & methods of operation.

- In Electronics, small signal amplifiers are commonly used devices as they have the ability to amplify a relatively small input signal, Eg: Sensor such as photo-device, into a much larger output signal to drive a relay, lamp or loud-speaker.
- The classification of an amplifier depends on the size of the signal, large or small, its physical configuration & how it processes the i/p signal that is the relationship between i/p signal & current flowing in the load.


→ what do we mean by Speed Limitations of circuits:

- It means what does the circuit do if we give high frequency to the circuit.
- Assume we bought the amplifier, & we gave a pulse s/g in time domain.

- I case :

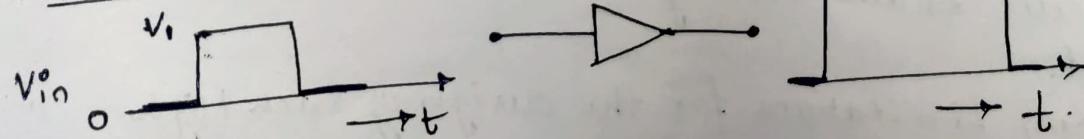

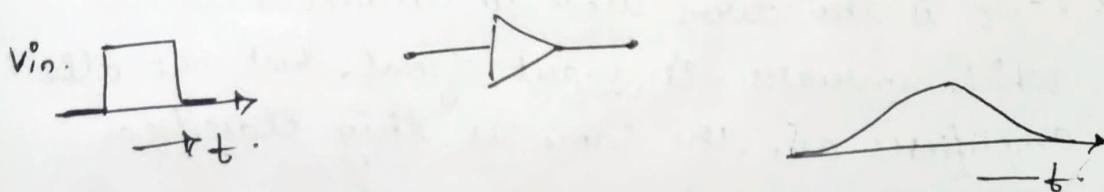- The above amplifier follows the i/p pretty well, jumps up the o/p i.e. amplified the i/p signal pretty well, it may be amplified the original voltage of 100mV to 200mV.
- So we can say that such amplifier are good, Fast amplifier because the o/p response quickly to the i/p changes.
- Now assume the II case,



- As the above amplifier is not capable of changing or response frequently due to the change happening in i/p.
 - So we can say that the above amplifier is a slow amplifier.
 - So that is how we need to study the limitation of the speed of the circuit.
 - why need to study this?
 - If you look around, there are lot of circuits you come across everyday which are high-speed circuits.
- for e.g:
- ① wi-fi - which operates around 2.4 GHz, 5GHz.
 - ② Bluetooth - operates 2.4 GHz.
 - ③ GPS - operates around 1.5 GHz.
 - ④ ~~Radar~~ RADAR - particularly automotive radars: 26 GHz - 75 GHz.
 - ⑤ microprocessors: 4- GHz - 5GHz .


- This is how we have lots of circuits which are even on high speed.-
- There are many limitations for the design of such high speed circuit.

(3)

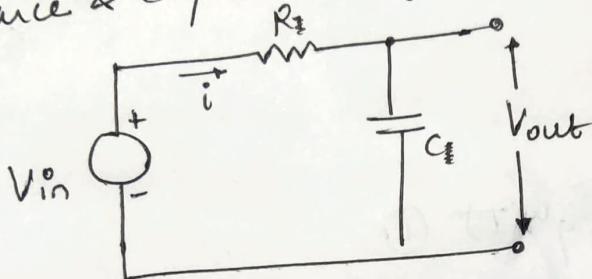(5)

I] R-C circuit Analysis:

- Let's assume the RC, simple circuit with input voltage V_{in} & output voltage, V_{out} . where R_L & C are the active resistance & capacitance of the circuit.



(a) Time Domain Analysis:

- Since it's 'i' the current flowing in the circuit is a function of 't', therefore current will be the function of time. i.e $i(t)$ likewise voltage i.e $V(t)$.
- Use KVL to the above circuit, V_{in} is equal to Voltage across Resistance + Voltage across the capacitor.

$$V_{in} = R_i i(t) + \underline{V(t)} \quad \text{Voltage across capacitor}$$

where $V(t) = \frac{1}{C} \int_0^t i(t) dt$ \rightarrow voltage across the capacitor. (1)

$$\therefore V_{in} = R_i i(t) + \frac{1}{C} \int_0^t i(t) dt$$

take derivative of above eqn.

$$\therefore 0 = R \frac{di(t)}{dt} + \frac{1}{C} i(t) \quad \begin{matrix} \leftarrow \\ \text{First order differential} \\ \text{Equation.} \end{matrix}$$

divide above eqn by 'R'

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = 0$$

Solving above equation. i.e Differential Equation.

$$i(t) = I_0 e^{-\frac{t}{\tau}}$$

(4)

where τ is a time constant,
 $\tau = RC$.

when $t=0$

$$i(0) = \frac{V_{in}}{R} \quad \therefore I_0 = \frac{V_{in}}{R} \Rightarrow \text{Substitute } I_0 \text{ in the } i(t) \text{ Eqn.}$$


$$i(t) = \frac{V_{in}}{R} e^{-\frac{t}{\tau}}$$

Substitute $i(t)$ in Eqn ~~①~~ ①

$$V_o(t) = \frac{1}{C} \int_0^t \frac{V_{in}}{R} e^{-\frac{t}{RC}} dt$$

$$\boxed{V_o(t) = V_{in} \left(1 - e^{-\frac{t}{\tau}} \right)}$$

$$\text{where } \boxed{\tau = RC}.$$

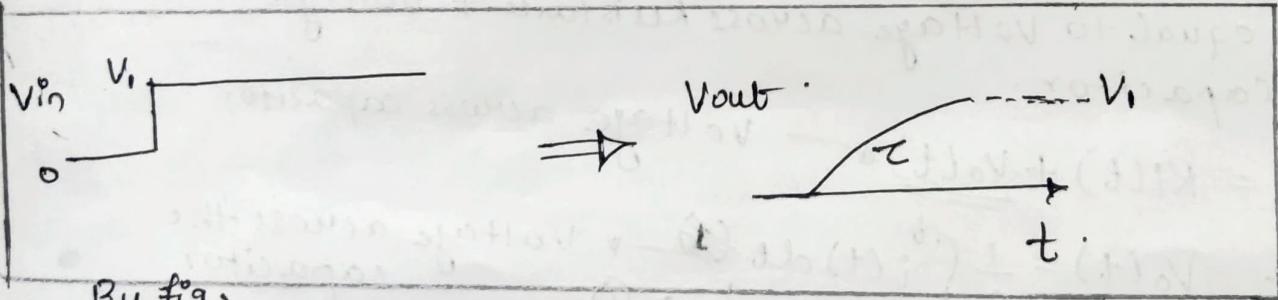

By fig,


- V_{in} is a function of time, where V_{out} is a exponential equation which is trying to reach V_i with time constant τ .
- This V_{out} cannot respond quickly to i/p change if this time constant (τ) is excessively long.
- So to improve the speed of the circuit we must minimize ' R, C '

(b) Frequency Domain Analysis: Preview:

- This frequency Domain analysis formulates the response to sinusoidal inputs
 - whereas sinusoidal means signals which are $\sin \omega t$ or $\cos \omega t$, $\omega \rightarrow$ frequency of sig.
 - Lets understand the output frequency of RC circuit by 3 cases, pictorial representation.


1 case:

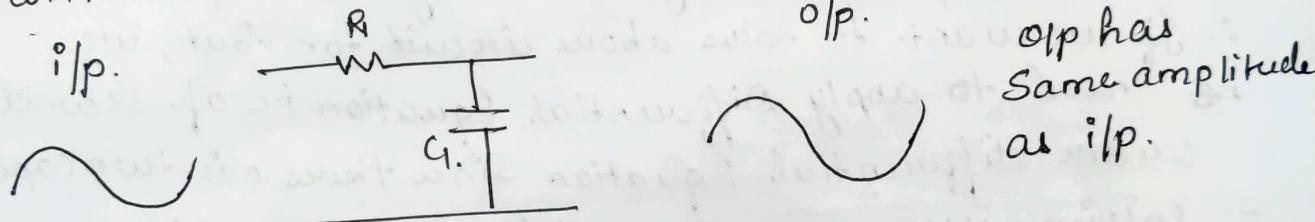1 case: with a normal sinusoidal signal with normal frequency :-




2 case:

with a higher frequency:

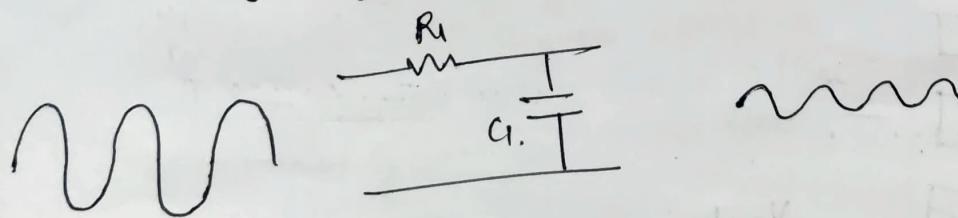

For higher freq.
ilp, the clp
attenuated &
given shorter
amplitude.

3 case:

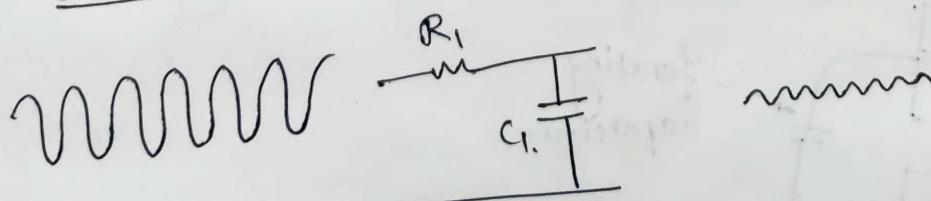


More attenuation to the op.

- So this is what we need to understand the complex circuit frequency analysis, how the given circuit response to the different higher frequency.


- As we see from the above pictorial representation, we can assume that as the frequency ω increases the signal experiences attenuation.

→ Why we go from time Domain Analysis to frequency Domain Analysis? / Need of Frequency Domain:

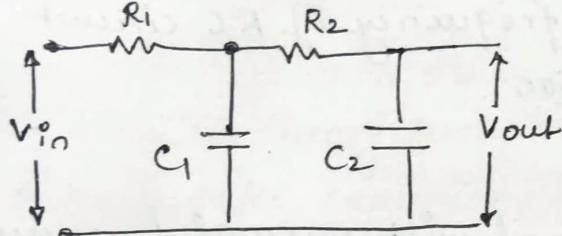- Let's assume the circuit other than RC simple circuit,



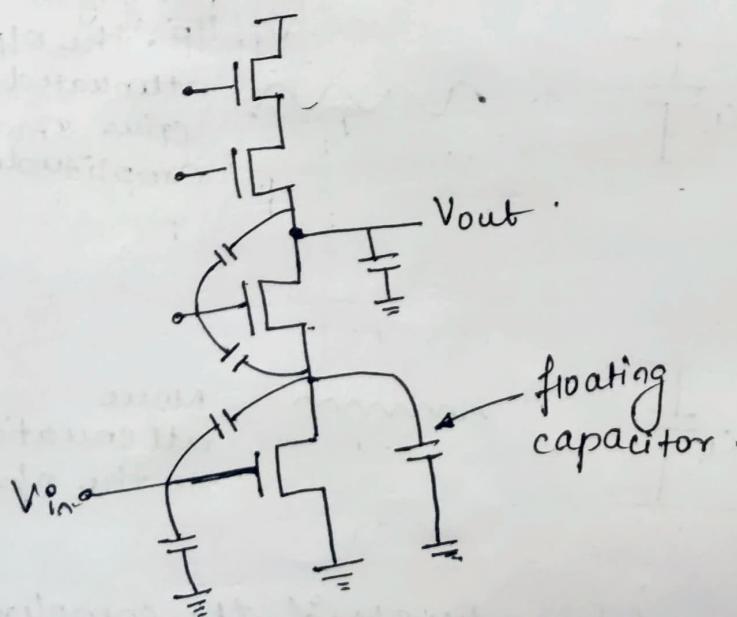- Since the capacitor charges & discharges w.r.t time
 \therefore If we want to solve above circuit for V_{out} , we need to apply Differential Equation i.e of Second Order differential Equation since there is two capacitors.
- Solving differential equation of higher order is not feasible.
- What if we have cascode circuit like below,




- If we are interested in frequency response above circuit, we need to assume lot of floating circuit between the MOSFET's.

- For so many capacitor, we need to solve Higher to Higher Order Differential Equation which is not feasible.
- To avoid the complexity, If we perform the analysis in frequency domain, the result interpretation will be easier than the Time Domain Analysis.

⇒ Lets Review circuit theory concepts:

- To proceed with other theory we require some circuit theory concepts.
- Lets take capacitor, since it is more complex component in any circuit.
- To Develop Higher circuit & complex we will proceed with basic circuit first.

①

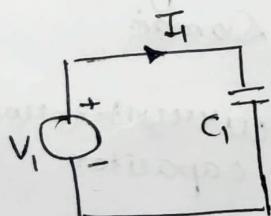

Time Domain.

- we already know,
the current flowing
through the capacitor
is equal to
the capacitor value times to the
derivative of voltage across the
capacitor.

i.e

$$I_1 = \frac{dV_1}{dt}$$

Freq. Domain.


$$I_1 = C_S V_1$$

$$\frac{V_1}{I_1} = \frac{1}{C_S}$$

where,

$\frac{V_1}{I_1}$ called as

- Impedance of the circuit.
- Impedance is similar to resistance Except it applies to reactive devices such as capacitor, inductor.

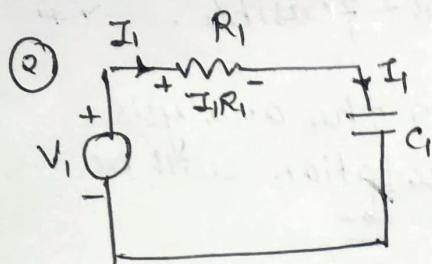Time Domain.

$$V_1 = \text{Voltage across Resistor} + \text{Voltage across Capacitor}$$

$$= R_1 I_1 + \frac{1}{C_1} \int I_1 dt$$

[we have, $I_1 = C_1 \frac{dv}{dt}$
Integrate to obtain
 v]

$$\therefore V_1 = R_1 I_1 + \frac{1}{C_1} \int I_1 dt$$


Frequency Domain.

$$V_1 = I_1 R_1 + \frac{I_1}{C_1 s}$$

$$\left[\frac{V_1}{I_1} = \frac{1}{C_1 s} \right]$$

$$\therefore V_1 = \frac{I_1}{C_1 s}$$

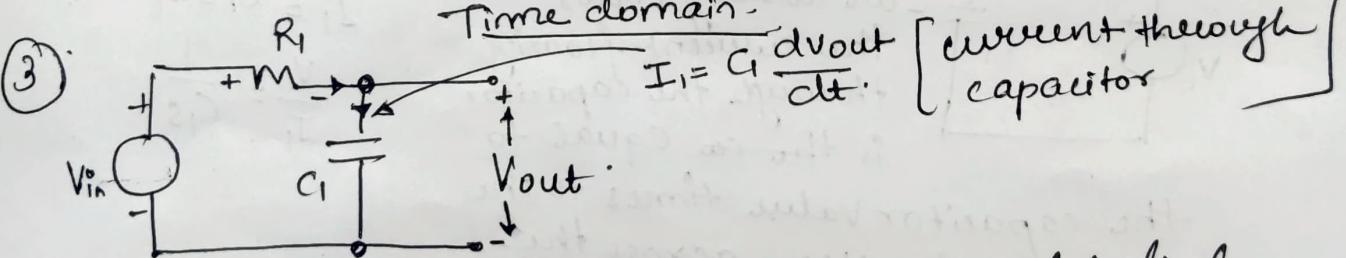\therefore The Equation obtained from frequency Domain analysis is easier to solve than Time Domain.



Take same circuit as above, now we need to find V_{out} i.e. output voltage.


- current flowing through capacitor is $I_1 = \frac{C_1 dv_{out}}{dt}$.
- Now same current going through R_1 which gives voltage drop of $R_1 C_1 \frac{dv_{out}}{dt}$. $\therefore V_R = R_1 I_1$

$$V_{in} = V_R + V_{out}$$

$$V_{in} = R_1 C_1 \frac{dv_{out}}{dt} + V_{out}$$

Frequency Domain.

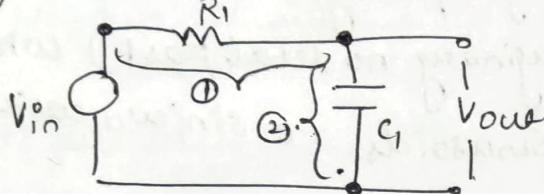- If you will see the R-C circuit there are two impedances through the terminals.



- These two impedances acting as a voltage divider of the circuit

$$\therefore V_{out} = \frac{\text{Impedance through capacitor}}{\text{Impedance through capacitor} + \text{Impedance through Resistor}} \times V_{in}$$

$$\boxed{V_{out} = \frac{\frac{1}{C_1 s}}{\frac{1}{C_1 s} + R_1} V_{in}} \quad \left\{ \begin{array}{l} \text{Parallel} \\ \text{circuit} \end{array} \right\}$$

$$\therefore V_{out} = \frac{\frac{1}{C_1 s}}{\frac{1 + R_1 C_1 s}{C_1 s}} \cdot V_{in}$$

$$\boxed{V_{out} = \frac{1}{R_1 C_1 s + 1} \cdot V_{in}}$$

where $\frac{1}{R_1 C_1 s + 1}$ is called as Transfer function of the circuit

since it is tell us how the i/p is transfer to the o/p.

this, $\frac{1}{R_1 C_1 s + 1}$ Represent as $H(s)$.

$$\therefore \boxed{H(s) = \frac{1}{R_1 C_1 s + 1}}$$

~~Complex number preview~~ \Rightarrow Transfer Function.

- 's' is generally a complex frequency, we can assume that $s = j\omega$, (just an imaginary no real part) when signals of interest are sinusoids. i.e. $\sin j\omega$, $\cos j\omega$.

~~Ques~~ - Let's the $H(s)$ we obtained through RC circuit,


$$H(s) = \frac{1}{R_1 C_1 s + 1}$$

If we say input signal i.e. V_{in} is a sinusoidal signal then $s = j\omega$.

$$\therefore H(j\omega) = \frac{1}{R_1 C_1 j\omega + 1}$$

= complex number preview:

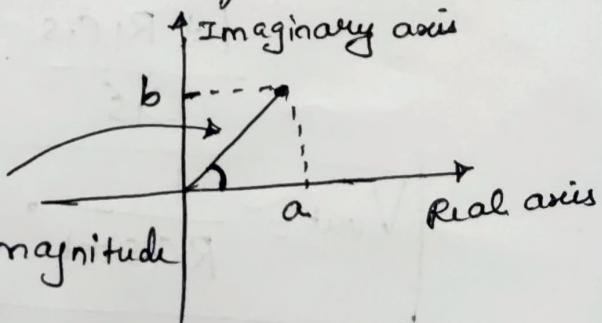A complex number ~~is~~ $a + jb$ can be represented in polar form:



- length of this line called as magnitude of complex No.

- The angle made by that line is called phase angle.

$$\boxed{\text{magnitude} = \sqrt{a^2 + b^2}}$$

$$\boxed{\text{phase} = \tan^{-1} \frac{b}{a}.}$$

Let's take the magnitude of Transfer function of RC circuit.

$$H(s) = \frac{1}{R_1 C_1 s + 1}$$


$$H(j\omega) = \frac{1}{R_1 C_1 j\omega + 1} \Rightarrow \frac{1}{1 + j R_1 C_1 \omega}$$

compare with $a + jb$.

where $a = 1$, $b = R_1 C_1 \omega$.

$$\therefore |H(j\omega)| = \frac{1}{\sqrt{1 + R_1^2 C_1^2 \omega^2}} \Rightarrow \frac{1}{\sqrt{R_1^2 C_1^2 \omega^2 + 1}}$$

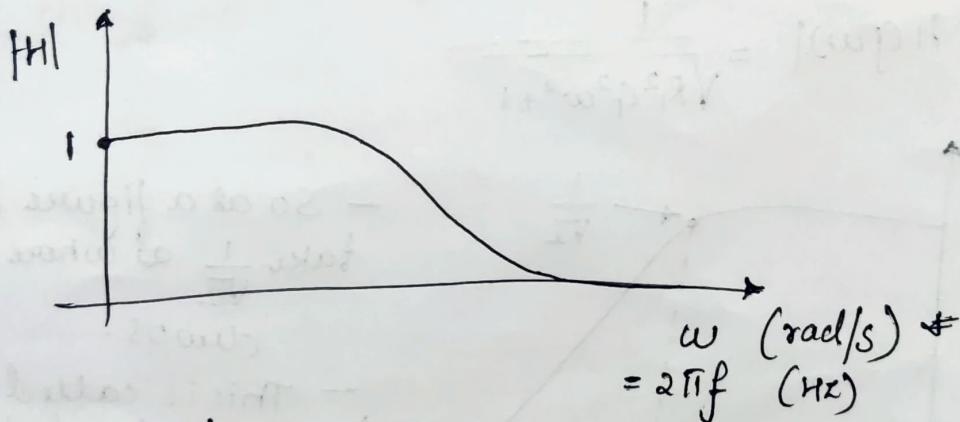Let's plot the above circuit Transfer function



$$\text{If } \omega = 0, |H| = 1$$

If we increase ω , the value ~~$R_1^2 C_1^2 \omega^2$~~ will drops.

If ~~the~~ ω reaches to infinity, the value will become 0.

- Therefore, $\omega \uparrow$ i.e. frequency increases, the circuit will drop.


- In the start we applied low frequency, the circuit gain is 1, as frequency increases the ~~the~~ gain drops & ultimately at High frequency the ~~the~~ gain is 0,

Shows nothing.


→ How to compute the frequency Response.

- ① Determine the Transfer Function, $H(s)$
- ② Replace s with $(j\omega)$ $\Rightarrow H(j\omega) \rightarrow$ (giant complex number)
- ③ Compute the magnitude of $H(j\omega)$ i.e $|H(j\omega)|$
 $|H(j\omega)| \Rightarrow$ frequency Response.
- ④ Plot the Response to interpret circuit is fast & slow.

Example:

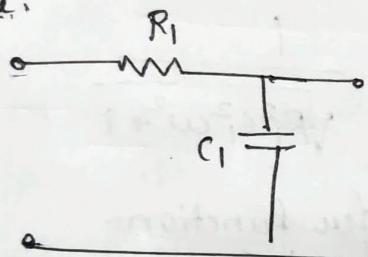

$$|H(j\omega)| = \frac{1}{\sqrt{R_1^2 + C_1^{-2}\omega^2}}$$

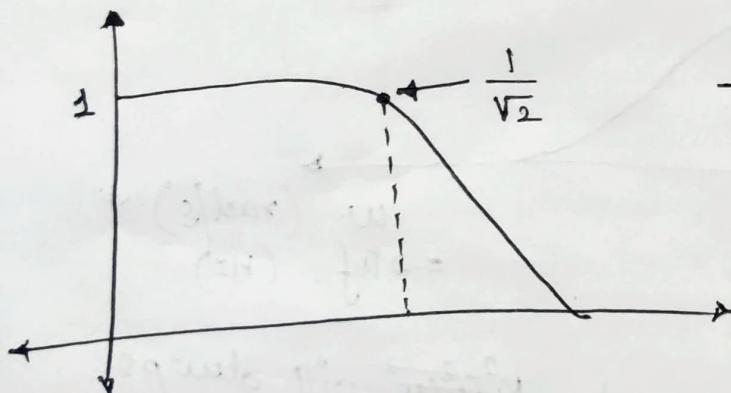


- So as a figure of merit take $\frac{1}{\sqrt{2}}$ where magnitude drops.
- This is called as bandwidth of circuit.

- we have one point to measure the goodness of the circuit i.e Bandwidth.

- Bandwidth means the freq. range across which the input signal will go the o/p.


- Analyse above plot.

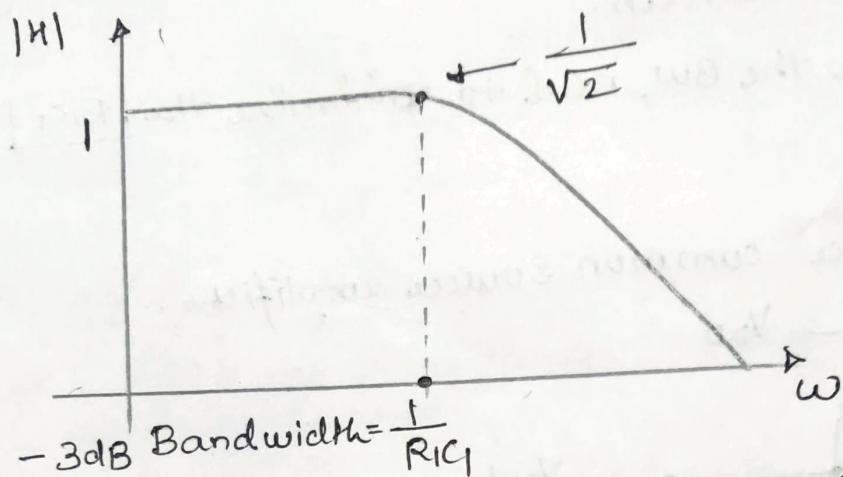- Equate $\frac{1}{\sqrt{R_1^2 + C_1^{-2}\omega^2}} = \frac{1}{\sqrt{2}} = \frac{1}{R_1 C_1}$



-3dB means the output is 3dB which is less than the input. ∵ the gain is $\frac{1}{\sqrt{2}} < 1$.

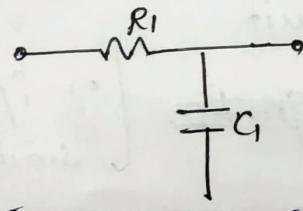
- why this circuit attenuates at this frequency?
- consider the above RC circuit



- In the start, The impedance $(\frac{1}{j\omega C_1})$ was large, ∵ ω is small.
- So we can consider as open circuit and Reduces to this.

It goes through this give gain = 1

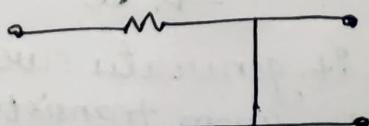- If High frequency passes, the impedance of capacitor drops, capacitor act as a short circuit. circuit will become short circuit.




- So we get nothing on the output circuit. That is why circuit attenuates on high frequency.


Wp.

- So from the previous interpretation, capacitors generally affects the Bandwidth.
- To maximize the BW, need to minimize the R_{C_1} i.e basically capacitor.

Example: Take common source amplifier.

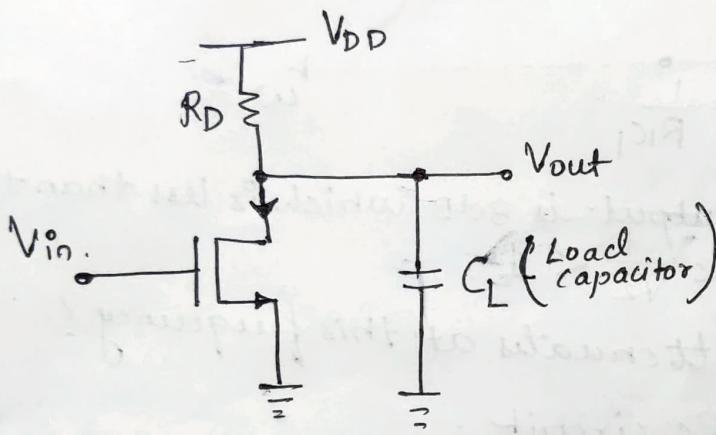

- $|Av|$ is a voltage gain of the circuit.
- where $|Av| = \frac{\text{Output Amplitude}}{\text{I/p Amplitude}} = \underline{gmR_D}$. $\left[\because \text{I/p is sinusoidal} \right]$
- At low freq. the capacitor (C_L) is an open circuit, because the current through the capacitor is small, so now there is only transistor & Resistor in circuit, so the gain is $\underline{-gmR_D}$, since it is magnitude.

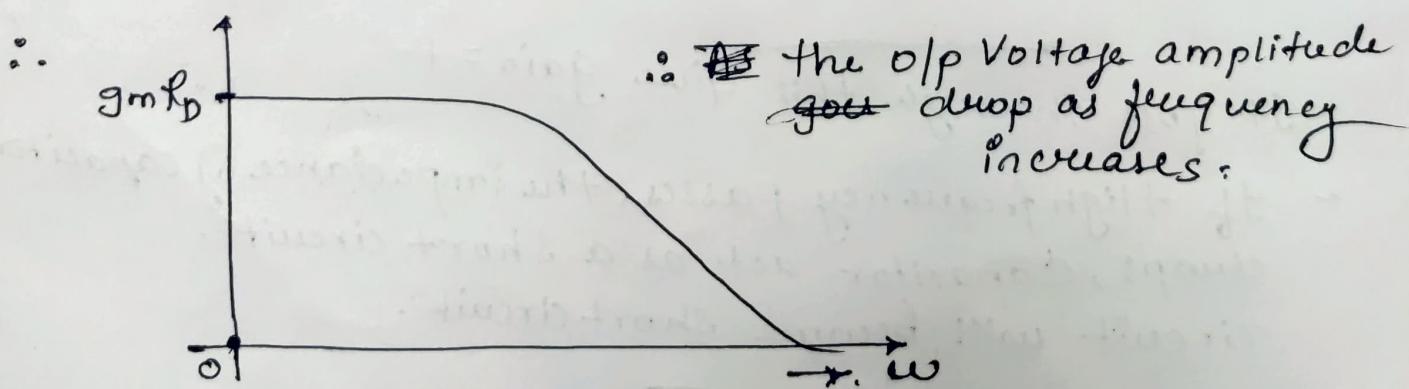

- As the frequency goes up, it generates current inside the transistor, this current coming from transistor, only less current coming from Resistor, The voltage across Resistor is small ∴ The o/p gain goes down.

\Rightarrow Poles & Zeros - Preview

$$H(s) = \frac{N(s)}{D(s)} = \frac{\text{Numerator}}{\text{Denominator}}$$

Generally, Roots of Numerator called as zeros &
Roots of Denominator called as poles.


\Rightarrow Bode's Rules :- To construct frequency response by using poles & zeros of transfer function.

Ist Rule : As 'w' approaches the pole


Ist Rule : As 'w' passes the pole frequency the slope of $|H(j\omega)|$ decreases by 20dB/dec .

- 20dB/dec means if frequency goes up by factor of 10 the magnitude changes the factor of 10

Example . ①

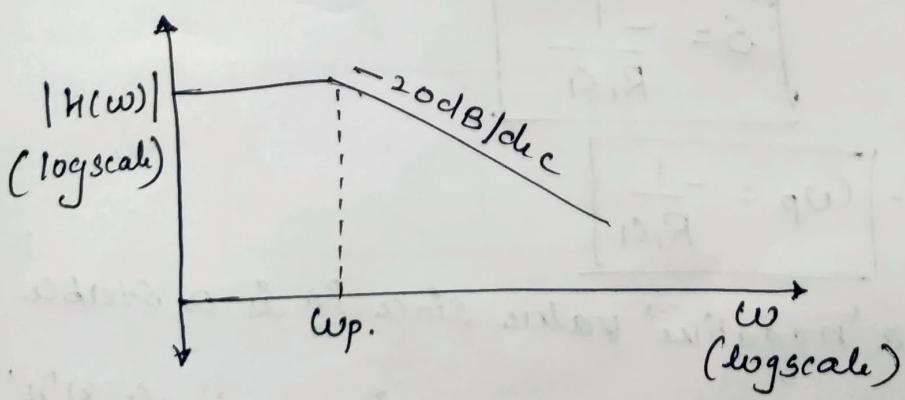


②

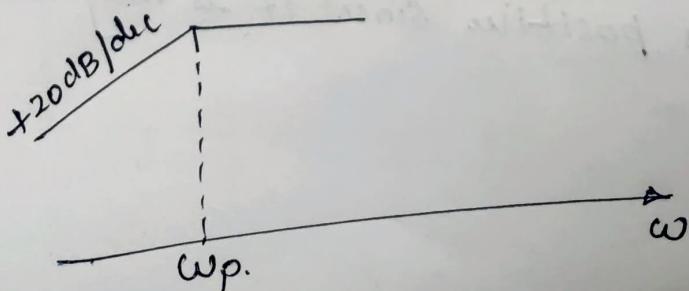


IInd Rule: As ω passes a zero frequency, the slope of $|H(\omega)|$ increases by 20 dB/dec .


Example ①

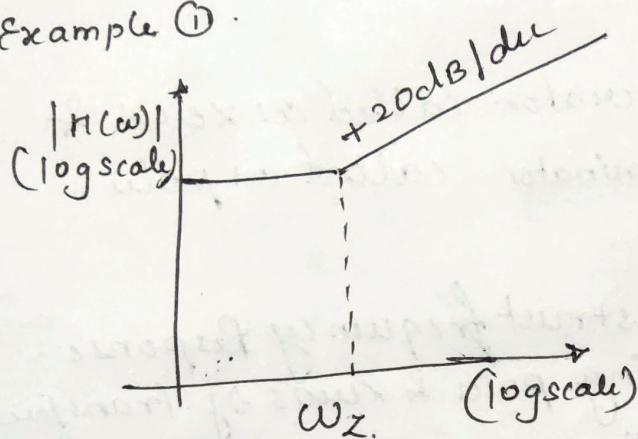

②

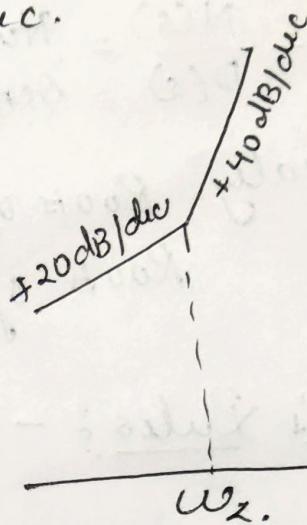

Example:

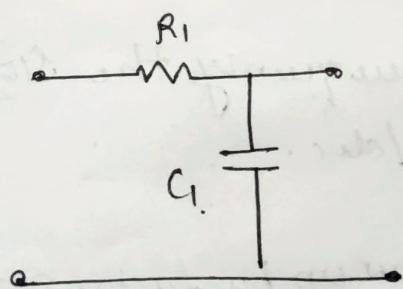

$$H(s) = \frac{1}{R_1 C_1 s + 1}$$

- There is NO zero.

- Roots of denominator to obtain pole frequency

$$R_1 C_1 s + 1 = 0$$

$$R_1 C_1 s = -1$$


$$\boxed{s = -\frac{1}{R_1 C_1}}$$

$$\therefore \boxed{\omega_p = -\frac{1}{R_1 C_1}}$$

- The pole has a 'negative' value since it is a stable circuit

- we take ω_p as positive since it is magnitude of H

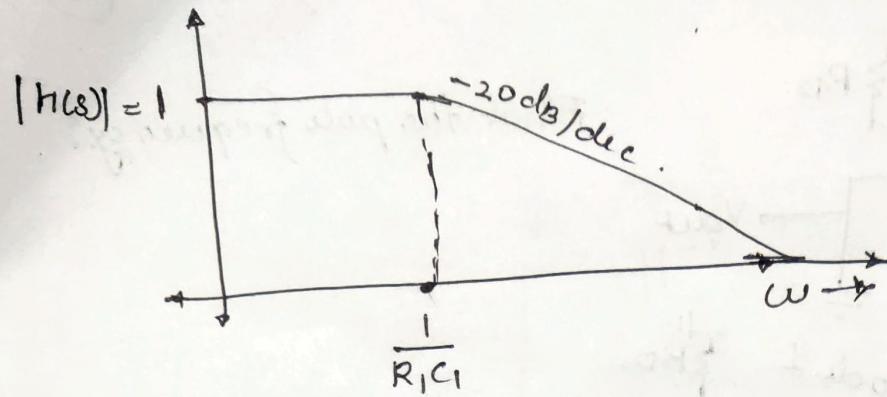
$$\therefore \omega_p = \frac{1}{R_1 C_1}$$



At low frequency, $\omega=0$ $|H(\omega)|=1$


\Rightarrow Finding poles by inspection:

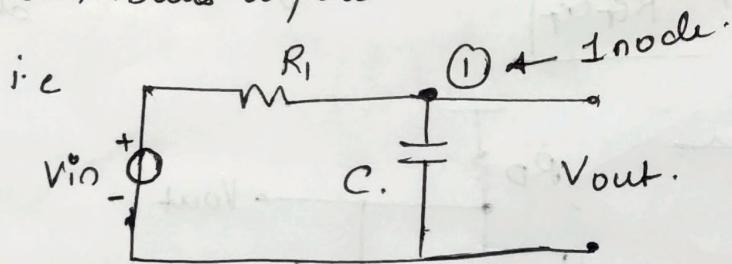- We can estimate or assume that each node in the signal path contributes a pole.




To calculate the pole:

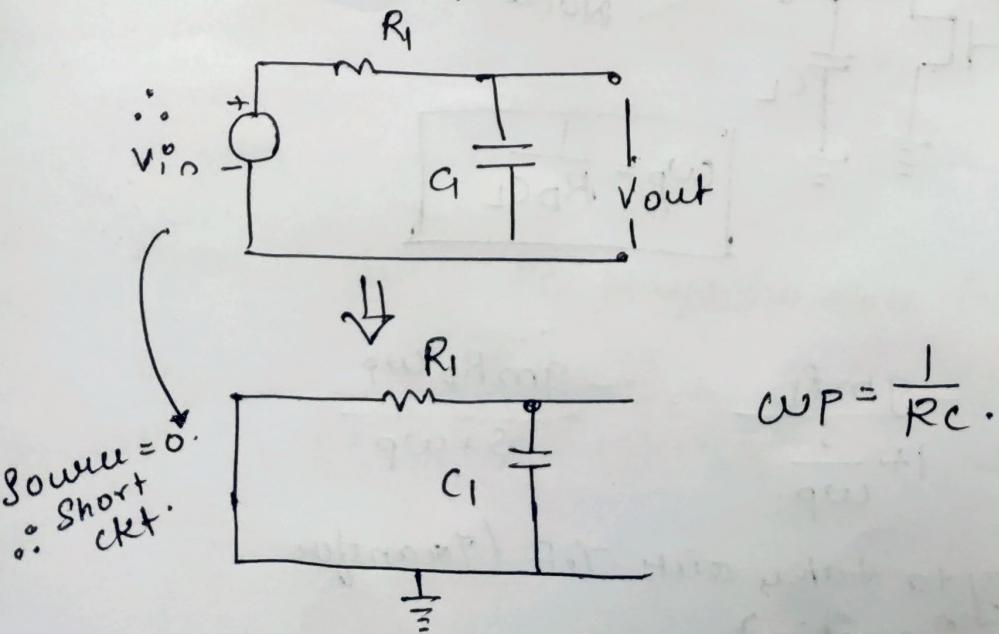
- (a) Find the Resistance from that pole to an AC ground.
 - (b) Find the capacitance from that node to an AC ground.
- Both cases applicable when $S_{out} = 0$.



Q.

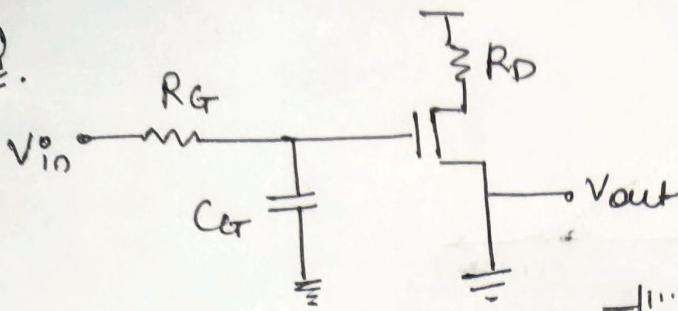


Find the pole frequency?

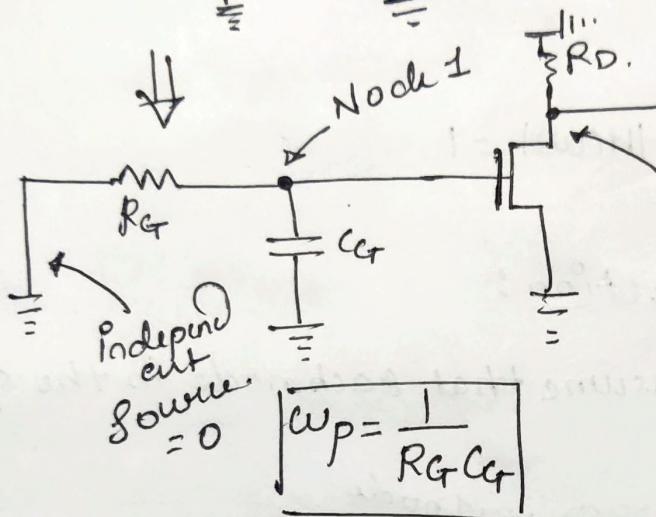


this can't be node because there is no capacitance from the node to AC Gnd only Resistance won't do.

Q.

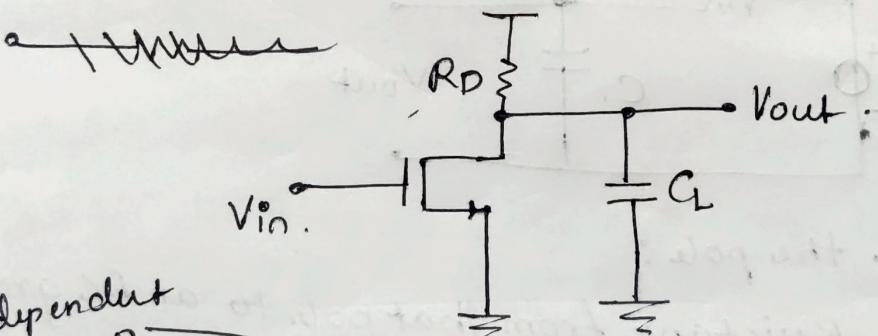

independent source = 0

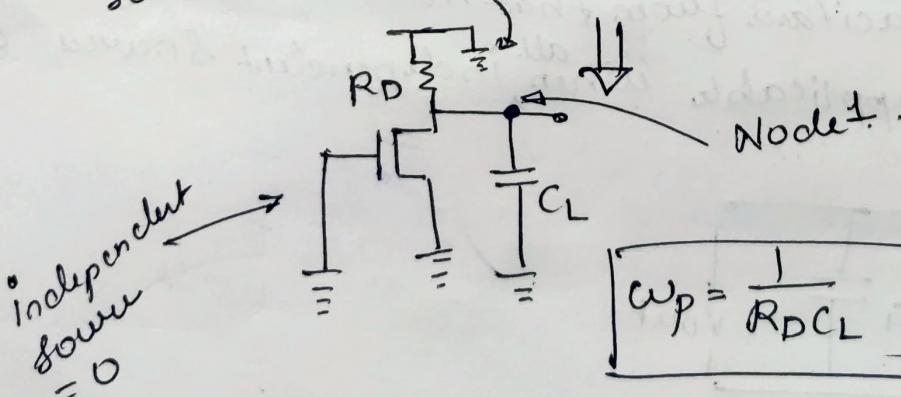


$$\omega_p = \frac{1}{R_D C_L}$$

$$T.O.F = \frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{1 + \frac{s}{\omega_p}} = \frac{-g_m R_D \omega_p}{s + \omega_p}$$

- Here we try to take out T.O.F (Transfer function by just inspection)


Example.

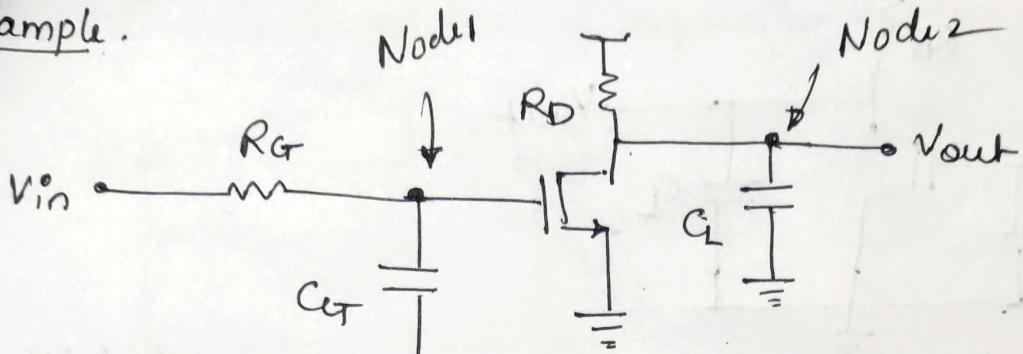

$$\omega_{p1} = \frac{1}{R_G C_{g1}} \quad \omega_{p2} = \frac{1}{R_D C_L}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

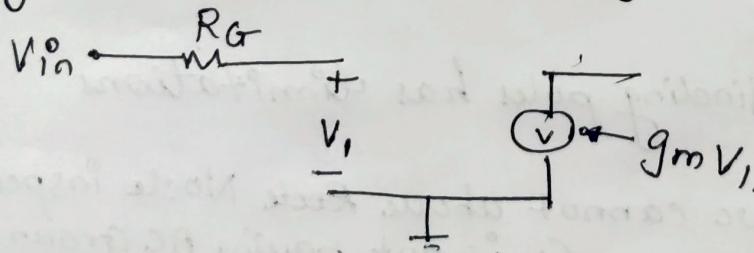- The above equation is derived by just inspection.
- Beside having R_G & R_D both the resistance in the circuit still the gain only have ' $g_m R_D$ ', R_G doesn't affect the circuit.
- If you will consider small signal model for the same.




$$V_1 = V_{in}$$

Because there is no current through R_G since it's an open circuit

∴ As low frequency R_G plays no role in Gain.

$$\therefore \frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{(1 + R_G C_g s)(1 + R_D C_L s)}$$


example.

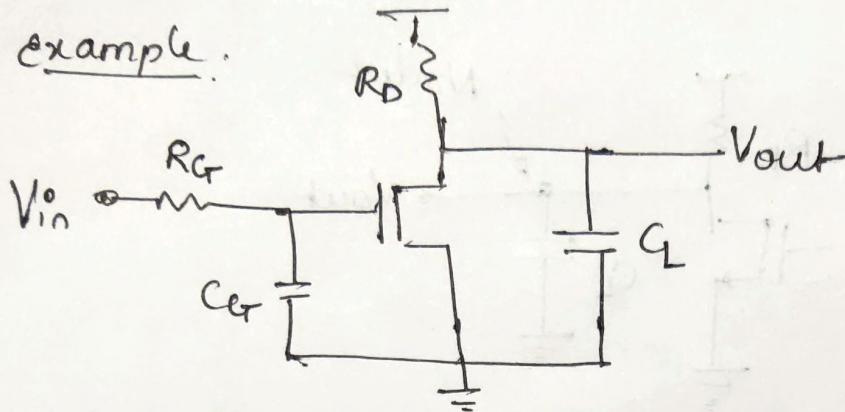


- These circuits are unwanted, we didn't add deliberately to the circuit.
- plot freq. Response.

$$\omega_{p1} = \frac{1}{R_G C_G} \quad \omega_{p2} = \frac{1}{R_D C_L}$$

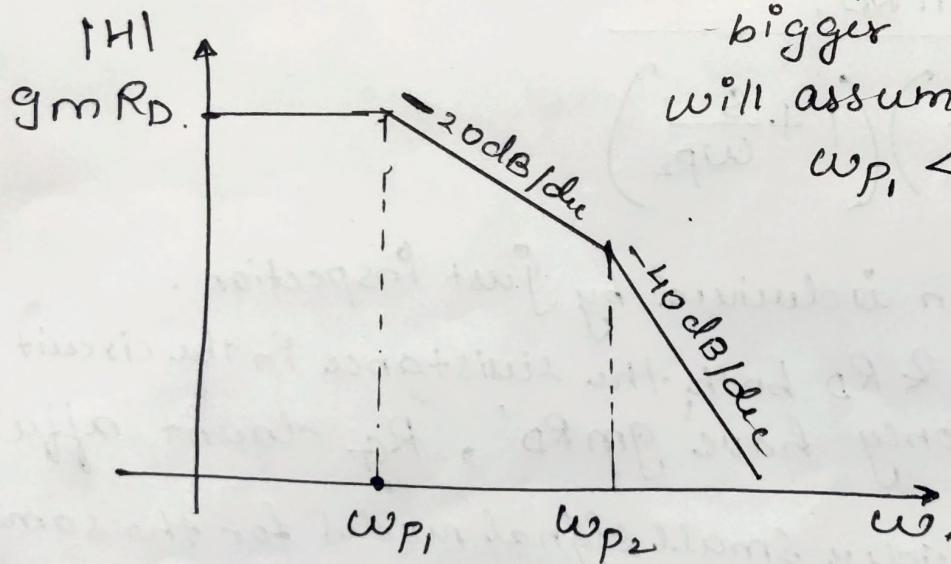we don't know which is bigger
will assume ~~$\omega_{p1} > \omega_{p2}$~~
 $\omega_{p1} < \omega_{p2}$.



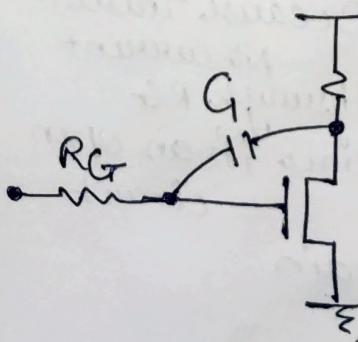
- This method of finding poles has limitations



- we cannot do Node inspection because C_1 is not having AC Ground.
- Since we have capacitor between two Nodes.

→ Millett's Theorem:

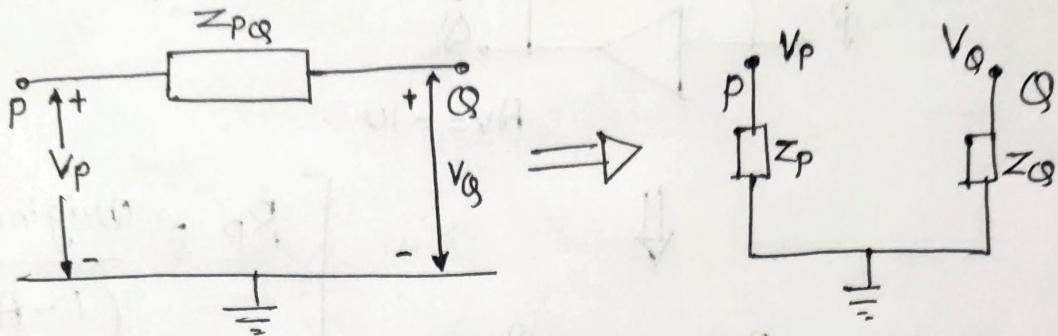- We can Decompose the floating capacitor to two grounded capacitor.



- current drawn from P from both the circuit which is equivalent, According to Millett's Theorem.

i.e $\frac{V_P - V_Q}{Z_{PQ}}$. ~~I_P~~

$$\frac{V_P - V_Q}{Z_{PQ}} = \frac{V_P}{Z_P}$$

$$\frac{Z_P}{Z_{PQ}} = \frac{V_P}{V_P - V_Q}$$

$$Z_P = \frac{Z_{PQ} V_P}{V_P - V_Q}$$

$$= \frac{Z_{PQ} V_P}{V_P \left(1 - \frac{V_Q}{V_P}\right)}$$



$$\therefore Z_P = \boxed{\frac{Z_{PQ}}{\left(1 - \frac{V_Q}{V_P}\right)}}$$

- current drawn from Q from both the circuit which is equivalent,

So similarly ,

$$\boxed{Z_Q = \frac{Z_{PQ}}{\left(1 - \frac{V_P}{V_Q}\right)}}$$

Example:

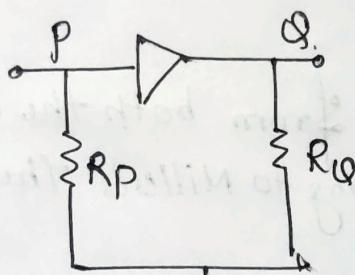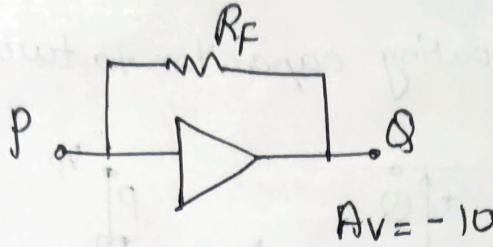

$$R_P = \frac{\text{Original Impedance}}{(1 - A_v)}$$

$$R_Q = \frac{\text{Original Impedance}}{(1 - \frac{1}{A_v})}$$

$$R_P = \frac{R_F}{1 - A_v} = \frac{R_F}{1 - (-10)} = \frac{R_F}{11}$$

$$\therefore \frac{V_Q}{V_P} = \frac{\text{O/p Voltage}}{\text{I/p Voltage}} = A_v$$

$$R_Q = \frac{R_F}{\left(1 - \frac{1}{A_v}\right)} = \frac{R_F}{\left(1 - \frac{1}{(-10)}\right)} = \frac{R_F}{\left(1 + \frac{1}{10}\right)} = \frac{R_F}{\frac{11}{10}} = \frac{R_F}{1.1}$$

4) The Miller Resistance

\Rightarrow Millett's Effect: $-z_{pq}$ is divided by $(1 - A_v)$ as it "appears" at the input.


- The I/p Resistance is less than the original floating Resistance..
- This can be used where we want less impedance.

Q. $A_v = +10$

$$R_P = \frac{R_F}{1 - 10} = -\frac{R_F}{9}$$

$$R_Q = \frac{R_F}{1 - \frac{1}{10}} = \frac{R_F}{\frac{9}{10}} = \frac{R_F}{0.9}$$

Example:

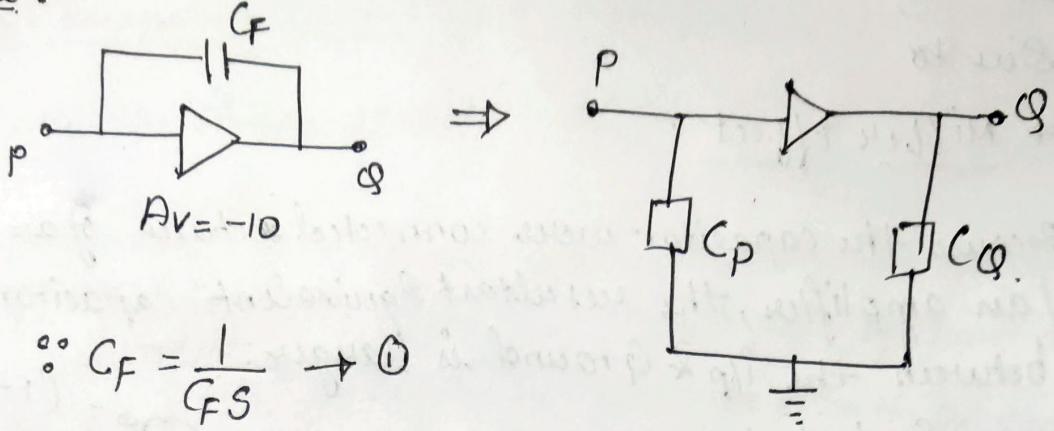

$$\text{Eq} = \frac{1}{C_{FS}(1-A_V)} \rightarrow ② \quad \text{Eq} = \frac{1}{C_{FS}\left(1-\frac{1}{A_V}\right)} \rightarrow ③$$

If we compare ① & ②.


$$\text{Equivalent capacitor} = C_F(1-A_V)$$

$$C_F = \frac{1}{C_{FS}(1-A_V)}$$

$$C_F(1-A_V) = \frac{1}{C_{FS}}$$

$$\therefore \text{Impedance at Node } P = C_F(1-A_V) \\ = C_F(1-(10)) \\ = 11C_F$$
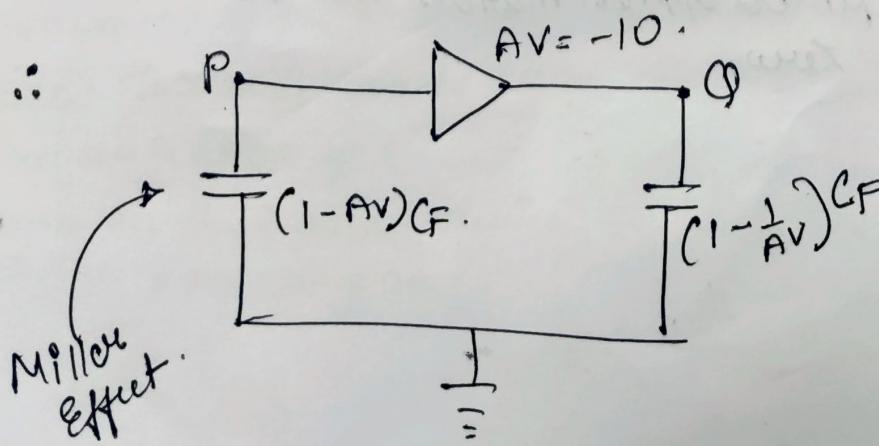
$$\text{Impedance at Node } Q = C_F\left(1-\frac{1}{A_V}\right) = 1.1C_F$$



- Due to


→ Miller Effect

- Because the capacitor were connected between the I/p of an amplifier, the resultant equivalent capacitor seen between the I/p & Ground is larger.

$$\text{Equivalent capacitor} = \text{Original capacitance} \times (1 + \frac{1}{AV})$$

- This is called as Miller Multiplication factor. [in this case]

Example: common-source Amplifier:

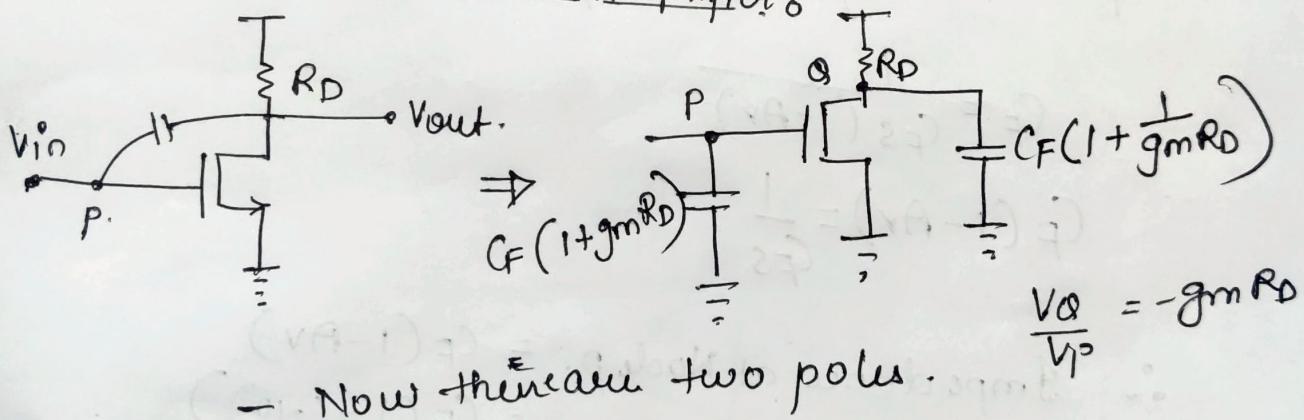


- Now there are two poles.

Caution: ① Miller's approximation has introduced a New pole.

② Miller's approximation has Eliminated the zero.


⇒ High-Frequency Model of Bipolar Transistor (BJT)

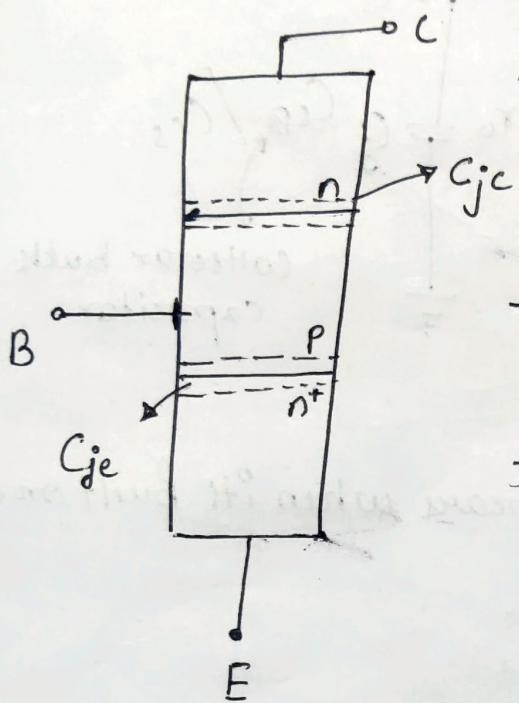- Let's take the simple structure of (npn) transistor.



- As we seen in Electronics I that there is a formation of junction capacitor associated with p-n junction
- C_{je} - associated with base-emitter junction
- C_{jc} - associated with ^{base} collector junction

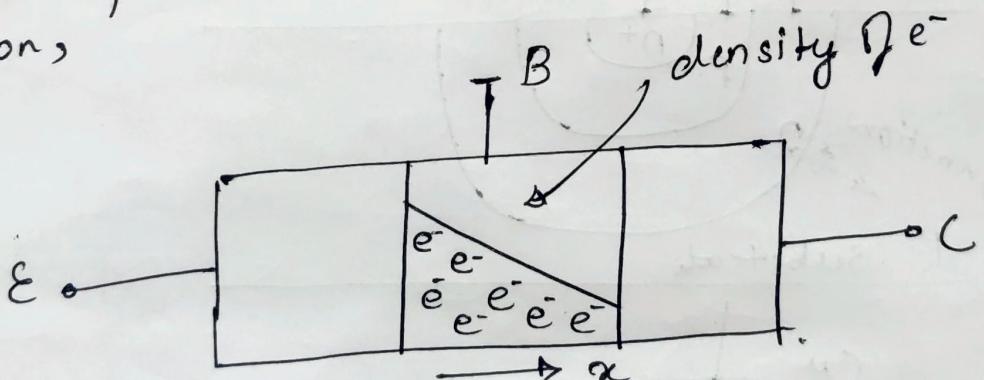
- When bipolar Tr is operating in the forward active Region,



- The e^- starts from the emitter pass through the base & enter the collector.
- The movement of the e^- inside the base area is by diffusion. To occur we need a gradient of concentration of e^- .
- To turn on the Bipolar device we have stored the some e^- to the base region.

- Low freq. which we already developed.


Model

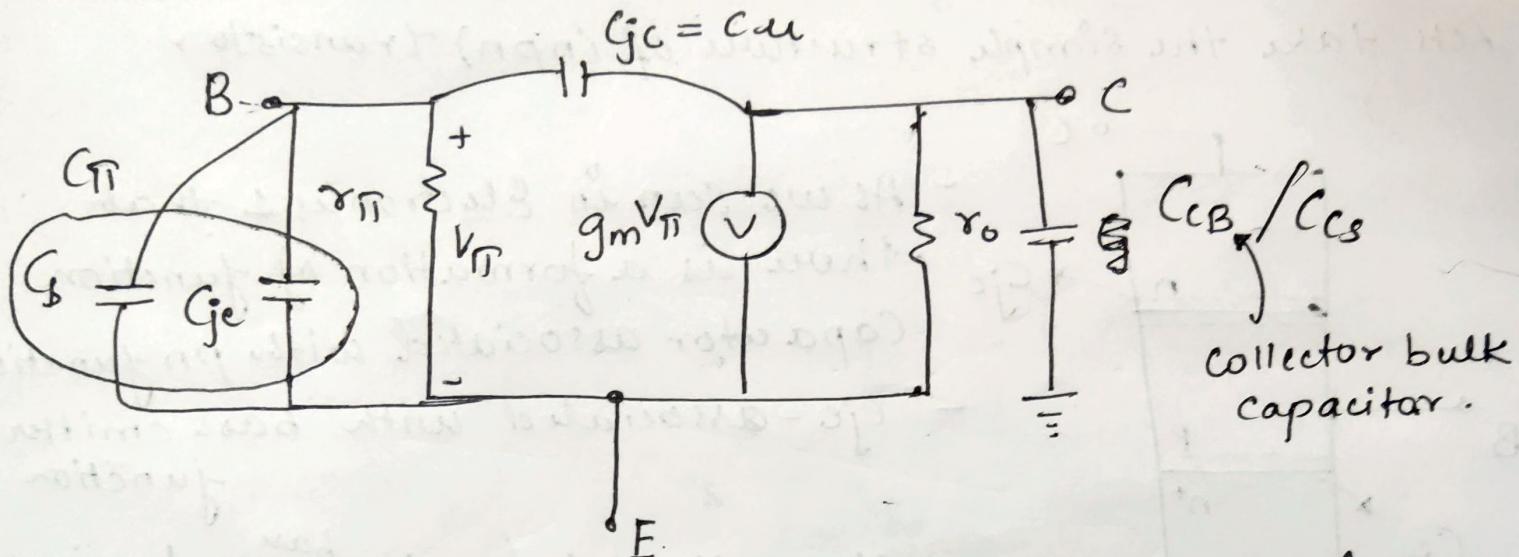


C_{CB}/C_{CS}

collector bulk
capacitor

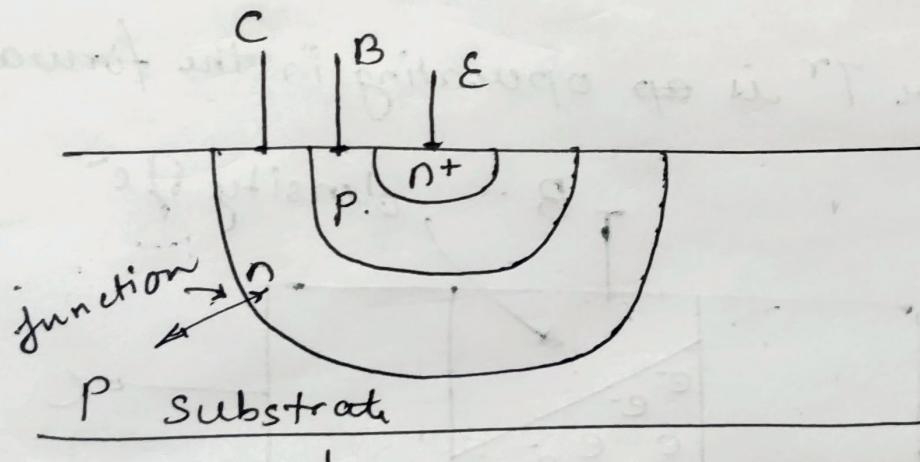
- This collector bulk capacitor appears when it's built on a wafer. Look at the below fig.




i.e.

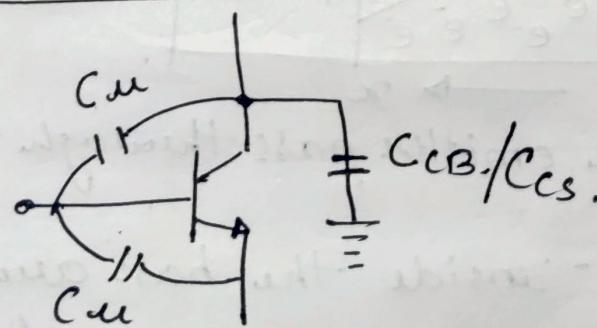

Example ① Bipolar Differential circuit

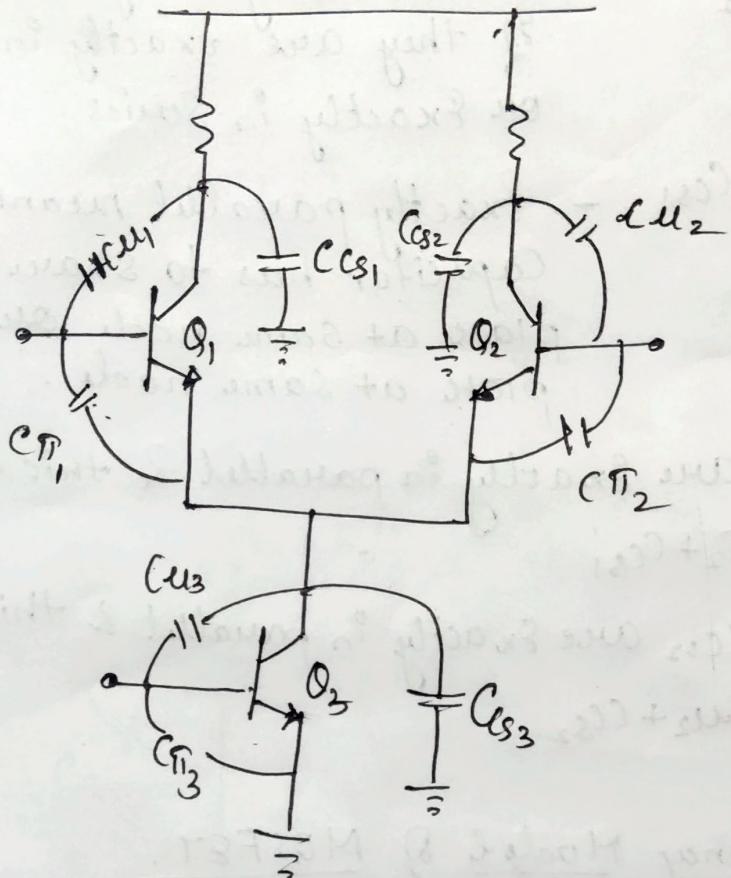


②

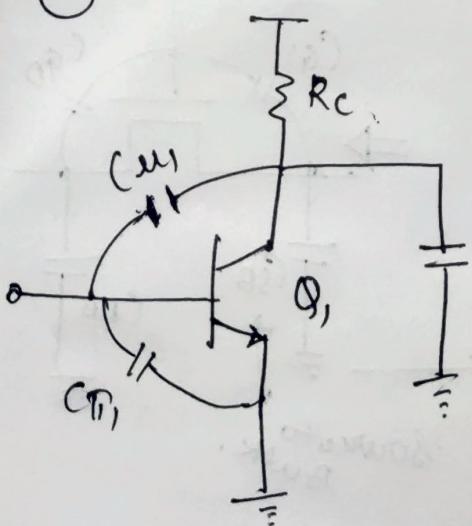

- Among this 3 capacitor which cap will Experience the Miller Effect or. Miller Multiplication -
- C_{pi1} will Experience the Miller Effect.

Example ③ Bipolar cascode amplifier:



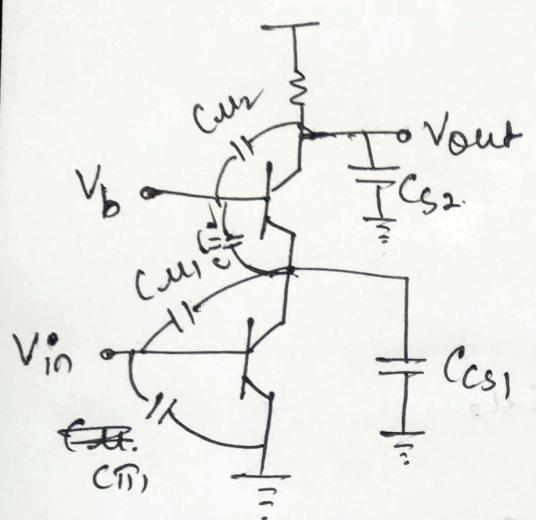



- can some of these capacitor can be merged?
- we can easily merge two capacitors if they are exactly in parallel or exactly in series.
- exactly parallel means two capacitor has to share the top plate at same node or bottom plate at same node.

∴ C_{π_2} & C_{CS_1} are exactly in parallel & this can be merged $\Rightarrow C_{\pi_2} + C_{CS_1}$

Also C_{M_2} & C_{CS_2} are exactly in parallel & this can be merged $\Rightarrow C_{M_2} + C_{CS_2}$


⇒ High frequency Model of MOSFET.

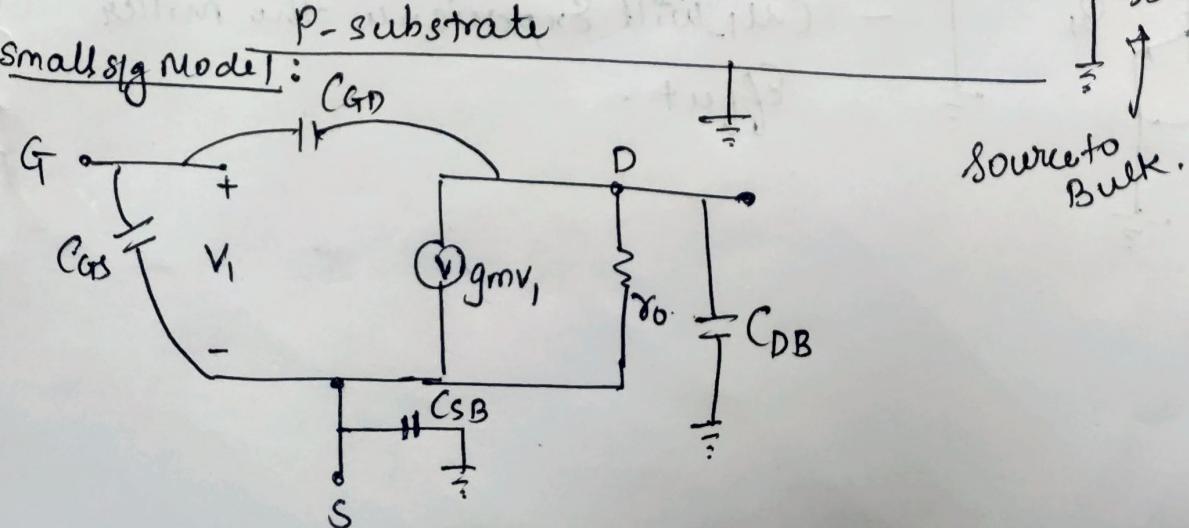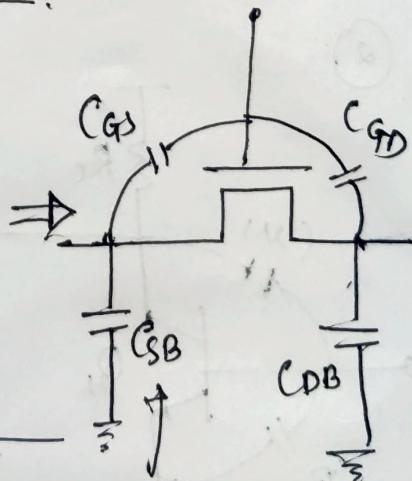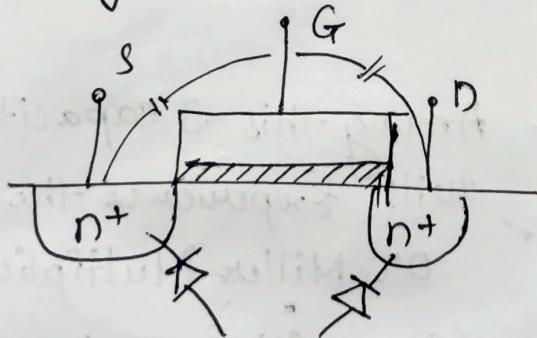

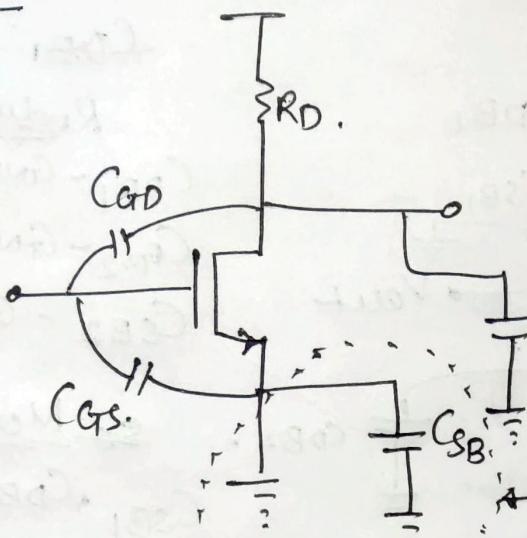Example ①.

C_{DB1} - only C_{GD1} experiences Miller Effect.


we can Reduce this capacitor by seeing that it is between the Ground.

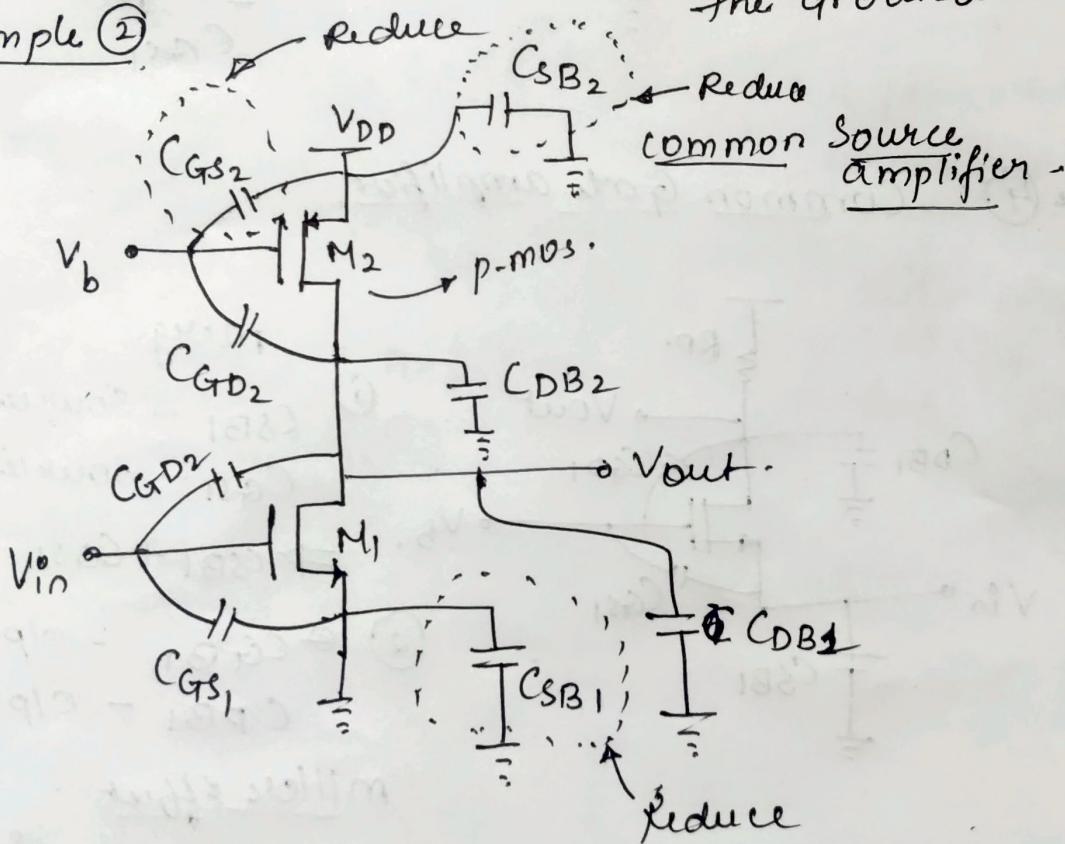Example ②.

- C_{DB1} , C_{GD1} , C_{DB2} , C_{GD2} - Output node to ground.
 \therefore This three can be merged.

$$\Rightarrow C_{DB1} + C_{GD2} + C_{DB2}$$

Example(3) Source Follower.

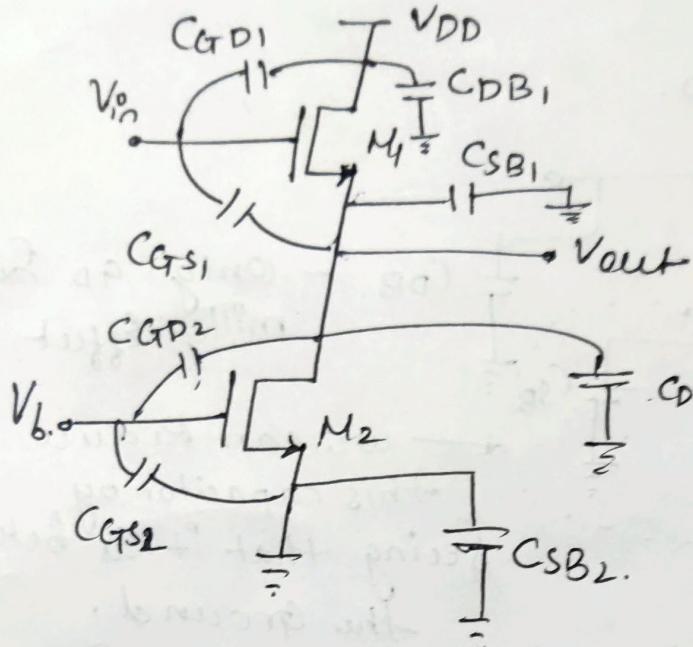

C_{DB1} Ground

Reduce.

C_{DB1} - GND to GND - X

C_{GS2} - GND to GND - X

C_{SB2} - GND to GND - X

~~Merge.~~


$C_{SB1}, C_{DB2}, C_{GD2}$

$\Rightarrow C_{SB1} + C_{DB2} + C_{GD2}$

Miller Effect

C_{GS1}

Example(4) Common Gate amplifier.

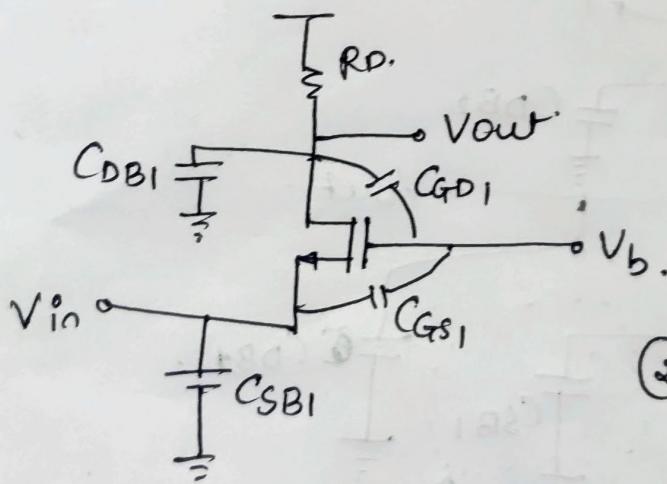

merge

C_{SB1} - Source to GND

C_{GS1} - Source to AC GND

$\Rightarrow C_{SB1} + C_{GS1}$

(2) ~~C_{GB1}~~ - O/p to AC GND.

C_{PB1} - O/p to AC GND.



Miller Effect.

No capacitor in the circuit you ~~for~~ i/p to from o/p.

\therefore common Gate amplifier

Don't have miller effect.

\Rightarrow Numericals.

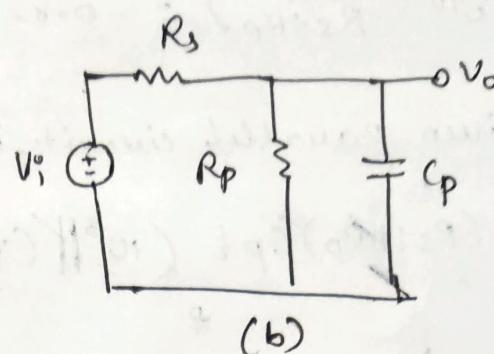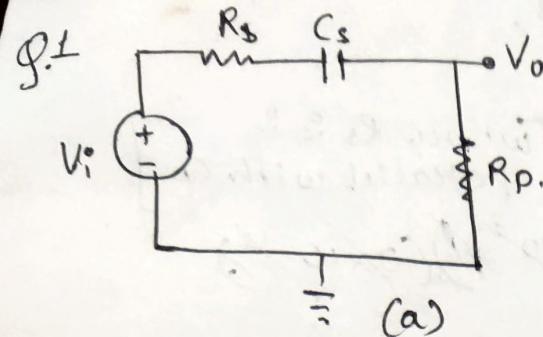

Find the corner frequencies & maximum magnitude asymptotes of the Bode plots for a given circuit.
where $R_s = 1\text{ k}\Omega$, $R_p = 10\text{ k}\Omega$, $C_s = 1\text{ }\mu\text{F}$, $C_p = 3\text{ pF}$.

Ans. \Rightarrow Time constant, $\tau = RC$

τ for given circuit (a),
series

$$\begin{aligned} \tau_s &= (R_s + R_p)C_s \quad [\text{where } R_s \text{ is in series with } R_p] \\ &= (10^3 + 10 \times 10^3)(10^{-6}) \\ &= 10^3(1+10)(10^{-6}) \\ &= 11 \times 10^{-3} \\ &= 1.1 \times 10^{-2} \text{ s or } 11 \text{ ms} \end{aligned}$$

For your understanding
corner frequencies means pole frequency

$$\begin{aligned} 1\text{ k}\Omega &= 10^3 \Omega \\ 1\text{ }\mu\text{F} &= 10^{-6} \text{ F} \\ 1\text{ pF} &= 10^{-12} \text{ F} \end{aligned}$$

$$\omega_p, \text{ pole frequency} = \frac{1}{RC} = \frac{1}{\tau}$$

$$\begin{aligned} \therefore f &= \frac{1}{2\pi RC} = \frac{1}{2\pi\tau} \\ &= \frac{1}{2\pi(11 \times 10^{-3})} = 14.5 \text{ Hz.} \end{aligned}$$

$$\text{magnitude } |H(s)| = \frac{R_p}{R_s + R_p} = \frac{10}{1+10} = 0.909.$$

$$\text{Or } 20 \log_{10} \left(\frac{R_p}{R_s + R_p} \right) = -0.828 \text{ dB.}$$

Z for given parallel circuit, b. [where R_s is in parallel with C_p]

$$Z_p = (R_s || R_p) C_p \approx \frac{10^3 \parallel (10 \times 10^{-3})}{(3 \times 10^{-12})}$$

$$= \frac{1}{\frac{1}{R_s} + \frac{1}{R_p}} \cdot C_p$$

$$= \frac{\frac{1}{R_p + R_s}}{\frac{R_p R_s}{R_p R_s}} \cdot C_p$$

$$= \frac{R_p R_s}{R_p + R_s} \cdot C_p = \frac{10^3 \times 10 \times 10^3 \cdot C_p}{10^3 + 10 \times 10^3} = \frac{10^3 \times 10 \times 10^3}{10^3 (1 + 10)} \cdot C_p$$

$$= \frac{10^3 \times 10^3 \cdot C_p}{10 (1 + 0.1)} = \frac{10^3}{1.1} \cdot C_p$$

$$= \frac{10^3}{1.1} \times 3 \times 10^{-12}$$

$$= \frac{3}{1.1} \times 10^{-9} = 2.73 \times 10^{-9} \text{ S}$$


$$= 58.3 \text{ MHz.}$$

$$f = \frac{1}{2\pi Z_p} = \frac{1}{2\pi \times (2.73 \times 10^{-9})}$$


maximum magnitude is the same as calculated,

$$0.909 \text{ or } -0.828 \text{ dB.}$$

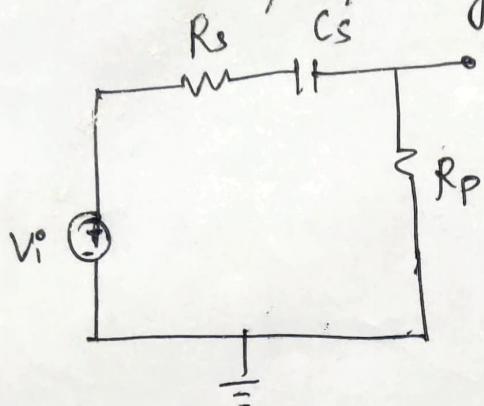Q.2 For the given circuit below where $R_s = R_p = 4k\Omega$
~~If~~ the corner frequency is $f = 20\text{Hz}$, determine the
 value of C_s .



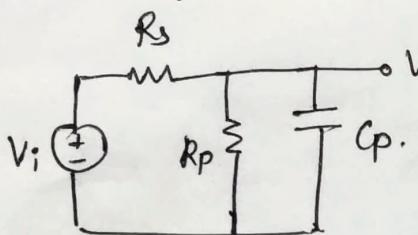Q3. For the given circuit below, with the parameters
 $R_s = R_p = 10k\Omega$. If the corner frequency is $f = 500\text{kHz}$,
 determine the value of C_p .



Q4. Determine the corner frequencies & Bandwidth
 of a passive circuit containing two capacitors,
 consider the below circuit where $R_s = 10k\Omega$, $R_p = 20k\Omega$,
 $C_s = 1\mu\text{F}$, $C_p = 4\text{pF}$.